

---

# INDEX

---

- acceptors, 376
- adders, *see* full-adders; half-adders
- alternating current (AC) circuits, 98
- amplifier, 287, 292–294
  - bipolar, 397–420
    - linear, 155–165, 290–294
    - linear applications of op amps, 294, 299, 306, 314, 316, 321, 322, 326
    - non-linear applications of op amps, 331, 332, 335, 336
    - small signal model, 397
- apparent, *see under* power
- arithmetic, 533
- arithmetic and logic unit (ALU), 611
- atoms, 1, 2
  
- battery, 5, 6, 30–33
- BiCMOS, 500
- binary numbers, 456, 527, 531
- Biot-Savart law, 49
- bipolar junction transistor (BJT), 374
  - biasing, 378–382
  - biasing PNP transistors, 396
  - biasing resistor divider, 387
  - as a circuit element, 377
  - common base configuration, 407
  - common collector configuration, 415
  - common emitter configuration, 399
  - electronic devices, 354
  - emitter degeneration resistor biasing, 391
  - follower configuration, *see* common collector configuration
  - self-biased, 394
  - small signal model, 397
- BJT, *see* bipolar junction transistor
- Bode plots, 238, 241, 244, 254, 257, 275, 278
- Boolean algebra, 460
- Boolean algebra postulates and theorems, 465
  
- canonical forms, *see* standard canonical forms
- capacitive reactance, 131–133, 152, 153
- capacitor, 111, 114, 123, 124, 126, 127, 131–133, 136–139, 142, 152
  - decoupling, 42–44, 304–306, 603, 628, 631–633
  - dielectric constant, 35, 36
  - electric component, 12
  - parallel-plate, 33, 35, 36, 94
  - power drawn by, 137, 139
  - pure, 131
  - time domain equations, 115
  - under sinusoidal steady-state, 114
  - voltage and current phasors, 134
- carry look ahead, 543
- central processing unit (CPU)
  - design, 603
  - instruction set, 603
- characteristic tables, *see* flip-flops

- charge, 1–3, 5, 6
- circuit, 156
  - analysis, 155
  - first order, 233, 236, 241, 246, 279
  - linear, *see* amplifiers
  - second order, 233, 265, 266, 275, 278, 279
  - theorems, 155
- clock, 550, 551, 559–567, 571–575, 584, 587, 590, 591–593, 595–599
  - cpu, 603, 604, 608, 609, 614, 617, 618, 626–628
- CMOS, 443, 497, 498–500
- coil, *see* inductor
- complex number, 115–122, 126, 128, 130, 131, 133–135
- controller, 618–620
- counter, program, 604, 611, 614, 615
- current
  - electric, 3–11
  - electronic, 6
  - source, 3, 5, 7–11
- current controlled current source (CCCS), 145–149, 154
- current controlled voltage source (CCVS), 145, 146, 147
- D flip-flop, 568, 581
- data path architecture, 615
- De Morgan laws, rules and theorems, 464
- decoder, 510–515
- decoupling, 628, 631
- de-multiplexers, 526
- dependent sources
  - current controlled current source (CCCS), 148, 149
  - current controlled voltage source (CCVS), 145–147
  - finding the Norton equivalent circuit, 175
  - establishing mesh equations when there are, 196
  - establishing nodal equations when there are, 207
  - Norton's theorem highlights, 211
  - Thevenin, 167
  - Thevenin theorem highlights, 211
  - voltage controlled current source (VCCS), 145, 146, 147
  - voltage controlled voltage source (VCVS), 145
- depletion mode, *see* metal oxide semiconductor field effect transistor
- dielectric constant, 35, 36
- difference amplifier, *see* operational amplifiers
- differentiator, *see* filters
- digital circuits, 456
- diode, 354–357, 363, 367, 369, 371, 372
- direct current (DC) circuits, 5, 87
- donors, 376
- don't care, 491
- dot rule, 68
- duality principle, 466
- effective value, 99, 105, 149; *see also* root mean square (RMS)
- electric charge, 1, 3, 34
- electric current, 3, 6, 12, 37, 45, 53, 88, 422
- electric voltage, 3, 27
- electromotive force (EMF), 51, 53, 54, 59
- electron, 1–3, 5, 6
- electronic devices, 354
- EMF, *see* electromotive force
- encoder, 510, 517
- enhancement mode, *see* metal oxide semiconductor field effect transistor
- Euler's form, 119–123
- excitation tables, *see* flip-flops
- Faraday's Induction Law, *see* induction
- fast carry generation, 543
- filters
  - differentiator, 263, 265, 279
  - first order, 233, 235
  - high-pass (HPF), 252–265, 279, 294
  - integrator, 251, 252, 279
  - low-pass (LPF), 235, 236, 238, 240–245, 246, 248–252, 254, 257, 260, 279, 280, 285
  - second order, 266, 275
- flip-flops
  - characteristic tables, 568–570, 576
  - D-type, 568, 581

- excitation tables, 576–578, 580–583, 586, 588
- JK, 565
- master/slave SR, 561
- timing, 572
- toggle or T-type, 568
- frequency domain, 111, 123, 235, 253
- frequency response plots, *see* Bode plots
- full adders, 533, 536
- full-wave rectifier, 360
  
- gates, 495
  - logic, electrical and timing characteristics, 495, 497
  - MOSFET, 424, 427, 429, 432
  
- half-adders, 533
- half-wave rectifier, 357
- hysteresis, 70, 336, 338–341, 630, 631
  
- impedance, 123, 124, 126, 127, 128, 129, 130–136, 140, 144, 151–153
- induction, 49–51, 53
  - electromagnetic, 53, 54, 62
  - Faraday law of, 53, 62, 64, 66
- inductive reactance, 130, 151, 152
- inductor
  - electric component, 12
  - mutual inductance, 62–70
  - non-linearity, 70–73
  - parallel, 60–62
  - power drawn by, 136, 139, 140
  - pure, 127, 128, 129, 130, 133
  - series, 58, 59
  - time domain equations, 115
  - under sinusoidal steady-state, 113
  - voltage and current phasors, 134
- integrator, *see* filters
  
- JK flip-flop, 565
  
- Karnaugh maps, 473, 474, 479, 484, 487
  - design examples, 473, 474, 479, 484, 487
- Kirchoff's current law (KCL), 73, 81, 173, 199
- Kirchoff's voltage law (KVL), 73, 79, 173
  
- latch, 552–559
  - characteristic table, 558, 560
- latch SR, 559
- linear amplifiers, *see* amplifiers
- linear function, 156–160
- load line, 108, 109
- logic gates, 495, 497, 499
- logic operation, *see* Boolean algebra
- loop, 77, 78
- Lorentz law, 49
- LVTTL, 499
  
- magnetic characteristic, 71
- magnetic field, 45–51, 53, 54, 58, 59–61, 70
- magnitude Bode plot, *see* Bode plot
- master/slave, 561, 565, 568
- maxterms, 472
- memory, 610
- mesh method, 179–181, 189, 196, 199, 210, 212, 213, 223, 225
  - with dependent sources, 196
- metal oxide semiconductor field effect transistor (MOSFET)
  - biasing techniques, 428
  - common drain or source follower, 439
  - common gate configuration, 437
  - common source configuration, 434
  - common source configuration with emitter degeneration, 436
  - electronic device, 354, 420
  - enhancement mode p-channel, and depletion mode n-channel and p-channel, 439
  - I-V characteristics, 424
  - small signal model, 427
- minterms, 467
- MOSFET, *see* metal oxide semiconductor field effect transistor
- multiplexers, 519, 521
- mutual inductance, *see* inductor
  
- nodal method, 199–207, 210
- non-linear applications, *see* amplifiers
- Norton's method, 172–175, 210
  
- Ohm's law, 25, 26, 29, 101
- one's complement, *see* binary numbers

- op amp, *see* operational amplifier
- operational amplifier, 287, 288, 294, 331, 341, 342
  - buffer, 309
  - data sheet, 344
  - decoupling, *see* capacitor
  - difference, 316
  - inverting, 294
  - inverting differentiator, 322
  - inverting integrator, 321
  - non-idealities, 341
  - non-inverting, 316
  - power dissipation, 344, 373, 374
  - selection, 341
  - unity gain, 309
- permeability, 45, 52, 53, 71, 95
- phase Bode plot, *see* Bode plots
- phasor, 115, 123–135, 138–140, 149, 153
- photodiode, 369
- polar form, 117–121, 123, 129, 132, 134, 135
- power, 98
  - AC instantaneous, 137, 138
  - active, 136, 137, 140, 141, 142, 143
  - apparent, 136, 137, 140, 141, 142, 143, 144, 149
  - average, 103, 106, 136, 137, 138, 140, 141
  - decoupling, *see* capacitor
  - instantaneous, 103, 104, 112, 113, 114, 136, 137, 138, 139, 140
  - reactive, 136, 137, 139, 140
  - triangle, 137, 140, 141, 142
- primary, *see* transformer
- program counter, 611
- RC circuit, *see* filters, high-pass and low-pass
- rectangular form, 115–122, 129, 130, 132, 135
- register, 547, 551, 569, 575, 605, 607
- reset, 322, 457, 552, 553–555, 558, 559, 561, 567–576, 578, 580, 581, 594, 603–605, 628–630
  - asynchronous, 571, 572, 582, 583, 584, 613, 614, 621, 622
  - synchronous, 572–574, 613, 631
- resistance, *see* resistor
- resistor, 98, 101, 102, 103, 104, 105, 106, 107, 111, 115, 123, 124, 126, 128, 134, 136, 137, 144, 146, 152, 153, 154
  - electric component, 12
  - internal, 9–11
  - parallel, 19
  - polarities, 13
  - powered by a DC source, 4
  - powered by an AC voltage, 105
  - power dissipation, 18, 105, 106
  - series, 19, 42, 355
  - temperature coefficient, 14–17
  - tolerances, 15
  - under sinusoidal steady-state, 112
- RLC circuit, 266, 271–275, 277, 286
- root mean square (RMS), 98, 99, 101, 103, 105, 106, 137, 138, 140, 143, 144, 149
- Schottky diode, 371, 629
- secondary, *see* transformer
- shift register, 575, 590–592
- simplification, *see* Karnaugh maps
- sinusoidal, 98, 99, 101, 102, 103, 106, 111, 113, 114, 124, 126
  - current, 106, 111, 127, 131, 137, 152
  - excitation, 112, 113, 114, 115
  - steady-state, 111, 112, 113, 115, 123, 130, 133, 134, 141
  - voltage, 99, 101, 103, 105, 111, 113, 123, 126, 127, 128, 131, 151, 152, 153
- waveform, 98, 99, 101, 105, 111, 124, 125
- source
  - AC voltage, 108, 111
  - current, 3
  - DC voltage, 108
  - dependant voltage, 145, 147
  - dependant current, 145, 146
  - follower, BJT, *see* common collector configuration
  - follower, MOSFET, *see* common drain configuration
  - ideal voltage, 98, 102, 103
  - real voltage, 100, 109
  - sinusoidal voltage, 103, 111

- transformation method, 174, 175, 177, 178, 210, 212, 213, 221, 222, 225, 229
- voltage, 3, 5, 7, 30, 73, 79, 82, 85, 88, 94, 98, 99, 100, 101, 103, 108
- source transformations, 174, 175, 177, 178, 210, 212, 213
- SR flip-flop, 561
- SR latch, 559
- standard canonical forms
  - product of sums (POS), 472
  - sum of products (SOP), 467
- state machines, 574
- subtracting, 540, 542
- superposition method, 156, 169, 171, 210, 213, 226
- synchronous state machines, 592
- T flip-flop, 568, 580
- Thevenin method, 165, 168, 172, 210
- time domain, 123, 244, 245, 257, 258
- timing, 571, 595, 626
- transformer, 67, 68, 70
- transistor
  - BJT, 354, 374, 420
  - MOSFET, 354
  - small signal model, 398, 399, 427
- TTL, 497, 498, 499
- two's complement, *see* binary numbers
- Venn diagrams, 467
- voltage, 1, 3, 29
  - electric, 3–11
  - polarities, 13
  - source, 25, 27
- voltage controlled current source (VCCS), 147, 148, 153
- voltage controlled voltage source (VCVS), 145