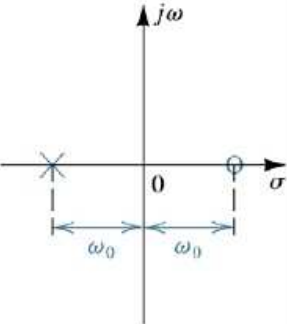
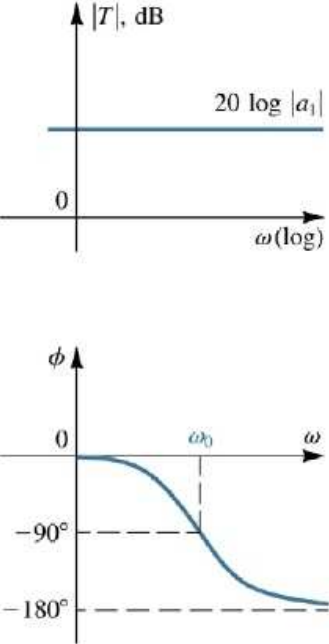
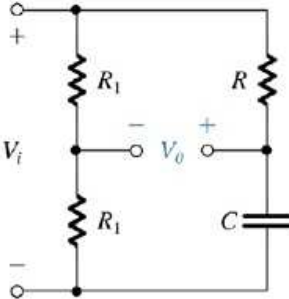
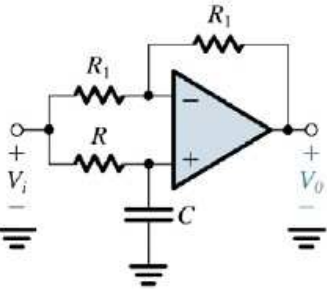


Filter Type and $T(s)$	s-Plane Singularities	Bode Plot for $ T $	Passive Realization	Op Amp-RC Realization
(a) Low-Pass (LP) $T(s) = \frac{a_0}{s + \omega_0}$			$CR = \frac{1}{\omega_0}$ dc gain = 1	$CR_2 = \frac{1}{\omega_0}$ dc gain = $-\frac{R_2}{R_1}$
(b) High-Pass (HP) $T(s) = \frac{a_1 s}{s + \omega_0}$			$CR = \frac{1}{\omega_0}$ High-frequency gain = 1	$CR_1 = \frac{1}{\omega_0}$ High-frequency gain = $-\frac{R_2}{R_1}$
(c) General $T(s) = \frac{a_1 s + a_0}{s + \omega_0}$			$(C_1 + C_2)(R_1 // R_2) = \frac{1}{\omega_0}$ $C_1 R_1 = \frac{a_0}{a_1}$ dc gain = $\frac{R_2}{R_1 + R_2}$ HF gain = $\frac{C_1}{C_1 + C_2}$	$C_2 R_2 = \frac{1}{\omega_0}$ $C_1 R_1 = \frac{a_0}{a_1}$ dc gain = $-\frac{R_2}{R_1}$ HF gain = $-\frac{C_1}{C_2}$

Sedra/Smith "Microelectronic Circuits" 4th. Ed.

$T(s)$	Singularities	$ T $ and ϕ	Passive Realization	Op Amp-RC Realization
$T(s) = -a_1 \frac{s - \omega_0}{s + \omega_0}$ $a_1 > 0$			 <p style="text-align: center;"> $CR = 1/\omega_0$ Flat gain (a_1) = 0.5 </p>	 <p style="text-align: center;"> $CR = 1/\omega_0$ Flat gain (a_1) = 1 </p>

Filter Type and $T(s)$	s -Plane Singularities	$ T $
<p>(a) Low-Pass (LP)</p> $T(s) = \frac{a_0}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$ <p>dc gain = $\frac{a_0}{\omega_0^2}$</p>		
<p>(b) High-Pass (HP)</p> $T(s) = \frac{a_2 s^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$ <p>High-frequency gain = a_2</p>		
<p>(c) Bandpass (BP)</p> $T(s) = \frac{a_1 s}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$ <p>Center-frequency gain = $\frac{a_1 Q}{\omega_0}$</p>		

<p>(d) Notch</p> $T(s) = a_2 \frac{s^2 + \omega_0^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$ <p>dc gain = high-frequency gain = a_2</p>		
<p>(e) Low-Pass Notch (LPN)</p> $T(s) = a_2 \frac{s^2 + \omega_n^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$ <p>$\omega_n \geq \omega_0$ dc gain = $a_2 \frac{\omega_n^2}{\omega_0^2}$ high-frequency gain = a_2</p>		$\omega_{\max} = \omega_0 \sqrt{\frac{\left(\frac{\omega_n^2}{\omega_0^2}\right)\left(1 - \frac{1}{2Q^2}\right) - 1}{\frac{\omega_n^2}{\omega_0^2} + \frac{1}{2Q^2} - 1}}$
<p>(f) High-Pass Notch (HPN)</p> $T(s) = a_2 \frac{s^2 + \omega_n^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$ <p>$\omega_n \leq \omega_0$ dc gain = $a_2 \frac{\omega_n^2}{\omega_0^2}$ high-frequency gain = a_2</p>		$T_{\max} = \frac{ a_2 \frac{ \omega_n^2 - \omega_{\max}^2 }{\sqrt{(\omega_0^2 - \omega_{\max}^2)^2 + \left(\frac{\omega_0}{Q}\right)^2 \omega_{\max}^2}}}$

(g) All-Pass
(AP)

$$T(s) = a_2 \frac{s^2 - s \frac{\omega_0}{Q} + \omega_0^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

Flat gain = a_2

