

|            |      |
|------------|------|
| Chapter 2  | 1    |
| Chapter 3  | 43   |
| Chapter 4  | 105  |
| Chapter 5  | 165  |
| Chapter 6  | 300  |
| Chapter 7  | 358  |
| Chapter 8  | 451  |
| Chapter 9  | 524  |
| Chapter 10 | 614  |
| Chapter 11 | 722  |
| Chapter 12 | 791  |
| Chapter 13 | 890  |
| Chapter 14 | 955  |
| Chapter 15 | 1052 |

1. (a)

$$n_i(T=300\text{K}) = 1.66 \cdot 10^{15} (300)^{3/2} \cdot \exp\left[\frac{-0.66\text{eV}}{2(1.38 \cdot 10^{-23}\text{J/K})(300\text{K})}\right]$$

$$= 2.5 \cdot 10^{13} \text{ cm}^{-3}$$

$$n_i(T=600\text{K}) = 1.66 \cdot 10^{15} (600)^{3/2} \cdot \exp\left[\frac{-0.66\text{eV}}{2(1.38 \cdot 10^{-23}\text{J/K})(600\text{K})}\right]$$

$$= 4.15 \cdot 10^{16} \text{ cm}^{-3}$$

Comparing these results with those in Example:

$$\frac{n_i(\text{Ge @ } 300\text{K})}{n_i(\text{Si @ } 300\text{K})} \approx 2315.$$

$$\frac{n_i(\text{Ge @ } 600\text{K})}{n_i(\text{Si @ } 600\text{K})} \approx 27.$$

At higher temperature, the exponential terms approaches one, which implies that  $n_i \sim T^{3/2}$ , independent of bandgap energy,  $E_g$ .

(b) For any doped material,  $n \cdot p = n_i^2$ . Assuming at  $T=300\text{K}$ ,

$$p = 5 \cdot 10^{16} \text{ cm}^{-3}$$

$$n = [n_i(T=300\text{K})]^2 / p = \frac{(2.5 \cdot 10^{13} \text{ cm}^{-3})^2}{5 \cdot 10^{16} \text{ cm}^{-3}} = 1.25 \cdot 10^{10} \text{ cm}^{-3}$$

2. (a) Mobility of electrons in Si =  $1350 \text{ cm}^2/\text{V}\cdot\text{s}$   
Mobility of holes in Si =  $480 \text{ cm}^2/\text{V}\cdot\text{s}$

$$\Rightarrow \text{velocity of electrons} = \mu_n E = \left(1350 \frac{\text{cm}^2}{\text{V}\cdot\text{s}}\right) \left(\frac{0.1 \text{ V}}{\mu\text{m}}\right)$$
$$= 1.35 \cdot 10^4 \text{ m/s}$$

$$\text{velocity of holes} = \mu_p E = \left(480 \frac{\text{cm}^2}{\text{V}\cdot\text{s}}\right) \left(\frac{0.1 \text{ V}}{\mu\text{m}}\right)$$
$$= 4.8 \cdot 10^3 \text{ m/s}$$

(b) Given  $E = 0.1 \text{ V}/\mu\text{m}$  hole current negligible  
 $\mu_n = 1350 \text{ cm}^2/\text{V}\cdot\text{s}$   $\mu_p = 480 \text{ cm}^2/\text{V}\cdot\text{s}$

$$J_{\text{tot}} = 1 \text{ mA}/\mu\text{m}^2 = q [\mu_n n E + \mu_p p E] \approx q \mu_n n E$$

$$\therefore n = \frac{J_{\text{tot}}}{q \mu_n E} = \frac{1 \text{ mA}/\mu\text{m}^2}{(1.6 \cdot 10^{-19} \text{ C})(1350 \text{ cm}^2/\text{V}\cdot\text{s})(0.1 \text{ V}/\mu\text{m})}$$
$$= 4.6 \cdot 10^{17} \text{ cm}^{-3}$$

3. Given  $L = 0.1 \mu\text{m}$      $A = (0.05 \mu\text{m})^2$      $V = 1 \text{V}$   
 $\mu_n = 1350 \text{ cm}^2/\text{V-s}$      $\mu_p = 480 \text{ cm}^2/\text{V-s}$   
 $n = 10^{17} \text{ cm}^{-3}$  (assuming n-type dopant)

$$(a) n_i(T=300\text{K}) = 5.2 \cdot 10^{15} (300)^{3/2} \exp\left[\frac{-1.12 \text{ eV}}{2(1.38 \cdot 10^{-23} \text{ J/K})(300\text{K})}\right]$$

$$= 1.08 \cdot 10^{10} \text{ cm}^{-3}$$

$$p = n_i^2/n = 1.17 \cdot 10^3 \text{ cm}^{-3} \quad E = V/L = 10 \text{ V}/\mu\text{m}$$

$$\therefore I_{\text{tot}} = A \cdot J_{\text{tot}} = A \cdot q [\mu_n n + \mu_p p] E$$

$$= A \cdot q [\mu_n n + \mu_p (n_i^2/n)] E$$

$$= (0.05 \mu\text{m})^2 (1.6 \cdot 10^{-19} \text{ C}) \left[ \frac{1350 \text{ cm}^2}{\text{V-s}} (10^{17} \text{ cm}^{-3}) + \frac{480 \text{ cm}^2}{\text{V-s}} (1.17 \cdot 10^3 \text{ cm}^{-3}) \right]$$

$$\cdot (10 \text{ V}/\mu\text{m})$$

$$\Rightarrow I_{\text{tot}} \approx 0.054 \text{ mA}$$

$$\begin{aligned}
 \text{(b) @ 400K : } n_i &= 3.7 \cdot 10^{12} \text{ cm}^{-3} \\
 p &= n_i^2/n = 1.4 \cdot 10^8 \text{ cm}^{-3} \\
 E &= 10 \text{ V}/\mu\text{m}
 \end{aligned}$$

$$\therefore I_{\text{tot}} = A \cdot q [ \mu_n n + \mu_p (n_i^2/n) ] E$$

$$\begin{aligned}
 &= (0.05 \mu\text{m})^2 (1.6 \cdot 10^{-19} \text{C}) \left[ 1350 \frac{\text{cm}^2}{\text{V}\cdot\text{s}} (10^{17} \text{cm}^{-3}) + 480 \frac{\text{cm}^2}{\text{V}\cdot\text{s}} (1.4 \cdot 10^8 \text{cm}^{-3}) \right] \\
 &\quad \cdot (10 \text{ V}/\mu\text{m})
 \end{aligned}$$

$$\Rightarrow I_{\text{tot}} \approx 0.054 \text{ mA}$$

4. Given  $L = 0.1 \mu\text{m}$      $A = (0.05 \mu\text{m})^2$      $V = 1 \text{V}$   
 $\mu_n = 3900 \text{ cm}^2/\text{V-s}$      $\mu_p = 1900 \text{ cm}^2/\text{V-s}$   
 $n = 10^{17} \text{ cm}^{-3}$  (assuming n-type dopant)

(a) From previous problem,

@ 300 K:  $n_i = 2.5 \cdot 10^{13} \text{ cm}^{-3}$      $p = n_i^2/n = 6.3 \cdot 10^9 \text{ cm}^{-3}$   
 $E = 10 \text{ V}/\mu\text{m}$

$$I_{\text{tot}} = A \cdot J_{\text{tot}} = A q [\mu_n n + \mu_p (n_i^2/n)] E$$

$$= (0.05 \mu\text{m})^2 (1.6 \cdot 10^{-19} \text{ C}) \left[ 3900 \frac{\text{cm}^2}{\text{V-s}} (10^{17} \text{ cm}^{-3}) + 1900 \frac{\text{cm}^2}{\text{V-s}} (6.3 \cdot 10^9 \text{ cm}^{-3}) \right]$$

$$\cdot (10 \text{ V}/\mu\text{m})$$

$\Rightarrow I_{\text{tot}} \approx 62.4 \text{ mA}$


(b) @ 400 K:  $n_i = 2.9 \cdot 10^{15} \text{ cm}^{-3}$      $p = 8.5 \cdot 10^{13} \text{ cm}^{-3}$   
 $E = 10 \text{ V}/\mu\text{m}$

$$I_{\text{tot}} = A q [\mu_n n + \mu_p (n_i^2/n)] E$$

$$= (0.05 \mu\text{m})^2 (1.6 \cdot 10^{-19} \text{ C}) \left[ 3900 \frac{\text{cm}^2}{\text{V-s}} (10^{17} \text{ cm}^{-3}) + 1900 \frac{\text{cm}^2}{\text{V-s}} (8.5 \cdot 10^{13} \text{ cm}^{-3}) \right]$$

$$\cdot (10 \text{ V}/\mu\text{m}) \quad \Rightarrow I_{\text{tot}} \approx 62.4 \text{ mA}$$

5.

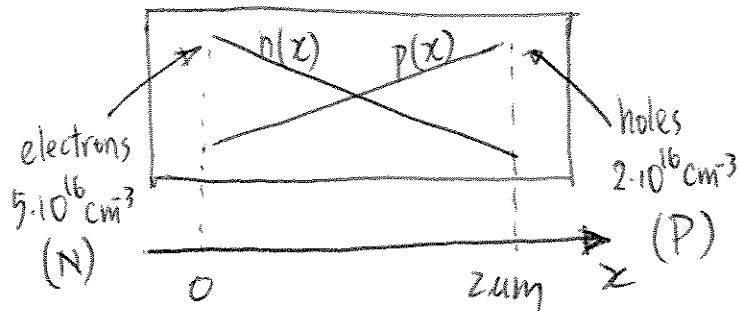

Given

$$D_n = 34 \text{ cm}^2/\text{s}$$

$$D_p = 12 \text{ cm}^2/\text{s}$$

$$L = 2 \mu\text{m}$$

$$A = (1 \mu\text{m})^2$$

The injected carriers diffuse from one end to the other.

$$I_{\text{tot}} = A \cdot J_{\text{tot}} = A \cdot q \left[ \frac{dn}{dx} D_n - \frac{dp}{dx} D_p \right]$$

$$= A \cdot q \left[ D_n \left( \frac{N}{L} \right) - D_p \left( \frac{P}{L} \right) \right]$$


$$= (1 \mu\text{m})^2 (1.6 \cdot 10^{-19} \text{ C}) \left[ \frac{34 \text{ cm}^2}{\text{s}} \left( \frac{5 \cdot 10^{16} \text{ cm}^{-3}}{2 \mu\text{m}} \right) - \frac{12 \text{ cm}^2}{\text{s}} \left( \frac{2 \cdot 10^{16} \text{ cm}^{-3}}{2 \mu\text{m}} \right) \right]$$

$$= -15.5 \mu\text{A}$$

b. Given Area = a

find total electrons stored.

$$n(x) = -\frac{N}{L}x + N$$

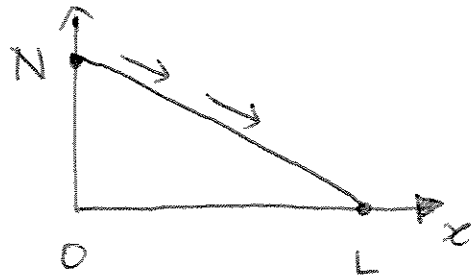

∴ total electrons stored

$$= \int a \cdot n(x) dx = \int_0^L a \left( -\frac{N}{L}x + N \right) dx$$


$$= aN \left( -\frac{x^2}{2L} + x \right) \Big|_0^L = \frac{aNL}{2}$$



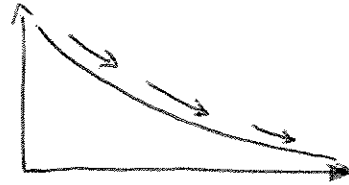7. Given Area = a

find total electrons stored.

$$n(x) = N \cdot \exp\left(\frac{-x}{L_d}\right)$$



∴ total electrons stored


$$= \int_0^{\infty} a \cdot n(x) \, dx = \int_0^{\infty} a \cdot N \cdot \exp\left(\frac{-x}{L_d}\right) \, dx$$

$$= aN \left( -L_d \cdot \exp\left(\frac{-x}{L_d}\right) \right) \Big|_0^{\infty} = aNL_d.$$

For the linear profile, the result depends on the length,  $L$ .

For the exponential profile, the result is constant (since  $L_d$  is constant.)

8.

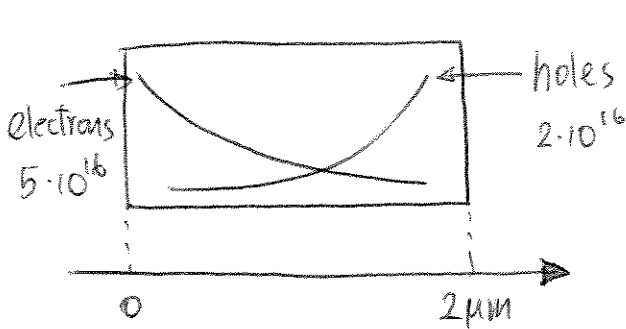

$$n(x) = N \exp(-x/L_d)$$

$$p(x) = P \exp\left(\frac{x-2}{L_d'}\right)$$

$$N = 5 \cdot 10^{16} \text{ cm}^{-3} \quad P = 2 \cdot 10^{16} \text{ cm}^{-3}$$

$$\text{total number of electrons} = \int a \cdot n \, dx$$

$$= \int_0^2 a \cdot n(x) \, dx = aN \left(-L_d \cdot \exp(-x/L_d)\right) \Big|_0^2$$

$$= aNL_d [1 - \exp(-2/L_d)]$$

$$\text{total number of holes} = \int a \cdot p \, dx$$

$$= \int_0^2 a \cdot p(x) \, dx = aP \left(L_d' \cdot \exp\left(\frac{x-2}{L_d'}\right)\right) \Big|_0^2$$


$$= aPL_d' [1 - \exp(-2/L_d')]$$

9. Drift is analogous to water flow in a river.

Water flows from top of mountain to bottom because of gravitational field; electron flows from one terminal to the other because of electric field.

| <u>DRIFT</u>   |   | <u>WATER FLOW</u>    |
|----------------|---|----------------------|
| electrons      | ↔ | water                |
| electric field | ↔ | gravitational field. |
| drift/current  | ↔ | water flow           |

10. (a)

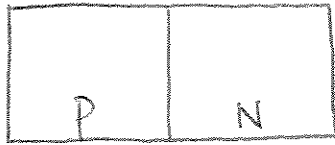

Assume Si.

$$\begin{aligned} N_A &= 4 \cdot 10^{16} \text{ cm}^{-3} & N_D &= 5 \cdot 10^{17} \text{ cm}^{-3} \end{aligned}$$

$$\begin{aligned} p_p &\approx N_A = 4 \cdot 10^{16} \text{ cm}^{-3} \\ n_p &= \frac{n_i^2}{p_p} = \frac{(1.08 \cdot 10^{10} \text{ cm}^{-3})^2}{4 \cdot 10^{16} \text{ cm}^{-3}} \approx 2.9 \cdot 10^3 \text{ cm}^{-3} \end{aligned}$$

$$\begin{aligned} n_n &\approx N_D = 5 \cdot 10^{17} \text{ cm}^{-3} \\ p_n &= \frac{n_i^2}{n_n} = \frac{(1.08 \cdot 10^{10} \text{ cm}^{-3})^2}{5 \cdot 10^{17} \text{ cm}^{-3}} \approx 2.3 \cdot 10^2 \text{ cm}^{-3} \end{aligned}$$

$$(b) \quad V_0 = \frac{kT}{q} \ln \left( \frac{N_A \cdot N_D}{n_i^2} \right)$$


$$@ 250 \text{ K} : V_0 = 0.905 \text{ V}$$

$$@ 300 \text{ K} : V_0 = 0.848 \text{ V}$$

$$@ 350 \text{ K} : V_0 = 0.789 \text{ V}$$

Towards higher temperatures,  $V_0 \sim T \ln\left(\frac{1}{T^3}\right)$ .  
That is, overall,  $V_0$  drops with higher  $T$ .

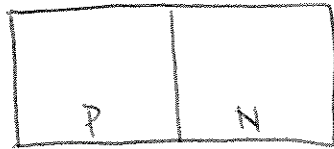11. Given  $N_D = 3 \cdot 10^{16} \text{ cm}^{-3}$        $n_i = 1.08 \cdot 10^{10} \text{ cm}^{-3}$



find  $V_0$ .

$$V_0 = \frac{kT}{q} \ln \left( \frac{N_D N_A}{n_i^2} \right) = \frac{kT}{q} \ln \left( \frac{N_D}{n_i} \right)$$

$$= \frac{(1.38 \cdot 10^{-23} \text{ J/K})(300 \text{ K})}{1.6 \cdot 10^{-19} \text{ C}} \ln \left( \frac{3 \cdot 10^{16} \text{ cm}^{-3}}{1.08 \cdot 10^{10} \text{ cm}^{-3}} \right)$$

$$= 0.384 \text{ V}$$

12. Given  $N_D = 3 \cdot 10^{16} \text{ cm}^{-3}$        $N_A = 2 \cdot 10^{15} \text{ cm}^{-3}$   
 $V_R = 1.6 \text{ V}$        $\epsilon_{Si} = 11.7 \times 8.85 \cdot 10^{-14} \frac{\text{F}}{\text{cm}^2}$

(a)  $n_i = 1.08 \cdot 10^{10} \text{ cm}^{-3}$

$$V_0 = \frac{kT}{q} \ln\left(\frac{N_A N_D}{n_i^2}\right) \approx (26 \text{ mV}) \ln\left[\frac{3 \cdot 10^{16} \times 2 \cdot 10^{15}}{(1.08 \cdot 10^{10})^2}\right]$$

$$= 0.698 \text{ V}$$

$$C_{j0} = \sqrt{\frac{\epsilon_{Si} \cdot q}{2} \cdot \frac{N_A N_D}{N_A + N_D} \cdot \frac{1}{V_0}}$$

$$= \left[ \frac{11.7 \times 8.85 \cdot 10^{-14} \times q}{2} \cdot \frac{3 \cdot 10^{16} \times 2 \cdot 10^{15}}{3 \cdot 10^{16} + 2 \cdot 10^{15}} \cdot \frac{1}{V_0} \right]^{\frac{1}{2}}$$

$$= 0.149 \text{ fF}/\mu\text{m}^2$$

$$\therefore C_j(V_R) = \left[1 + \frac{1.6}{V_0}\right]^{-\frac{1}{2}} \times C_{j0} = 0.082 \text{ fF}/\mu\text{m}^2$$

(b) Given  $C_{j,\text{new}} = 2 \cdot C_{j,\text{old}}$

$$\Rightarrow \sqrt{\frac{\frac{q \epsilon_{Si}}{2} \cdot \frac{N_A N_D}{N_A + N_D} \cdot \frac{1}{V_0}}{1 + \frac{V_R}{V_0}}} = \sqrt{\frac{\frac{q \epsilon_{Si}}{2} \cdot \frac{N_A N_D'}{N_A + N_D'} \cdot \frac{1}{V_0'}}{1 + \frac{V_R}{V_0'}}} \times 2$$

Squaring both sides & simplifying gives:

$$\frac{\left(\frac{N_D}{N_A + N_D}\right)}{V_0 + V_R} = 4 \cdot \frac{\left(\frac{N_{D'}}{N_A + N_{D'}}\right)}{V_0' + V_R}, \text{ where } N_{D'} = \text{old value.}$$

Here, there is only one variable,  $N_D$  (new value). The solution can be found iteratively by solving this equation. But we can make an assumption that  $V_0 + V_R \approx V_0' + V_R$  since  $V_R = 1.6 \text{ V}$ , the dominant term. Then we verify  $V_0$  &  $V_0'$  afterwards.

$$\Rightarrow \frac{N_D}{N_A + N_D} = 4 \frac{N_{D'}}{N_A + N_{D'}}$$


$$\Rightarrow N_D = \frac{4N_{D'}N_A}{N_A - 3N_{D'}} = \frac{4(2 \cdot 10^{15})(3 \cdot 10^{16})}{(3 \cdot 10^{16}) - 3 \cdot (2 \cdot 10^{15})} \approx 1.00 \cdot 10^{16} \text{ cm}^{-3}$$

$$\Rightarrow \frac{N_D}{N_{D'}} = \frac{1 \cdot 10^{16}}{2 \cdot 10^{15}} \approx 5$$

Verify:  $V_{0, \text{old}} = 0.698 \text{ V} \Rightarrow V_0 + V_R \approx 2.3 \text{ V}$   
 $V_{0, \text{new}} = 0.740 \text{ V} \Rightarrow V_0 + V_R \approx 2.3 \text{ V} \quad (\checkmark)$

$\therefore$  Increase  $N_D$  by 5 times.

B.

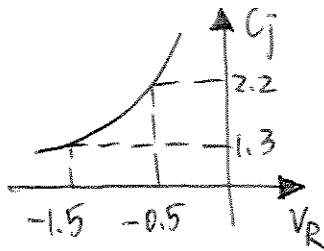

$$\frac{C_{j0}}{\sqrt{1 + \frac{0.5}{V_0}}} = 2.2 \quad \text{--- ①}$$

$$\frac{C_{j0}}{\sqrt{1 + \frac{1.5}{V_0}}} = 1.3 \quad \text{--- ②}$$

$$\text{①} \div \text{②} : \quad \frac{1 + \frac{1.5}{V_0}}{1 + \frac{0.5}{V_0}} = \left(\frac{2.2}{1.3}\right)^2 \Rightarrow V_0 = 0.0365 \text{ V}$$

Substitute  $V_0$  into ①:

$$C_{j0} = 2.2 \sqrt{1 + \frac{0.5}{V_0}} \approx 8.43 \text{ fF}/\mu\text{m}^2$$

$$\begin{aligned} \Rightarrow \frac{N_A N_D}{N_A + N_D} &= (C_{j0})^2 \cdot V_0 \cdot \frac{2}{\epsilon_{\text{eff}}} \\ &= \left(8.43 \frac{\text{fF}}{\mu\text{m}^2}\right)^2 \times (0.0365 \text{ V}) \cdot \frac{2}{\epsilon_{\text{eff}}} \approx 3.13 \cdot 10^{11} \text{ cm}^{-3} \end{aligned}$$



Fix a value for  $N_A > \frac{N_A N_D}{N_A + N_D} \cong \eta$

$$\begin{aligned} N_A = 2 \cdot 10^{18} \text{ cm}^{-3} &\Rightarrow N_D = \frac{\eta N_A}{N_A - \eta} \\ &= \frac{(3.13 \cdot 10^{17} \text{ cm}^{-3})(2 \cdot 10^{18} \text{ cm}^{-3})}{(2 \cdot 10^{18} - 3.13 \cdot 10^{17}) \text{ cm}^{-3}} \\ &\approx 3.71 \cdot 10^{17} \text{ cm}^{-3} \end{aligned}$$

14 (a) In forward bias,  $I_D = 1 \text{ mA}$ ,  $V_D = 750 \text{ mV}$


$$\begin{aligned}\therefore I_S &\approx I_D e^{-\frac{V_D}{V_T}} = (1 \text{ mA}) \exp[-750 \text{ mV}/26 \text{ mV}] \\ &= 2.97 \cdot 10^{-16} \text{ A}\end{aligned}$$

(b) Since  $I_S \propto \text{Area}$ , doubling area implies doubling  $I_S$ . From (a),

$$I_D = 1 \text{ mA} = 2 \times I_S e^{\frac{V_D}{V_T}}$$

$$\begin{aligned}\therefore V_D &= V_T \ln\left(\frac{I_D}{2I_S}\right) = (26 \text{ mV}) \ln\left(\frac{1 \text{ mA}}{2 \cdot 2.97 \cdot 10^{-16} \text{ A}}\right) \\ &= 0.732 \text{ V}\end{aligned}$$

15 (a)

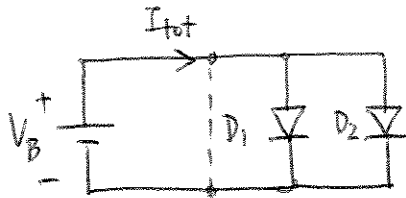

$$I_{tot} = I_{D_1} + I_{D_2} = I_{S_1} (e^{V_B/V_T} - 1) + I_{S_2} (e^{V_B/V_T} - 1)$$

$$= (I_{S_1} + I_{S_2}) (e^{V_B/V_T} - 1)$$

Therefore, the parallel combination operates as an exponential device, with an equivalent saturation current of  $I_{S_1} + I_{S_2}$ .

(b) By KVL,  $V_{D_1} = V_{D_2}$

$$\Rightarrow V_T \ln\left(\frac{I_{D_1}}{I_{S_1}}\right) = V_T \ln\left(\frac{I_{D_2}}{I_{S_2}}\right)$$


$$\text{Also, } I_{tot} = I_{D_1} + I_{D_2} \Rightarrow I_{D_2} = I_{tot} - I_{D_1}$$

$$\therefore V_T \ln\left(\frac{I_{D_1}}{I_{S_1}}\right) = V_T \ln\left(\frac{I_{tot} - I_{D_1}}{I_{S_2}}\right)$$

$$\Rightarrow I_{D_1} = I_{tot} \left( \frac{I_{S_1}}{I_{S_1} + I_{S_2}} \right)$$

$$\Rightarrow I_{D_2} = I_{tot} \left( \frac{I_{S_2}}{I_{S_1} + I_{S_2}} \right)$$

1b. (a)

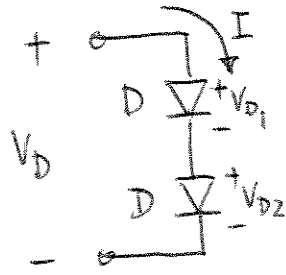


Suppose  $I_1 = I_s (e^{\frac{V_{D1}}{V_T}} - 1)$   
 $I_{D2} = I_s (e^{\frac{V_{D2}}{V_T}} - 1)$

By KCL,  $I_{D1} = I_{D2} = I$

$$\Rightarrow (e^{\frac{V_{D1}}{V_T}} - 1) = (e^{\frac{V_{D2}}{V_T}} - 1) \Rightarrow V_{D1} = V_{D2} = \frac{V_D}{2}$$
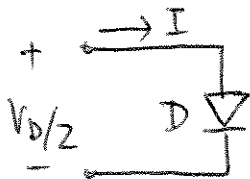
$$\therefore I = I_s (e^{\frac{(V_D/2)}{V_T}} - 1)$$




Therefore, a series combination can be viewed as a single two-terminal device with exponential characteristics.

(b) Suppose  $V_i$  = initial  $V_D$  . Need 10x increase in  $I$ .  
 $V_f$  = final  $V_D$

$$\Rightarrow 10 = \frac{I_s (e^{\frac{V_f}{V_T}} - 1)}{I_s (e^{\frac{V_i}{V_T}} - 1)} \approx e^{\frac{V_f - V_i}{V_T}}$$

$$\therefore \Delta V = V_f - V_i = V_T \ln(10) = (26 \text{ mV}) \ln(10) \approx 60. \text{ mV.}$$

17.

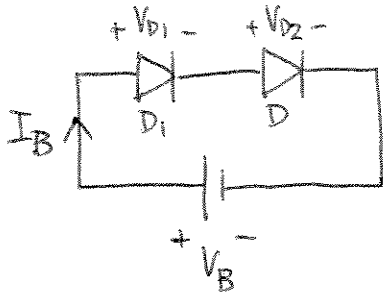

Find  $I_B$ ,  $V_{D1}$ ,  $V_{D2}$  in terms of  $V_B$ ,  $I_1$ ,  $I_{S2}$

$$\text{By KVL, } V_B = V_{D1} + V_{D2} = V_T \ln\left(\frac{I_B}{I_{S1}}\right) + V_T \ln\left(\frac{I_B}{I_{S2}}\right)$$


$$\Rightarrow V_B = V_T \ln\left(\frac{I_B^2}{I_{S1} I_{S2}}\right)$$

$$\therefore I_B = \sqrt{I_{S1} I_{S2}} \cdot \exp\left(\frac{V_B}{2V_T}\right) = \sqrt{I_{S1} I_{S2}} \cdot \exp\left(\frac{V_B}{2V_T}\right)$$

$$\begin{aligned} V_{D1} &= V_T \ln\left(\frac{I_B}{I_{S1}}\right) = V_T \ln\left(\frac{\sqrt{I_{S1} I_{S2}} \cdot \exp\left(\frac{V_B}{2V_T}\right)}{I_{S1}}\right) \\ &= V_T \ln\left(\sqrt{\frac{I_{S2}}{I_{S1}}}\right) + \frac{V_B}{2} \end{aligned}$$

$$\begin{aligned} V_{D2} &= V_T \ln\left(\frac{I_B}{I_{S2}}\right) = V_T \ln\left(\frac{\sqrt{I_{S1} I_{S2}} \cdot \exp\left(\frac{V_B}{2V_T}\right)}{I_{S2}}\right) \\ &= V_T \ln\left(\sqrt{\frac{I_{S1}}{I_{S2}}}\right) + \frac{V_B}{2} \end{aligned}$$

18.

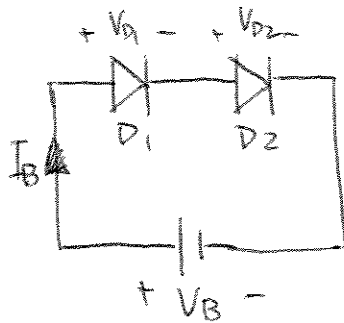

$$V_B = V_T \ln \frac{I_B}{I_{S1}} + V_T \ln \frac{I_B}{I_{S2}} = V_T \ln \left( \frac{I_B^2}{I_{S1} I_{S2}} \right)$$

$$\Rightarrow I_B = \sqrt{I_{S1} I_{S2}} \cdot \exp \frac{V_B}{2V_T}$$


Increase  $I_B$  by 10 times:

$$I_{B, \text{new}} = 10 I_B$$

$$\begin{aligned} \Rightarrow V_{B, \text{new}} &= V_T \ln \left( \frac{I_{B, \text{new}}^2}{I_{S1} I_{S2}} \right) = V_T \ln \left[ \frac{(10 I_B)^2}{I_{S1} I_{S2}} \right] \\ &= V_T \ln \left( \frac{I_B^2}{I_{S1} I_{S2}} \right) + V_T \ln 100 \\ &= V_B + V_T \ln 100 \approx V_B + 0.120 \text{ V} \end{aligned}$$

$\therefore V_B$  increases by 0.120 V.

19.

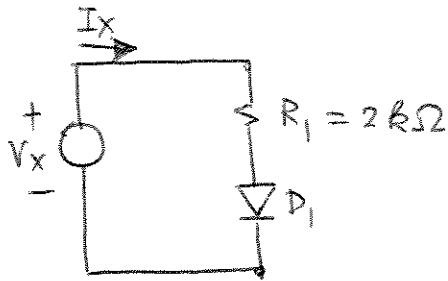

$$I_{D_1} = I_S \left( e^{\frac{V_{D_1}}{V_T}} - 1 \right)$$

$$I_S = 2 \cdot 10^{-15} \text{ A}$$

By KVL,  $V_x = I_x R_1 + V_{D_1}$

$$= I_x R_1 + V_T \ln \left( \frac{I_{D_1}}{I_S} \right)$$

$$= I_x R_1 + V_T \ln \left( \frac{I_x}{I_S} \right)$$

This can be solved directly with special programs or graphing calculators. But this can be solved iteratively, by hand.

$$\boxed{V_x = 0.5 \text{ V}}$$


We suppose that  $D_1$  is on.

$\Rightarrow$  current flows through  $D_1$ .

Assume a  $V_{D_1, \text{ON}}$ :

$$\Rightarrow V_{D_1} = 0.4 \text{ V}$$
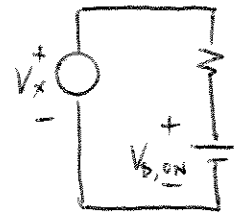
$$\Rightarrow I_x = \frac{V_x - V_{D_1}}{R_1} = \frac{(0.5 - 0.4) \text{ V}}{2 \text{ k}\Omega} = 0.05 \text{ mA}$$



$$V_{D_1} = V_T \ln \left( \frac{I_x}{I_S} \right) = (0.026 \text{ V}) \ln \left( \frac{0.05 \text{ mA}}{2 \cdot 10^{-15} \text{ A}} \right) \approx 0.62 \text{ V}$$

$\therefore$  Contradiction because  $V_{D_1}$  exceeds  $V_x$  !!

This means our assumption is incorrect

$$\Rightarrow D_1 \text{ is OFF} \Rightarrow V_{D_1} = V_x = 0.5 \text{ V} \quad I_x = 0$$

$V_x = 0.8 \text{ V}$  Suppose  $D_1$  is on. (This is a reasonable assumption since most diodes turn on at around  $V_D = 0.7 \text{ V}$ .)

For startup, use  $V_{D_1} = 0.7 \text{ V}$ .

$$V_{D_1} = 0.7 \text{ V} \Rightarrow I_x = \frac{V_x - V_{D_1}}{R_1} = 0.05 \text{ mA}$$

$$\Rightarrow V_{D_1} = V_T \ln(I_x / I_{S_1}) \approx 0.622 \text{ V}$$

$$V_{D_1} = 0.622 \text{ V} \Rightarrow I_x = \frac{(0.8 - 0.622) \text{ V}}{2 \text{ k}\Omega} = 0.089 \text{ mA}$$

$$\Rightarrow V_{D_1} = (0.026 \text{ V}) \ln\left(\frac{0.089 \text{ mA}}{2 \cdot 10^{-15} \text{ A}}\right) \approx 0.637 \text{ V}$$

$$V_{D_1} = 0.637 \text{ V} \Rightarrow I_x = \frac{(0.8 - 0.637) \text{ V}}{2 \text{ k}\Omega} = 0.082 \text{ mA}$$

$$\Rightarrow V_{D_1} = (0.026 \text{ V}) \ln\left(\frac{0.082 \text{ mA}}{2 \cdot 10^{-15} \text{ A}}\right) \approx 0.635 \text{ V}$$

$$V_{D_1} = 0.635 \text{ V} \Rightarrow I_x = \frac{(0.8 - 0.635) \text{ V}}{2 \text{ k}\Omega} = 0.083 \text{ mA}$$

$$\Rightarrow V_{D_1} = (0.026 \text{ V}) \ln\left(\frac{0.083 \text{ mA}}{2 \cdot 10^{-15} \text{ A}}\right) \approx 0.635 \text{ V}$$

∴ With an accuracy of three decimal points,

$V_{D_1} \approx 0.635 \text{ V}$  (of course, more iterations

$I_x \approx 0.082 \text{ mA}$  give a more accurate result.)



$V_x = 1\text{ V}$  Suppose, again, that  $D_1$  is on. Use  $V_{D_1}$  from previous calculations as starting point.

$$V_{D_1} = 0.635\text{ V} \Rightarrow I_x = \frac{(1 - 0.635)\text{ V}}{2\text{ k}\Omega} = 0.18\text{ mA}$$

$$\Rightarrow V_{D_1} = (0.026\text{ V}) \ln\left(\frac{0.18\text{ mA}}{2 \cdot 10^{-15}\text{ A}}\right) \approx 0.656\text{ V}$$

$$V_{D_1} = 0.656\text{ V} \Rightarrow I_x = \frac{(1 - 0.656)\text{ V}}{2\text{ k}\Omega} = 0.17\text{ mA}$$

$$\Rightarrow V_{D_1} = (0.026\text{ V}) \ln\left(\frac{0.17\text{ mA}}{2 \cdot 10^{-15}\text{ A}}\right) \approx 0.655\text{ V}$$

$$V_{D_1} = 0.655\text{ V} \Rightarrow I_x = \frac{(1 - 0.655)\text{ V}}{2\text{ k}\Omega} = 0.17\text{ mA}$$

$$\Rightarrow V_{D_1} = 0.655\text{ V}$$

$$\therefore V_{D_1} \approx 0.655\text{ V}$$

$$I_x \approx 0.17\text{ mA}$$

$V_x = 1.2\text{ V}$  Using similar assumptions as those in previous calculations,

$$V_{D_1} = 0.655\text{ V} \Rightarrow I_x = 0.27\text{ mA} \Rightarrow V_{D_1} \approx 0.667\text{ V}$$

$$V_{D_1} = 0.667\text{ V} \Rightarrow I_x = 0.27\text{ mA} \Rightarrow V_{D_1} \approx 0.666\text{ V}$$


$$V_{D_1} = 0.666\text{ V} \Rightarrow I_x = 0.27\text{ mA} \Rightarrow V_{D_1} \approx 0.666\text{ V}$$

$$\therefore I_x \approx 0.27\text{ mA}$$

$$V_{D_1} = 0.666\text{ V}$$

For more than 3x increase in  $I_x$ ,  $V_{D1}$  only increases by  $\sim 30\text{mV}$ , which is less than 10% of the turn-on voltage of the diode. In other words, once the diode conducts current, its voltage varies marginally (expected due to its exponential characteristic). This also implies that the diode, once on, can allow any amount of current to flow through (until  $V_{D1} \times I_{D1}$  becomes so large that the diode simply "breaks down").

20.

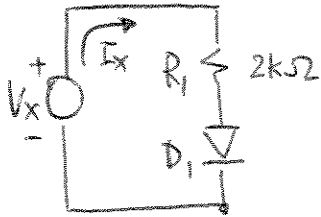

Since  $I_{s1} \propto \text{Area}$ ,  $I_{D1}$  becomes:

$$I_{D1} = \frac{10 \times (2 \cdot 10^{-15} \text{ A})}{I_{s1}'} \left( e^{\frac{V_{D1}}{V_T}} - 1 \right)$$

$V_x = 0.8 \text{ V}$  Suppose  $D_1$  is on. Assume  $V_{D1} = 0.7 \text{ V}$

$$V_{D1} = 0.7 \text{ V} \Rightarrow I_x = \frac{V_x - V_{D1}}{R_1} = \frac{0.1 \text{ V}}{2 \text{ k}\Omega} = 0.05 \text{ mA}$$

$$\Rightarrow V_{D1} = V_T \ln\left(\frac{I_x}{I_{s1}'}\right) = (0.026 \text{ V}) \ln\left(\frac{0.05 \text{ mA}}{20 \cdot 10^{-15} \text{ A}}\right) \\ = 0.563 \text{ V}$$

$$V_{D1} = 0.563 \text{ V} \Rightarrow I_x = \frac{(0.8 - 0.563) \text{ V}}{2 \text{ k}\Omega} = 0.12 \text{ mA}$$

$$\Rightarrow V_{D1} = (0.026 \text{ V}) \ln\left(\frac{0.12 \text{ mA}}{20 \cdot 10^{-15} \text{ A}}\right) \approx 0.585 \text{ V}$$

$$V_{D1} = 0.585 \text{ V} \Rightarrow I_x = \frac{(0.8 - 0.585) \text{ V}}{2 \text{ k}\Omega} = 0.11 \text{ mA}$$

$$\Rightarrow V_{D1} = (0.026 \text{ V}) \ln\left(\frac{0.11 \text{ mA}}{20 \cdot 10^{-15} \text{ A}}\right) \approx 0.583 \text{ V}$$

$$V_{D1} = 0.583 \text{ V} \Rightarrow I_x = \frac{(0.8 - 0.583) \text{ V}}{2 \text{ k}\Omega} = 0.11 \text{ mA}$$

$$\Rightarrow V_{D1} = 0.583 \text{ V}$$

$$\therefore V_{D1} \approx 0.583 \text{ V}$$

$$I_x \approx 0.11 \text{ mA}$$

$V_x = 1.2 \text{ V}$  Suppose  $D_1$  is on. Use results from previous calculations as starting point.

$$V_{D_1} = 0.583 \text{ V} \Rightarrow I_x = \frac{(1.2 - 0.583) \text{ V}}{2 \text{ k}\Omega} = 0.31 \text{ mA}$$

$$\Rightarrow V_{D_1} = (0.026 \text{ V}) \ln\left(\frac{0.31 \text{ mA}}{20 \times 10^{-15} \text{ A}}\right) \approx 0.610 \text{ V}$$

$$V_{D_1} = 0.610 \text{ V} \Rightarrow I_x = \frac{(1.2 - 0.610) \text{ V}}{2 \text{ k}\Omega} = 0.30 \text{ mA}$$

$$\Rightarrow V_{D_1} = (0.026 \text{ V}) \ln\left(\frac{0.30 \text{ mA}}{20 \times 10^{-15} \text{ A}}\right) \approx 0.609 \text{ V}$$

$$V_{D_1} = 0.609 \text{ V} \Rightarrow I_x = \frac{(1.2 - 0.609) \text{ V}}{2 \text{ k}\Omega} = 0.30 \text{ mA}$$


$$\Rightarrow V_{D_1} = 0.609 \text{ V}$$

$$\therefore V_{D_1} \approx 0.609 \text{ V}$$

$$I_x \approx 0.30 \text{ mA}$$

By increasing the cross-section area of  $D_1$ , intuitively this means  $D_1$  can conduct same amount of current with less  $V_{D_1}$ . The results have shown that in this problem,  $V_{D_1}$  is less and  $I_x$  is more.


21.

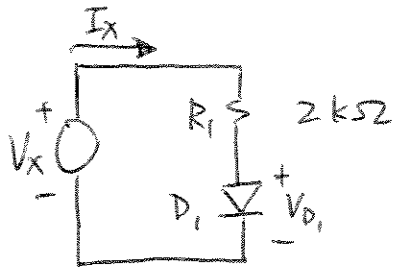Given: @  $V_x = 2V$ ,  $V_{D_1} = 850mV$ 

$$\Rightarrow I_x = \frac{V_x - V_{D_1}}{R_1} = 0.58 \text{ mA}$$

$$\begin{aligned} \therefore I_s &= \frac{I_x}{(e^{V_{D_1}/V_T} - 1)} \approx I_x \exp[-V_{D_1}/V_T] \\ &= (0.58 \text{ mA}) \exp[-0.85/0.026] \approx 3.64 \cdot 10^{-18} \text{ A} \end{aligned}$$

22.

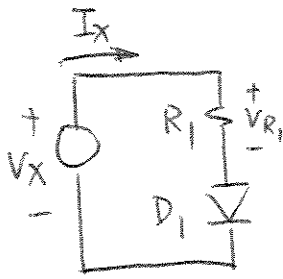

Given  $V_{R_1} = V_x/2$ , find  $V_x$ .  
 $I_s = 2 \cdot 10^{-16} \text{ A}$ .

By KCL,

$$\frac{V_{R_1}}{R_1} = I_s (e^{V_{D_1}/V_T} - 1)$$

Also,  $V_{R_1} = V_{D_1} = V_x/2$  (KVL).

$$\therefore \frac{V_x/2}{R_1} = I_s \cdot \left( \exp\left[\frac{V_{D_1}/2}{V_T}\right] - 1 \right)$$

This must be solved iteratively. From experience, suppose  $V_x = 2 \text{ V}$ .

$$V_x = 2 \text{ V} \Rightarrow I_x = \frac{V_x/2}{R_1} = \frac{1 \text{ V}}{2 \text{ k}\Omega} = 5 \text{ mA}$$

$$\begin{aligned} \Rightarrow V_x &= 2 \cdot V_{D_1} = 2V_T \ln(I_x/I_s) \\ &= 2(0.026 \text{ V}) \ln\left(\frac{5 \text{ mA}}{2 \cdot 10^{-16} \text{ A}}\right) \approx 1.48 \text{ V} \end{aligned}$$


$$V_x = 1.48 \text{ V} \Rightarrow I_x = \frac{1.48/2 \text{ V}}{2 \text{ k}\Omega} = 0.37 \text{ mA}$$

$$\Rightarrow V_x = 2(0.026 \text{ V}) \ln\left(\frac{0.37 \text{ mA}}{2 \cdot 10^{-16} \text{ A}}\right) \approx 1.47 \text{ V}$$

$$V_x = 1.47 \text{ V} \Rightarrow I_x = \frac{(1.47)/2 \text{ V}}{2 \text{ k}\Omega} = 0.37 \text{ mA}$$

$$\Rightarrow V_x = 1.47 \text{ V}$$

23.

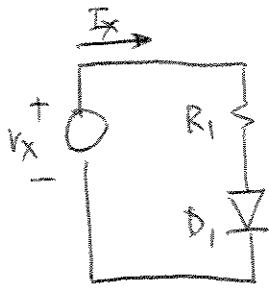

$$\text{Given } V_x = 1V \Rightarrow I_x = 0.2\text{mA}$$

$$V_x = 2V \Rightarrow I_x = 0.5\text{mA}$$

Find  $R_1$  and  $I_s$ .

$$\text{By KVL, } V_{D_1} = V_x - I_x R_1 = V_T \ln\left(\frac{I_x}{I_s}\right)$$

$$\Rightarrow 1 - (0.2\text{mA})R_1 = (0.026\text{V}) \ln\left(\frac{0.2\text{mA}}{I_s}\right) \quad \text{--- (1)}$$

$$2 - (0.5\text{mA})R_1 = (0.026\text{V}) \ln\left(\frac{0.5\text{mA}}{I_s}\right) \quad \text{--- (2)}$$

$$\text{(2) - (1) : } 1 - (0.3\text{mA})R_1 = (0.026\text{V}) \ln\left(\frac{0.5}{0.2}\right)$$

$$\Rightarrow R_1 = \frac{1 - (0.026) \ln\left(\frac{0.5}{0.2}\right)}{0.3\text{mA}} = 3.25\text{ k}\Omega$$

Substitute  $R_1$  into (1):

$$I_s = I_x \cdot \exp\left[-\frac{V_x - I_x R_1}{V_T}\right]$$

$$= (0.2\text{mA}) \exp\left[-\frac{1 - (0.2\text{mA})(3.25\text{k})}{0.026}\right] \approx 2.94 \cdot 10^{-10}\text{A}$$

$$\therefore R_1 \approx 3.25\text{ k}\Omega$$

$$I_s \approx 2.94 \cdot 10^{-10}\text{A}$$

24.

Given  $I_s = 3 \cdot 10^{-16} \text{ A}$ ,  
find  $V_{D_1}$ .



$$\text{By KCL, } I_x = \frac{V_{D_1}}{R_1} + I_{D_1} = \frac{V_T}{R_1} \ln\left(\frac{I_{D_1}}{I_s}\right) + I_{D_1}$$

Since  $I_x$ ,  $V_T$ ,  $R_1$  and  $I_s$  are known, this can be solved directly with special programs or graphing calculators. However, this can be also solved by iterations. Assume a  $V_{D_1}$ , calculate  $I_{D_1}$ , and re-iterate on  $V_{D_1}$ .

Assume  $V_{D_1} = 0.7 \text{ V}$  as starting point.

$$\boxed{I_x = 1 \text{ mA}}$$

$$V_{D_1} = 0.7 \text{ V} \Rightarrow I_{D_1} = I_x - \frac{V_{D_1}}{R_1} = 1 \text{ mA} - \frac{0.7 \text{ V}}{1 \text{ k}\Omega} = 0.3 \text{ mA}$$

$$\begin{aligned} \Rightarrow V_{D_1} &= V_T \ln\left(\frac{I_x}{I_s}\right) \\ &= (0.026 \text{ V}) \ln\left(\frac{0.3 \text{ mA}}{3 \cdot 10^{-16} \text{ A}}\right) \approx 0.718 \text{ V} \end{aligned}$$

$$V_{D_1} = 0.718 \text{ V} \Rightarrow I_{D_1} = 1 \text{ mA} - \frac{0.718 \text{ V}}{1 \text{ k}\Omega} = 0.28 \text{ mA}$$

$$\Rightarrow V_{D_1} = (0.026 \text{ V}) \ln\left(\frac{0.28 \text{ mA}}{3 \cdot 10^{-16} \text{ A}}\right) \approx 0.717 \text{ V}$$



$$V_{D_1} = 0.717 \text{ V} \Rightarrow I_{D_1} = 1 \text{ mA} - \frac{0.717 \text{ V}}{1 \text{ k}\Omega} = 0.28 \text{ mA}$$

$$\Rightarrow V_{D_1} = 0.717 \text{ V}$$

$$\therefore V_{D_1} \approx 0.717 \text{ V.}$$

$I_X = 2 \text{ mA}$  Assume  $V_{D_1} = 0.717 \text{ V}$  from previous result.

$$V_{D_1} = 0.717 \text{ V} \Rightarrow I_{D_1} = 2 \text{ mA} - \frac{0.717 \text{ V}}{1 \text{ k}\Omega} = 1.28 \text{ mA}$$

$$\Rightarrow V_{D_1} = (0.026 \text{ V}) \ln \left( \frac{1.28 \text{ mA}}{3 \cdot 10^{-16} \text{ A}} \right) \approx 0.756 \text{ V}$$

$$V_{D_1} = 0.756 \text{ V} \Rightarrow I_{D_1} = 2 \text{ mA} - \frac{0.756 \text{ V}}{1 \text{ k}\Omega} = 1.24 \text{ mA}$$

$$\Rightarrow V_{D_1} = (0.026 \text{ V}) \ln \left( \frac{1.24 \text{ mA}}{3 \cdot 10^{-16} \text{ A}} \right) \approx 0.755 \text{ V}$$

$$V_{D_1} = 0.755 \text{ V} \Rightarrow I_{D_1} = 2 \text{ mA} - \frac{0.755 \text{ V}}{1 \text{ k}\Omega} = 1.24 \text{ mA}$$

$$\Rightarrow V_{D_1} = 0.755 \text{ V}$$

$$\therefore V_{D_1} = 0.755 \text{ V}$$

$I_x = 4 \text{ mA}$  Assume  $V_{D_1} = 0.755 \text{ V}$  from previous result.

$$V_{D_1} = 0.755 \text{ V} \Rightarrow I_{D_1} = 4 \text{ mA} - \frac{0.755 \text{ V}}{1 \text{ k}\Omega} = 3.25 \text{ mA}$$

$$\Rightarrow V_{D_1} = (0.026 \text{ V}) \ln \left( \frac{3.25 \text{ mA}}{3 \cdot 10^{-16} \text{ A}} \right) \approx 0.780 \text{ V}$$


$$V_{D_1} = 0.780 \text{ V} \Rightarrow I_{D_1} = 4 \text{ mA} - \frac{0.780 \text{ V}}{1 \text{ k}\Omega} = 3.22 \text{ mA}$$

$$\Rightarrow V_{D_1} = (0.026 \text{ V}) \ln \left( \frac{3.22 \text{ mA}}{3 \cdot 10^{-16} \text{ A}} \right) \approx 0.780 \text{ V}$$

$\therefore V_{D_1} \approx 0.780 \text{ V}$ .

Note: As  $I_x$  increases,  $I_{D_1}$  increases, while  $(V_{D_1}/R_1)$  stays relatively the same. Because of the exponential characteristic, the diode, once on, will absorb as much current as necessary to satisfy KCL.

25.

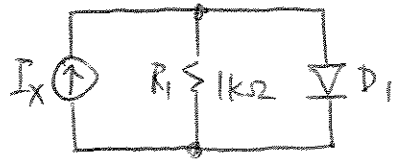


Given  $I_{D_1} = 0.5 \text{ mA}$  when  $I_x = 1.3 \text{ mA}$ , find  $I_s$ .

$$\begin{aligned} \text{This means } V_{D_1} &= (I_x - I_{D_1}) R_1 \\ &= (0.8 \text{ mA}) 1k\Omega = 0.8 \text{ V} \end{aligned}$$

$$\begin{aligned} \Rightarrow I_s &= I_{D_1} \cdot \exp[-V_{D_1}/V_T] \\ &= (0.5 \text{ mA}) \exp[-0.8 \text{ V}/0.026 \text{ V}] \\ &\approx 2.17 \cdot 10^{-17} \text{ A} \end{aligned}$$

26

Given  $I_{R_1} = I_x/2$   
 $I_s = 3 \cdot 10^{-16} \text{ A}$

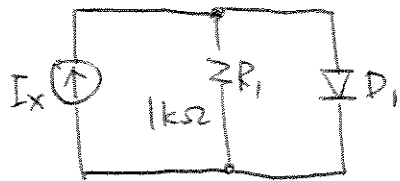find  $I_x$ .

$$V_{D_1} = \frac{I_x}{2} \cdot R_1 = V_T \ln \left( \frac{I_x/2}{I_s} \right)$$

This can be solved directly with special programs or graphing calculators. Alternatively, one can solve this iteratively by hand.

Assume  $V_D = 0.8 \text{ V}$ .

$$V_D = 0.8 \text{ V} \Rightarrow \frac{I_x/2}{R_1} = \frac{V_D}{1 \text{ k}\Omega} = \frac{0.8 \text{ V}}{1 \text{ k}\Omega} = 0.8 \text{ mA}$$

$$\Rightarrow V_D = V_T \ln \left( \frac{I_x/2}{I_s} \right) = (0.026 \text{ V}) \ln \left( \frac{0.8 \text{ mA}}{3 \cdot 10^{-16} \text{ A}} \right)$$

$$\approx 0.744 \text{ V}$$

$$V_D = 0.744 \text{ V} \Rightarrow \frac{I_x/2}{1 \text{ k}\Omega} = \frac{0.744 \text{ V}}{1 \text{ k}\Omega} = 0.744 \text{ mA}$$


$$\Rightarrow V_D = (0.026 \text{ V}) \ln \left( \frac{0.744 \text{ mA}}{3 \cdot 10^{-16} \text{ A}} \right) \approx 0.742 \text{ V}$$

$$V_D = 0.742V \Rightarrow I_x/2 = \frac{0.742V}{1k\Omega} = 0.742 \text{ mA}$$

$$\Rightarrow V_D = (0.026V) \ln\left(\frac{0.742 \text{ mA}}{3 \cdot 10^{-16} \text{ A}}\right) \approx 0.742V$$

$$\therefore I_x = 2(0.742 \text{ mA}) = 1.48 \text{ mA}$$

27.

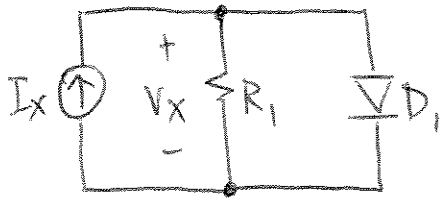

Given  $I_x = 1\text{mA} \rightarrow V_x = 1.2\text{V}$   
 $I_x = 2\text{mA} \rightarrow V_x = 1.8\text{V}$

find  $R_1$  and  $I_s$ .

$$I_{D_1} = I_x - V_x/R_1 \quad (\text{KCL})$$

$$\text{By KVL, } V_x = V_T \ln\left(\frac{I_{D_1}}{I_s}\right) = V_T \ln\left(\frac{I_x - V_x/R_1}{I_s}\right)$$

$$\Rightarrow (1.2\text{V}) = (0.026\text{V}) \ln\left[\frac{(1\text{mA}) - (1.2\text{V})/R_1}{I_s}\right] \quad \text{--- ①}$$

$$(1.8\text{V}) = (0.026\text{V}) \ln\left[\frac{(2\text{mA}) - (1.8\text{V})/R_1}{I_s}\right] \quad \text{--- ②}$$


$$\text{②} - \text{①}: 0.6\text{V} = (0.026\text{V}) \ln\left(\frac{2\text{mA} - 1.8\text{V}/R_1}{1\text{mA} - 1.2\text{V}/R_1}\right)$$

$$\Rightarrow R_1 = \frac{1.2 \cdot \exp\left[\frac{0.6}{0.026}\right] - 1.8}{1\text{mA} \cdot \exp\left[\frac{0.6}{0.026}\right] - 2\text{mA}} \approx 1.2\text{ k}\Omega$$

$$I_s = I_D \exp\left[-\frac{V_x}{V_T}\right] = \left(2\text{mA} - \frac{1.8\text{V}}{1.2\text{k}\Omega}\right) \exp\left[-\frac{1.8\text{V}}{0.026\text{V}}\right]$$

$$\approx 4.29 \cdot 10^{-34}\text{ A.}$$

28.

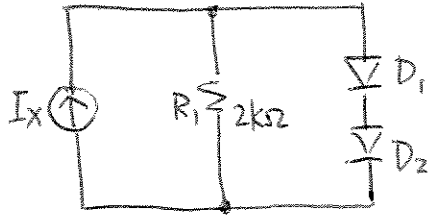

Given  $D_1 = D_2$  with  
 $I_s = 5 \cdot 10^{-16} \text{ A}$

Find  $V_{R_1}$  for  $I_x = 2 \text{ mA}$ .

Current through the diodes =  $I_D$   
 $= I_x - \frac{V_{R_1}}{R_1}$  where  $V_{R_1}$  = voltage across  $R_1$

$$\Rightarrow V_{R_1} = 2 \cdot V_T \ln\left(\frac{I_D}{I_s}\right) = 2 \left[ V_T \ln\left(\frac{I_x}{I_s} - \frac{V_{R_1}}{I_s R_1}\right) \right]$$

This can be solved directly with special programs or graphing calculators or by hand iteratively.

Assume a  $V_{R_1}$ , calculate  $I_D$ , and re-iterate on new  $V_{R_1} = (2 \times V_{D_1})$ . From experience, most diodes conduct at  $V_D \approx 0.7 \text{ V}$ . Assume  $V_{R_1} = 1.4 \text{ V}$ .

$$V_{R_1} = 1.4 \text{ V} \Rightarrow I_D = I_x - \frac{V_{R_1}}{R_1} = 2 \text{ mA} - \frac{1.4 \text{ V}}{2 \text{ k}\Omega} = 1.3 \text{ mA}$$

$$\Rightarrow V_{R_1} = 2 V_T \ln\left(\frac{I_D}{I_s}\right)$$

$$= 2(0.026 \text{ V}) \ln\left(\frac{1.3 \text{ mA}}{5 \cdot 10^{-16} \text{ A}}\right) \approx 1.49 \text{ V}$$

$$V_{R_1} = 1.49V \Rightarrow I_D = 2mA - \frac{1.49}{2k\Omega} = 1.26mA$$

$$\Rightarrow V_{R_1} = 2(0.026V) \ln\left(\frac{1.26mA}{5 \cdot 10^{-16}A}\right) \approx 1.48V$$


$$V_{R_1} = 1.48V \Rightarrow I_D = 2mA - \frac{1.48V}{2k\Omega} = 1.26mA$$

$$\Rightarrow V_{R_1} = 1.48V$$

∴ voltage across  $R_1 = 1.48V$



29.

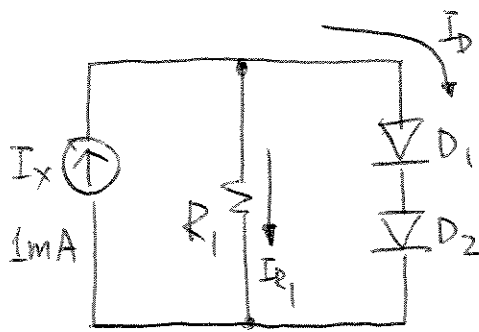

Given  $I_{R_1} = 0.5\text{ mA}$ ,  
 $I_s = 5 \cdot 10^{-16}\text{ A}$  for  
 each diode.

Find  $R_1$ .


$$\text{By KCL, } I_D = I_x - I_{R_1} = 0.5\text{ mA}$$

$$\Rightarrow V_{D_1} = V_{D_2} = V_T \ln\left(\frac{I_D}{I_s}\right) = 0.026 \ln\left(\frac{0.5\text{ mA}}{5 \cdot 10^{-16}\text{ A}}\right)$$

$$\approx 0.718\text{ V}$$


$$\therefore R_1 = \frac{V_{R_1}}{I_{R_1}} = \frac{2V_{D_1}}{I_{R_1}} = \frac{2(0.718\text{ V})}{0.5\text{ mA}} = 2.87\text{ k}\Omega$$

30.

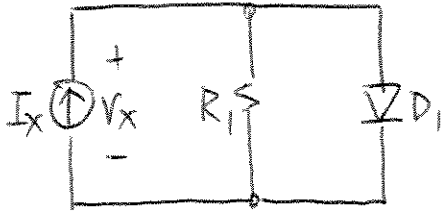

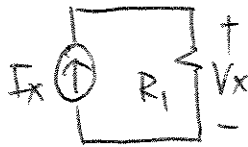
(a) Constant-voltage model:

Consider, first, the extreme cases: when  $D_1$  is off, we have the following:




This implies  $V_x$  is linearly proportional to  $I_x$

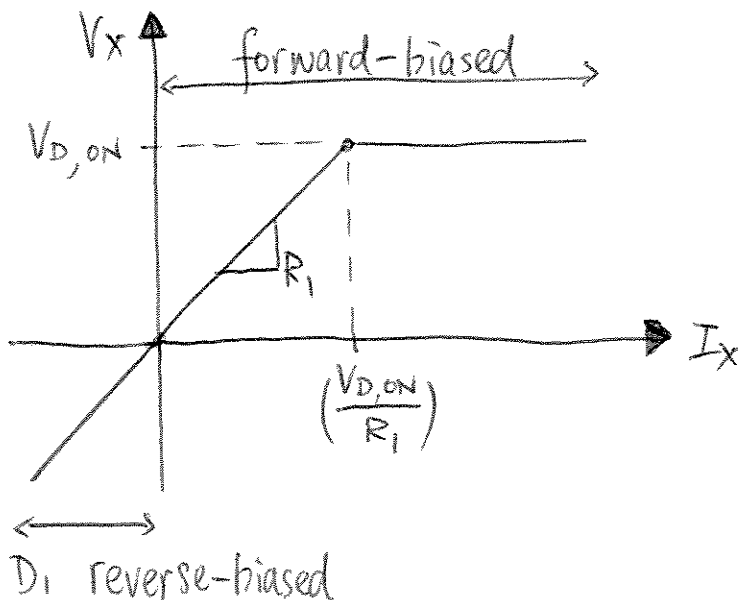When  $D_1$  is on,  $V_x$  is fixed (by KVL) by  $D_1$  ( $= V_{D,ON}$ ). This implies that any additional current from  $I_x$  cannot flow through  $R_1$ , which means  $D_1$  will absorb all the currents to satisfy KVL.



(b) exponential model :

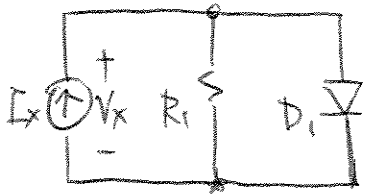

Assume  $I_s$  negligible.


When  $D_1$  is off, most of  $I_x$  flows through  $R_1$ . When  $D_1$  is on,  $V_{D_1} (= V_x)$  follows this relationship:

$$V_{D_1} = V_x = V_T \ln\left(\frac{I_{D_1}}{I_s}\right) = V_T \ln\left(\frac{I_x - \frac{V_x}{R_1}}{I_s}\right)$$


$$\Rightarrow I_x = I_s \exp(V_x/V_T) + V_x/R_1$$

$$\approx I_s \exp(V_x/V_T) \quad \text{when } D_1 \text{ is forward-biased } (V_x > V_T)$$


i.e.  $V_x \approx V_T \ln(I_x/I_s)$

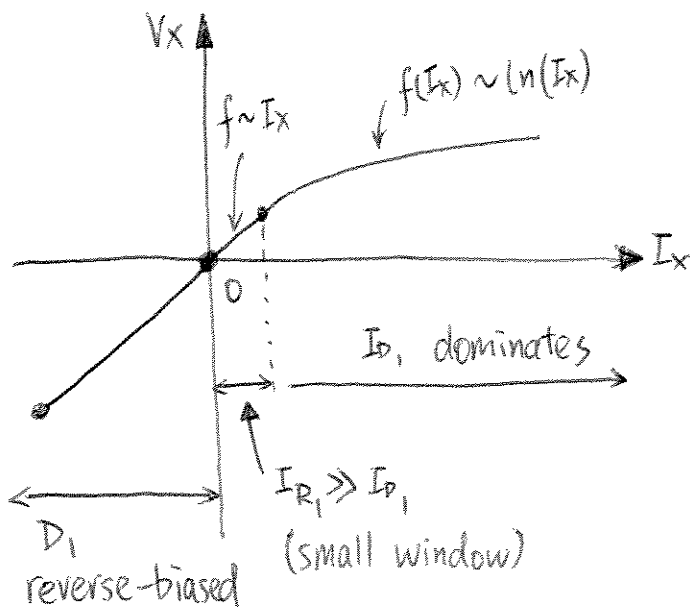

①


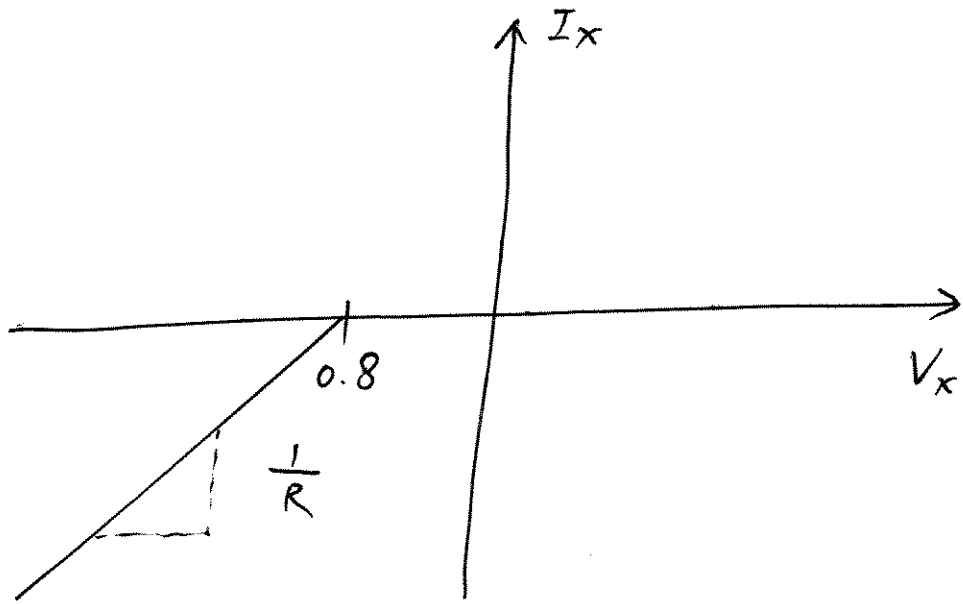


(2)


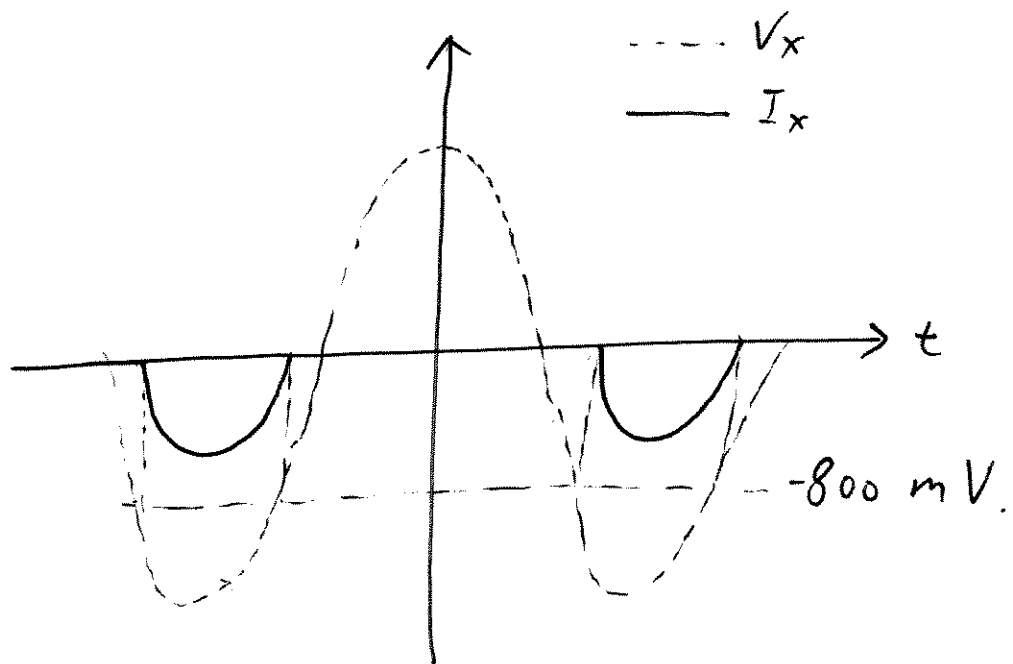


④


$V_B = -1V$

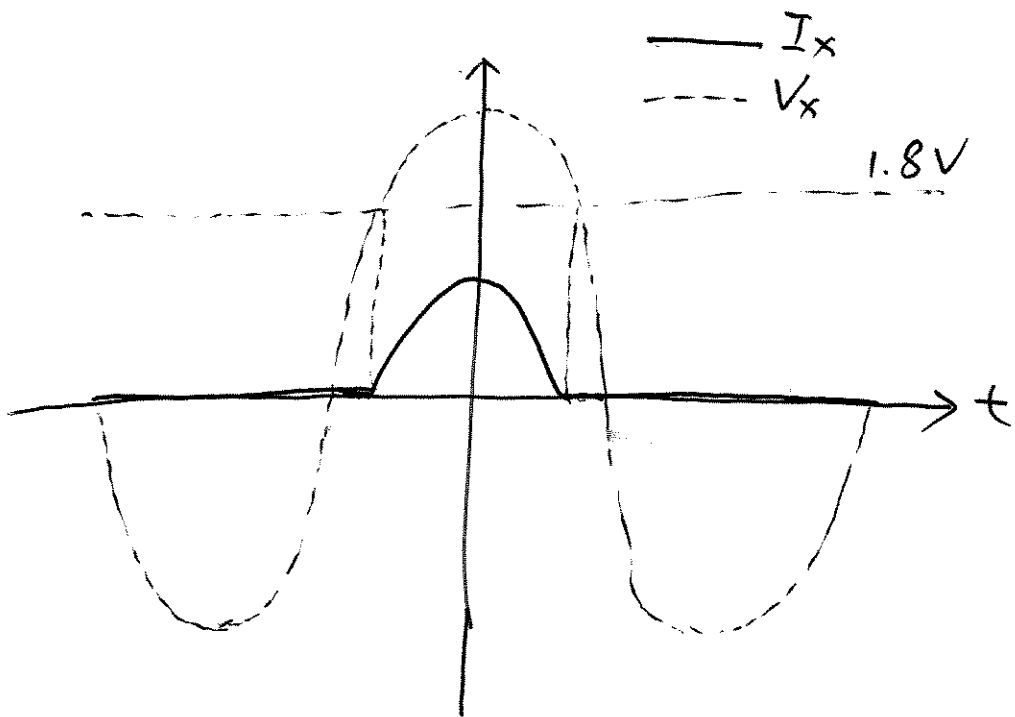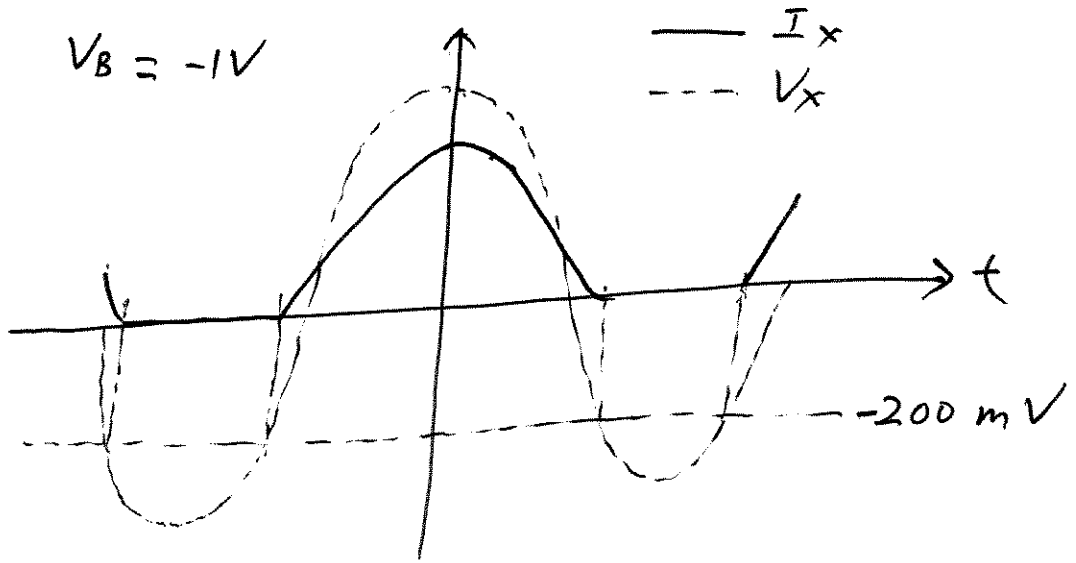

(5)

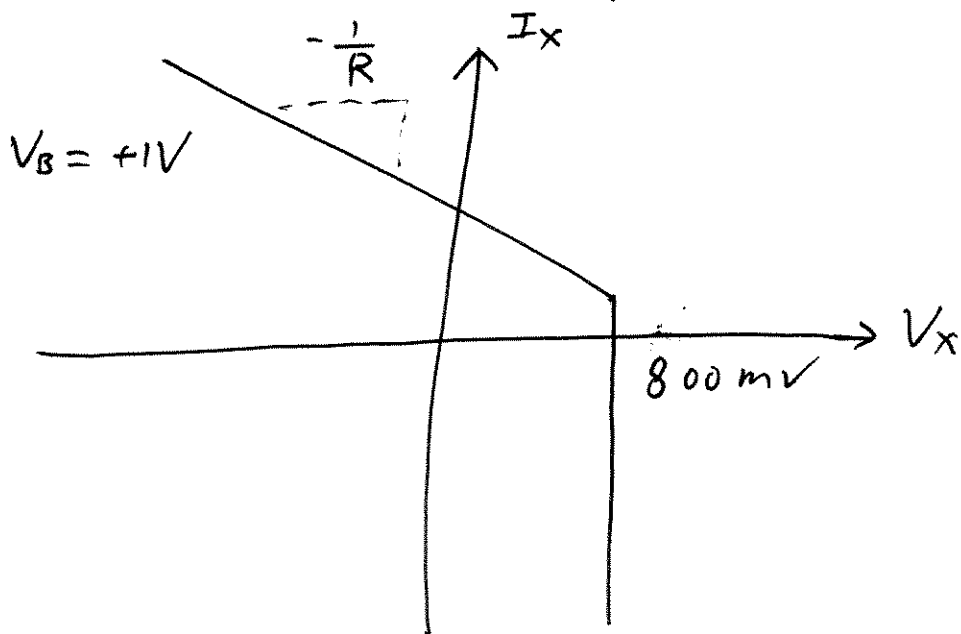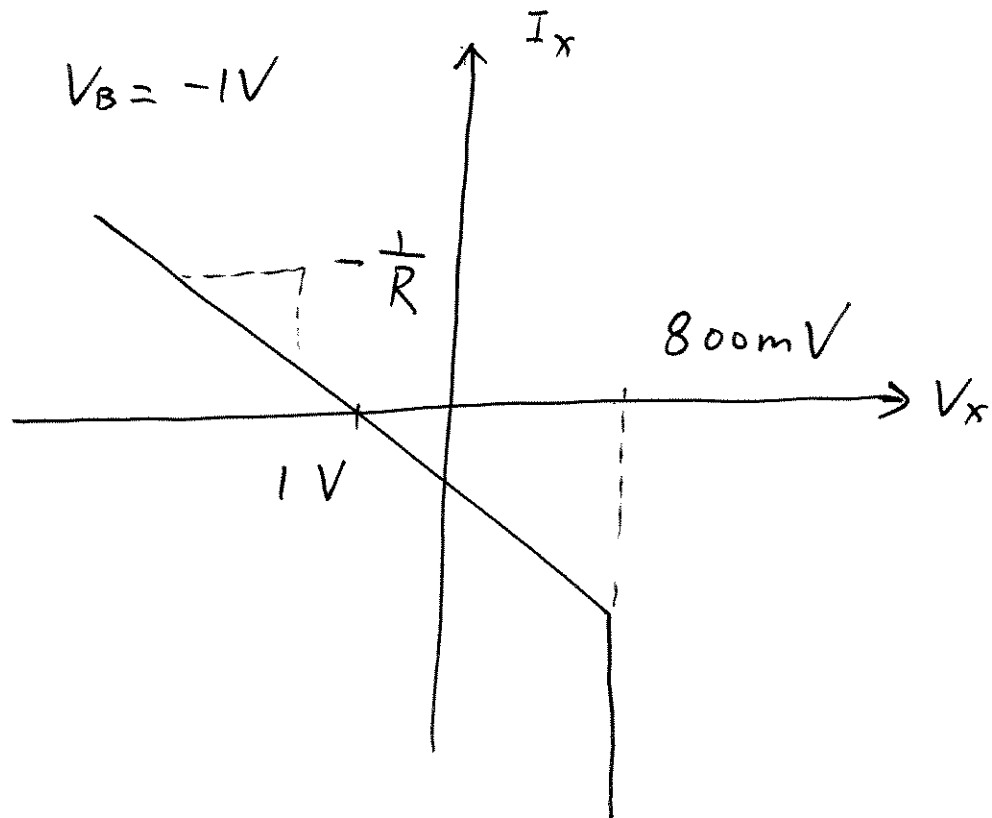

⑥




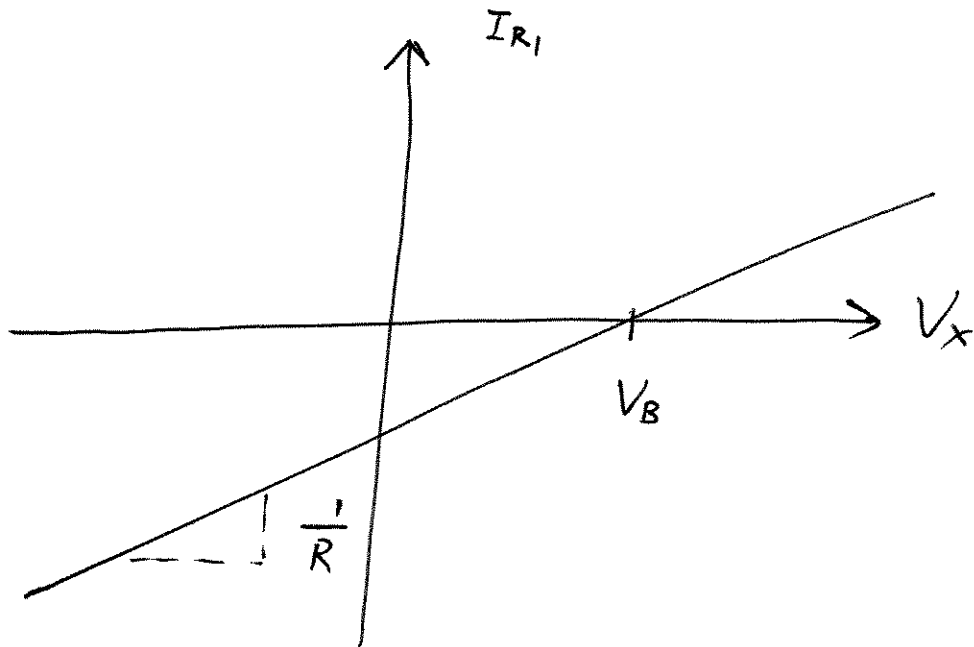


$I_{D_1} = 0$  for all  $V_x$





( $\because V_B > 0$ ,  $D_1$  is reverse-biased)



(7)

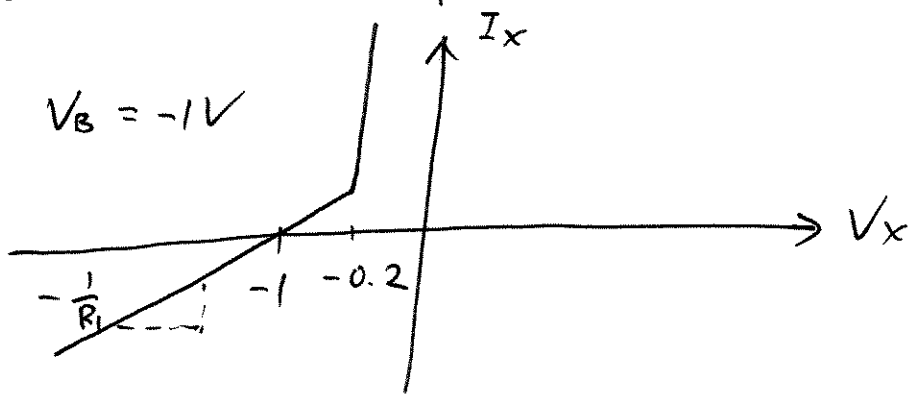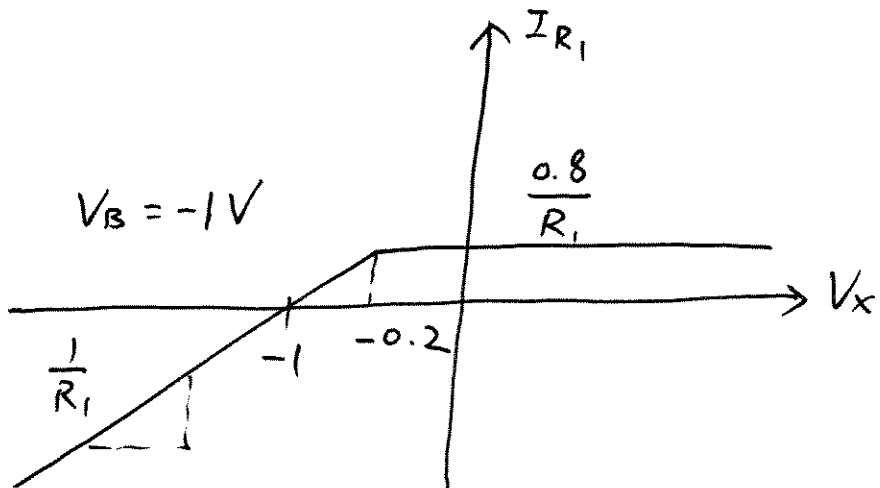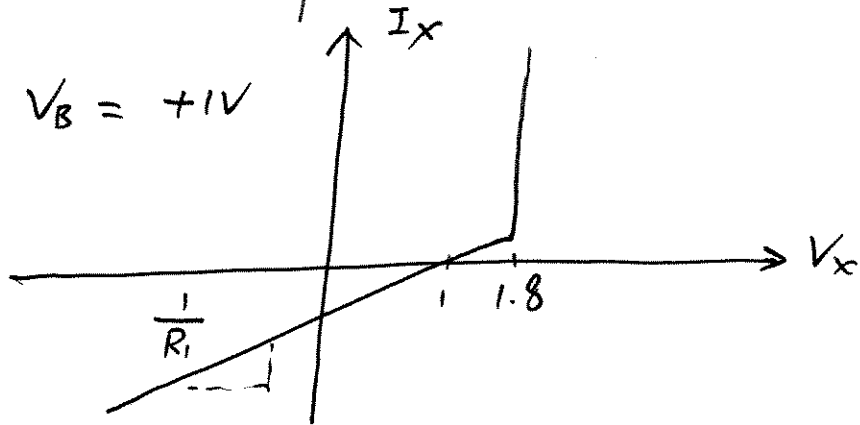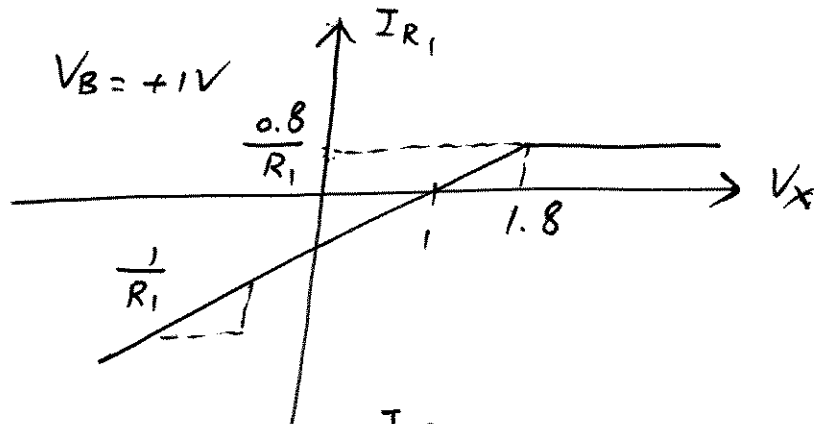


8

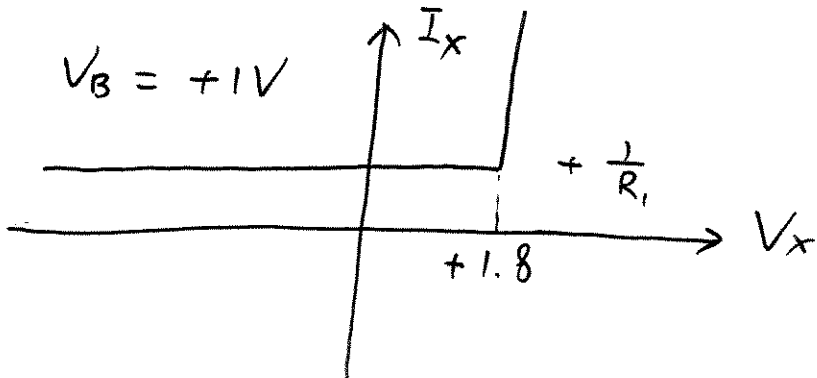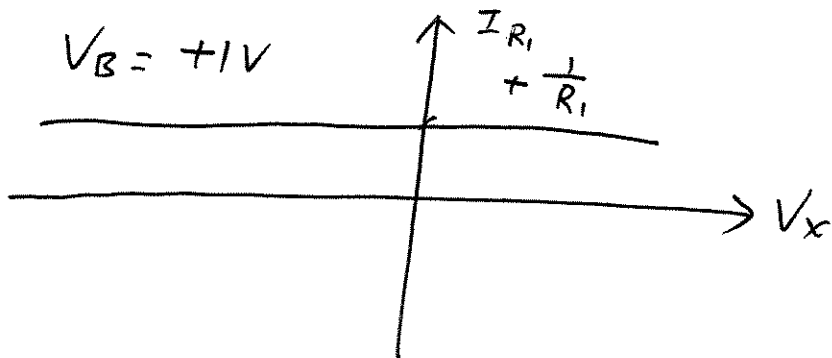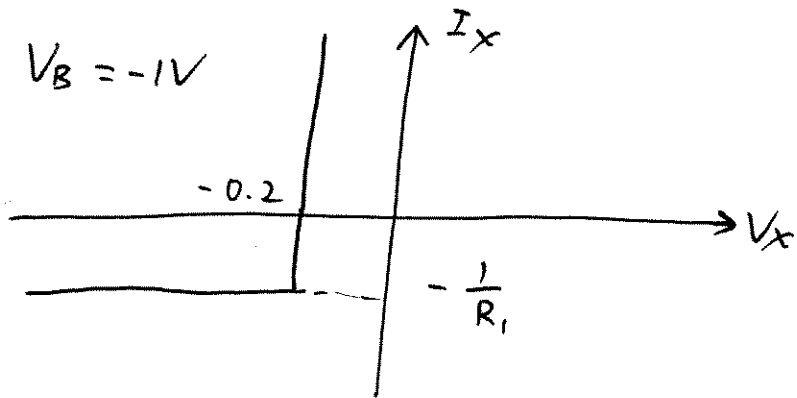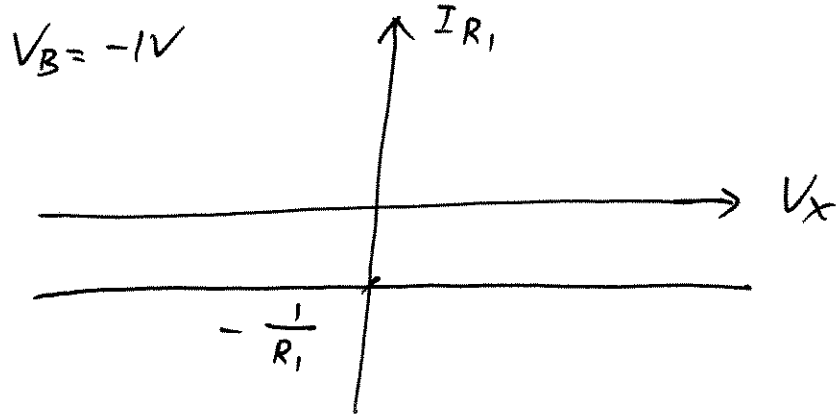


(9)


a)

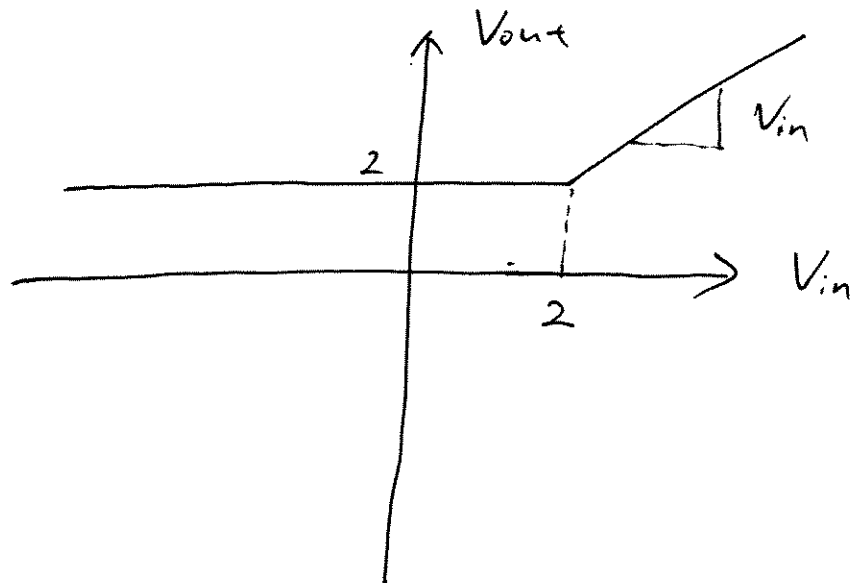


b)

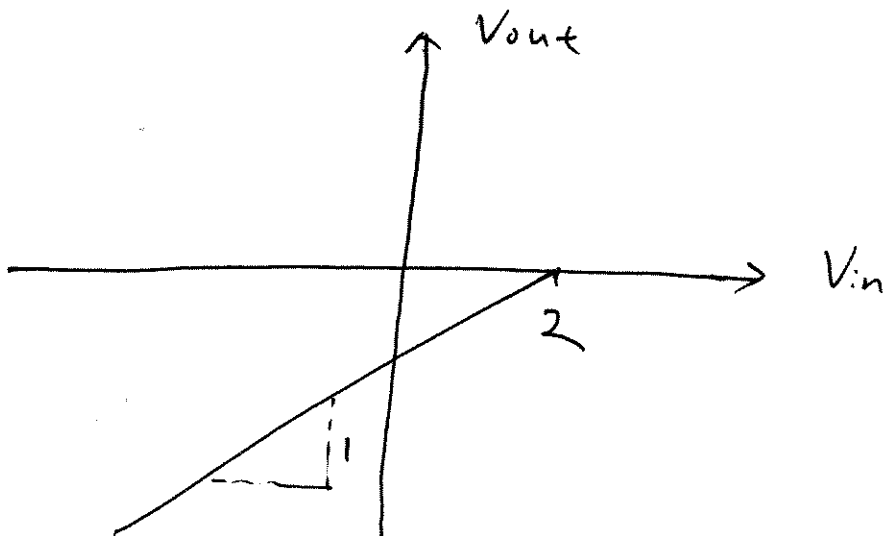


c)

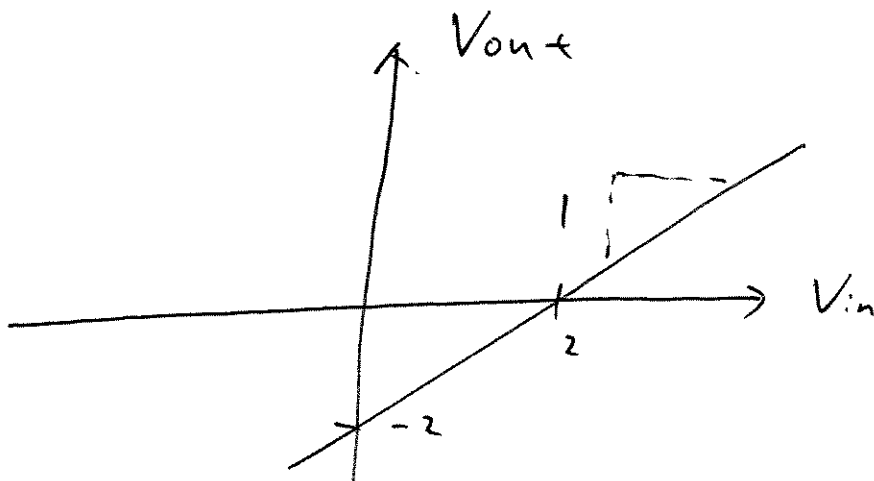


d)

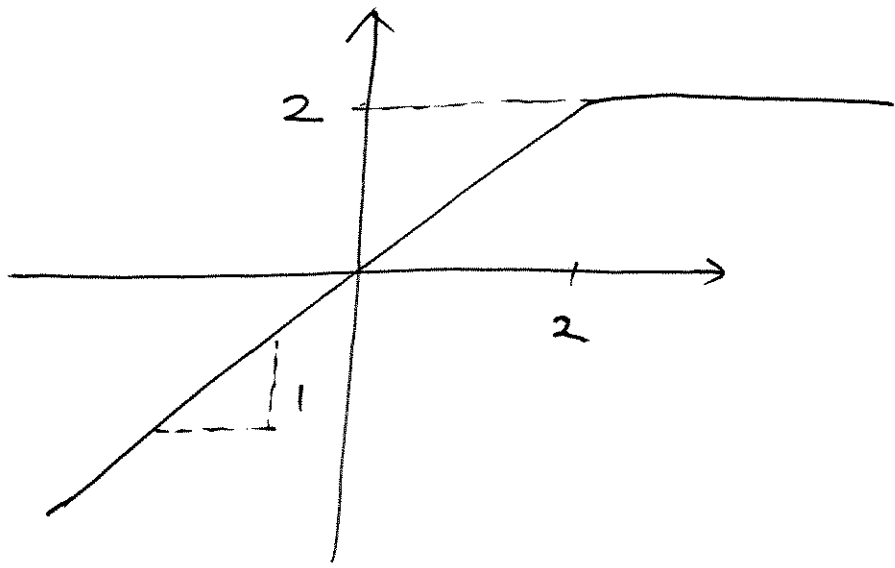


e)

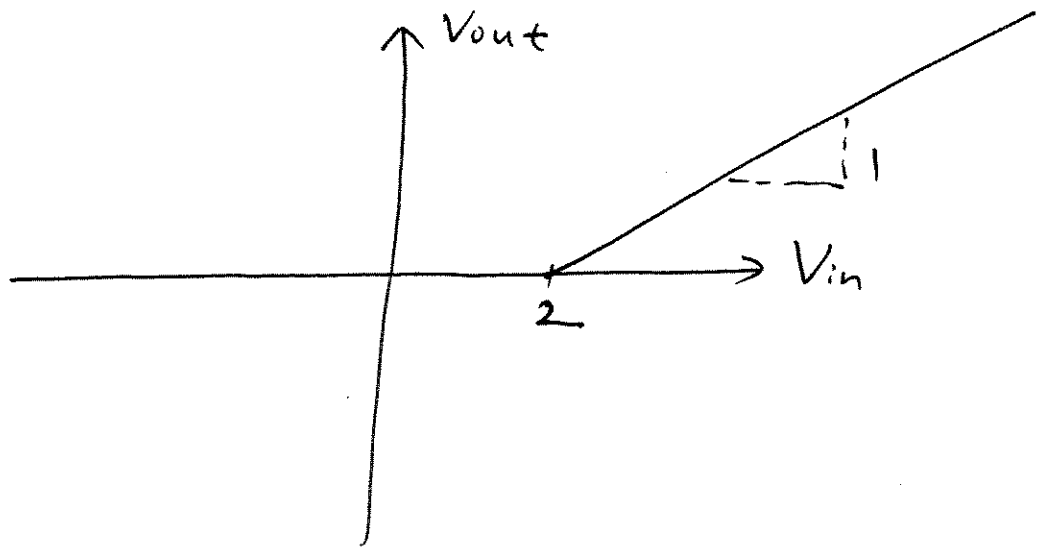


(10) a/

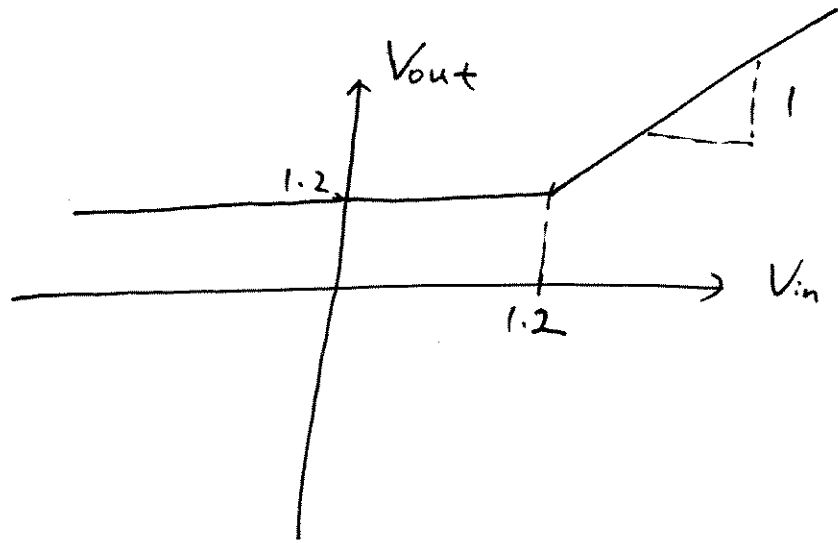


b/

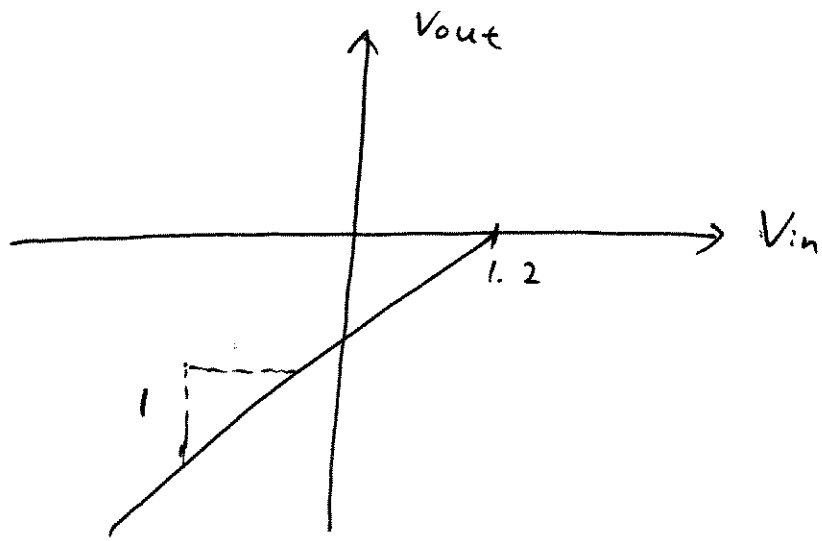


c/

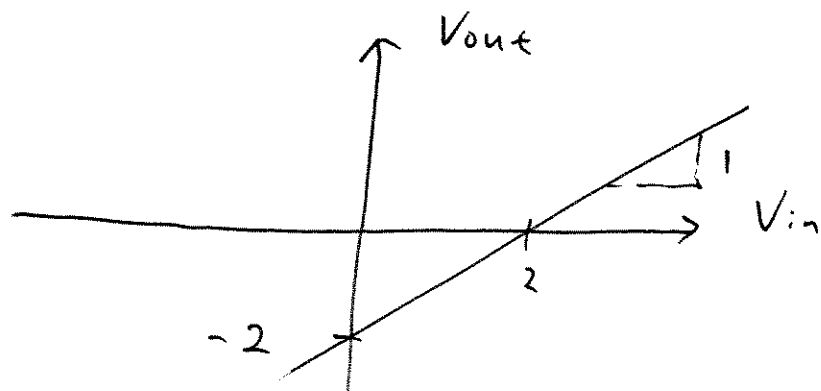


d)

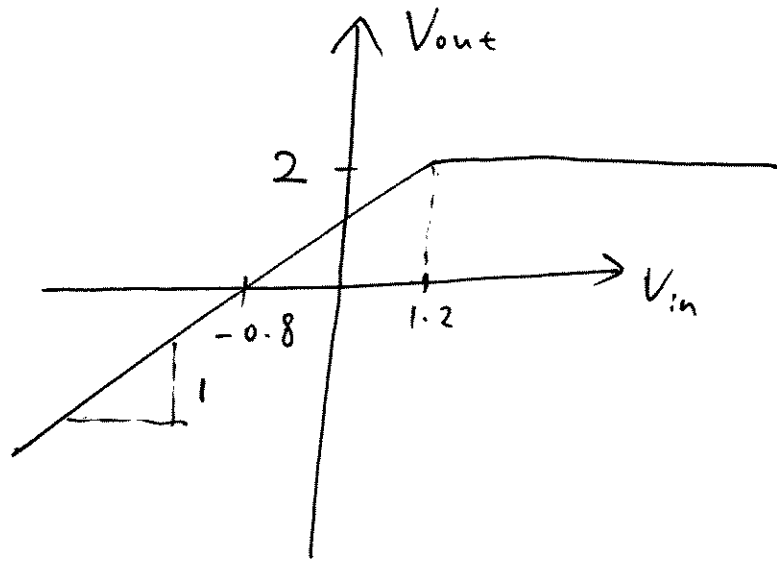

e)

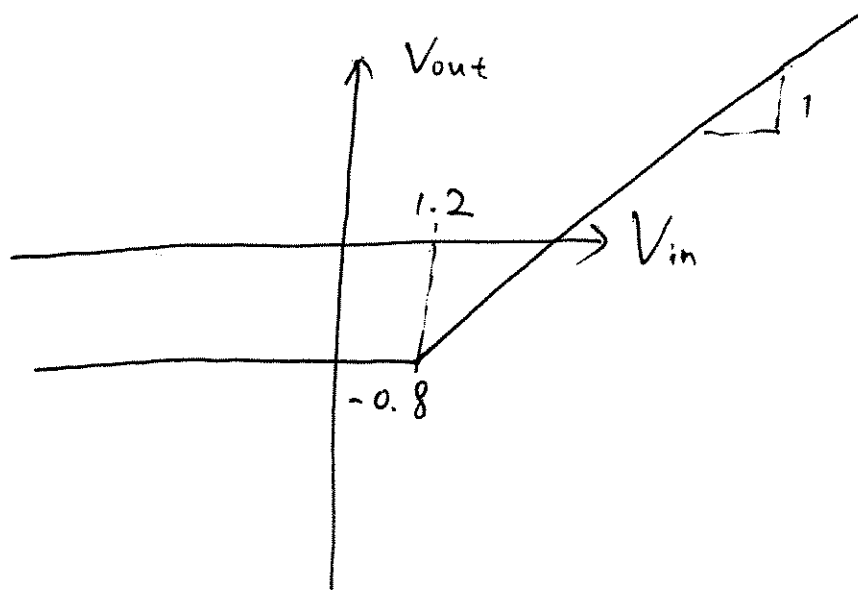


⑪ a)

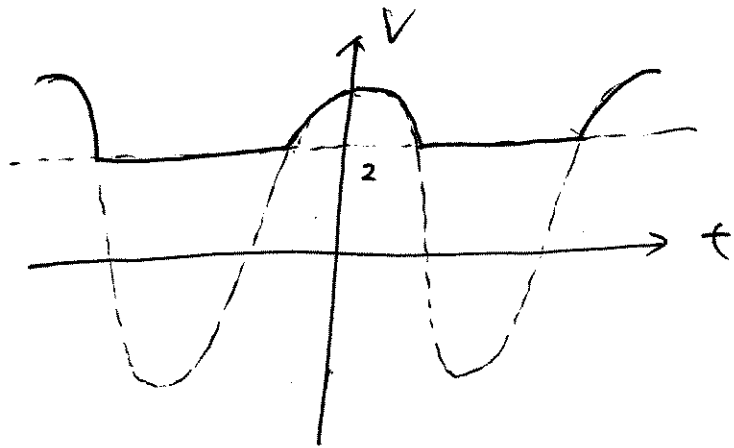


—  $V_{out}$   
- - -  $V_{in}$

b)

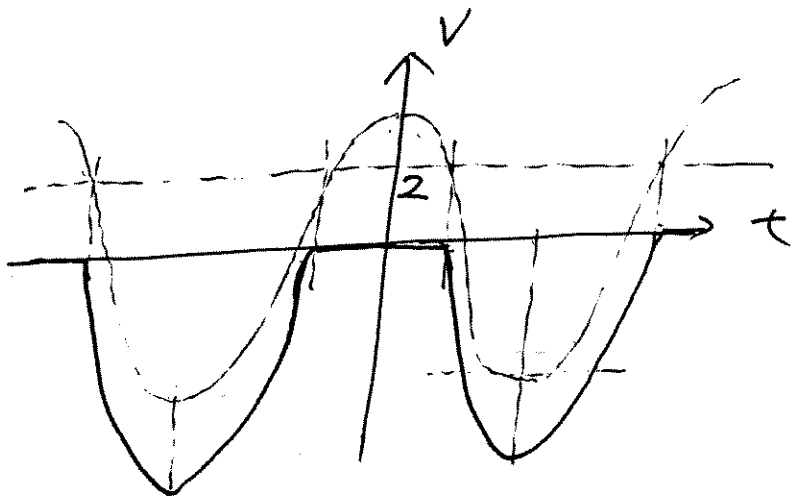


—  $V_{out}$   
- - -  $V_{in}$

c)

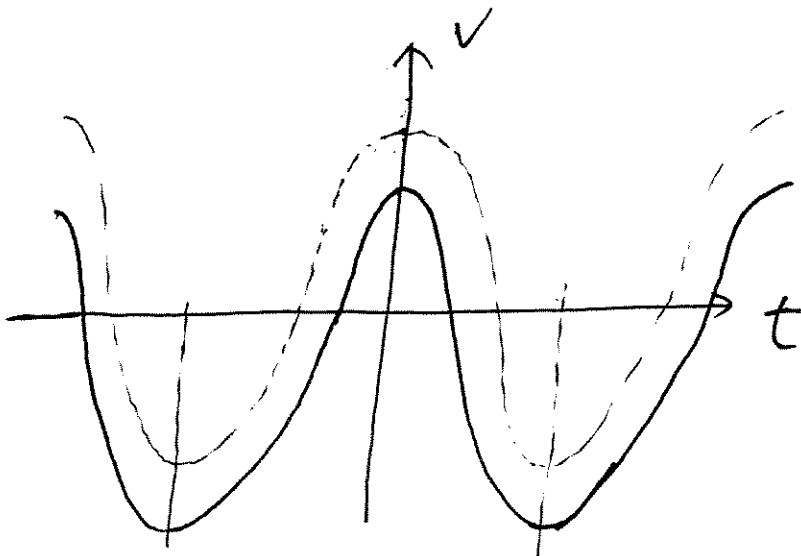


—  $V_{out}$   
- - -  $V_{in}$

d)

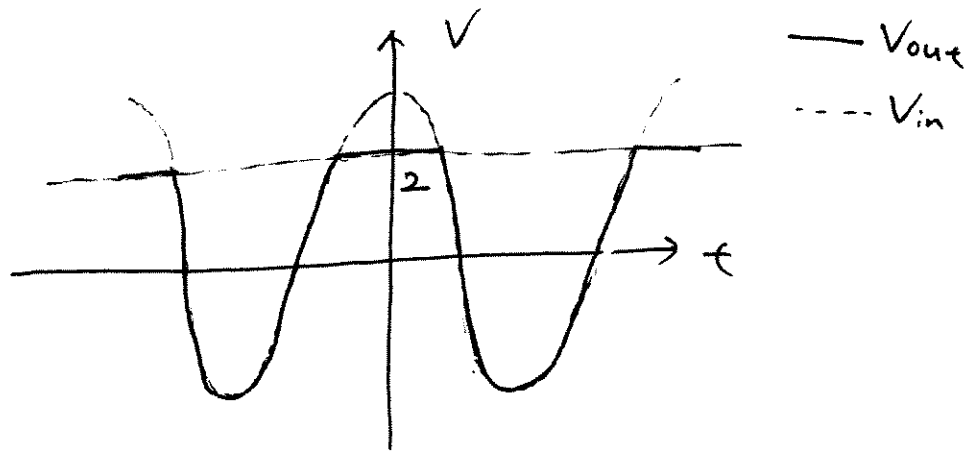


e)

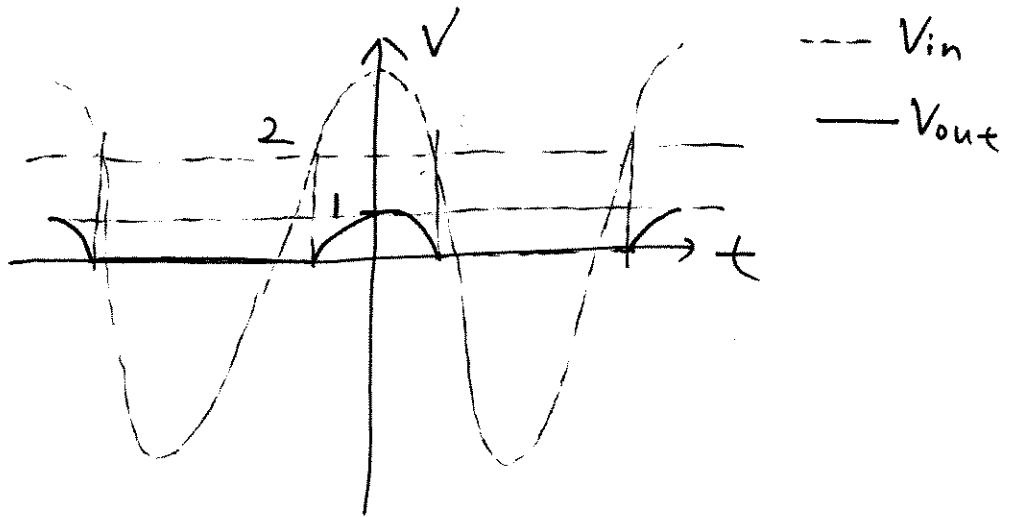





⑫ a)

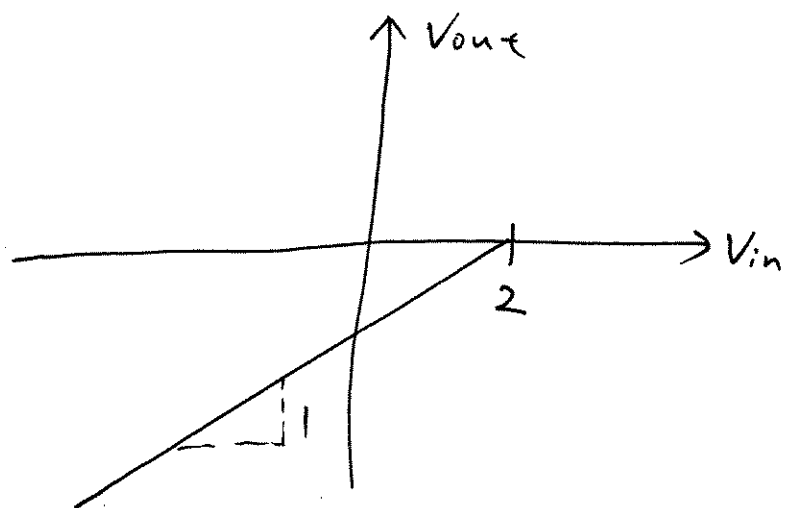


b)

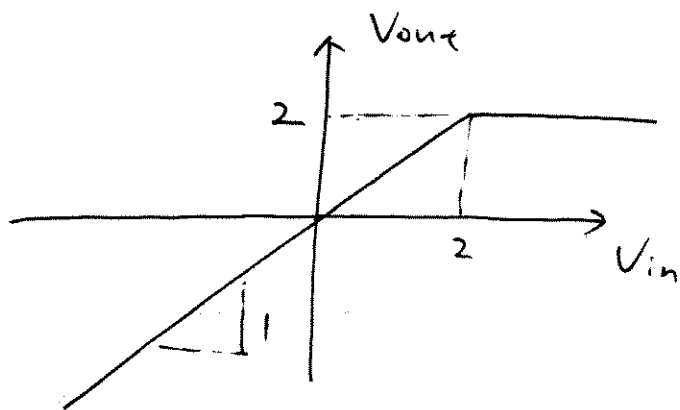


c)

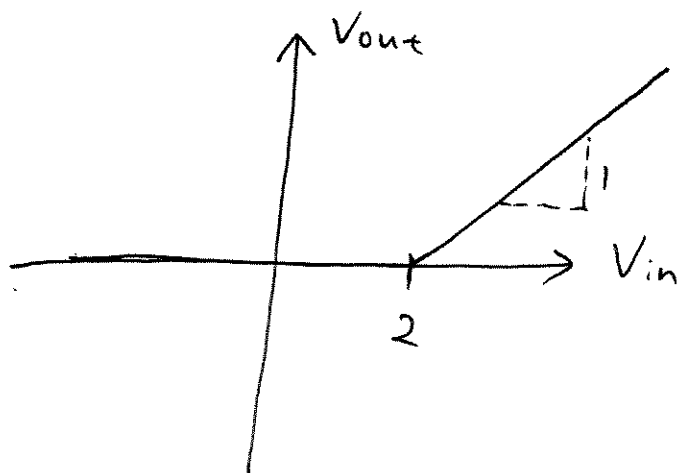


d)

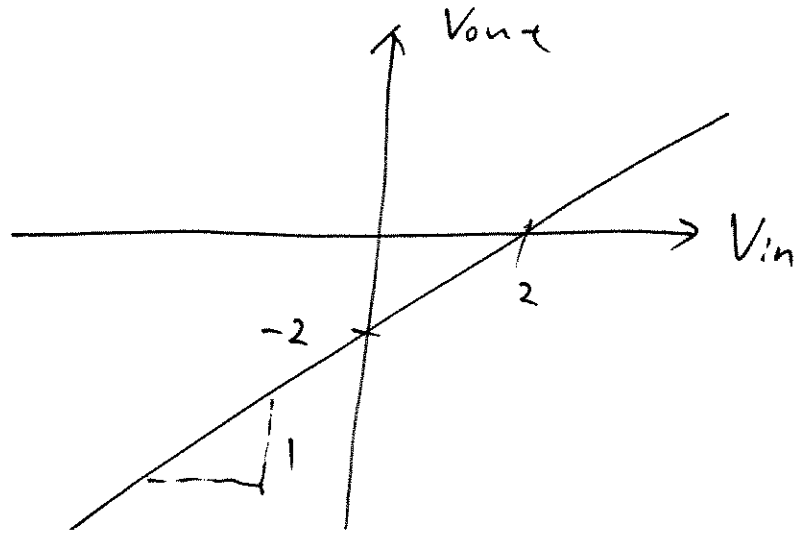


e)

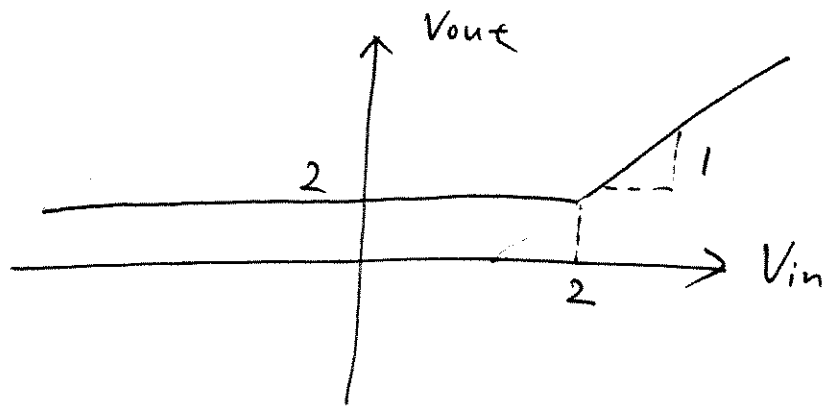


⑬ a)

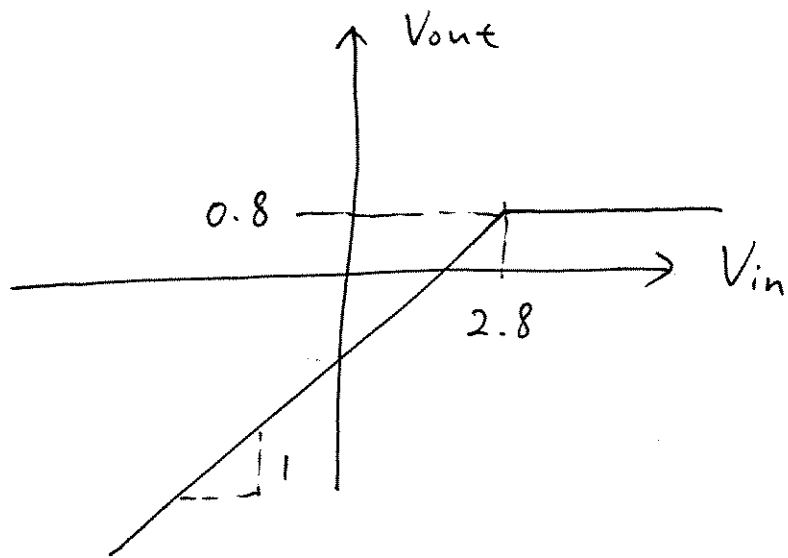


b)

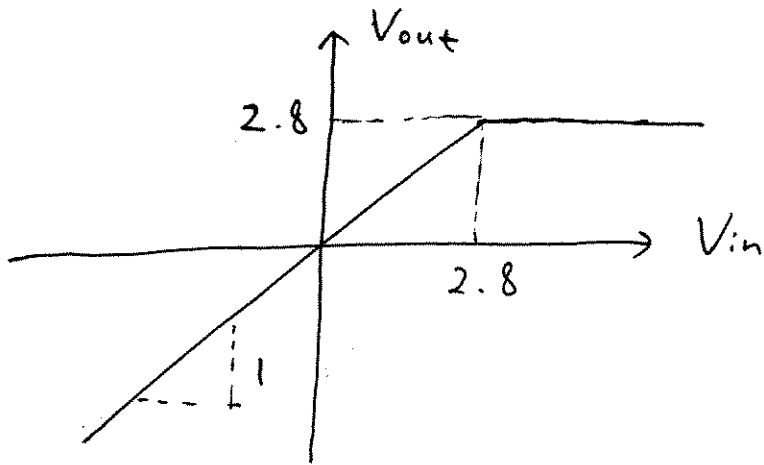


c)

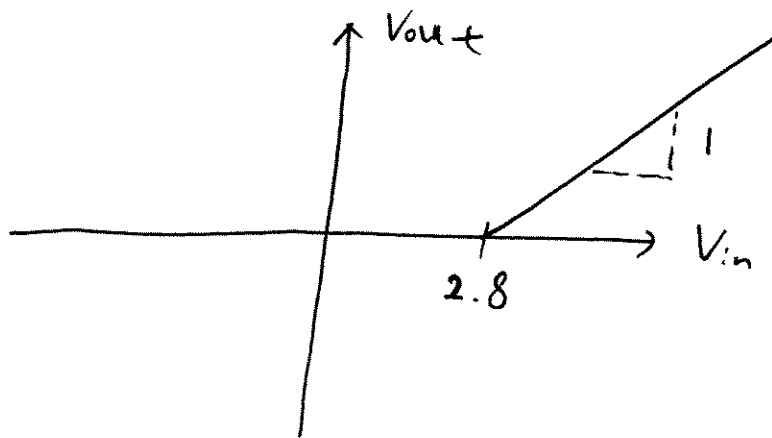


d)

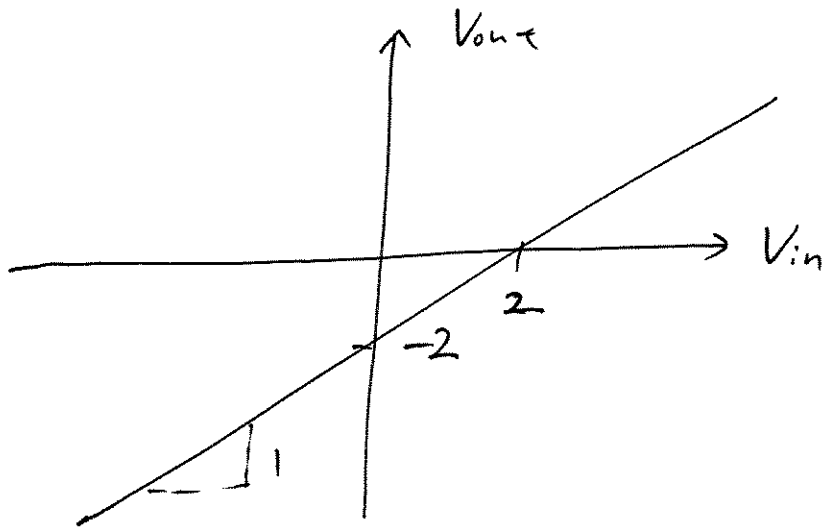


e)

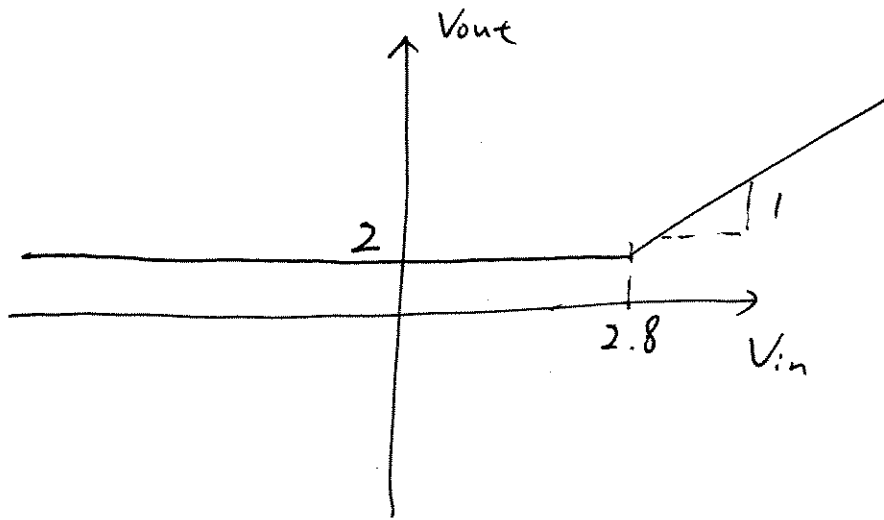


(14) a)

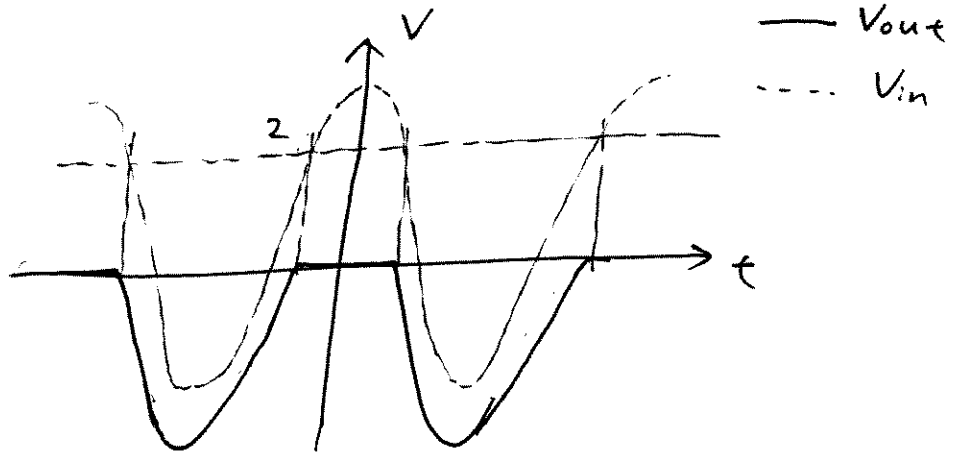


b)

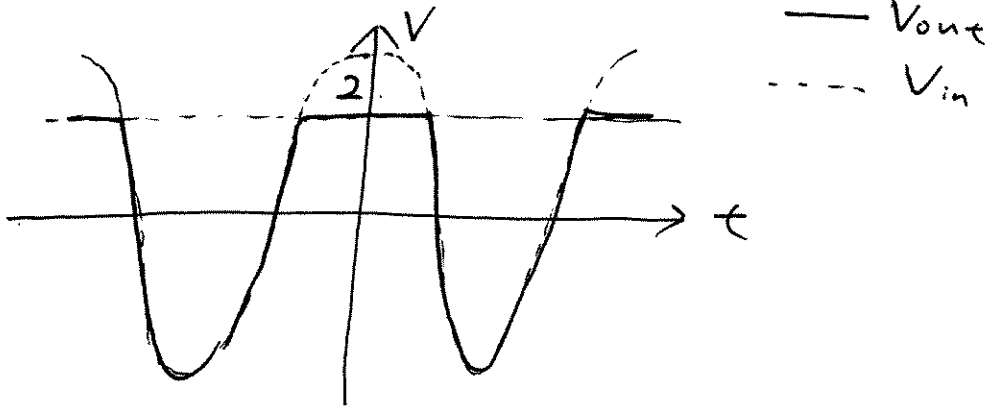


c)

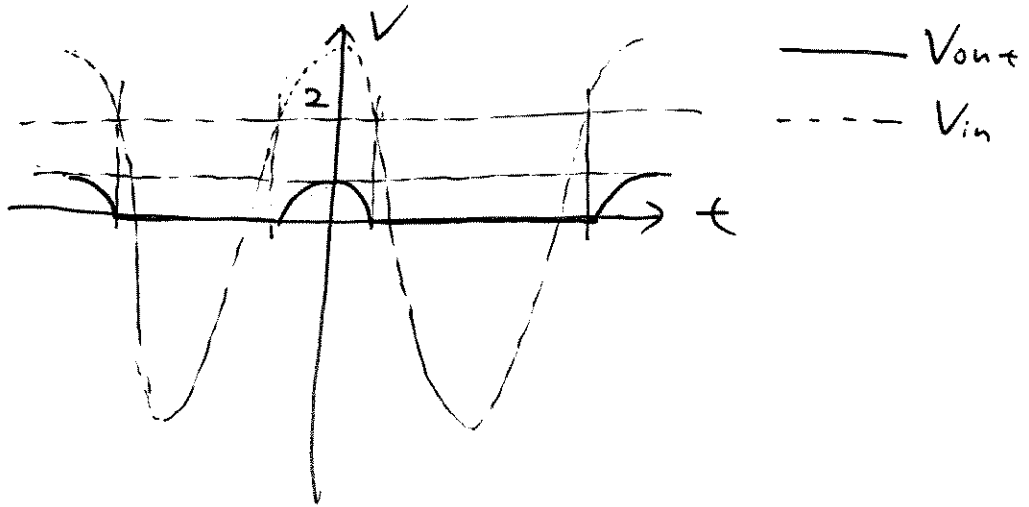


d)

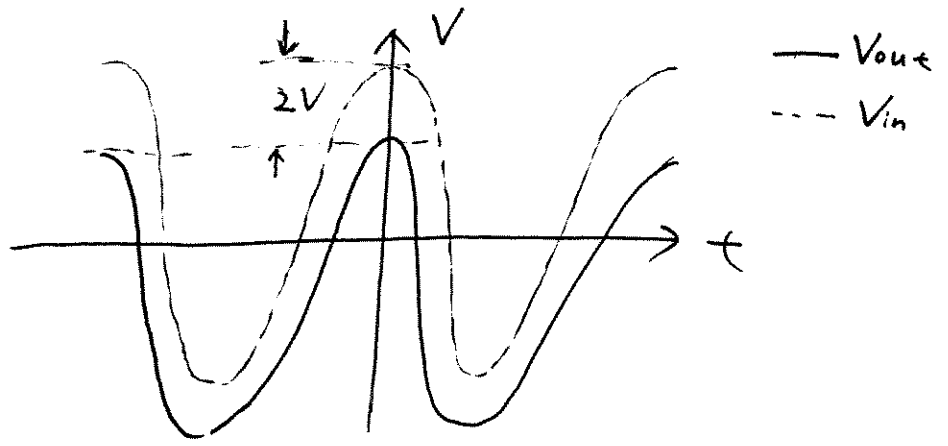


e)

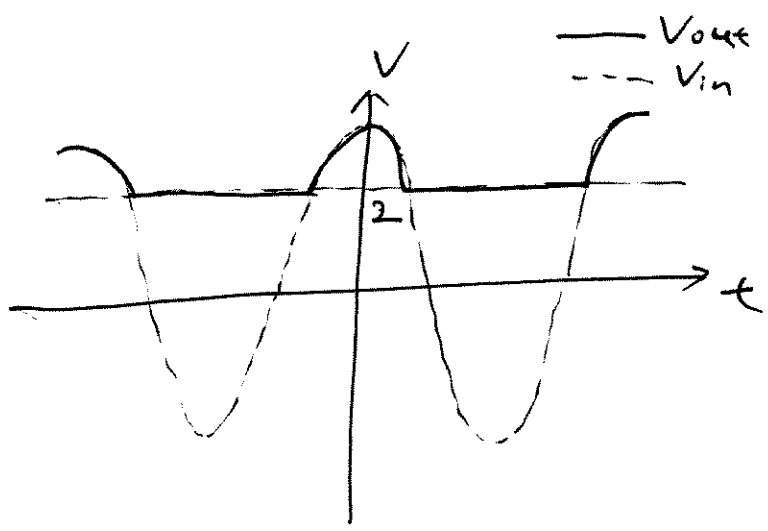


(15) a)

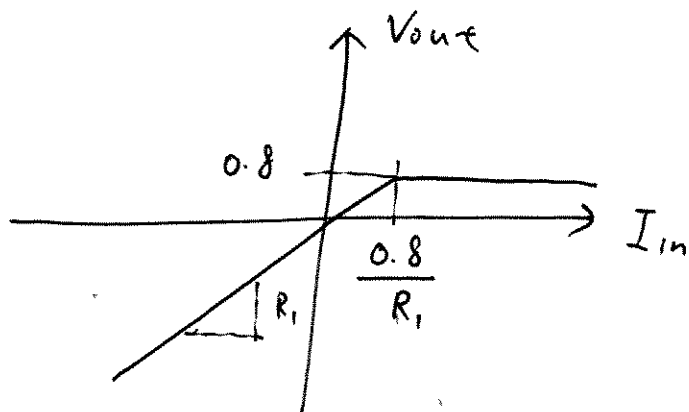


b)

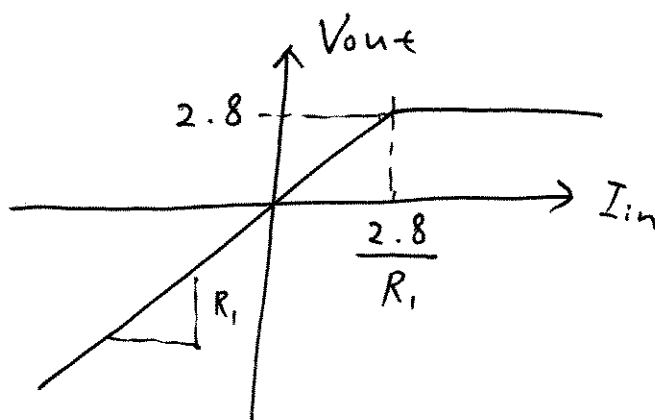


c)

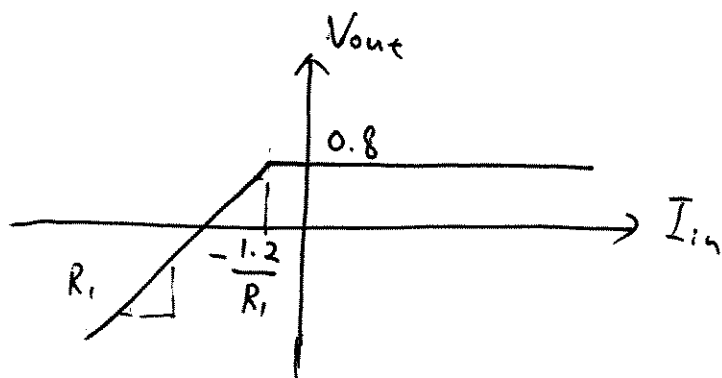


d)

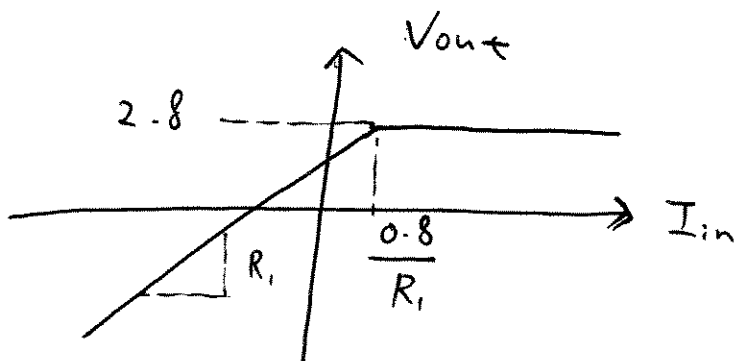


16 a)

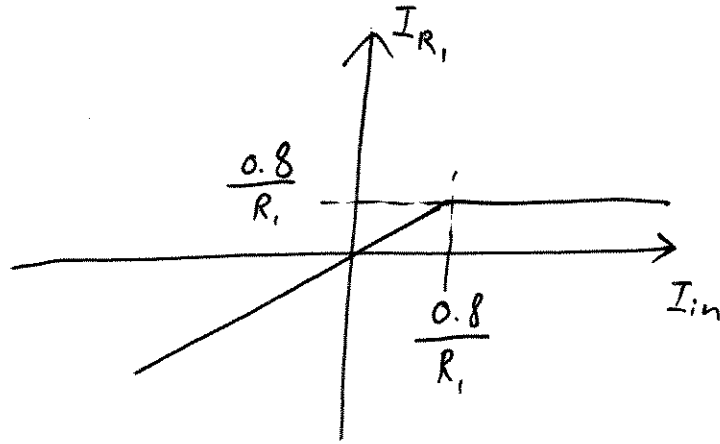


b)

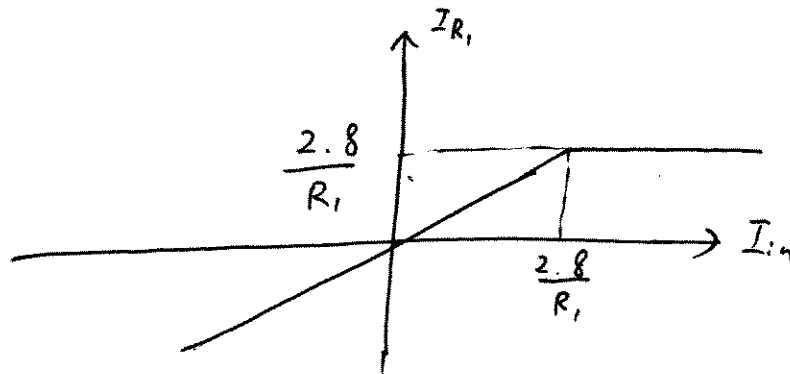

c)

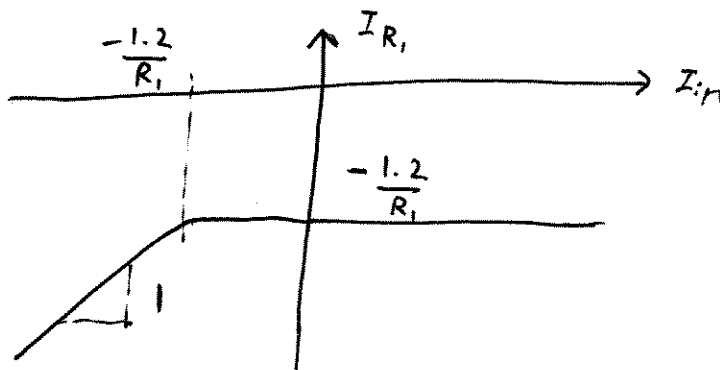


d)

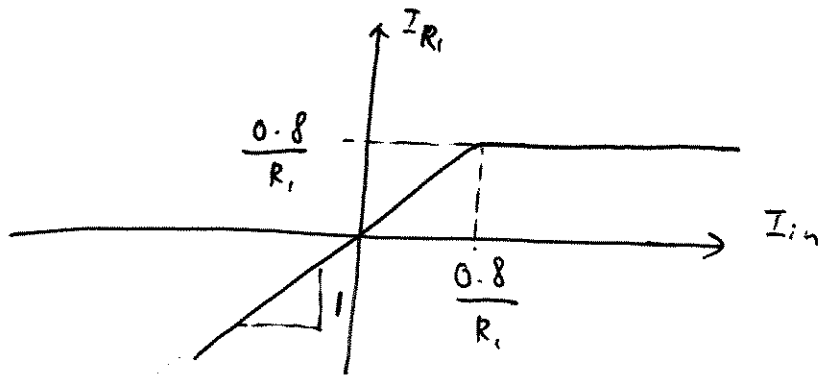





(17) a)

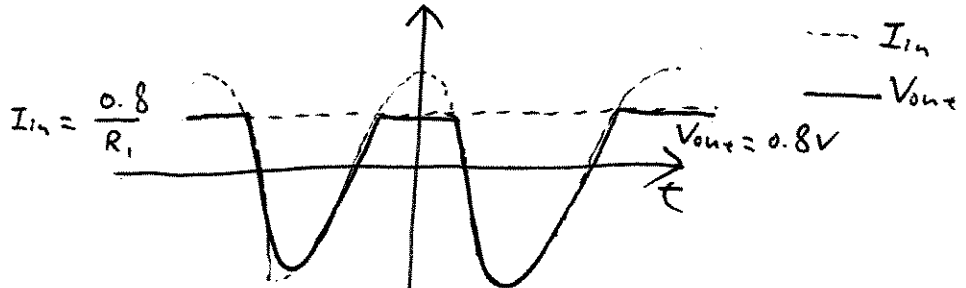


b)

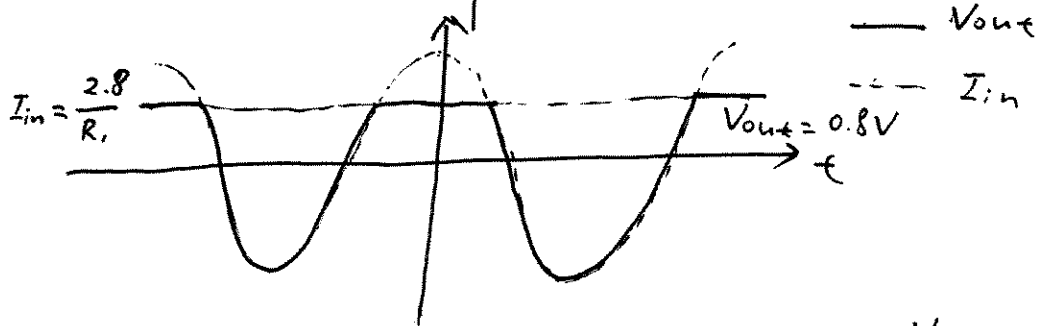

c)

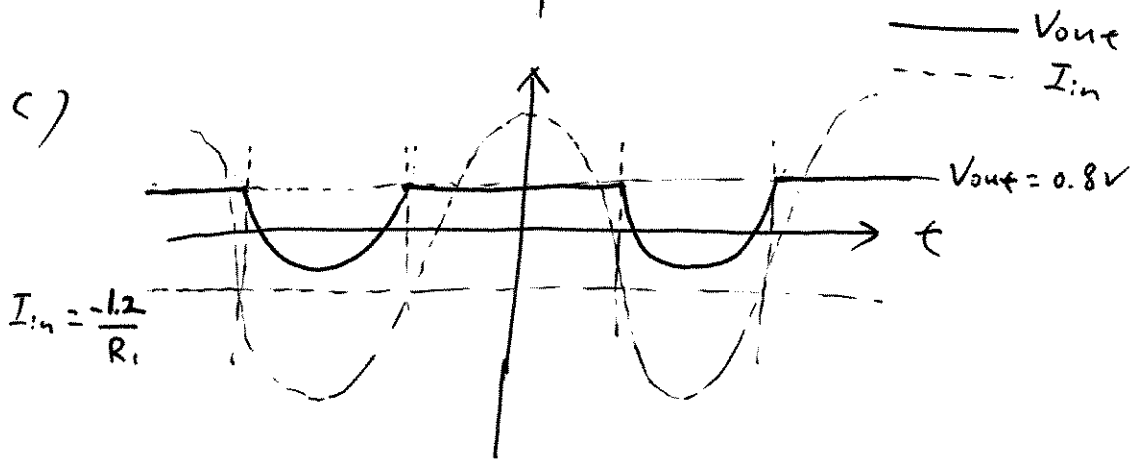


d)

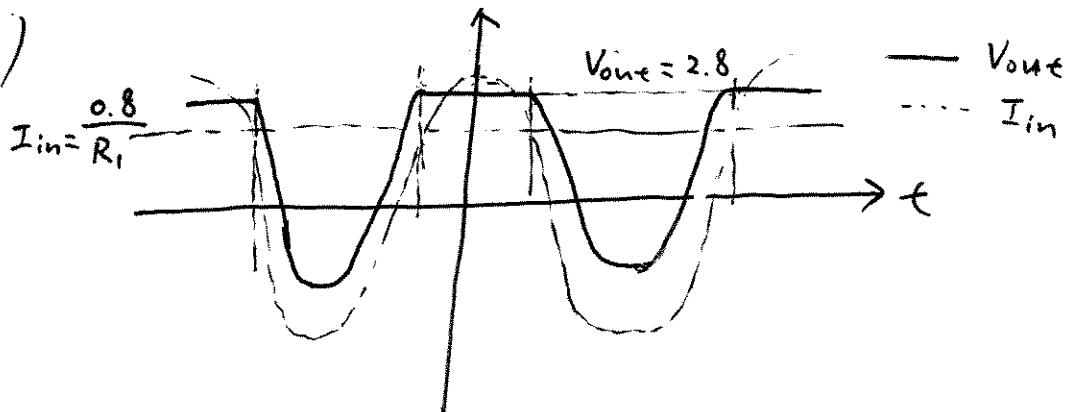


18


a)

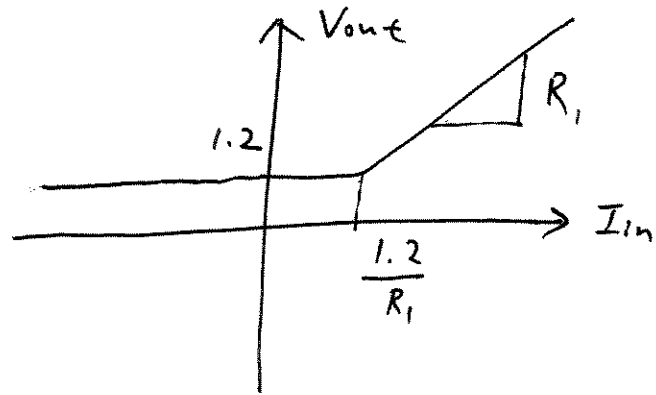


b)

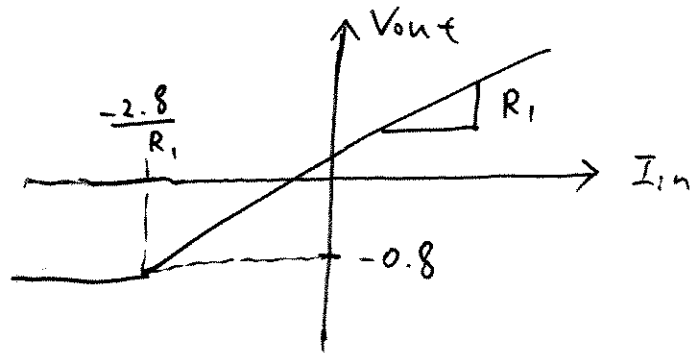


c)

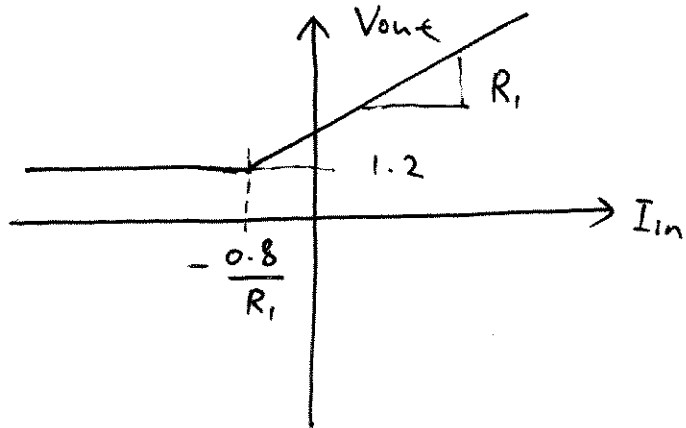


(19) a)

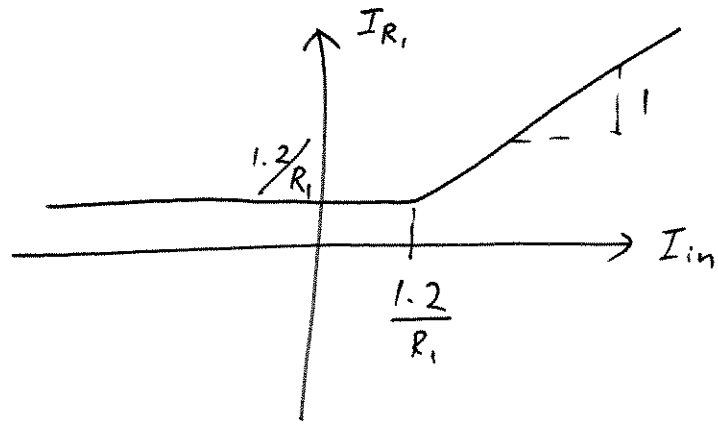

b)

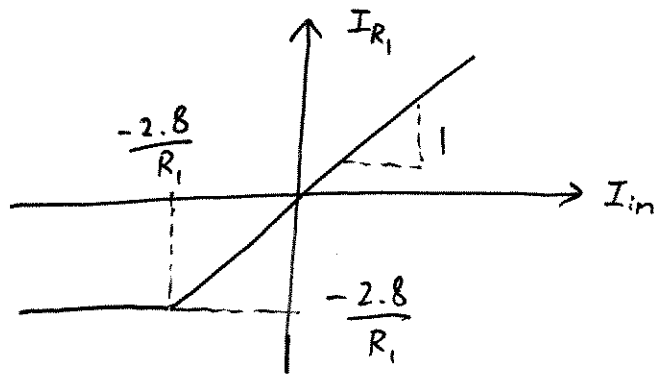


c)

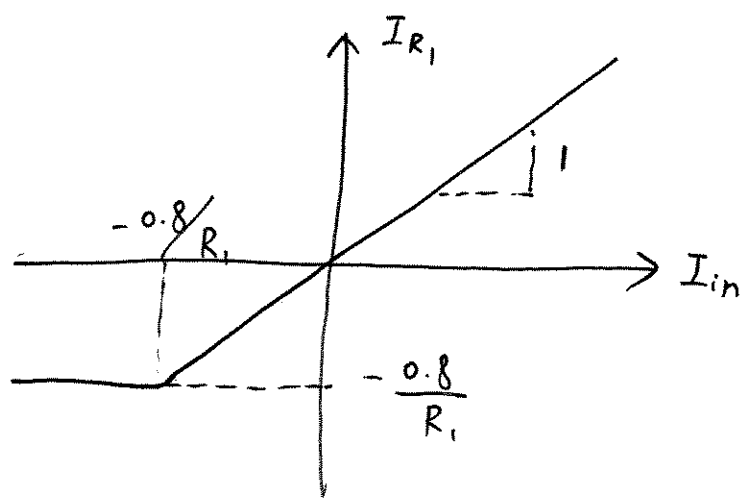


20


a)

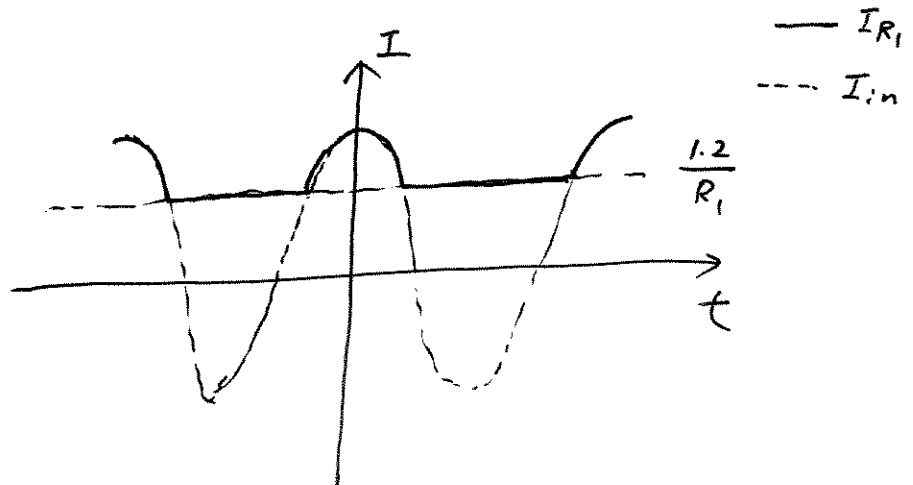


b)

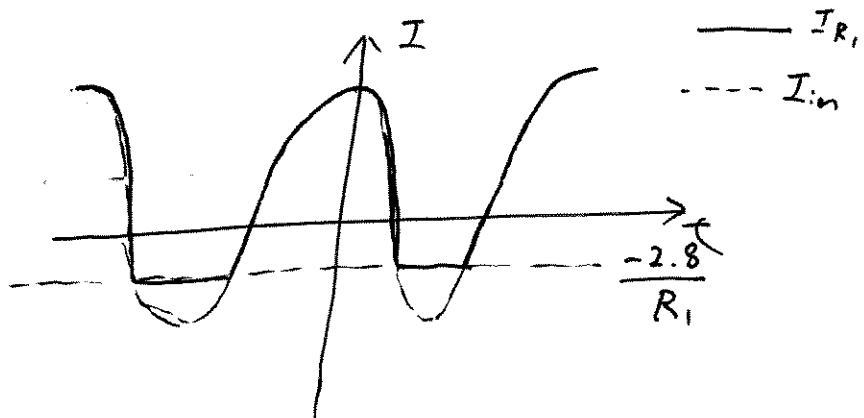


c)

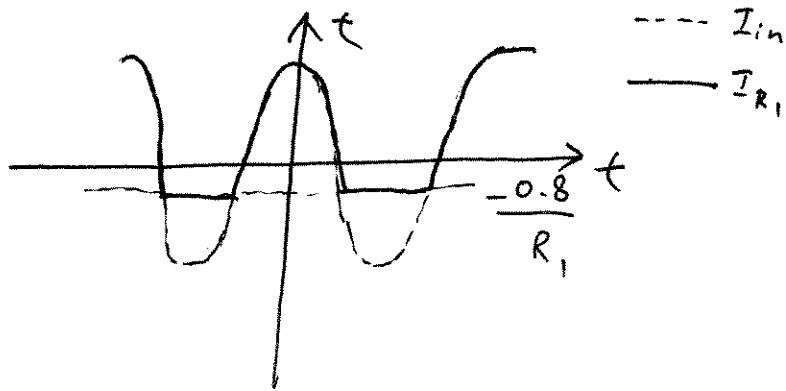


(21) a)

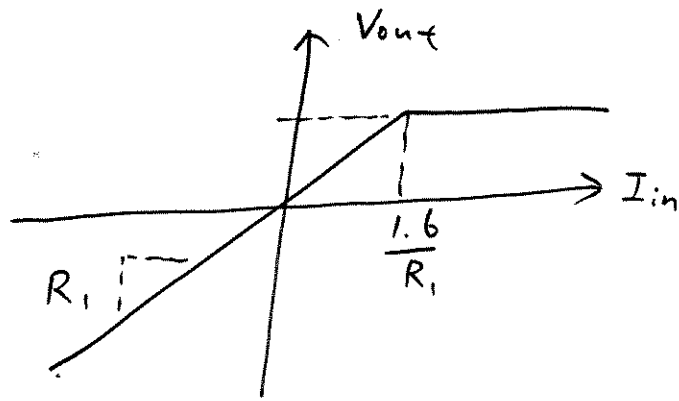


b)




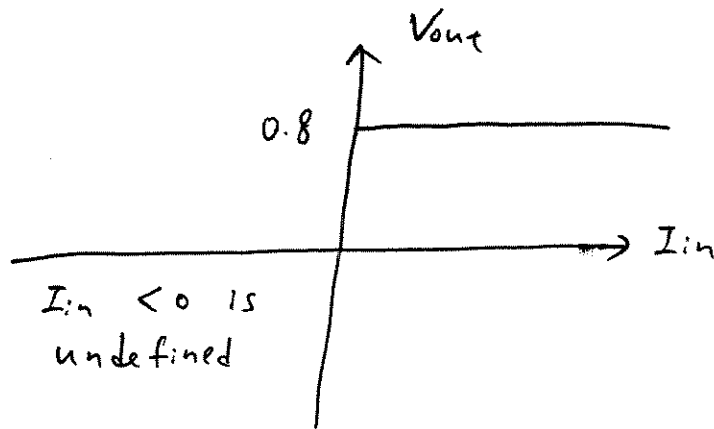


c)

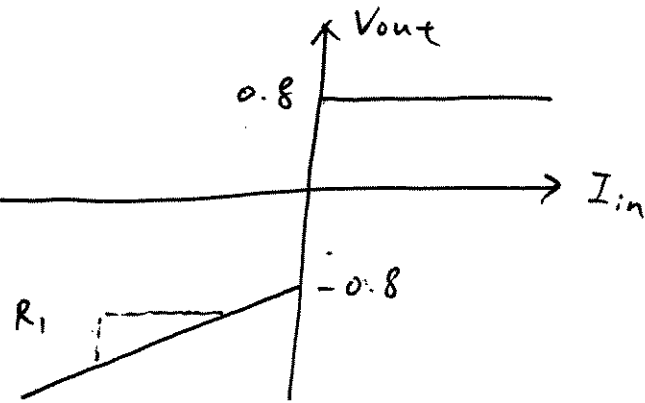


d)

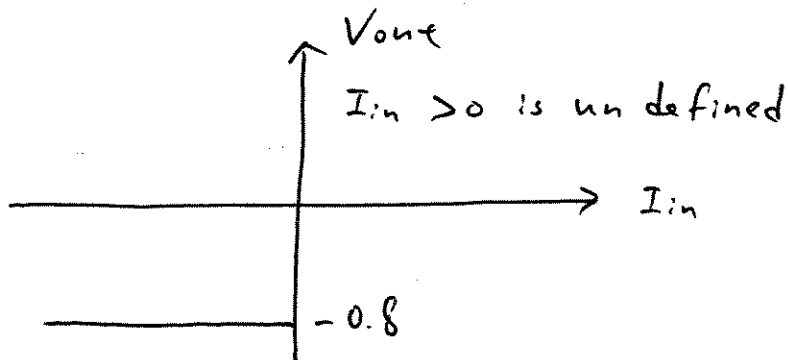

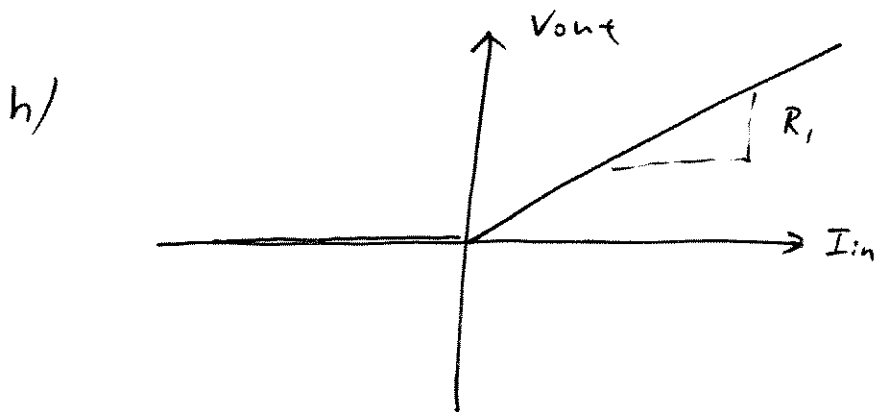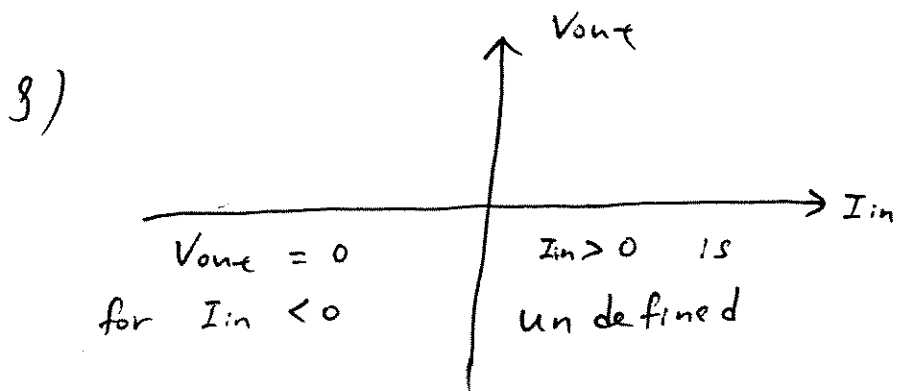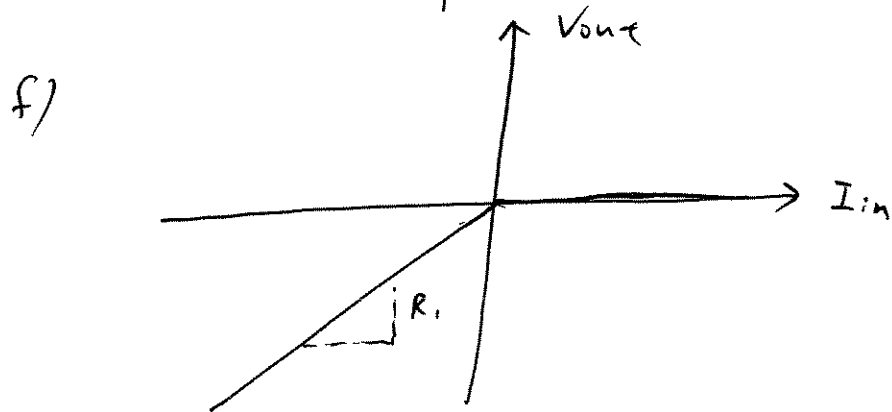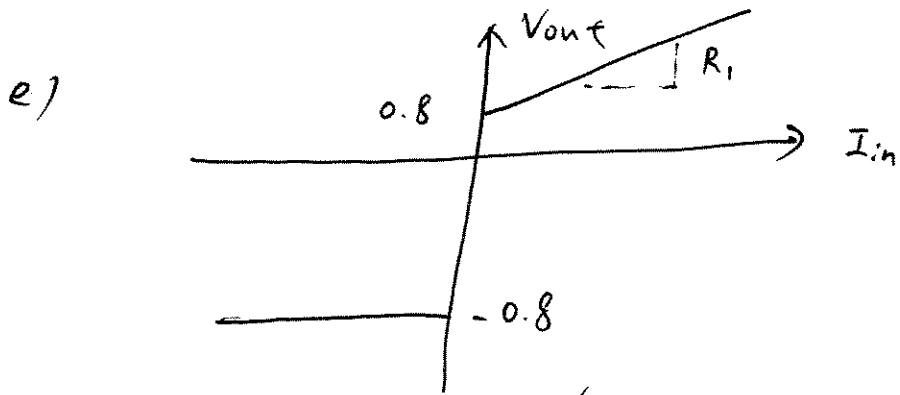


22


a)

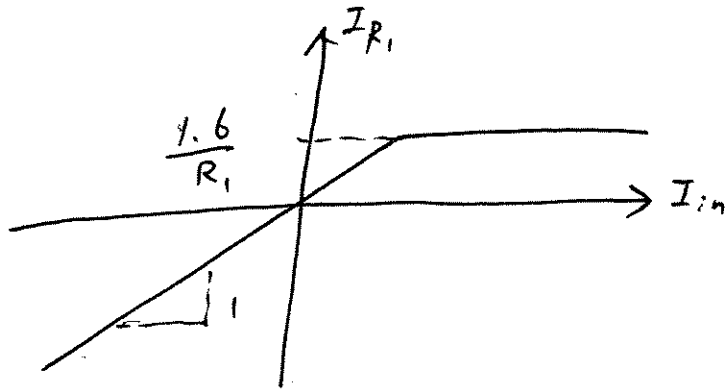


b)

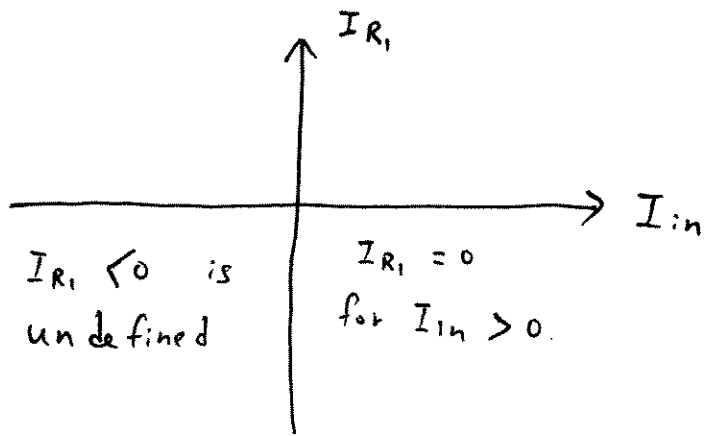


c)

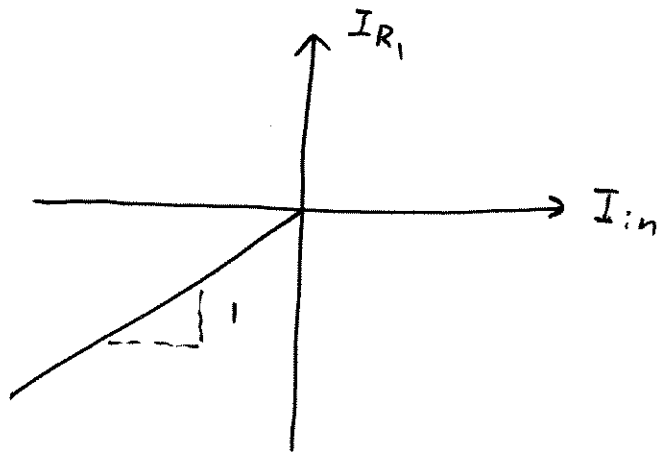


d)

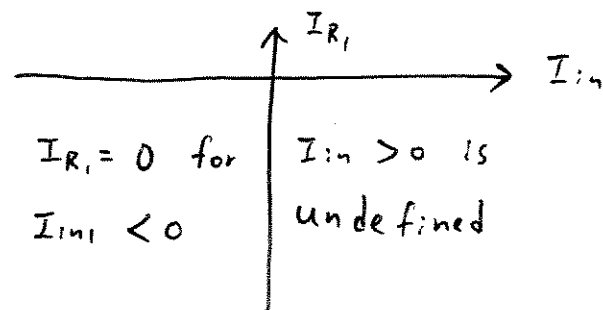


e)

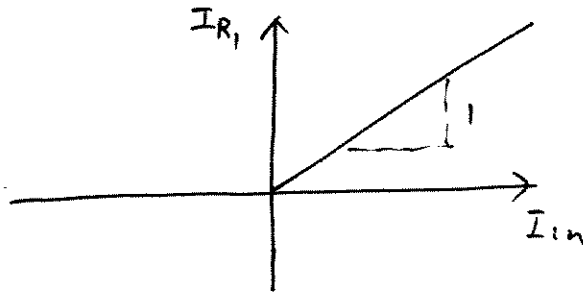


f)

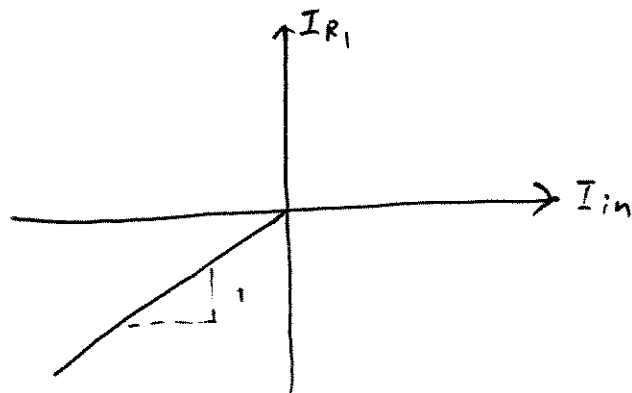

g)

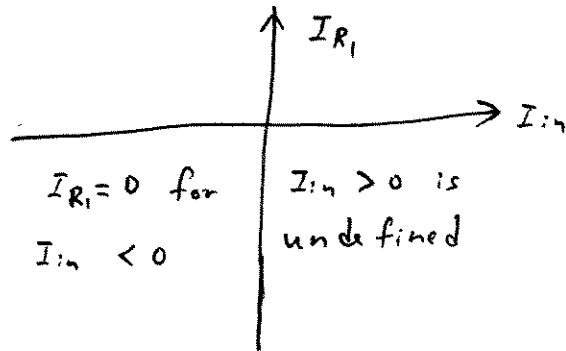


h)

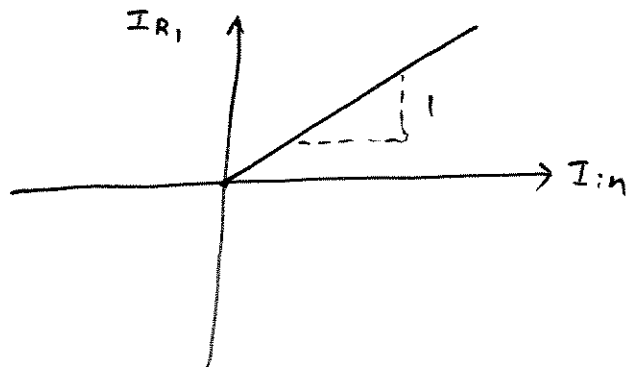




23 a)

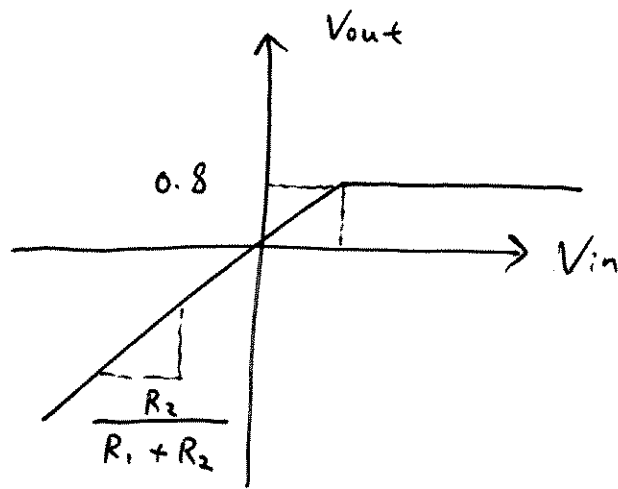

b)

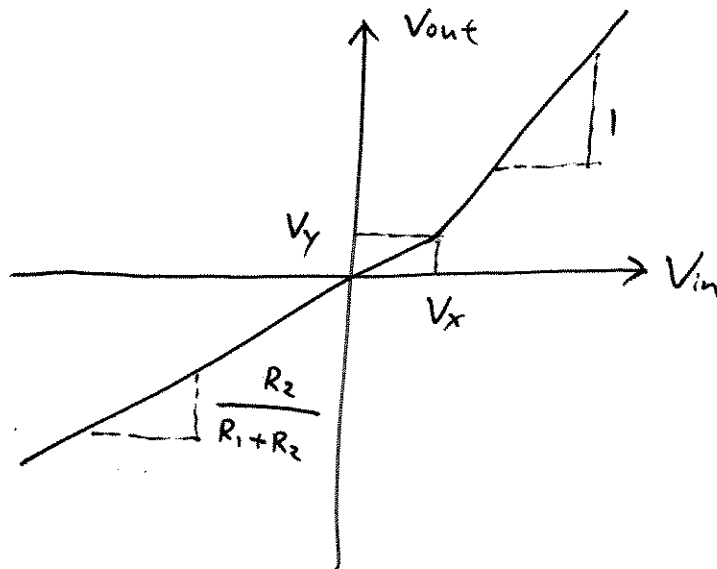


Note: at the turning point when  $D_1$  starts to conduct,  $V_x, V_y$  need to satisfy 2 conditions:

$$V_x - V_y = 0.8 \quad \text{--- (1)}$$


$$V_y = \frac{R_2}{R_1 + R_2} V_x \quad \text{--- (2)}$$

24

a)

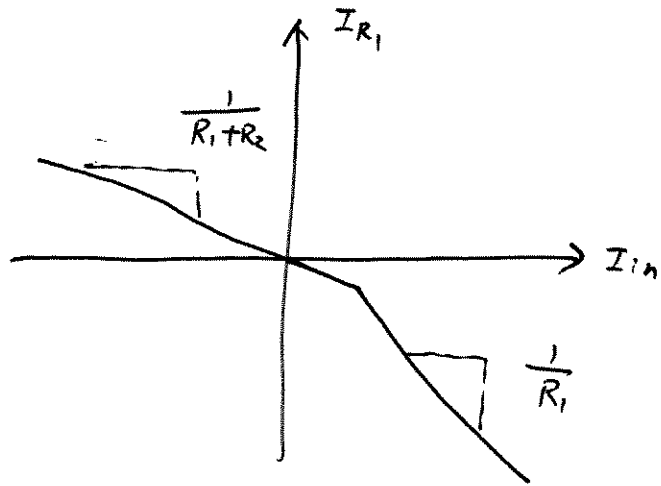


b)

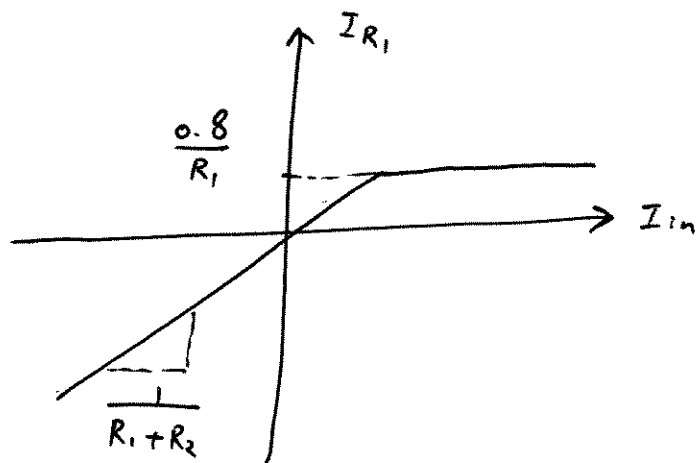


25


a)

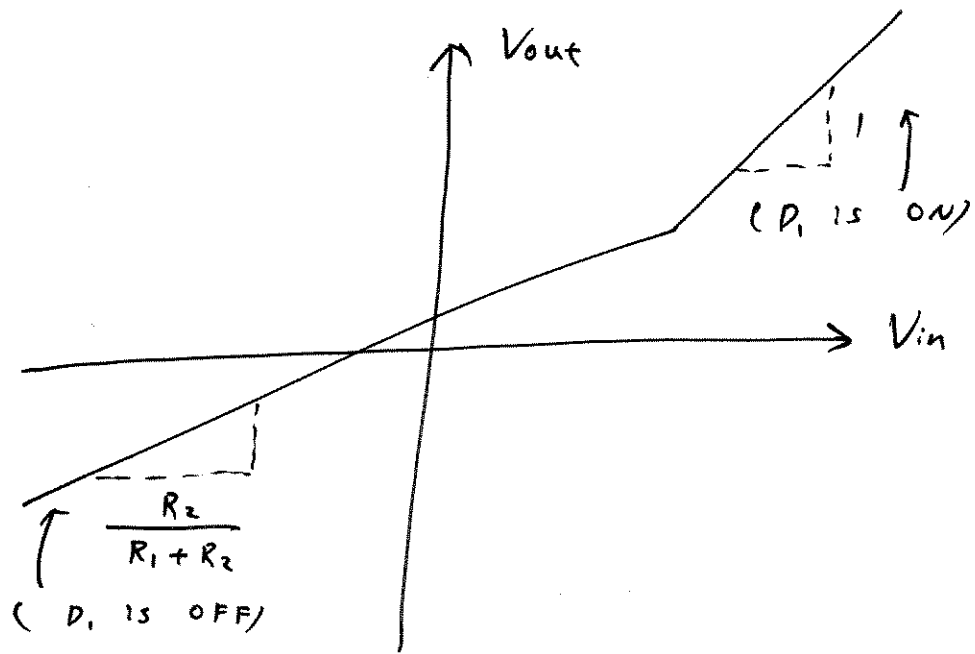


b)

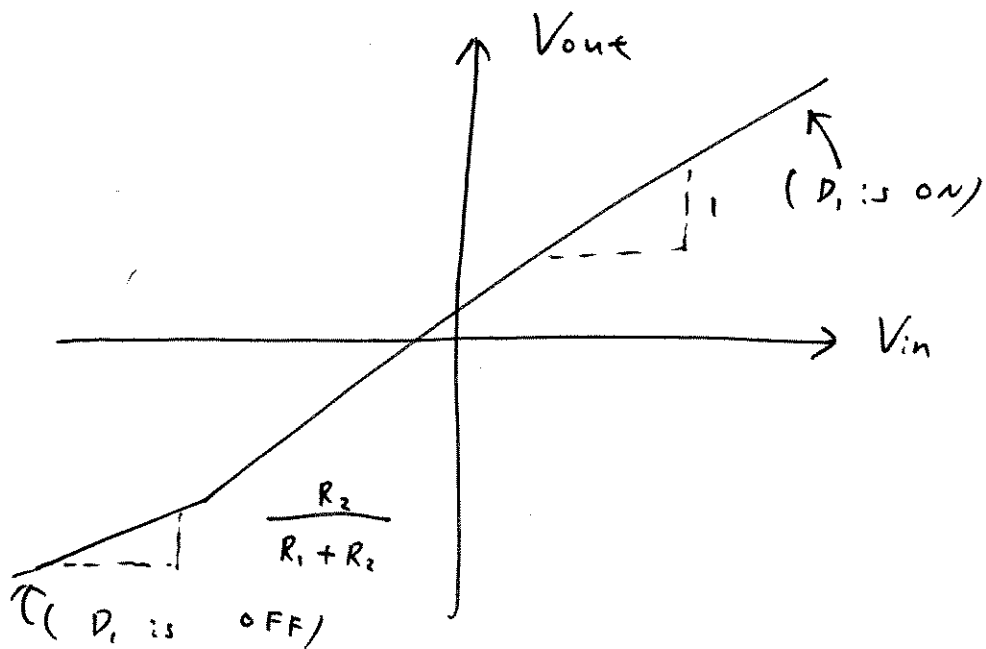


c)

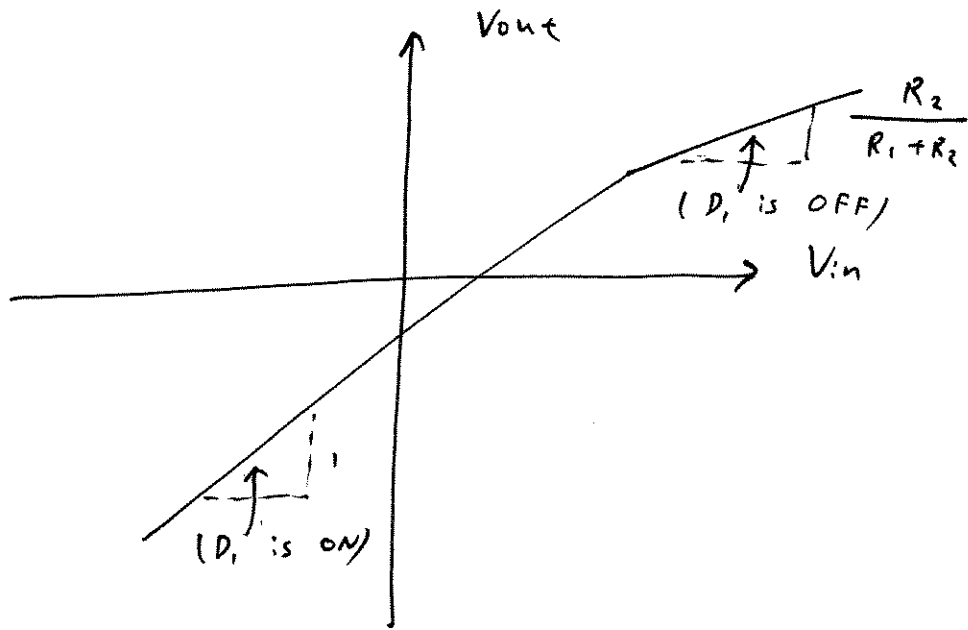


d)

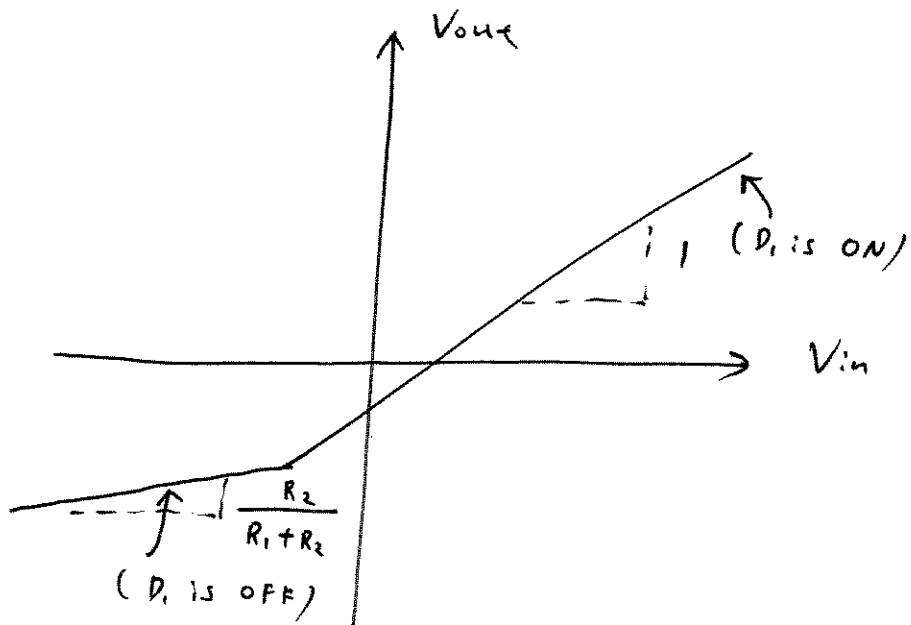


(26) a)

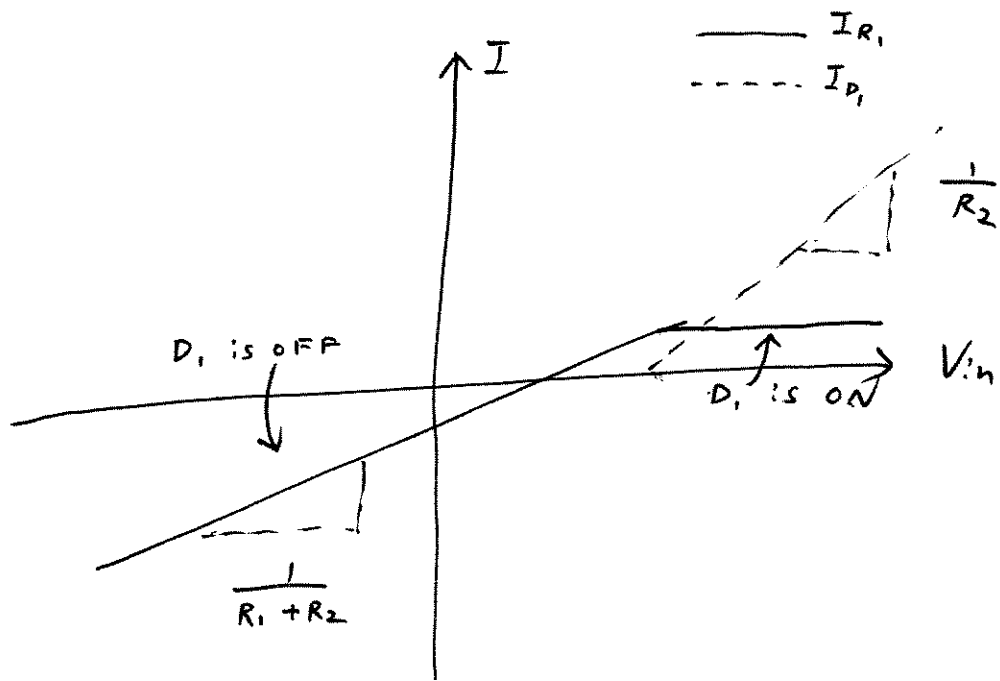


b)

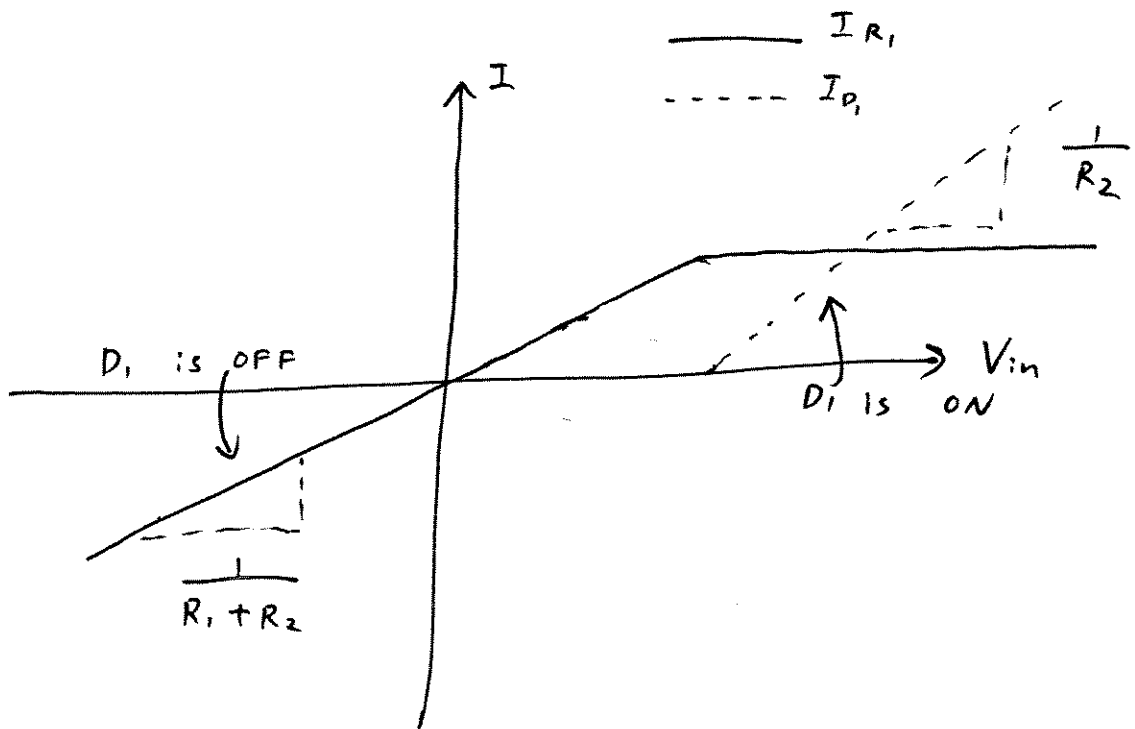

c/

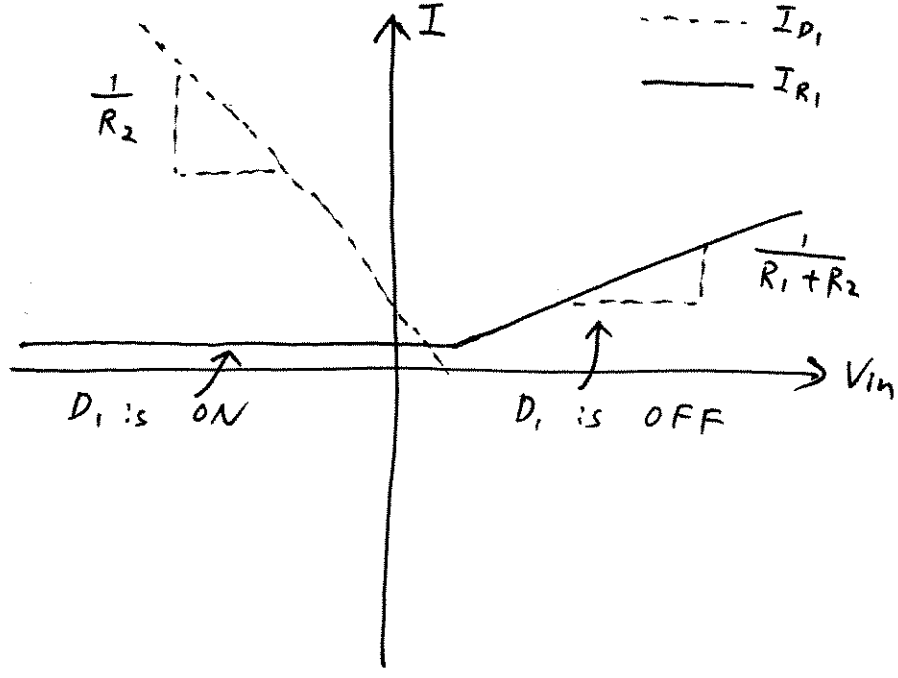


d/

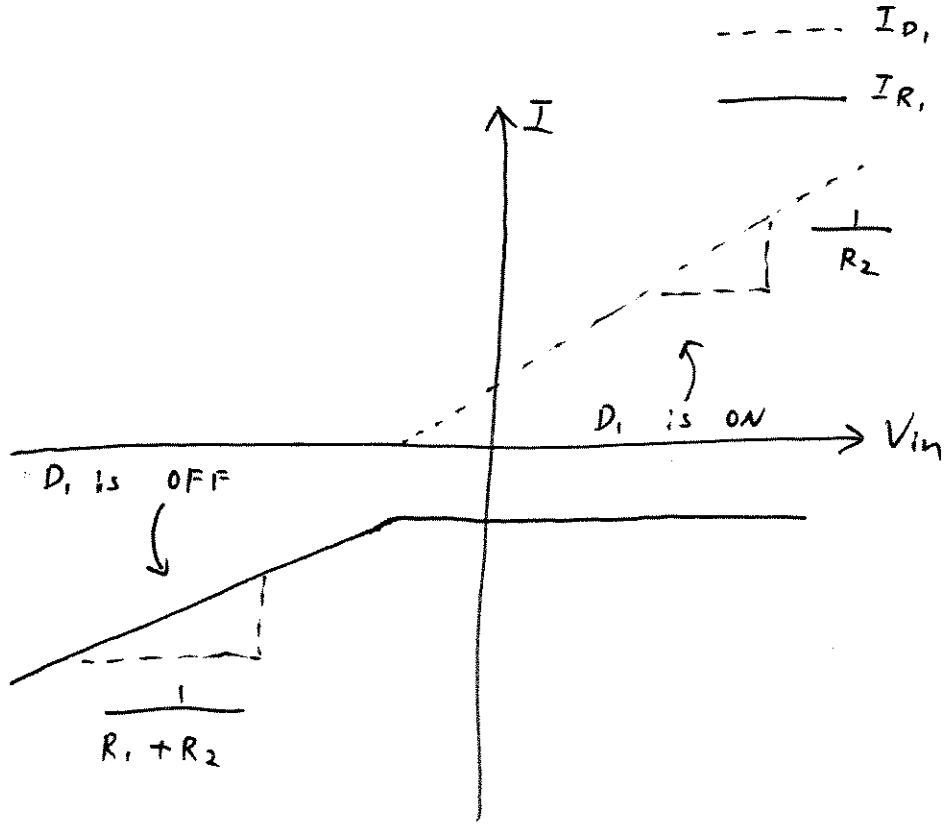


(27)


a)

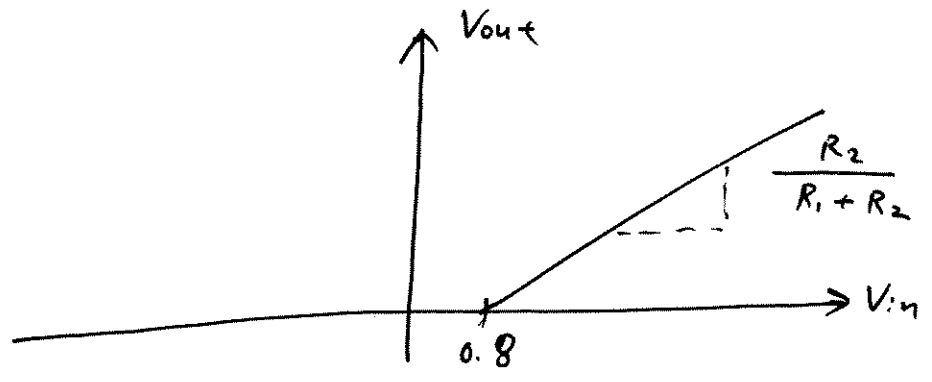


b)

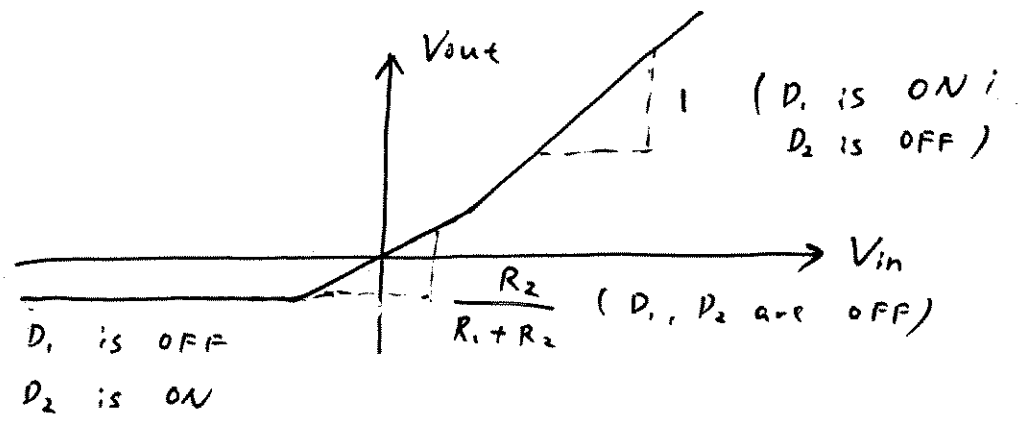


c)

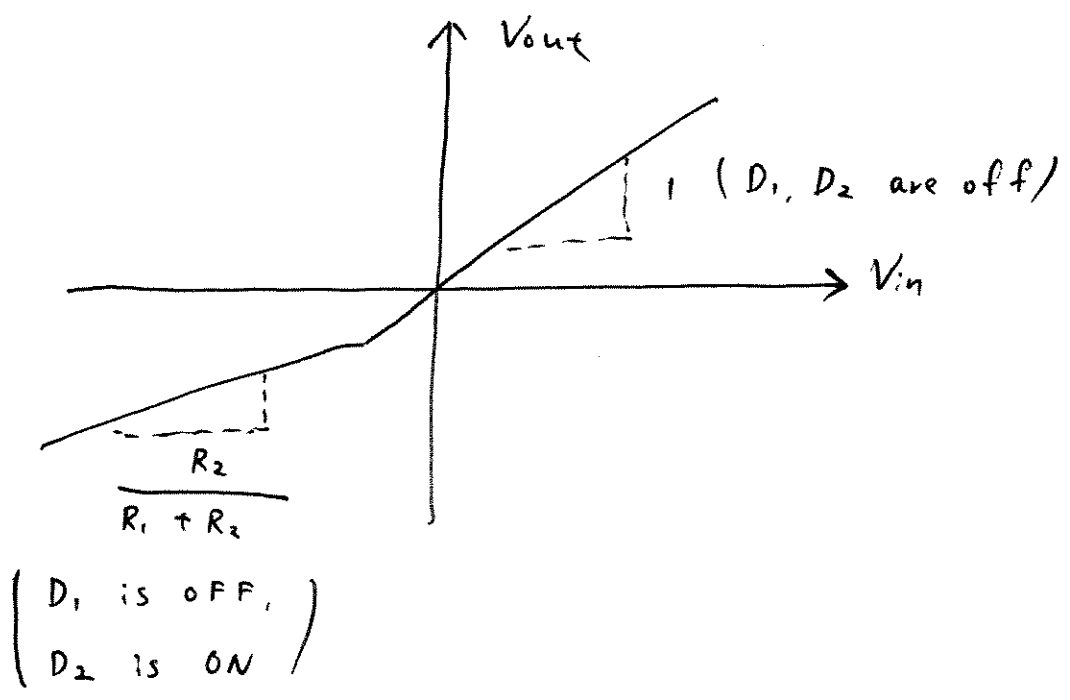

d/

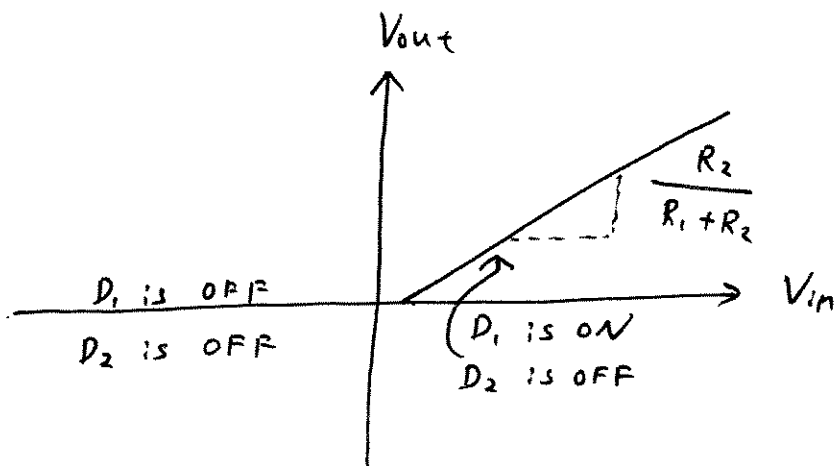


e/

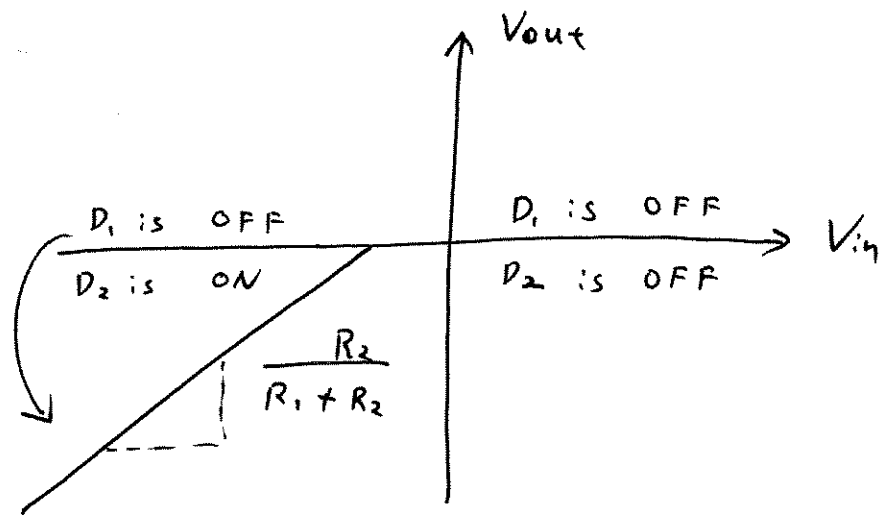




28


a)

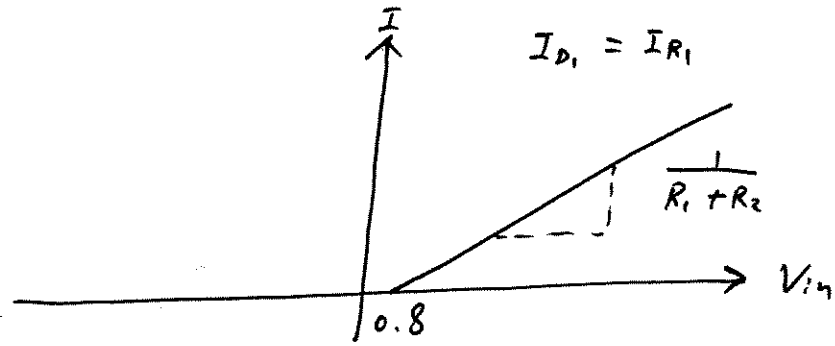


b)

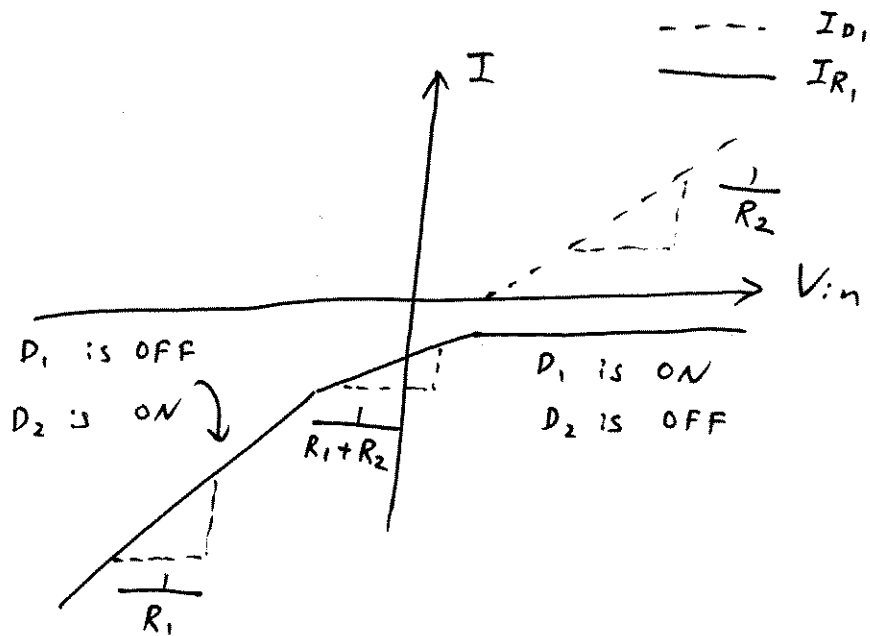


c)

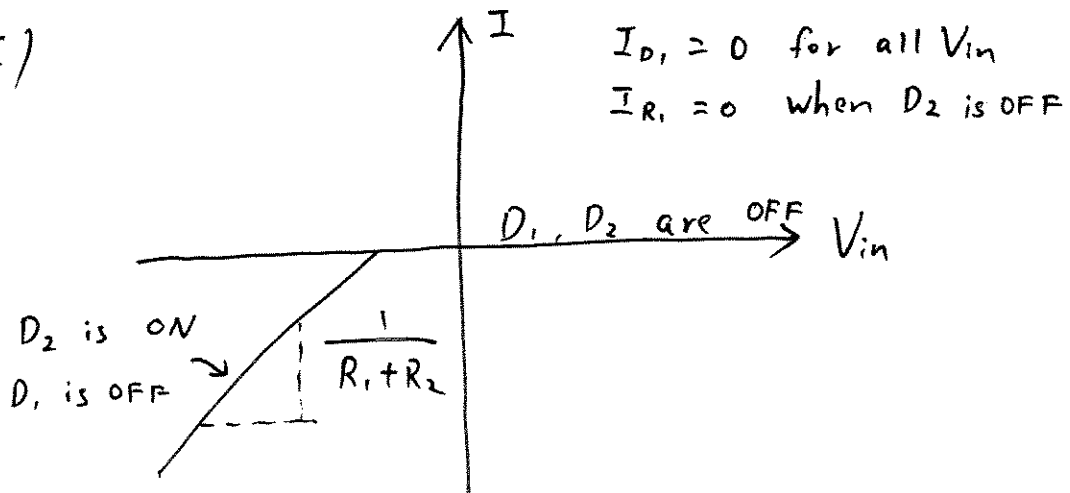

d)

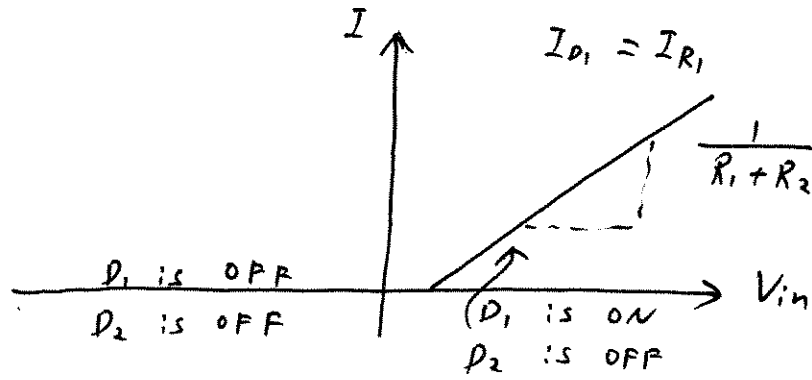


e)

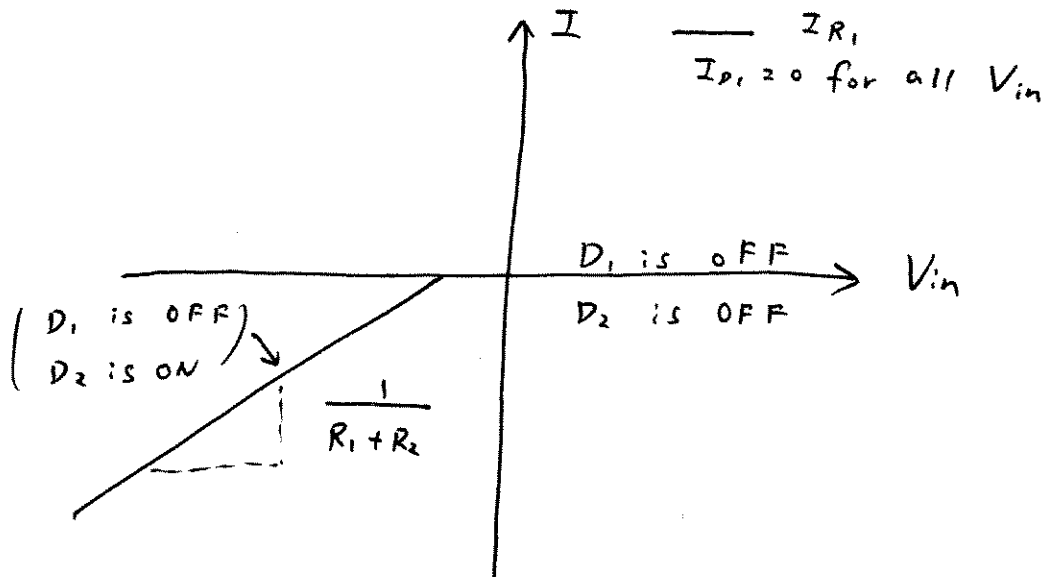


29


a)

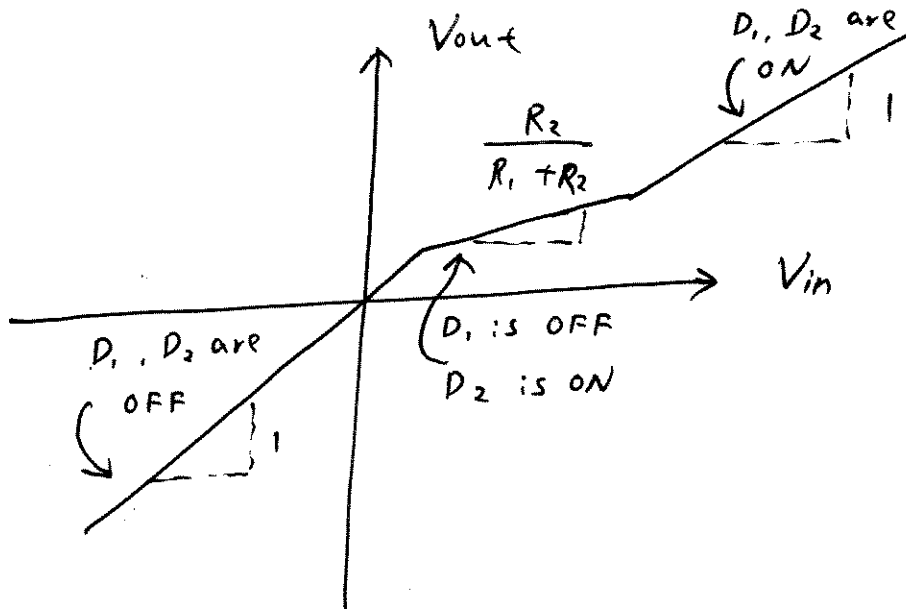


b)

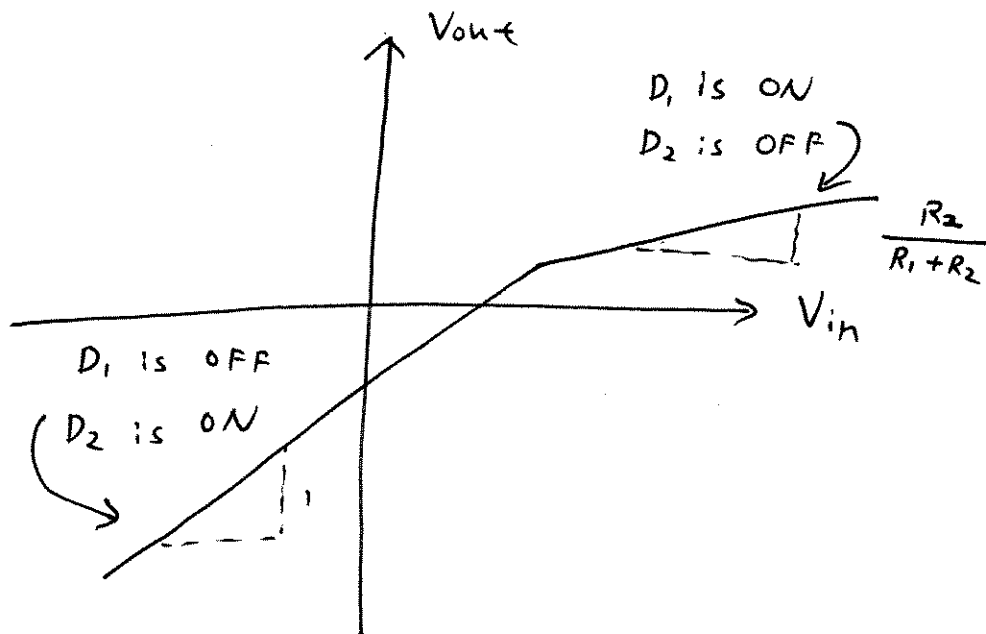

c)

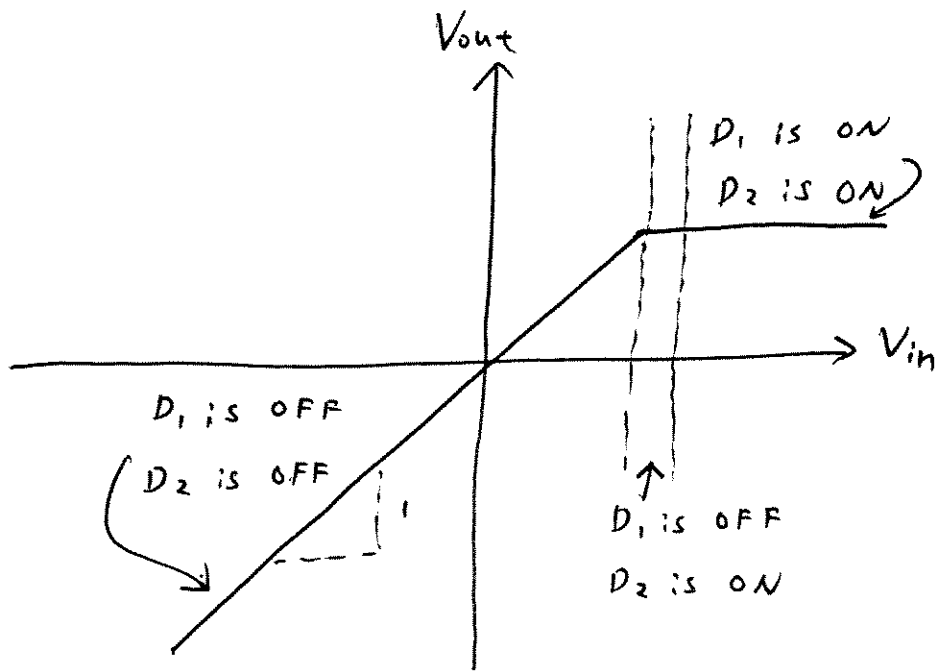


d)

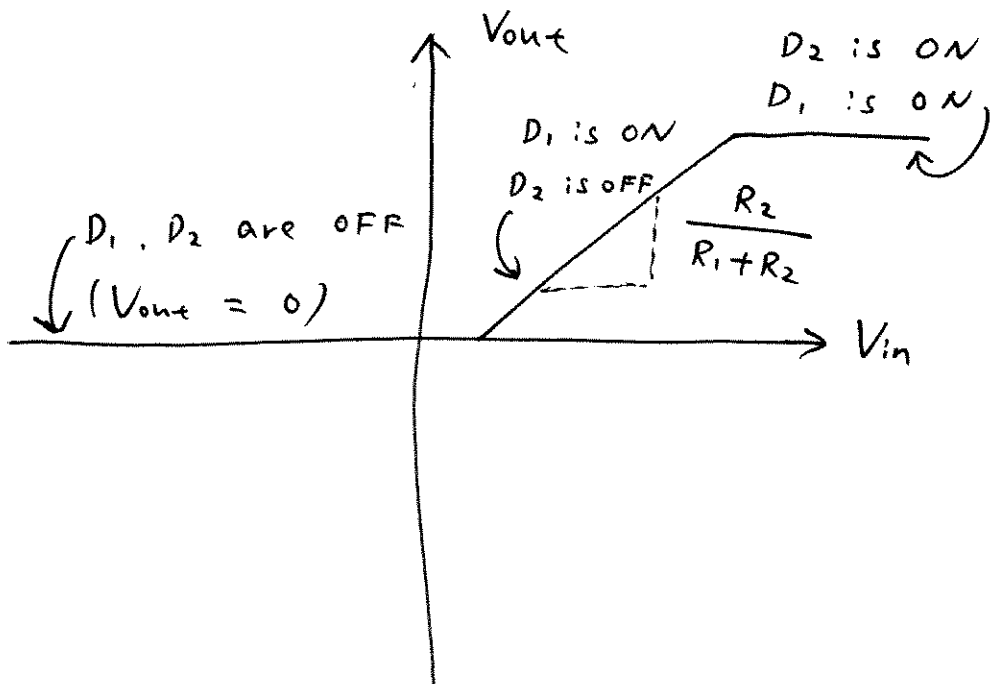


30


a)

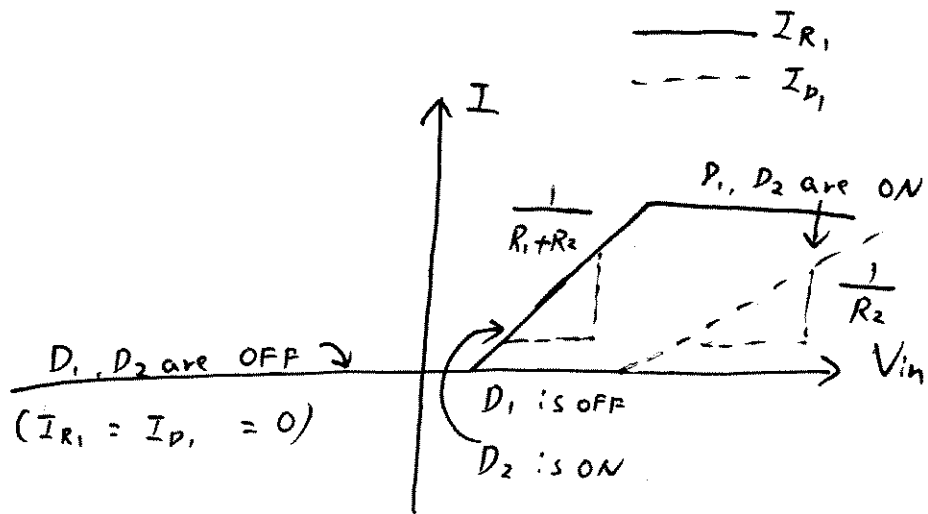


b)

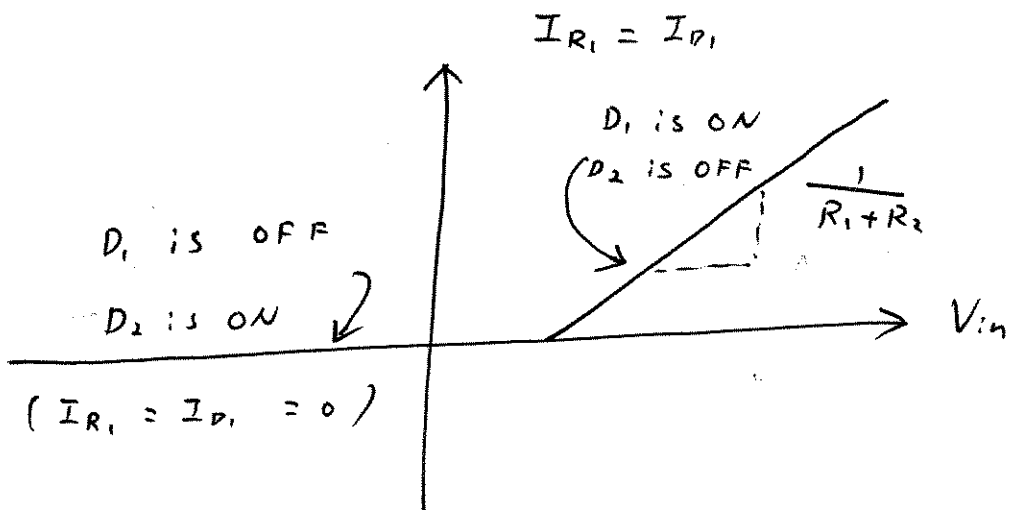

c)

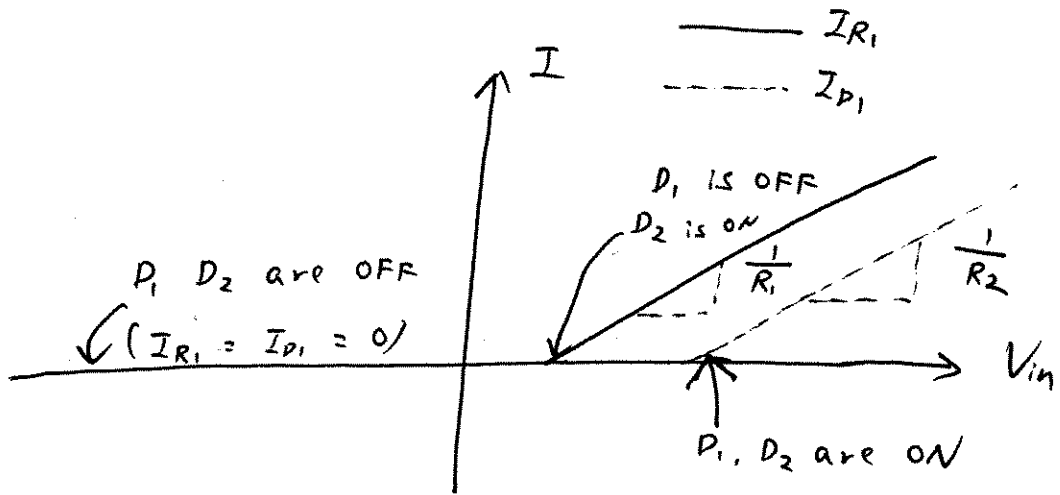

d)

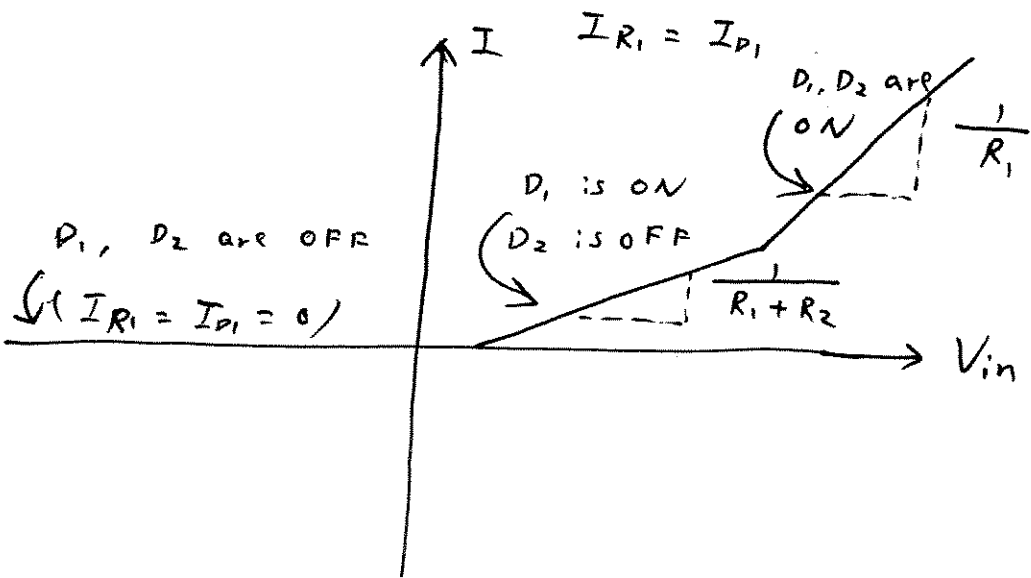

③1 a) when  $V_{in}$  changes from  $+2.4V$  to  $+2.5V$ ,  
 $D_1$  is ON throughout the change.

$$\therefore V_{out} \approx V_{in} - 0.8V,$$

i.e.,  $V_{out}$  changes from  $+1.6V$  to  $+1.7V$ .

b) when  $V_{in}$  changes from  $+2.4V$  to  $+2.5V$ ,  
 $D_1$  and  $D_2$  are both ON.

$$\therefore V_{out} = V_{in} - V_{ON, D_1},$$

i.e.,  $V_{out}$  changes from  $+1.6V$  to  $+1.7V$ .

c) when  $V_{in}$  changes from  $+2.4V$  to  $+2.5V$ ,  
 $D_1$  and  $D_2$  are both ON.

$$V_{out} = V_{ON, D_2},$$

i.e.,  $V_{out}$  stays at  $+0.8V$ .

d) when  $V_{in}$  changes from  $+2.4V$  to  $+2.5V$ ,

$D_2$  is ON.

$$\therefore V_{out} \approx V_{ON, D_2},$$

i.e.,  $V_{out}$  stays at  $+0.8V$

$$\begin{aligned}
 \textcircled{32} \quad a) \quad V_{out} &= i \times R_1 \\
 &= 0.1 \text{ mA} \times 1 \text{ k}\Omega \\
 &= 0.1 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 b) \quad r_{d1} = r_{d2} &= \frac{26 \text{ mV}}{3 \text{ mA}} \quad (\text{Eq. 3.58}) \\
 &\approx 8.67 \Omega.
 \end{aligned}$$

$$\begin{aligned}
 V_{out} &= i \times (R_1 + r_{d2}) \\
 &= 0.1 \text{ mA} (1.00867 \text{ k}\Omega) \\
 &\approx 1.009 \times 10^{-1} \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 c) \quad V_{out} &= i \times r_{d2} \\
 &= 0.1 \text{ mA} \times 8.67 \quad (\text{from (b)}) \\
 &= 0.867 \text{ mV}
 \end{aligned}$$

$$\begin{aligned}
 d) \quad V_{out} &= i \times (R_2 \parallel r_{d2}) \\
 &\approx i \times r_{d2} \quad (\because R_2 \gg r_{d2}) \\
 &= 0.867 \text{ mV}
 \end{aligned}$$




$$\textcircled{33} \text{ a) } \quad i_{r_1} = i_{in} \\ = 0.1 \text{ mA}$$

$$\text{b) } \quad i_{r_1} = i_{in} \\ = 0.1 \text{ mA}$$


$$\text{c) } \quad i_{r_1} = i_{in} \\ = 0.1 \text{ mA}$$

$$\text{d) } \quad i_{r_1} = i_{in} \\ = 0.1 \text{ mA}$$

34

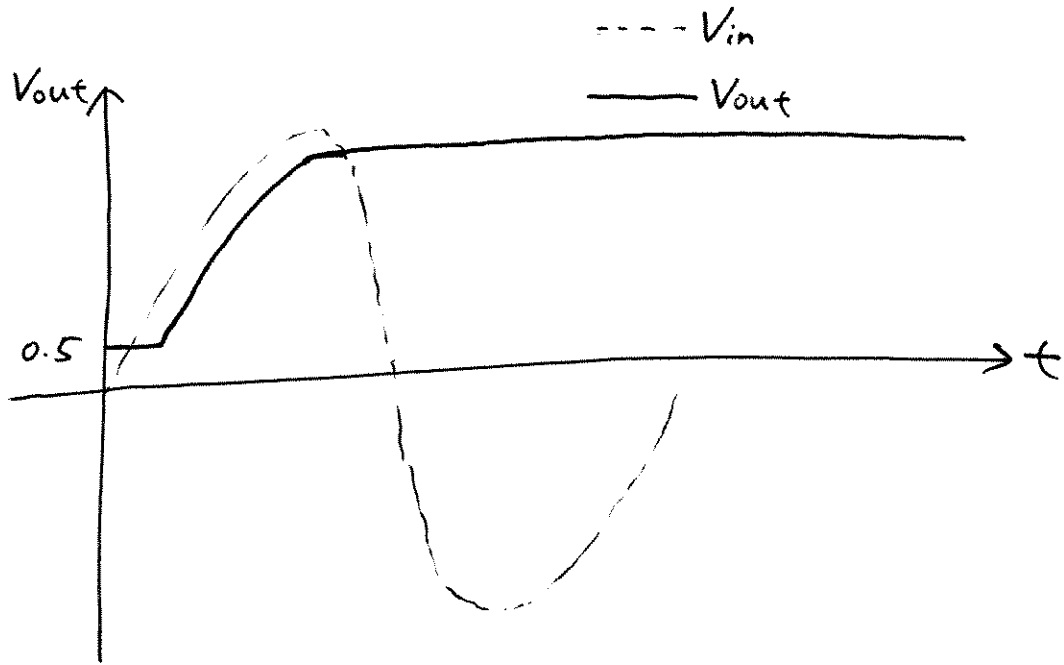

35

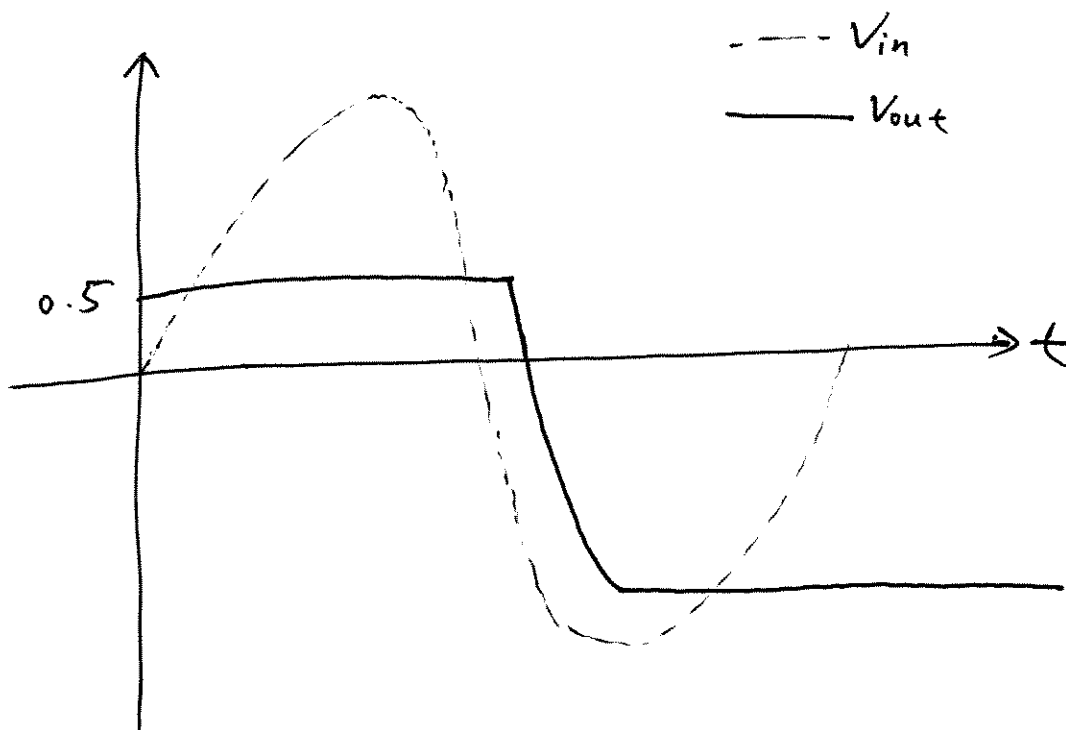

③⑥ From eq. (3.80),

$$\text{Ripple amplitude, } V_R \approx \frac{V_P - V_{D,on}}{R_L C f_{in}}$$

$$= \frac{3.5 - 0.8}{10 \cdot 1000 \times 10^{-6} \times 60}$$

$$= 0.45 \text{ V}$$

(37)

From Eq. (3.83),

$$V_R = \frac{I_L}{C f_{in}}$$

$$\therefore V_R \leq 300 \text{ mV}$$


$$\frac{I_L}{C f_{in}} \leq 300 \text{ mV}$$

$$\therefore C \geq \frac{I_L}{f_{in} \times 0.3}$$

$$C \geq \frac{0.5}{60 \times 0.3}$$


$$\text{i.e. } C \geq 0.278 \text{ F}$$

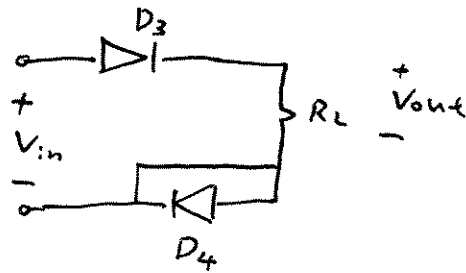③⑧ In the positive half of the cycle, when  $V_{in+} > V_{in-}$ , the circuit is operating as :



$D_4$  is shunted, and  $D_3 - R_L$  forms a half-wave rectifier.

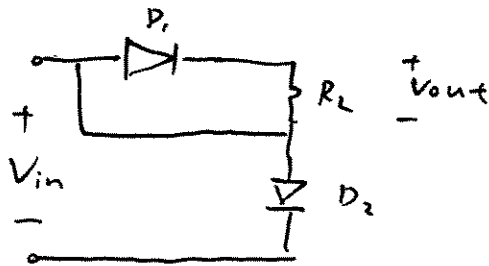In the negative half of the cycle, when  $V_{in-} > V_{in+}$ , the circuit becomes:




$D_1$  is shunted and is off.

Thus,  $V_{out} = 0$ .

Shunting the resistor load with a capacitor has no effect in the above two cases.


39

(i)

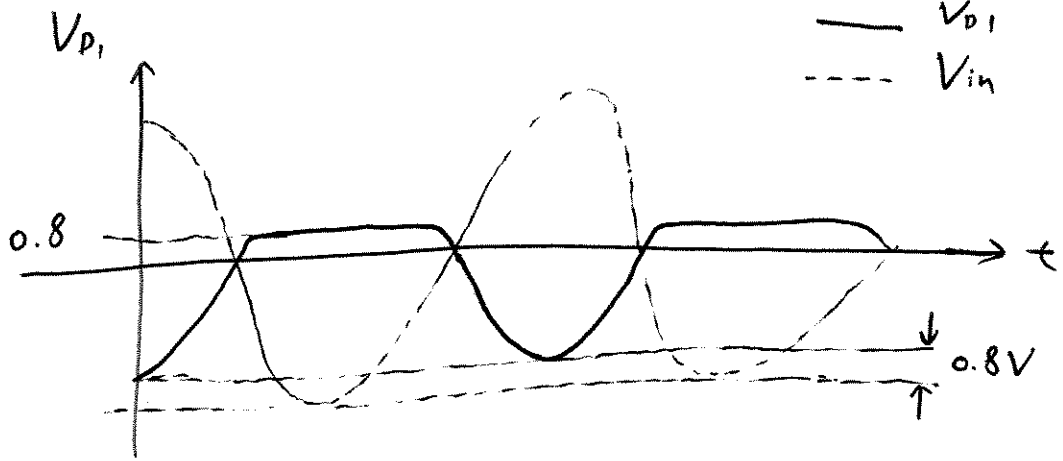


(ii)  $V_{D2}$  is same as  $V_{D1}$  (above)

(iii)

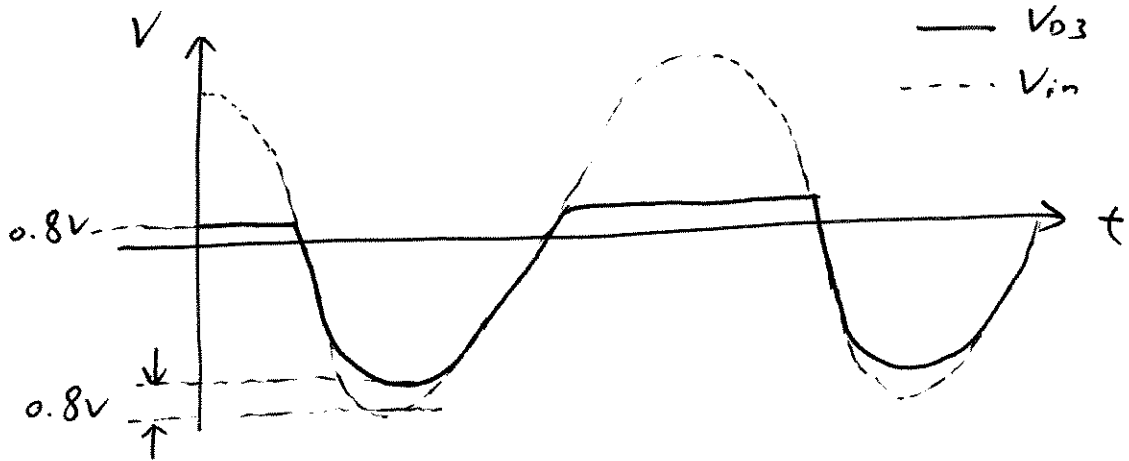

(iv)

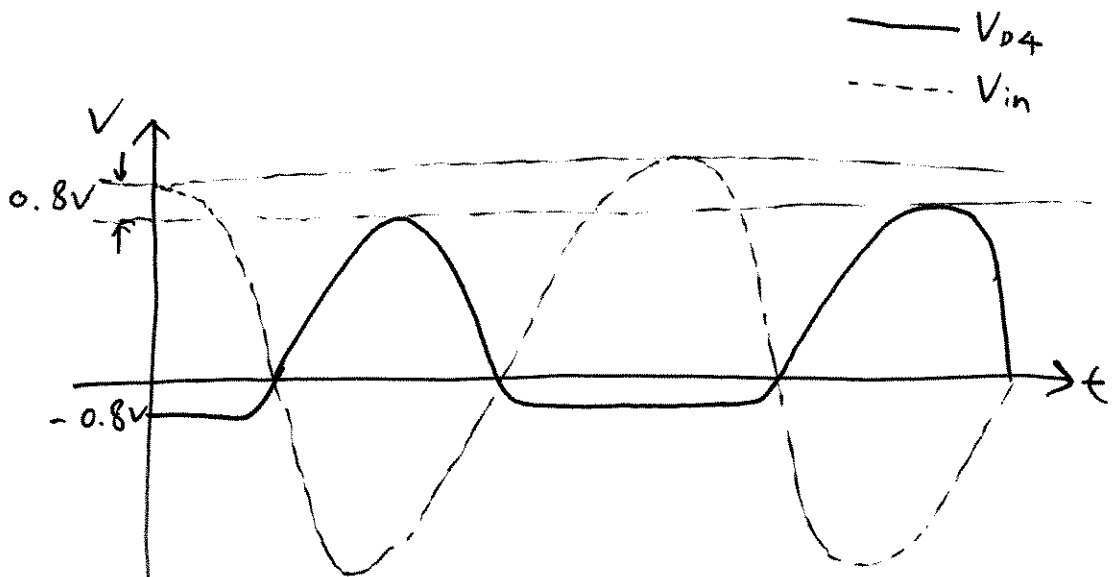

④ - This circuit would fail to function as a full-wave rectifier.

- It only rectifies for  $V_{in-} > V_{in+}$   
(Current flows through  $D_1$  and  $D_2$ )

- But for  $V_{in+} > V_{in-}$ , there is no conduction path through the load.


- Thus, this circuit behave like a half-wave rectifier



④ Using Eq. (3.94),

$$\begin{aligned}V_R &\approx \frac{1}{2} \cdot \frac{V_P - 2 V_{P,ON}}{R_L C_1 f_{in}} \\&= \frac{1}{2} \cdot \frac{3 - 2 \times 0.8}{30 \times 1000 \times 10^{-6} \times 60} \\&= 0.389V\end{aligned}$$


(42)

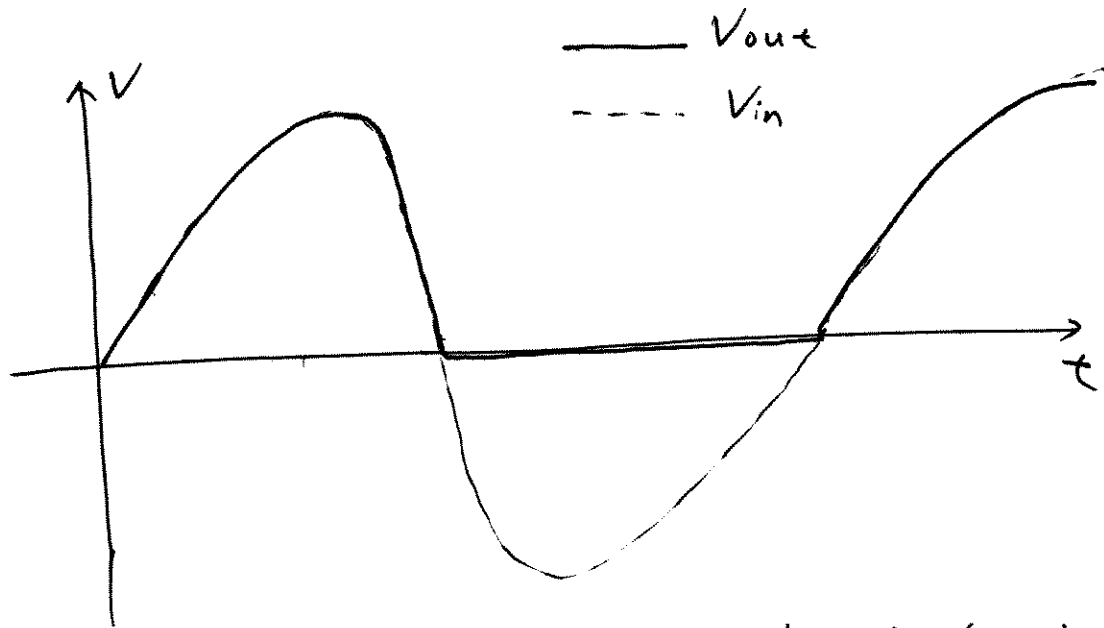

- With the two negative terminals shorted together, the circuit behaves like a half-wave rectifier.
- When  $V_{in+} > V_{in-}$ ,  $D_3$  and  $D_4$  conduct as usual. There will be an additional path that bypasses  $D_4$ , since  $V_{in-}$  and  $V_{out-}$  are shorted. But this additional path causes no change to the  $V_{out}$  waveform.
- When  $V_{in-} > V_{in+}$ , both  $V_{out+}$  and  $V_{out-}$  track  $V_{in-}$ .  $V_{out+}$  connects to  $V_{in-}$  through  $D_1$ ;  $V_{out-}$  connects to  $V_{in-}$  through the additional shorted path.
- Thus  $(V_{out+}) - (V_{out-}) = 0$ , i.e.  $V_{out} = 0$

(43)

The circuit can be simplified as:

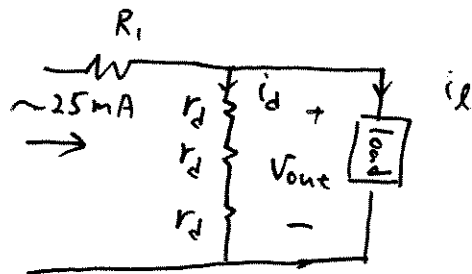

First, find  $r_d$ :

$$r_d = \frac{V_T}{I_D} \quad (\text{from eq. 3.60})$$

$$= \frac{26\text{mV}}{5\text{mA}}$$

$$= 5.2\ \Omega$$

Since  $i_L = +1\text{mA}$ .

$$i_d = -1\text{mA}.$$

$\therefore$  change in  $V_{out}$ ,

$$\text{ie. } V_{out} = (-1\text{mA})(3 \times 5.2)$$

$$= -15.6\text{mV}$$

(44)

a) From Eq. (3.94),

$$\begin{aligned} \text{the ripple amplitude, } V_R &= \frac{1}{2} \cdot \frac{V_p - 2V_{D, on}}{R_L C_1 f_n} \\ &= \frac{1}{2} \cdot \frac{5 - 2 \times 0.8}{1000 \times 100 \times 10^{-6} \times 60} \\ &= 0.283 \text{ V} \end{aligned}$$

b) The ripple across the load,

$$V_L = i \times 3r_d,$$



where  $i$  is the change in current flowing through  $R_1$ , in series with the 3 diodes.

$$\begin{aligned} \therefore r_d &= \frac{V_T}{I_D} \\ &\approx \frac{26 \text{ mV}}{5/R_1} = 5.2 \Omega \end{aligned}$$

$$\begin{aligned} i &\approx \frac{V_R}{R_1 + 3r_d} \\ &= 0.279 \text{ mA} \end{aligned}$$

$$\begin{aligned} \therefore V_L &= 0.279 \text{ mA} \times 3 \times 5.2 \\ &= 4.35 \text{ mV} \end{aligned}$$

(45)

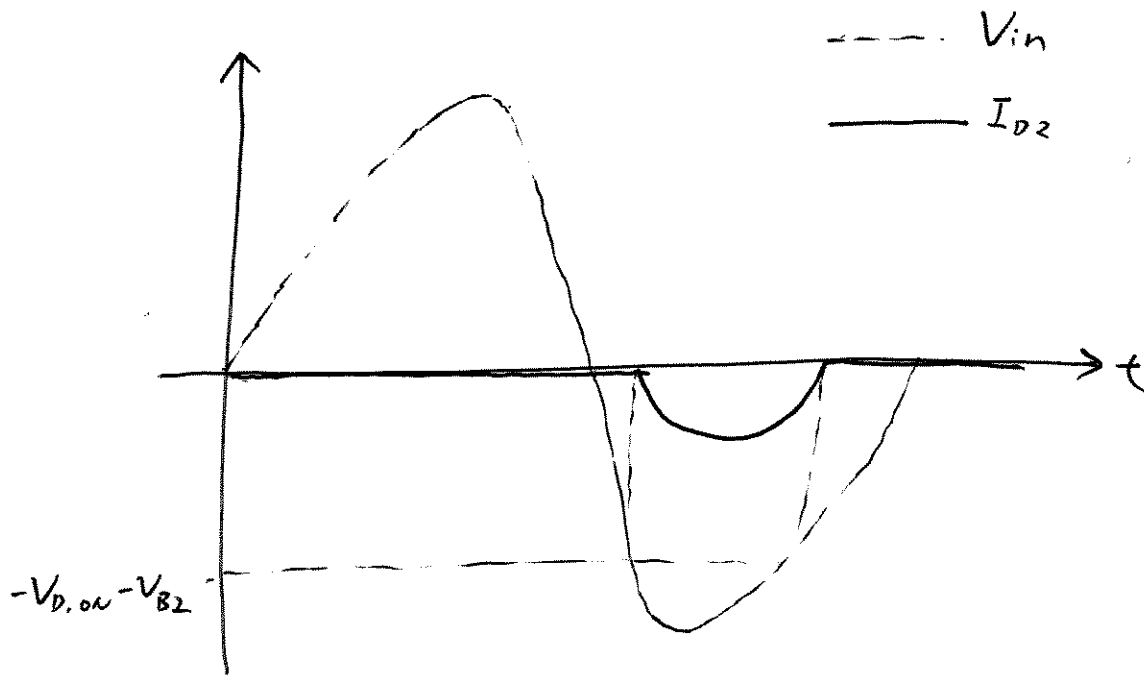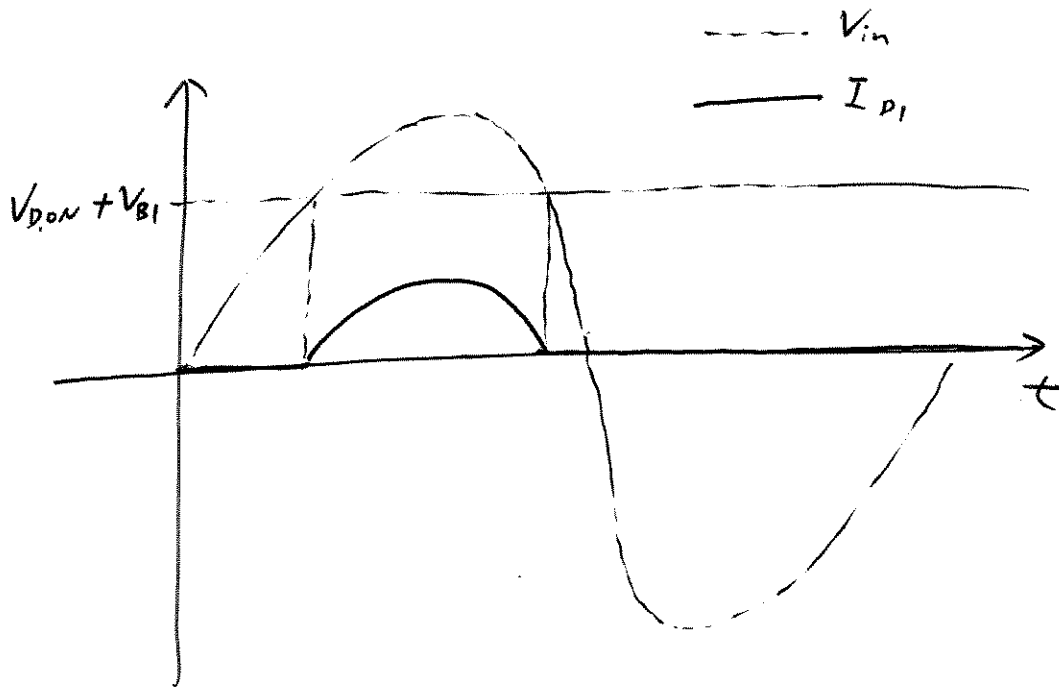

(46) With positive threshold = +2.2V,

$$\begin{aligned}V_{B1} &= 2.2 - 0.8 \\ &= +1.4V\end{aligned}$$

With negative threshold = -1.9V,

$$\begin{aligned}-V_{B2} &= -1.9 + 0.8 \\ &= -1.1V.\end{aligned}$$

$$V_{B2} = 1.1V$$

To meet the maximum current criterion,

Since  $I_{R1} = I_{D1}$  or  $I_{D2}$ ,

$I_{D1}$  or  $I_{D2}$  is at max when

$I_{R1}$  is at max.

$I_{R1}$  is at max when  $|V_R|$  is max,


$$\begin{aligned}\text{ie. } |V_R| &= 5 - 1.9 \\ &= 3.1V.\end{aligned}$$

Since  $I_{R1} \leq 2 \text{ mA}$ .

$$R_1 \geq \frac{3.1}{2 \text{ mA}}, \text{ ie. } R_1 \geq 1550\Omega$$

(47)

The required circuit is:

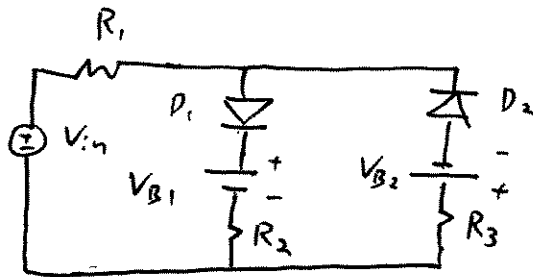

Similar to Example 3.34,

$$\begin{aligned} V_{B1} &= V_{B2} = (2 - 0.8) \text{ V} \\ &= 1.2 \text{ V} \end{aligned}$$

To find  $R_2$ ,


For  $V_{in} > 2 \text{ V}$ ,  $\frac{V_{out}}{V_{in}}$  has a slope of 0.5.

This implies  $R_2 = R_1$   
( $R_1$  and  $R_2$  forms a volt. divider).

Similarly,  $R_3 = R_1$ .


Thus, set  $R_1 = R_2 = R_3 = 1 \text{ k}\Omega$ .

The resulting circuit is:

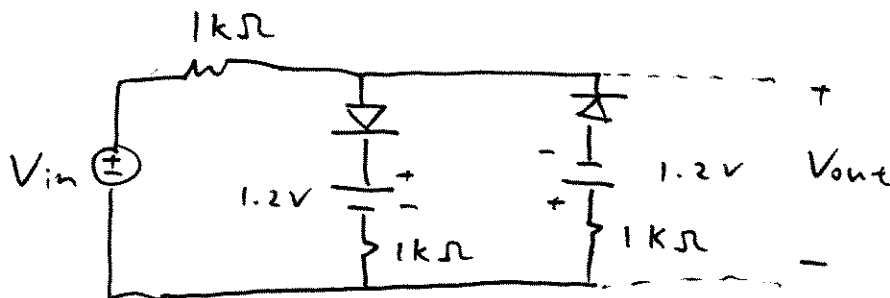


(48) For  $|V_{in}| < 4V$ , the  $V_{out} - V_{in}$  characteristic is similar to prob. (47).

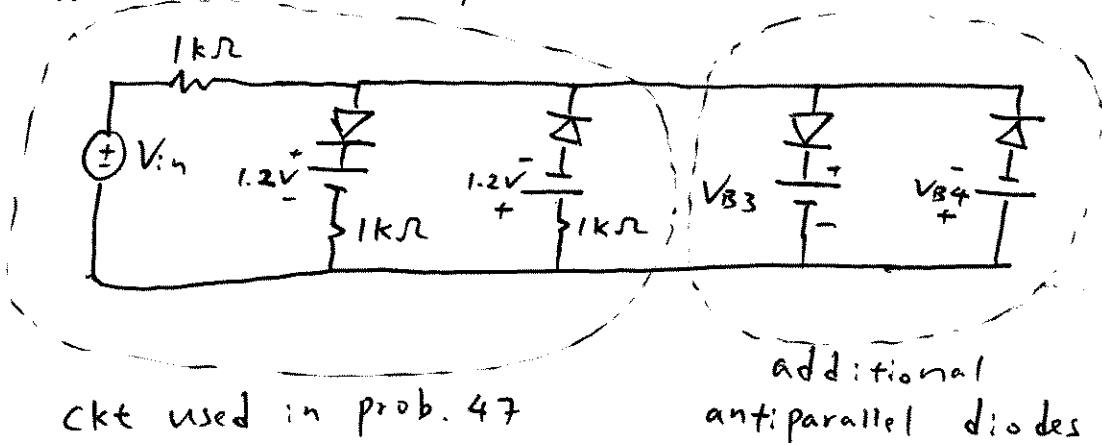To get voltage limiting characteristic for  $V_{in} > 4V$ , and  $V_{in} < -4V$ , we can shunt the circuit used in prob(47) with two anti parallel diodes as below:




$$V_{B3} = V_{B4} = 4 - 0.8 = 3.2V$$

Resulting circuit is:

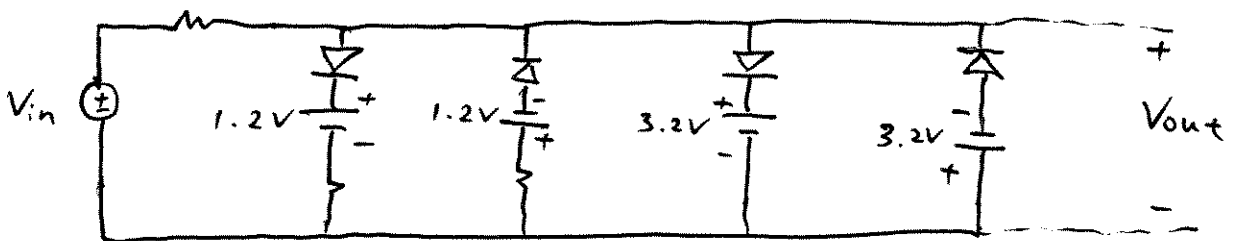




49

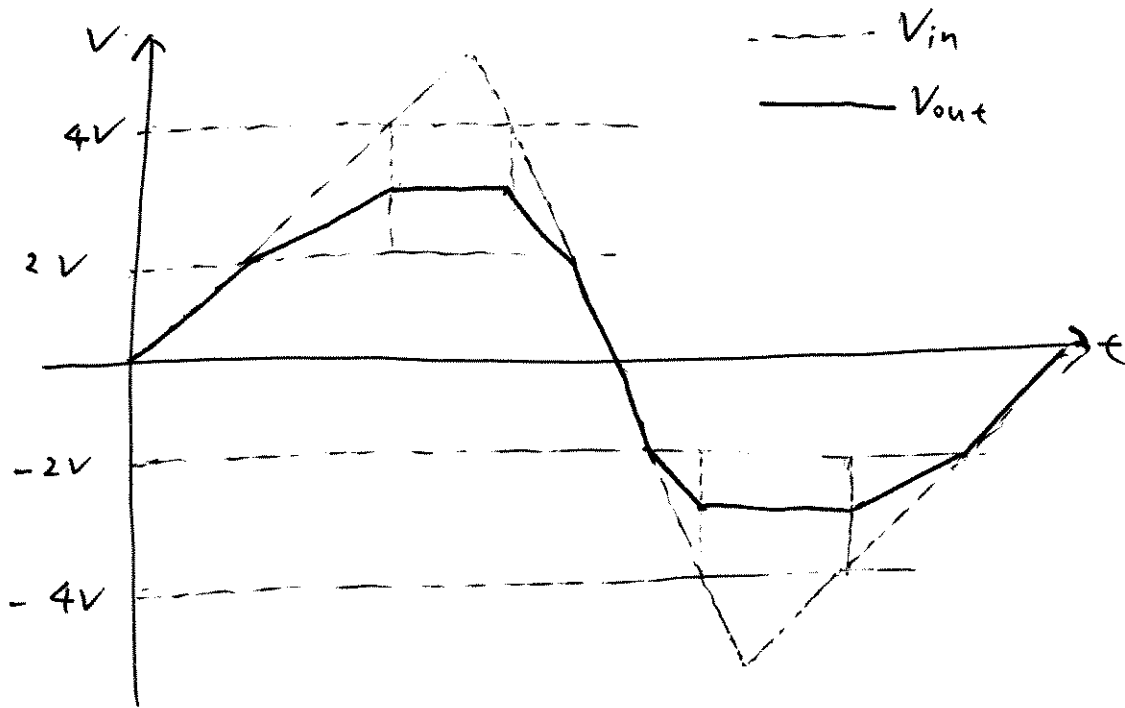


To get a better approximate of a sinusoid, the slope of the input-output characteristic should decrease more gradually from 1 to 0 through more sections.

eg :

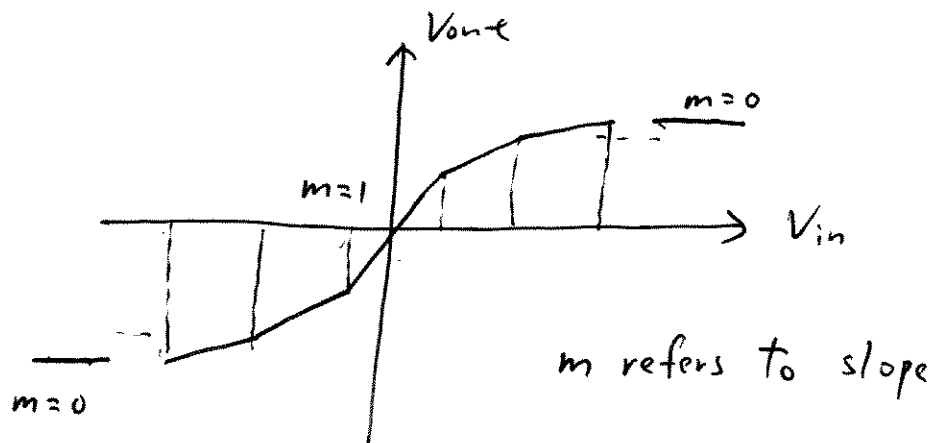

## chapter 4

4.1

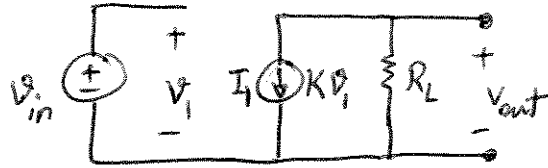

$$K = 20 \text{ mA/V}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = 15 \quad V_{in} = V_1$$


$$V_{out} = -I_1 R_L = -K R_L V_{in}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = -K R_L \Rightarrow \left| \frac{V_{out}}{V_{in}} \right| = K R_L$$

$$\Rightarrow K R_L = 15 \Rightarrow R_L = \frac{15}{20 \text{ mA/V}} = 750 \Omega$$

$$\boxed{R_L = 750 \Omega}$$

4.2

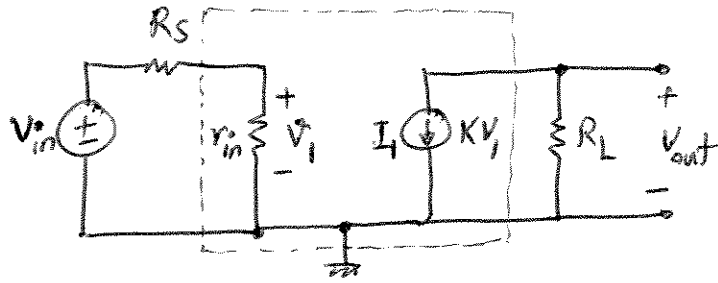

$$\frac{V_{out}}{V_{in}} = ?$$

$$V_1 = \frac{r_{in}}{r_{in} + R_S} V_{in}$$

$$I_1 = K V_1$$

$$V_{out} = -R_L I_1$$

$$\left. \begin{array}{l} V_1 = \frac{r_{in}}{r_{in} + R_S} V_{in} \\ I_1 = K V_1 \\ V_{out} = -R_L I_1 \end{array} \right\} \Rightarrow V_{out} = -K R_L V_1$$

$$\Rightarrow V_{out} = -K R_L \frac{r_{in}}{r_{in} + R_S} V_{in}$$

$$\Rightarrow A_V = \frac{V_{out}}{V_{in}} = -K R_L \frac{r_{in}}{r_{in} + R_S}$$

4.3 From solution for problem 4.2,

$$a > 0$$


$$b > 0$$

$$x \gg 0$$

$$A_v = -KR_L \frac{r_{in}}{r_{in} + R_S}$$

$$\begin{array}{l} r_{in} = a/x \\ K = bx \end{array} \rightarrow A_v = -bx R_L \frac{a/x}{a/x + R_S} = -bR_L \frac{a}{\frac{a}{x} + R_S}$$
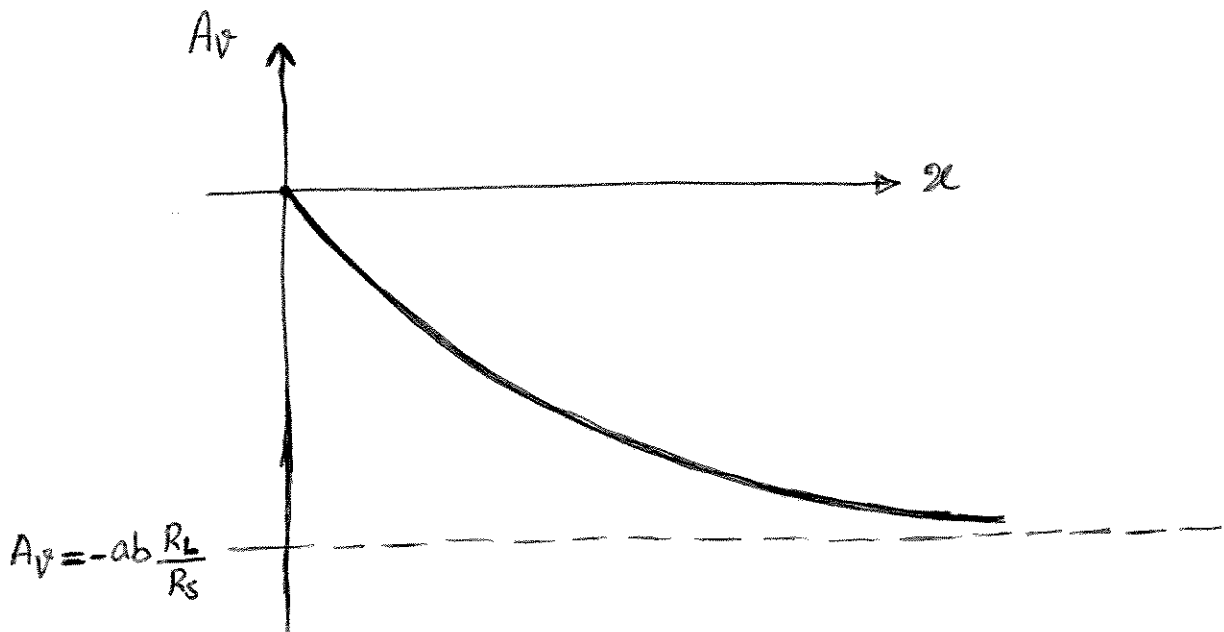
$$\Rightarrow A_v = -bR_L \left( \frac{x}{1 + \frac{R_S}{a} x} \right)$$




4.4 From equation (4.8) page 136,

$$I_C = \frac{A_E q D_n n_p^2}{N_E W_B} e^{\frac{V_{BE}}{V_T}} \quad W_B \equiv \text{width of the Base}$$

if  $W_B \uparrow 2 \Rightarrow I_C \downarrow 2$

Collector current decreases by a factor of two

4.5

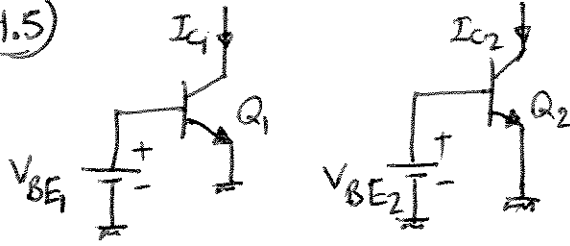

$$V_T = 26 \text{ mV}$$

$$I_{C1} = I_{C2}$$

$$V_{BE1} - V_{BE2} = 20 \text{ mV}$$

$$I_C = \frac{A_E q D_n n_i^2}{N_E W_B} \left( e^{\frac{V_{BE}}{V_T}} - 1 \right) \quad \text{equation (4.8) page 136}$$

$$\Rightarrow I_C \approx \frac{A_E q D_n n_i^2}{N_E W_B} e^{\frac{V_{BE}}{V_T}} \quad A_E \equiv \text{Cross Section}$$

if  $I_{C1} = I_{C2}$

$$\Rightarrow \frac{A_{E1} q D_n n_i^2}{N_E W_B} e^{\frac{V_{BE1}}{V_T}} = \frac{A_{E2} q D_n n_i^2}{N_E W_B} e^{\frac{V_{BE2}}{V_T}}$$

$$\Rightarrow \frac{A_{E2}}{A_{E1}} = \frac{e^{\frac{V_{BE1}}{V_T}}}{e^{\frac{V_{BE2}}{V_T}}}$$

$$\Rightarrow \frac{A_{E2}}{A_{E1}} = e^{\frac{(V_{BE1} - V_{BE2})}{V_T}} = e^{\frac{20 \text{ mV}}{26 \text{ mV}}}$$

$$\Rightarrow \boxed{\frac{A_{E2}}{A_{E1}} = e^{\frac{20}{26}} \approx 2.16}$$

$$\textcircled{6a} \quad I_x = 1^{\text{mA}} \Rightarrow I_{Q_1} = I_{Q_2} = 0.5^{\text{mA}}$$

$$I_{Q_1} = I_{S_1} e^{\frac{V_{BE1}}{V_T}} \Rightarrow 5 \times 10^{-4} = 3 \times 10^{-16} e^{\frac{V_B}{26 \text{mV}}}$$

$$\Rightarrow V_B = 26^{\text{mV}} \ln\left(\frac{5}{3} \times 10^{12}\right) \Rightarrow$$

$$\boxed{V_B \approx 731.7^{\text{mV}}}$$

$$\textcircled{6b} \quad I_y = I_{S_3} e^{\frac{V_B}{V_T}}$$

$$\Rightarrow I_{S_3} = I_y e^{-\frac{V_B}{V_T}} = 2.5 \times 10^{-3} \times e^{-\frac{V_B}{26 \text{mV}}} = 2.5 \times 10^{-3} \times \frac{1}{\frac{5}{3} \times 10^{12}}$$

$$\Rightarrow \boxed{I_{S_3} = 1.5 \times 10^{-15} \text{ A}}$$

$$\textcircled{7a} \quad I_x = I_1 + I_2$$

$$\Rightarrow I_x = I_{s1} e^{\frac{V_B}{V_T}} + I_{s2} e^{\frac{V_B}{V_T}} \Rightarrow I_x = (I_{s1} + I_{s2}) e^{\frac{V_B}{V_T}}$$

$$\Rightarrow V_B = V_T \ln \left( \frac{I_x}{I_{s1} + I_{s2}} \right) \xrightarrow{I_{s1} = 2I_{s2}} \boxed{V_B = V_T \ln \left( \frac{I_x}{\frac{3}{2} I_{s1}} \right)}$$

$$V_B = 26 \times 10^{-3} \ln \left( \frac{1.2 \times 10^{-3}}{\frac{3}{2} \times 5 \times 10^{-16}} \right) \Rightarrow \boxed{V_B \approx 730.6 \text{ mV}}$$

$\textcircled{7b}$  Transistors at the edge of the active mode  $\Rightarrow V_C = V_B$

applying KVL, we have:

$$V_{CC} = R_C I_x + V_B \Rightarrow \boxed{R_C = \frac{V_{CC} - V_B}{I_x}}$$

$$\Rightarrow R_C = \frac{2.5 - 0.73}{1.2 \times 10^{-3}}$$

$$\Rightarrow \boxed{R_C \approx 1475 \Omega}$$



8a) Same as 7a,

$$V_B \approx 730.6 \text{ mV}$$

8b) According to 7b,

$$R_C = \frac{V_{CC} - V_B}{I_X} = \frac{1.5 - 0.73}{1.2 \times 10^{-3}}$$

$$\Rightarrow R_C \approx 642 \Omega$$

④  $Q_1$  is at the edge of the active region  $\Rightarrow V_C = V_B$


applying KVL, we have:

$$V_{CC} = R_C I_C + V_C$$

$$\xrightarrow{V_C = V_B} V_{CC} = R_C I_C + V_B$$

$$\Rightarrow V_{CC} = R_C I_S e^{\frac{V_B}{V_T}} + V_B$$
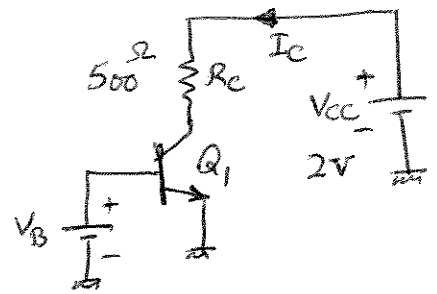
$$\Rightarrow 500 \Omega \times 5 \times 10^{-16} e^{\frac{V_B}{26 \text{ mV}}} + V_B = 2 \text{ V}$$



Using numerical methods or simply, trial & error:

$$\boxed{V_B \approx 760 \text{ mV}}$$

⑩  $Q_1$  at the edge of saturation  $\Rightarrow V_C = V_B$



Hence:  $V_{CC} = R_C I_C + V_B$

$\Rightarrow V_{CC} = R_C I_S e^{\frac{V_B}{V_T}} + V_B$

$I_S = 3 \times 10^{-16} \text{ A}$

$V_{CC} = 3 \times 10^{-13} e^{\frac{V_B}{V_T}} + V_B$

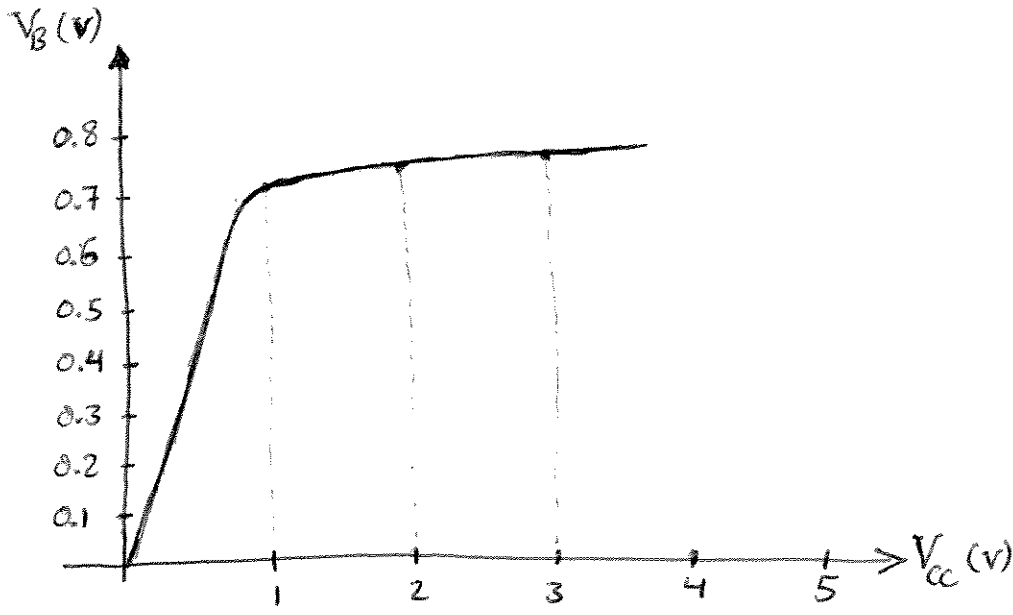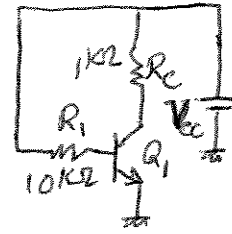with  $V_{CC} = 2 \text{ V}$   $V_B \approx 755 \text{ mV}$



⑪ Assuming  $I_E \approx I_C$ , we can write:

$$\text{Applying KVL: } 1.5V = V_{BE} + V_X \quad \text{where } V_X = 1^{k\Omega} \times I_E$$


$$\text{Hence: } 1.5 = V_{BE} + 1^{k\Omega} \times I_C$$

$$\Rightarrow 1.5 = V_{BE} + 1^{k\Omega} \times I_S e^{\frac{V_{BE}}{V_T}}$$

$$\frac{I_S = 6 \times 10^{-16} \text{ A}}{V_T = 26 \text{ mV}} \quad 1.5 = V_{BE} + 6 \times 10^{-13} e^{\frac{V_{BE}}{26 \text{ mV}}} \Rightarrow \boxed{V_{BE} \approx 724.5 \text{ mV}}$$

$$V_X = 1.5 - V_{BE} \Rightarrow \boxed{V_X \approx 775.5 \text{ mV}}$$

(12)

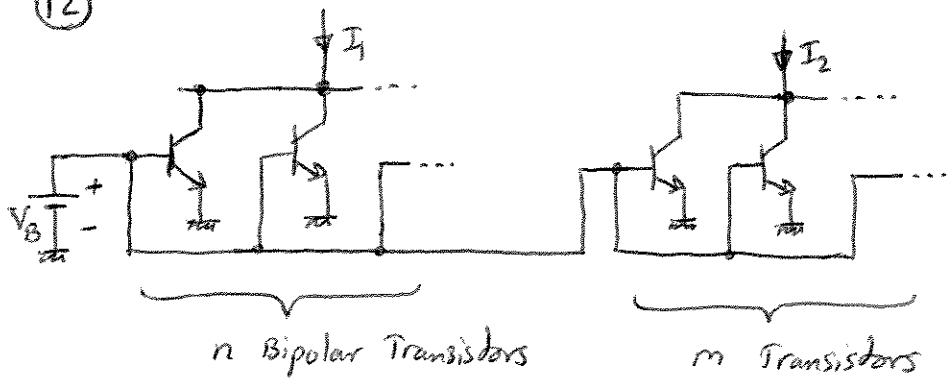

$$\left. \begin{aligned} I_1 &= n I_c = n I_s e^{\frac{V_B}{V_T}} \\ I_2 &= m I_c = m I_s e^{\frac{V_B}{V_T}} \end{aligned} \right\} \Rightarrow \frac{I_1}{I_2} = \frac{n}{m}$$

$$\Rightarrow \frac{n}{m} = \frac{1 \text{ mA}}{1.5 \text{ mA}} = \frac{2}{3} \quad \xrightarrow{\text{choose}} \quad \begin{cases} n=2 \\ m=3 \end{cases}$$

$$I_1 = n I_c = n I_s e^{\frac{V_B}{V_T}}$$

$$\Rightarrow I_1 = n \times 3 \times 10^{-16} e^{\frac{V_B}{26 \text{ mV}}} = 1 \text{ mA} \quad n=2 \quad \Rightarrow \quad \boxed{V_B \approx 750 \text{ mV}}$$

⑬ Using the same technique as in <sup>problem</sup> 12, we have:

$$\frac{n_1}{I_1} = \frac{n_2}{I_2} = \frac{n_3}{I_3}$$

$$\Rightarrow \frac{n_1}{0.2} = \frac{n_2}{0.3} = \frac{n_3}{0.45} \Rightarrow \boxed{\frac{n_1}{4} = \frac{n_2}{6} = \frac{n_3}{9}}$$

So let's choose  $\begin{cases} n_1 = 4 \\ n_2 = 6 \\ n_3 = 9 \end{cases}$


Hence,

$$I_1 = n_1 I_S e^{\frac{V_B}{V_T}} \Rightarrow 0.2 \times 10^{-3} = 4 \times 3 \times 10^{-16} e^{\frac{V_B}{26 \text{ mV}}}$$

$$\Rightarrow \boxed{V_B \approx 672 \text{ mV}}$$

⑭ From KVL,

$$V_B = R_1 I_B + V_{BEQ_1}$$

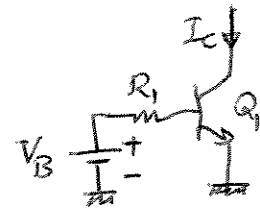

$$I_B = \frac{I_C}{\beta} = \frac{1 \text{ mA}}{100} \Rightarrow \boxed{I_B = 10^{-5} \text{ A}}$$

$$V_{BEQ_1} = V_T \ln\left(\frac{I_C}{I_S}\right) = 26 \times 10^{-3} \ln\left(\frac{10^{-3}}{7 \times 10^{-16}}\right)$$

$$\Rightarrow \boxed{V_{BEQ_1} \approx 727.7 \text{ mV}}$$

Therefore,

$$V_B = R_1 I_B + V_{BEQ_1}$$

$$\approx 10 \text{ k}\Omega \times 10^{-5} \text{ A} + 728 \times 10^{-3}$$

$$\Rightarrow V_B \approx 0.1 + 0.728 \Rightarrow \boxed{V_B \approx 0.828 \text{ V}}$$

⑤ According to the solution for problem 14, we have:

$$\text{Applying KVL: } V_B = R_B I_B + V_{BE}$$

$$\Rightarrow V_B = R_B \frac{I_C}{\beta} + V_T \ln\left(\frac{I_C}{I_S}\right)$$

$$\Rightarrow 0.8 = 10^4 \times \frac{I_C}{100} + 26 \times 10^{-3} \ln\left(\frac{I_C}{7 \times 10^{-16}}\right)$$


$$\Rightarrow 0.8 = 100 I_C + 26 \times 10^{-3} \ln\left(\frac{I_C}{7 \times 10^{-16}}\right)$$

using trial & error or numerical methods,

$$\boxed{I_C \approx 7.85 \times 10^{-4} \text{ A} = 785 \mu\text{A}}$$


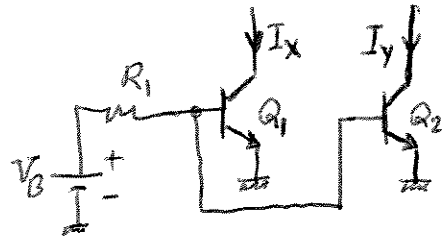
$$\textcircled{16} \begin{cases} I_x = I_{S1} \exp\left(\frac{V_{BE1}}{V_T}\right) \\ I_y = I_{S2} \exp\left(\frac{V_{BE2}}{V_T}\right) \\ V_{BE1} = V_{BE2} = V_{BE} \end{cases}$$



$$\Rightarrow \frac{I_x}{I_y} = \frac{I_{S1}}{I_{S2}} = \frac{2I_{S2}}{I_{S2}} \Rightarrow \boxed{\frac{I_x}{I_y} = 2} \begin{cases} I_x = \beta_1 I_{B1} \\ I_y = \beta_2 I_{B2} \\ \beta_1 = \beta_2 \end{cases}$$

$$\Rightarrow \boxed{\frac{I_{B1}}{I_{B2}} = \frac{I_x}{I_y} = 2}$$

Applying KVL:

$$V_B = R_1 (I_{B1} + I_{B2}) + V_{BE}$$

$$V_{BE} = V_{BE1} = V_T \ln\left(\frac{I_x}{I_{S1}}\right) = 26 \text{ mV} \ln\left(\frac{1 \text{ mA}}{4 \times 10^{-16}}\right) \approx 742 \text{ mV}$$

$$I_{B1} = \frac{I_x}{\beta} \xrightarrow{\beta=100} I_{B1} = \frac{1 \text{ mA}}{100} = 10 \mu\text{A}$$

$$\frac{I_{B1}}{I_{B2}} = 2 \longrightarrow I_{B2} = \frac{I_{B1}}{2} = \frac{10 \mu\text{A}}{2} \Rightarrow I_{B2} = 5 \mu\text{A}$$

$$\text{Hence: } V_B = 5 \times 10^3 \Omega (10 \mu\text{A} + 5 \mu\text{A}) + 0.742 \text{ V}$$

$$= 0.075 + 0.742 \Rightarrow \boxed{V_B = 0.817 \text{ V}}$$

(17) Applying KVL:

$$V_B = R_1 (I_{B1} + I_{B2}) + V_{BE} \stackrel{\beta_1 = \beta_2 = \beta}{=} \frac{R_1}{\beta} (I_{C1} + I_{C2}) + V_{BE}$$

$$\Rightarrow V_B = \frac{R_1}{\beta} (I_{S1} + I_{S2}) \exp\left(\frac{V_{BE}}{V_T}\right) + V_{BE}$$

$$\stackrel{\beta=100}{\Rightarrow} 0.8 \text{ V} = \frac{5000^{\Omega}}{100} (3 \times 10^{-16} + 5 \times 10^{-16}) \exp\left(\frac{V_{BE}}{26 \text{ mV}}\right) + V_{BE}$$

$$\Rightarrow 0.8 \text{ V} = 4 \times 10^{-14} \cdot \exp\left(\frac{V_{BE}}{26 \text{ mV}}\right) + V_{BE}$$

Numerical methods or Trial & error  $\Rightarrow$   $V_{BE} \approx 732 \text{ mV}$

$$I_x = I_{S1} \exp\left(\frac{V_{BE}}{V_T}\right) = 3 \times 10^{-16} \left[ \exp\left(\frac{732}{26}\right) \right] \Rightarrow I_x \approx 506 \mu\text{A}$$

$$I_y = I_{S2} \exp\left(\frac{V_{BE}}{V_T}\right) = 5 \times 10^{-16} \exp\left(\frac{732}{26}\right) \Rightarrow I_y \approx 843 \mu\text{A}$$

⑮ Since Transistor is in Forward active region,


No change across  $V_{BE}$



No change in  $I_B$



No change in  $I_C$

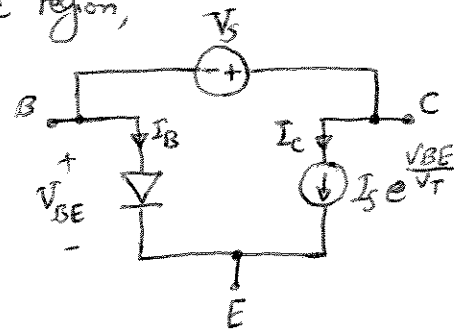

$$\textcircled{19} \quad g_m = \frac{I_c}{V_T}$$

$$\Rightarrow g_m = \frac{I_S \exp\left(\frac{V_{BE}}{V_T}\right)}{V_T} \Rightarrow \boxed{V_{BE} = V_T \ln\left(\frac{g_m V_T}{I_S}\right)}$$

$$\begin{array}{l} I_S = 6 \times 10^{-16} \text{ A} \\ g_m = \frac{1}{13 \Omega} \end{array} \rightarrow V_{BE} = 26 \text{ mV} \cdot \ln\left(\frac{\frac{1}{13 \Omega} \times 26 \times 10^{-3}}{6 \times 10^{-16}}\right)$$

$$\Rightarrow \boxed{V_{BE} \approx 750 \text{ mV}}$$

20

$$g_m = \frac{I_c}{V_T}$$

$$\Delta g_m = \frac{\Delta I_c}{V_T} = \frac{1}{V_T} \Delta \left( I_s e^{\frac{V_{BE}}{V_T}} \right) \approx \frac{I_s}{V_T^2} e^{\frac{V_{BE}}{V_T}} \Delta V_{BE}$$

$$\Rightarrow \boxed{\Delta g_m \approx \frac{I_c}{V_T^2} \Delta V_{BE}}$$


$$\Rightarrow \Delta g_m \approx \frac{g_m}{V_T} \Delta V_{BE}$$

$$\Rightarrow \boxed{\frac{\Delta g_m}{g_m} \approx \frac{1}{V_T} \Delta V_{BE}}$$


$$\left. \frac{\Delta g_m}{g_m} \right|_{I_c=1\text{mA}}^{\text{max}} 0.1 \Rightarrow \Delta V_{BE, \text{max}} = 0.1 V_T$$

$$\Rightarrow \boxed{\Delta V_{BE} \leq 2.6 \text{ mV}}$$

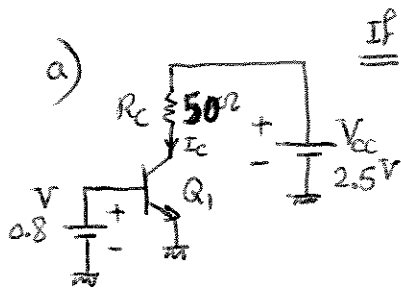②  $V_A = \infty \Rightarrow r_o = \infty$ ,  $I_S = 8 \times 10^{-16} \text{ A}$ ,  $\beta = 100$




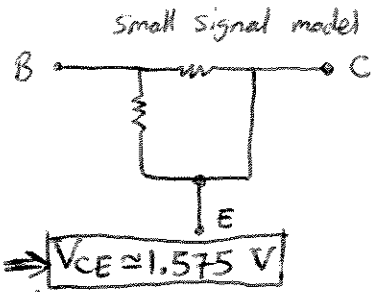If in Forward active region,  
 $I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right)$   
 $= 8 \times 10^{-16} \exp\left(\frac{0.8}{26}\right)$   
 $\Rightarrow I_C \approx 18.5 \text{ mA}$



Hence Transistor should be in Forward Active

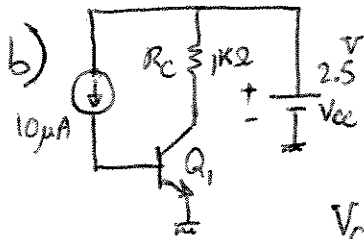$I_{CQ} = \frac{V_{CC} - V_{CE}}{R_C} = \frac{2.5 - 1.575}{50 \Omega} = \frac{0.925}{50} \Rightarrow I_C \approx 18.5 \text{ mA}$   
 which matches with  $I_C$





Assuming in Forward active region,

$I_C = \beta I_B = 100 \times 10^{-6} \text{ A} \Rightarrow I_C = 1 \text{ mA}$

$V_{CE} = V_{CC} - R_C I_C = 2.5 - 1 \times 1 \text{ mA} \Rightarrow V_{CE} = 1.5 \text{ V}$

$g_m = \frac{I_C}{V_T} = \frac{1 \text{ mA}}{26 \text{ mV}} \Rightarrow g_m = \frac{1}{26} \Omega^{-1}$

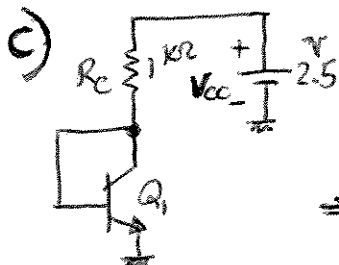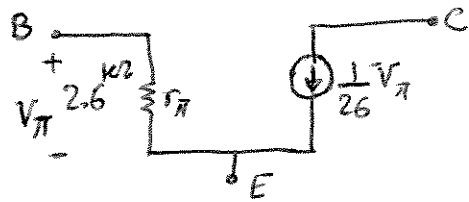$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{1/26} \Rightarrow r_{\pi} \approx 2600 \Omega$




Applying KVL,

$V_{CC} \approx R_C I_C + V_{BE}$


$\Rightarrow 2.5 \text{ V} \approx 1 \text{ k} \times I_C + V_{BE}$

$\Rightarrow 2.5 \text{ V} \approx 8 \times 10^{-13} \cdot \exp\left(\frac{V_{BE}}{V_T}\right) + V_{BE} \Rightarrow V_{BE} \approx 739 \text{ mV}$

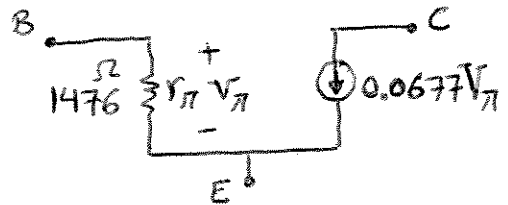$g_m = \frac{I_C}{V_T} = \frac{V_{CC} - V_{BE}}{R_C V_T} \Rightarrow g_m = \frac{2.5 - 0.739}{1 \text{ k} \times 0.026} \Rightarrow g_m \approx 67.7 \text{ mS}, I_C \approx 1.76 \text{ mA}$



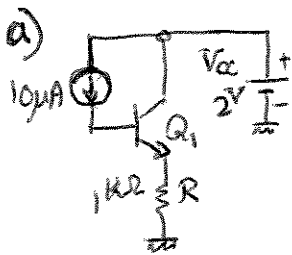
②  $V_A = \infty \Rightarrow r_o = \infty$ ,  $I_S = 8 \times 10^{-16} \text{ A}$ ,  $\beta = 100$



$I_C = \beta I_B = 100 \times 10^{-5} \text{ A} \Rightarrow I_C = 1 \text{ mA}$

$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 26 \text{ mV} \times \ln\left(\frac{10^{-3}}{8 \times 10^{-16}}\right)$

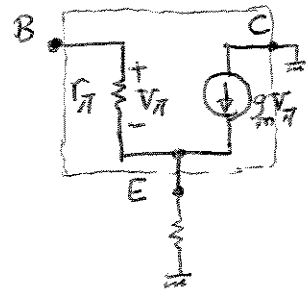
$\Rightarrow V_{BE} \approx 724 \text{ mV}$



$V_{CE} = V_{CC} - R I_E \approx V_{CC} - R I_C = 2 - 1 \text{ k}\Omega \times 1 \text{ mA} \Rightarrow V_{CE} = 1 \text{ V}$

$g_m = \frac{I_C}{V_T} = \frac{1 \text{ mA}}{26 \text{ mV}} \Rightarrow g_m = \frac{1}{26 \text{ }\Omega}$

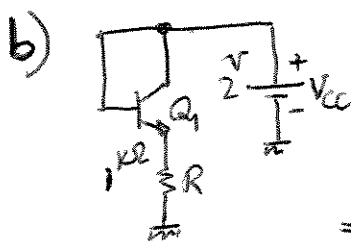
$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{\frac{1}{26}} \Rightarrow r_{\pi} = 2.6 \text{ k}\Omega$



Applying KVL,

$V_{CC} = V_{BE} + R I_E$

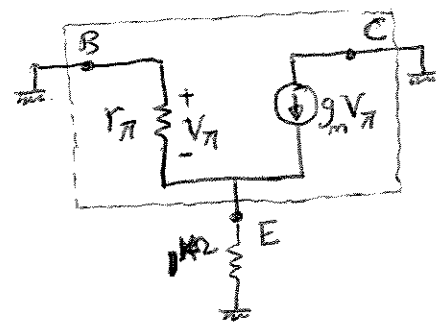$\Rightarrow V_{CC} \approx V_{BE} + R I_C$



$\Rightarrow V_{CC} = V_{BE} + R I_S \exp\left(\frac{V_{BE}}{V_T}\right)$


$\Rightarrow 2 \text{ V} \approx V_{BE} + 8 \times 10^{-13} \exp\left(\frac{V_{BE}}{26 \text{ mV}}\right) \Rightarrow V_{BE} \approx 730 \text{ mV}$

$V_{CE} = V_{BE} = 730 \text{ mV}$        $I_C = 8 \times 10^{-16} \exp\left(\frac{730}{26}\right) \Rightarrow I_C \approx 1.2 \text{ mA}$

$g_m = \frac{I_C}{V_T} = \frac{1.2 \text{ mA}}{26 \text{ mV}} \Rightarrow g_m \approx 46 \text{ mS}$

$r_{\pi} = \frac{\beta}{g_m} \xrightarrow{\beta=100} r_{\pi} \approx 2167 \text{ }\Omega$

22) Continued...

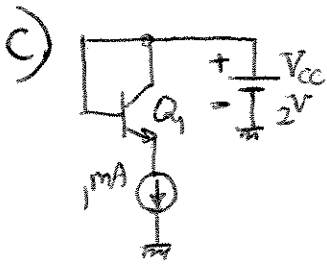

$$I_C \approx I_E = 1 \text{ mA}$$



$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 26 \text{ mV} \ln\left(\frac{1 \text{ mA}}{8 \times 10^{-16}}\right)$$

$$\Rightarrow V_{BE} \approx 724 \text{ mV}$$

$$V_{CE} = V_{BE} = 724 \text{ mV}$$

$$g_m = \frac{I_C}{V_T} = \frac{1 \text{ mA}}{26 \text{ mV}} \Rightarrow g_m = \frac{1}{26 \Omega}$$
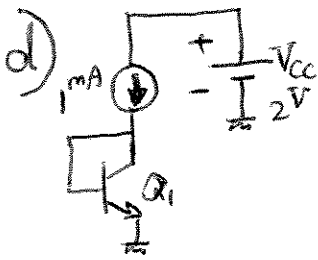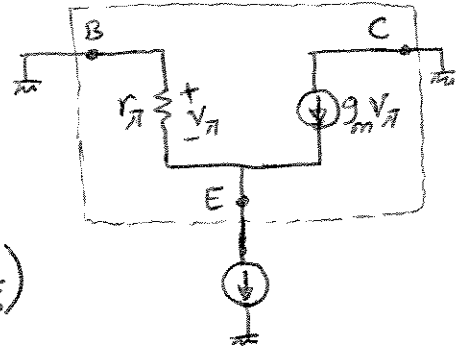
$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{\frac{1}{26}} \Rightarrow r_{\pi} \approx 2.6 \text{ k}\Omega$$




As in part c, we have,

$$I_C \approx 1 \text{ mA}$$

$$V_{CE} \approx 724 \text{ mV}$$

$$g_m = \frac{1}{26 \Omega}$$

$$r_{\pi} = 2.6 \text{ k}\Omega$$

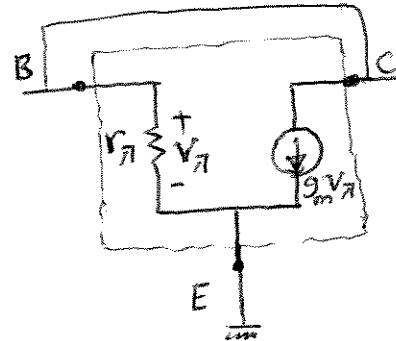




$$(23) \quad I_C = I_S \exp\left(\frac{V_{BE}}{nV_T}\right) \quad I_C = \beta I_B$$

$$g_m = \frac{\partial I_C}{\partial V_{BE}} = \frac{1}{nV_T} I_S \exp\left(\frac{V_{BE}}{nV_T}\right) = \frac{I_C}{nV_T}$$

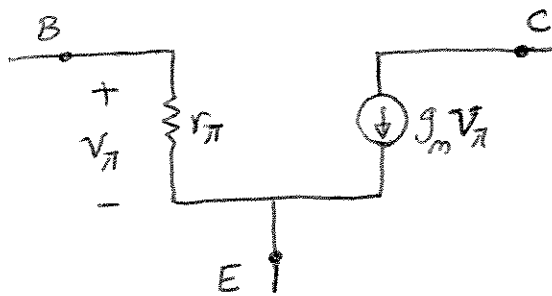
$$r_{\pi} = \frac{\partial V_{BE}}{\partial I_B} = \frac{\partial V_{BE}}{\frac{1}{\beta} \partial I_C} = \frac{\beta}{g_m} = \frac{n\beta V_T}{I_C}$$



$$(24) \quad I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right), \quad I_C = \alpha I_B^2 \Rightarrow \frac{\partial I_B}{\partial I_C} = \frac{1}{2\sqrt{\alpha I_C}}$$

$$g_m = \frac{\partial I_C}{\partial V_{BE}} = \frac{I_S}{V_T} \exp\left(\frac{V_{BE}}{V_T}\right) = \frac{I_C}{V_T}$$
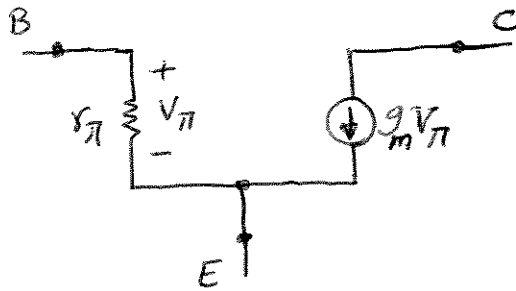
$$r_{\pi} = \frac{\partial V_{BE}}{\partial I_B} = \frac{\partial V_{BE}}{\frac{1}{2\sqrt{\alpha I_C}} \partial I_C} = \frac{2\sqrt{\alpha I_C}}{g_m} = \frac{2\sqrt{\alpha I_C}}{\frac{I_C}{V_T}} = 2V_T \sqrt{\frac{\alpha}{I_C}}$$



$$\textcircled{25} \quad I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{V_{CE}}{V_A}\right] \quad V_{BE} \text{ is Constant}$$

$$\Delta I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \frac{1}{V_A} \Delta V_{CE}$$

$$\Rightarrow \frac{\Delta I_C}{I_C} = \frac{I_S \exp\left(\frac{V_{BE}}{V_T}\right) \frac{1}{V_A} \cdot \Delta V_{CE}}{I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{V_{CE}}{V_A}\right]} = \frac{\Delta V_{CE}}{V_A + V_{CE}}$$

$$\frac{\Delta I_C}{I_{C_{\min}}} < 0.05 \Rightarrow \frac{\Delta V_{CE}}{V_A + V_{CE_{\min}}} < 0.05$$

$$\Rightarrow 20 \Delta V_{CE} < V_A + V_{CE_{\min}}$$

$$\left. \begin{array}{l} \Delta V_{CE} = 2 \text{ V} \\ V_{CE_{\min}} = 1 \text{ V} \end{array} \right\} \Rightarrow 40 < V_A + 1 \Rightarrow \boxed{V_A > 39 \text{ V}}$$

26

$$a) I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) = 5 \times 10^{-17} \exp\left(\frac{800 \text{ mV}}{26 \text{ mV}}\right) \approx \boxed{1.15 \text{ mA}}$$

$$V_X = V_{CC} - R_C I_C = 2.5 \text{ V} - 1 \text{ k}\Omega \times 1.15 \text{ mA}$$

$$\boxed{V_X = 1.35 \text{ V}}$$

Transistor is in Forward Active Region

$$b) I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{V_{CE}}{V_A}\right]$$

$$\Rightarrow I_C = 5 \times 10^{-17} \exp\left(\frac{800}{26}\right) \left[1 + \frac{V_X}{5 \text{ V}}\right] \quad \text{equation 1}$$

$$\text{Also we know: } V_X = V_{CC} - R_C I_C \Rightarrow I_C = \frac{V_{CC} - V_X}{R_C} \quad \text{equation 2}$$

$$\text{equations 1, 2} \Rightarrow \frac{V_{CC} - V_X}{R_C} = 5 \times 10^{-17} \exp\left(\frac{800}{26}\right) \left[1 + \frac{V_X}{5}\right]$$


$$\Rightarrow V_X + 5 \times 10^{-14} \exp\left(\frac{800}{26}\right) \left[1 + \frac{V_X}{5}\right] = 2.5$$

$$\Rightarrow 1.2306 V_X \approx 1.347$$

$$\Rightarrow \boxed{V_X \approx 1.095 \text{ V}} \quad \text{equation 1} \Rightarrow \boxed{I_C \approx 1.406 \text{ mA}}$$

Transistor is in Forward Active Region

(27)

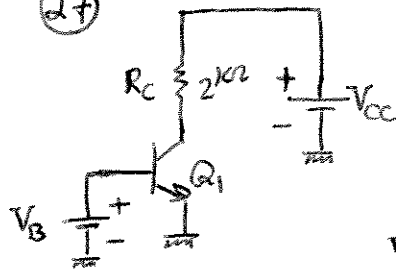

$$I_S = 1 \times 10^{-17} \text{ A} \quad V_A = 5 \text{ V}$$

Applying KVL:

$$V_{CC} = R_C I_C + V_{CE}$$

$$\Rightarrow V_{CC} = R_C I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{V_{CE}}{V_A}\right] + V_{CE}$$

$V_{BE}$  Constant  $\Rightarrow$

$$\Delta V_{CC} = \left[ R_C I_S \exp\left(\frac{V_{BE}}{V_T}\right) \frac{1}{V_A} + 1 \right] \cdot \Delta V_{CE} \quad \text{equation 1}$$

$$I_C = I_S e^{\frac{V_{BE}}{V_T}} \left[1 + \frac{V_{CE}}{V_A}\right] \Rightarrow \Delta I_C = I_S e^{\frac{V_{BE}}{V_T}} \times \frac{1}{V_A} \Delta V_{CE}$$

$$\Rightarrow \Delta V_{CE} = \frac{1}{I_S e^{\frac{V_{BE}}{V_T}} \times \frac{1}{V_A}} \cdot \Delta I_C \quad \text{equation 2}$$

equations 1, 2  $\Rightarrow$


$$\Delta I_C = \frac{I_S e^{\frac{V_{BE}}{V_T}} \times \frac{1}{V_A}}{1 + R_C I_S e^{\frac{V_{BE}}{V_T}} \times \frac{1}{V_A}} \cdot \Delta V_{CC}$$

$$\Rightarrow \Delta I_C = \frac{I_S \exp\left(\frac{V_{BE}}{V_T}\right)}{V_A + R_C I_S \exp\left(\frac{V_{BE}}{V_T}\right)} \cdot \Delta V_{CC} = \frac{1}{r_o + R_C} \cdot \Delta V_{CC}$$

could also be obtained using small signal model  $\uparrow$

$$\Rightarrow \Delta I_C = \frac{2.31 \times 10^{-4}}{5 + 0.4613} \times 0.5 \Rightarrow \Delta I_C \approx 0.021 \text{ mA}$$

(28)

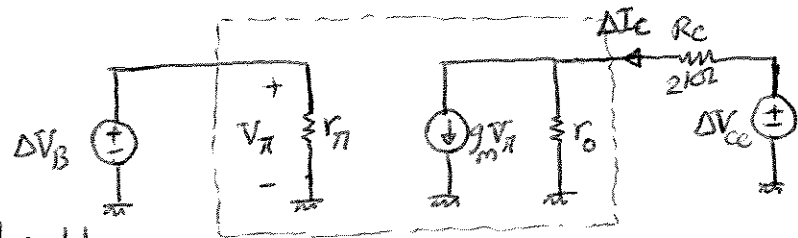

We use small signal model,

Assuming that the required  $\Delta V_B$  is small enough.

Applying superposition,

$$\Delta I_C = \left( \frac{1}{r_o + R_C} \right) \Delta V_{CC} + \left( \frac{g_m r_o}{r_o + R_C} \right) \Delta V_B$$

$$\Delta I_C = 0 \Rightarrow \boxed{\Delta V_B = - \frac{1}{g_m r_o} \Delta V_{CC}}$$


$$\Delta V_B = - \frac{1}{\frac{I_C}{V_T} \cdot \frac{V_A}{I_C}} \Delta V_{CC} \Rightarrow \Delta V_B = - \frac{V_T}{V_A} \Delta V_{CC}$$

$$\Rightarrow \Delta V_B = - \frac{26 \times 10^{-3}}{5} \times (3 - 2.5)$$

$$\Rightarrow \boxed{\Delta V_B = -2.6 \text{ mV}}$$

which is small enough

for small signal model

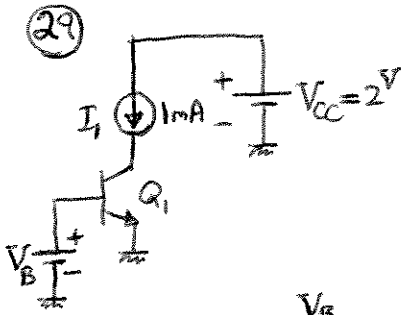

$$I_S = 3 \times 10^{-17} \text{ A}$$

$$a) I_C = I_S e^{\frac{V_B}{V_T}} \Rightarrow V_B = V_T \ln\left(\frac{I_C}{I_S}\right) = 26 \text{ mV} \ln\left(\frac{10^{-3}}{3 \times 10^{-17}}\right)$$

$$\Rightarrow \boxed{V_B \approx 809.6 \text{ mV}}$$

$$b) I_C = I_S e^{\frac{V_B}{V_T}} \left(1 + \frac{V_{CE}}{V_A}\right)$$

$$10^{-3} = 3 \times 10^{-17} e^{\frac{V_B}{V_T}} \left(1 + \frac{1.5}{5}\right) \Rightarrow e^{\frac{V_B}{V_T}} = \frac{10}{3.9}$$

$$\Rightarrow V_B = 26 \text{ mV} \ln\left(\frac{10}{3.9}\right) \Rightarrow \boxed{V_B \approx 802.8 \text{ mV}}$$

$$\textcircled{30} \quad I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{V_{CE}}{V_A}\right]$$

$$r_o^{-1} = \frac{dI_C}{dV_{CE}} = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \cdot \frac{1}{V_A} \approx \frac{I_C}{V_A} \quad \Rightarrow \quad r_o \approx \frac{V_A}{I_C}$$

$$r_o > 10^4 \Omega \quad \Rightarrow \quad \frac{V_A}{I_C} > 10^4 \Omega$$


$$\Rightarrow V_A > 10^4 \Omega \times 2^{\text{mA}}$$

$$\Rightarrow \boxed{V_A > 20 \text{ V}}$$



③  $I_S = 5 \times 10^{-16} \text{ A}$ ,  $V_A = 8 \text{ V}$
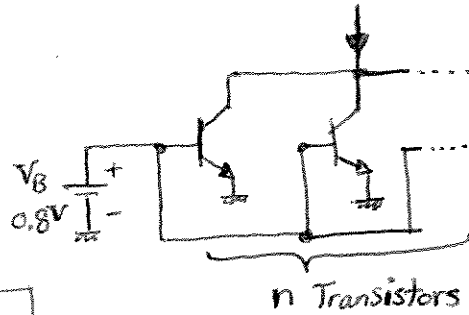
$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{V_{CE}}{V_A}\right]$$




$$g_{m_{Total}} = \frac{I_{C_{Total}}}{V_T} \approx \frac{n I_S \exp\left(\frac{V_{BE}}{V_T}\right)}{V_T}$$

$$\Rightarrow g_{m_{Total}} \approx \frac{n \times 5 \times 10^{-16} \exp\left(\frac{800}{26}\right)}{26 \text{ mV}} \Rightarrow g_{m_{Total}} \approx 0.4435 \text{ n}$$


$$r_o^{-1} = \frac{\partial I_{C_{Total}}}{\partial V_{CE}} = \frac{\partial}{\partial V_{CE}} \left[ n I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{V_{CE}}{V_A}\right] \right]$$

$$\Rightarrow r_o = \frac{V_A}{n I_S \exp\left(\frac{V_{BE}}{V_T}\right)}$$
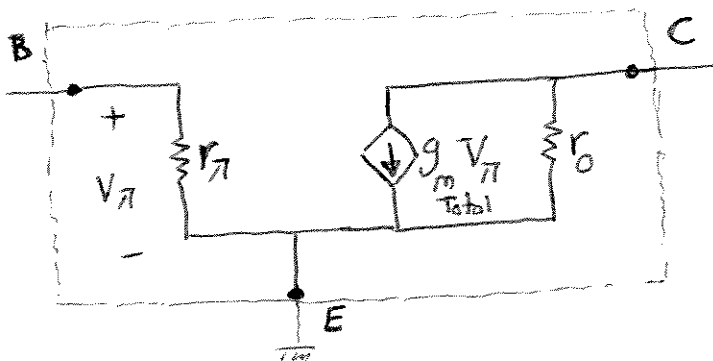
$$r_{\pi} = \frac{\beta}{g_{m_{Total}}} \approx \frac{\beta=100}{0.4435 \text{ n}} \approx \frac{225.5}{\text{n}}$$



32

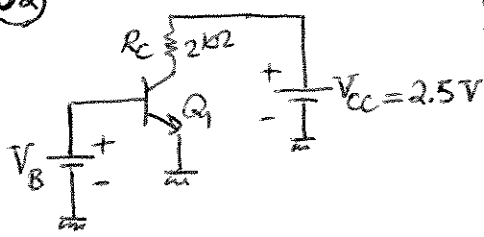

$$I_S = 6 \times 10^{-16} \text{ A}, \quad V_A = \infty$$

a)  $Q_1$  at the edge of the active region  $\Rightarrow V_{CE} = V_{BE}$

applying KVL,  $V_{CC} = R_C I_C + V_{CE}$

at the edge  $\Rightarrow V_{CC} = R_C I_C + V_{BE} \Rightarrow R_C I_S e^{\frac{V_{BE}}{V_T}} + V_{BE} = V_{CC}$

$$\Rightarrow 2 \text{ k}\Omega \times 6 \times 10^{-16} \text{ A} e^{\frac{V_B}{26 \text{ mV}}} + V_B = 2.5 \Rightarrow \boxed{V_B \approx 728.5 \text{ mV}}$$

b) Applying KVL,  $V_{CC} = R_C I_C + V_{CE}$

Soft Saturation  $\Rightarrow V_{CE} = V_{BE} - 0.2 \text{ V}$


$$\Rightarrow V_{CC} = R_C I_C + V_{BE} - 0.2 \text{ V}$$

$$\Rightarrow 2 \text{ k}\Omega \times 6 \times 10^{-16} \text{ A} e^{\frac{V_B}{26 \text{ mV}}} + V_B = 2.7 \text{ V}$$

$$\Rightarrow \boxed{V_B \approx 731.5 \text{ mV}}$$

So  $V_B$  can increase by 3 mV

33

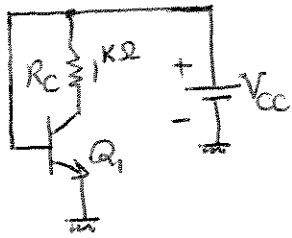

$$I_S = 7 \times 10^{-16} \text{ A}, \quad V_A = \infty$$
$$\Downarrow$$
$$r_o = \infty$$

Applying KVL,

$$V_{CC} = R_C I_C + V_{CE} \xrightarrow{V_{CE} = V_{BE} - 0.2 \text{ V}} R_C I_C + V_{BE} - 0.2 \text{ V} = V_{CC}$$

$$\Rightarrow R_C I_S e^{\frac{V_{BE}}{V_T}} + V_{BE} - 0.2 \text{ V} = V_{CC}$$


$$\xrightarrow{V_{BE} = V_{CC}} R_C I_S e^{\frac{V_{CC}}{V_T}} + V_{CC} - 0.2 = V_{CC}$$

$$\Rightarrow R_C I_S e^{\frac{V_{CC}}{V_T}} = 0.2 \text{ V}$$

$$\Rightarrow 1 \text{ k}\Omega \times 7 \times 10^{-16} e^{\frac{V_{CC}}{26 \text{ mV}}} = 0.2 \text{ V}$$

$$\Rightarrow \boxed{V_{CC} \approx 686 \text{ mV}}$$

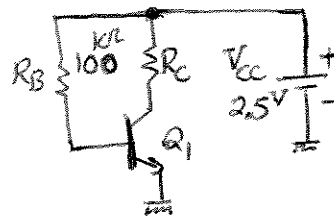34)  $I_S = 2 \times 10^{-17} \text{ A}$ ,  $V_A = \infty$   $\beta = 100$



$$\begin{cases} V_{CC} = R_C I_C + V_{CE}, & V_{CE} = V_{BE} - 0.2 \text{ V} \\ V_{CC} = R_B I_B + V_{BE} \Rightarrow V_{CC} = R_B \frac{I_C}{\beta} + V_{BE} \end{cases}$$

$$R_B \frac{I_C}{\beta} + V_{BE} = V_{CC} \Rightarrow \frac{R_B}{\beta} I_S e^{\frac{V_{BE}}{V_T}} + V_{BE} = V_{CC}$$

$$\Rightarrow \frac{100}{100} \times 2 \times 10^{-17} e^{\frac{V_{BE}}{26 \text{ mV}}} + V_{BE} = 2.5 \text{ V}$$

$$\Rightarrow \boxed{V_{BE} \approx 833.5 \text{ mV}}$$


Soft saturation  $\Rightarrow V_{CE} = V_{BE} - 0.2 \text{ V} \Rightarrow \boxed{V_{CE} = 692.5 \text{ mV}}$

$$V_{CC} = R_C I_C + V_{CE} \Rightarrow R_C = \frac{V_{CC} - V_{CE}}{I_C}$$

$$\Rightarrow R_C = \frac{V_{CC} - V_{CE}}{I_S \exp\left(\frac{V_{BE}}{V_T}\right)} = \frac{2.5 - 0.6925}{2 \times 10^{-17} \exp\left(\frac{892.5}{26}\right)}$$

$$\Rightarrow \boxed{R_C \approx 112 \Omega}$$

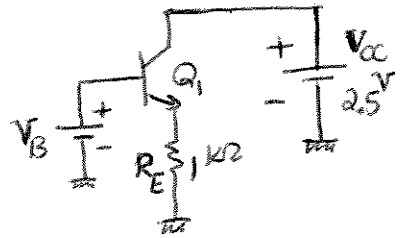③⑤  $I_S = 5 \times 10^{-16} \text{ A}$ ,  $V_A = \infty \Rightarrow r_o = \infty$



Soft saturation  $\Rightarrow V_{BC} = 200 \text{ mV}$

$\Rightarrow V_B = V_C + 0.2 \text{ V} \Rightarrow \boxed{V_B = 2.7 \text{ V}}$

Applying KVL  $\Rightarrow V_B = V_{BE} + R_E I_E \xrightarrow{I_E \approx I_C} V_B = V_{BE} + R_E I_C$

$\Rightarrow V_{BE} + 1 \text{ k}\Omega \times I_S e^{\frac{V_{BE}}{V_T}} = 2.7 \text{ V}$


$\Rightarrow V_{BE} + 5 \times 10^{-13} e^{\frac{V_{BE}}{V_T}} = 2.7 \text{ V} \Rightarrow \boxed{V_{BE} \approx 754 \text{ mV}}$

$I_C = I_S e^{\frac{V_{BE}}{V_T}} = 5 \times 10^{-16} e^{\frac{0.754}{0.026}} \Rightarrow \boxed{I_C \approx 2 \text{ mA}}$

$$\textcircled{36} \quad \beta = 100, \quad V_A = \infty \Rightarrow r_o = \infty$$

$$V_{BC} = 0.2 \text{ V} \Rightarrow R_p I_C = 0.2 \text{ V}$$
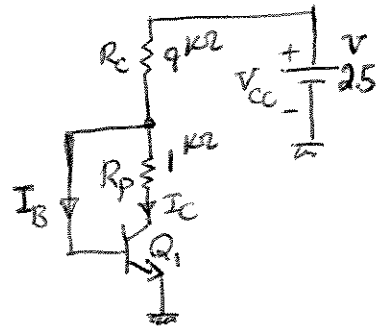
$$\Rightarrow \boxed{I_C = \frac{0.2 \text{ V}}{R_p}}$$



$$V_{BE} = V_{CC} - R_C (I_B + I_C)$$

$$\xrightarrow{\beta=100} V_{BE} = V_{CC} - \frac{\beta+1}{\beta} R_C I_C \Rightarrow \boxed{V_{BE} = V_{CC} - \frac{\beta+1}{\beta} \frac{R_C \times 0.2}{R_p}}$$

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \Rightarrow I_S = I_C \exp\left(-\frac{V_{BE}}{V_T}\right)$$

$$\Rightarrow \boxed{I_S = \frac{0.2}{R_p} \exp\left[\frac{0.2}{V_T} \cdot \frac{\beta+1}{\beta} \cdot \frac{R_C}{R_p} - \frac{V_{CC}}{V_T}\right]}$$

$$\xrightarrow{\beta=100} \boxed{I_S \approx \frac{0.2}{R_p} \exp\left[\frac{0.2}{V_T} \frac{R_C}{R_p} - \frac{V_{CC}}{V_T}\right]}$$

$$\Rightarrow \boxed{I_S \approx 4.06 \times 10^{-16} \text{ A}}$$


$$\textcircled{37} \quad I_{S_1} = 3I_{S_2} = 6 \times 10^{-16} \text{ A}$$

$$I_1 = I_{S_1} \exp\left(\frac{V_{EB_1}}{V_T}\right) = 6 \times 10^{-16} \exp\left(\frac{300}{26}\right) \Rightarrow \underline{I_1 \approx 6.155 \times 10^{-11} \text{ A}}$$

$$I_2 = I_{S_2} \exp\left(\frac{V_{EB_2}}{V_T}\right) = 2 \times 10^{-16} \exp\left(\frac{820}{26}\right) \Rightarrow \underline{I_2 \approx 10 \text{ mA}}$$

$$I_X = I_1 + I_2 \Rightarrow \boxed{I_X \approx 10 \text{ mA}}$$
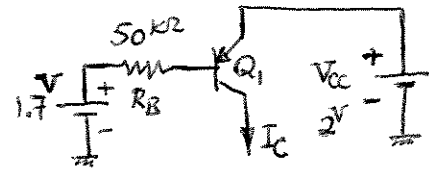
$$(38) \quad I_S = 2 \times 10^{-17} \text{ A} \quad \beta = 100$$



Applying KVL,

$$V_{CC} = V_{EB} + R_B I_B + 1.7 \text{ V}$$

$$\Rightarrow 2 \text{ V} = V_{EB} + R_B \frac{I_C}{\beta} + 1.7 \text{ V}$$

$$\Rightarrow 0.3 \text{ V} = V_{EB} + \frac{50 \text{ k}\Omega}{100} I_C$$

$$\Rightarrow 0.3 \text{ V} = V_{EB} + 500 \times I_S e^{\frac{V_{EB}}{V_T}}$$

$$\Rightarrow 0.3 \text{ V} = V_{EB} + 10^{-14} e^{\frac{V_{EB}}{26 \text{ mV}}} \Rightarrow \boxed{V_{EB} \approx 0.3 \text{ V}}$$


$$I_C = I_S e^{\frac{V_{EB}}{V_T}} \Rightarrow I_C = 2 \times 10^{-17} e^{\frac{300}{26}}$$

$$\Rightarrow \boxed{I_C \approx 2.05 \times 10^{-12} \text{ A}}$$



③⑨  $I_C = 3\text{mA}$ ,  $\beta = 100$ ,  $R_B = 23\text{k}\Omega$

Applying KVL,

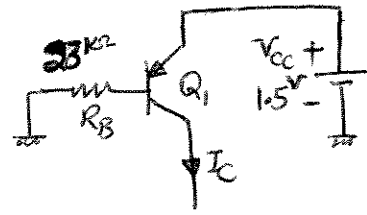

$$V_{CC} = V_{EB} + R_B I_B \Rightarrow V_{CC} = V_{EB} + R_B \frac{I_C}{\beta}$$

$$\Rightarrow -I_C \frac{R_B}{\beta} + V_{CC} = V_{EB}$$

$$I_C = I_S e^{\frac{V_{EB}}{V_T}}$$

$$\Rightarrow I_S = I_C e^{\frac{-V_{EB}}{V_T}}$$


$$\Rightarrow I_S = I_C e^{\frac{1}{V_T} \left( \frac{R_B I_C}{\beta} - V_{CC} \right)}$$

$$\Rightarrow I_S \approx 8.85 \times 10^{-17} \text{ A}$$

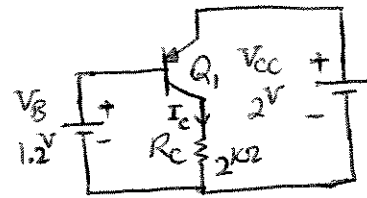40) At the edge of active  $\Rightarrow V_{BC} = 0$

$$I_C = \frac{V_B - V_{BC}}{R_C} = \frac{V_B}{R_C}$$

$$\Rightarrow I_C = \frac{1.2\text{V}}{2\text{k}\Omega} \Rightarrow \boxed{I_C \approx 0.6\text{ mA}}$$




$$I_C = I_S \exp\left(\frac{V_{EB}}{V_T}\right) \Rightarrow I_S = I_C \exp\left(-\frac{V_{EB}}{V_T}\right)$$

$$\Rightarrow I_S = 0.6 \times 10^{-3} \exp\left(-\frac{800}{26}\right)$$

$$\Rightarrow \boxed{I_S \approx 2.6 \times 10^{-17}\text{ A}}$$

④  $I_S = 8 \times 10^{-16} \text{ A}$

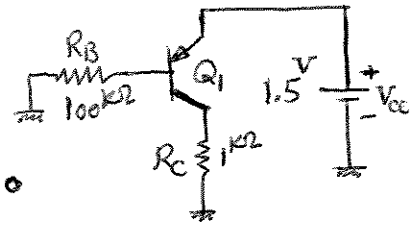

At the edge of the active mode  $\Rightarrow V_{BC} = 0$

$\Rightarrow V_{EB} = V_{EC}$

Applying KVL,

$V_{CC} = V_{EC} + R_C I_C \xrightarrow{V_{EB} = V_{EC}} V_{CC} = V_{EB} + R_C I_C$

$\Rightarrow V_{EB} + R_C I_S e^{\frac{V_{EB}}{V_T}} = V_{CC}$

$\Rightarrow V_{EB} + 8 \times 10^{-13} e^{\frac{V_{EB}}{26 \text{ mV}}} = 1.5 \Rightarrow \boxed{V_{EB} \approx 718 \text{ mV}}$

$I_C = I_S e^{\frac{V_{EB}}{V_T}} \Rightarrow \boxed{I_C \approx 0.788 \text{ mA}}$


Applying KVL,

$V_{BC} = 0 \Rightarrow V_B = V_C \Rightarrow R_B I_B = R_C I_C$

$\Rightarrow R_B \frac{I_C}{\beta} = R_C I_C \Rightarrow \boxed{\beta = \frac{R_B}{R_C}}$

$\Rightarrow \beta = \frac{100 \text{ k}\Omega}{1 \text{ k}\Omega} \Rightarrow \boxed{\beta = 100}$
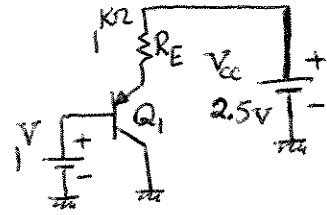
$$(42) I_S = 3 \times 10^{-17} \text{ A}$$



Applying KVL,

$$V_{CC} = R_E I_E + V_{EB} + 1 \text{ V} \quad \xrightarrow{I_E = I_C} \quad V_{CC} = R_E I_C + V_{EB} + 1 \text{ V}$$

$$\Rightarrow 2.5 = 1 \text{ k}\Omega \times 3 \times 10^{-17} e^{\frac{V_{EB}}{26 \text{ mV}}} + V_{EB} + 1 \text{ V}$$

$$\Rightarrow V_{EB} + 3 \times 10^{-14} e^{\frac{V_{EB}}{26 \text{ mV}}} = 1.5 \text{ V}$$

$$\Rightarrow \boxed{V_{EB} \approx 800.5 \text{ mV}}$$

$$I_C = I_S e^{\frac{V_{EB}}{V_T}} = 3 \times 10^{-17} e^{\frac{800.5}{26}} \Rightarrow \boxed{I_C \approx 0.705 \text{ mA}}$$

$$(43) I_S = 3 \times 10^{-17} \text{ A}, \beta = 100, V_A = \infty \Rightarrow r_D = \infty$$


$$a) V_{EB} = 2.5 - 1.7 = 0.8 \text{ V}$$

$$I_C = I_S \exp\left(\frac{V_{EB}}{V_T}\right) = 3 \times 10^{-17} \exp\left(\frac{0.8}{26}\right) \Rightarrow I_C \approx 0.692 \text{ mA}$$

$$V_{EC} = V_{CC} - R_C I_C = 2.5 - 1 \times 0.692 \Rightarrow V_{EC} \approx 1.808 \text{ V}$$

$$g_m = \frac{I_C}{V_T} = \frac{0.692 \text{ mA}}{26 \text{ mV}} \Rightarrow g_m \approx 26.6 \text{ mS}$$
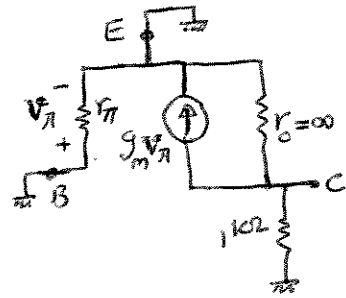
$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{26.6 \times 10^{-3}} \Rightarrow r_{\pi} \approx 3.76 \text{ k}\Omega$$



$$b) V_{EB} = V_T \ln\left(\frac{I_C}{I_S}\right) \Rightarrow V_{EB} = V_T \ln\left(\frac{\beta I_B}{I_S}\right)$$


$$\Rightarrow V_{EB} = 26 \text{ mV} \times \ln\left(\frac{100 \times 20 \times 10^{-6}}{3 \times 10^{-17}}\right)$$

$$\Rightarrow V_{EB} \approx 827.6 \text{ mV}$$

$$I_C = \beta I_B \Rightarrow I_C = 2 \text{ mA}$$

$$V_{EC} = V_{CC} - R_C I_C = 2.5 - 0.5 \times 2 \Rightarrow V_{EC} = 1.5 \text{ V}$$
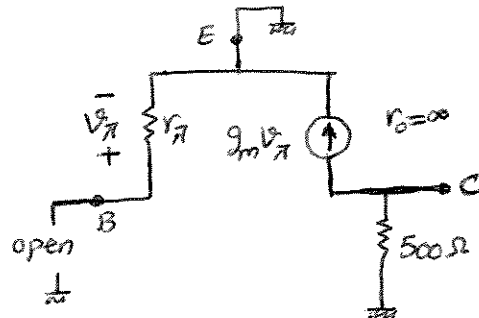
$$g_m = \frac{I_C}{V_T} = \frac{2 \text{ mA}}{26 \text{ mV}} \Rightarrow g_m \approx 77 \text{ mS} \quad r_{\pi} = \frac{\beta}{g_m} \Rightarrow r_{\pi} \approx 1.3 \text{ k}\Omega$$



43) Continued .....

c) Applying KVL,

$$V_{cc} = V_{EB} + (I_C + I_B) \times 2^{k\Omega} \approx V_{EB} + 2^{k\Omega} \times I_C$$


$$\Rightarrow V_{EB} + 2^{k\Omega} \times I_S e^{\frac{V_{EB}}{V_T}} = V_{cc}$$

$$\Rightarrow V_{EB} + 6 \times 10^{-14} e^{\frac{V_{EB}}{26^{mV}}} = 2.5^V \Rightarrow \boxed{V_{EB} \approx 805^{mV}}$$

$$I_C = \frac{V_{cc} - V_{EB}}{R} = \frac{2.5 - 0.805}{2^{k\Omega}} \Rightarrow \boxed{I_C \approx 847.5 \mu A}$$

$$g_m = \frac{I_C}{V_T} = \frac{0.8475 \times 10^{-3}}{0.026} \Rightarrow \boxed{g_m \approx 32.6 \text{ mS}}$$
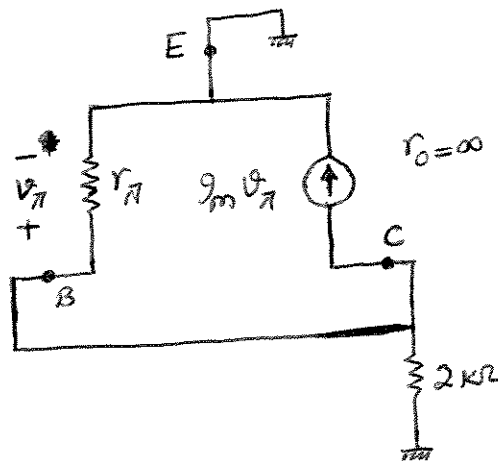
$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{32.6 \times 10^{-3}} \Rightarrow \boxed{r_{\pi} \approx 3068 \Omega}$$




44)  $I_S = 3 \times 10^{-17} \text{ A}$ ,  $\beta = 100$ ,  $V_A = \infty \Rightarrow r_o = \infty$

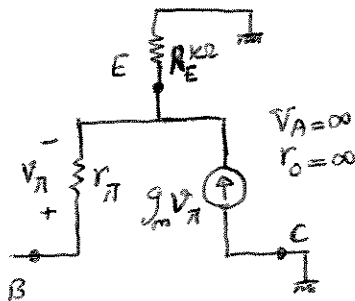a) Applying KVL,

$$V_{CC} = R_E I_E + V_{EC} \xrightarrow{I_E \approx I_C} V_{EC} = V_{CC} - R_E I_C \quad \boxed{I_C = \beta I_B = 0.2 \text{ mA}}$$

$$\Rightarrow \boxed{V_{EC} = V_{CC} - \beta R_E I_B} \xrightarrow[\substack{R_E = 2 \text{ k}\Omega \\ V_{CC} = 2.5 \text{ V}}]{I_B = 2 \mu\text{A}} \boxed{V_{EC} = 2.1 \text{ V}}$$



Transistor is in  
Forward Active Region

b) Applying KVL,


$$V_{CC} = R_E I_E + V_{EB} \Rightarrow V_{CC} = R_E I_C + V_{EB}$$

$$\Rightarrow 2.5 = 5 \text{ k}\Omega \times 3 \times 10^{-17} e^{V_{EB}/V_T} + V_{EB}$$

$$\Rightarrow \boxed{V_{EB} \approx 781.9 \text{ mV}}$$

Forward  
Active  
Region

From Circuit  
 $V_{EC} = V_{EB}$

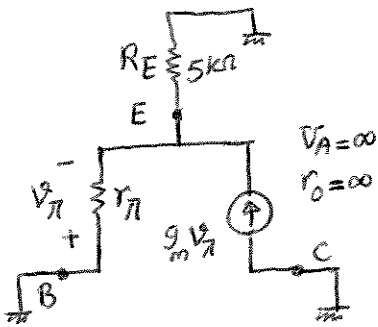

$$g_m = \frac{I_C}{V_T} = \frac{3 \times 10^{-17} e^{\frac{781.9}{26}}}{0.026} \Rightarrow \boxed{g_m \approx 0.0133 \text{ S}}$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{0.0133} \Rightarrow \boxed{r_{\pi} \approx 7538 \Omega}$$

④ Continued.....


c)  $I_E = 0.5 \text{ mA} \Rightarrow I_C \approx 0.5 \text{ mA}$

$$I_C = I_S e^{\frac{V_{EB}}{V_T}} \Rightarrow 0.5 \text{ mA} = 3 \times 10^{-17} e^{\frac{V_{EB}}{26 \text{ mV}}} \Rightarrow V_{EB} \approx 791.6 \text{ mV}$$

In the given circuit:  $V_{EC} = V_{EB}$

$$g_m = \frac{I_C}{V_T} = \frac{0.5 \text{ mA}}{26 \text{ mV}} \Rightarrow g_m \approx 19.2 \text{ mS}$$
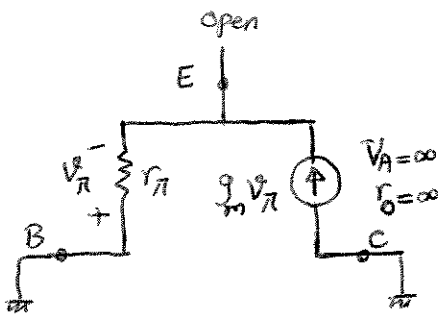
$$r_\pi = \frac{\beta}{g_m} = \frac{100}{0.0192} \Rightarrow r_\pi \approx 5.2 \text{ k}\Omega$$




Forward Active Region



45)  $I_S = 5 \times 10^{-17} \text{ A}$

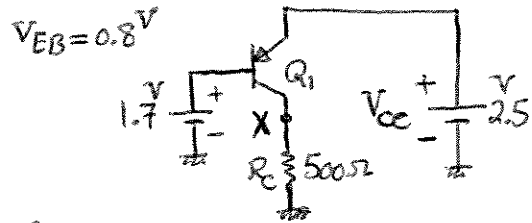a)  $V_A = \infty \Rightarrow r_o = \infty$



$$I_c = I_S e^{\frac{V_{EB}}{V_T}} \Rightarrow I_c = 5 \times 10^{-17} e^{\frac{0.8}{0.026}} \Rightarrow \boxed{I_c = 1.15 \text{ mA}}$$

$$V_x = R_c I_c = 0.5 \times 1.15 \text{ mA} \Rightarrow \boxed{V_x = 0.58 \text{ V}}$$

b)  $V_A = 6 \text{ V}$

$$I_c = I_S e^{\frac{V_{EB}}{V_T}} \left( 1 + \frac{V_{EC}}{V_A} \right), \quad V_{EC} = V_{CC} - R_c I_c$$

$$\Rightarrow I_c = I_S e^{\frac{V_{EB}}{V_T}} \left( 1 + \frac{V_{CC} - R_c I_c}{V_A} \right)$$

$$\Rightarrow I_c = I_S e^{\frac{V_{EB}}{V_T}} \left( 1 + \frac{V_{CC}}{V_A} \right) - \frac{I_S R_c}{V_A} e^{\frac{V_{EB}}{V_T}} I_c$$

$$\Rightarrow \boxed{I_c = \frac{I_S e^{\frac{V_{EB}}{V_T}} \left( 1 + \frac{V_{CC}}{V_A} \right)}{1 + \frac{I_S R_c}{V_A} e^{\frac{V_{EB}}{V_T}}} = \frac{5 \times 10^{-17} e^{\frac{0.8}{0.026}} \left( 1 + \frac{2.5}{6} \right)}{1 + \frac{5 \times 10^{-17} \times 0.5}{6} e^{\frac{0.8}{0.026}}}}$$

$$\Rightarrow \boxed{I_c = 1.49 \text{ mA}} \quad V_x = R_c I_c = 500 \times 1.49 \times 10^{-3} \Rightarrow \boxed{V_x = 0.745 \text{ V}}$$

$$(46) \quad r_o = 60 \text{ k}\Omega, \quad I_C = 2 \text{ mA}$$

$$r_o = \frac{V_A}{I_C} \Rightarrow 60 \times 10^3 \Omega = \frac{V_A}{2 \times 10^{-3} \text{ A}} \Rightarrow \boxed{V_A = 120 \text{ V}}$$

$$\textcircled{47} \quad r_o = 60 \text{ k}\Omega, \quad I_C = 1 \text{ mA}$$

$$r_o = \frac{V_A}{I_C} \Rightarrow \boxed{V_A = r_o \cdot I_C} \Rightarrow \boxed{V_A \propto I_C}$$


$$\Rightarrow V_A = 60 \text{ k}\Omega \times 1 \text{ mA}$$

$$\Rightarrow \boxed{V_A = 60 \text{ V}}$$

$V_A$  is half the value in <sup>problem</sup> 46 as  $V_A$  is proportional to  $I_C$ .

48)  $V_A = 5\text{V}$

a) At the edge of active mode

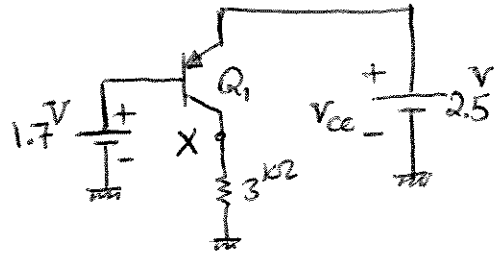

$$\Rightarrow \boxed{V_X = V_B = 1.7\text{V}}$$

$$I_C = \frac{V_X}{R_C} = \frac{1.7\text{V}}{3\text{k}\Omega} \Rightarrow \boxed{I_C \approx 0.567\text{mA}}$$

$$I_C = I_S e^{\frac{V_{BE}}{V_T}} \left(1 + \frac{V_{CE}}{V_A}\right) \Rightarrow \boxed{I_S = \frac{I_C e^{-\frac{V_{BE}}{V_T}}}{1 + \frac{V_{CE}}{V_A}}}$$

$$I_S = \frac{0.567 \times 10^{-3} e^{-\frac{800}{26}}}{1 + \frac{2.5 - 1.7}{5}} \Rightarrow \boxed{I_S \approx 2.118 \times 10^{-17}\text{A}}$$

b)  $V_A = \infty$

$$I_C = I_S e^{\frac{V_{BE}}{V_T}} \Rightarrow \boxed{I_S = I_C e^{-\frac{V_{BE}}{V_T}}}$$

$$I_S = 0.567 \times 10^{-3} e^{-\frac{800}{26}} \Rightarrow \boxed{I_S \approx 2.457 \times 10^{-17}\text{A}}$$


$I_S$  increases

④ The direction of currents in large-signal model shows how currents would flow when the PNP transistor is properly DC biased.

The direction of currents in small-signal model shows how the AC currents flow when AC voltage across Base-Emitter increases.

⑤  $I_S = 6 \times 10^{-16} \text{ A}$ ,  $V_A = 5 \text{ V}$ ,  $I_1 = 2 \text{ mA}$

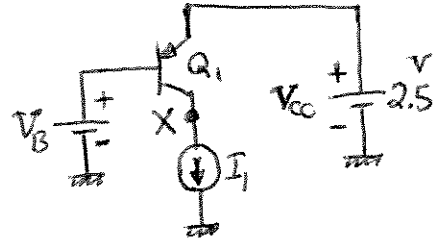a)  $I_C = I_S e^{\frac{V_{EB}}{V_T}} \left( 1 + \frac{V_{EC}}{V_A} \right)$



$\Rightarrow V_{EB} = V_T \ln \left( \frac{I_C}{I_S \left( 1 + \frac{V_{EC}}{V_A} \right)} \right)$

$V_{EC} = V_{CC} - V_X$   
 $V_{EB} = V_{CC} - V_B$

$$V_B = V_{CC} - V_T \ln \left( \frac{I_C}{I_S \left( 1 + \frac{V_{CC} - V_X}{V_A} \right)} \right)$$

$\Rightarrow V_B = 2.5 - 0.026 \ln \left( \frac{2 \times 10^{-3}}{6 \times 10^{-16} \left( 1 + \frac{2.5 - 1}{5} \right)} \right) \Rightarrow V_B \approx 1.757 \text{ V}$

b)  $I_C = I_S e^{\frac{V_{EB}}{V_T}} \left( 1 + \frac{V_{EC}}{V_A} \right) \Rightarrow 1 + \frac{V_{EC}}{V_A} = \frac{I_C}{I_S} e^{-\frac{V_{EB}}{V_T}}$

$V_{EC} = V_{CC} - V_X$   
 $V_{EB} = V_{CC} - V_B$

$$V_X = V_{CC} - V_A \left( \frac{I_C}{I_S} e^{-\frac{V_{EB}}{V_T}} - 1 \right)$$

$\Delta V_X \approx \frac{dV_X}{dV_{EB}} \Delta V_{EB} \Rightarrow \Delta V_X \approx \frac{V_A}{V_T} \cdot \frac{I_C}{I_S} e^{-\frac{V_{EB}}{V_T}} \Delta V_{EB}$


$\Delta V_{EB} = -\Delta V_B$

$$\Delta V_X \approx -\frac{V_A}{V_T} \cdot \frac{I_C}{I_S} e^{-\frac{V_{EB}}{V_T}} \Delta V_B$$

$\Rightarrow \Delta V_X \approx -\frac{5}{0.026} \times \frac{2 \times 10^{-3}}{6 \times 10^{-16}} \exp \left( -\frac{2.5 - 1.757}{0.026} \right) \times 0.1 \times 10^{-3} \Rightarrow \Delta V_X \approx -24.9 \text{ mV}$

50) Continued .....

c)

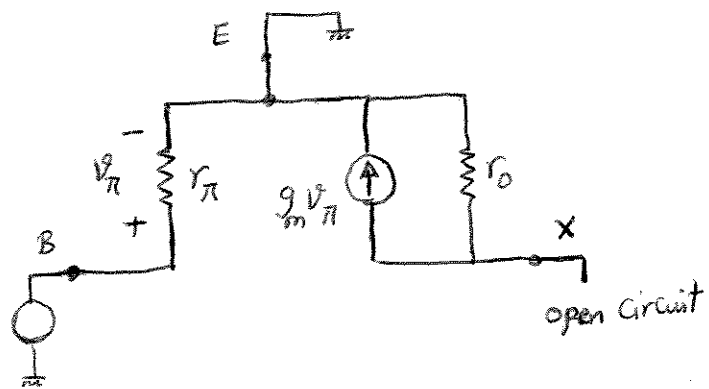


$$r_o = \frac{V_A}{I_C} = \frac{5\text{V}}{2\text{mA}} \Rightarrow \boxed{r_o \approx 2.5\text{ k}\Omega}$$

$$g_m = \frac{I_C}{V_T} = \frac{2\text{mA}}{0.026\text{V}} \Rightarrow \boxed{g_m \approx 76.9\text{ mS}}$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{\frac{2}{26}} \Rightarrow \boxed{r_{\pi} = 1.3\text{ k}\Omega}$$

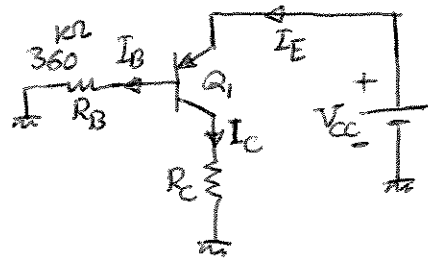⑤  $\beta = 100, V_A = \infty \Rightarrow r_o = \infty$   
 $R_B = 360 \text{ k}\Omega$



a) given:  $V_C = V_B + 0.2 \text{ V}$

$$\Rightarrow R_C I_C = R_B I_B + 0.2 \text{ V}$$

$$\Rightarrow R_C I_C = R_B \frac{I_C}{\beta} + 0.2 \text{ V} \Rightarrow \boxed{I_C = \frac{0.2 \text{ V}}{R_C - \frac{R_B}{\beta}}} \Rightarrow \boxed{I_C = 0.5 \text{ mA}}$$

$$I_C = I_S e^{+\frac{V_{EB}}{V_T}} \Rightarrow I_S = I_C e^{-\frac{V_{EB}}{V_T}} \Rightarrow I_S = I_C e^{-\left(\frac{V_{CC} - R_B I_B}{V_T}\right)}$$

$$\Rightarrow \boxed{I_S = \left(\frac{0.2}{R_C - \frac{R_B}{\beta}}\right) \exp\left[-\frac{1}{V_T} \left(V_{CC} - R_B \times \frac{0.2 \text{ V}}{\beta \left(R_C - \frac{R_B}{\beta}\right)}\right)\right]}$$

$$\Rightarrow \boxed{I_S \approx 10^{-15} \text{ A} = 1 \text{ fA}}$$

b)  $g_m = \frac{I_C}{V_T}$

$$\Rightarrow \boxed{g_m = \frac{0.2 \text{ V}}{V_T \left(R_C - \frac{R_B}{\beta}\right)}} \Rightarrow \boxed{g_m \approx 19.23 \text{ mS}}$$



$$\textcircled{52} \quad I_S = 5 \times 10^{-16} \text{ A}, \quad \beta = 100, \quad V_A = \infty \Rightarrow r_o = \infty$$

$$\text{a) } V_{EB} = 0 \Rightarrow Q_1 \text{ is off} \quad I_C = 0$$

$$\text{b) } I_B = 0 \Rightarrow Q_1 \text{ is off}$$

$$\text{c) Applying KVL: } V_{CC} = V_{EB} + 1 \text{ k}\Omega \times I_C$$

$$\Rightarrow V_{EB} + 1 \text{ k}\Omega \times I_S e^{\frac{V_{EB}}{V_T}} \approx V_{CC} \Rightarrow V_{EB} + 5 \times 10^{-13} e^{\frac{V_{EB}}{26 \text{ mV}}} \approx 2.5 \text{ V}$$

$$\Rightarrow \boxed{V_{EB} \approx 751 \text{ mV}} \quad I_C = 5 \times 10^{-16} e^{\frac{0.751}{0.026}} \Rightarrow \boxed{I_C \approx 1.8 \text{ mA}}$$

With this current, transistor is saturated. Note  $V_B < V_C$  Always

$$\text{d) } V_{BC} = 0 \Rightarrow \text{Transistor is at the edge of saturation}$$

$$\text{e) } I_C \approx 0.5 \text{ mA} \Rightarrow V_{EB} = V_T \ln\left(\frac{I_C}{I_S}\right) = 26 \text{ mV} \ln\left(\frac{0.5 \text{ mA}}{5 \times 10^{-16}}\right)$$

$$\Rightarrow \boxed{V_{EB} \approx 718 \text{ mV}}$$

$$V_{\text{collector}} = 500 \Omega \times I_C \Rightarrow \boxed{V_C = 0.25 \text{ V}}$$

As  $V_B = 0$ ,  $V_C = 0.25 \text{ V} \Rightarrow$  Transistor is soft saturated


53)  $I_{S1} = 3I_{S2} = 5 \times 10^{-16} \text{ A}$ ,  $\beta_1 = 100$ ,  $\beta_2 = 50$ ,  $V_A = \infty \Rightarrow r_o = \infty$

a)  $V_{B2} = 0 \text{ V}$   $\xrightarrow{\text{BC } Q_2 \text{ Forward Bias by } 200 \text{ mV max}}$   $V_{C2} = 0.2 \text{ V max}$

$\Rightarrow I_{C2 \text{ max}} = \frac{V_{C2 \text{ max}}}{R_C} = \frac{0.2 \text{ V}}{500 \Omega}$

$\Rightarrow \boxed{I_{C2 \text{ max}} = 0.4 \text{ mA}}$

As shown  $I_{C1} = I_{C2}$

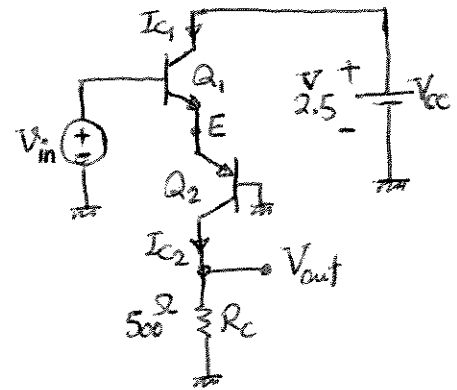

$V_{in \text{ max}} = V_{BE1 \text{ max}} + V_{EB2 \text{ max}} = V_T \ln \frac{I_{C1 \text{ max}}}{I_{S1}} + V_T \ln \frac{I_{C2 \text{ max}}}{I_{S2}}$

$\Rightarrow V_{in \text{ max}} = 26 \text{ mV} \cdot \left[ \ln \frac{0.4 \times 10^{-3}}{5 \times 10^{-16}} + \ln \frac{0.4 \times 10^{-3}}{\frac{5}{3} \times 10^{-16}} \right] \Rightarrow \boxed{V_{in \text{ max}} = 1.454 \text{ V}}$

b)  $g_{m1} = \frac{I_{C1}}{V_T} = \frac{0.4 \text{ mA}}{26 \text{ mV}}$


$g_{m2} = \frac{I_{C2}}{V_T} = \frac{0.4 \text{ mA}}{26 \text{ mV}}$

$\Rightarrow \boxed{g_{m1} = g_{m2} \approx 15.4 \text{ mS}}$

$r_{\pi 1} = \frac{\beta_1}{g_{m1}} = \frac{100}{\frac{0.4}{26}} \Rightarrow \boxed{r_{\pi 1} = 6.5 \text{ k}\Omega}$

$r_{\pi 2} = \frac{\beta_2}{g_{m2}} = \frac{50}{\frac{0.4}{26}} \Rightarrow \boxed{r_{\pi 2} = 3.25 \text{ k}\Omega}$

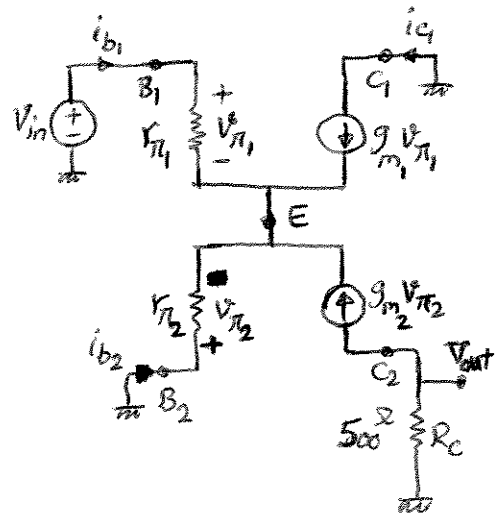
$V_A = \infty \Rightarrow \boxed{r_o = \infty}$



54)  $I_{S1} = 3I_{S2} = 5 \times 10^{-16} \text{ A}$ ,  $\beta_1 = 100$ ,  $\beta_2 = 50$ ,  $V_A = \infty$

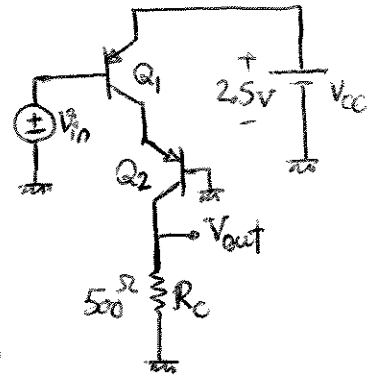a)  $V_{B2} = \phi$   $\xrightarrow[\text{Forward biased by } 200\text{mV}]{Q_2 \text{ Base-Collector}}$   $V_{C2} = 0.2 \text{ V}$

$\Rightarrow I_{C2} = \frac{V_{C2\text{max}}}{R_c} = \frac{0.2 \text{ V}}{500 \Omega} \Rightarrow \boxed{I_{C2} = 0.4 \text{ mA}_{\text{max}}}$



As shown:  $I_{C1} \approx I_{C2}$  (Note:  $I_{C1} = I_{E2} = \frac{\beta_2 + 1}{\beta_2} I_{C2}$  precisely)

$I_{C1} \approx I_{S1} e^{\frac{V_{EB1}}{V_T}} \Rightarrow V_{EB1} = V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right) \Rightarrow V_{CC} - V_{in} = V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right)$


$\Rightarrow \boxed{V_{in} = V_{CC} - V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right)} \Rightarrow V_{in} = 2.5 - 0.026 \ln\left(\frac{4 \times 10^{-4}}{5 \times 10^{-16}}\right)$

$\Rightarrow \boxed{V_{in} = 1.787 \text{ V}}$  This is minimum acceptable  $V_{in}$

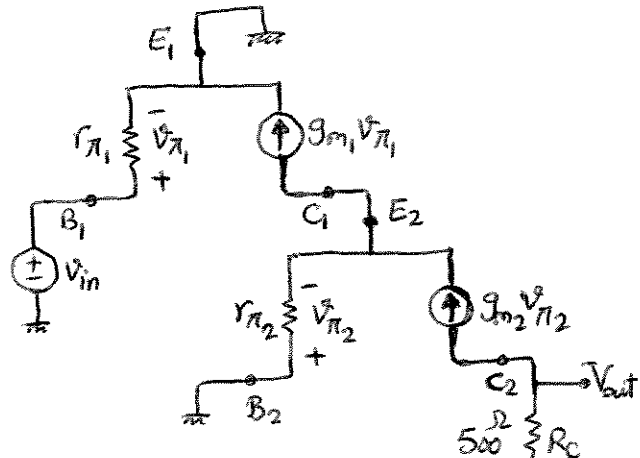b)  $g_{m1} = \frac{I_{C1}}{V_T} \approx \frac{0.4 \text{ mA}}{26 \text{ mV}}$

$g_{m2} = \frac{I_{C2}}{V_T} = \frac{0.4 \text{ mA}}{26 \text{ mV}}$

$\Rightarrow \boxed{g_{m1} = g_{m2} \approx 15.4 \text{ mS}}$



$r_{\pi 1} = \frac{\beta_1}{g_{m1}} = \frac{100}{\frac{0.4}{26}} \Rightarrow \boxed{r_{\pi 1} = 6.5 \text{ k}\Omega}$


$r_{\pi 2} = \frac{\beta_2}{g_{m2}} = \frac{50}{\frac{0.4}{26}} = \boxed{3.25 \text{ k}\Omega}$

$V_{EB2} = V_T \ln\left(\frac{I_{C2}}{I_{S2}}\right) = 26 \text{ mV} \ln\left(\frac{0.4 \times 10^{-3}}{5 \times 10^{-16}}\right) \Rightarrow \boxed{V_{EB2} \approx 741 \text{ mV}} \Rightarrow \boxed{V_{EC1} \approx 1.759 \text{ V}}$

$Q_1$  in active mode

55)  $I_{S1} = 3I_{S2} = 5 \times 10^{-16} \text{ A}$ ,  $\beta_1 = 100$ ,  $\beta_2 = 50$ ,  $V_A = \infty$

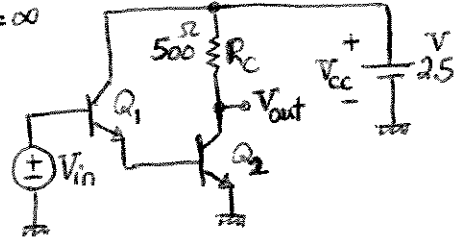a)  $Q_2$  is softly saturated  $\Rightarrow V_{BC_2} = 0.2 \text{ V}$



$$V_{BC_2} = 0.2 \text{ V} \Rightarrow V_{B_2} - V_{C_2} = 0.2 \text{ V} \Rightarrow V_{BE_2} - (V_{CC} - R_C I_{C_2}) = 0.2 \text{ V}$$

$$\Rightarrow V_{BE_2} + R_C I_{S_2} e^{\frac{V_{BE_2}}{V_T}} = V_{CC} + 0.2$$

$$\Rightarrow V_{BE_2} + 500 \times \frac{5}{3} \times 10^{-16} e^{\frac{V_{BE_2}}{V_T}} = 2.5 + 0.2 \Rightarrow \boxed{V_{BE_2} \approx 800 \text{ mV}}$$

$$V_{BE_1} = V_T \ln\left(\frac{I_{C_1}}{I_{S_1}}\right) \quad I_{C_2} = I_{S_2} e^{\frac{V_{BE_2}}{V_T}} = \frac{5}{3} \times 10^{-16} e^{\frac{800}{26}} \Rightarrow \boxed{I_{C_2} \approx 3.8 \text{ mA}}$$

$$V_{BE_1} = V_T \ln\left(\frac{I_{C_2}/\beta_2}{I_{S_1}}\right) = 26 \text{ mV} \ln\left(\frac{3.8 \times 10^{-3}}{50 \times 5 \times 10^{-16}}\right) \Rightarrow \boxed{V_{BE_1} \approx 669.4 \text{ mV}}$$

$$V_{in} = V_{BE_1} + V_{BE_2} \Rightarrow \boxed{V_{in} = 1.469 \text{ V}} \text{ Maximum allowable value for } V_{in}$$

b)


$$g_{m_1} = \frac{I_{C_1}}{V_T} = \frac{I_{C_2}/\beta_2}{V_T} = \frac{3.8 \text{ mA}}{26 \text{ mV}}$$

$$\Rightarrow \boxed{g_{m_1} \approx 2.9 \text{ mS}}$$

$$g_{m_2} = \frac{I_{C_2}}{V_T} = \frac{3.8 \text{ mA}}{26 \text{ mV}} \Rightarrow \boxed{g_{m_2} \approx 146 \text{ mS}}$$

$$r_{\pi_1} = \frac{\beta_1}{g_{m_1}} = \frac{100}{2.9 \times 10^{-3}} \Rightarrow \boxed{r_{\pi_1} \approx 3421 \Omega}$$
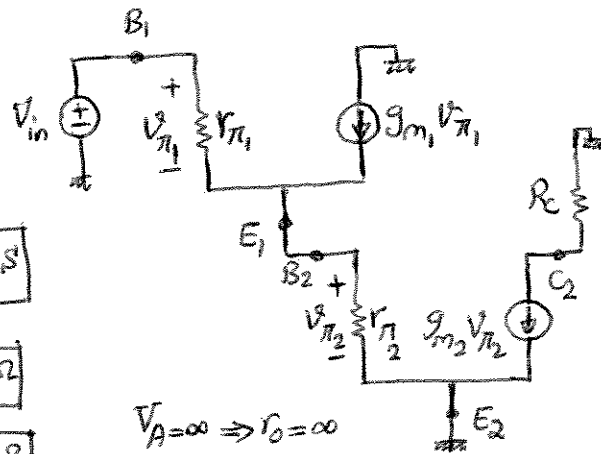
$$r_{\pi_2} = \frac{\beta_2}{g_{m_2}} = \frac{50}{146 \times 10^{-3}} \Rightarrow \boxed{r_{\pi_2} \approx 342 \Omega}$$




56)  $I_{S1} = 2I_{S2} = 6 \times 10^{-17} \text{ A}$ ,  $\beta_1 = 80$ ,  $\beta_2 = 100$

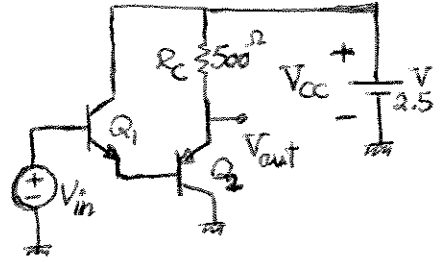a)  $I_{C2} = 2 \text{ mA}$

$$V_{EB2} = V_T \ln \frac{I_{C2}}{I_{S2}} = 26 \text{ mV} \ln \left( \frac{2 \times 10^{-3}}{3 \times 10^{-17}} \right) \approx 827.6 \text{ mV}$$

$$V_{BE1} = V_T \ln \frac{I_{C1}}{I_{S1}} = 26 \text{ mV} \ln \left( \frac{2 \times 10^{-3}}{6 \times 10^{-17}} \right) \approx 689.9 \text{ mV}$$



$$V_{in} = V_{CC} - R_C I_{C2} - V_{EB2} + V_{BE1} = 2.5 - 0.5 \times 2 - 0.8276 + 0.6899$$

$$\Rightarrow V_{in} = 1.362 \text{ V}$$

b)  $g_{m2} = \frac{I_{C2}}{V_T} = \frac{2 \text{ mA}}{26 \text{ mV}} \Rightarrow g_{m2} \approx 76.9 \text{ mS}$


$$g_{m1} = \frac{I_{C1}}{V_T} = \frac{2 \text{ mA}}{26 \text{ mV}} \Rightarrow g_{m1} \approx 76.9 \text{ mS}$$

$$r_{\pi 1} = \frac{\beta_1}{g_{m1}} = \frac{80}{1/1300}$$


$$\Rightarrow r_{\pi 1} = 104 \text{ k}\Omega$$

$$r_{\pi 2} = \frac{\beta_2}{g_{m2}} = \frac{100}{2/26} \Rightarrow r_{\pi 2} = 1300 \Omega$$
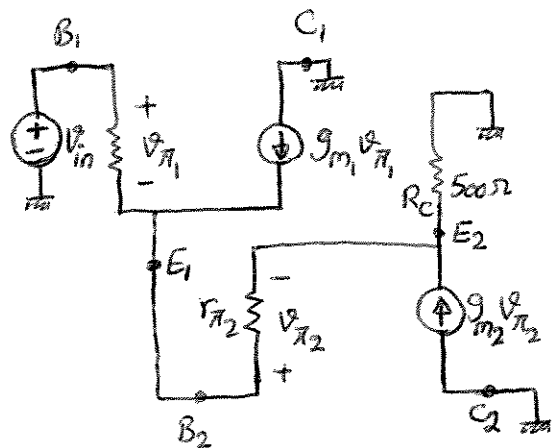
$$V_A = \infty \Rightarrow r_o = \infty$$




1)

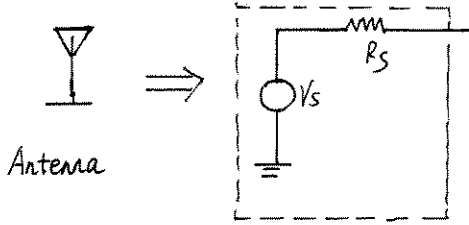

Thevenin Equivalent:

$$V_s = V_0 \cos \omega t$$

$$R_s = R_{out}$$

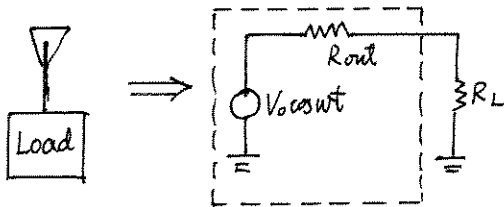

Average power delivered to load =  $(I_{RMS})^2 R_L$ ,

$$I_{RMS} = \frac{V_{RMS}}{R_{out} + R_L}, \quad V_{RMS} = \frac{V_0}{\sqrt{2}} \Rightarrow I_{RMS} = \frac{V_0}{\sqrt{2}(R_{out} + R_L)}$$

$$\text{Average power} = (I_{RMS})^2 R_L = \frac{V_0^2 R_L}{2(R_{out} + R_L)^2} \quad (\text{Eq. 1})$$

Plot of Average Power

When  $R_L$  is small, Eq. 1 is small.

When  $R_L$  is large, Eq. 1 is also small.


So for some  $R_L$  between zero and infinity, the average power will reach its peak. Let's take the derivative of Eq. 1 with respect to  $R_L$  to find the optimum  $R_L$ .

$$\frac{\partial}{\partial R_L} \left[ \frac{V_0^2 R_L}{2(R_{out} + R_L)^2} \right] = \frac{V_0^2}{2(R_{out} + R_L)^2} - \frac{V_0^2 R_L}{(R_{out} + R_L)^3}$$


Setting it to zero and solve for  $R_L$

$$\frac{V_0^2}{2(R_{out} + R_L)^2} = \frac{V_0^2 R_L}{(R_{out} + R_L)^3} \Rightarrow \frac{(R_{out} + R_L)}{2} = R_L$$

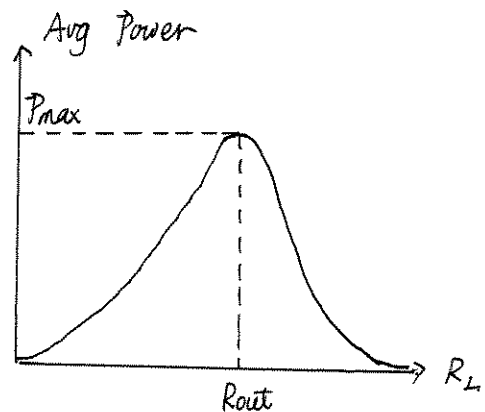
$$\Rightarrow R_{out} + R_L = 2R_L \Rightarrow R_L = R_{out}$$



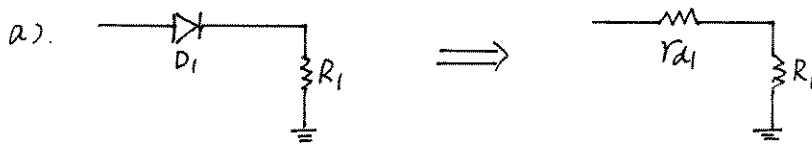
2) In small signal operation, a diode can be replaced by a linear resistor if charges are small.



$$R_{in} = r_{d1} + R_1$$

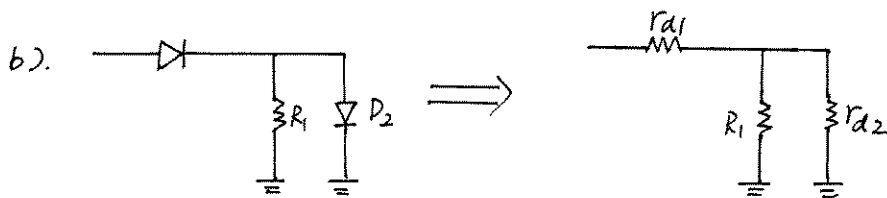

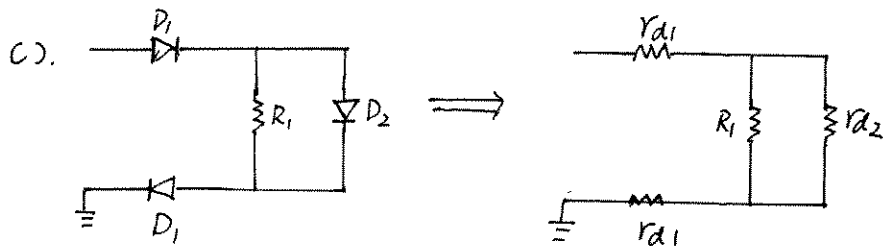
$$R_{in} = r_{d1} + R_1 // r_{d2} \quad ( // \text{ means in parallel } )$$





$$R_{in} = 2r_{d1} + R_1 // r_{d2}$$

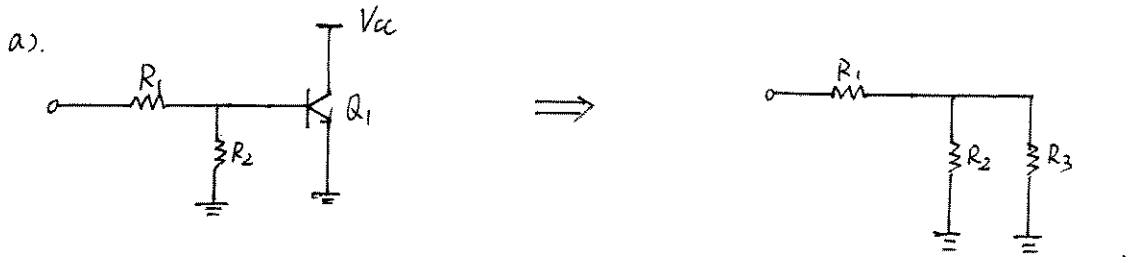3). When  $V_A = \infty$ ,  $V_o = \infty$ .





Replacing  $Q_1$  by its equivalent resistance seen at base

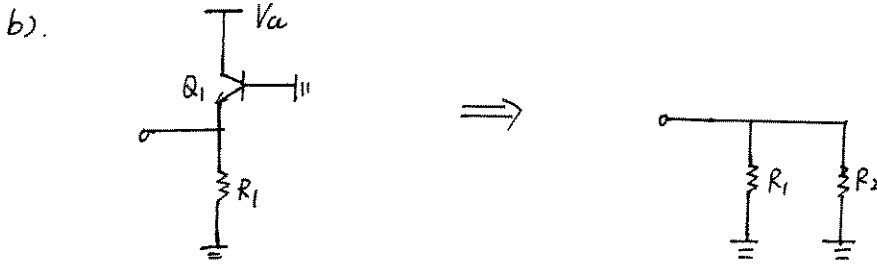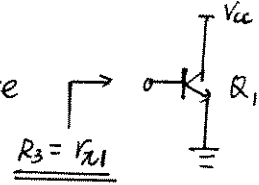So  $R_{in} = R_1 + R_2 \parallel R_3 = R_1 + R_2 \parallel r_{\pi 1}$




Replacing  $Q_1$  by its equivalent resistance seen at emitter

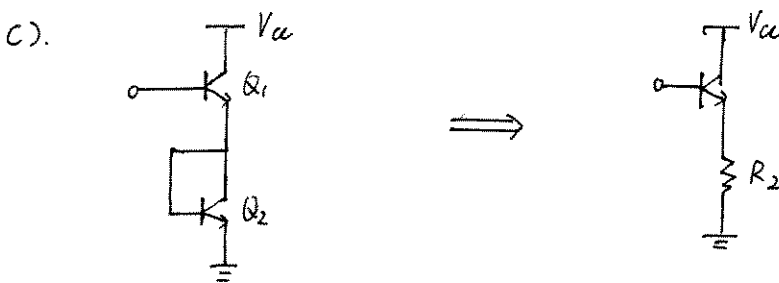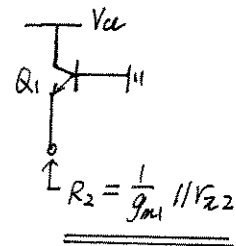So  $R_{in} = R_1 \parallel R_2 = r_{in} \parallel (\frac{1}{g_{m1}} \parallel r_{\pi 1})$



Replacing  $Q_2$  by its equivalent diode-connected resistance

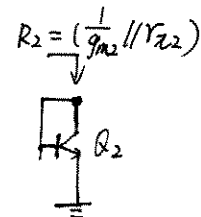
So  $R_{in} = r_{\pi 1} + (1 + \beta)R_2 = r_{\pi 1} + (1 + \beta)(\frac{1}{g_{m2}} \parallel r_{\pi 2})$






3).

d).

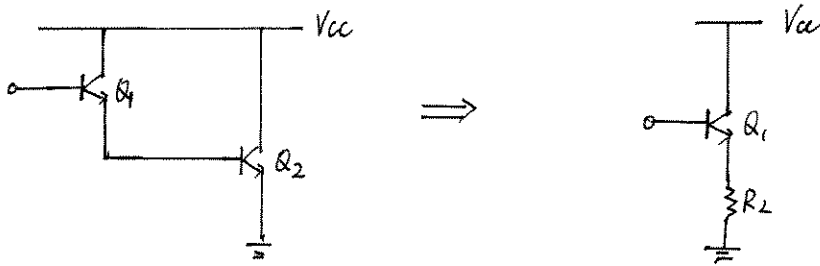

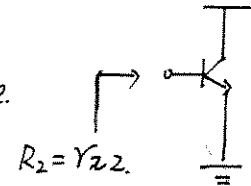Replacing  $Q_2$  by its equivalent resistance seen at base.



$$\text{So } R_{in} = r_{\pi 1} + (1 + \beta) R_2 = r_{\pi 1} + (1 + \beta) r_{z2}.$$

(Please refer to the textbook for all the equivalent resistances.)


4). Since the problem doesn't say  $V_A = \infty$ ,  $r_o$  must be considered in derivation.

a). Short  $V_B$  since it's a DC source, and replace  $Q_1$  with an ideal transistor with its output resistance.



$$So R_{out} = R_1 \parallel r_o \parallel \infty = R_1 \parallel r_o$$


b).

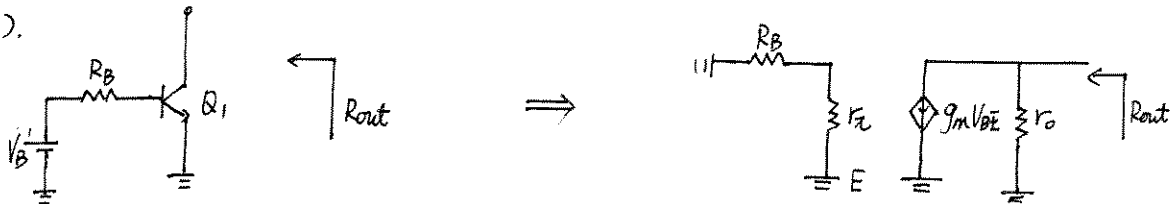

By drawing the small-signal model, it's easy to tell  $V_{BE} = 0$  and  $R_{out} = r_o$

c). Replace  $Q_1$  with an ideal transistor and an output impedance  $r_{o1}$ .

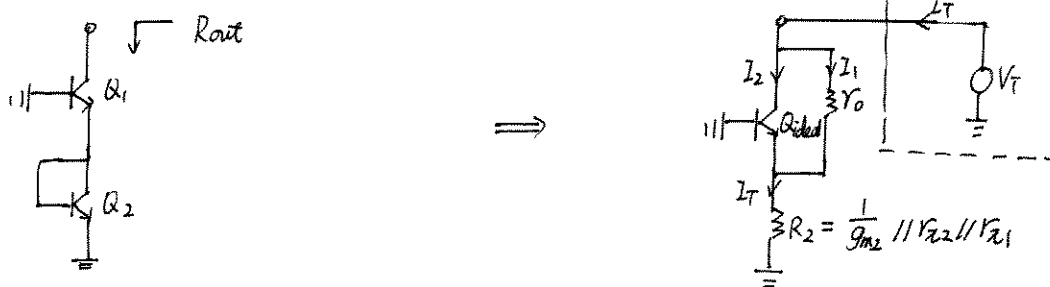Replace  $Q_2$  with a resistor  $\frac{1}{g_{m2}} \parallel r_{e2} \parallel r_{e1}$



Here,  $r_{e1}$  is included in  $R_2$  because it is also connected from emitter to ground and it accounts for the base current of  $Q_1$ .

$$4) I_1 = \frac{V_T - I_T R_2}{r_o}, \quad I_2 = g_{m1} (0 - I_T R_2)$$

$$I_T = I_1 + I_2 = \frac{V_T - I_T R_2}{r_o} - g_{m1} I_T R_2$$

$$\Rightarrow I_T + \frac{I_T R_2}{r_o} + g_{m1} I_T R_2 = \frac{V_T}{r_o}$$

$$\Rightarrow \frac{V_T}{I_T} = r_o \left( 1 + \frac{R_2}{r_o} + g_{m1} R_2 \right)$$

$$\Rightarrow R_{out} = \frac{V_T}{I_T} = r_o (1 + g_{m1} R_2) + R_2$$


$$= r_o \left[ 1 + g_{m1} \left( \frac{1}{g_{m2} \parallel r_{\alpha 2} \parallel r_{\alpha 1}} \right) \right] + \frac{1}{g_{m2} \parallel r_{\alpha 2} \parallel r_{\alpha 1}}$$

Usually  $\frac{1}{g_m} \ll r_{\alpha 2}$ , and if  $\alpha_1 = \alpha_2$

$$R_{out} \approx \frac{1}{g_m} + 2r_o$$


5).  $V_A = \infty, r_o = \infty$

a).

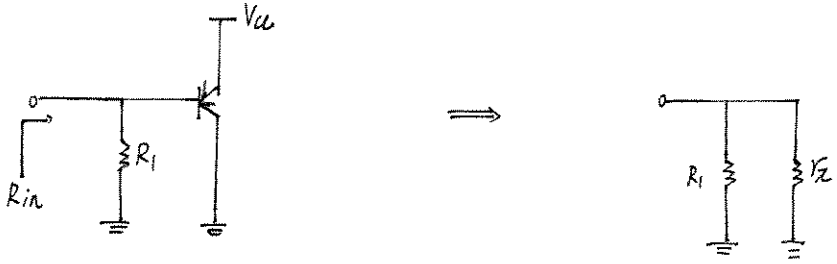


$$R_{in} = R_1 \parallel R_{E1}$$

b).

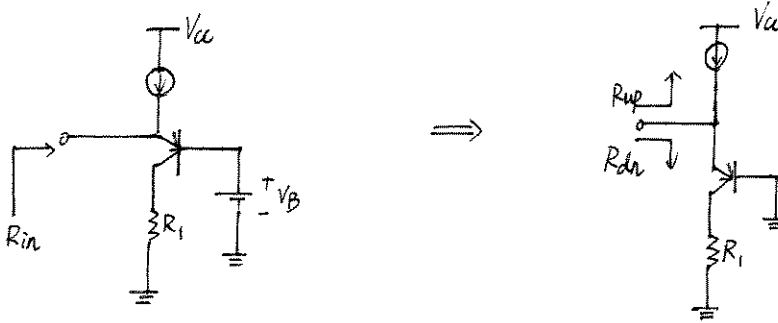

$$R_{in} = R_{up} \parallel R_{dn}, \quad R_{up} = \infty, \text{ since a DC current source is open.}$$

Finding  $R_{dn}$ :

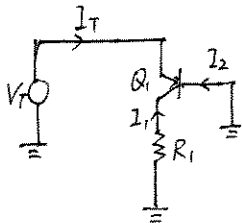

$$I_T = -(I_1 + I_2)$$

$$I_1 = g_m (0 - V_T) = -g_m V_T$$

$$I_2 = \frac{I_1}{\beta}$$



$$\text{So } I_T = -(-g_m V_T - \frac{g_m V_T}{\beta}) = (g_m + \frac{g_m}{\beta}) V_T$$

$$\frac{V_T}{I_T} = \frac{1}{(g_m + \frac{g_m}{\beta})} = \frac{1}{g_m} \parallel R_E$$


$$R_{dn} = \frac{V_T}{I_T} = \frac{1}{g_m} \parallel R_E$$

$$\text{So } R_{in} = R_{up} \parallel R_{dn} = \infty \parallel \frac{1}{g_m} \parallel R_E = \frac{1}{g_m} \parallel R_E$$

5) c)

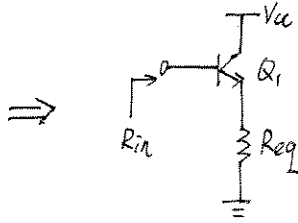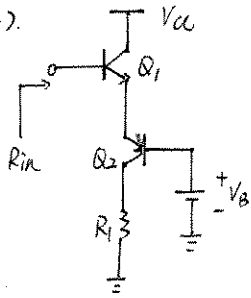




From b), we know that

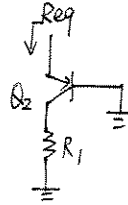

$$R_{eq} = \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

$$\text{So } R_{in} = r_{\pi 1} + (1 + \beta) R_{eq} = r_{\pi 1} + (1 + \beta) \left( \frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$


d)

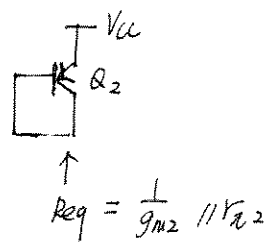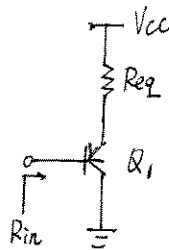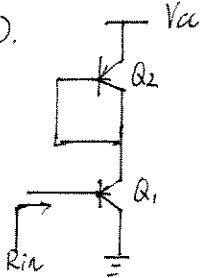

$$R_{eq} = \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

$$R_{in} = r_{\pi 1} + (1 + \beta) R_{eq} = r_{\pi 1} + (1 + \beta) \left( \frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$


e)

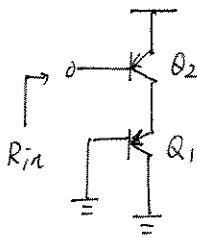


$R_{in} = r_{\pi 2}$ .  $Q_1$  plays no role here since it's connected to the collector of  $Q_2$ .

It can not be seen from the base of  $Q_2$ .

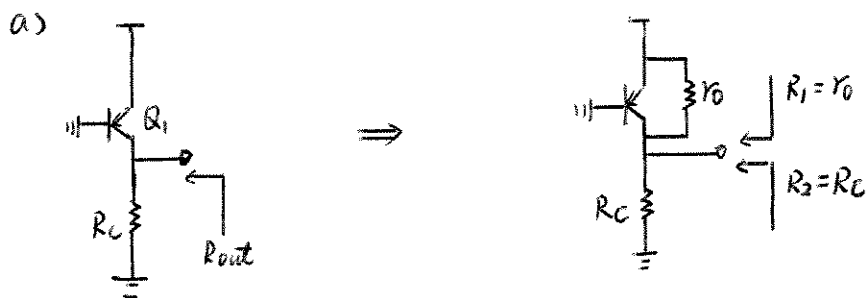b) Since the problem doesn't state  $V_A = \infty$ ,  $r_o$  is not  $\infty$ .



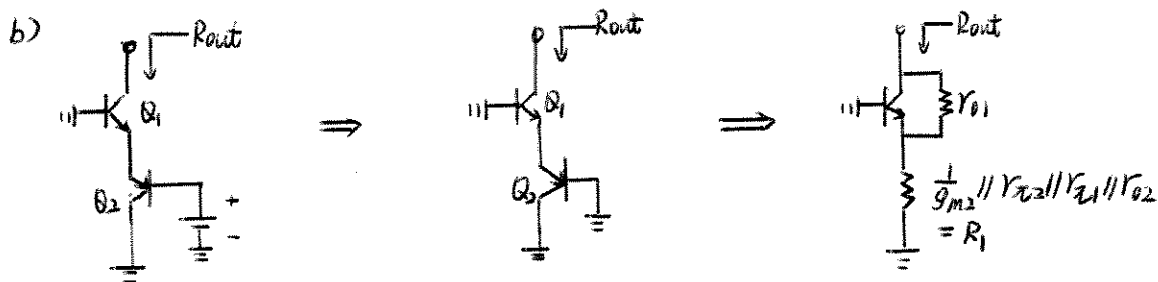
$$R_{out} = R_1 \parallel R_2 = R_C \parallel r_o$$



As shown in problem 4) c).

$$R_{out} = R_1 + r_{o1} + g_{m2} r_{o1} R_1 = r_{o1} + (1 + g_{m2} r_{o1}) R_1$$
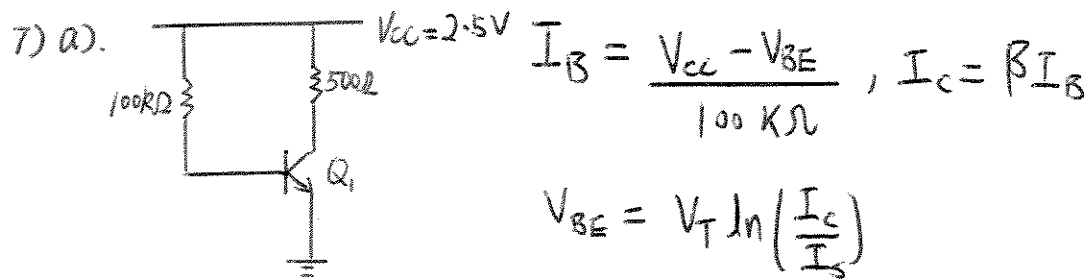
$$= r_{o1} + (1 + g_{m2} r_{o1}) \left( \frac{1}{g_{m2}} \parallel r_{o2} \parallel r_{e1} \parallel r_{o2} \right)$$



Guess  $V_{BE} = 0.7V$ ,

$$I = \beta \left( \frac{V_{CC} - V_{BE}}{100\text{ k}\Omega} \right) = 1.8\text{ mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.747\text{ V, not } 0.7\text{ V, reiterate}$$

$$V_{BE} = 0.747\text{ V, } I_C = 1.753\text{ mA}$$

$$\text{Verify } V_{BE}, \quad V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.746\text{ V, converged}$$

$$V_{CE} = 2.5 - (1.753)(0.5\text{ k}) = 1.62\text{ V}$$

$V_{CE} > V_{BE}$ ,  $Q_1$  in forward active region.

$$I_C = 1.754\text{ mA}$$


$$V_{CE} = 1.62\text{ V}$$

$$I_B = 17.54\text{ }\mu\text{A}$$

$$V_{BE} = 0.746\text{ V}$$

↑  
operating point

7). b).

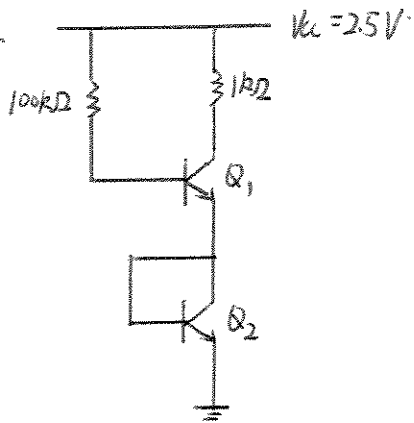

$$I_{B1} = \frac{2.5 - (V_{BE1} + V_{BE2})}{100k\Omega}$$

$$I_{C1} = \beta I_{B1}$$

$$V_{BE1} = V_T \ln\left(\frac{I_{C1}}{I_S}\right), \quad V_{BE2} = V_T \ln\left(\frac{I_{C2}}{I_S}\right)$$

Assume  $V_{BE1} = V_{BE2} = 0.8V$

$$I_{C1} = \beta \left( \frac{2.5 - 1.6}{100k} \right) = 0.9mA$$

$$V_{BE1} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.728V, \text{ not } 0.8V, \text{ reiterate}$$

$I_{C2} = 0.9mA$ , since  $\beta$ 's are the same

$$V_{BE2} = 0.728V$$

$$I_{C1} = \beta \left( \frac{2.5 - (2)(0.728)}{100k\Omega} \right) = 1.042mA = I_{C2}$$

$$V_{BE1} = V_{BE2} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.733V, \text{ iterate once more}$$

$$I_{C1} = I_{C2} = \beta \left( \frac{2.5 - (2)(0.733)}{100k\Omega} \right) = 1.034mA$$



7) b)

$$I_{c1} = I_2 = 1.034 \text{ mA}$$

$$V_{BE1} = V_{BE2} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.733, \text{ converges.}$$

$$V_{CE1} = 2.5 - 0.733 - (1.034)(1 \text{ k}\Omega) = 0.733 \text{ V}$$

$V_{CE} = V_{BE}$ ,  $Q_2$  at the edge of active region.

$$V_{BE2} = V_{CE2} = 0.733 \text{ V}$$

operating point:

$$I_{c1} = 1.034 \text{ mA}$$

$$I_{B1} = 0.01 \text{ mA}$$

$$V_{BE1} = 0.733 \text{ V}$$

$$V_{CE1} = 0.733 \text{ V}$$

$$I_{c2} = 1.034 \text{ mA}$$


$$I_{B2} = 0.01 \text{ mA}$$

$$V_{BE2} = 0.733 \text{ V}$$

$$V_{CE2} = 0.733 \text{ V}$$

Although, for  $Q_2$   $V_{BE} = V_{CE}$ , it is at the edge of active region, the situation is not as severe as  $Q_1$ 's. Since  $Q_2$ 's configuration will always render  $V_{BE} = V_{CE}$ , whereas for  $Q_1$ ,  $V_{CE}$  may drop below  $V_{BE}$ .

7) c).

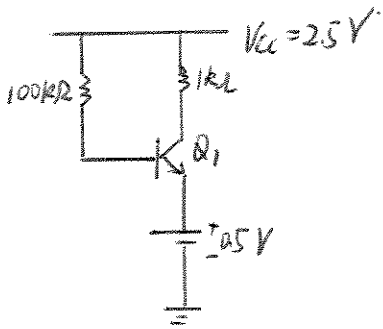

$$I_B = \frac{V_{cc} - (V_{BE} + 0.5)}{100k}$$

$$I_c = \beta I_B$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right)$$

Guess  $V_{BE} = 0.8V$ ,

$$I_c = \beta \left( \frac{2.5 - 1.3}{100k} \right) = 1.2mA$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.736V, \text{ not } 0.8, \text{ reiterate}$$

$$V_{BE} = 0.736V, \quad I_c = \beta \left( \frac{2.5 - (0.736 + 0.5)}{100k\Omega} \right) = 1.26mA$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.738V, \text{ converges.}$$



$$V_{CE} = (2.5 - 0.5) - (1.26)(1k\Omega) = 0.74$$

$V_{CE} > V_{BE}$ ,  $Q_1$  in forward active region

Operating point



$$I_c = 1.26mA \quad V_{BE} = 0.738V$$

$$I_B = 0.0126mA \quad V_{CE} = 0.74V$$

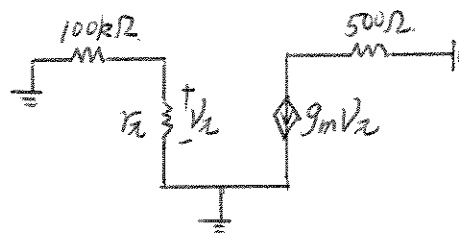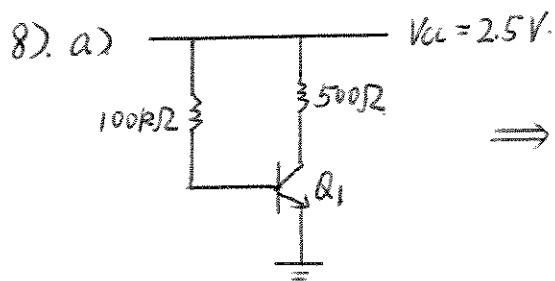

$$g_m = \frac{I_C}{V_T} = \frac{1.754mA}{26mV} = 0.0675 S$$
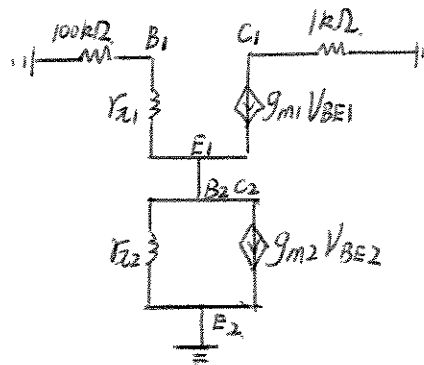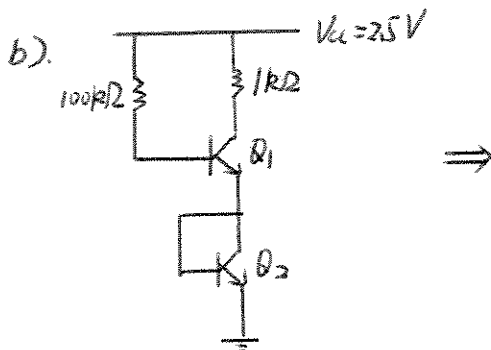
$$r_{\pi 1} = \frac{\beta}{g_m} = \frac{100}{0.0675} \Omega = 1482.3 \Omega$$





$$g_{m1} = \frac{I_{C1}}{V_T} = \frac{1.034mA}{26mV} = 0.04 S$$

$$r_{\pi 1} = \frac{\beta}{g_{m1}} = \frac{100}{0.04} \Omega = 2500 \Omega$$


$$g_{m2} = \frac{I_{C2}}{V_T} = \frac{1.034mA}{26mV} = 0.04 S$$
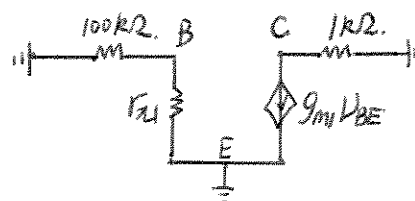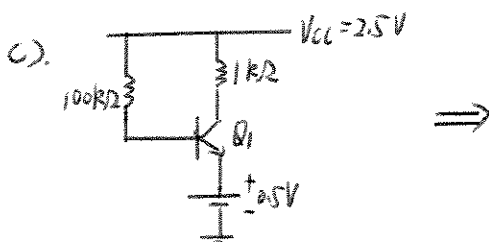
$$r_{\pi 2} = \frac{\beta}{g_{m2}} = \frac{100}{0.04} \Omega = 2500 \Omega$$



$$g_{m1} = \frac{I_C}{V_T} = \frac{1.26mA}{26mV} = 0.048 S$$
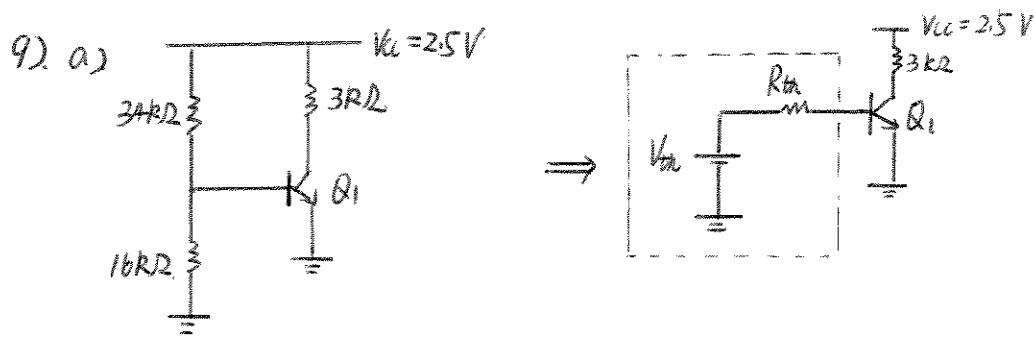
$$r_{\pi 1} = \frac{\beta}{g_{m1}} = \frac{100}{0.048} \Omega = 2083 \Omega$$



Thevenin Equivalent  $R_{th} = \frac{34 \times 16}{34 + 16} k\Omega = 10.88 k\Omega$

$$V_{th} = \frac{2.5V \times 16}{34 + 16} = 0.8V.$$

$$I_c = \beta \left( \frac{0.8 - V_{BE}}{10.88k} \right), \quad V_{BE} = V_T \ln \left( \frac{I_c}{I_s} \right)$$

Assume  $V_{BE} = 0.7,$

$$I_c = \beta \left( \frac{0.8 - 0.7}{10.88k\Omega} \right) = 0.92mA$$

$$V_{BE} = V_T \ln \left( \frac{I_c}{I_s} \right) = 0.734V$$

Iterate,  $V_{BE} = 0.734V$

$$I_c = \beta \left( \frac{0.8 - 0.734}{10.88k\Omega} \right) = 0.61mA$$

$$V_{BE} = V_T \ln \left( \frac{I_c}{I_s} \right) = 0.724V$$

Iterate,  $V_{BE} = 0.724V$

$$I_c = \beta \left( \frac{0.8 - 0.724}{10.88k\Omega} \right) = 0.699mA$$

9)

a)

$$I_c = 0.699 \text{ mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.727 \text{ V}$$

Iterate,

$$V_{BE} = 0.727 \text{ V}$$

$$I_c = \beta \left( \frac{0.8 - 0.727}{10.88 \text{ k}\Omega} \right) = 0.67 \text{ mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.726 \text{ V}, \text{ Converged!!}$$

$$V_{CE} = 2.5 - (0.67)(3 \text{ k}\Omega) = 0.49$$

$$V_{BE} - V_{CE} = 0.236 \text{ V}, \text{ Soft-saturation, still OK.}$$


Operating point:

$$I_c = 0.67 \text{ mA}$$

$$V_{BE} = 0.726 \text{ V}$$

$$I_B = 6.7 \mu\text{A}$$

$$V_{CE} = 0.49 \text{ V}$$

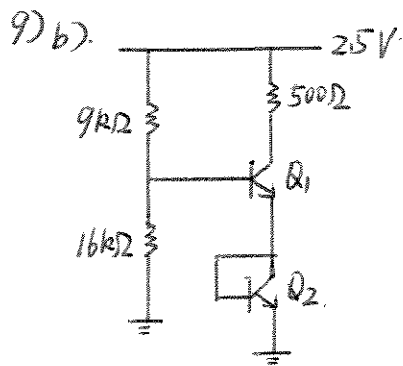


$$R_{th} = \frac{9 \times 16}{9 + 16} \text{ k}\Omega = 5.76 \text{ k}\Omega$$

$\Rightarrow$

$$V_{th} = 25 \text{ V} \times \frac{16}{9 + 16} = 1.6 \text{ V}$$

$\Downarrow$

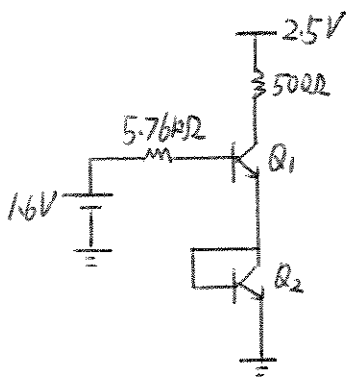

$$I_{C1} = \beta \left( \frac{1.6 - (V_{BE1} + V_{BE2})}{5.76 \text{ k}\Omega} \right)$$

$$V_{BE} = V_{BE1} = V_{BE2} = V_T \ln \left( \frac{I_C}{I_S} \right)$$

$$I_{C1} = I_{C2} = I_C$$

Guess  $V_{BE1} = V_{BE2} = 0.7 \text{ V}$

$$I_C = \beta \left( \frac{1.6 - 1.4}{5.76 \text{ k}\Omega} \right) = 3.47 \text{ mA}$$

$$V_{BE} = V_T \ln \left( \frac{I_C}{I_S} \right) = 0.769 \text{ V}$$

Iterate,  $V_{BE} = 0.769 \text{ V}$

$$I_C = \beta \left( \frac{1.6 - (2)(0.769)}{5.76 \text{ k}\Omega} \right) = 1.08 \text{ mA}$$

9)

b)

$$I_c = 1.08 \text{ mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.738 \text{ V}$$

Iterate,  $V_{BE} = 0.738 \text{ V}$

$$I_c = \beta \left( \frac{1.6 - 2(0.738)}{5.76 \text{ k}\Omega} \right) = 2.15 \text{ mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.756 \text{ V}$$

Iterate,  $V_{BE} = 0.756 \text{ V}$

$$I_c = \beta \left( \frac{1.6 - 2(0.756)}{5.76 \text{ k}\Omega} \right) = 1.53 \text{ mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.747 \text{ V}$$

Iterate... (for 3 more times)

$$V_{BE} = 0.75 \text{ V}, \quad I_c = 1.74 \text{ mA} \quad \text{converged}$$

$$V_{CE} = 2.5 - 0.75 - (1.74)(0.5) = 0.88 \text{ V}$$

Operating Point

$$I_{c1} = 1.74 \text{ mA}$$

$$I_{B1} = 17.4 \mu\text{A}$$

$$V_{BE} = 0.75 \text{ V} \quad (\text{Forward active})$$


$$V_{CE} = 0.88 \text{ V}$$

$$I_{c2} = 1.74 \text{ mA}$$

$$I_{B2} = 17.4 \mu\text{A}$$

$$V_{BE2} = 0.75 \text{ V} \quad (\text{Edge of forward active})$$

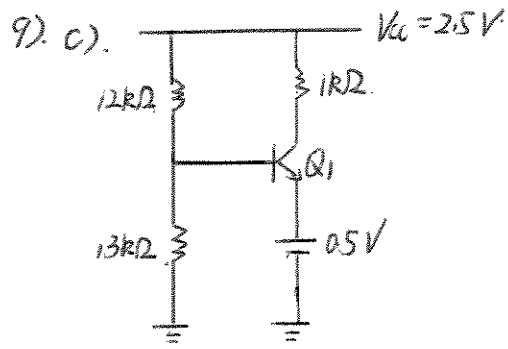
$$V_{CE2} = 0.75 \text{ V} \quad (\text{active})$$



$$V_{th} = 2.5V \times \frac{13}{12+13} = 1.3V$$

⇒
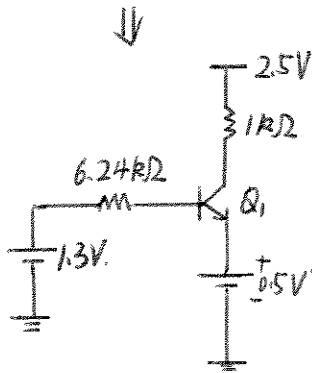
$$R_{th} = \frac{12 \times 13}{12+13} k\Omega = 6.24k\Omega$$



$$I_c = \beta \left( \frac{1.3 - (V_{BE} + 0.5)}{6.24k\Omega} \right)$$

$$V_{BE} = V_T \ln \left( \frac{I_c}{I_s} \right)$$

Guess  $V_{BE} = 0.743V$

$$I_c = \beta \left( \frac{1.3 - (0.743 + 0.5)}{6.24k\Omega} \right) = 0.913mA$$

$$V_{BE} = V_T \ln \left( \frac{I_c}{I_s} \right) = 0.734V$$

Iterate,  $V_{BE} = 0.734V$

$$I_c = \beta \left( \frac{1.3 - (0.734 + 0.5)}{6.24k\Omega} \right) = 1.06mA$$

$$V_{BE} = V_T \ln \left( \frac{I_c}{I_s} \right) = 0.738V$$



9)  
c)

Iterate,  $V_{BE} = 0.738V$

$$I_C = \beta \left( \frac{1.3 - (0.738 + 0.5)}{6.24k\Omega} \right) = 0.99mA$$

$$V_{BE} = V_T \ln \left( \frac{I_C}{I_S} \right) = 0.736V$$

$$V_{CE} = 2.5 - 0.5 - (0.99)(1k\Omega) = 1.01V$$

$V_{CE} > V_{BE} \Rightarrow$  Forward Active Region




operating point

$$I_C = 0.99mA$$

$$V_{BE} = 0.736V$$




$$I_B = 9.9\mu A$$

$$V_{CE} = 1.01V$$

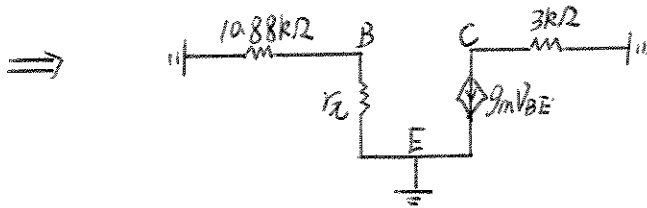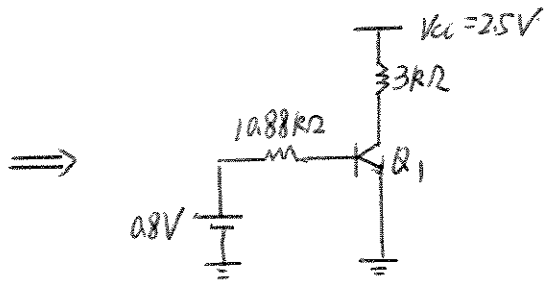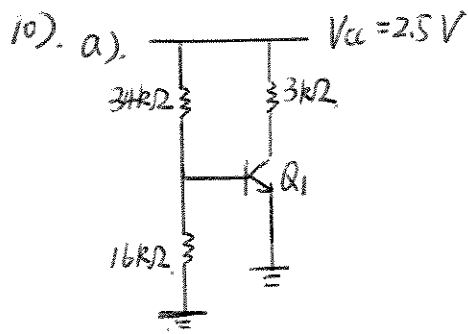

$$g_m = \frac{I_C}{V_T} = \frac{0.67mA}{26mV} = 0.026S$$
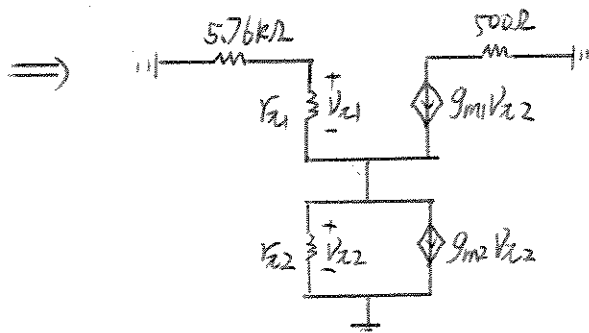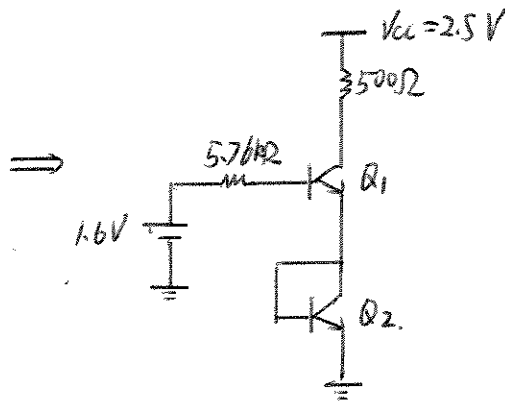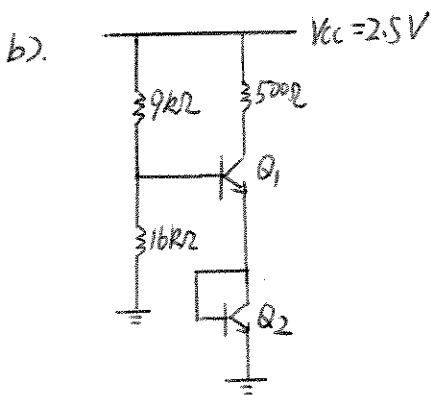
$$r_c = \frac{\beta}{g_m} = \frac{100}{0.026} \Omega = 3846\Omega$$




$$g_{m1} = \frac{1.74mA}{26mV} = 0.067S$$

$$r_{c1} = \frac{\beta_1}{g_{m1}} = 1494.3\Omega$$



$$g_{m2} = 0.067S$$

$$r_{c2} = 1494.3\Omega$$

10) c).

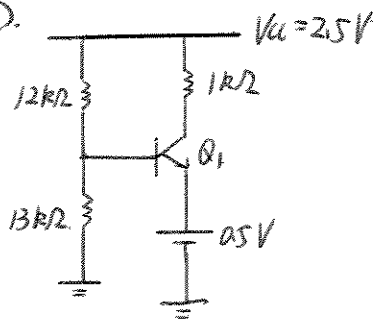


⇒

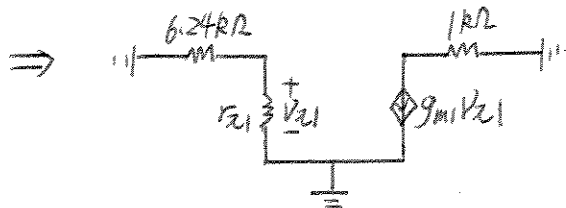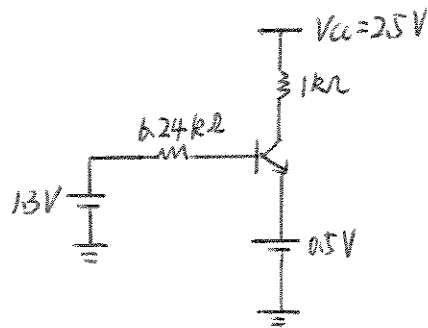

$$g_{m1} = \frac{I_C}{V_T} = \frac{0.99 \text{ mA}}{26 \text{ mV}} = 0.038 \text{ S}$$

$$r_{\pi 1} = \frac{\beta}{g_{m1}} = \frac{100}{0.038} \Omega = 2632 \Omega$$

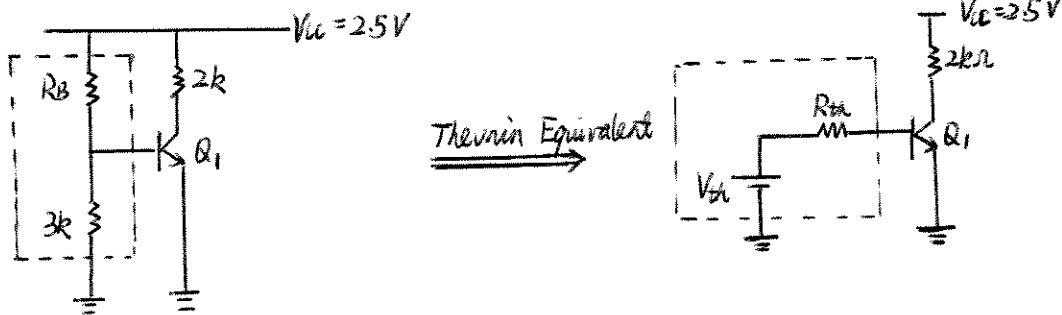11) a). Find the minimum  $R_B$  that guarantees forward active region.



$$R_{th} = \frac{R_B \times 3}{R_B + 3}, \quad V_{th} = \frac{25 \times 3}{R_B + 3}$$

To maintain  $Q_1$  in forward-active region,  $V_{CE} \geq V_{BE}$  (\*)

$$V_{CE} = V_{CC} - I_C \cdot 2k, \quad I_C = \beta I_B, \quad I_B = \frac{V_{th} - V_{BE}}{R_{th}}$$

$$\text{So } V_{CE} = V_{CC} - \beta \left( \frac{V_{th} - V_{BE}}{R_{th}} \right) \cdot 2k$$

From (\*)

$$V_{CC} - \beta \left( \frac{V_{th} - V_{BE}}{R_{th}} \right) \cdot 2k \geq V_{BE} \quad (1)$$

$$\text{And } V_{BE} = V_T \ln(I_C/I_S) = V_T \ln[\beta (V_{th} - V_{BE})/R_{th}/I_S] \quad (2)$$

Find the minimum  $R_B$  by iteration. Guess  $V_{BE} = 0.8$  as initial condition.

Use  $V_{BE} = 0.8$ , and substitute  $R_{th}$  and  $V_{th}$  into (1), it can be calculated

$$R_B \geq 6.178k$$

Check the validity of  $V_{BE}$ . With  $R_B \geq 6.178k$ , from (2)

$$V_{BE} = 0.727V$$

So the initial guess of  $V_{BE}$  is not accurate.

Reiterate with  $V_{BE} = 0.727$ , it can be calculated from (1)

$$R_B \geq 7.058k$$

11) With  $R_B \geq 706k$ , from ②

$$V_{BE} = 0.728$$

It's very close to 0.727. So the results have converged. (Satisfy both ① & ②)

The final answer is

$$R_B \geq 706k$$

b).  $\beta$  changes from 100 to 200, so  $\partial\beta$  is 100

$$V_{CB} = 2.5 - I_C(2k) - V_{BE} = 2.5 - \left(\frac{V_{TH} - V_{BE}}{R_{TH}}\right)\beta \cdot (2k) - V_{BE}$$

$$\frac{\partial V_{CB}}{\partial \beta} = - \left(\frac{V_{TH} - V_{BE}}{R_{TH}}\right) \cdot 2k$$



$$\partial V_{CB} = - \left(\frac{V_{TH} - V_{BE}}{R_{TH}}\right) \cdot 2k \cdot (\partial\beta) = -1.6627$$

(Forward bias sustained during  $\beta$ 's rising: 1.663V)

$$\text{Original } V_{CB} = 0.01428$$

Total net forward bias after  $\beta$  has rose to 200:

$$1 - 1.6627 + 0.01428 = 1.648 (V)$$

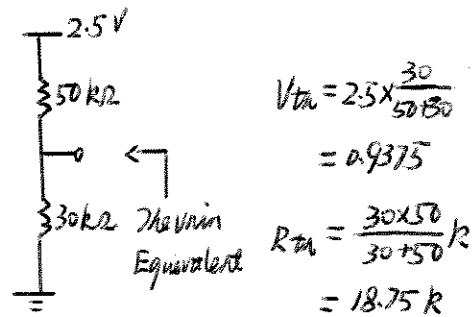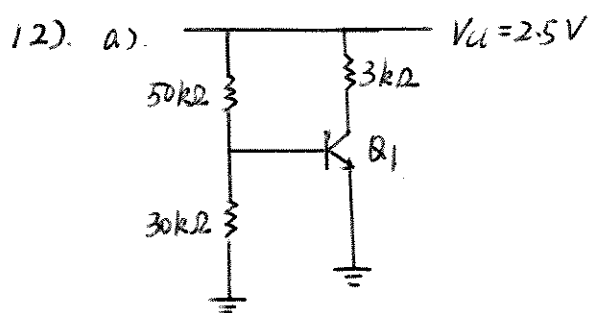

Since  $I_C = 0.5 \text{ mA}$ ,  $I_B = \frac{I_C}{\beta} = 0.005 \text{ mA}$ .

$$I_B = \frac{V_{th} - V_{BE}}{R_{th}} \Rightarrow V_{BE} = V_{th} - I_B \cdot R_{th} = 0.84375$$

$$I_C = I_S e^{\left(\frac{V_{BE}}{V_T}\right)} \Rightarrow I_S = \frac{I_C}{e^{\left(\frac{V_{BE}}{V_T}\right)}} = 4.03 \times 10^{-15} \text{ (mA)}$$

b). At the edge of saturation means  $V_{BE} - V_{CE} = 0$ .

(soft saturation not allowed)


$$V_{CE} = 2.5 - I_C \cdot (3k), \text{ in which } I_C = \beta I_B = \beta \left( \frac{V_{th} - V_{BE}}{R_{th}} \right)$$

$$\text{SO } V_{BE} = 2.5 - \beta \left( \frac{V_{th} - V_{BE}}{R_{th}} \right) \cdot (3k)$$

Solve this equation:

$$V_{BE} = 0.83.$$
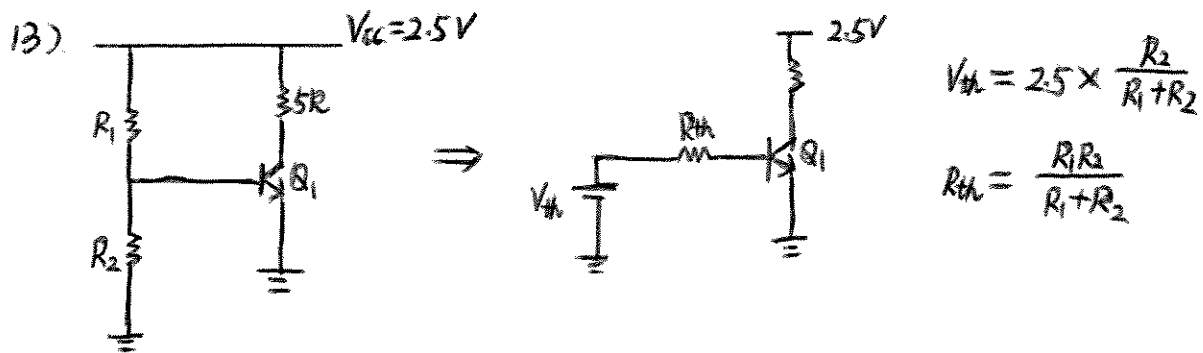
$$I_S = \frac{I_C}{e^{\left(\frac{V_{BE}}{V_T}\right)}} = \frac{\beta \left( \frac{V_{th} - V_{BE}}{R_{th}} \right)}{e^{\left(\frac{V_{BE}}{V_T}\right)}} = 7.84 \times 10^{-15} \text{ (mA)}$$



$$R_{in} = R_{th} \parallel \frac{V_T}{I_C} = R_{th} \parallel \frac{\beta}{g_m} = R_{th} \parallel \frac{V_T \beta}{I_C} > 10 k\Omega$$

$$g_m \geq \frac{1}{260\Omega} = 0.0038 S$$

Let's choose  $g_m$  to be  $0.0038 S$

$$g_m = \frac{I_C}{V_T} \Rightarrow I_C = g_m V_T = 0.104 (mA)$$

$$V_{BE} = V_T \ln \left( \frac{I_C}{I_S} \right) = 0.76 V$$

Let  $R_{in} = 10 k\Omega$

$$R_{in} = R_{th} \parallel \frac{V_T \beta}{I_C} \Rightarrow R_{th} = 16.13 k\Omega \quad \textcircled{1}$$

$$I_B = \frac{I_C}{\beta} = \frac{V_{th} - V_{BE}}{R_{th}} \Rightarrow V_{th} = V_{BE} + \frac{I_C \cdot (R_{th})}{\beta} = 0.78 V \quad \textcircled{2}$$

$$\textcircled{2} \Rightarrow 2.5 \times \frac{R_2}{R_1 + R_2} = 0.78 V$$

$$\textcircled{1} \Rightarrow \frac{R_1 R_2}{R_1 + R_2} = 16.13 k\Omega$$

It can be solved that  $R_1 = 51.7 k\Omega$ ,  $R_2 = 23.44 k\Omega$

This is only one possible solution set. The thought process is more important.

14). If  $g_m$  at least  $\frac{1}{26} = 0.03848$  ( $\Omega^{-1}$ )

$$\text{Let } g_m = 0.03848 = \frac{I_c}{V_T} \Rightarrow I_c = 0.99996 \text{ (mA)}$$

$$V_{BE} = V_T \ln \left( \frac{I_c}{I_S} \right) = 0.82 \text{ V}$$

$$V_{CE} = V_{CC} - I_c \cdot 5k = -2.5$$

No solution exists because the transistor is in saturation mode where  $g_m$  is essentially zero.

Whereas for problem 13),


$$V_{CE} = V_{CC} - I_c \cdot 5k = 2.5 - 0.104 \times 5 = 1.98 \text{ V}$$

$$V_{BE} = 0.76 \text{ V}$$

$$V_{CE} > V_{BE}$$

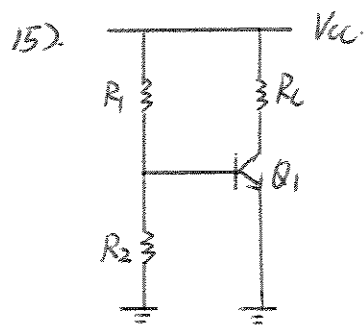So  $Q_1$  is still in forward-active region.





$$\text{Gain} = A_o$$

$$R_{out} = R_o = R_c$$

$$R_{in} = \frac{R_1 R_2}{R_1 + R_2} \parallel r_{\pi}, \quad r_{\pi} = \frac{\beta}{g_m}$$

$$R_{in} = \frac{R_1 R_2}{R_1 + R_2} \parallel \frac{\beta}{g_m}$$

$$\text{Gain} = A_o = g_m R_o \Rightarrow g_m = \frac{A_o}{R_o} = \frac{I_c}{V_T} \Rightarrow I_c = \frac{A_o V_T}{R_o}$$

( $I_c$  is set)

Bias point analysis:

$$\frac{\frac{V_{cc} R_2}{R_1 + R_2} - V_{BE}}{\frac{R_1 R_2}{R_1 + R_2}} = \frac{A_o V_T}{R_o}$$


$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = V_T \ln\left(\frac{A_o V_T}{R_o I_s}\right)$$

$$15) \frac{\frac{V_{cc} R_2}{R_1 + R_2} - V_T \ln\left(\frac{A_0 V_T}{R_0 I_s}\right)}{\frac{R_1 R_2}{R_1 + R_2}} = \frac{A_0 V_T}{R_0}$$

$$\frac{R_1 R_2}{R_1 + R_2} = \frac{\frac{V_{cc} R_2}{R_1 + R_2} - V_T \ln\left(\frac{A_0 V_T}{R_0 I_s}\right)}{\frac{A_0 V_T}{R_0}}$$

Max  $R_{in}$ :
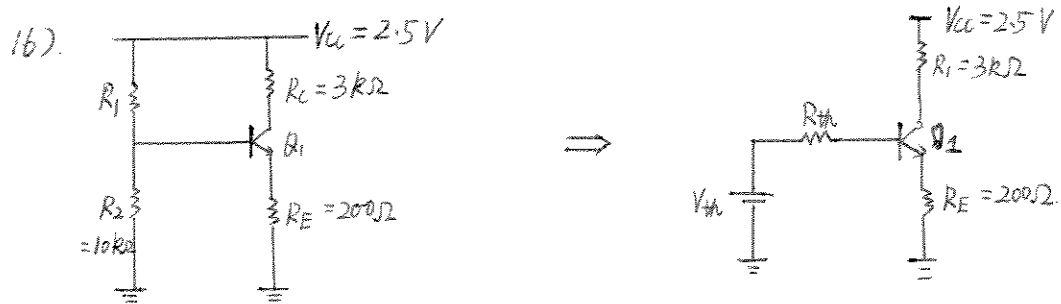
$$\frac{\frac{V_{cc} R_2}{R_1 + R_2} - V_T \ln\left(\frac{A_0 V_T}{R_0 I_s}\right)}{\frac{A_0 V_T}{R_0}} \approx \beta \frac{R_0}{A_0}$$



$$a) V_{th} = V_{CC} \cdot \frac{R_2}{R_1 + R_2} = 2.5 \times \frac{10k}{10k + R_1},$$

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{R_1 \cdot (10k)}{R_1 + 10k}$$

$$V_{th} = I_B R_{th} + V_{BE} + I_E R_E \quad (*)$$

Since  $I_E = 0.25mA$ ,  $I_B = 0.0025mA$ ,  $I_E = \frac{0.25mA}{99} = 0.2525mA$ .

$$V_{BE} = V_T \ln \left( \frac{I_C}{I_S} \right) = 0.696V$$

(\*) becomes

$$2.5 \times \frac{10k}{10k + R_1} = 0.0025 \times \frac{R_1 \cdot (10k)}{R_1 + 10k} + 0.696 + 0.2525 \times 0.2$$

So

$$R_1 = 22.73k$$

b) If  $R_E$  deviates by 5%, changes in  $R_E$  is  $10\Omega$ .

$$I_B = \frac{V_{th} - (V_{BE} + I_E R_E)}{R_{th}} \Rightarrow \frac{I_C}{\beta} = \frac{V_{th} - (V_{BE} + \frac{I_C}{\alpha} R_E)}{R_{th}}$$

$$\Rightarrow I_C = \frac{\beta \alpha (V_{th} - V_{BE})}{\alpha R_{th} + \beta R_E}$$


$$\Rightarrow \partial I_C = - \frac{\beta^2 \alpha (V_{th} - V_{BE})}{(\alpha R_{th} + \beta R_E)^2} \partial R_E$$

$$16) \partial R_E = 10, V_{TH} = 0.764, V_{BE} = 0.7465, R_{TH} = 6.94k, \alpha = 0.99, \beta = 100$$

$$\text{So } \partial I_C = -0.0024 \text{ (mA)}$$

$$\text{The error is } \frac{0.0024}{0.25} \times 100\% = 0.96\% \text{ in } I_C.$$

17).

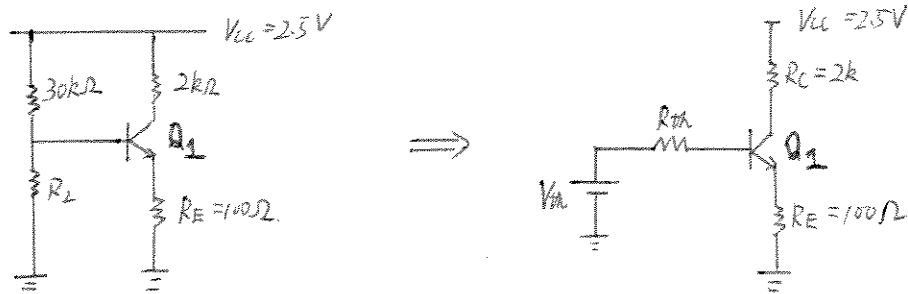

$$V_{th} = \frac{R_2 \times 2.5}{30k + R_2}, \quad R_{th} = \frac{30k \times R_2}{30k + R_2}$$

$V_{CE} \geq V_{BE}$  (To be guaranteed in active mode, soft saturation is not allowed.)

$$V_{CE} = V_{CC} - (I_C \cdot 2k + I_E \cdot 100)$$

$$I_C = \frac{\beta \alpha (V_{th} - V_{BE})}{\alpha R_{th} + \beta R_E} \quad \left( \because I_C = \frac{V_{th} - (V_{BE} + \frac{I_C}{\alpha} R_E)}{R_{th}} \right)$$

$$\text{So } V_{CE} = V_{CC} - \left[ \frac{\beta \alpha (V_{th} - V_{BE})}{\alpha R_{th} + \beta R_E} \cdot 2k + \frac{\beta (V_{th} - V_{BE})}{\alpha R_{th} + \beta R_E} \times 100 \right]$$

$V_{CE} \geq V_{BE}$  means

$$2.5 - \left[ \frac{99 \left( \frac{R_2 \times 2.5}{30k + R_2} - V_{BE} \right)}{0.99 \times \frac{30k \times R_2}{30k + R_2} + 100 \times 100} \times 2k + \frac{100 \left( \frac{R_2 \times 2.5}{30k + R_2} - V_{BE} \right)}{0.99 \times \frac{30k \times R_2}{30k + R_2} + 100 \times 100} \times 100 \right] \geq V_{BE} \quad (1)$$

And


$$V_{BE} = V_T \ln \left( \frac{I_C}{I_S} \right) = V_T \ln \left[ \frac{\beta \alpha (V_{th} - V_{BE})}{I_S (\alpha R_{th} + \beta R_E)} \right] \quad (2)$$

There are two unknowns ( $R_2$  and  $V_{BE}$ ) and two equations (1) and (2)

Since (2) is a nonlinear equation, the problem can be solved by iteration.

$$\text{Maximum } R_2 = 20.343k$$

18b)

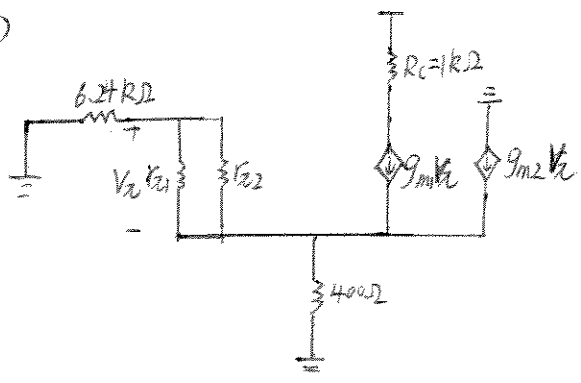


Small - Signal


$$g_{m1} = \frac{I_c}{V_T} = 0.02855 \text{ (S)}$$

$$g_{m2} = 0.0142 \text{ (S)}$$

$$r_{21} = 3571.4 \text{ (}\Omega\text{)}$$
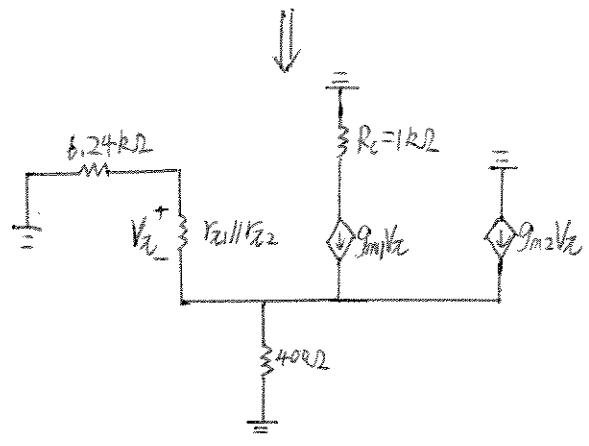
$$r_{22} = 7042.3 \text{ (}\Omega\text{)}$$



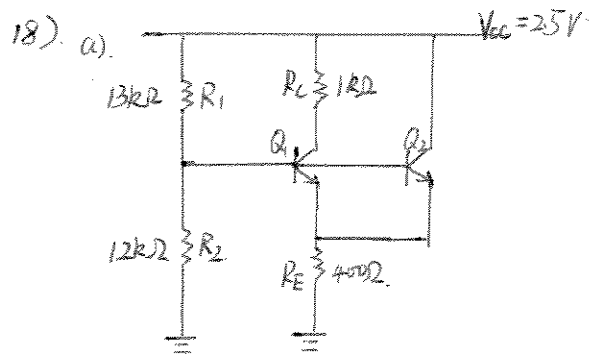


$$I_{S1} = 2 I_{S2} = 5 \times 10^{-16} \text{ A}$$

$$\beta_1 = \beta_2 = 100$$

$$I_{S2} = 2.5 \times 10^{-16} \text{ A}$$

$$V_{th} = V_{CC} \times \frac{R_2}{R_1 + R_2} = 1.2 \text{ V}$$
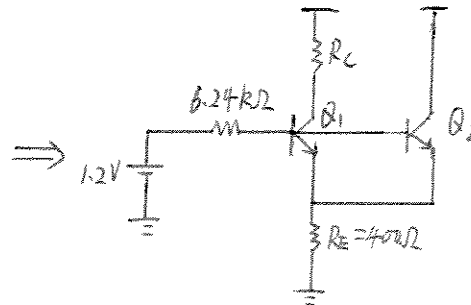
$$R_{th} = R_1 \parallel R_2 = 6.24 \text{ k}\Omega$$



$$I_{B2} = \frac{1.2 - (V_{BE} + 3I_{E2} \cdot R_E)}{6.24 \text{ k}\Omega}, \quad \text{and} \quad I_{B2} = \frac{I_{C2}}{\beta}$$

$$\text{SO } \frac{I_{C2}}{\beta} = \frac{1.2 - (V_{BE} + 3I_{C2}/\alpha \cdot 0.4 \text{ k}\Omega)}{6.24 \text{ k}\Omega}$$

$$\beta = 100, \quad \alpha = 0.99$$

$$\Rightarrow I_{C2} = \frac{(1.2 - V_{BE}) \cdot (\beta \alpha)}{(\alpha \cdot 6.24 \text{ k}\Omega + 3\beta \cdot 0.4 \text{ k}\Omega)} = \frac{(1.2 - V_{BE})(99)}{126.1776} \text{ (mA)}$$


$$\text{GUESS } V_{BE} = 0.8, \quad I_{C2} = 0.314 \text{ mA}$$

$$V_{BE} = V_T \ln \left( \frac{I_{C2}}{I_{S2}} \right) = 0.724, \text{ not } 0.8, \text{ so reiterate.}$$

$$I_{C2} = \frac{(1.2 - 0.724)(99)}{126.1776} = 0.3735$$

$$V_{BE} = 26 \ln \left( \frac{0.3735}{2.5 \times 10^{-16}} \right) = 0.728, \text{ close, iterate again}$$
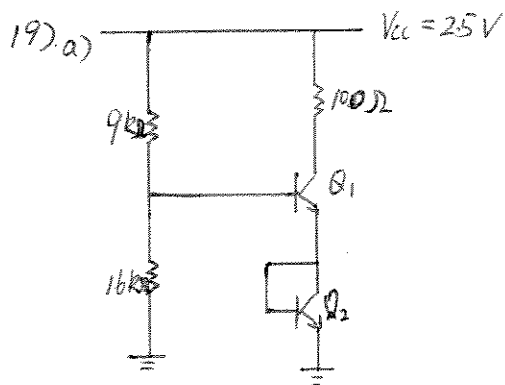
$$\Rightarrow V_{BE} \approx 0.729 \text{ (V)}, \quad I_{C2} = 0.37 \text{ (mA)}, \quad I_{C1} = 0.74 \text{ (mA)}$$




$$I_{S1} = I_{S2} = 4 \times 10^{-16} \text{ A}$$

$$\beta_1 = \beta_2 = 100$$

$$V_A = \infty$$

$$V_{th} = \frac{(2.5)(16k)}{9k + 16k} = 1.6 \text{ (V)}$$

$$R_{th} = 9k // 16k = 5.76k (\Omega)$$

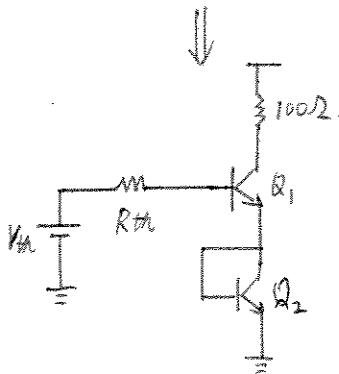

$$I_{B1} = \frac{V_{th} - 2(V_{BE})}{R_{th}}, \quad I_{C1} = \beta I_{B1} = \beta \frac{V_{th} - 2(V_{BE})}{R_{th}} \quad (1)$$

$$V_{BE} = V_T \ln \left( \frac{I_{C1}}{I_{S1}} \right) \quad (2)$$

GUESS  $V_{BE} = 0.7$ ,

$$(1) \Rightarrow I_{C1} = 100 \times \frac{1.6 - 2 \times 0.7}{5.76} = 3.47 \text{ (mA)}$$

$$(2) \Rightarrow V_{BE} = V_T \ln \left( \frac{3.47}{4 \times 10^{-16}} \right) = 0.7746, \text{ not } 0.7, \text{ reiterate}$$

$$(1) \Rightarrow I_{C1} = 0.8819$$

$$(2) \Rightarrow V_{BE} = 0.739, \text{ not } 0.7746, \text{ reiterate } \dots$$

After several iterations,  $V_{BE}$  converges to 0.755



19) a)  $V_{BE} = 0.755 \text{ (V)}$

$$I_{B1} = \frac{V_{Th} - 2V_{BE}}{R_{Th}} = 0.0156 \text{ (mA)}$$

$$I_{C2} = \beta I_{B1} = 1.56 \text{ (mA)}$$


$$V_{CE} = V_{CC} - [I_C \cdot (0.1) + V_{BE}] = 1.589 \text{ (V)}$$

$$I_{C2} = 1.56 \text{ (mA)}$$

$$I_{B2} = (1/\beta) I_{C2} = 0.0156 \text{ (mA)}$$

$$V_{CE2} = V_{BE} = 0.755 \text{ (V)}$$


b).

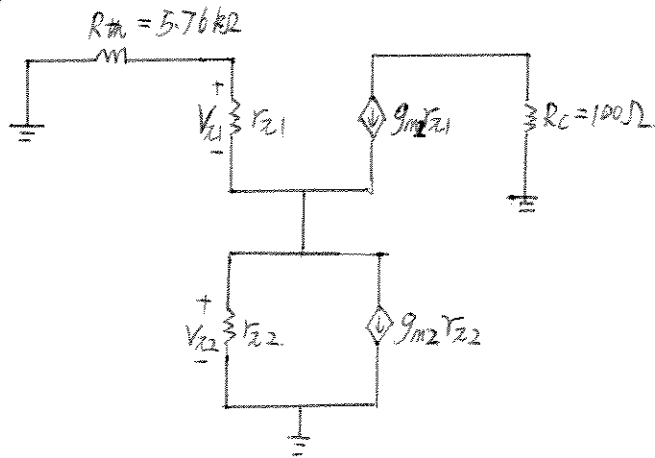

$$g_{m1} = g_{m2} = \frac{I_C}{V_T} = 0.065 \text{ (S)}$$

$$r_{e1} = r_{e2} = \frac{\beta}{g_m} = 1666.7 \text{ (}\Omega\text{)}$$

20)

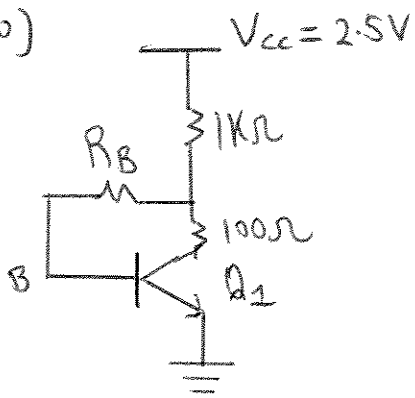

$$I_C = 1\text{mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.750\text{V}$$

$$V_B = 2.5 - (I_E (1\text{k}\Omega) + I_B R_B) = 0.750\text{V}$$

$$I_E = 1.01\text{mA}$$


$$I_B = 0.01\text{mA}$$

$$V_B = 2.5 - 1.01 - 0.01 R_B = 0.750$$

$$0.74 = 0.01 R_B$$

$$R_B = 74\text{k}\Omega$$

21)

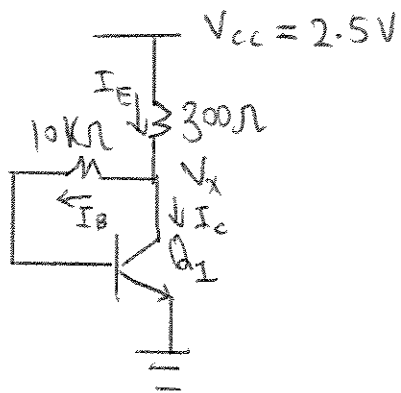

$$V_x = 1.1V$$

$$\beta = 100$$

$$I_s = ?$$

$$I_E = I_B + I_C$$

$$I_E = \frac{2.5 - 1.1}{300\Omega} = 4.67 \text{ mA}$$

$$I_B = \frac{I_C}{\beta}$$

$$I_E = \frac{I_C}{\beta} + I_C = 4.67 \text{ mA}$$


$$I_C = 4.624 \text{ mA}$$

$$I_s = \frac{I_C}{e^{\left(\frac{V_{BE}}{V_T}\right)}}, \quad V_{BE} = 1.1 - \frac{4.624(10K)}{100} = 0.6376V$$

$$I_s = 1.035 \times 10^{-10} \text{ mA}$$

$$I_s = 1.035 \times 10^{-13} \text{ A}$$

22.

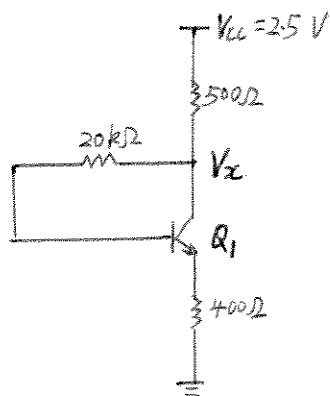

$$I_S = 6 \times 10^{-16} A$$

$$\beta = 100$$

$$V_A = \infty$$

$$\frac{V_{CC} - V_x}{0.5k} = I_C + I_B = I_C \left(1 + \frac{1}{\beta}\right) \Rightarrow V_x = 2.5 - 0.5k \cdot \frac{I_C}{\alpha} \quad (1)$$

$$\frac{V_x - (V_{BE} + I_E \cdot 0.4k)}{20k} = \frac{I_C}{\beta} \Rightarrow V_x = (20k) \left(\frac{I_C}{\beta}\right) + V_{BE} + \frac{I_C}{\alpha} \cdot (0.4k) \quad (2)$$

Equating  $V_x$  in (1) and (2)

$$2.5 - (0.5k) \left(\frac{I_C}{\alpha}\right) = (20k) \left(\frac{I_C}{\beta}\right) + V_{BE} + \frac{I_C}{\alpha} \cdot (0.4k)$$

$$I_C = \frac{2.5 - V_{BE}}{\frac{0.9k}{\alpha} + \frac{20k}{\beta}} = \frac{2.5 - V_{BE}}{1.11k} \quad (3)$$

First iteration  $V_{BE} = 0.8$ .

$$(3) \Rightarrow I_C = 1.53 \text{ (mA)}$$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.743, \text{ not } 0.8, \text{ reiterate}$$


$$(3) \Rightarrow I_C = \frac{2.5 - 0.743}{1.11} = 1.583 \text{ (mA)}$$

$$V_{BE} = V_T \ln\left(\frac{1.583}{I_S}\right) = 0.744, \text{ converged.}$$

$$\text{So, } V_{BE} = 0.74 \text{ (V)} \quad I_C = 1.58 \text{ (mA)}, \quad I_B = I_C / \beta = 0.0158 \text{ (mA)}$$

$$V_C = 2.5 - \frac{1.583}{0.99} \times 0.5 = 1.7 \text{ (V)}, \quad V_E = V_C - (I_B \cdot 20k + V_{BE}) = 0.644 \text{ (V)}, \quad V_{CE} = V_C - V_E = 1.056 \text{ (V)}$$

23).

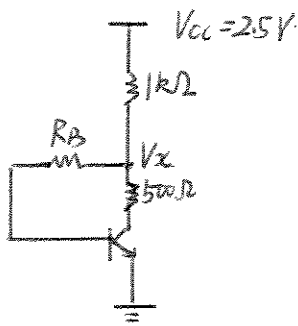

$$I_c = \beta \left( \frac{2.5 - I_E(1k) - V_{BE}}{R_B} \right)$$

$$\frac{I_c R_B}{\beta} = 2.5 - I_E(1k) - V_{BE}$$

$(I_E = \frac{I_c}{\alpha})$

$$I_c = \frac{2.5 - V_{BE}}{\frac{R_B}{\beta} + \frac{1k}{\alpha}} \quad (1)$$

$$V_{BC} \leq 0.2V$$

$$(V_x - I_B R_B) - (V_x - I_c 0.5) \leq 0.2V$$

$$I_c \left( 0.5 - \frac{R_B}{\beta} \right) \leq 0.2V$$

$$\left( \frac{2.5 - V_{BE}}{\frac{R_B}{\beta} + \frac{1k}{\alpha}} \right) \left( 0.5 - \frac{R_B}{\beta} \right) \leq 0.2V \quad (2)$$

Guess  $V_{BE} = 0.75V \Rightarrow R_B \geq 34.513k\Omega$  (From (2))

Let  $R_B = 34.513k\Omega$

$$I_c = 1.291mA, \text{ (From (1))}$$

$$V_{BE} = V_T \ln \left( \frac{I_c}{I_s} \right) = 0.7564V, \text{ not } 0.75, \text{ Iterate}$$

$$V_{BE} = 0.7564V. \Rightarrow R_B \geq 34.461k\Omega$$

23)

$$\text{Let } R_B = 34.461 \text{ k}\Omega$$

$$I_C = 1.287 \text{ mA (From (1))}$$


$$V_{BE} = V_T \ln \left( \frac{I_C}{I_S} \right) = 0.7563 \text{ V, converged!!}$$

$$\text{So } I_C = 1.287 \text{ mA, } R_B = 34.46 \text{ k}\Omega$$

$$\text{Check } V_{BC} : V_{BC} = (1.287)(0.5) - \left( \frac{1.287}{100} \right)(34.46)$$

$$V_{BC} = 0.1999998, \text{ less than } 0.2 \text{ V}$$

24). a).

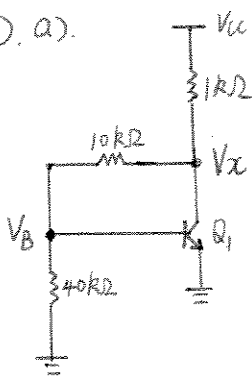

$$I_S = 8 \times 10^{-16} \text{ A}$$

$$\beta = 100$$

$$V_A = \infty$$

$$V_C = 2.5 - \left( \frac{I_C}{\alpha} + \frac{V_B}{40k} \right) \cdot 1k$$

$$V_C = \left( \frac{V_B}{40k} + 2I_B \right) 10k + V_B = \left( \frac{V_B}{40k} + \frac{I_C}{\beta} \right) 10k + V_B$$

$$\text{Equating } V_C \Rightarrow 2.5 - \left( V_B + \frac{V_B \cdot 1k}{40k} + \frac{V_B \cdot 10k}{40k} \right) = \frac{I_C}{\alpha} \cdot 1k + \frac{I_C}{\beta} \cdot 10k.$$

$$\Rightarrow I_C = \frac{2.5 - 1.275V_B}{\frac{1k}{\alpha} + \frac{10k}{\beta}}$$

Guess  $V_B = 0.8$

$$I_C = \frac{1.48}{\frac{1k}{0.99} + \frac{10k}{100}} = 1.33 \text{ mA}$$

Then

$$V_B = V_T \ln \left( \frac{I_C}{I_S} \right) = 0.732, \text{ not } 0.8.$$

Reiterate

$$I_C = \frac{1.5667}{1.11} = 1.4113 \text{ mA}$$

$$V_B = V_T \ln \left( \frac{I_C}{I_S} \right) = 0.733$$

So  $V_B$  converges to 0.73V


$$I_C = 1.41 \text{ mA}$$

$$I_B = 14.1 \mu\text{A}$$

$$V_{CE} = 2.5 \text{ V} - \left( \frac{1.41}{0.99} + \frac{0.73}{40} \right) \times 1 \text{ V} = 1.06 \text{ V}.$$

$$V_{BE} = 0.73 \text{ V}$$

24 b) Small Signal

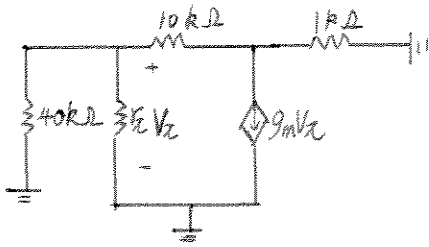


$$g_m = \frac{I_C}{V_T} = 0.054 \text{ S}$$

$$r_z = \frac{\beta}{g_m} = 1844 \Omega$$



25)

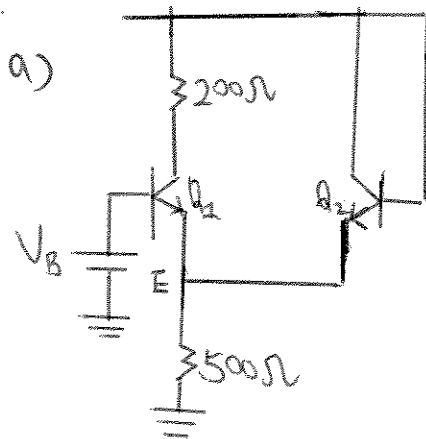

$$I_{C1} = 1\text{mA}, I_{E1} = 1.01\text{mA}$$

$$I_{S1} = I_{S2} = 3 \times 10^{-16}\text{A}$$

$$V_A = \infty$$

$$\beta = 100$$

$$V_E = (I_{E1} + I_{E2}) 0.5\text{k}, V_{BE1} = V_T \ln\left(\frac{I_{C1}}{I_S}\right) = 0.75\text{V}$$

$$V_E = 2.5 - V_{BE2}$$

$$V_B - (1.01 + I_{E2}) 0.5 = 0.75\text{V}$$

Guess  $V_{BE2} = 0.7\text{V}$

$$V_E = 1.8 \Rightarrow I_{E1} + I_{E2} = 3.6\text{mA} \Rightarrow I_{E2} = 2.59\text{mA}$$

$$I_{C2} = 2.5641\text{mA} \Rightarrow V_{BE2} = V_T \ln\left(\frac{I_{C2}}{I_S}\right) = 0.774\text{V}$$

Reiterate

$$V_E = 1.726 \Rightarrow I_{E2} = 2.442\text{mA}, I_{C2} = 2.4176\text{mA}$$

$$V_{BE2} = V_T \ln\left(\frac{I_{C2}}{I_S}\right) = 0.773, \text{ converged!!}$$

$$V_{BE} = 0.773\text{V}, I_{C2} = 2.42\text{mA}, I_{E2} = 2.44\text{mA}$$

$$V_B = 0.75 + (1.01 + 2.44) 0.5 = 2.475\text{V}$$


$$V_C = 2.5 - (1 \times 0.2) = 2.3$$

$Q_1$  in soft-saturation region.

25

b)

Small Signal Model

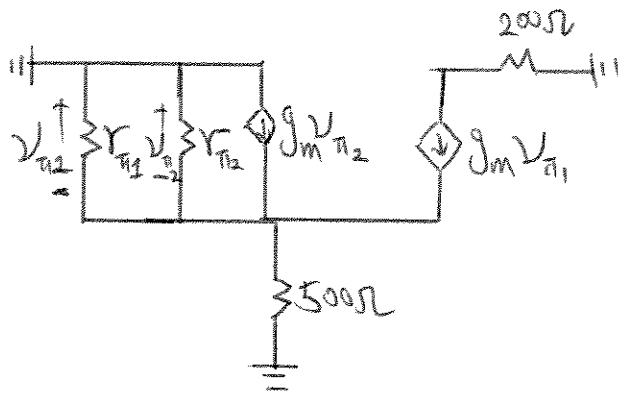

$$g_{m1} = \frac{1 \text{ mA}}{26 \text{ mV}} = 0.0385 \left( \frac{1}{\Omega} \right) \text{ S}$$

$$r_{\pi1} = \frac{100}{0.0385} = 2.6 \text{ k}\Omega$$


$$g_{m2} = \frac{2.42 \text{ mA}}{26 \text{ mV}} = 0.0931 \left( \frac{1}{\Omega} \right) \text{ S}$$

$$r_{\pi2} = \frac{100}{0.0931} = 1.07 \text{ k}\Omega$$


2b).  $\beta_{npn} = 2\beta_{pnp} = 100$

$I_S = 9 \times 10^{-16} \text{ A}$

$V_A = \infty$

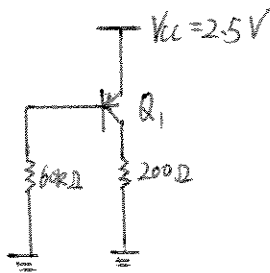

(a)

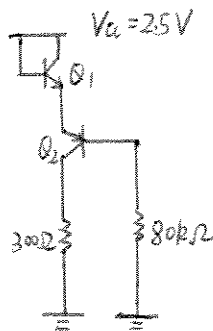

(b)

a)  $I_C = \frac{2.5 - |V_{BE}|}{60k} \beta_{pnp}$ ,  $V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right)$

Guess  $|V_{BE}| = 0.8 \Rightarrow I_C = 1.42 \text{ mA}$

$|V_{BE}| = 26 \times 10^{-3} \ln\left(\frac{1.42}{9 \times 10^{-16}}\right) = 0.730 \text{ (V)}$ , not 0.8

Reiterate,  $I_C = \frac{2.5 - 0.73}{60k} \times 50 = 1.475 \text{ mA}$

$|V_{BE}| = 26 \times 10^{-3} \ln\left(\frac{1.42}{9 \times 10^{-16}}\right) = 0.731 \text{ (V)}$

Reiterate,  $I_C = \frac{2.5 - 0.731}{60k} \times 50 = 1.474 \text{ mA}$

$|V_{BE}| = 26 \times 10^{-3} \ln\left(\frac{1.474}{9 \times 10^{-16}}\right) = 0.731 \text{ (V)}$ , converged.

$Q_1$ :  $|V_{BE}| = 0.731 \text{ V}$ ,  $I_C = 1.47 \text{ mA}$ ,  $I_B = 29.4 \mu\text{A}$ .

$|V_{CE}| = 2.206 \text{ V}$ .

In forward active region.

26)

b).

$$I_{C2} = \frac{2.5 - (V_{BE1} + |V_{BE2}|)}{80k} \quad (1)$$

$$I_{C2} \cdot \frac{\beta_{npn} + 1}{\beta_{npn}} = \frac{I_{C1} (\beta_{npn} + 1)}{\beta_{npn}} \quad \Rightarrow I_{C1} = \frac{2(\beta_{npn} + 1)}{2\beta_{npn} + 1} I_{C2} = 1.0099 I_{C2} \quad (2)$$

$$\beta_{npn} = 2\beta_{pnp} = 100$$

$$V_{BE1} = V_T \ln \left( \frac{I_{C1}}{I_S} \right) \quad (3)$$

$$V_{BE2} = V_T \ln \left( \frac{I_{C2}}{I_S} \right) \quad (4)$$

Four unknowns:  $I_{C1}$ ,  $I_{C2}$ ,  $V_{BE1}$ ,  $V_{BE2}$ . Four equations: (1), (2), (3), (4)

Solve by iteration since (3) and (4) are exponential equations.

Guess  $V_{BE2} = V_{BE1} = 0.8$

$$(1) \Rightarrow I_{C2} = 50 \times \left( \frac{2.5 - 1.6}{80k} \right) A = 0.5625 mA$$

$$(2) \Rightarrow I_{C1} = 0.568 mA$$

$$(3) \Rightarrow V_{BE1} = V_T \ln \left( \frac{0.568}{9 \times 10^{-13}} \right) V = 0.706 V$$

$$(4) \Rightarrow V_{BE2} = V_T \ln \left( \frac{0.5625}{9 \times 10^{-13}} \right) V = 0.706 V$$

Reiterate,

$$I_{C2} = 0.68 mA, \quad I_{C1} = 0.6867 mA, \quad V_{BE1} = 0.711 V, \quad V_{BE2} = 0.711 V.$$

Reiterate,

$$I_{C2} = 0.674 mA, \quad I_{C1} = 0.680 mA, \quad V_{BE1} = 0.711 V, \quad V_{BE2} = 0.711 V$$

So,

$$I_{C1} = 0.680 mA$$

$$I_{B1} = 0.8 \mu A$$

$$V_{BE1} = 0.711 V$$

$$V_{CE1} = 0.711 V$$


$$I_{C2} = 0.674 mA$$

$$I_{B2} = 13.48 \mu A$$

$$|V_{BE2}| = 0.711 V$$

$$|V_{CE2}| = 2.5 V - 0.711 V - (0.674)(0.3) V = 1.5868 V.$$


27. a)

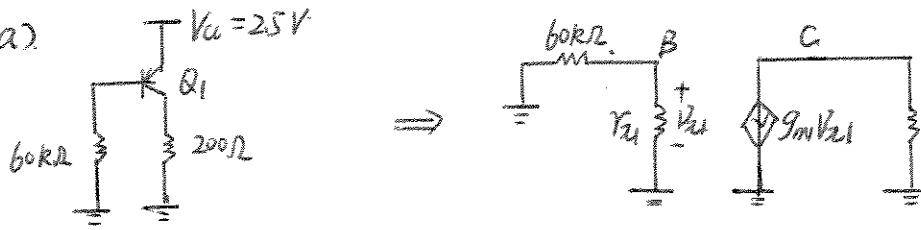

$$g_{m1} = \frac{I_c}{V_T} = \frac{1.47 \text{ mA}}{26 \text{ mV}} = 0.0565 \text{ S}$$

$$r_{z1} = \frac{\beta}{g_{m1}} = 884 \Omega$$

b)

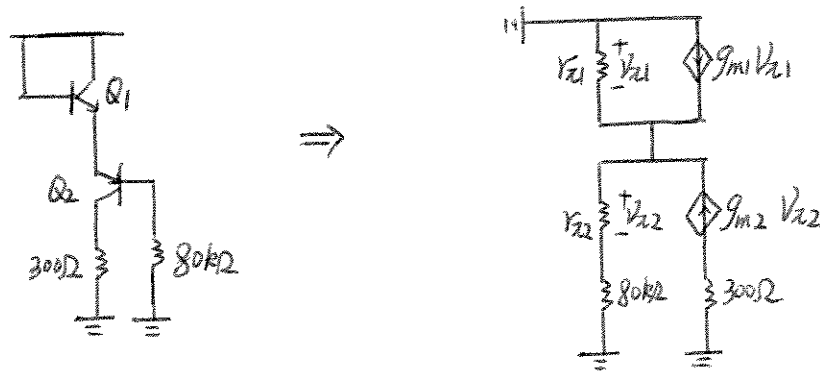


$$g_{m1} = \frac{I_{c1}}{V_T} = 0.02615 \text{ S}$$

$$r_{z1} = 3823.5 \Omega$$

$$g_{m2} = \frac{I_{c2}}{V_T} = 0.0259 \text{ S}$$

$$r_{z2} = 1928.8 \Omega$$

28)

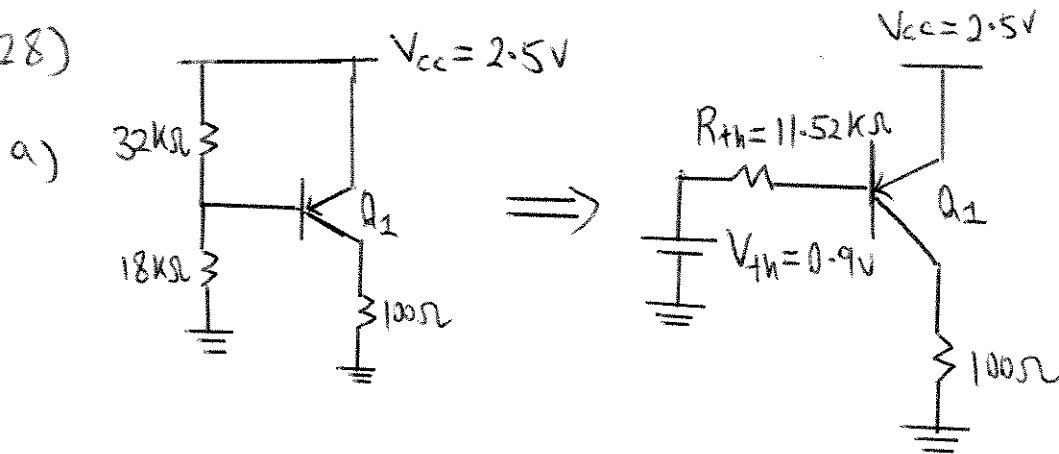

$$I_c = \beta_{Pnp} \left( \frac{2.5 - |V_{BE}| - V_{th}}{R_{th}} \right)$$

Guess  $|V_{BE}| = 0.7 \text{ V}$ ,  $I_c = 3.91 \text{ mA}$

$$|V_{BE}| = V_T \ln \left( \frac{I_c}{I_s} \right) = 0.757 \text{ V}$$

Reiterate,  $|V_{BE}| = 0.757 \text{ V}$ ,  $I_c = 3.66 \text{ mA}$

$$|V_{BE}| = V_T \ln \left( \frac{I_c}{I_s} \right) = 0.755 \text{ V}$$

Reiterate,  $|V_{BE}| = 0.755 \text{ V}$ ,  $I_c = 3.67 \text{ mA}$

$$|V_{BE}| = V_T \ln \left( \frac{I_c}{I_s} \right) = 0.755 \text{ V, Converged!!}$$

$$V_c = (3.67 \text{ mA})(0.1 \text{ k}\Omega) = 0.367 \text{ V}, \quad V_B = 2.5 - 0.755 = 1.745 \text{ V}$$


$Q_1$  in forward active.

Bias point:

$$I_c = 3.67 \text{ mA} \quad |V_{BE}| = 0.755$$

$$I_B = 73.4 \text{ }\mu\text{A} \quad |V_{CE}| = 2.5 - 0.367 = 2.133 \text{ V}$$

28)  
b)

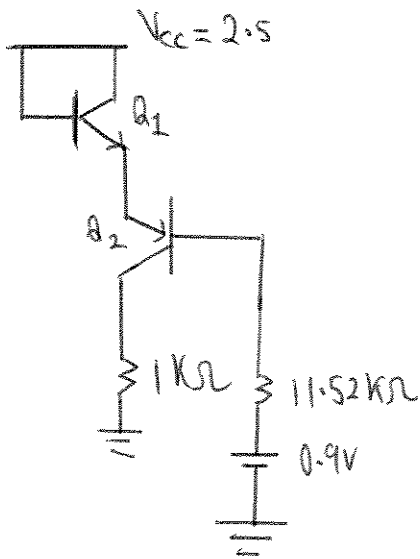

$$I_{c2} = \frac{(2.5 - (V_{BE1} + V_{BE2}) - 0.9)}{11.52 \text{ k}} \cdot 50$$

$$I_{c1} = I_{c2} (1.00997)$$

(From  $\beta$  relation)

$$V_{BE1} = V_T \ln\left(\frac{I_{c1}}{I_S}\right)$$

$$|V_{BE2}| = V_T \ln\left(\frac{I_{c2}}{I_S}\right)$$

Guess,  $V_{BE1} = V_{BE2} = 0.7 \text{ V}$

$$I_{c2} = 0.868 \text{ mA}, \quad I_{c1} = 0.877 \text{ mA}$$

$$V_{BE1} = V_T \ln\left(\frac{I_{c1}}{I_S}\right) = 0.718 \text{ V}, \quad |V_{BE2}| = V_T \ln\left(\frac{I_{c2}}{I_S}\right) = 0.717 \text{ V}$$

Reiterate,  $V_{BE1} = 0.718 \text{ V}, \quad |V_{BE2}| = 0.717 \text{ V}$

$$I_{c2} = 0.716 \text{ mA}, \quad I_{c1} = 0.723 \text{ mA}$$

$$V_{BE1} = V_T \ln\left(\frac{I_{c1}}{I_S}\right) = 0.713 \text{ V}, \quad |V_{BE2}| = V_T \ln\left(\frac{I_{c2}}{I_S}\right) = 0.712 \text{ V}$$

Reiterate,  $V_{BE1} = 0.713 \text{ V}, \quad |V_{BE2}| = 0.712 \text{ V}$

$$I_{c2} = 0.760 \text{ mA}, \quad I_{c1} = 0.767 \text{ mA}$$

$$V_{BE1} = 0.714 \text{ V}, \quad |V_{BE2}| = 0.714 \text{ V}$$

28)

b)

$$\text{Reiterate, } V_{BE_1} = 0.714 \text{ V, } |V_{BE_2}| = 0.714 \text{ V}$$

$$I_{C_2} = 0.747 \text{ mA, } I_{C_1} = 0.754 \text{ mA}$$

$$V_{BE_1} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.714 \text{ V,}$$

$$|V_{BE_2}| = 0.714 \text{ V}$$

$$V_{B_2} = \frac{(0.747 \text{ mA})(11.52 \text{ k}\Omega) + 0.9}{50} = 1.07 \text{ V}$$

$$V_{C_2} = (0.747 \text{ mA})(1 \text{ k}\Omega) = 0.747 \text{ V}$$

$Q_2$  is in forward-active region.  $Q_1$  is always in forward-active region.

Bias point:

$$V_{BE_1} = 0.714 \text{ V}$$

$$I_{C_1} = 0.754 \text{ mA}$$

$$I_{B_1} = 7.54 \mu\text{A}$$

$$V_{CE_1} = 0.714 \text{ V}$$

$$|V_{BE_2}| = 0.714 \text{ V}$$

$$I_{C_2} = 0.747 \text{ mA}$$


$$I_{B_2} = 14.94 \mu\text{A}$$

$$|V_{CE_2}| = 2.5 - 0.714 - 0.747 = 1.039 \text{ V}$$




29)

a)

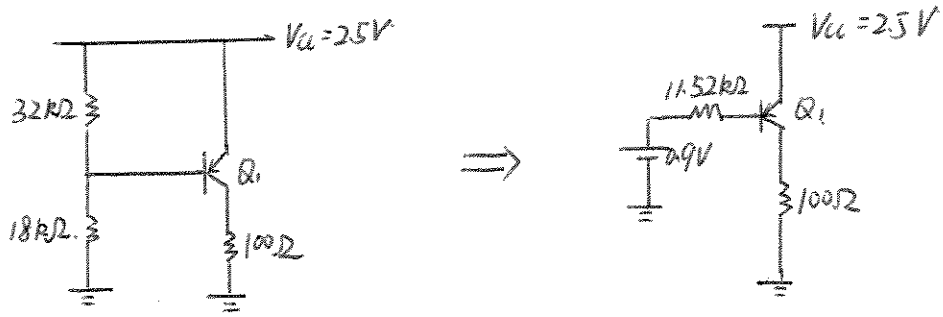


Small Signal:

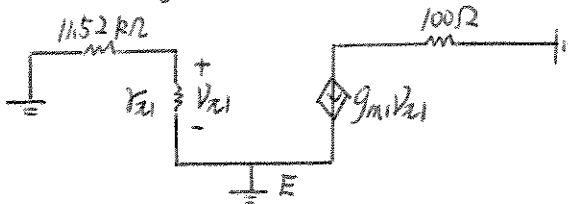

$$g_{m1} = \frac{3.67 \text{ mA}}{26 \text{ mV}} = 0.141 \text{ S}$$

$$r_{21} = \frac{50}{0.141} \Omega = 354.2 \Omega$$

b)

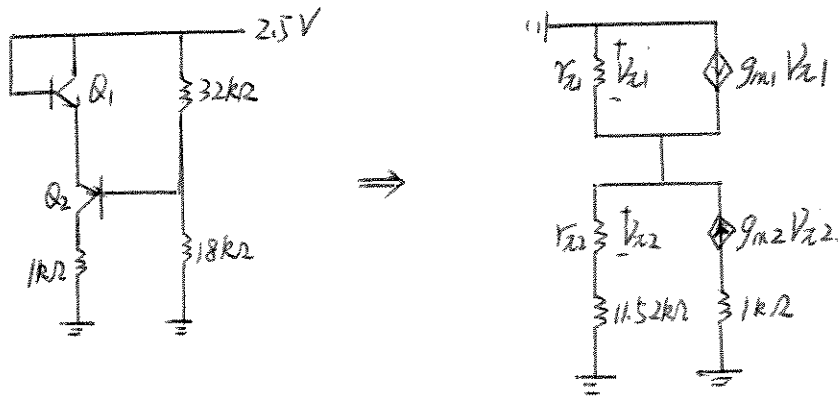


$$g_{m1} = 0.029 \text{ S}$$

$$r_{21} = 3448.3 \Omega$$

$$g_{m2} = 0.0287 \text{ S}$$


$$r_{22} = 17403 \Omega$$

30)

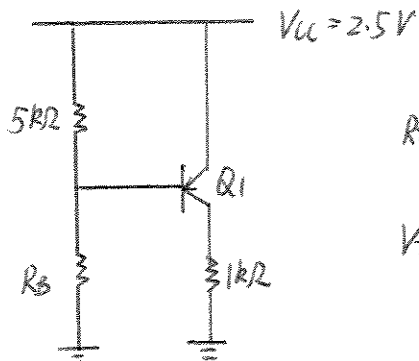

$$R_{th} = \frac{(R_B)(5k\Omega)}{R_B + 5k\Omega}$$
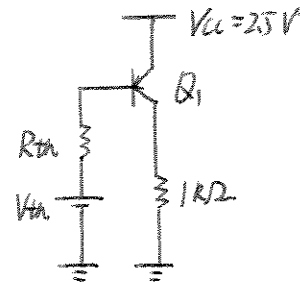
$$V_{th} = \frac{R_B}{R_B + 5k\Omega} \cdot 2.5V$$



$$\beta = 50, \quad I_s = 8 \times 10^{-16} A, \quad V_A = \infty$$

Edge of saturation:  $|V_{BE}| = |V_{CE}|$

$$I_c = \frac{50(2.5 - |V_{BE}| - V_{th})}{R_{th}}, \quad |V_{CE}| = 2.5 - I_c(1k\Omega) = |V_{BE}|$$

$$2.5 - \frac{50(2.5 - |V_{BE}| - V_{th})(1k\Omega)}{R_{th}} = |V_{BE}|$$

Substitute in  $R_{th}$  and  $V_{th}$  and rearrange:

$$12.5R_B + 50|V_{BE}|R_B - |V_{BE}|(5k)R_B = 625 - |V_{BE}|250 \quad (1)$$

$$\text{Guess } |V_{BE}| = 0.7V, \quad (1) \Rightarrow 44R_B = 450 \Rightarrow R_B = 10.23k\Omega$$

$$V_{th} = 1.68V \quad I_c = 1.7857mA$$

$$R_{th} = 3.36k\Omega \quad |V_{BE}| = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.739V, \text{ not } 0.7V, \text{ Iterate}$$

$$|V_{BE}| = 0.739V, \quad (1) \Rightarrow 45.755R_B = 440.25$$

$$R_B = 9.62k\Omega$$

$$V_{th} = 1.645V \quad I_c = 1.763mA$$

$$R_{th} = 3.29k\Omega \quad |V_{BE}| = 0.739V, \text{ Converged.}$$

3°)

$50 \pm 5\%$  of  $9.62 \text{ k}\Omega$ .

+5% Case:

$$9.62 \text{ k}\Omega + 5\% = 10.101 \text{ k}\Omega$$

$$V_{th} = 1.67 \text{ V}, R_{th} = 3.345 \text{ k}\Omega$$

$$I_c = \frac{(2.5 - 0.74 - 1.67)}{3.345} 50 = 1.3455 \text{ mA}$$

(Assume  $|V_{BE}| = 0.74 \text{ V}$ )

check for  $|V_{BE}| = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.732 \text{ V}$ , iterate once

$$I_c = 1.4651 \text{ mA}, |V_{BE}| = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.734 \text{ V}, \text{ converged}$$

$$|V_{BE}| \approx 0.734, |V_{CE}| = 2.5 - 1.4651(1 \text{ k}\Omega) = 1.0349 \text{ V}$$

$$V_{BC} = 0.3009 \text{ V} \text{ (Reverse bias)}$$

-5% Case:

$$9.62 \text{ k}\Omega - 5\% = 9.139 \text{ k}\Omega$$

$$V_{th} = 1.616 \text{ V}, R_{th} = 3.23184 \text{ k}\Omega$$

$$I_c = \frac{(2.5 - 0.74 - 1.616)}{3.23184} 50 = 2.228 \text{ mA}, |V_{BE}| = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.745 \text{ V}$$


( $|V_{BE}| = 0.7$ )

$$\text{reiterate: } |V_{BE}| = 0.745 \text{ V}, I_c = 2.150 \text{ mA}$$

$$\text{Verify } V_{BE}, |V_{BE}| = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.744 \text{ V}, \text{ converged}$$

$$|V_{CE}| = 2.5 - 2.150(1 \text{ k}\Omega) = 0.35, |V_{BE}| = 0.744 \text{ V}, V_{BC} = -0.394 \text{ V} \text{ (Forward Bias)}$$

31)

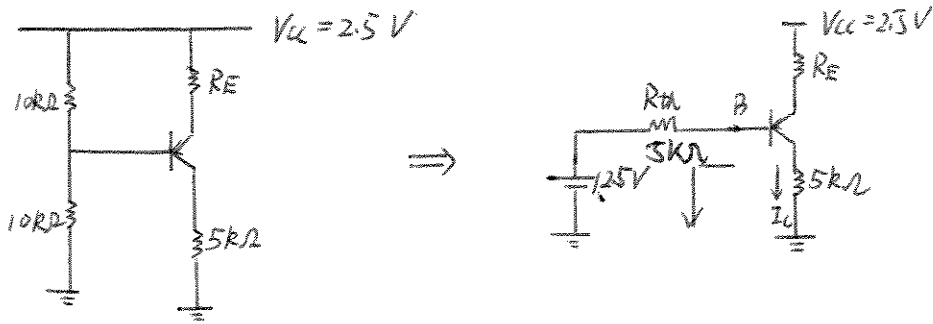

$$V_{BC} = 1.25 + I_B R_{TH} - I_C 5K = 0.3$$

$$1.25 + \frac{I_C 5}{\beta} - I_C 5K = 0.3$$

$$\beta = 50 \Rightarrow I_C = 0.1939 \text{ mA}$$

$$|V_{BE}| = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.682 \text{ V}$$

$$I_B = \frac{(2.5 - \frac{I_C R_E}{\alpha} - |V_{BE}|) - 1.25}{5K}$$

$$\alpha = 0.9804$$

$$I_B = 0.003878 \text{ mA}$$

$$|V_{BE}| = 0.682 \text{ V}$$

$$I_C = 0.1939 \text{ mA}$$

$$R_E = 2.89 \text{ k}\Omega$$

If  $R_E$  is halved  $\Rightarrow R_E = 1.44 \text{ k}\Omega$

$$I_C = \beta \left( \frac{2.5 - |V_{BE}| - 1.25 - \alpha I_C R_E}{5K} \right)$$

$$I_C = \frac{62.5 - 50|V_{BE}|}{78.44}, \quad \text{Guess } |V_{BE}| = 0.682 \text{ V}$$

31)

$$I_c = 0.3621 \text{ mA}$$

Verify  $|V_{BE}| = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.698 \text{ V}$ , not  $0.682 \text{ V}$   
reiterate

$$I_c = \frac{62.5 - 50(0.698)}{78.44} = 0.352 \text{ mA}$$


Verify  $|V_{BE}| = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.697 \text{ V}$ , converged

so  $I_c = 0.352 \text{ mA}$ , which is 1.82 times of  $0.1939 \text{ mA}$

$$V_{BC} = 1.25 + \frac{(0.352)(5 \text{ k}\Omega)}{50} - (0.352)(5 \text{ k}\Omega) = -0.4748 \text{ V}$$

which drive  $Q_1$  into saturation.

322

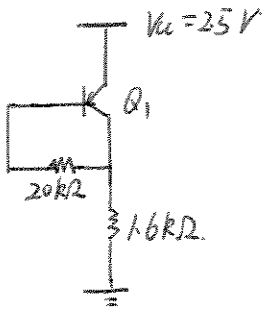

$$\beta = 80$$

$$V_A = \infty$$

$$V_B = (I_B)(20k\Omega) + I_E(1.6k\Omega)$$

$$I_C = 1\text{mA}$$

$$I_B = \frac{1}{80}\text{mA}, \quad I_E = \frac{1}{0.98765}\text{mA} = 1.0125\text{mA}$$

$$V_B = \left(\frac{1}{80}\right)(20)V + (1.0125)(1.6)V$$


$$= 1.87V$$

$$|V_{BE}| = 25V - 1.87V = 0.63V$$

$$I_C = I_S e^{\left(\frac{V_{BE}}{V_T}\right)} \Rightarrow I_S = \frac{I_C}{e^{\left(\frac{V_{BE}}{V_T}\right)}} = \frac{1\text{mA}}{e^{\left(\frac{0.63}{0.026}\right)}}$$

$$I_S = 3 \times 10^{-11}\text{mA}$$

33)

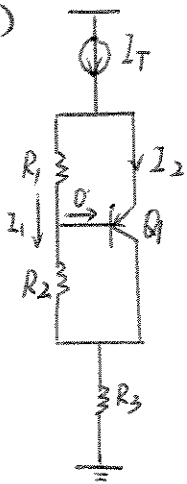

If Base current is neglected,  $I_C = I_E$


$$I_1 = \frac{V_E - V_C}{R_1 + R_2}$$

$$|V_{BE}| = I_1 R_1 = \frac{V_E - V_C}{R_1 + R_2} R_1 = \frac{|V_{CE}|}{R_1 + R_2} R_1$$

$$\text{So } \frac{|V_{CE}|}{|V_{BE}|} = \frac{R_1 + R_2}{R_1}$$

Let  $A = \frac{R_1 + R_2}{R_1}$ ,  $|V_{CE}| = A |V_{BE}|$ , thus  $|V_{BE}|$  is multiplied.

34)

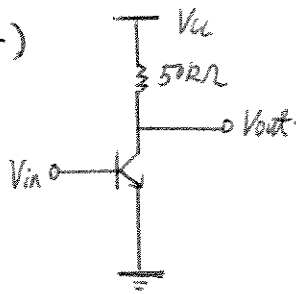

$$A_V = g_m R_C = 20$$

$$\frac{I_C R_C}{V_T} = 20 \Rightarrow I_C = \frac{20 V_T}{R_C}$$


$$I_C = 0.0104 \text{ mA}$$

$$V_{CC} - (50 \text{ k}\Omega) (0.0104 \text{ mA}) = V_{BE}$$

$$\Rightarrow V_{CC} - 50 \times 0.0104 \text{ V} = 0.8 \text{ V}$$

$$\Rightarrow V_{CC} = 1.32 \text{ V}$$



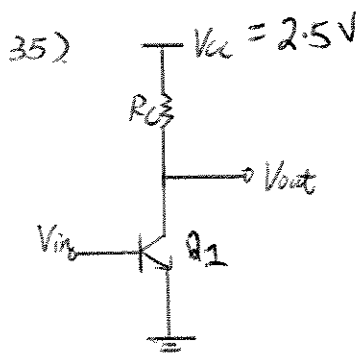

$$V_A = 10V, r_o = \frac{V_A}{I_C}, g_m = \frac{I_C}{V_T}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = g_m (R_C // r_o) = g_m \left( \frac{R_C r_o}{R_C + r_o} \right) = \frac{R_C V_A}{V_T \left( R_C + \frac{V_A}{I_C} \right)}$$

As the equation above shows, a large gain means a large  $I_C$ . However, a large  $I_C$  will drive  $Q_1$  into saturation. So a tradeoff must be made. The maximum limit for  $I_C$  is when it drives  $Q_1$  into the edge of saturation, namely,  $V_{BE} = V_{CE}$ .


$$V_{CE} = V_{CC} - I_C (1K)$$

$$V_{BE} = 0.8V, V_{CC} = 2.5V$$

$$0.8 = 2.5 - I_C 1K$$

$$I_C = 1.7mA$$

36)

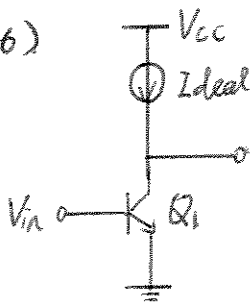


$$A_v = 50$$

$$R_{out} = R_o = 10k\Omega$$

$$A_v = g_m R_{out} = \frac{I_c}{V_T} R_{out} = 50$$

$$I_c = 50 \left( \frac{V_T}{R_{out}} \right) = 0.13mA$$

37).

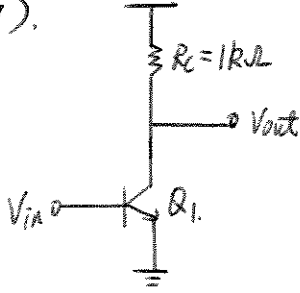


$$I_c = I_s \exp\left(\frac{V_{BE}}{2V_T}\right)$$

$$g_m = \frac{\partial I_c}{\partial V_{BE}} = \frac{I_c}{2V_T}$$

$$R_{out} = R_c$$

$$\left|\frac{V_{out}}{V_{in}}\right| = g_m R_{out} = \frac{I_c R_c}{2V_T} = \frac{(1mA)(1K\Omega)}{(2)(0.026V)} = 19.23$$

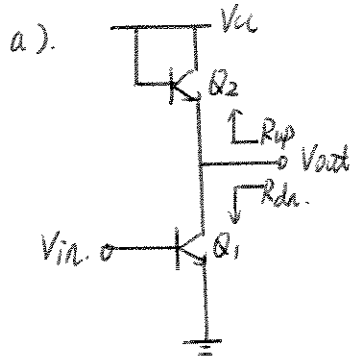38). (Find  $A_v$ ,  $R_{in}$ ,  $R_{out}$ )



$$V_A = \infty$$


$$R_{out} = R_{up} // R_{dn}$$

$$R_{up} = \frac{1}{g_{m2}} // Y_{\pi 2}, \quad R_{dn} = \infty$$

$$R_{out} = \frac{1}{g_{m2}} // Y_{\pi 2}$$

$$R_{in} = Y_{\pi 1}$$

$$A_v = \left| \frac{V_{out}}{V_{in}} \right| = g_{m1} \left( \frac{1}{g_{m2}} // Y_{\pi 2} \right)$$

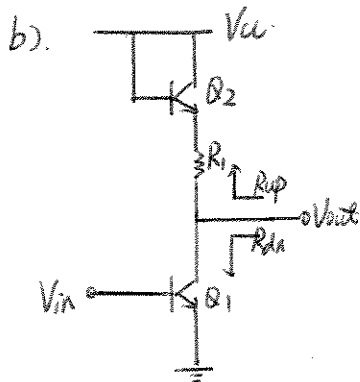

$$V_A = \infty$$

$$R_{up} = R_1 + \frac{1}{g_{m2}} // Y_{\pi 2}$$


$$R_{dn} = \infty$$

$$R_{out} = R_{up} // R_{dn} = R_1 + \frac{1}{g_{m2}} // Y_{\pi 2}$$

$$R_{in} = Y_{\pi 1}$$

$$A_v = \left| \frac{V_{out}}{V_{in}} \right| = g_{m1} \left( R_1 + \frac{1}{g_{m2}} // Y_{\pi 2} \right)$$

38  
c).

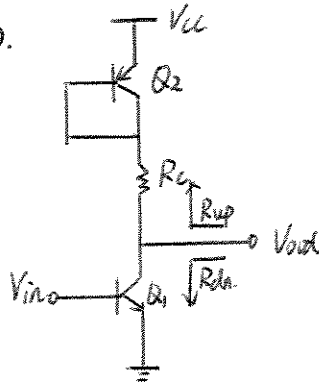


$$V_A = \infty$$


$$R_{up} = R_c + \left( \frac{1}{g_{m2}} \parallel Y_{\pi 2} \right), R_{dn} = \infty$$

$$R_{out} = R_c + \left( \frac{1}{g_{m2}} \parallel Y_{\pi 2} \right), R_{in} = Y_{\pi 1}$$
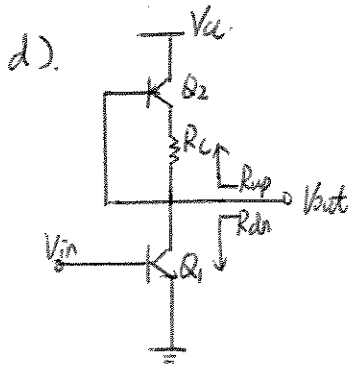
$$A_v = g_{m2} \left( R_c + \left( \frac{1}{g_{m2}} \parallel Y_{\pi 2} \right) \right)$$



Find  $R_{up}$ :

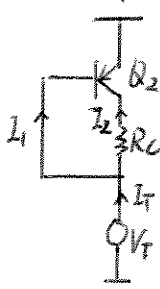

$$I_T = I_1 + I_2 = \frac{I_2}{\beta} + I_2$$

$$I_2 = g_m V_T, I_T = \frac{g_m V_T}{\beta} + g_m V_T$$

$$\frac{V_T}{I_T} = R_{up} = \frac{1}{\left( \frac{g_m}{\beta} + g_m \right)} = Y_{\pi 2} \parallel \frac{1}{g_{m2}}$$

$$R_{dn} = \infty$$


$$R_{out} = R_{up} \parallel R_{dn} = Y_{\pi 2} \parallel \frac{1}{g_{m2}}$$

$$R_{in} = Y_{\pi 1}$$

$$A_v = g_{m2} \left( Y_{\pi 2} \parallel \frac{1}{g_{m2}} \right)$$

38).

e).

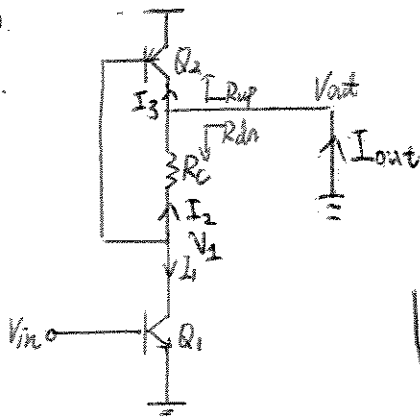

$$R_{up} = \infty$$

$$R_{dn} = R_c + r_{\pi 2}$$

$$R_{out} = R_c + r_{\pi 2}$$

$$|A_v| = G_m R_{out}$$

$$\text{where } G_m = \left| \frac{I_{out}}{V_{in}} \right|$$

$$I_{out} + I_2 = I_3, \quad I_2 = \frac{V_1}{R_c}$$

$$I_3 = V_1 g_{m2}$$

$$V_1 = -I_2 (R_c \parallel r_{\pi 2}) = -g_{m1} V_{in} (R_c \parallel r_{\pi 2})$$


$$I_{out} = I_3 - I_2 = V_1 \left( g_{m2} - \frac{1}{R_c} \right)$$

$$I_{out} = -g_{m1} V_{in} (R_c \parallel r_{\pi 2}) \left( g_{m2} - \frac{1}{R_c} \right)$$

$$G_m = \left| \frac{I_{out}}{V_{in}} \right| = g_{m1} (R_c \parallel r_{\pi 2}) \left( g_{m2} - \frac{1}{R_c} \right)$$

$$|A_v| = g_{m1} (R_c \parallel r_{\pi 2}) \left( g_{m2} - \frac{1}{R_c} \right) (R_c + r_{\pi 2})$$

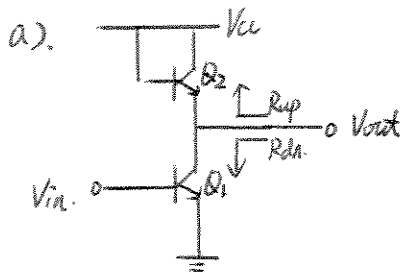39).  $V_A < \infty$ , find  $A_v$ ,  $R_{in}$ ,  $R_{out}$




$$R_{up} = \frac{1}{g_{m2}} \parallel r_{e2} \parallel r_{o2}, \quad R_{dn} = r_{o1}$$

$$R_{out} = \frac{1}{g_{m2}} \parallel r_{e2} \parallel r_{o1} \parallel r_{o2}$$

$$R_{in} = r_{e1}$$

$$|A_v| = g_{m1} \left( \frac{1}{g_{m2}} \parallel r_{e1} \parallel r_{o1} \parallel r_{o2} \right)$$

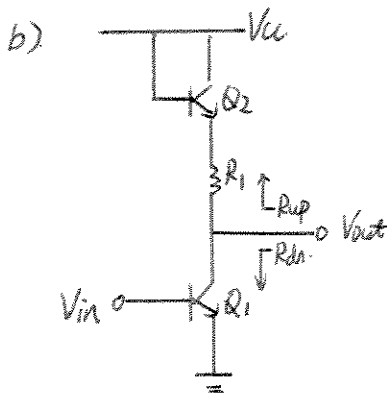


$$R_{up} = R_1 + \frac{1}{g_{m2}} \parallel r_{e2} \parallel r_{o2}$$

$$R_{dn} = r_{o1}$$

$$R_{out} = r_{o1} \parallel \left( R_1 + \frac{1}{g_{m2}} \parallel r_{e2} \parallel r_{o2} \right)$$

$$R_{in} = r_{e1}$$

$$|A_v| = g_{m1} \left[ r_{o1} \parallel \left( R_1 + \frac{1}{g_{m2}} \parallel r_{e2} \parallel r_{o2} \right) \right]$$

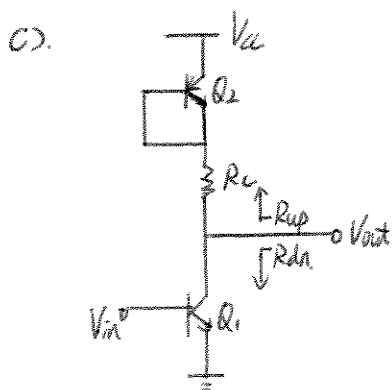

$$R_{up} = R_c + \frac{1}{g_{m2}} \parallel r_{e2} \parallel r_{o2}$$


$$R_{dn} = r_{o1}$$

$$R_{in} = r_{e1}$$


$$R_{out} = r_{o1} \parallel \left( R_c + \frac{1}{g_{m2}} \parallel r_{e2} \parallel r_{o2} \right)$$

$$|A_v| = g_{m1} \left[ r_{o1} \parallel \left( R_c + \frac{1}{g_{m2}} \parallel r_{e2} \parallel r_{o2} \right) \right]$$

39 d)

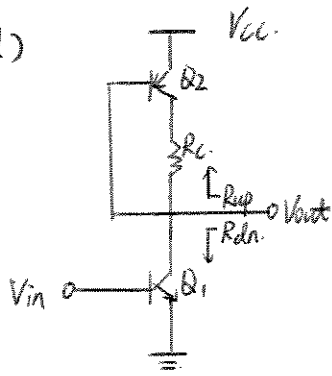

Find  $R_{up}$ :

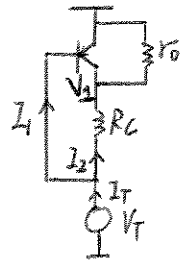

$$I_T = I_1 + I_2$$

$$I_2 = \frac{V_T - V_1}{R_c}, \quad I_1 = \frac{g_m V_T}{\beta}$$

$$V_1 = (I_2 - g_m V_T) r_o$$

$$I_2 = \frac{V_T - (I_2 - g_m V_T) r_o}{R_c}$$

$$I_2 = \frac{(1 + g_m r_o) V_T}{R_c + r_o}$$

$$I_T = \frac{g_m V_T}{\beta} + \frac{(1 + g_m r_o) V_T}{R_c + r_o}$$

$$\frac{V_T}{I_T} = R_{up} = \frac{1}{\frac{g_m}{\beta} + \frac{(1 + g_m r_o)}{R_c + r_o}}$$

$$R_{up} = Y_{\pi 2} \parallel \frac{(R_c + Y_{o2})}{1 + g_{m2} Y_{o2}}$$

$$R_{dn} = Y_{o1}$$

$$R_{out} = Y_{\pi 2} \parallel \frac{(R_c + Y_{o2})}{1 + g_{m2} Y_{o2}} \parallel Y_{o1}$$


$$R_{in} = Y_{\pi 2}$$

$$|A| = \left| \frac{V_{out}}{V_{in}} \right| = g_{m2} \left( Y_{\pi 2} \parallel \frac{(R_c + Y_{o2})}{1 + g_{m2} Y_{o2}} \parallel Y_{o1} \right)$$

$$R_{up} = Y_{\pi 2} \parallel \frac{R_c + r_o}{(1 + g_m r_o)}$$



39 e).

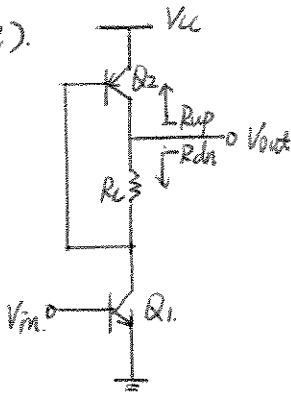

$$R_{up} = r_{o2}$$


$$R_{dn} = R_C + (r_{o1} \parallel r_{z2})$$

$$R_{in} = r_{z1}$$

$$R_{out} = r_{o2} \parallel [R_C + (r_{o1} \parallel r_{z2})]$$

$$|A_v| = G_m R_{out}$$

Finding  $G_m$ :

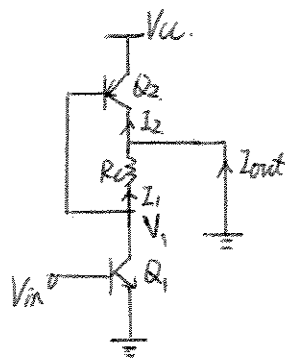

$$G_m = \left| \frac{I_{out}}{V_{in}} \right|$$

$$I_{out} + I_1 = I_2$$

$$I_{out} = I_2 - I_1$$

$$I_1 = \frac{V_1}{R_C} \quad I_2 = V_1 g_{m2}$$

$$V_1 = -(g_{m1} V_{in}) (r_{o1} \parallel R_C \parallel r_{z2})$$

$$I_{out} = V_1 \left( g_{m2} - \frac{1}{R_C} \right) = -g_{m1} V_{in} (r_{o1} \parallel R_C \parallel r_{z2}) \left( g_{m2} - \frac{1}{R_C} \right)$$

$$G_m = \left| \frac{I_{out}}{V_{in}} \right| = g_{m1} (r_{o1} \parallel R_C \parallel r_{z2}) \left( g_{m2} - \frac{1}{R_C} \right)$$

$$|A_v| = g_{m1} (r_{o1} \parallel R_C \parallel r_{z2}) \left( g_{m2} - \frac{1}{R_C} \right) \left[ r_{o2} \parallel [R_C + (r_{o1} \parallel r_{z2})] \right]$$

40)

Gain of a degenerated CE stage ( $V_A = \infty$ )

$$A_v = \frac{-R_c}{\frac{1}{g_m} + R_E} = \frac{-R_c g_m}{1 + R_E g_m}$$

$$\frac{\partial A_v}{\partial I_c} = R_c \left( \frac{g_m R_E}{(1 + R_E g_m)^2} \frac{\partial g_m}{\partial I_c} - \frac{\partial g_m / \partial I_c}{1 + g_m R_E} \right)$$

$$\frac{\partial g_m}{\partial I_c} = \frac{1}{V_T} = \frac{1}{26 \text{ mV}} = 38.46 \left( \frac{1}{\text{V}} \right)$$

a)  $g_m R_E = 3$

$$\frac{\partial A_v}{\partial I_c} = R_c (-2.404) \quad , \quad \partial I_c = 0.1 I_c$$

$$\partial A_v = -R_c I_c (0.24)$$

$$\text{Relative change in gain} = \frac{\partial A_v}{A_v} = \frac{-0.24 (R_c I_c)}{-\frac{R_c I_c}{V_T (1 + R_E g_m)}} = 2.5\%$$

40)


$$b) g_m R_E = 7$$

$$\frac{\partial A_v}{\partial I_c} = -R_c \cdot 0.6$$

$$\partial A_v = -R_c I_c (0.06)$$

Relative change in gain
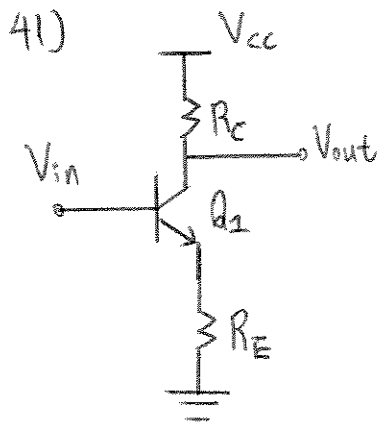
$$\frac{\partial A_v}{A_v} = \frac{-0.06 (R_c I_c)}{\frac{-R_c I_c}{V_T (1 + R_E g_m)}} = 1.25\%$$



$$V_A = \infty$$

$$R_C I_C = 20 V_T$$

$$R_E I_C = 5 V_T$$


$$|A_v| = \frac{R_C}{R_E + \frac{1}{g_m}} = \frac{R_C}{R_E + \frac{V_T}{I_C}} = \frac{R_C I_C}{R_E I_C + V_T}$$

Assume  $\beta$  is large, so  $I_C = I_E$ .

$$R_C I_C = 20 V_T, \quad R_E I_C = 5 V_T$$

$$|A_v| = \frac{20 V_T}{5 V_T + V_T} = \frac{20 V_T}{6 V_T} = 3.33$$

42)

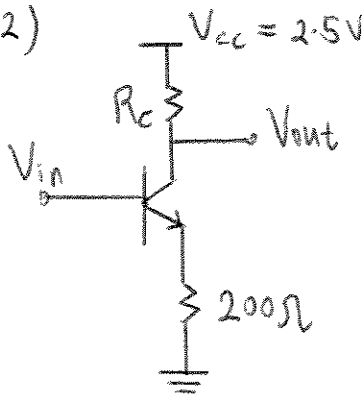

$$|A_v| = \frac{R_c I_c}{R_E I_c + V_T} = 10$$

Edge of Saturation

$$V_{CE} = V_{BE} = 2.5 - I_c (R_c + R_E)$$

$$V_{BE} = 0.8 \text{ V} \Rightarrow I_c R_c = 1.7 - I_c 0.2 \quad (\text{operating point})$$

$$|A_v| = 10 \Rightarrow R_c I_c = 10 (R_E I_c + V_T) \quad (\text{Gain Equation})$$

Equating the two equations above  $\Rightarrow$ 

$$1.7 - 0.2 I_c = 2 I_c + 0.26 \Rightarrow I_c = 0.655 \text{ mA}$$

Check for  $V_{BE} \Rightarrow V_{BE} = V_T \ln\left(\frac{I_c}{I_0}\right) = 0.725$ , not 0.8, Reiterate

$$I_c R_c = 1.775 - I_c 0.2 \quad (\text{operating point})$$

$$I_c R_c = 2 I_c + 0.26 \quad (\text{Gain equation})$$

Equating the two equations  $\Rightarrow I_c = 0.689 \text{ mA}$ Check for  $V_{BE} \Rightarrow V_{BE} = V_T \ln\left(\frac{I_c}{I_0}\right) = 0.727 \text{ V}$ , iterate 1 more time

$$I_c R_c = 1.773 - I_c 0.2 \quad (\text{operating point})$$

$$I_c R_c = 2 I_c + 0.26 \quad (\text{Gain equation})$$

42)

Equating the two equations  $\Rightarrow I_c = 0.688 \text{ mA}$

Check for  $V_{BE} \Rightarrow V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.727 \text{ V}$ , converged

$$I_c = 0.688 \text{ mA}$$


$$R_c = \frac{2I_c + 0.26}{I_c} = \frac{(2 \times 0.688) + 0.26}{0.688}$$

$$R_c = 2.38 \text{ k}\Omega$$

$$R_{in} = r_{\pi} + (1 + \beta) R_E$$

$$R_{in} = \frac{\beta}{g_m} + (101)(0.2) = 24.0 \text{ k}\Omega$$

43)

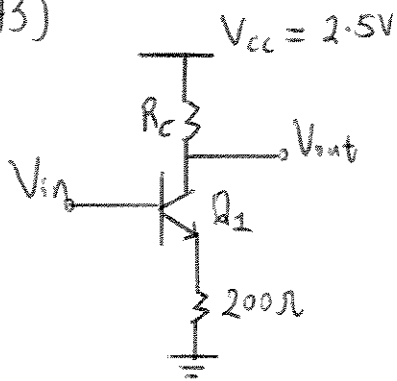

$|A_v| = 100$   
(Voltage gain)

$$|A_v| = 100 \Rightarrow R_c I_c = 100 (R_E I_c + V_T)$$

$$R_c I_c = 20 I_c + 2.6 \quad (1)$$

$$R_c I_c = 1.7 - I_c 0.2 \quad (2) \quad (\text{Assume } V_{BE} = 0.8)$$

Equating (1) and (2) yield

$$1.7 - I_c 0.2 = 20 I_c + 2.6 \Rightarrow I_c = -0.04455 \text{ mA}$$

A negative  $I_c$  in forward active region is impossible, therefore, a solution does not exist. The reason is because  $R_c I_c$  is too large to produce a gain of 100 that drive  $Q_1$  into saturation region.

Maximum gain achievable:

$$\frac{R_c I_c}{R_E I_c + V_T} = |A_v| \quad (\text{Gain Equation})$$

$$2.5 = R_c I_c + V_{CE} + R_c I_c \quad (\text{Operating Point Equation})$$

Let  $A = \text{Maximum gain}$

43)

$$AI_c 0.2 + A 0.026 = 1.7 - I_c 0.2$$

$$\Rightarrow I_c = \frac{1.7 - A 0.026}{A 0.2 + 0.2}$$

Since  $I_c$  cannot be zero, set

$$\frac{1.7 - A 0.026}{A 0.2 + 0.2} > 0$$



$$1.7 - A 0.026 > 0$$

$$1.7 > A 0.026$$

$$A < \frac{1.7}{0.026} = 65.4 \text{ (Maximum gain achievable)}$$



44)  $V_A = \infty$

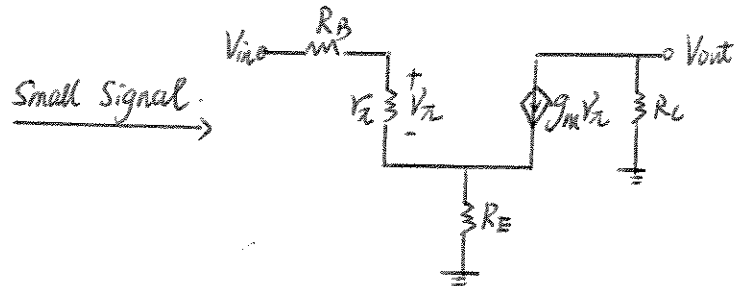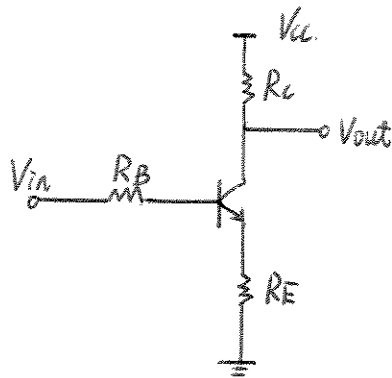


$$V_{out} = -g_m v_{\pi} R_C$$

$$v_{\pi} = \frac{V_{in} r_{\pi}}{R_B + r_{\pi} + (\beta + 1) R_E}$$


$$V_{out} = \frac{-g_m r_{\pi} R_C V_{in}}{R_B + r_{\pi} + (\beta + 1) R_E} = \frac{-\beta R_C V_{in}}{R_B + r_{\pi} + (\beta + 1) R_E} = \frac{-R_C V_{in}}{\frac{R_B}{\beta} + \frac{1}{g_m} + \frac{\beta + 1}{\beta} R_E}$$

$$\frac{V_{out}}{V_{in}} \approx \frac{-R_C}{\frac{R_B}{\beta + 1} + \frac{1}{g_m} + R_E}$$

45)

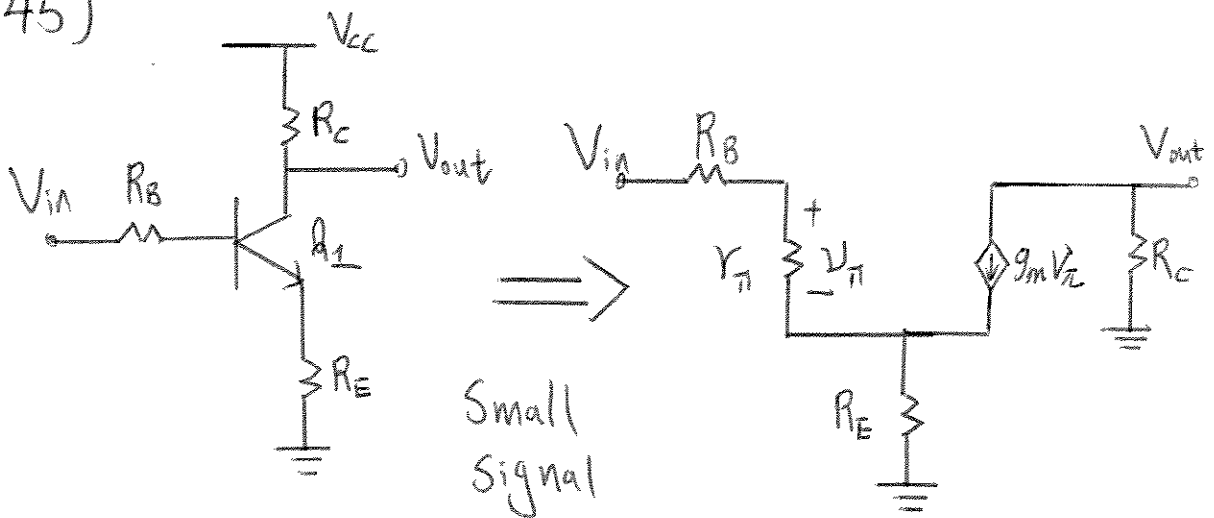

$R_{out}$  Calculation:

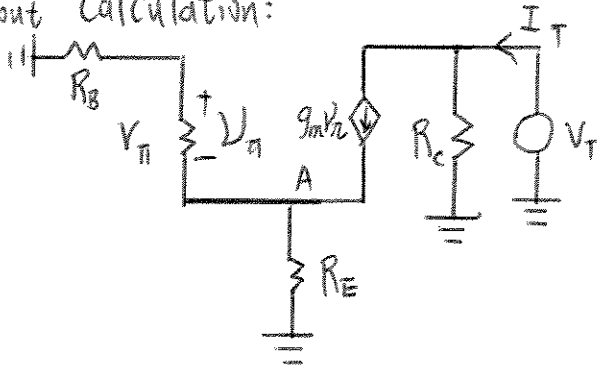

$$V_A = g_m V_{\pi} (R_E \parallel R_B + r_{\pi}) \quad (1)$$


$$V_{\pi} = -\frac{V_A r_{\pi}}{r_{\pi} + R_B} \Rightarrow V_A = -\frac{V_{\pi} (r_{\pi} + R_B)}{r_{\pi}} \quad (2)$$

The only possible solution for 1) and 2) is  $V_{\pi} = V_A = 0$ ,  
 since 1) is positive and 2) is negative.

$$V_{\pi} = 0 \Rightarrow g_m V_{\pi} \Rightarrow 0 \Rightarrow \frac{V_T}{I_T} = R_C$$

Therefore,  $R_{out} = R_C$

4b)  $V_A = \infty$

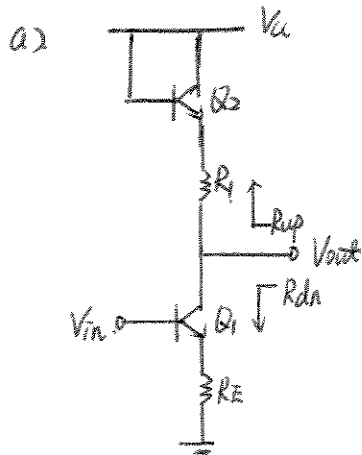


$$R_{up} = R_1 + \frac{1}{g_{m2}} \parallel r_{e2}$$

$$R_{dn} = \infty$$

$$R_{out} = R_1 + \frac{1}{g_{m2}} \parallel r_{e2}$$

$$R_{in} = r_{e1} + (1 + \beta) R_E$$

$$|A_v| = \frac{R_1 + \frac{1}{g_{m2}} \parallel r_{e2}}{R_E + \frac{1}{g_{m1}}}$$

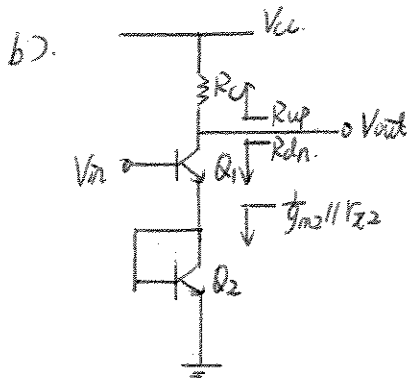


$$R_{up} = R_C$$

$$R_{dn} = \infty$$

$$R_{out} = R_C$$

$$R_{in} = r_{e1} + (\beta + 1) \left( \frac{1}{g_{m2}} \parallel r_{e2} \right)$$

$$|A_v| = \frac{R_C}{\frac{1}{g_{m2}} \parallel r_{e2} + \frac{1}{g_{m1}}}$$

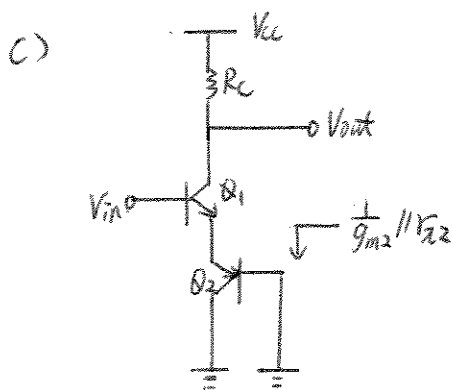


$$R_{out} = R_C$$

$$R_{in} = r_{e1} + (\beta + 1) \left( \frac{1}{g_{m2}} \parallel r_{e2} \right)$$

$$|A_v| = \frac{R_C}{\frac{1}{g_{m2}} \parallel r_{e2} + \frac{1}{g_{m1}}}$$

4b).  
d).

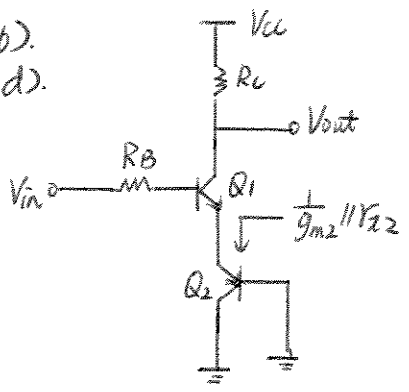


$$R_{out} = R_C$$


$$R_{in} = R_B + r_{e1} + (\beta + 1) \left( \frac{1}{g_{m2}} \parallel r_{E2} \right)$$

$$|A_v| = \frac{R_C}{\frac{1}{g_{m2}} \parallel r_{E2} + \frac{1}{g_{m1}} + \frac{R_B}{\beta + 1}}$$

e)

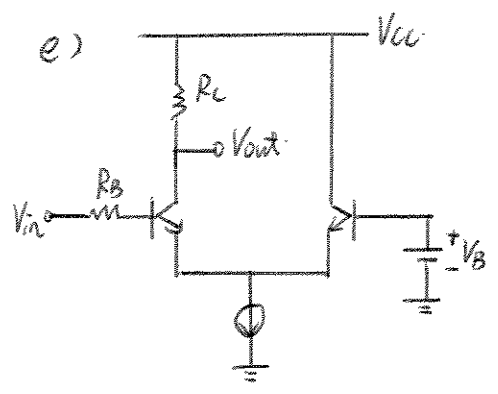

⇒

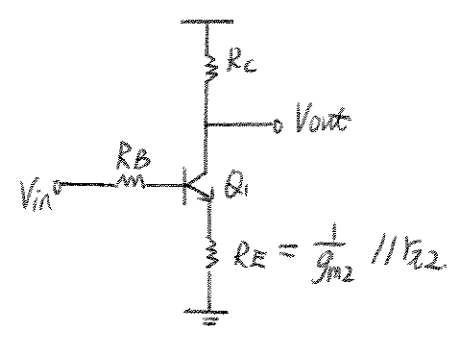


$$R_{out} = R_C$$

$$R_{in} = R_B + r_{e1} + (\beta + 1) \left( \frac{1}{g_{m2}} \parallel r_{E2} \right)$$

$$|A_v| = \frac{R_C}{\frac{1}{g_{m2}} \parallel r_{E2} + \frac{1}{g_{m1}} + \frac{R_B}{\beta + 1}}$$

47)  $V_A = \infty$ .

a)

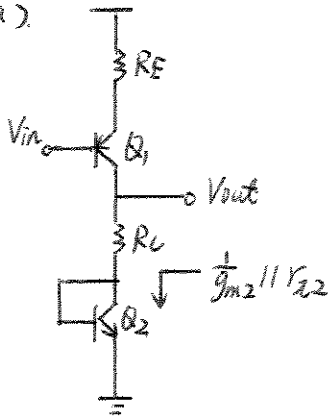

$$R_{out} = R_C + \frac{1}{g_{m2} \parallel Y_{L2}}$$


$$R_{in} = r_{\pi 1} + (1 + \beta) R_E$$

$$|A_v| = \frac{R_C + \frac{1}{g_{m2} \parallel Y_{L2}}}{R_E + \frac{1}{g_{m1}}}$$


b)  $R_{out} = \frac{1}{g_{m2} \parallel Y_{L2}}$

$$R_{in} = r_{\pi 1} + (1 + \beta) R_E$$

$$|A_v| = \frac{\frac{1}{g_{m2} \parallel Y_{L2}}}{R_E + \frac{1}{g_{m1}}}$$

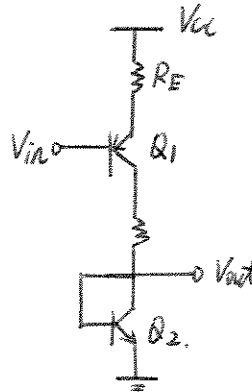

c)

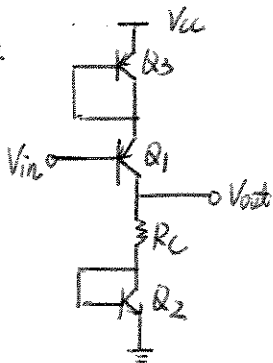

$$R_{out} = R_C + \frac{1}{g_{m2} \parallel Y_{L2}}$$


$$R_{in} = r_{\pi 1} + (1 + \beta) \left( \frac{1}{g_{m3} \parallel Y_{L3}} \right)$$

$$|A_v| = \frac{R_C + \frac{1}{g_{m2} \parallel Y_{L2}}}{\frac{1}{g_{m1}} + \frac{1}{g_{m3} \parallel Y_{L3}}}$$


d)  $R_{out} = R_C \parallel Y_{L2}$

$$R_{in} = r_{\pi 1} + (\beta + 1) R_E$$

$$|A_v| = \frac{R_C \parallel Y_{L2}}{R_E + \frac{1}{g_{m1}}}$$

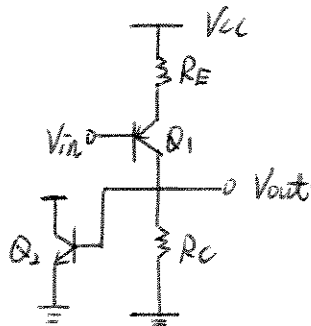


48)

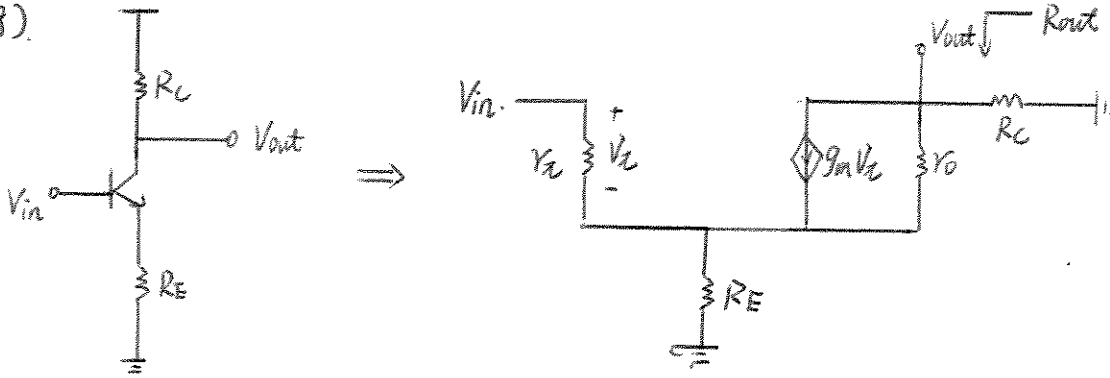

$$R_{out} = R_c \parallel R_{eq}$$

Solve for  $R_{eq}$ .

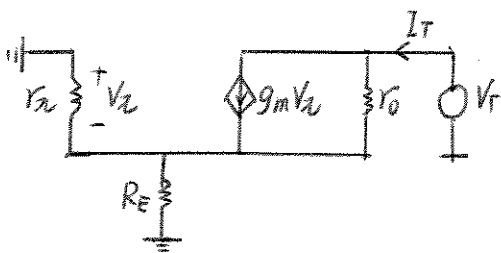

$$I_T = g_m v_{\pi} + \frac{(V_T + v_{\pi})}{r_o}$$

$$v_{\pi} = -I_T (r_{\pi} \parallel R_E)$$

$$I_T = -g_m I_T (r_{\pi} \parallel R_E) + \frac{(V_T - I_T (r_{\pi} \parallel R_E))}{r_o}$$

$$\frac{V_T}{I_T} = r_o \left( 1 + \frac{(r_{\pi} \parallel R_E)}{r_o} \right) + g_m (r_{\pi} \parallel R_E)$$

$$\frac{V_T}{I_T} = r_o + (1 + g_m r_o) (r_{\pi} \parallel R_E)$$


$$R_{eq} = r_o + (1 + g_m r_o) (r_{\pi} \parallel R_E)$$

$$R_{out} = R_c \parallel r_o + (1 + g_m r_o) (r_{\pi} \parallel R_E)$$

$$R_{out} \approx R_c \parallel r_o (1 + g_m (r_{\pi} \parallel R_E)) \quad \text{since } g_m r_o \gg 1$$

49).  $\beta \gg 1$  and  $V_A < \infty$  to have meaningful result.

a).

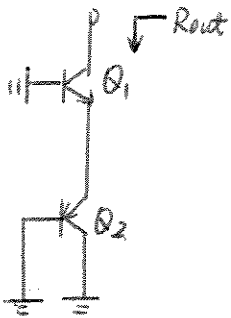


$$\frac{1}{g_{m2}} \parallel r_{e2} \approx \frac{1}{g_{m2}}, \text{ since } \beta \gg 1$$

$$R_{out} = r_{o1} + (1 + g_{m1} r_{o1}) \left( \frac{1}{g_{m2}} \parallel r_{e2} \right)$$

$$= r_{o1} (1 + g_{m1}/g_{m2})$$

b).

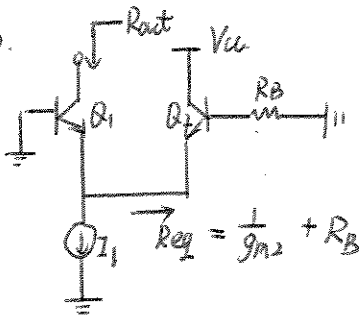


$$R_{out} = r_{o1} + (1 + g_{m1} r_{o1}) \left[ \left( \frac{1}{g_{m2}} + \frac{R_B}{\beta + 1} \right) \parallel r_{e1} \right]$$

$$\approx r_{o1} + (1 + g_{m1} r_{o1}) \left( \frac{1}{g_{m2}} + \frac{R_B}{\beta} \right)$$

$$\approx r_{o1} \left[ 1 + g_{m1} \left( \frac{1}{g_{m2}} + \frac{R_B}{\beta} \right) \right]$$

c).

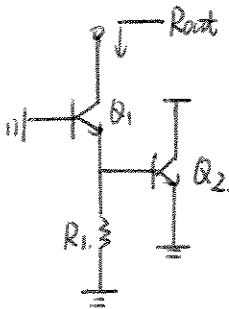


$$R_{out} = r_{o1} + (1 + g_{m1} r_{o1}) (R_1 \parallel r_{e2} \parallel r_{e1})$$

$$R_1 \parallel r_{e1} \parallel r_{e2} \approx R_1, \text{ since } \beta \gg 1.$$


$$R_{out} \approx r_{o1} (1 + g_{m1} R_1)$$

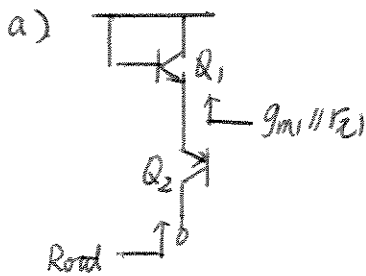50)  $\beta \gg 1$ ,  $V_A \gg 10$ , for meaningful results



$$R_{out} = r_{O2} + (1 + g_{m2} r_{O2}) \left( \frac{1}{g_{m1}} \parallel r_{O1} \right)$$

$$\approx r_{O2} (1 + g_{m2} / g_{m1})$$

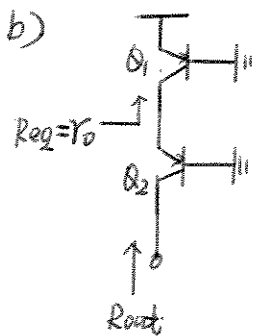

$$R_{out} = r_{O2} + (1 + g_{m2} r_{O2}) (r_{O1} \parallel r_{O2})$$

$$\approx r_{O2} [1 + g_{m2} (r_{O1} \parallel r_{O2})]$$

The output impedance in b) is larger than a) because  $Q_2$ 's connected for a high impedance load, whereas in a) it's connected to a low impedance load.



$$51). r_2 = \beta V_T / I_C.$$


$$R_{in} = r_2 \parallel R_B = \frac{\frac{\beta V_T}{I_C} R_B}{\frac{\beta V_T}{I_C} + R_B} = \frac{V_T R_B}{V_T + \frac{I_C}{\beta} R_B} = \frac{V_T R_B}{V_T + 2R_B}$$

$$\text{Since } I_B R_B \gg V_T \Rightarrow R_{in} \approx \frac{V_T R_B}{I_B R_B} = \frac{V_T}{I_B} = \frac{V_T}{\frac{I_C}{\beta}} = \frac{\beta V_T}{I_C} \approx r_2$$


$$\text{So } R_{in} = r_2 \parallel R_B \approx r_2.$$

52)  $I_S = 8 \times 10^{-6} \text{ A}$ ,  $\beta = 100$ ,  $V_A = \infty$

a).

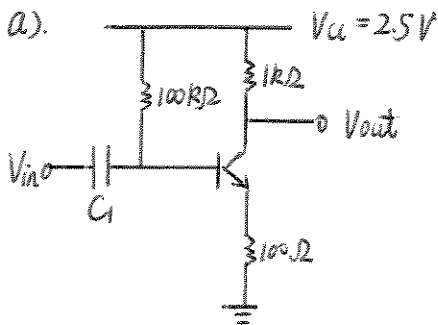

DC Analysis

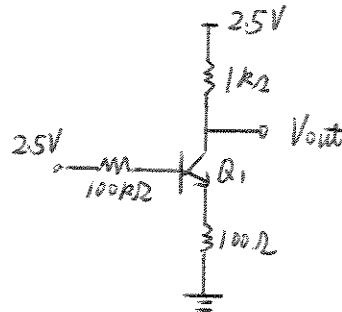

$$I_c = \frac{\beta (2.5 - (V_{BE} + \frac{I_c}{\alpha} 0.1))}{100k} \Rightarrow I_c = \frac{100 (2.5 - V_{BE})}{100k + 10.1k}$$

Guess  $V_{BE} = 0.75 \text{ V}$ ,  $I_c = 1.59 \text{ mA}$

Verify  $V_{BE} = V_T \ln(\frac{I_c}{I_S}) = 0.736 \text{ V}$ , not  $0.75 \text{ V}$ , reiterate


$V_{BE} = 0.736 \text{ V}$ ,  $I_c = 1.60 \text{ mA}$

Verify  $V_{BE} = V_T \ln(\frac{I_c}{I_S}) = 0.736 \text{ V}$ , converged !!

$I_c = 1.60 \text{ mA}$

$g_m = \frac{I_c}{V_T} = \frac{1.60 \text{ mA}}{26 \text{ mV}} = 0.0615 (\frac{1}{\Omega}) \text{ S}$

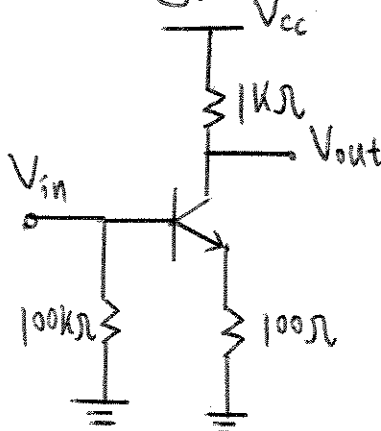
$r_{\pi} = \frac{\beta}{g_m} = 1.63 \text{ k}\Omega$



$$A_v = \left| \frac{V_{out}}{V_{in}} \right| = \frac{1k}{0.1 + \frac{1}{g_m}} = 8.6$$

52)

b)

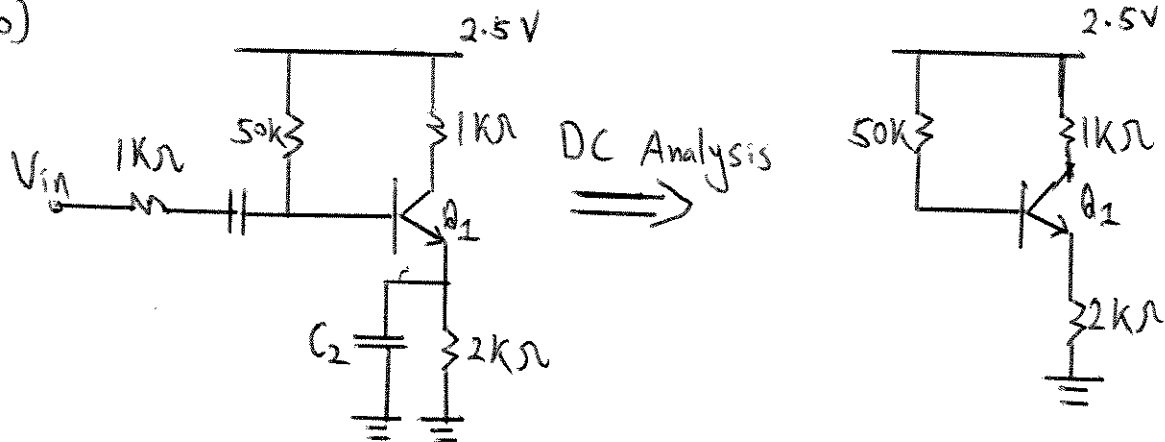

$$I_c = \beta \left( \frac{2.5 - (V_{BE} + I_E 2K)}{50K} \right) \Rightarrow I_c = \frac{100(2.5 - V_{BE})}{50K + 202K}$$

Guess  $V_{BE} = 0.7V$ ,  $I_c = 0.714 mA$

Verify  $V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.7155V$ , reiterate.

$V_{BE} = 0.7155V$ ,  $I_c = 0.708 mA$


Verify  $V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.715V$ , converged!!

$I_c = 0.708 mA$

$g_m = \frac{I_c}{V_T} = 0.02723 \left(\frac{1}{\Omega}\right) S$

$V_{BE} = 0.715V$

AC Analysis:

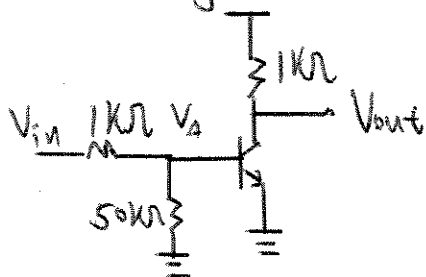


$$\left| \frac{V_{out}}{V_{in}} \right| = \left| \frac{V_{out}}{V_A} \right| \left| \frac{V_A}{V_{in}} \right| = 21.1$$

$$\left| \frac{V_{out}}{V_A} \right| = g_m 1K\Omega = 27.23$$

$$\left| \frac{V_A}{V_{in}} \right| = \frac{50K // V_{\pi}}{50K // V_{\pi} + 1K} = 0.77$$

52 )

c)

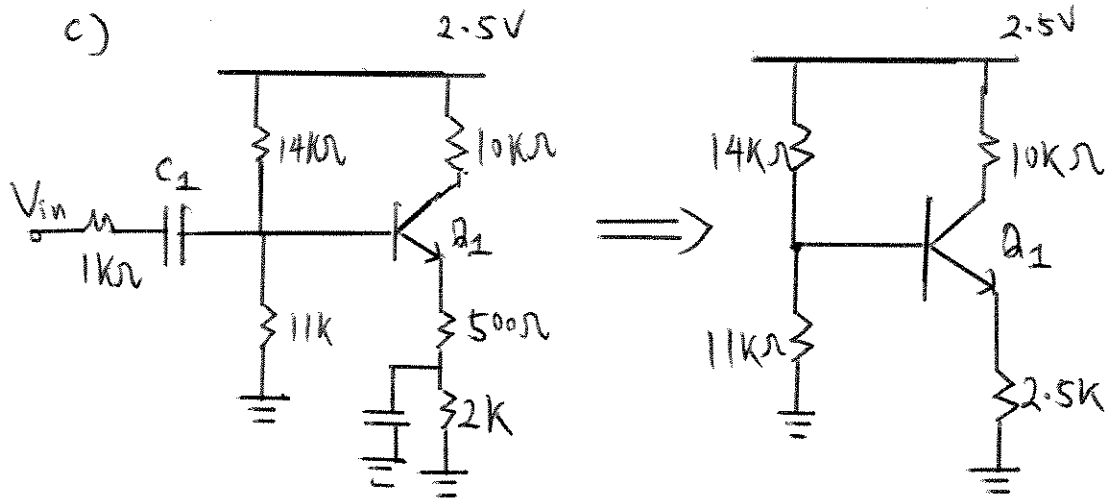

$$I_c = \beta \left( \frac{1.1 - (V_{BE} + \frac{I_c \cdot 2.5}{\alpha})}{14k\Omega // 11k\Omega} \right) \Rightarrow I_c = \frac{100 \cdot (1.1 - V_{BE})}{6.16 + 252 \cdot 53}$$

Guess  $V_{BE} = 0.7V$ ,  $I_c = 0.1546mA$


Verify  $V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.676V$ , not 0.7V, reiterate

$V_{BE} = 0.676V$ ,  $I_c = 0.164mA$

Verify  $V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.677V$ , converged !!

$I_c = 0.164mA$ ,  $V_{BE} = 0.677V$ ,  $g_m = 0.00631 \left(\frac{1}{\Omega}\right)S$ ,  
 $r_{\pi} = 15.85k$

AC Analysis:

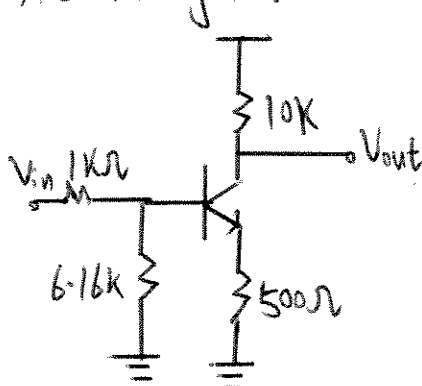


$$\left| \frac{V_{out}}{V_{in}} \right| = \left| \frac{V_{out}}{V_A} \right| \left| \frac{V_A}{V_{in}} \right| = 12.9$$

$$\left| \frac{V_{out}}{V_A} \right| = \frac{10k}{\frac{1}{g_m} + 0.5} = 15.2$$

$$\left| \frac{V_A}{V_{in}} \right| = \frac{6.16k // (15.85k + 10 \cdot 0.5)}{6.16k // (15.85k + 10 \cdot 0.5) + 1k} = 0.85$$

53).

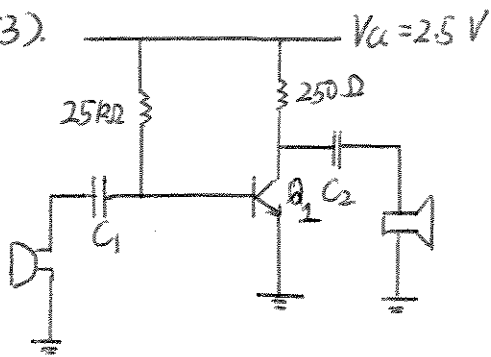

$$R_B = 25 \text{ k}\Omega$$

$$R_C = 250 \Omega$$

$$I_S = 5 \times 10^{-17} \text{ A}$$

$$V_A = \infty$$

DC Analysis: Assume collector bias voltage is still 1.5V. So 1V across  $R_C \Rightarrow I_C = 4 \text{ mA}$ .

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.832$$


$$I_B = \frac{2.5 - V_{BE}}{25 \text{ k}} = 0.06673 \text{ mA}$$

$$\beta = \frac{I_C}{I_B} = \frac{0.832 \text{ mA}}{0.06673 \text{ mA}} = 60$$

$$A_v = \left| \frac{V_{out}}{V_{in}} \right| = g_m (250 \Omega / 8 \Omega) = 1.2, \text{ (Greater than unity)}$$

$$g_m = \frac{4 \text{ mA}}{26 \text{ mV}} = 0.1538 \left(\frac{1}{\Omega}\right) \text{ S}$$

54)

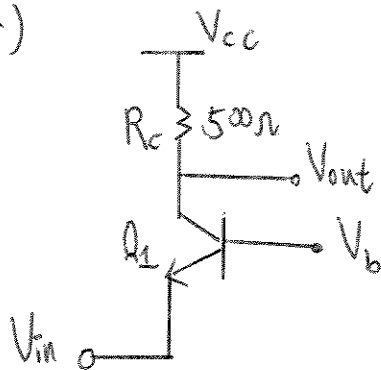

$$I_c = 2 \text{ mA}$$

$$V_A = \infty$$

$$g_m = \frac{I_c}{V_T} = 0.0769 \left(\frac{1}{\text{V}}\right) \text{ S}, \quad \frac{1}{g_m} = 13 \Omega$$

a)


$$|A_v| = g_m R_c = \frac{0.5}{0.013} = 38.5$$

$$R_{in} = \frac{1}{g_m} \parallel r_{\pi} \approx \frac{1}{g_m} = 13 \Omega \quad (\text{Since } \beta \text{ is usually large})$$

$$R_{out} = 500 \Omega$$


b) Since  $|A_v| = g_m R_c$ , and  $g_m$  is fixed by  $I_c$ . The only way to maximize  $|A_v|$  is to maximize  $R_c$ . However a large  $R_c$  will push  $Q_1$  into saturation, losing its gain altogether. Therefore,  $V_B$  has to be as small as possible to provide enough room for  $V_C$  to drop  $\Rightarrow$  large  $R_c \Rightarrow$  large gain.

55)  $V_A = \infty$

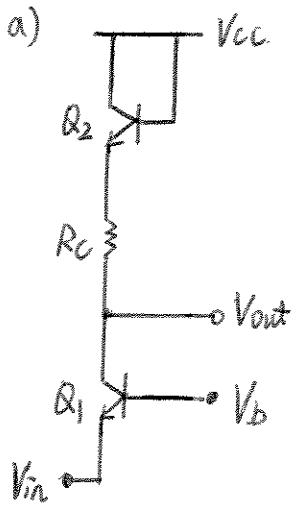


$$|A_v| = \frac{R_c + \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}}}$$
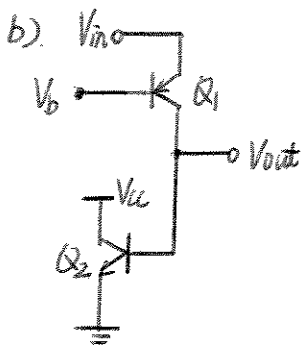
$$= g_{m1} (R_c + \frac{1}{g_{m2}} \parallel r_{\pi 2})$$



$$|A_v| = \frac{r_{\pi 2}}{\frac{1}{g_{m1}}} = g_{m1} r_{\pi 2}$$

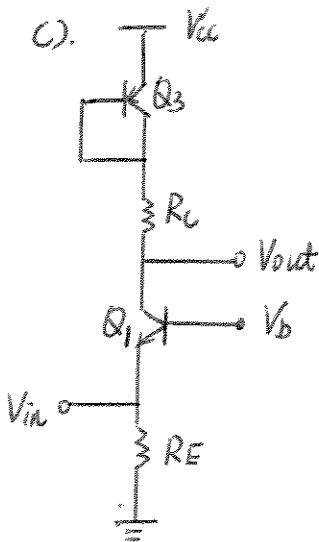


$$|A_v| = \frac{R_c + \frac{1}{g_{m3}} \parallel r_{\pi 3}}{\frac{1}{g_{m1}}}$$

$$= g_{m1} (R_c + \frac{1}{g_{m3}} \parallel r_{\pi 3})$$

55).

d).

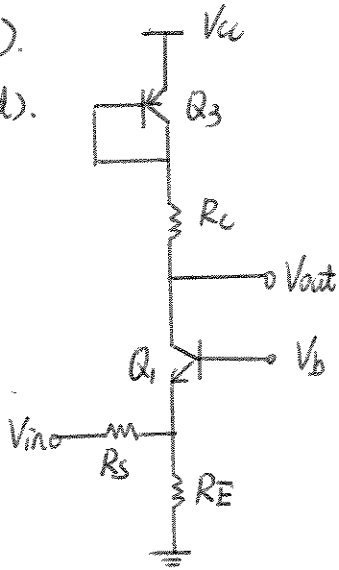


$$|A_v| = \left| \frac{V_{out}}{V_A} \right| \left| \frac{V_A}{V_{in}} \right|$$

$$= \left[ g_{m1} \left( R_C + \frac{1}{g_{m3} \parallel R_{L3}} \right) \right] \left( \frac{R_E \parallel \frac{1}{g_{m1}}}{R_E \parallel \frac{1}{g_{m1}} + R_S} \right)$$




56)  $V_A = \infty$

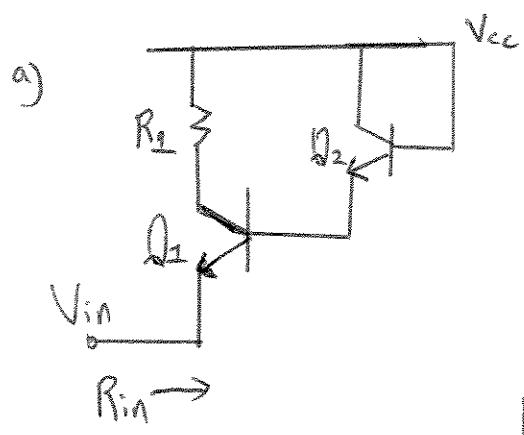

$$R_{in} = \frac{1}{g_{m1}} \parallel r_{\pi 1} + \frac{\frac{1}{g_{m2}} \parallel r_{\pi 2}}{\beta_2 + 1}$$

Since  $\beta$  is usually very large
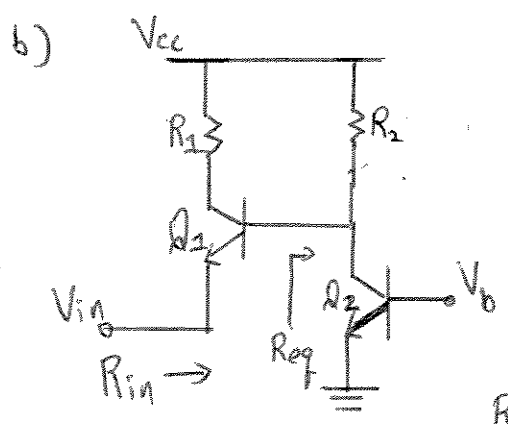
$$R_{in} \approx \frac{1}{g_{m1}} + \frac{1}{g_{m2}(\beta_2 + 1)}$$




$$R_{eq} = R_2 \parallel \infty = R_2$$

$$R_{in} = \frac{1}{g_{m1}} \parallel r_{\pi 1} + \frac{R_2}{\beta_2 + 1}$$

Since  $\beta$  is usually very large

$$R_{in} = \frac{1}{g_{m1}} + \frac{R_2}{\beta_2 + 1}$$

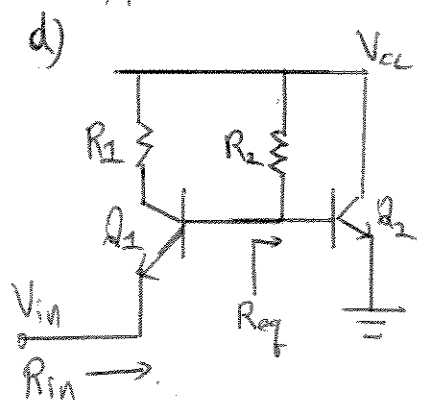\* Note, part c) and d) have swapped places.



$$R_{eq} = R_2 \parallel r_{\pi 2}$$


$$R_{in} = \frac{1}{g_{m1}} \parallel r_{\pi 1} + \frac{R_2 \parallel r_{\pi 2}}{\beta_2 + 1}$$

Since  $\beta$  is usually very large

$$R_{in} \approx \frac{1}{g_{m1}} + \frac{R_2 \parallel r_{\pi 2}}{\beta_2 + 1}$$

56) \* Note, part c) and d) have swapped places

c)

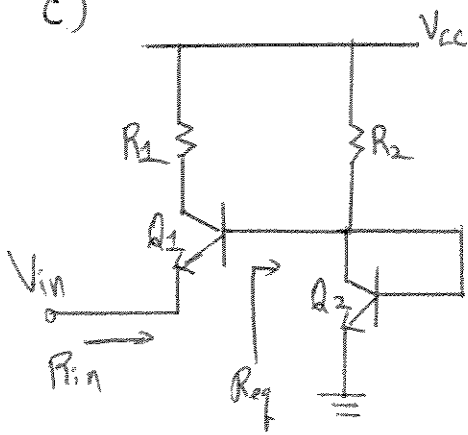


$$R_{eq} = R_2 \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

$$R_{in} = \frac{1}{g_{m1}} \parallel r_{\pi 1} + \frac{R_2 \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\beta_1 + 1}$$

Since  $\beta$  is usually very large

$$R_{in} \approx \frac{1}{g_{m1}} + \frac{R_2 \parallel \frac{1}{g_{m2}}}{\beta + 1}$$

57)

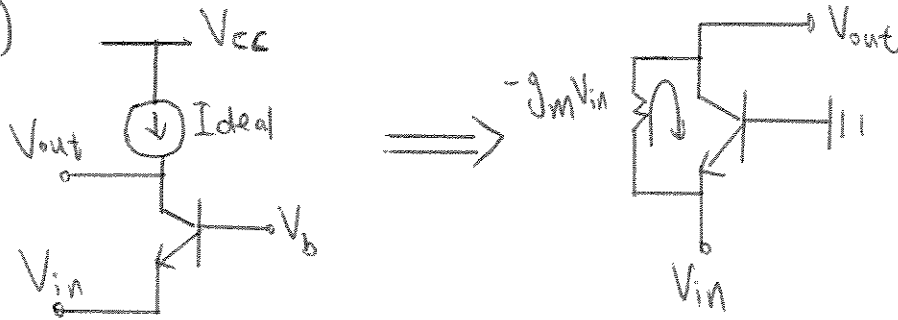

Since an ideal current source is an open circuit, the signal current produced by the transistor has nowhere to go but  $R_o$ .

$$\text{So } V_{out} = -(g_m (0 - V_{in})) R_o + V_{in}$$


$$V_{out} = g_m R_o V_{in} + V_{in}$$

$$V_{out} = V_{in} (g_m R_o + 1)$$

$$\frac{V_{out}}{V_{in}} = 1 + g_m R_o$$

58)

b) AC Analysis

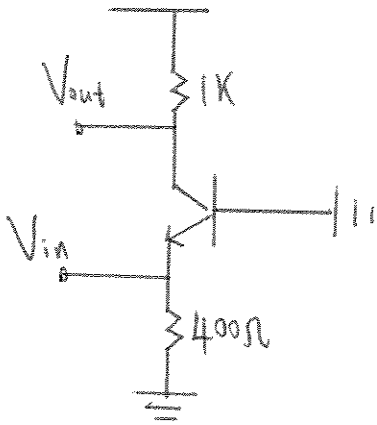

$$A_v = \left| \frac{V_{out}}{V_{in}} \right| = g_m 1K$$


$$g_m = 0.0391 \left( \frac{1}{\Omega} \right) S$$

$$A_v = 39.1$$

$$R_{in} = 400\Omega \parallel \frac{1}{g_m} = 400\Omega \parallel 25.583\Omega = 24.0\Omega$$

$$R_{out} = 1K$$

58)

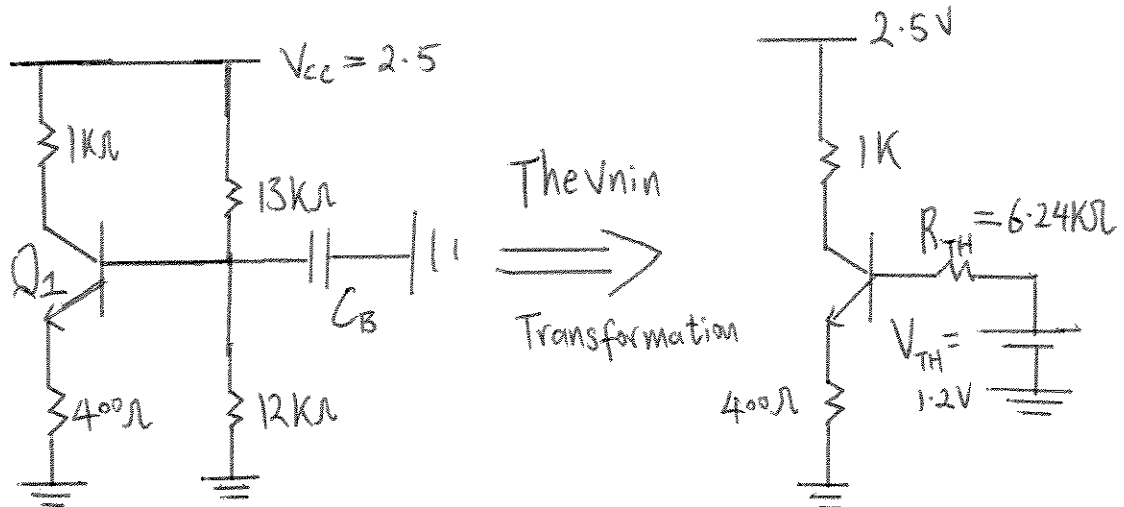

$$\beta = 100, \quad I_s = 8 \times 10^{-16} \text{ A}, \quad V_A = \infty, \quad C_B = \text{Very large}$$

a) DC Analysis:

$$I_c = \beta \left( \frac{1.2 - (V_{BE} + I_E 0.4)}{6.24} \right) \Rightarrow \frac{\beta (1.2 - V_{BE})}{6.24 + \frac{0.4\beta}{\alpha}}$$

$$\text{Guess } V_{BE} = 0.7 \Rightarrow I_c = 1.072 \text{ mA}$$

$$\text{Verify } V_{BE}: \quad V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.726 \text{ V, not } 0.7 \text{ V, reiterate.}$$

$$V_{BE} = 0.726 \text{ V}; \quad I_c = 1.0163 \text{ mA}$$

$$\text{Verify } V_{BE}: \quad V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.725 \text{ V, converged!!}$$

$$V_{BE} = 0.725, \quad V_{CE} = 2.5 - \left[ (0.0163)(1\text{k}) + 0.4 \left( \frac{1.0163}{0.99} \right) \right]$$

$$V_{CE} = 1.07$$

$$I_c = 1.0163 \text{ mA}, \quad I_B = 10.163 \text{ } \mu\text{A}$$

59)

$$C_B = 0$$

a) Since  $C_B$  was not considered during DC analysis, it has no effect on operating point analysis. So it is still the same as 58).


$$V_{BE} = 0.725 \text{ V}$$

$$I_C = 1.0163 \text{ mA}$$

$$I_B = 10.163 \mu\text{A}$$

$$V_{CE} = 1.07 \text{ V}$$

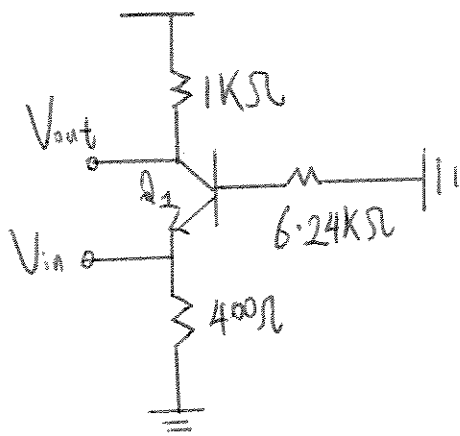b) Since capacitor is frequency dependent, the circuit's AC analysis will be different.




$$|A_v| = \frac{1\text{k}}{\frac{1}{g_m} + \frac{6.24\text{k}\Omega}{\beta + 1}} = 11.4$$

$$R_{in} = 400\Omega \parallel \left( \frac{1}{g_m} + \frac{6.24\text{k}\Omega}{\beta + 1} \right)$$

$$R_{in} = 71.7\Omega$$

$$R_{out} = 1\text{k}\Omega$$

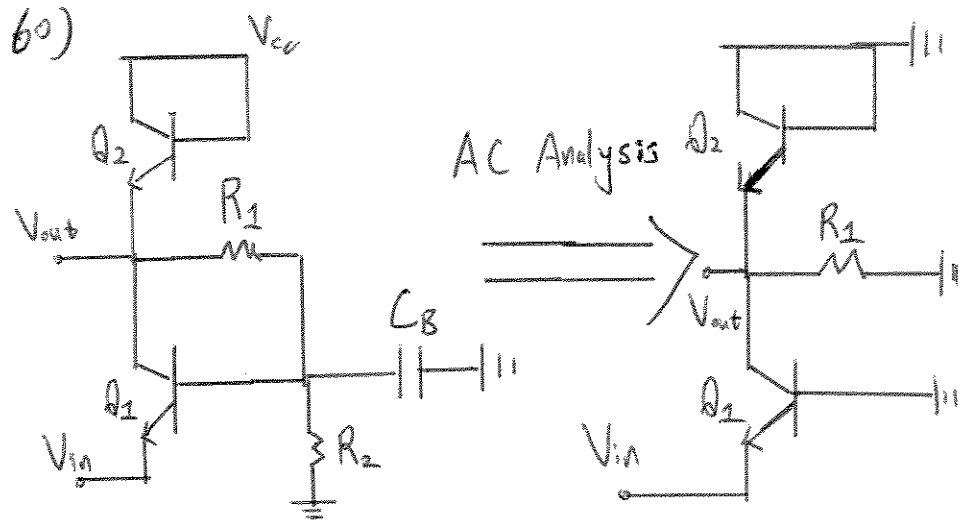Note:  $6.24\text{k}\Omega$  is  $R_{THEV}$   
of  $13\text{k}\Omega$  and  $12\text{k}\Omega$   
combination.




$$R_{out} = \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel R_1 \approx \frac{1}{g_{m2}} \parallel R_1$$

$$A_v = \left| \frac{V_{out}}{V_{in}} \right| = g_{m1} \left( \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel R_1 \right) \approx g_{m1} \left( \frac{1}{g_{m2}} \parallel R_1 \right)$$


$$R_{in} = \frac{1}{g_{m1}} \parallel r_{\pi 1} \approx \frac{1}{g_{m1}}$$

61)

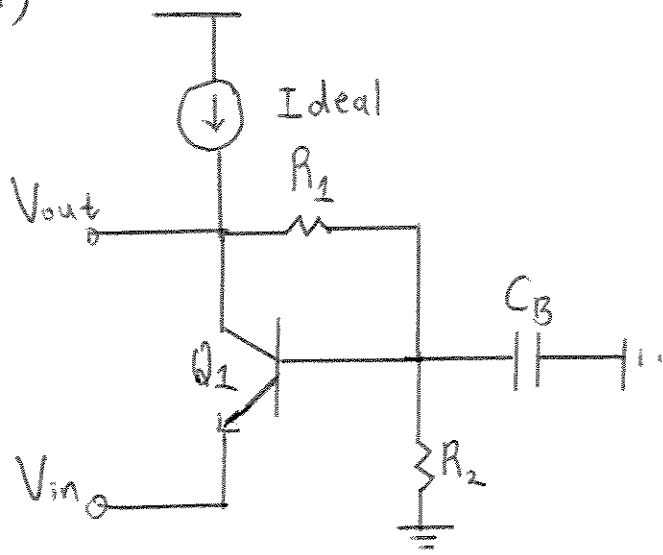

$V_A = \infty$   
 $C_B$  large

AC Analysis

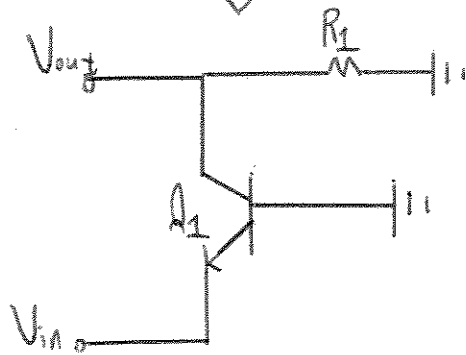

( $R_2$  shorted out)


$$R_{out} = R_1$$

$$R_{in} = \frac{1}{g_{m1}} \parallel r_{\pi 1} \approx \frac{1}{g_{m1}}$$

$$|A_v| = g_{m1} R_1$$



62)

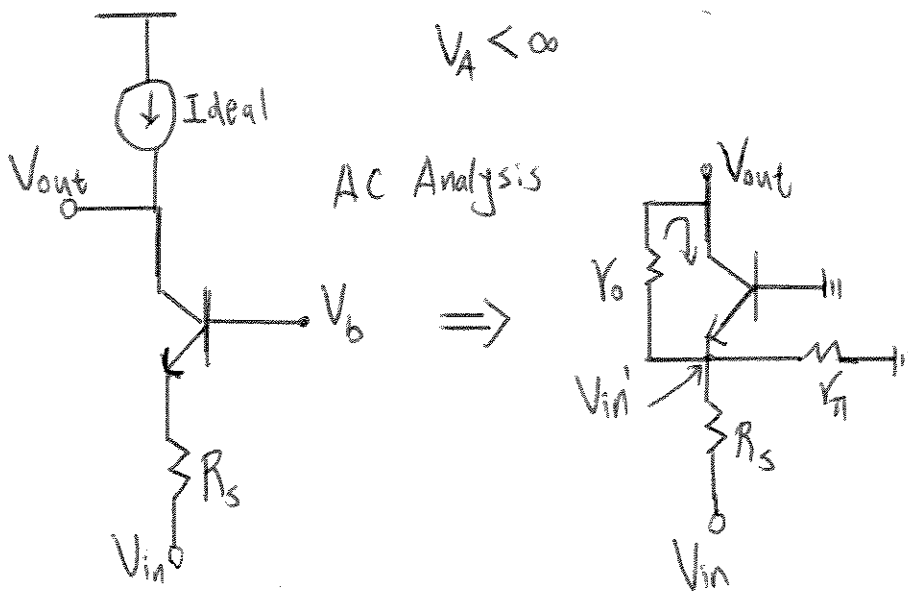


$$A_v = \frac{V_{out}}{V_{in}} = \left( \frac{V_{in'}}{V_{in}} \right) \left( \frac{V_{out}}{V_{in'}} \right), \quad \left( \frac{V_{in'}}{V_{in}} \right) = \frac{r_\pi}{r_\pi + R_s}$$

Since  $V_{out}$  is float, so looking at emitter and  $r_o$ , we will see an infinite impedance.

$$\frac{V_{out}}{V_{in'}} \Rightarrow -g_m (-V_{in'}) r_o + V_{in'} = V_{out} \Rightarrow \frac{V_{out}}{V_{in'}} = (g_m r_o + 1)$$

$$A_v = (g_m r_o + 1) \left( \frac{r_\pi}{r_\pi + R_s} \right)$$

63)

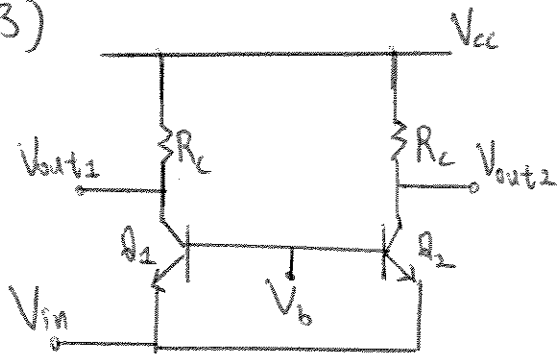

$$V_A = \infty$$

$$I_{S1} = 2I_{S2}$$

$$\left| \frac{V_{out1}}{V_{in}} \right| = g_{m1} R_c, \quad \left| \frac{V_{out2}}{V_{in}} \right| = g_{m2} R_c$$


$$g_{m1} = \frac{V_T}{I_{c1}} = \frac{V_T}{2I_{S2} e^{(V_{BE}/V_T)}}, \quad \text{Since } I_{S1} = 2I_{S2}$$

$$g_{m2} = \frac{V_T}{I_{c2}} = \frac{V_T}{I_{S2} e^{(V_{BE}/V_T)}}$$

$$(V_{BE1} = V_{BE2} = V_{BE})$$

$$\Rightarrow g_{m1} = \frac{g_{m2}}{2} \Rightarrow \left| \frac{V_{out1}}{V_{in}} \right| = \frac{1}{2} \left| \frac{V_{out2}}{V_{in}} \right|$$

64)

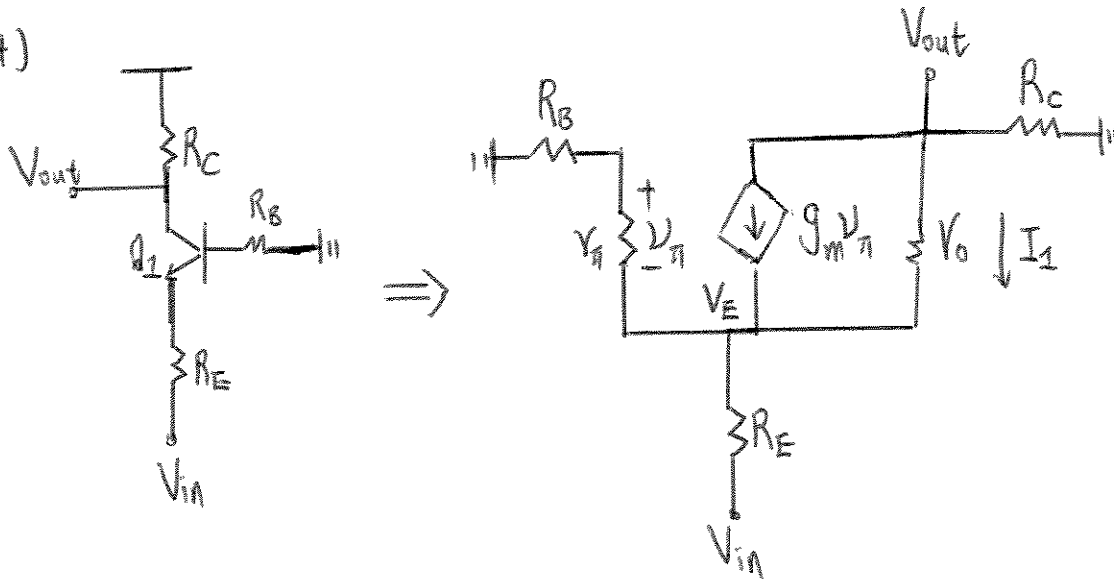

$$V_{out} = -(I_1 + g_m v_\pi) R_C, \quad I_1 = \frac{V_{out} - V_E}{Y_o}$$

$$V_{out} = -\left(\frac{V_{out} - V_E}{Y_o} + g_m v_\pi\right) R_C, \quad V_E = -\frac{g_m v_\pi}{\beta} (r_\pi + R_B)$$

$$V_{out} = -\left(\frac{V_{out} + \frac{g_m v_\pi (r_\pi + R_B)}{\beta}}{Y_o} + g_m v_\pi\right) R_C$$

Rearranging

$$v_\pi = \frac{-(1 + \frac{R_C}{Y_o}) V_{out}}{\frac{g_m (r_\pi + R_B) R_C}{\beta Y_o} + g_m R_C} = A V_{out}$$

Summing the voltage at node E.

$$V_E - \left( \left(1 + \frac{1}{\beta}\right) g_m v_\pi + \frac{V_{out} - V_E}{Y_o} \right) R_E = V_{in} \quad (1)$$

64) Writing  $V_E$  in terms of  $V_{\pi}$ , and  $V_{\pi}$  in terms of  $V_{out}$

1) becomes

$$-\frac{g_m A V_{out}}{\beta} (Y_{\pi} + R_B) \left(1 + \frac{R_E}{Y_0}\right) - \left(1 + \frac{1}{\beta}\right) g_m A V_{out} R_E - \frac{V_{out} R_E}{Y_0} = V_{in}$$


Solving  $V_{out} / V_{in} \Rightarrow$

$$\frac{V_{out}}{V_{in}} = \frac{1}{-\frac{g_m A}{\beta} (Y_{\pi} + R_B) \left(1 + \frac{R_E}{Y_0}\right) - \left(1 + \frac{1}{\beta}\right) g_m A R_E - \frac{R_E}{Y_0}}$$

substituting A into equation

$$\frac{V_{out}}{V_{in}} = \frac{g_m (Y_{\pi} + R_B) R_C + g_m R_C}{g_m \left(1 + \frac{R_E}{Y_0}\right) (Y_{\pi} + R_B) \left(1 + \frac{R_E}{Y_0}\right) + \left(1 + \frac{1}{\beta}\right) g_m \left(1 + \frac{R_C}{Y_0}\right) R_E - \frac{R_E}{Y_0} \left(\frac{g_m (Y_{\pi} + R_B) R_C}{\beta Y_0} + g_m R_C\right)}$$

65)

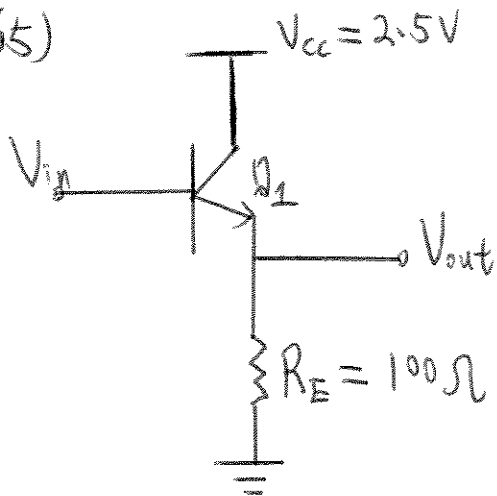

$$R_E = 100\Omega$$

$$V_A = \infty$$

$$|A_v| = 0.8$$


$$|A_v| = \frac{R_E}{R_E + \frac{1}{g_m}} = \frac{R_E I_c}{R_E I_c + V_T} = 0.8$$

$$\Rightarrow R_E I_c = 0.8(R_E I_c + V_T), \quad R_E = 100\Omega$$

$$\Rightarrow 0.1 I_c = 0.08 I_c + 0.0208 \Rightarrow 0.02 I_c = 0.0208$$

$$\Rightarrow I_c = 1.04 \text{ mA}$$

6b)

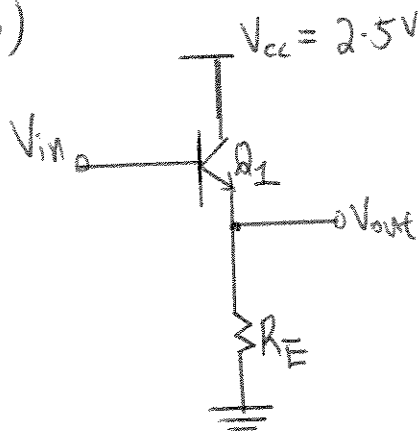

$$|A_v| > 0.9$$

$$R_{in} > 10\text{K}\Omega$$

$$|A_v| = \frac{R_E I_C}{R_E I_C + V_T} > 0.9 \Rightarrow R_E I_C > 0.9 [R_E I_C + V_T]$$

$$\Rightarrow R_E I_C > 9V_T = 234\text{mV}, \text{ Let } R_E I_C = 240\text{mV}$$

$$R_{in} = r_{\pi} + (1 + \beta) R_E > 10\text{K} \Rightarrow 100V_T + (101)R_E I_C > 10\text{K}\Omega I_C$$

substituting  $R_E I_C = 240\text{mV} \Rightarrow I_C < 2.684\text{mA}$


$$\text{Choose } I_C \text{ to be } 2.5\text{mA} \Rightarrow R_E = 96\Omega$$

To Verify:

$$R_{in} = \frac{100(0.026)}{2.5} + (101)0.096 = 10.74\text{K}\Omega$$

$$|A_v| = \frac{(0.096)(2.5)}{(0.096)(2.5) + 0.026} = 0.902$$

67)

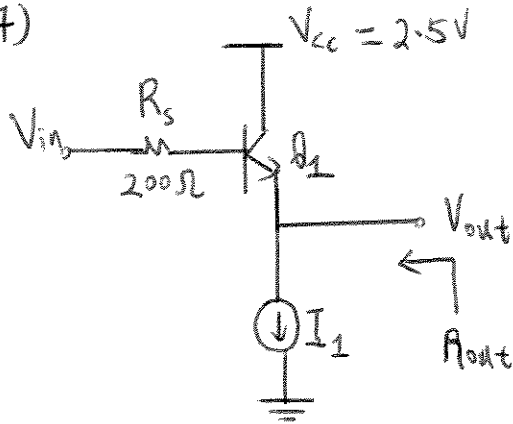

$$\beta = 100$$

$$V_A = \infty$$

$$R_{out} = \frac{1}{g_m} + \frac{R_s}{(\beta + 1)} \leq 5 \Omega \quad (\text{Assuming } Y_{\pi} \gg \frac{1}{g_m})$$


$$R_{out} = 0.026 + \frac{200 \Omega I_c}{101} \leq 5 \Omega I_c$$

$$\Rightarrow I_c \geq 0.0086 \text{ A}$$

$$\text{pick } I_c = 0.009 \text{ A}$$


$$R_{out} = \frac{0.026 \text{ V}}{0.009 \text{ A}} + \frac{200}{101} = 4.87 \Omega$$

68). a)

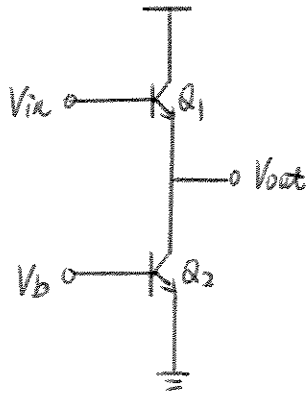

$$V_A = \infty$$

$\Rightarrow$

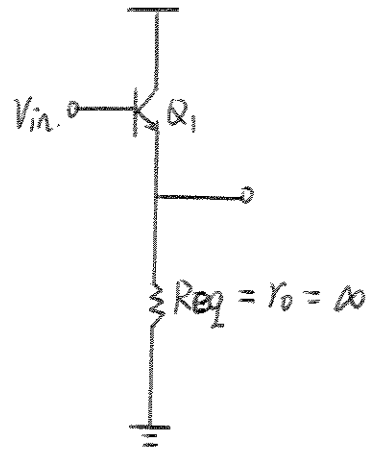


$$|A_v| = \frac{r_o}{r_o + \frac{1}{g_m}} \quad , \quad \text{Since } r_o = \infty$$


$$|A_v| = 1.$$

$$R_{in} = \infty \quad (\text{since } r_o = \infty)$$
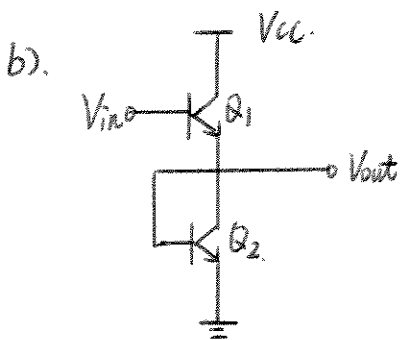
$$R_{out} = \infty \parallel \frac{1}{g_{m1}} \parallel r_{\pi 1} = \frac{1}{g_{m1}} \parallel r_{\pi 1}$$



$\Rightarrow$

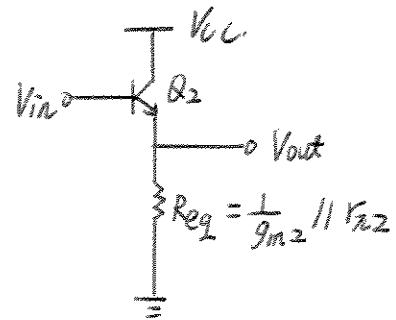

$$|A_v| = \frac{\frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m2}} \parallel r_{\pi 2} + \frac{1}{g_{m1}}}$$


$$R_{in} = r_{\pi 1} + (1 + \beta) \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

$$R_{out} = \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel \frac{1}{g_{m1}} \parallel r_{\pi 1}$$


( If  $I_{S1} = I_{S2}$ ,  $g_{m1} = g_{m2} = g_m$ ,  $r_{\pi 1} = r_{\pi 2} = r_{\pi}$ ,  $R_{out} = \frac{1}{2g_m} \parallel \frac{r_{\pi}}{2}$  )



c).

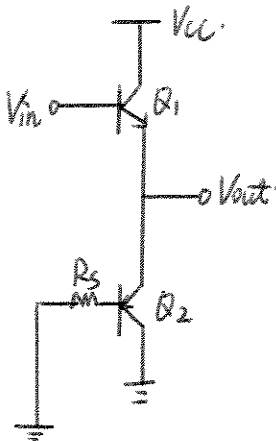

⇒

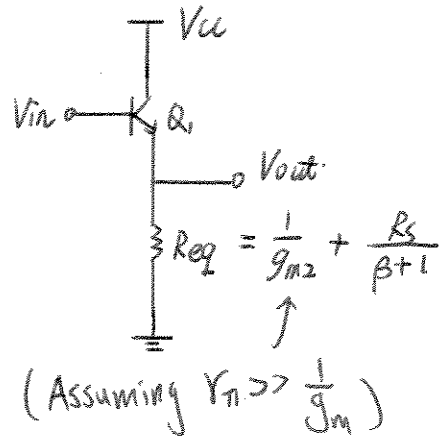


$$|A_v| = \frac{\frac{1}{g_{m2}} + \frac{R_s}{\beta+1}}{\frac{1}{g_{m2}} + \frac{R_s}{\beta+1} + \frac{1}{g_{m1}}}$$

$$R_{in} = r_{\pi} + (1+\beta) \left( \frac{1}{g_{m2}} + \frac{R_s}{\beta+1} \right)$$


$$R_{out} = \left( \frac{1}{g_{m2}} + \frac{R_s}{\beta+1} \right) \parallel \left( \frac{1}{g_{m1}} \parallel r_{\pi 1} \right)$$

$$R_{out} \approx \left( \frac{1}{g_{m2}} + \frac{R_s}{\beta+1} \right) \parallel \frac{1}{g_{m1}}$$

d).

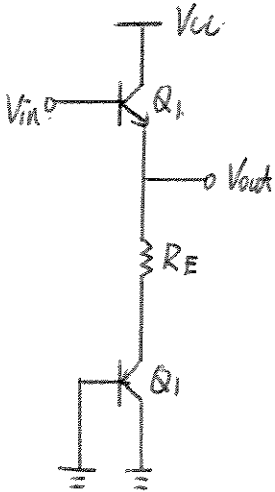

⇒

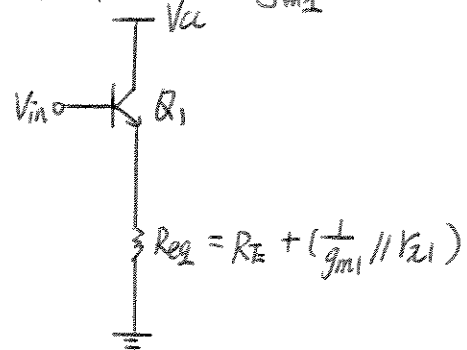


$$|A_v| = \frac{R_E + \left( \frac{1}{g_{m1}} \parallel r_{\pi 1} \right)}{R_E + \left( \frac{1}{g_{m1}} \parallel r_{\pi 1} \right) + \frac{1}{g_{m1}}}$$


$$R_{in} = r_{\pi} + (1+\beta) \left[ R_E + \left( \frac{1}{g_{m1}} \parallel r_{\pi 1} \right) \right]$$

$$R_{out} = \left[ R_E + \left( \frac{1}{g_{m1}} \parallel r_{\pi 1} \right) \right] \parallel \left( \frac{1}{g_{m1}} \parallel r_{\pi 1} \right)$$

68). e).

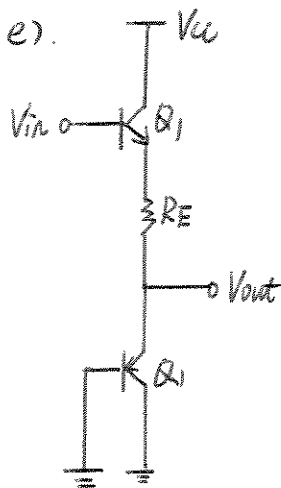

$\Rightarrow$

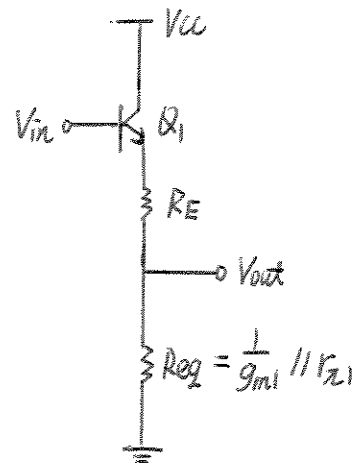


$$|A_v| = \frac{\frac{1}{g_{m1}} \parallel r_{L1}}{\frac{1}{g_{m1}} \parallel r_{L1} + R_E + \frac{1}{g_{m1}}}$$

$$R_{in} = r_L + (1 + \beta) \left[ R_E + \frac{1}{g_{m1}} \parallel r_{L1} \right]$$


$$R_{out} = \left( \frac{1}{g_{m1}} \parallel r_{L1} \right) \parallel \left( R_E + \frac{1}{g_{m1}} \parallel r_{L1} \right).$$

69 a)

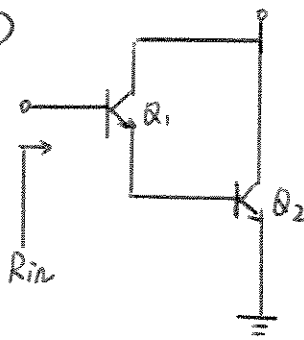

$$R_{in} = r_{\pi 1} + (1 + \beta) r_{\pi 2}$$

b).

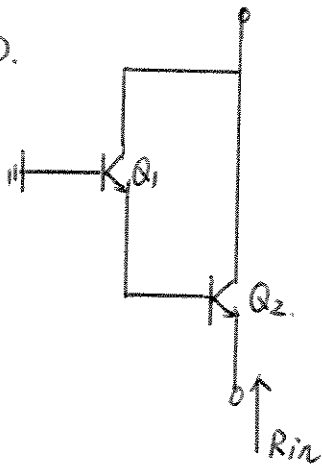


$$R_{in} = \frac{1}{g_{m2}} + \frac{1}{g_{m2}(\beta + 1)} \quad (\text{Assume } r_{\pi} \gg \frac{1}{g_m})$$

$$c) \text{ Current Gain} = \frac{I_{c1} + I_{c2}}{I_{B1}} = \beta + \frac{I_{c2}}{I_{B1}} = \beta + \frac{\beta I_{B2}}{I_{B1}}$$

$$\text{Since } I_{B2} = I_{c1} = \beta I_{B1}$$


$$\text{Current Gain} = \beta + \beta^2 = \beta(\beta + 1), \quad (\text{Assuming } \beta_1 = \beta_2 = \beta)$$

70).

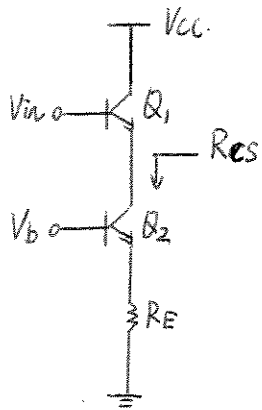


$$u) R_{cs} = Y_{o2} + (1 + g_{m2} Y_{o2})(R_E // Y_{\pi 2})$$

b).

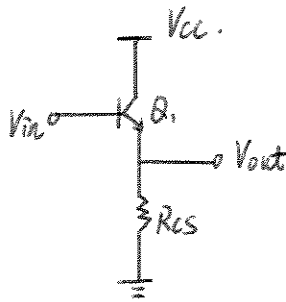

$$A_v = \frac{R_{cs} // Y_{o1}}{R_{cs} // Y_{o1} + \frac{1}{g_{m1}}}$$
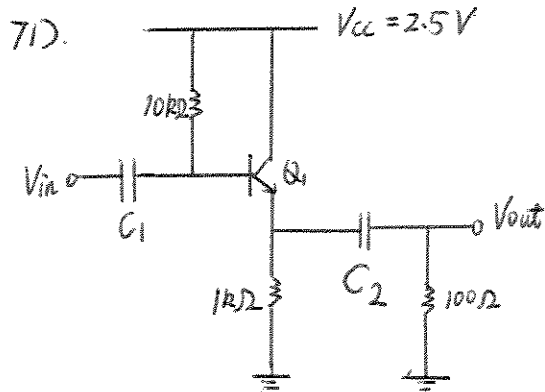
$$A_v = \frac{(Y_{o2} + (1 + g_{m2} Y_{o2})(R_E // Y_{\pi 2})) // Y_{o1}}{(Y_{o2} + (1 + g_{m2} Y_{o2})(R_E // Y_{\pi 2})) // Y_{o1} + \frac{1}{g_{m1}}}$$




$$I_s = 7 \times 10^{-16} \text{ A}$$

$$\beta = 100$$

$$V_A = 5 \text{ V}$$

DC Analysis: (Ignore  $V_o$ 's effect).

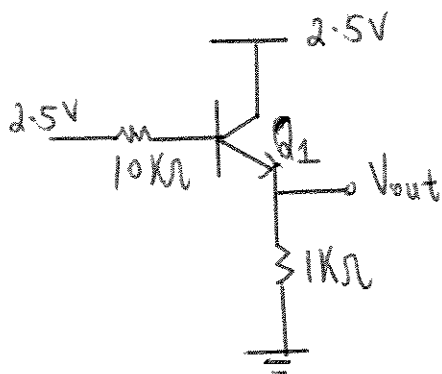

$$I_c = \beta \left( \frac{2.5 - (V_{BE} + \frac{I_c}{\alpha} 1 \text{ k}\Omega)}{10 \text{ k}\Omega} \right)$$

Rearrange

$$I_c = \frac{2.5 - V_{BE}}{\frac{10 \text{ k}\Omega}{\beta} + \frac{1 \text{ k}\Omega}{\alpha}}$$

Guess:  $V_{BE} = 0.7 \text{ V}$ ,  $I_c = 1.621 \text{ mA}$

check for  $V_{BE}$ :  $V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.740 \text{ V}$ , not 0.7, reiterate


$V_{BE} = 0.740 \text{ V}$ ,  $I_c = 1.59 \text{ mA}$

check for  $V_{BE}$ :  $V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.740 \text{ V}$ , converged.

So  $I_c = 1.59 \text{ mA}$ ,  $g_m = 0.0612 \left(\frac{1}{\Omega}\right) \text{ S}$ ,  $\frac{1}{g_m} = 16.34 \Omega$ ,  
 $V_o = 3.14 \text{ k}\Omega$


71)

AC Analysis: (Include  $V_o$ )

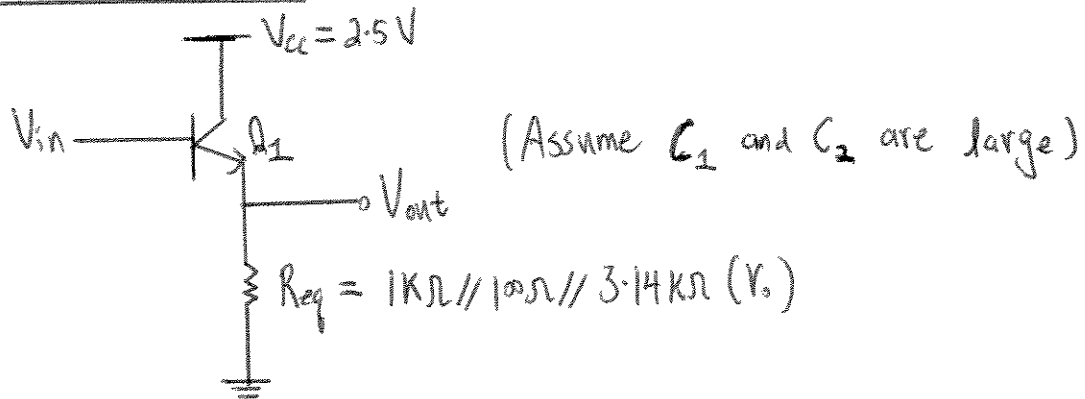

$$A_v = \frac{(1\text{k}\Omega // 100\Omega // 3.14\text{k}\Omega)}{16.34\Omega + (1\text{k}\Omega // 100\Omega // 3.14\text{k}\Omega)} = 0.84$$

72).

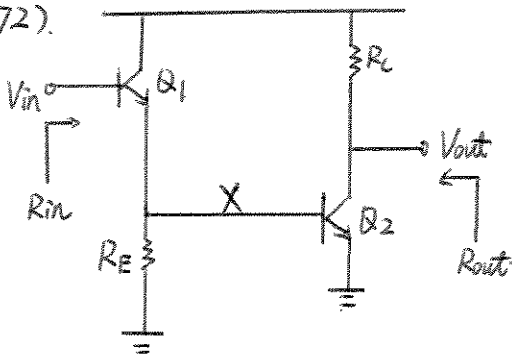

$$V_A < \infty$$


$$a) R_{in} = Y_{\pi 1} + (1 + \beta)(R_E \parallel Y_{\pi 2} \parallel Y_{o 2})$$

$$R_{out} = R_C \parallel Y_{o 2}$$

$$b) \left| \frac{V_{out}}{V_{in}} \right| = \left| \frac{V_x}{V_{in}} \right| \left| \frac{V_{out}}{V_x} \right|$$

$$\left| \frac{V_x}{V_{in}} \right| = \frac{(R_E \parallel Y_{\pi 2} \parallel Y_{o 1})}{\frac{1}{g_{m 1}} + R_E \parallel Y_{\pi 2} \parallel Y_{o 1}}, \quad \left| \frac{V_{out}}{V_x} \right| = g_{m 2} R_C$$

$$\left| \frac{V_{out}}{V_{in}} \right| = (g_{m 2} R_C) \left[ \frac{R_E \parallel Y_{\pi 2} \parallel Y_{o 1}}{\frac{1}{g_{m 1}} + R_E \parallel Y_{\pi 2} \parallel Y_{o 1}} \right]$$

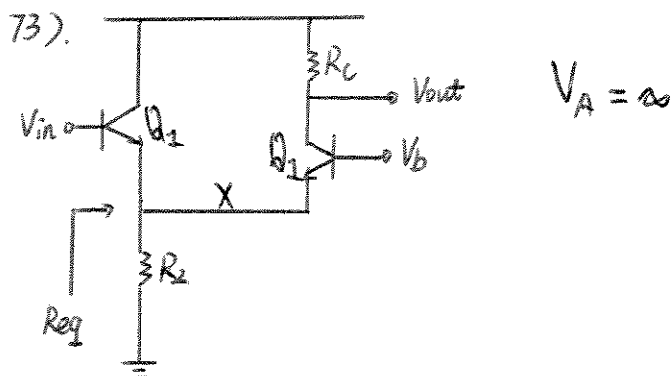

$$a) R_{eq} = R_E \parallel Y_{\pi 1} \parallel \frac{1}{g_{m1}}$$

$$R_{in} = Y_{\pi 1} + (1 + \beta) \left[ R_E \parallel Y_{\pi 1} \parallel \frac{1}{g_{m1}} \right]$$


$$R_{out} = R_C$$

$$b) \left| \frac{V_{out}}{V_{in}} \right| = \left| \frac{V_x}{V_{in}} \right| \left| \frac{V_{out}}{V_x} \right|$$

$$\left| \frac{V_x}{V_{in}} \right| = \frac{R_E \parallel \frac{1}{g_{m2}} \parallel Y_{\pi 1}}{\frac{1}{g_{m1}} + R_E \parallel \frac{1}{g_{m1}} \parallel Y_{\pi 1}}, \quad \left| \frac{V_{out}}{V_x} \right| = g_{m2} R_C$$

$$\left| \frac{V_{out}}{V_{in}} \right| = (g_{m2} R_C) \left( \frac{R_E \parallel \frac{1}{g_{m2}} \parallel Y_{\pi 1}}{R_E \parallel \frac{1}{g_{m1}} \parallel Y_{\pi 1} + \frac{1}{g_{m1}}} \right)$$



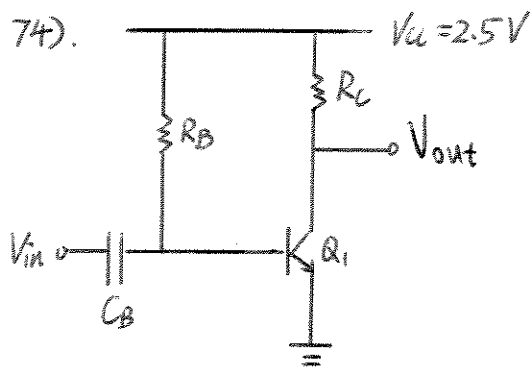

$$A_v = 10$$

$$R_{in} > 5K\Omega$$

$$R_{out} = 1K, R_C = 1K\Omega$$

$$A_v = \frac{R_C}{\frac{1}{g_m}} = 10 = \frac{I_C R_C}{V_T} \Rightarrow I_C = 0.26mA$$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.697V.$$

$$I_C = 100 \left( \frac{2.5 - 0.697}{R_B} \right) \Rightarrow R_B = 693K\Omega, r_{\pi} = \frac{\beta V_T}{I_C} = 10K\Omega$$

$$R_{in} = 693K // 10K = 9.86K\Omega$$


$$\frac{1}{2\pi(200)C_B} = \frac{1}{10} \frac{1}{g_m} = 10\Omega \Rightarrow C_B = 80\mu f$$

(To avoid gain degradation).

$$R_C = 1K\Omega \quad \Rightarrow \quad A_v = 10$$

$$R_B = 693K \quad \Rightarrow \quad R_{out} = 1K\Omega$$
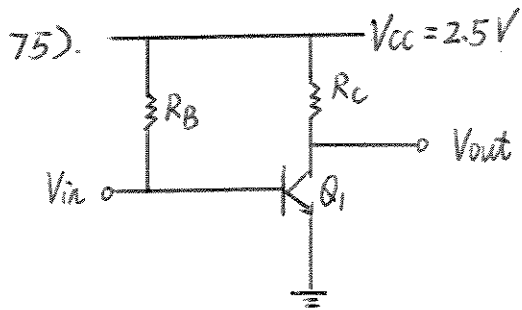
$$C_B = 80\mu f \quad \Rightarrow \quad R_{in} = 9.86K\Omega$$



$$A_v = \text{Maximum}$$

$$R_{out} \leq 500\Omega$$

$$V_{BC} \leq 400\text{ mV}$$

$$A_v = g_m R_c = \frac{I_c R_c}{V_T}, \text{ gain is maximized by maximize } I_c R_c$$

$$R_{out} = R_c \leq 500\Omega, \text{ choose } R_c = 450\Omega, R_{out} = 450\Omega$$

$$V_{BC} = V_{BE} - (2.5 - I_c R_c) \leq 400\text{ mV}$$

Guess  $V_{BE} = 0.7$ , and let  $V_{BC} = 400\text{ mV}$  to maximize  $I_c R_c$ .

$$0.7 - (2.5 - I_c \cdot 0.450) = 0.4$$

$$I_c = 4.89\text{ mA}, V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.773$$

Not 0.7, Iterate.

$$0.773 - 2.5 + I_c \cdot 0.450 = 0.4$$

$$I_c = 4.73\text{ mA}, V_{BE} = 0.772 \text{ converged!!}$$

$$A_v = \left(\frac{I_c}{V_T}\right) R_c = \left(\frac{4.73}{26}\right) (450) = 81.9$$


$$R_B = 100 \left( \frac{2.5 - 0.772}{4.73} \right) = 36.5\text{ K}$$

$$R_B = 36.5\text{ K} \Rightarrow A_v = 81.9$$

$$R_c = 450\Omega \Rightarrow V_{BC} = 0.4\text{ V}$$

$$R_{out} = 450\Omega$$

76)

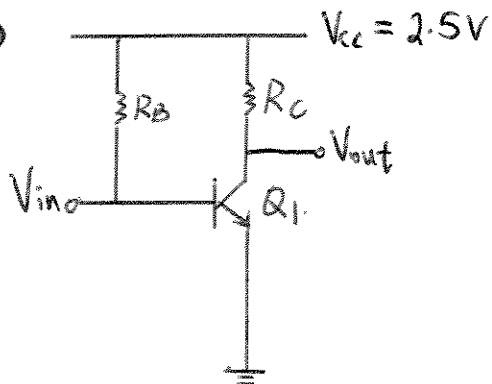 $R_{in}$  : Maximum

$$A_v \geq 20$$

$$R_{out} = R_c = 1K$$

$$A_v = g_m R_c = \frac{I_c R_c}{V_T} \geq 20 \Rightarrow I_c \geq 0.52 \text{ mA}$$

$$R_{in} = R_B // r_{\pi} = \frac{\beta R_B V_T}{R_B I_c + V_T \beta} \quad 1), \quad I_c = \beta \left( \frac{2.5 - V_{BE}}{R_B} \right) \quad 2)$$

As we can see from 1), higher  $I_c$  means lower  $R_{in}$ .


So set  $I_c$  as low as possible,  $I_c = 0.52 \text{ mA}$ .

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.715 \text{ V}$$

$$\text{From 2), } R_B = \frac{100(2.5 - 0.715)}{0.52} = 343.3K\Omega, \quad r_{\pi} = 5K\Omega$$

$$R_{in} = 4.93K\Omega$$
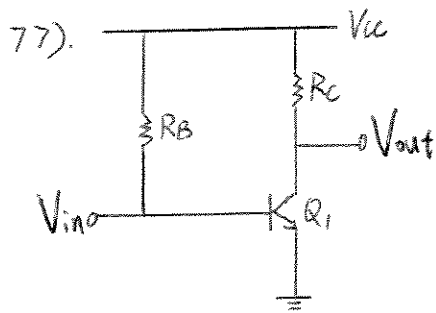
$$\begin{aligned} R_c = 1K\Omega & \Rightarrow A_v = 20 \\ R_B = 343.3K\Omega & R_{in} = 4.93K\Omega \\ & R_{out} = 1K\Omega \end{aligned}$$



Minimum Supply

$$A_v = 15$$

$$R_{out} = 2\text{K}\Omega, R_c = 2\text{K}\Omega$$

$$V_{BC} \leq 0.4\text{V}$$

$$A_v = g_m R_c = \frac{I_c R_c}{V_T} = 15 \Rightarrow I_c = 0.195\text{mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.689$$

$$V_{BC} = V_{BE} - (V_{cc} - I_c R_c) \leq 0.4\text{V}, I_c R_c = 0.39\text{V}$$

$$V_{cc} \geq 0.689 + 0.39 - 0.4 = 0.679\text{V}$$

Since the problem is concerned with minimum power supply, let  $V_{cc} = 0.69\text{V}$ , since  $V_{BE} = 0.679\text{V}$  ( $V_{cc} > V_{BE}$ )

$$I_c = \beta \left( \frac{V_{cc} - 0.689}{R_B} \right) \Rightarrow R_B = 100 \left( \frac{0.69 - 0.689}{0.195} \right) = 512.8\Omega$$


$$R_c = 2\text{K}\Omega$$

$$R_B = 512.8\Omega$$

$$V_{cc} = 0.69\text{V}$$

$$\Rightarrow A_v = 15$$

$$R_{out} = 2\text{K}\Omega$$

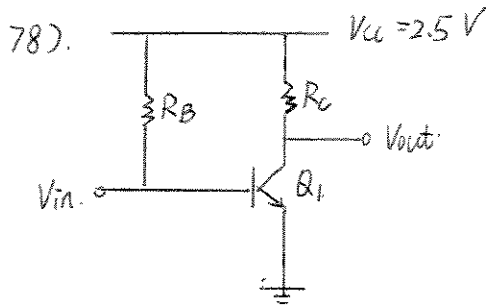


$$A_o = g_m R_c$$

$$A_o = \frac{I_c R_c}{V_T}, \quad \text{Power Dissipation} = I_c V_{cc}$$

$$R_{out} = R_c = \frac{A_o V_T}{I_c}$$

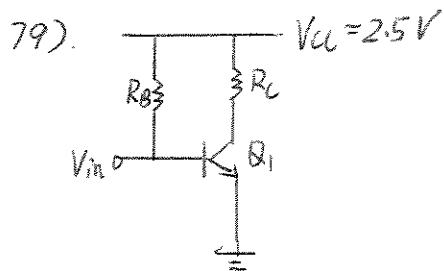For large  $R_{out}$ ,  $I_c$  has to be small, which decreases power.  
 So small power dissipation and small output impedance cannot be satisfied simultaneously.



Power Budget = 1mW  
 $A_v = 20$

$$A_v = g_m R_c = \frac{I_c R_c}{V_T} = 20, \quad V_{cc} I_c = 1\text{mW}$$

$$I_c = 0.4\text{mA}, \quad R_c = 1.3\text{K}$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.708\text{V}, \quad I_c = \beta \left( \frac{V_{cc} - V_{BE}}{R_B} \right) = 100 \left( \frac{2.5 - 0.708}{R_B} \right)$$

$$\Rightarrow R_B = 448\text{K}, \quad R_{in} = 448 \parallel \left( 100 \left( \frac{26}{0.4} \right) \right) = 6.4\text{K}$$

$$R_B = 448\text{K}$$


$$R_c = 1.3\text{K}$$

$$\Rightarrow A_v = 20$$

$$\text{Power Budget} = 1\text{mW}$$

$$R_{out} = 1.3\text{K}\Omega$$

$$R_{in} = 6.4\text{K}$$

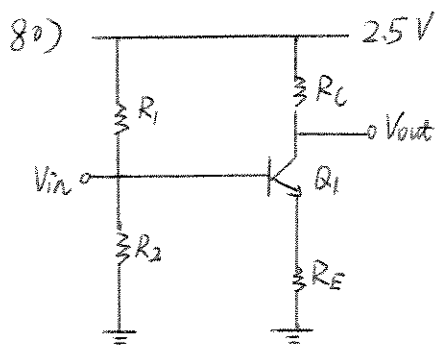

$$A_V = 5$$

$$R_{out} = R_C = 500\Omega$$

$$R_E I_C \approx 300\text{mV}$$

$$A_V = \frac{R_C I_C}{R_E I_C + V_T} = \frac{R_C I_C}{300 + 26} \Rightarrow R_C I_C = 1.63\text{V} \Rightarrow I_C = 3.26\text{mA}$$

$$R_E I_C \approx 300\text{mV} \Rightarrow R_E = 92\Omega$$

$$R_1 = \frac{2.5 - (V_{BE} + 0.3)}{10 I_B}, \quad V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.7624$$

$$10 I_B = 0.326\text{mA}$$

$$R_1 = \frac{2.5 - (0.7624 + 0.3)}{0.326} = 4.41\text{k}$$

$$R_2 = \frac{(0.7624 + 0.3)}{(9 \times 0.0326)} = 3.62\text{k}$$

$$V_{CE} = 2.5 - 1.63 - 0.3 = 0.57, \quad V_{BE} = 0.7624.$$

$Q_1$  is in soft saturation region, so active region characteristics

still apply.

$$R_C = 500\Omega$$


$$R_1 = 4.41\text{k}\Omega$$

$$R_2 = 3.62\text{k}\Omega$$

$$R_E = 92\Omega$$

$$\Rightarrow A_V = 5$$

$$R_{out} = 500\Omega$$

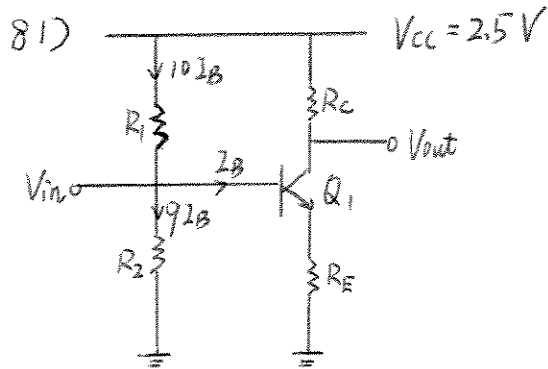

$$A_v = \text{Maximum}$$

$$R_{out} = R_c \leq 1K\Omega$$

$$V_{BC} = 0.4V$$

$$R_E I_c \approx 200mV$$

$$V_{BC} = (V_{BE} + 0.2) - (2.5 - I_c R_c) = 0.4 \quad 1)$$

$$A_v = \frac{R_c I_c}{R_E I_c + V_T} = \frac{R_c I_c}{0.226}$$

Rearrange, 1) becomes  $I_c R_c = 0.4 + 2.5 - (V_{BE} + 0.2)$

$$\text{Guess } V_{BE} = 0.7 \Rightarrow I_c R_c = 2V$$

$$\text{Let } R_c = 1K \Rightarrow I_c = 2mA$$

check for  $V_{BE}$ :  $V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.750$ , not 0.7, reiterate

$$V_{BE} = 0.75 \Rightarrow I_c R_c = 1.95V$$

$$R_c = 1K \Rightarrow I_c = 1.95mA$$

check for  $V_{BE}$ :  $V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.750$ , converged!!

$$I_c = 1.95mA, R_E I_c = 200mV \Rightarrow R_E = 103\Omega$$

$$I_B = 0.0195mA$$

$$R_1 = \frac{2.5 - (0.750 + 0.2)}{(10)(0.0195)} = 7.95K$$

$$R_2 = \frac{(0.750 + 0.2)}{(9)(0.0195)} = 5.41K$$



81)

$$A_v = \frac{R_c I_c}{R_E I_c + V_T} = \frac{1.95}{0.226} = 8.63$$

This is the maximum gain we would get  
when  $R_{out}$  is  $1k\Omega$  and  $V_{bc}$  is at  $0.4V$ .

Since anything larger will violate either requirement.


$$R_c = 1k\Omega$$

$$R_E = 103\Omega$$

$$R_1 = 7.95k\Omega$$

$$R_2 = 5.41k\Omega$$
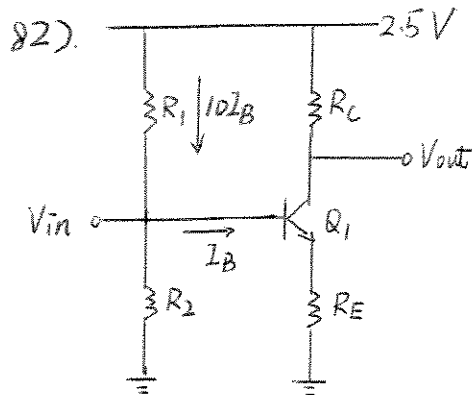
$$\Rightarrow \begin{matrix} A_v = 8.63 \\ R_{out} = 1k\Omega \end{matrix}$$



Power budget = 5 mW

$$A_v = 5$$

$$R_E I_C \approx 200 \text{ mV}$$

$$V_{CC} \left( I_C + \frac{I_C}{10} \right) = 5 \text{ mW} \Rightarrow I_C = 1.82 \text{ mA}, I_B = 0.0182 \text{ mA}$$

$$V_{BE} = V_T \ln \left( \frac{I_C}{I_S} \right) = 0.747$$

$$A_v = \frac{R_C I_C}{R_E I_C + V_T} = \frac{R_C I_C}{0.226} = 5 \Rightarrow R_C I_C = 1.13 \text{ V} \Rightarrow R_C = 621 \Omega$$

$$R_1 = \frac{2.5 - (0.747 + 0.2)}{(10)(0.0182)} = 8.53 \text{ K}\Omega$$

$$R_2 = \frac{(0.747 + 0.2)}{(9)(0.0182)} = 5.78 \text{ K}\Omega$$

$$R_E I_C \approx 200 \text{ mV} \Rightarrow R_E = 110 \Omega$$

$$R_C = 621 \Omega$$


$$R_E = 110 \Omega$$

$$R_1 = 8.53 \text{ K}\Omega$$

$$R_2 = 5.78 \text{ K}\Omega$$

$$\Rightarrow A_v = 5$$

$$\text{Power Budget} = 5 \text{ mW}$$

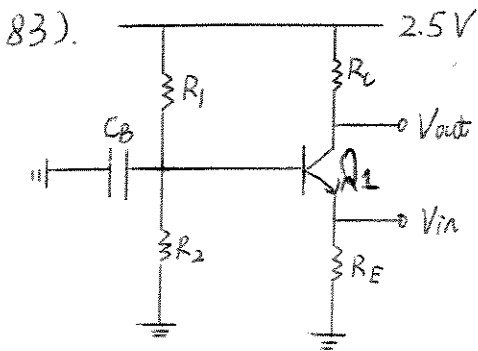

$$A_V = 20$$

$$R_{in} = 50\Omega$$

$$R_E I_C \approx 10 V_T = 260 \text{ mV}$$

$$R_{in} = \frac{1}{g_m} = 50\Omega, \text{ since } R_E \text{ doesn't affect input impedance.}$$

$$\frac{V_T}{I_C} = 50\Omega \Rightarrow I_C = \frac{V_T}{50\Omega} = 0.52 \text{ mA}, I_B = 0.0052 \text{ mA}$$

$$A_V = \frac{R_C}{1/g_m} = \frac{I_C R_C}{V_T} = 20 \Rightarrow R_C = 1 \text{ k}\Omega$$

$$R_1 = \frac{2.5 - (0.715 + 0.260)}{(10)(0.0052)} = 29.3 \text{ k}\Omega$$

$$R_2 = \frac{(0.715 + 0.260)}{(9)(0.0052)} = 20.83 \text{ k}\Omega$$


$$R_E I_C \approx 260 \text{ mV} \Rightarrow R_E \approx 500\Omega$$

$$\frac{1}{C_B (2\pi)(200)} = \frac{1}{10 g_m} = 5\Omega \Rightarrow C_B = 159.1 \mu\text{f}$$

$$R_C = 1 \text{ k}\Omega, R_E = 500\Omega, R_1 = 29.3 \text{ k}\Omega, R_2 = 20.83 \text{ k}\Omega, C_B = 159.1 \mu\text{f}$$

$$\Rightarrow A_V = 20, R_{in} = 50\Omega$$

84)

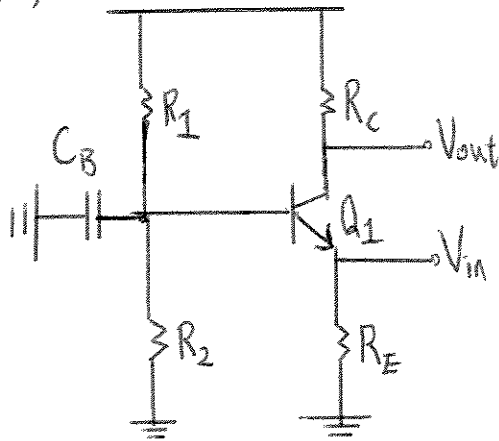

$$A_v = 8$$

$$R_{out} = 500\Omega$$

$$R_{out} = R_c = 500\Omega$$

$$A_v = \frac{I_c R_c}{V_T} = 8 \Rightarrow I_c = 0.416 \text{ mA}, I_B = 0.00416 \text{ mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.709$$

$$R_E \approx \frac{260 \text{ mV}}{I_c} = 625\Omega, R_1 = \frac{2.5 - (0.709 + 0.260)}{(10)(0.00416)} = 36.8 \text{ k}\Omega$$

$$R_2 = \frac{(0.709 + 0.260)}{(9)(0.00416)} = 25.9 \text{ k}\Omega$$

$$\frac{1}{g_m} = \frac{V_T}{I_c} = 62.5\Omega, \frac{1}{C_B 200(2\pi)} = \frac{62.5}{10} \Rightarrow C_B = 127.3 \text{ }\mu\text{f}$$

$$C_B = 127.3 \text{ }\mu\text{f}$$

$$R_1 = 36.8 \text{ k}\Omega$$

$$R_2 = 25.9 \text{ k}\Omega$$


$$R_c = 500\Omega$$

$$R_E = 625\Omega$$

$$\Rightarrow A_v = 8$$

$$R_{out} = 500\Omega$$

85)

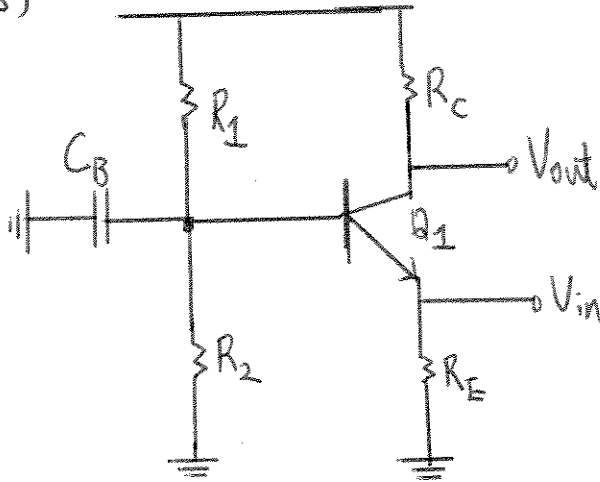

$$A_v = 20$$

$$R_c = 200\Omega$$

$$(R_c = R_{out})$$


$$A_v = \frac{I_c R_c}{V_T} = 20 \Rightarrow I_c = 2.6 \text{ mA}$$

$$I_B = 0.026 \text{ mA}, \quad 10I_B = 0.26 \text{ mA}$$

$$\text{Power} = V_{cc} (I_c + 10I_B) = 2.5 (0.26 \text{ mA} + 2.6 \text{ mA}) = 7.15 \text{ mW}$$

This is the minimum power dissipation, since anything lower will lower the voltage gain.

86)

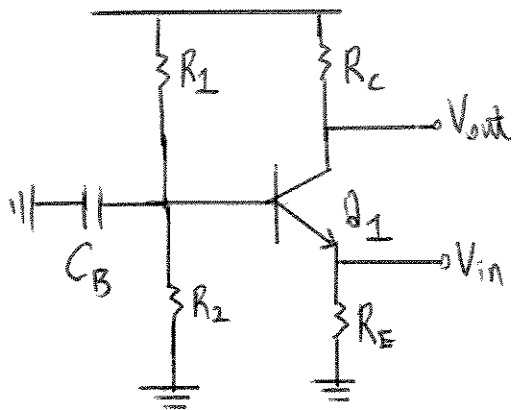

$$\text{Power} = 5 \text{ mW}$$

$$A_v = 10$$

$$V_{cc} I_c + V_{cc} \frac{I_c}{10} = 5 \text{ mW}, \quad V_{cc} I_c \cdot 1.1 = 5 \text{ mW}, \quad I_c = 1.82 \text{ mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.747$$

$$A_v = g_m R_c = \frac{I_c R_c}{V_T} = 10 \Rightarrow R_c = 0.143 \text{ k}\Omega$$

$$I_c R_E \approx 260 \text{ mV}, \quad R_E \approx 142.9 \Omega$$


$$R_1 = \frac{2.5 - (0.747 + 0.260)}{(10)(0.0182)} = 8.2 \text{ k}\Omega, \quad R_2 = \frac{(0.747 + 0.260)}{(9)(0.0182)} = 6.15 \text{ k}\Omega$$

$$\frac{1}{g_m} = \frac{V_T}{I_c} = 14.3 \Omega, \quad \frac{1}{C_B 2\pi(200)} = \frac{14.3}{10} \Rightarrow C_B = 556.5 \text{ nF}$$

$$R_c = 143 \Omega, \quad R_E = 143 \Omega, \quad R_1 = 8.2 \text{ k}\Omega, \quad R_2 = 6.15 \text{ k}\Omega, \quad C_B = 556.5 \text{ nF}$$

$$\Rightarrow A_v = 10, \quad \text{Power} = 5 \text{ mW}$$

87)

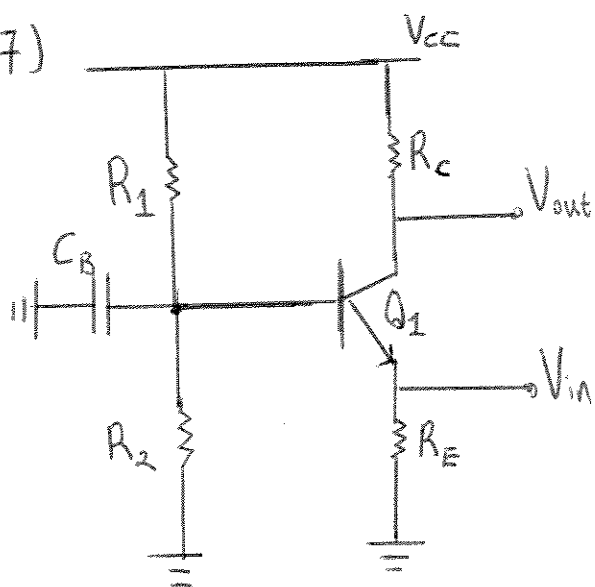

$$R_{in} = 50 \Omega$$

$$A_v = 20$$

Assume  $R_E$  doesn't affect  $R_{in}$  significantly,

$$R_{in} \approx \frac{1}{g_m} = 50 \Omega$$

$$A_v = \frac{R_c}{1/g_m} = 20 \Rightarrow R_c = 1 \text{ k}\Omega, \quad \frac{1}{g_m} = \frac{V_T}{I_c} \Rightarrow I_c = \frac{26 \text{ mV}}{50 \Omega} = 0.52 \text{ mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.715 \text{ V}, \quad R_E I_c = 260 \text{ mV} \Rightarrow R_E = 500 \Omega$$

$$V_{cc} = I_c R_c + V_{CE} + I_c R_E = 0.52 + V_{CE} + 0.260$$

$$V_{BC} \text{ is forward biased to } 0.4 \text{ V}, \quad V_{CE} = V_{BE} - 0.4 = 0.315 \text{ V}$$

$$V_{cc} = 0.52 + 0.315 + 0.260 = 1.1 \text{ V. (Minimum supply voltage)}$$


$$R_1 = \frac{1.1 - (0.715 + 0.260)}{0.052} = 2.4 \text{ k}\Omega, \quad R_2 = \frac{(0.715 + 0.260)}{(1)(0.0052)} = 20.83 \text{ k}\Omega$$

$$\frac{1}{C_B 2\pi 200} = \frac{1}{10} \frac{1}{g_m} = 5 \Rightarrow C_B = 159.2 \text{ }\mu\text{f}$$

$$V_{cc} = 1.1 \text{ V}, \quad R_1 = 2.4 \text{ k}\Omega, \quad R_2 = 20.83 \text{ k}\Omega, \quad R_c = 1 \text{ k}\Omega, \quad R_E = 500 \Omega, \quad C_B = 159.2 \text{ }\mu\text{f}$$

$$\Rightarrow R_{in} = 50 \Omega, \quad A_v = 20$$

88)

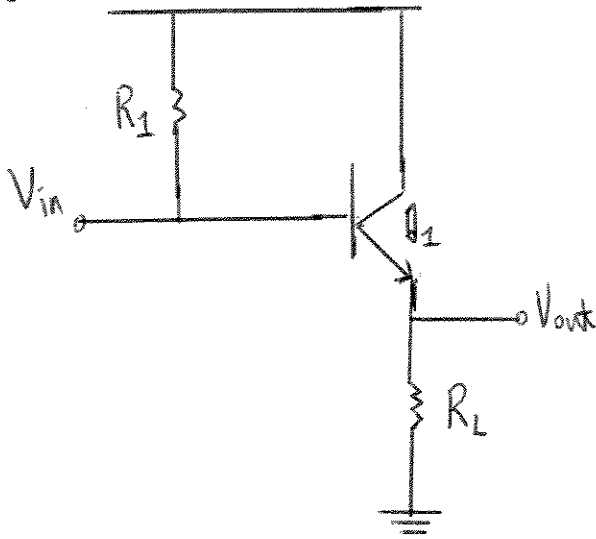

$$A_v = 0.85$$

$$R_{in} > 10\text{K}\Omega$$

$$R_L = 200\Omega$$

$$A_v = \frac{R_L}{R_L + \frac{1}{g_m}} = 0.85 \Rightarrow \frac{200}{200 + \frac{1}{g_m}} = 0.85$$

$$\Rightarrow 200 = 0.85 \left( 200 + \frac{1}{g_m} \right) \Rightarrow \frac{1}{g_m} = 35.294\Omega$$

$$\Rightarrow I_c = \frac{26\text{mV}}{35.294\Omega} = 0.737\text{mA}, \quad V_{BE} = V_T \ln\left(\frac{0.737}{6 \times 10^{-8}}\right) = 0.724\text{V}$$

$$R_{in} = R_1 \parallel (r_{\pi} + (1 + \beta)(200\Omega))$$

$$R_{in} = R_1 \parallel 23.73\text{K}$$

$$R_{in} = \frac{R_1 \cdot 23.73\text{K}}{R_1 + 23.73\text{K}} > 10\text{K} \Rightarrow R_1 > 17.28\text{K} \text{ (Input Impedance Requirement)}$$

To support an  $I_c$  of 0.737,  $R_1$  must be determined.



88)


$$R_1 = \frac{2.5 - (0.724 + (0.737)(0.2)/0.99)}{0.737 / 100}$$

$$R_1 = 220.77 \text{ k}\Omega$$

$$R_1 = 220.77 \text{ k}\Omega \Rightarrow R_{in} = 220.77 \text{ k}\Omega // 23.73 \text{ k}\Omega$$
$$R_{in} = 21.43 \text{ k}\Omega > 10 \text{ k}\Omega$$

$$\begin{array}{l} R_1 = 220.77 \text{ k}\Omega \\ R_L = 200 \Omega \end{array} \Rightarrow \begin{array}{l} A_v = 0.85 \\ R_{in} = 21.43 \text{ k}\Omega \end{array}$$

89)

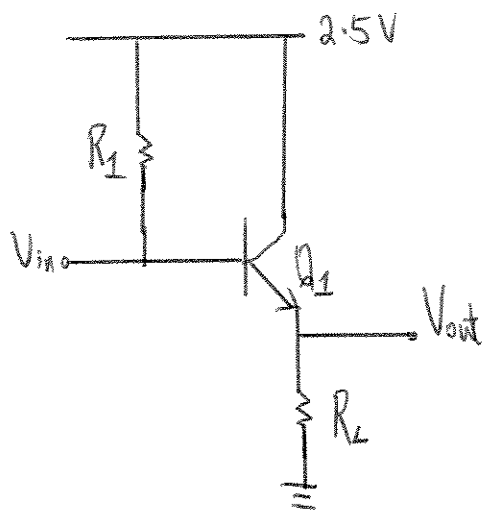

$$\text{Power} = 5 \text{ mW}$$

$$A_v = 0.9$$

$$A_v = \frac{R_L}{R_L + \frac{1}{g_m}} = 0.9 \Rightarrow R_L = 0.9 \left( R_L + \frac{1}{g_m} \right)$$


$$R_L = 9 \frac{1}{g_m}$$

$$\text{Power} = 2.5 \left( I_c + \frac{I_c}{\beta} \right) \Rightarrow I_c = 1.98 \text{ mA}$$

$$\frac{1}{g_m} = \frac{V_T}{I_c} = \frac{26 \text{ mV}}{1.98 \text{ mA}} = 13.13 \Omega$$

$$R_L = (9)(13.13) = 118.17 \Omega$$

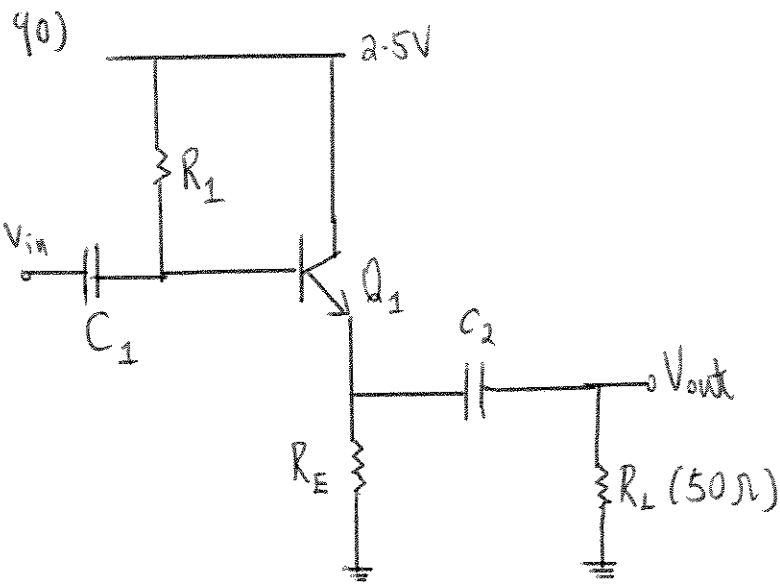This is the minimum load resistance, since anything lower will lower the voltage gain.



$A_v = 0.8$   
 Since  $R_E$  doesn't affect voltage gain significantly.

$$A_v \approx \frac{R_L}{R_L + \frac{1}{g_m}} = 0.8$$

$$R_L = 0.8 \left( R_L + \frac{1}{g_m} \right)$$

$$0.2 R_L = 0.8 \frac{1}{g_m}$$

$$R_L = 4 \frac{1}{g_m} \Rightarrow \frac{R_L}{4} = \frac{1}{g_m} = 12.5 = \frac{V_T}{I_c}$$

$$I_c = \frac{26 \text{ mV}}{12.5 \Omega} = 2.08 \text{ mA}$$

$$V_{BE} = V_T \ln \left( \frac{I_c}{I_s} \right) = 0.751 \text{ V}$$

$$\text{Let } R_E I_c = 20 V_T, \quad R_E = \frac{20}{g_m} = 250 \Omega$$

(0.52V)

$$R_L = \frac{2.5 - (0.751 + 0.52)}{0.0208 \text{ mA}} = 59.1 \text{ K}$$

90)

$$\frac{1}{(2\pi)(100 \times 10^6)C_1} = \frac{1}{10} \frac{1}{g_m} \Rightarrow C_1 = 1.27 \text{ nf}$$

$$\frac{1}{(2\pi)(100 \times 10^6)C_2} = \frac{1}{10} 50 \Rightarrow C_2 = 0.32 \text{ nf}$$

So  $C_2$  will not load  $Q_1$ .

$$C_1 = 1.27 \text{ nf}$$

$$C_2 = 0.32 \text{ nf}$$


$$R_1 = 59.1 \text{ k}\Omega$$

$$R_{E1} = 250 \Omega$$


$$R_L = 50 \Omega$$

$$\Rightarrow A_V = 0.8$$


1.

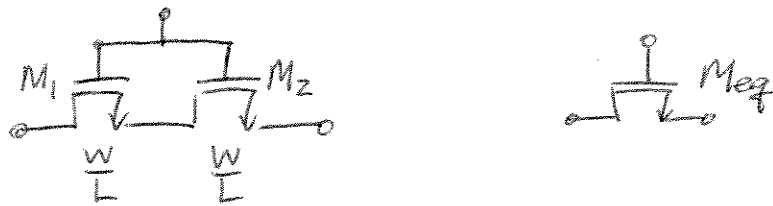

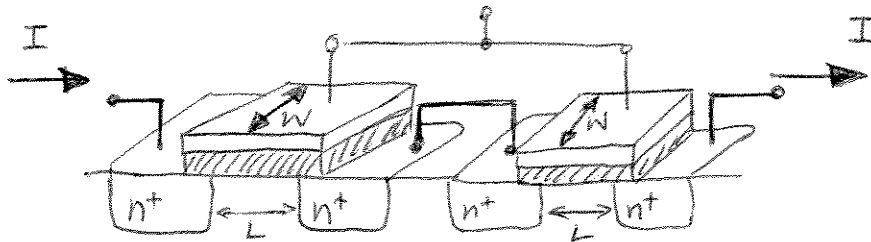Intuitively, this is similar to having twice of the original channel length:



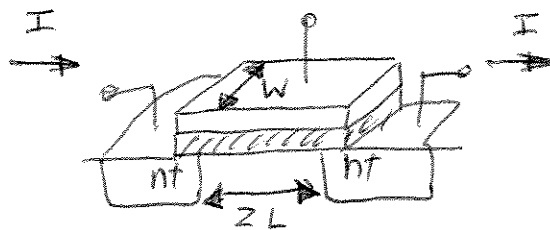
Since current flowing into either non-gate terminals must come out at the other terminal (KCL) and the intermediate node is equipotential, this is as if we have a  $M_{eq}$  with width  $W$  & length  $2L$ :



This approximation can simplify a lot of calculations.

2. A key point to remember: the charge density APPROACHES zero (not EQUALS) at pinch-off. In other words,  $Q$  is never exactly equal to zero (albeit very close.) Another way to view this phenomenon is by observing  $I = Q \cdot v$ : recognize that  $v$  is finite. Since we get some finite value of  $I$  at pinch-off, we expect  $Q \neq 0$ .

Consider the following:

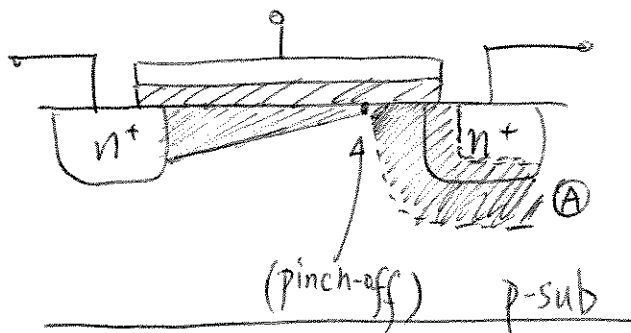

The shaded region,  $\textcircled{A}$ , represents a reverse-biased pn junction. Just as a diode, there exist minority

profiles on p & n sides, which  $\neq 0$ .

Pinch-off implies that the depletion region created no longer has free carriers. The depletion still sweeps all electrons from inversion channel to drain.

3. Given :  $C_{ox} = 10 \text{ fF}/\mu\text{m}^2$      $W = 5 \mu\text{m}$      $L = 0.1 \mu\text{m}$   
 $V_{gs} - V_{TH} = 1 \text{ V}$      $V_{ds} = 0$



Find : total charge stored in channel,  $Q_{tot}$

$$Q_{tot} = W C_{ox} (V_{gs} - V_{TH}) L$$

$$= (5 \mu\text{m})(10 \text{ fF}/\mu\text{m}^2)(1 \text{ V})(0.1 \mu\text{m}) = 5 \text{ fC}$$

$$4. (a) Q = W C_{ox} (V_{GS} - V_{TH} - V(x))$$
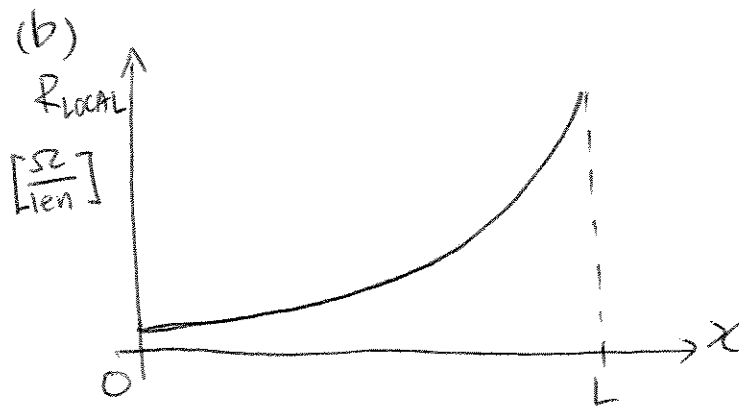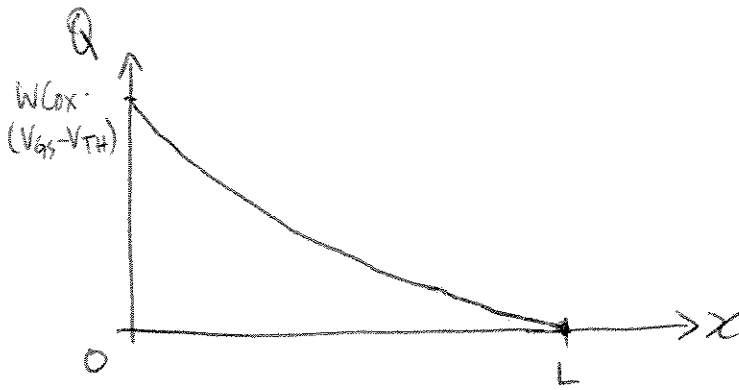
$$= -W C_{ox} \cdot V(x) + W C_{ox} (V_{GS} - V_{TH})$$



$$R \propto \frac{L}{\mu Q}$$

↑  
mobility  
of  
charge.



$$5. \quad I_D = W C_{ox} [V_{GS} - V(x) - V_{TH}] \mu_n \frac{dV(x)}{dx}$$

$$\text{Define: } A = \frac{I_D}{W C_{ox} \mu_n}, \quad B = V_{GS} - V_{TH}$$

$$\Rightarrow A = (B - V) \frac{dV}{dx} = \frac{d}{dx} \left( BV - \frac{V^2}{2} \right)$$

Integrating  $A = \frac{d}{dx} (BV - V^2/2)$  gives:

$$Ax = BV - V^2/2 \Rightarrow V^2 - 2BV + 2Ax = 0$$


Using quadratic formula:

$$\begin{aligned} V_{+,-} &= \frac{2B \pm \sqrt{4B^2 - 4 \cdot 2A \cdot x}}{2} = B \pm \sqrt{B^2 - 2Ax} \\ &= B \left( 1 \pm \sqrt{1 - 2 \left( \frac{A}{B^2} \right) x} \right) \end{aligned}$$

$$= (V_{GS} - V_{TH}) \left\{ 1 \pm \sqrt{1 - \left[ 2 \cdot \frac{I_D}{W C_{ox} \mu_n (V_{GS} - V_{TH})^2} \right] x} \right\}$$


We know that  $0 \leq V(x) \leq V_{GS} - V_{TH}$  (pinch-off), and the term inside the square root is  $> 0$ . Therefore, we take  $V_-$  as the solution.
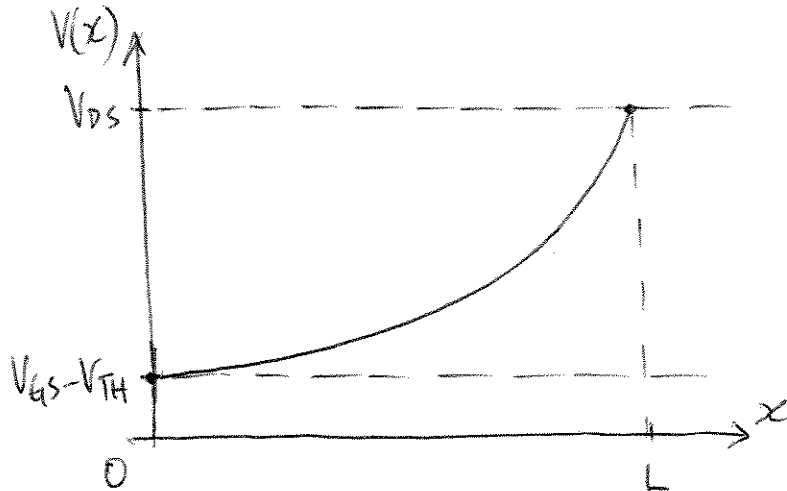
$$\text{i.e. } V(x) = (V_{GS} - V_{TH}) \left\{ 1 - \sqrt{1 - \left[ \frac{2I_D}{WCoxLn(V_{GS} - V_{TH})^2} \right] x} \right\}$$



$\because I_D \propto W$   
 $\Rightarrow V(x)$  is independent of  $W$ .
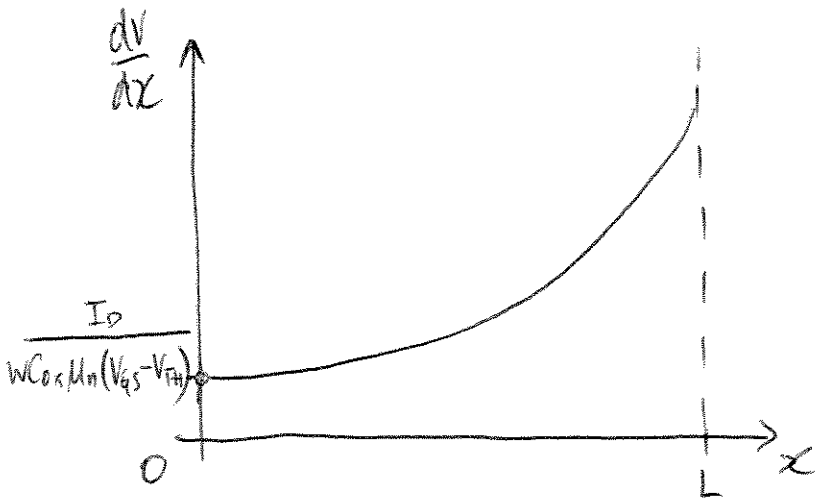
$$\frac{dV}{dx} = \frac{I_D}{WCoxLn(V_{GS} - V_{TH})} \cdot \left[ 1 - \frac{2I_D \cdot x}{WCoxLn(V_{GS} - V_{TH})^2} \right]^{-\frac{1}{2}}$$



6. No.

By varying  $V_{GS} - V_{TH}$  &  $V_{DS}$ , we can only obtain  $\mu_n C_{ox} \frac{W}{L}$ , but not  $\mu_n C_{ox}$  &  $\frac{W}{L}$

individually.

7. Given : NMOS  $I_D = 1 \text{ mA}$   $V_{GS} - V_{TH} = 0.6 \text{ V}$   
 $I_D = 1.6 \text{ mA}$   $V_{GS} - V_{TH} = 0.8 \text{ V}$   
(triode region)  $\mu_n C_{ox} = 200 \frac{\text{mA}}{\text{V}^2}$

Find  $V_{DS}$  &  $W/L$ .

$$1 \text{ mA} = \mu_n C_{ox} \frac{W}{L} \left[ (0.6) V_{DS} - \frac{V_{DS}^2}{2} \right] \quad \text{--- ①}$$

$$1.6 \text{ mA} = \mu_n C_{ox} \frac{W}{L} \left[ (0.8) V_{DS} - \frac{V_{DS}^2}{2} \right] \quad \text{--- ②}$$

$$\text{②} \div \text{①} : 1.6 = \frac{0.8 V_{DS} - \frac{V_{DS}^2}{2}}{0.6 V_{DS} - \frac{V_{DS}^2}{2}} = \frac{1.6 - V_{DS}}{1.2 - V_{DS}}$$

$$\Rightarrow V_{DS} = \frac{1.6(0.2)}{0.6} \approx 0.533 \text{ V}$$

$$\begin{aligned} \Rightarrow \frac{W}{L} &= \frac{I_D}{\mu_n C_{ox} \left[ (V_{GS} - V_{TH}) V_{DS} - \frac{V_{DS}^2}{2} \right]} \\ &= \frac{1 \text{ mA}}{200 \frac{\text{mA}}{\text{V}^2} \left[ (0.6 \text{ V})(0.533 \text{ V}) - \frac{(0.533 \text{ V})^2}{2} \right]} \\ &\approx 28. \end{aligned}$$

$$8. \quad I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} [2(V_{GS} - V_{TH}) V_{DS} - V_{DS}^2]$$

$$g_m \triangleq \frac{\partial I_D}{\partial V_{GS}} = \frac{1}{2} \mu C_{ox} \frac{W}{L} \cdot 2 V_{DS} = \mu C_{ox} \frac{W}{L} V_{DS}$$

$$g_m |_{V_{DS}=0} = 0.$$

Intuitively, when  $V_{GS} > V_{TH}$ , mobile charges (channel) become available. This determines the on-resistance. But since there is no  $I_D$  ( $\because V_{DS}=0$ ), it does not matter if there is an incremental change in  $V_{GS}$  (i.e.  $\partial V_{GS}$ ). Since varying  $V_{GS}$  gives no change in  $I_D$ ,  $g_m |_{V_{DS}=0} = 0$ .

9. Given:  $V_{DD} = 1.8 \text{ V}$      $\frac{W}{L} = 20$      $\mu_n C_{ox} = 200 \frac{\mu\text{A}}{\text{V}^2}$   
 $V_{TH} = 0.4 \text{ V}$

Find minimum-on resistance.

$$R_{on} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{DD} - V_{TH})}$$
$$= \frac{1}{\left(200 \frac{\mu\text{A}}{\text{V}^2}\right) (20) (1.8 - 0.4) \text{ V}} = 179. \Omega$$

$$10. \quad 500 = \frac{1}{\mu_n C_{ox} \frac{W}{L} (1 - V_{TH})}$$

$$400 = \frac{1}{\mu_n C_{ox} \frac{W}{L} (1.5 - V_{TH})}$$

For the same NMOS,  $\mu_n C_{ox}$  &  $\frac{W}{L}$  are fixed

$$\Rightarrow 500(1 - V_{TH}) \stackrel{?}{=} 400(1.5 - V_{TH})$$
$$500(0.6) \neq 400(1.1)$$

$\therefore$  This is not possible.

$$11. \quad I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} [2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2]$$

$$r_{DS, tri} \triangleq \left( \frac{\partial I_D}{\partial V_{DS}} \right)^{-1} = \left[ \frac{\partial}{\partial V_{DS}} \left\{ \frac{1}{2} \mu C_{ox} \frac{W}{L} [2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2] \right\} \right]^{-1}$$

$$= \left[ \mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) - \mu C_{ox} \frac{W}{L} V_{DS} \right]^{-1}$$

$$= \frac{1}{\mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH} - V_{DS})}$$



12. When MOS operates as a resistor,


$$R_{on} = \frac{1}{\mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH})}$$

$$\Rightarrow \tau = R_{on} C_{GS} = \frac{WL C_{ox}}{\mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH})} = \frac{L^2}{\mu (V_{GS} - V_{TH})}$$

To minimize the time constant,

- 1) use minimum channel length, and
- 2) maximize overdrive voltage.


13.

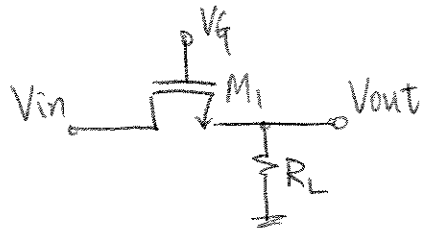

Given  $V_{in} \approx 0$   
 $V_G = 1.8 \text{ V}$   
 $R_L = 100 \Omega$

Find  $\frac{W}{L}$  such that signal output attenuates by only 5%.

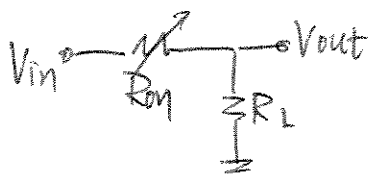$V_{in} \approx 0$  implies that we can approximate  $M_1$  as a linear resistance controlled by  $V_G$ . Therefore, the equivalent circuit becomes a resistive divider:



$$V_{out} = 0.95 V_{in}$$


$$= \frac{R_L}{R_{on} + R_L} V_{in}$$

$$\Rightarrow R_{on} \approx 5.3 \Omega$$

$$\therefore \frac{W}{L} = \frac{1}{\mu C_{ox} (V_{GS} - V_{TH}) R_{on}} \approx \frac{1}{200 \frac{\mu\text{A}}{\text{V}^2} (1.8 - 0.4)(5.352)}$$

$$= 674.$$

14.

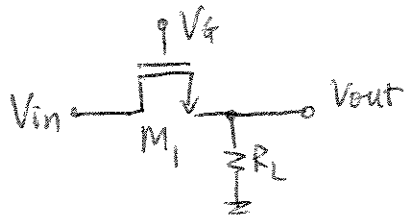

$V_0 \sim \text{few mV.}$

(a)  $V_{in} = V_0 \cos \omega t$        $V_{out} = 0.95 (V_0 \cos \omega t)$

$$V_{out} = \frac{R_L}{R_{on} + R_L} V_{in} \quad \Rightarrow \quad \frac{R_L}{R_{on} + R_L} = 0.95 V_0$$

$$R_{on} = \frac{R_L}{0.95 V_0} = \frac{1}{\left(\frac{0.95 V_0}{1 - 0.95 V_0}\right) \mu_n C_{ox} \frac{W}{L} (V_G - V_{TH})}$$

$$\therefore \frac{W}{L} = \frac{0.95 V_0 / (1 - 0.95 V_0)}{\mu_n C_{ox} R_L (V_G - V_{TH})}$$


(b)  $V_{out} = 0.95 V_{in} = 0.95 (V_0 \cos \omega t + 0.5)$   
 $\approx 0.95 \times 0.5 = 0.475$   
 ( $\because V_0$  is relatively small)

$$\therefore R_{on} = \frac{R_L}{0.9} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_G - V_{TH})}$$


$$\Rightarrow \frac{W}{L} = \frac{0.9}{\mu_n C_{ox} R_L (V_G - V_{TH})}$$

Results show that if there is no DC voltage as input, the  $R_{on}$  varies with changing sinewave. With a DC bias voltage,  $R_{on}$  becomes more stable (independent of  $V_o$ ).

15.

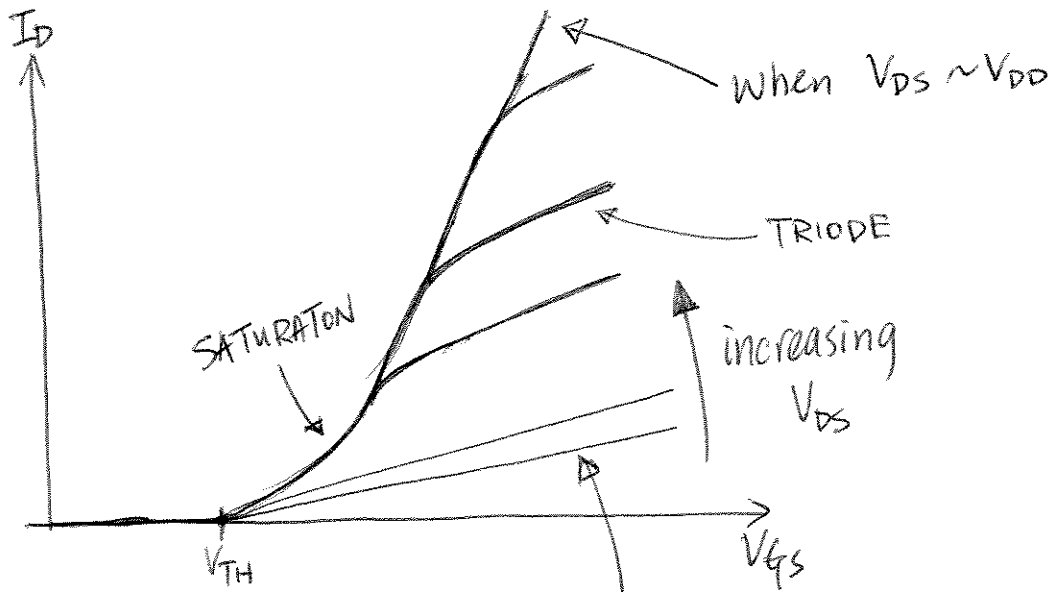

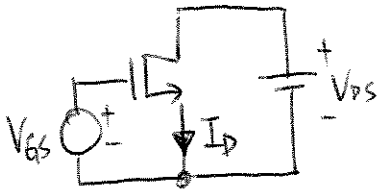TRIODE (once  $V_{GS} > V_{TH}$ )  
( $V_{DS}$  so small that it never reaches saturation.)



16. The peak of the parabola signifies pinch-off (i.e.  $V_{DS} = V_{GS} - V_{TH}$ ). This means that (with  $\lambda = 0$ )  $I_D$  cannot be increased further by increasing  $V_{DS}$ . Since this curve must be continuous, the peak  $I_D$  must originate from the peak of the parabola.

$$17. \quad I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^\alpha, \quad \alpha < 3$$

$$g_m \triangleq \frac{\partial I_D}{\partial V_{GS}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \cdot \alpha (V_{GS} - V_{TH})^{\alpha-1}$$

$$= \frac{\alpha}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^{\alpha-1}$$

$$= \frac{\alpha I_D}{(V_{GS} - V_{TH})}$$

$$18. \quad I_D = W C_{ox} (V_{GS} - V_{TH}) v_{SAT}$$

$$g_m \triangleq \frac{\partial I_D}{\partial V_{GS}} = W C_{ox} v_{SAT}$$



19. (a) OFF  $\because V_{GS} = 0$

(b) SATURATION  $\because V_{GS} > V_{TH}$  &  $V_{DS} > V_{GS} - V_{TH}$

(c) TRIODE (LINEAR)  $\because V_{GS} > V_{TH}$  &  
 $V_{DS} \ll 2(V_{GS} - V_{TH})$

(d) TRIODE  $\because V_{GS} > V_{TH}$  &  $V_{DS} < V_{GS} - V_{TH}$   
(REMEMBER: MOSFET IS SYMMETRIC)

(e) TRIODE  $\because V_{GS} > V_{TH}$  &  $V_{DS} < V_{GS} - V_{TH}$

(f) OFF  $\because V_{GS} = 0$

(g) SATURATION  $\because V_{GS} > V_{TH}$  &  $V_{DS} > V_{GS} - V_{TH}$

(h) SATURATION  $\because V_{GS} > V_{TH}$  &  $V_{DS} > V_{GS} - V_{TH}$

(i) SATURATION  $\because V_{GS} > V_{TH}$  &  $V_{DS} > V_{GS} - V_{TH}$


20. (a) OFF  $\because V_{GS} = 0$  ( $V_{GS} < V_{TH}$ )

(b) OFF  $\because V_{GS} = 0$  ( $V_{GS} < V_{TH}$ )

(c) TRIODE (LINEAR)  $\because V_{GS} > V_{TH}$  &  
 $V_{DS} \ll 2(V_{GS} - V_{TH})$

(d) SATURATION  $\because V_{GS} > V_{TH}$  &  $V_{DS} > V_{GS} - V_{TH}$

21.

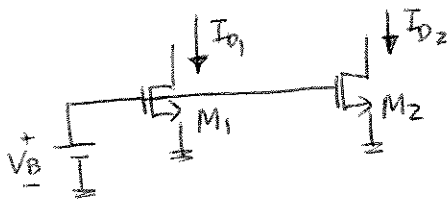

$$0.99I_{D2} < I_{D1} < 1.01I_{D2}$$

Since  $M_1$  &  $M_2$  are treated as current sources, they are assumed to be in saturation.

Evaluate  $\lambda$  at boundaries:

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_B - V_{TH})^2 (1 + \lambda V_{DS1}) \quad \text{--- (1)}$$


$$I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_B - V_{TH})^2 (1 + \lambda V_{DS2}) \quad \text{--- (2)}$$

$$\text{(1)} \div \text{(2)} : \frac{I_{D1}}{I_{D2}} = \frac{0.99 I_{D2}}{I_{D2}} = \frac{1 + \lambda V_{DS1}}{1 + \lambda V_{DS2}}$$

$$\therefore \lambda = \frac{0.01}{0.99 V_{DS2} - V_{DS1}} = \frac{0.01}{0.99(1V) - (0.5V)} = 0.02 V^{-1}$$

Maximum tolerable  $\lambda = 0.02 V^{-1}$

22.

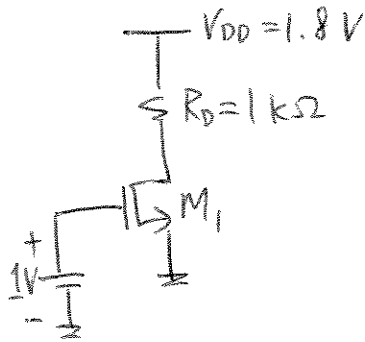

$$\lambda = 0, V_{TH} = 0.4\text{ V}$$

$$\mu_n C_{ox} = 200 \frac{\mu\text{A}}{\text{V}^2}$$

$M_1$  sits at the edge of saturation when  $V_{DS} = V_{GS} - V_{TH}$ .

$$\Rightarrow V_{DS, \text{edge}} = (1 - 0.4)\text{ V} = 0.6\text{ V}$$

$$\text{By KCL, } I_{D1} = I_{R_D} = \frac{V_{DD} - V_{DS}}{R_D} = \frac{1.2\text{ V}}{1\text{ k}\Omega} = 1.2\text{ mA}$$

$$\therefore I_{D1} = 1.2\text{ mA} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$\Rightarrow \frac{W}{L} = \frac{2I_{D1}}{\mu_n C_{ox} (V_{GS} - V_{TH})^2} = \frac{2(1.2\text{ mA})}{\left(200 \frac{\mu\text{A}}{\text{V}^2}\right) (1 - 0.4)^2 \text{ V}^2}$$

$$\approx 33.$$

23. If gate oxide thickness,  $t_{ox}$ , doubles, the corresponding capacitance,  $C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$ , is halved.

$\Rightarrow \mu_n C_{ox}$  is also halved


$\Rightarrow I_{D_1}$  is halved  $\Rightarrow V_{DS}$  increases

$\Rightarrow M_1$  stays in saturation ( $V_{DS} > V_{GS} - V_{TH}$ )

$$I_{D_1} = \frac{1.2 \text{ mA}}{2} = 0.6 \text{ mA}$$

$$\Rightarrow V_{DS} = (1.8 \text{ V}) - (0.6 \text{ mA})(1 \text{ k}\Omega) = 1.2 \text{ V}$$

24.

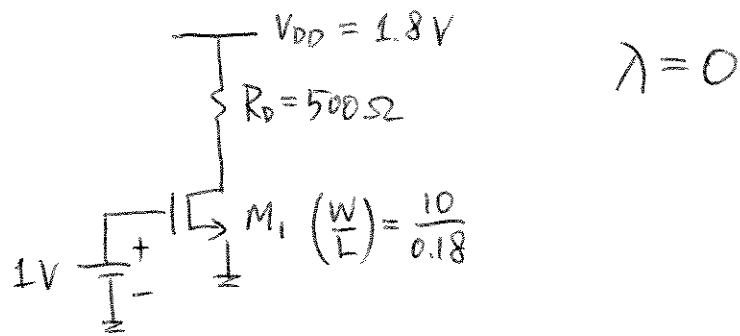

To avoid triode region,  $V_{DS} \geq V_{GS} - V_{TH}$ .

$$\Rightarrow V_{DS} \geq 1 - 0.4 = 0.6V$$


$$\begin{aligned} \Rightarrow I_{D1} &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \\ &= \frac{1}{2} \left( 200 \frac{\mu A}{V^2} \right) \left( \frac{10}{0.18} \right) (0.6)^2 = 2 \text{ mA} \end{aligned}$$

By KCL,  $\frac{V_{DD} - V_{DS}}{R_D} = 2 \text{ mA}$

$$\therefore V_{DD} = (2 \text{ mA})(500\Omega) + 0.6V = 1.6V$$

Minimum  $V_{DD} = 1.6V$

25.

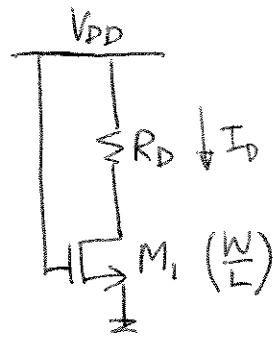


$$\lambda = 0$$

When  $M_1$  operates at the edge of saturation,  $V_{DS} = V_{GS} - V_{TH}$ . Also, by KCL:

$$I_{R_D} = I_{D_1} \Rightarrow \frac{V_{DD} - (V_{DD} - V_{TH})}{R_D} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{DD} - V_{TH})^2$$

$$\therefore V_{TH} = R_D \cdot \underbrace{\frac{1}{2} \mu_n C_{ox} \frac{W}{L}}_{I_D} (V_{DD} - V_{TH})^2$$

26.

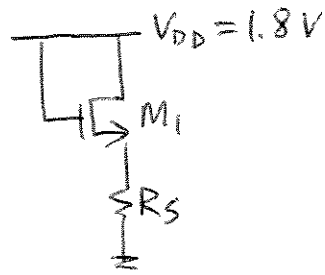

$$\lambda = 0$$

Find  $\left(\frac{W}{L}\right)$  with bias current =  $I_1$ .

Since  $V_{DS} = V_{GS}$  for  $M_1$ , this device always operates in saturation region (given  $V_{GS} > V_{TH}$ ).


By KCL,  $I_1 = I_{RS}$ ; by Ohm's law,  $V_S = I_1 R_S$

$$\Rightarrow \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{DD} - I_1 R_S - V_{TH})^2 = I_1$$

$$\therefore \frac{W}{L} = \frac{2 I_1}{\mu_n C_{ox} (V_{DD} - I_1 R_S - V_{TH})^2}$$



27.

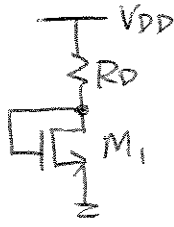

Calculate  $I_1$  if  $\lambda = 0$ .  
Assume  $V_{GS} > V_{TH}$

By KCL,  $I_{RD} = I_1$

$$\Rightarrow \underbrace{\frac{1}{2} \mu_n C_{ox} \frac{W}{L}}_{\triangleq B} (V_{GS} - V_{TH})^2 = \frac{V_{DD} - V_{GS}}{R_D}$$

Re-arrange this to quadratic form:

$$V_{GS}^2 (BR_D) - V_{GS} (2BR_D V_{TH} - 1) + (V_{TH}^2 \cdot BR_D - V_{DD}) = 0$$



$$\Rightarrow V_{GS_{1,2}} = \frac{(BR_D V_{TH} - 1) \pm \sqrt{BR_D (V_{DD} - V_{TH}) + 1}}{BR_D}$$

$$= \frac{(\frac{1}{2} \mu_n C_{ox} (\frac{W}{L}) \cdot R_D \cdot V_{TH} - 1) \pm \sqrt{\frac{1}{2} \mu_n C_{ox} (\frac{W}{L}) R_D (V_{DD} - V_{TH}) + 1}}{\frac{1}{2} \mu_n C_{ox} (\frac{W}{L})}$$



Whether the answer is  $V_{GS_1}$  or  $V_{GS_2}$  depends on other parameters. Also note that since  $M_1$  is diode-connected, it never goes into triode (i.e. either OFF or SATURATION.) This helps in eliminating one of the solutions.

After solving  $V_{GS}$ ,  $I_D = I_1 = \frac{V_{DD} - V_{GS}}{R_D}$



28. (a)

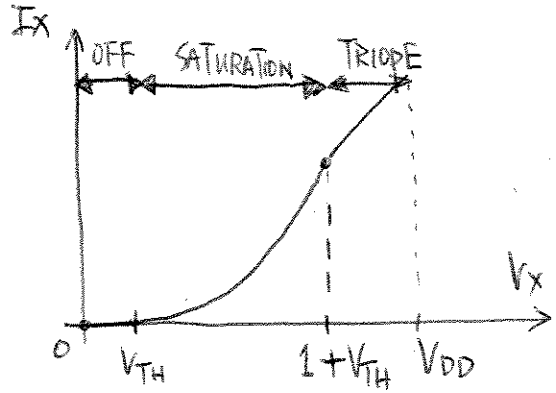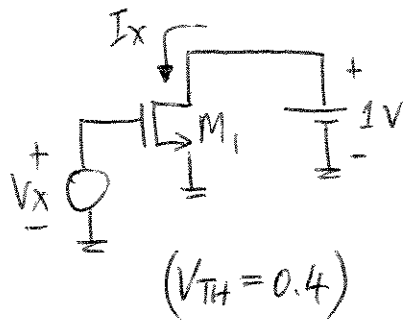



(b)

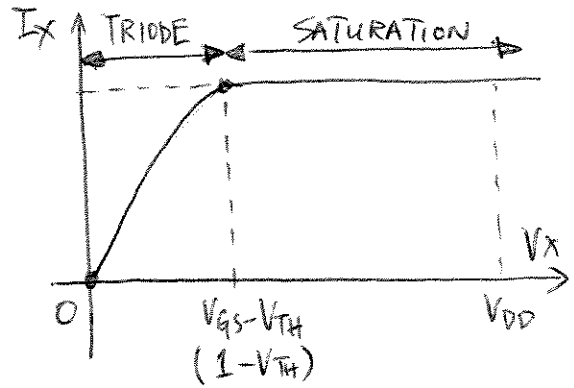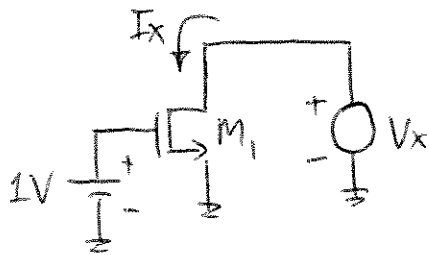


(c)

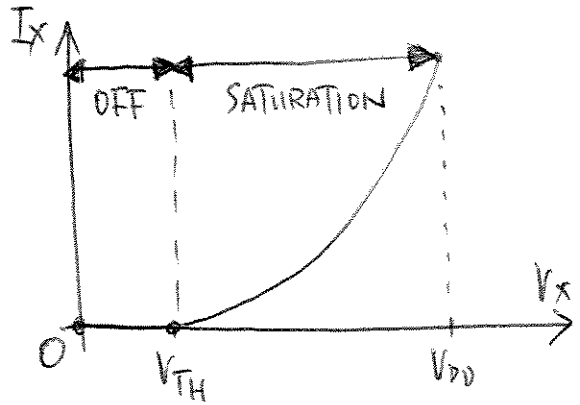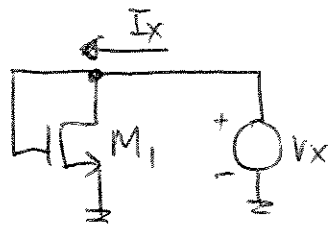

(d)

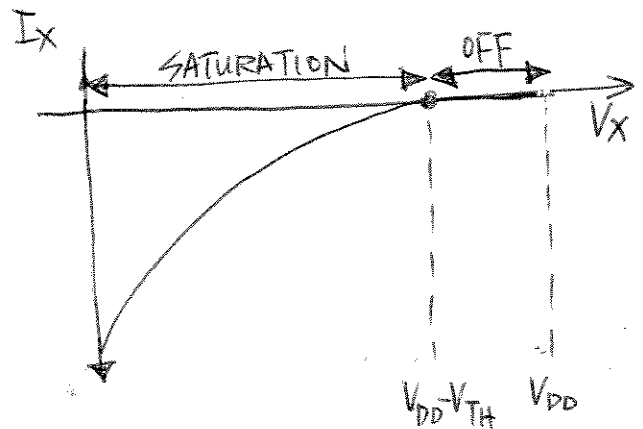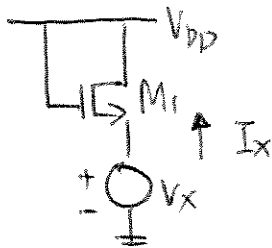

29.

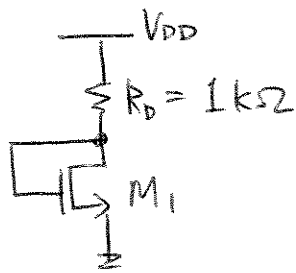

$$\left(\frac{W}{L}\right) = \frac{10}{0.18}, \quad \lambda = 0.1 \text{ V}^{-1}$$

Find  $I_{D1}$ .

Since  $M_1$  is diode-connected, it operates in saturation.


By KCL, 
$$\frac{V_{DD} - V_G}{R_D} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_G - V_{TH})^2 (1 + \lambda V_G)$$

One can solve this by (1) using a graphing calculator, (2) trial-and-error, (3) or iteratively finding  $V_G$ .

Using any method gives  $V_G \approx 0.807 \text{ V}$

$$\Rightarrow I_D = \frac{V_{DD} - V_G}{R_D} \approx 1 \text{ mA}$$

30.

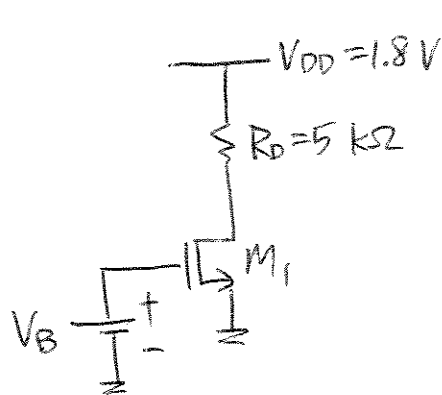

$$\frac{W}{L} = \frac{20}{0.18}, \quad \lambda = 0.1 \text{ V}^{-1}$$

At the edge of saturation,

$$I_{D1} = \frac{V_{DD} - (V_B - V_{TH})}{R_D} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_B - V_{TH})^2 (1 + \lambda(V_B - V_{TH}))$$

This equation can be solved by using a graphing calculator, special programs, or iteratively.

Using any method gives  $V_B \approx 0.57 \text{ V}$   
 $(I_D \approx 0.33 \text{ mA})$

31. An NMOS device with  $\lambda = 0$  must provide a transconductance of  $\frac{1}{50} \frac{1}{\Omega}$ .

(a) Given  $I_D = 0.5 \text{ mA}$ , find  $W/L$ .

$$g_m = \frac{1}{50} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$$\Rightarrow \frac{W}{L} = \frac{g_m^2}{2 \mu_n C_{ox} I_D} = \frac{\left(\frac{1}{50} \frac{1}{\Omega}\right)^2}{2 \left(\frac{200 \mu\text{A}}{\text{V}^2}\right) (0.5 \text{ mA})} \approx 2000$$

(b) Given  $V_{GS} - V_{TH} = 0.5 \text{ V}$ , find  $W/L$ .

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})$$

$$\Rightarrow \frac{W}{L} = \frac{g_m}{\mu_n C_{ox} (V_{GS} - V_{TH})} = \frac{\left(\frac{1}{50} \frac{1}{\Omega}\right)}{\left(\frac{200 \mu\text{A}}{\text{V}^2}\right) (0.5 \text{ V})} \approx 200$$

(c) Given  $V_{GS} - V_{TH} = 0.5 \text{ V}$ , find  $I_D$ .

$$\Rightarrow I_D = \frac{g_m (V_{GS} - V_{TH})}{2} = \frac{\left(\frac{1}{50} \frac{1}{\Omega}\right) (0.5 \text{ V})}{2} \approx 5 \text{ mA}$$

$$32. (a) \quad g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} \quad (I_D \text{ constant})$$

Doubling  $(W/L)$  implies a  $\sqrt{2}$  times increase in  $g_m$ :  $g_{m_{NEW}} = \sqrt{2 \mu_n C_{ox} (2 \frac{W}{L}) I_D} = \sqrt{2} g_m$ .

$$(b) \quad g_m = \frac{2 I_D}{V_{GS} - V_{TH}} \quad (I_D \text{ constant})$$

Doubling  $(V_{GS} - V_{TH})$  decreases  $g_m$  by half:

$$g_{m_{NEW}} = \frac{2 I_D}{2(V_{GS} - V_{TH})} = \frac{1}{2} g_m$$



$$(c) \quad g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} \quad (W/L \text{ constant})$$

Doubling  $I_D$  increases  $g_m$  by  $\sqrt{2}$  times.

$$(d) \quad g_m = \frac{2 I_D}{V_{GS} - V_{TH}} \quad (V_{GS} - V_{TH} \text{ constant})$$

Doubling  $I_D$  increases  $g_m$  by 2 times.

33. (a)

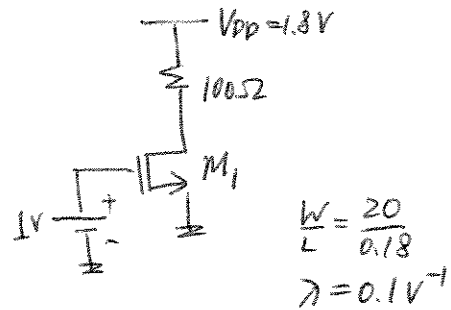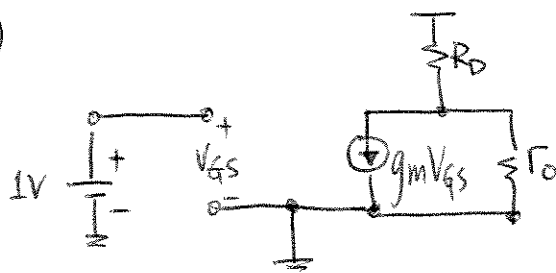

First, verify  $M_1$  is in saturation:

$$V_{DS} = V_{DD} - I_D R_D = V_{DD} - R_D \cdot \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$= 1.8 - 100 \cdot \frac{1}{2} \frac{200 \mu A}{V^2} \left( \frac{20}{0.18} \right) (1 - 0.4)^2 (1 + \lambda V_{DS})$$

Solving this gives  $V_{DS} \approx 1.35 V > V_{GS} - V_{TH}$ .



$$\therefore g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) = \left( \frac{200 \mu A}{V^2} \right) \left( \frac{20}{0.18} \right) (1 - 0.4 V)$$

$$\approx 0.013 \text{ } \frac{1}{\Omega}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{\lambda \left( \frac{V_{DD} - V_{DS}}{R_D} \right)} = \frac{1}{0.1 V^{-1} \left( \frac{0.45 V}{100.52} \right)} \approx 2222. \Omega$$



(b)

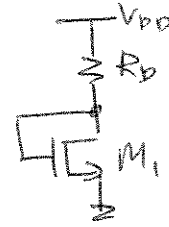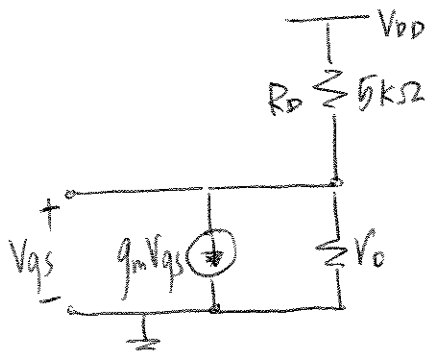

$$\text{By KCL, } \frac{V_{DD} - V_{GS}}{R_D} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{GS})$$



Solving this yields  $V_{GS} \approx 0.546 \text{ V} > V_{TH}$

$$\Rightarrow g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) = \frac{200 \mu\text{A}}{\text{V}^2} \left( \frac{20}{0.18} \right) (0.146 \text{V})$$
$$\approx 0.00324 \text{ } \mu\text{S}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{\lambda \left( \frac{V_{DD} - V_{GS}}{R_D} \right)} = \frac{1}{0.1 \text{V}^{-1} \left( \frac{1.8 - 0.546}{5 \text{k}} \right)}$$

$$\approx 40. \text{ k}\Omega$$

(c)

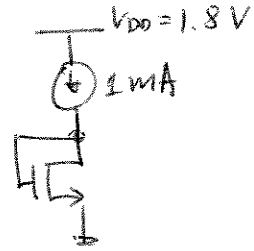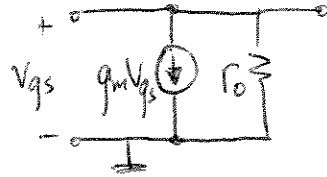


(Note: ideal current source is open in small signal)

$$g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} = \sqrt{2 \left( \frac{200 \mu A}{V^2} \right) \left( \frac{20}{0.18} \right) (1 \text{ mA})}$$
$$\approx 0.0067 \text{ } \frac{1}{\Omega}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.1 \text{ V}^{-1})(1 \text{ mA})} = 10 \text{ k}\Omega$$

(d)

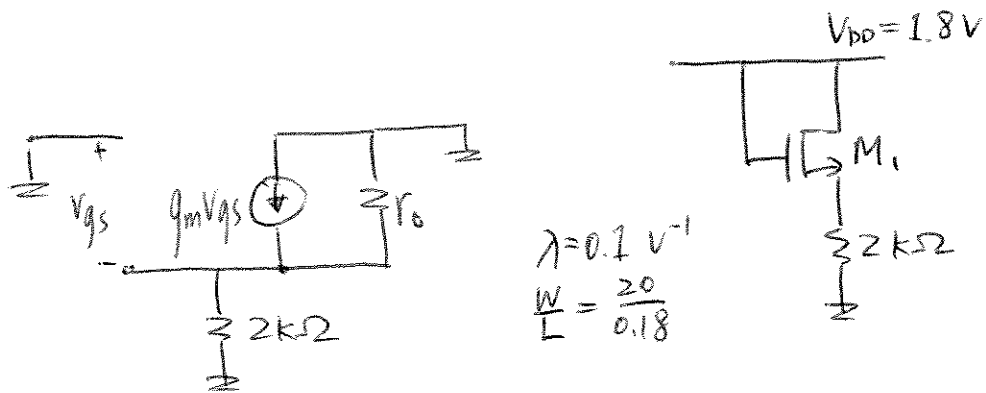

(Note: ideal voltage source is shorted; to GND in this problem because  $V_{DD}$  is si -ended.)

By KCL,  $I_D = I_R$

$$\Rightarrow \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left[ (V_{DD} - V_s) - V_{TH} \right]^2 \left[ 1 + \lambda (V_{DD} - V_s) \right] = V_s / 2\text{ k}\Omega.$$


Solving this (analytically or numerically) gives  $V_s \approx 1.18\text{ V}$

$$\Rightarrow I_D = V_s / 2\text{ k}\Omega \approx 0.59\text{ mA}.$$

$$g_m = \frac{2 I_D}{V_{GS} - V_{TH}} = \frac{2(0.59\text{ mA})}{(1.8 - 1.18 - 0.4)\text{ V}} \approx 0.0054\text{ V}^{-1}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.1\text{ V}^{-1})(0.59\text{ mA})} \approx 16.9\text{ k}\Omega$$

(e)

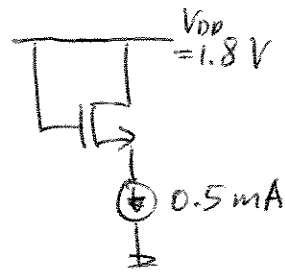

$$0.5 \text{ mA} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [(V_{DD} - V_S) - V_{TH}]^2 [1 + \lambda (V_{DD} - V_S)]$$


Solving this equation gives  $V_S \approx 1.19 \text{ V}$

$$\Rightarrow g_m = \frac{2 I_D}{V_{GS} - V_{TH}} = \frac{2(0.5 \text{ mA})}{(1.8 - 1.19 - 0.4) \text{ V}} \approx 0.0048 \frac{1}{\Omega}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.1 \text{ V}^{-1})(0.5 \text{ mA})} = 20 \text{ k}\Omega.$$

$$34. \quad g_m = \sqrt{2\mu C_{ox} \frac{W}{L} I_D} \quad r_o = \left( \frac{\partial I_D}{\partial V_{DS}} \right)^{-1} = \frac{1}{\lambda I_D}$$


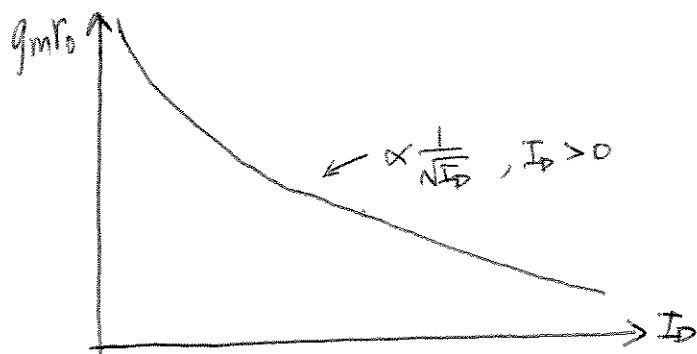
$$g_m r_o = \frac{\sqrt{2\mu C_{ox} \left( \frac{W}{L} \right) I_D}}{\lambda I_D} = \frac{1}{\lambda} \sqrt{\frac{2\mu C_{ox} \left( \frac{W}{L} \right)}{I_D}}$$



$$35 \quad (a) \quad g_m = \mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH})$$

$$r_o = \frac{1}{\lambda I_D}$$
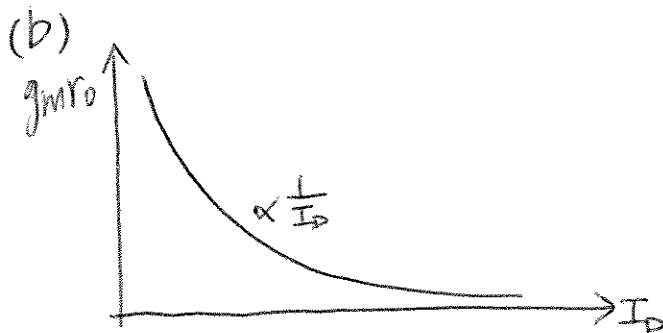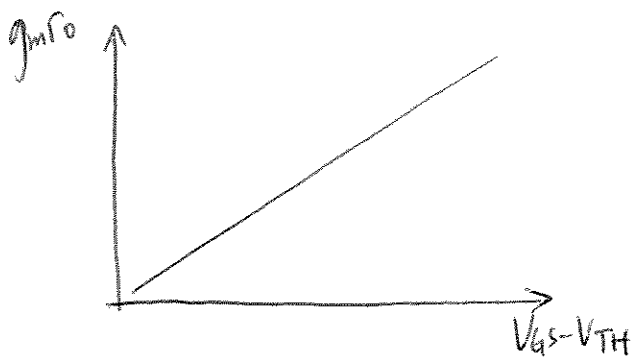
$$g_m r_o = \frac{\mu C_{ox} (W/L) (V_{GS} - V_{TH})}{\lambda I_D}$$




3b. Given NMOS with  $\lambda = 0.1 \text{ V}^{-1}$   $g_m r_o = 20$   
 $V_{DS} = 1.5 \text{ V}$   
 determine  $W/L$  if  $I_D = 0.5 \text{ mA}$ .

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.1 \text{ V}^{-1})(0.5 \text{ mA})} = 20 \text{ k}\Omega$$

$$\Rightarrow g_m = \frac{20}{20 \text{ k}\Omega} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$$\begin{aligned} \therefore \frac{W}{L} &= \left( \frac{20}{20 \text{ k}\Omega} \right)^2 \frac{1}{2 \mu_n C_{ox} I_D} \\ &= \left( \frac{1}{1 \text{ k}\Omega} \right)^2 \frac{1}{2 \left( \frac{200 \mu\text{A}}{\text{V}^2} \right) (0.5 \text{ mA})} \approx 5. \end{aligned}$$

37.

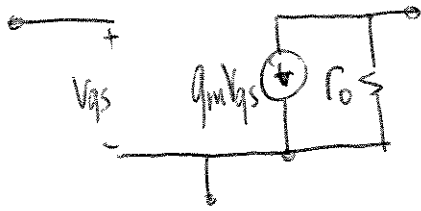Given  $\lambda = 0.2 \text{ V}^{-1}$ 

$$g_m r_o = 20$$

$$V_{DS} = 1.5 \text{ V}$$

$$I_D = 0.5 \text{ mA}$$

Calculate  $\frac{W}{L}$ .


$$g_m = \frac{20}{r_o} = 20 \cdot \lambda I_D = 20 (0.2 \text{ V}^{-1}) (0.5 \text{ mA}) = 0.002 \text{ V}^{-1} \Omega$$

$$\Rightarrow g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$


$$\therefore \frac{W}{L} = \frac{g_m^2}{2 \mu_n C_{ox} I_D} = \frac{(0.0002 \text{ V}^{-1} \Omega)^2}{2 \left( \frac{200 \mu\text{A}}{\text{V}^2} \right) (0.5 \text{ mA})} = 20$$




38. (a)

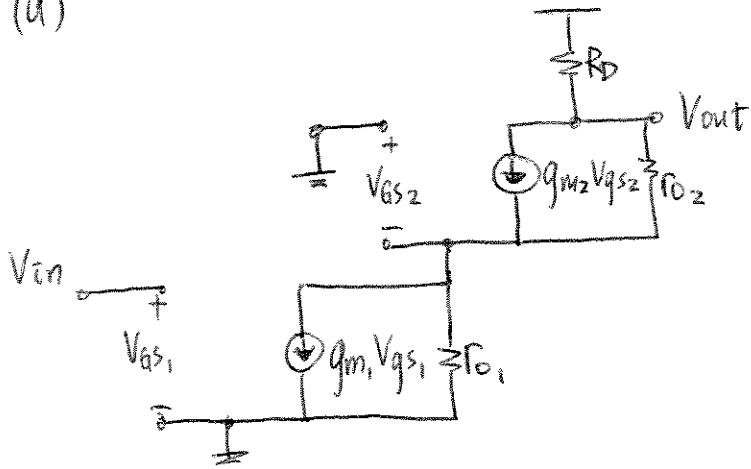


(b)

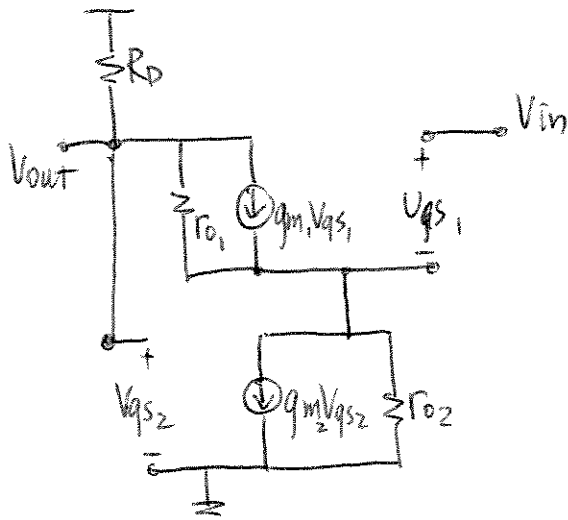


(c)

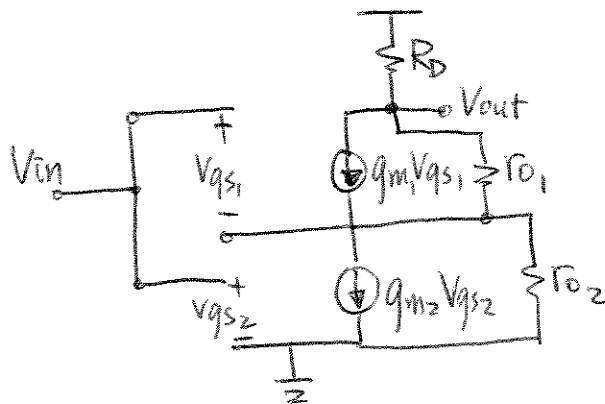

(d)

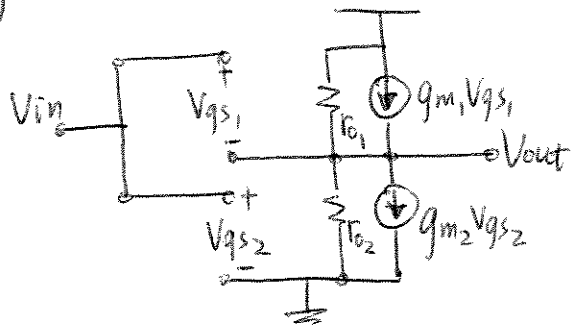

(e)

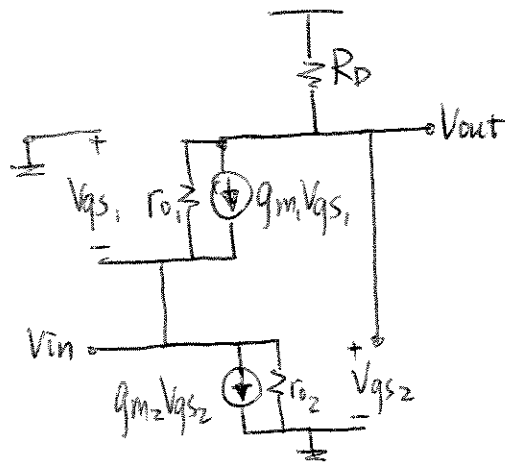

39. (a) OFF  $\because |V_{SG}| = 0$

(b) OFF  $\because |V_{SG}| < |V_{TH}| = 0.4V$

(c) SATURATION  $\because |V_{SD}| > |V_{SG}| - |V_{TH}|$

(d) OFF  $\because V_{SG} < |V_{TH}|$


40. (a) SATURATION  $\because V_{SD} > V_{SG} - |V_{TH}|$

(b) LINEAR (RESISTIVE)  $\because V_{SG} > |V_{TH}|$   
 $V_{SD} \ll 2(V_{SG} - |V_{TH}|)$

(c) (EDGE OF) SATURATION  $\because V_{SG} > |V_{TH}|$   
 $V_{SD} = V_{SG} - |V_{TH}|$

(d) TRIODE  $\because V_{SG} > |V_{TH}|$   
 $V_{SD} < V_{SG} - |V_{TH}|$

41.

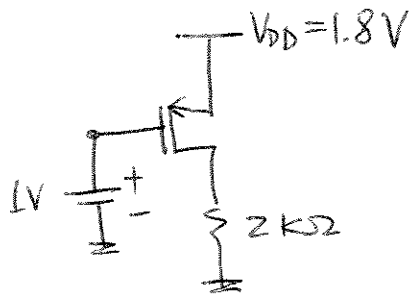

At the edge of saturation,  $V_{SD} = V_{SG} - |V_{TH}|$   
 $\Rightarrow V_D = 1.4V$ .


By KCL,  $I_{D1} = I_R$

$$\Rightarrow \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_{TH}|)^2 = \frac{V_D}{2k\Omega}$$

$$\therefore \frac{W}{L} = \frac{V_D}{2k\Omega} \cdot \frac{2}{\mu_p C_{ox} (V_{SG} - |V_{TH}|)^2}$$

$$= \frac{1.4V}{2k\Omega} \cdot \frac{2}{100 \frac{\mu A}{V^2} (0.8V - 0.4V)^2} \approx 87.5$$

42.

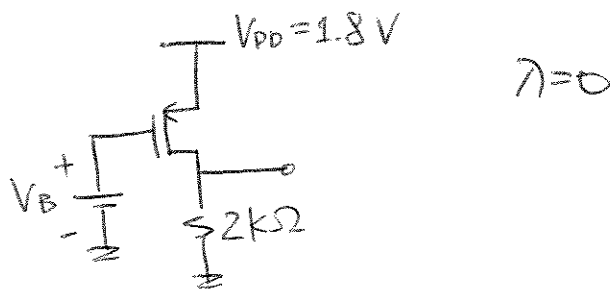

When  $V_B = 1V$ ,  $W/L = 87.5$

When  $V_B = 0.8V$ ,

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_{TH}|)^2$$

$$= \frac{1}{2} \left( \frac{100 \mu A}{V^2} \right) (87.5) (1 - 0.4)^2 V^2 \approx 16 \text{ mA}$$

$\Rightarrow V_D = I_D (2k\Omega) \approx 3.2V$ , which exceeds the supply voltage!

$\therefore$  PMOS goes into triode:  
 ( $\because I_D$  is too large)


By KCL,

$$\frac{1}{2} \mu_p C_{ox} \frac{W}{L} [(V_{SG} - |V_{TH}|) \cdot 2V_{SD} - V_{SD}^2] = (V_{DD} - V_{SD}) / 2k\Omega$$

Solving this equation numerically (or trial-and-error) gives  $V_{SD} \approx 0.18 \text{ V}$

$$\Rightarrow I_D = \frac{V_{DD} - V_{SD}}{2 \text{ k}\Omega} = \frac{(1.8 - 0.18) \text{ V}}{2 \text{ k}\Omega} \approx 0.81 \text{ mA}$$

43 (a)

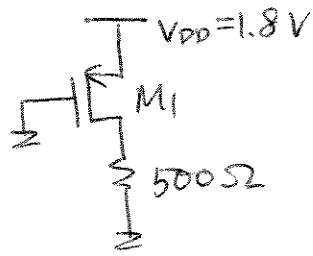

Assume  $M_1$  in triode (since  $V_{sg}$  is large). Note: if assumption is incorrect, results will show that.

By KCL,  $I_D = I_R$


$$\Rightarrow \frac{1}{2} \mu_p C_{ox} \frac{W}{L} \left[ (V_{sg} - |V_{TH}|) \cdot 2V_{SD} - V_{SD}^2 \right] = \frac{V_{DD} - V_{SD}}{500\ \Omega}$$

This is a quadratic relation on  $V_{SD}$ .  
Solving it yields  $V_{SD} \approx 0.42\text{ V}$

Verify assumption:  $V_{SD} \stackrel{?}{<} V_{sg} - |V_{TH}|$   
 $0.42 < 1.8 - 0.4 = 1.4\ (\checkmark)$
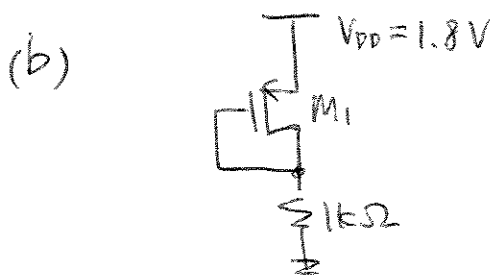
$$I_D = \frac{V_{DD} - V_{SD}}{500\ \Omega} = \frac{(1.8 - 0.42)\text{ V}}{500\ \Omega} \approx 2.8\text{ mA}$$





$$\frac{W}{L} = \frac{10}{0.18} \quad \lambda = 0$$


$$\mu_p C_{ox} = 100 \frac{\mu\text{A}}{\text{V}^2}$$

By KCL,

$$\frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_{TH}|)^2 = \frac{V_{DD} - V_{SG}}{1\text{k}\Omega}$$

Solving this quadratic equation gives  
 $V_{SG} \approx 0.61\text{V}$
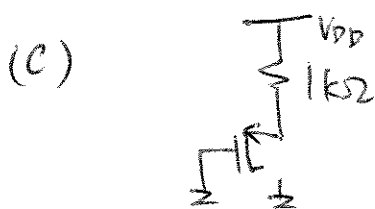
$$\Rightarrow I_D = \frac{V_{DD} - V_{SG}}{1\text{k}\Omega} = \frac{(1.8 - 0.61)\text{V}}{1\text{k}\Omega} \approx 1.2\text{mA}$$





By KCL,

$$\frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_{TH}|)^2 = \frac{V_{DD} - V_{SG}}{1\text{k}\Omega}$$



Solving this gives  $V_{SG} \approx 0.61\text{V}$

$$\Rightarrow I_D = \frac{V_{DD} - V_{SG}}{1\text{k}\Omega} \approx 1.2\text{mA}$$



44. (a)

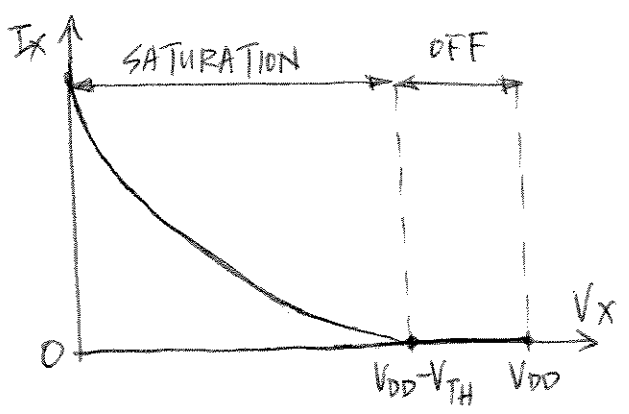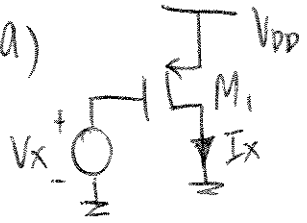



(b)

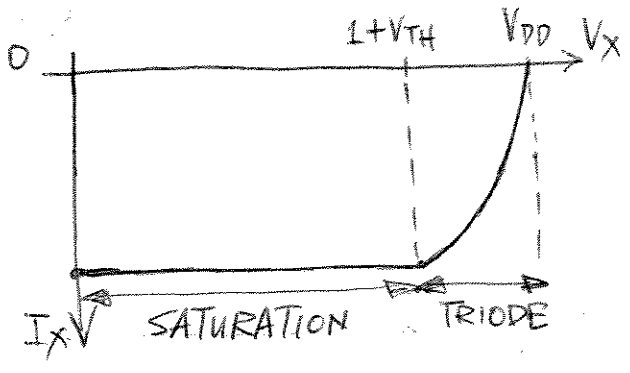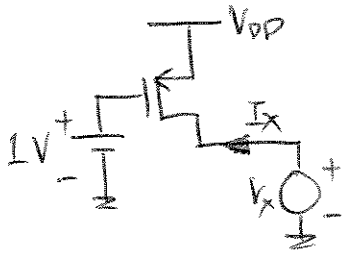



(c)

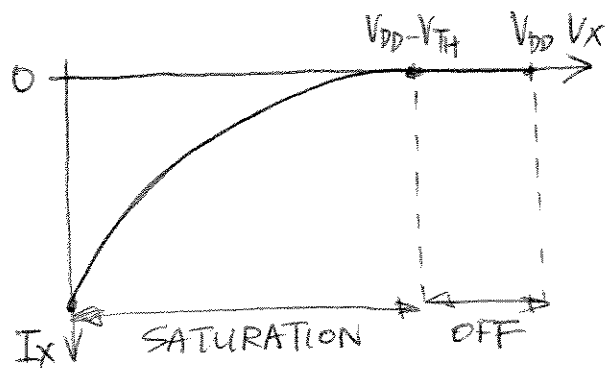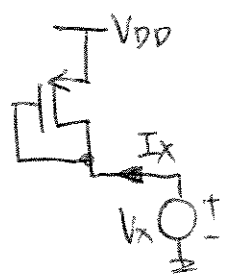



(d)

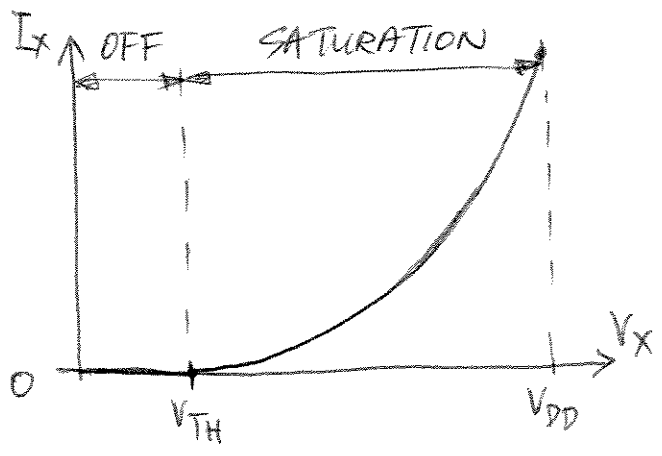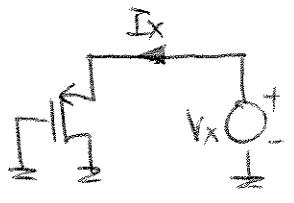



45. (a)

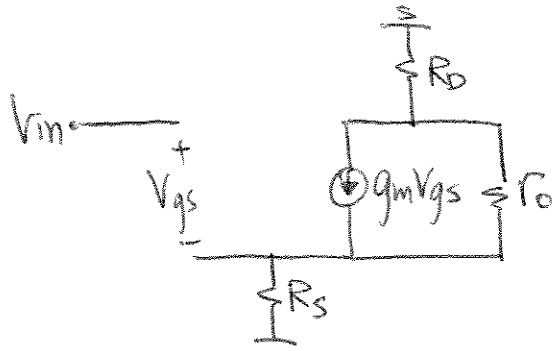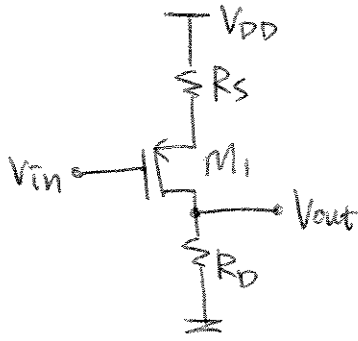



(b)

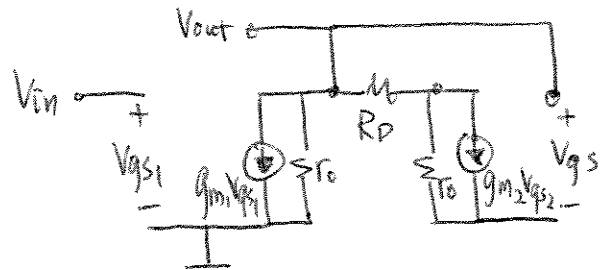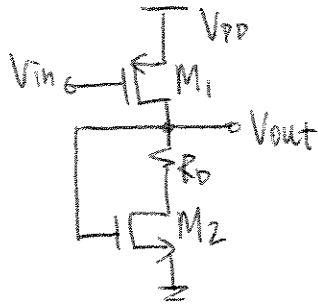



(c)

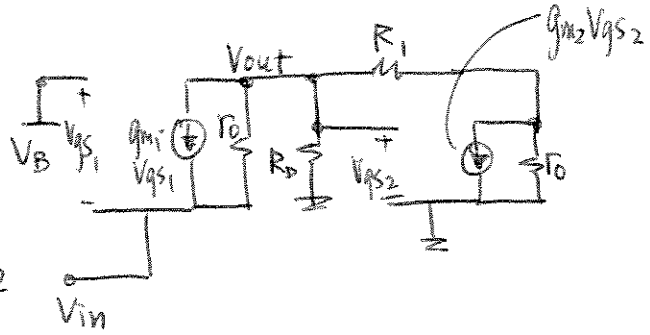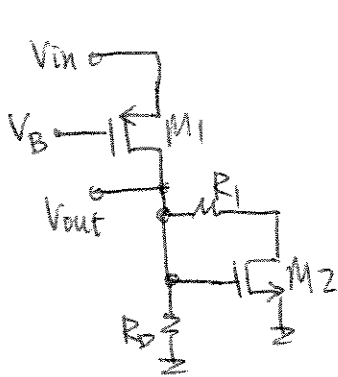


(d)

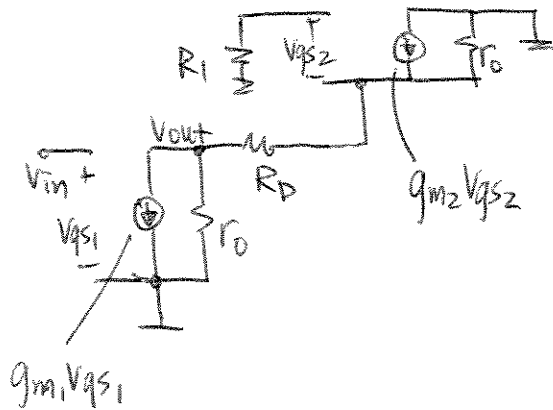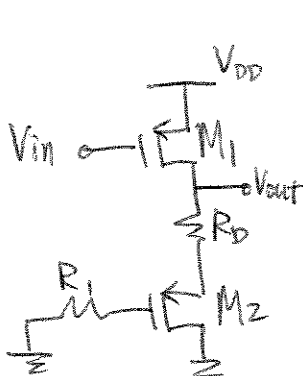

(e)

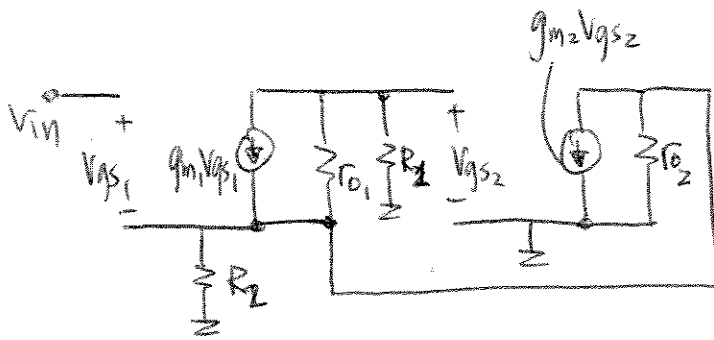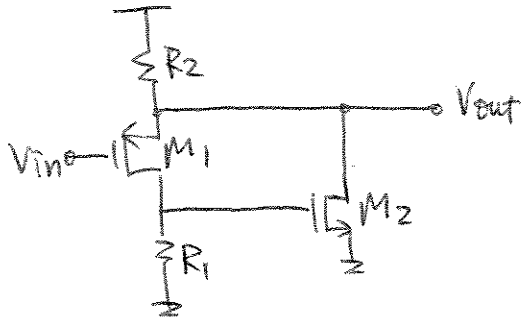


4b.

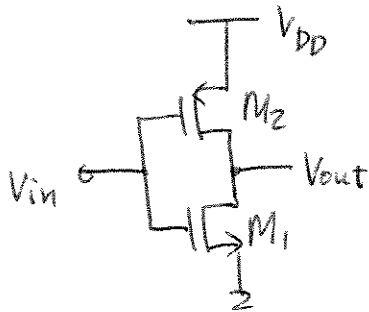


Assume  $\lambda_n$  &  $\lambda_p$ .

(a)

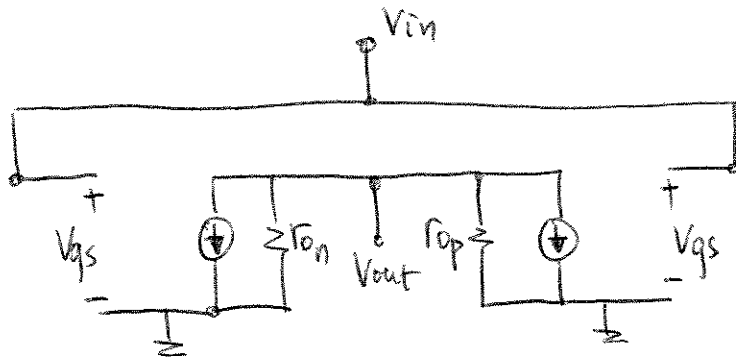

They are in "parallel" because from the small-signal model, both their respective SOURCE and DRAIN nodes are the same.

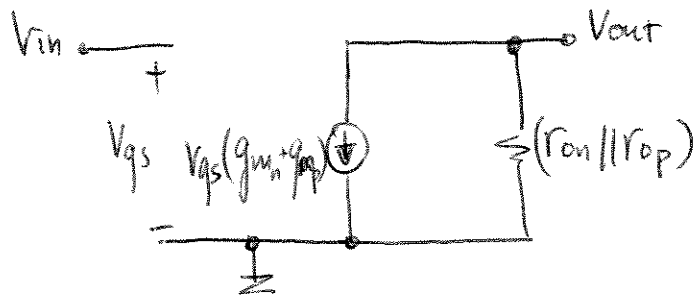(b) Assuming both  $M_1$  &  $M_2$  are in saturation, we can combine  $r_o$ 's &  $g_m$ 's :



$$\therefore \frac{V_{out}}{V_{in}} = -(g_{m_n} + g_{m_p})(r_{on} || r_{op})$$

① For  $M_1$  to stay in saturation,

$$V_{DS} > V_{GS} - V_{TH}$$

i.e.  $V_{DS} > V_{DD} - V_{TH}$

$$V_{DS} > 1.4$$

$$\therefore V_{DS} = V_{DD} - I_{DS} (R_L)$$

where  $R_L = 1 \text{ k}\Omega$ .

and 
$$I_{DS} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH})^2$$

$$= \frac{1}{2} \times 200 \times 10^{-6} \left(\frac{W}{L}\right)_1 (1.4)^2$$

$$\therefore V_{DS} = V_{DD} - 10^{-4} \left(\frac{W}{L}\right)_1 (1.96) \times 1000$$

i.e.  $1.8 - 1.96 \times 10^{-4} \left(\frac{W}{L}\right)_1 > 1.4$

$$\frac{0.4}{1.96 \times 10^{-1}} > \left(\frac{W}{L}\right)_1$$

Maximum allowable  $\left(\frac{W}{L}\right)_1$  is 2.

② To get  $I_{DS} = 1 \text{ mA}$ ,

$$\frac{1}{2} \mu C_{ox} \left(\frac{W}{L}\right)_n (V_{GS} - V_{TH})^2 = 1 \times 10^{-3} \text{ A.}$$

$$\frac{1}{2} (200 \times 10^{-6}) \left(\frac{20}{0.18}\right)_n (V_{GS} - V_{TH})^2 = 10^{-3}$$

$$(V_{GS} - V_{TH})^2 = 0.09$$

$$V_{GS} - V_{TH} = 0.3,$$

$$\text{i.e. } V_{GS} = 0.7.$$

Since  $V_{GS} = \frac{R_2}{R_1 + R_2} \times 1.8$

$$0.7 = \frac{R_2}{R_1 + R_2} \times 1.8$$

$$0.7 R_1 = R_2,$$

$$\therefore \frac{R_1}{R_2} = \frac{11}{7} \quad \text{————— ①}$$

To get input impedance  $\geq 20 \text{ k}$ .

$$R_1 \parallel R_2 \geq 20 \text{ k}\Omega. \quad \text{————— ②}$$

By inspection, setting  $R_1 = 55 \text{ k}\Omega$  and  $R_2 = 35 \text{ k}\Omega$  will satisfy both ① and ②.



$$\textcircled{3} \quad V_G = 1.8 \text{ V}$$

$$V_S = I_{DS} (100)$$

$$V_D = 1.8 - 1000 I_{DS}$$

For  $M_1$  to be in saturation,

$$V_{DS} \geq V_{GS} - V_{TH}$$

$$\therefore V_D - V_S \geq V_G - V_S - V_{TH}$$

$$V_D \geq V_G - V_{TH}$$

$$V_D \geq 1.4 \text{ V}$$

$$\therefore I_{DS, \max} = \frac{1.8 - 1.4}{1000} = 0.4 \text{ mA}$$

$$\text{and } \therefore V_S = (0.4 \times 10^{-3}) / (100)$$

$$= 0.004 \text{ V}$$

$$V_{GS} = 1.76 \text{ V}$$

$$f_{m, \max} = \frac{2 I_{DS, \max}}{(1.76 - 0.4)}$$

$$= 0.588 \text{ mS} //$$

$$\textcircled{4} \text{ a) } \therefore V_{RS} = 200 \text{ mV},$$

$$\therefore I_{DS} R_S = 200 \text{ mV}$$

$$I_{DS} = \frac{0.2}{100}$$

$$I_{DS} = 2 \text{ mA}.$$

For  $M_1$  to stay in saturation,

$$V_{DS} \geq V_{GS} - V_{TH}.$$

$$\begin{aligned} \therefore V_{DS} &= V_D - V_S \\ &= [1.8 - (2 \times 10^{-3}) \times 500] - 0.2 \\ &= 0.6, \end{aligned}$$

$$\therefore V_{GS} - V_{TH} \leq 0.6,$$

Since  $I_{DS} = \frac{1}{2} (M_n C_{ox}) \left(\frac{W}{L}\right) (V_{GS} - V_{TH})^2,$

$\left(\frac{W}{L}\right)$  is min. when  $(V_{GS} - V_{TH})$  is max,

$$\therefore \text{min. } \left(\frac{W}{L}\right), \text{ is when } (V_{GS} - V_{TH}) = 0.6 \text{ V},$$

$$2 \times 10^{-3} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{W}{L}\right) (0.6)^2$$

$$\therefore \text{min. } \left(\frac{W}{L}\right), \approx 56$$

b) With  $(V_{GS} - V_{TH}) = 0.6$ ,

$$V_{GS} = 1,$$

$$\therefore V_G = 1 + V_S$$

$$V_G = 1.2V,$$

$$\text{i.e. } 1.8x \frac{R_2}{R_1 + R_2} = 1.2V,$$

$$\frac{R_2}{R_1} = 2 \quad \text{--- ①}$$

$$\text{Input impedance} = R_2 // R_1,$$

$$\text{i.e. } R_2 // R_1 \geq 30k\Omega \quad \text{--- ②}$$

Set  $R_1 = 50k\Omega$  and  $R_2 = 100k\Omega$

will satisfy both ① & ②.

⑤.

$$\begin{aligned}V_S &= V_{RS} \\ &= I_{D1} (200) = 0.1 \text{ V}\end{aligned}$$

$$I_{DS} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH})^2$$

$$0.5 \text{ mA} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{20}{0.18}\right) (V_{GS} - V_{TH})^2$$

$$\therefore V_{GS} = 0.612 \text{ V}$$

$$\begin{aligned}\therefore V_G &= 0.612 + 0.1 \\ &= 0.712.\end{aligned}$$

$$\therefore V_G = V_{DD} - I_{R1} \times R_1$$

$$R_1 = \underline{\underline{21.76 \text{ k}\Omega}}$$

$$\text{and } V_{GS} = I_{R2} \times R_2$$

$$\therefore R_2 = \frac{0.712}{0.05 \times 10^{-3}}$$

$$= \underline{\underline{14.24 \text{ k}\Omega}}$$

⑥.

$$f_m = \sqrt{2\beta I_{DS}} = \frac{1}{100},$$

$$\therefore I_{DS} = 1\text{mA}, \quad \beta = 0.05,$$

$$\text{and } I_{DS} = \frac{1}{2} \beta (V_{GS} - V_{TH})^2,$$

$$\text{where } \beta = \mu_n C_{ox} \left(\frac{W}{L}\right),$$

$$\therefore 1\text{mA} = \frac{1}{2} (0.05) (V_{GS} - V_{TH})^2.$$

$$V_{GS} = 0.6.$$

$$\therefore V_{GS} = V_{DS} = V_{DD} - I_{DS} R_D,$$

$$0.6 = 1.8 - (0.5 \times 10^{-3}) R_D,$$

$$R_D = \underline{\underline{2.4 \text{ k}\Omega}}$$

(7)

$$I_{D_S} = \frac{1}{2} (\mu_n C_{ox}) \left(\frac{W}{L}\right) (V_{GS} - V_{TH})^2$$

$$0.5 \times 10^{-3} = (100 \times 10^{-6}) \left(\frac{50}{0.18}\right) (V_{GS} - V_{TH})^2$$

$$\therefore V_{GS} = 0.534 \text{ V}$$

$$\therefore R_2 = \frac{0.534}{0.05 \times 10^{-3}}$$

$$R_2 = \underline{\underline{10.68 \text{ k}\Omega}}$$

$$\therefore V_{D1} = 1.8 - (1.1 \times I_{D_S} \times 2 \text{ k}\Omega) = 0.1 I_{D_S} (R_1 + R_2),$$

$$\therefore 14 \text{ k}\Omega = R_1 + 10.68 \text{ k}\Omega.$$

$$\therefore R_1 = \underline{\underline{3320 \Omega}}$$

⑧ Without defect,

$$V_{GS} = V_{DS}, \quad (\text{i.e. } V_G = V_D)$$

$$\therefore \frac{20k}{10k+20k} \times 1.8 = 1.8 - I_{DS} (1k\Omega)$$

$$I_{DS} = 0.6 \text{ mA}$$

$$\begin{aligned} \therefore V_{GS} &= V_G - V_S \\ &= 1.2 - (0.6 \times 10^{-3}) (200) \\ &= 1.08 \end{aligned}$$

$$\text{and } 0.6 \text{ mA} = \frac{1}{2} (200 \times 10^{-6}) \left( \frac{W}{L} \right) (V_{GS} - 0.4)^2$$

$$\frac{W}{L} \approx 13 //$$

With  $R_P$

$$V_{GS} = V_{DS} + V_{TH}$$

$$1.2 = V_{DS} + 0.4$$


$$\therefore V_{DS} = 0.8 \text{ V}$$

$$\therefore V_{DS} = V_{DD} - V_{1k\Omega} - V_{200\Omega}$$

$$\begin{aligned} \therefore I_{D_1} + I_{R_P} &= \frac{1 \text{ V}}{1k\Omega + 200\Omega} \\ &= 0.833 \text{ mA} \end{aligned}$$

$$\therefore I_{R_P} = \frac{V_{DS}}{R_P} = \frac{0.8}{R_P}$$
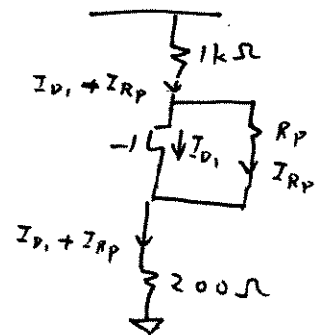
$$\text{and } I_{D_1} = 0.6 \text{ mA} \quad (\text{from above})$$



$$\therefore \frac{0.8V}{R_p} + 0.6 \text{ mA} = 0.833 \text{ mA}$$

$$R_p \approx 3430 \Omega //$$



⑨ With out defects,

$$V_{GS} = 1.8V,$$

$$\text{i.e. } V_{DS} = (1.8 - 0.1)V$$

$$= 1.7V$$

$$I_{DS} = \frac{(1.8 - 1.7)V}{2000 \Omega} = 0.05 \text{ mA.}$$

$$\therefore 0.05 \text{ mA} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{W}{L}\right) (1.8 - 0.4)^2$$

$$\therefore \left(\frac{W}{L}\right) = 0.255 //$$

b) With defects,

$$V_{GS} = V_{DS} + 50 \text{ mV}$$

$$\therefore V_{RP} = 50 \text{ mV}$$

$$I_{RP} = \frac{50 \text{ mV}}{R_P}$$

$$V_{GS} = 1.8V - \frac{0.05V}{R_P} \times 30 \text{ k}\Omega \quad \text{--- (1)}$$

$$\therefore V_{DD} - \left(I_{DS} - \frac{50 \text{ mV}}{R_P}\right) 2 \text{ k}\Omega = V_{DS}$$

$$V_{DD} - \left(I_{DS} - \frac{50 \text{ mV}}{R_P}\right) 2 \text{ k}\Omega = \underline{V_{GS} - 50 \text{ mV}} \quad \text{--- (2)}$$

$$\begin{aligned}
 \therefore I_{DS} &= \frac{1}{2} \left( \frac{W}{L} \right) (M_n C_{ox}) (V_{GS} - V_{TH})^2 \\
 &= \frac{1}{2} (0.255) (200 \times 10^{-6}) (V_{GS} - 0.4)^2 \\
 &= 2.55 \times 10^{-5} (V_{GS} - 0.4)^2
 \end{aligned}$$

\(\therefore\) From ②,

$$\begin{aligned}
 1.8 - \left[ 2.55 \times 10^{-5} (V_{GS} - 0.4)^2 - \frac{0.2}{R_P} \right] 2000 \\
 = V_{GS} - 0.05.
 \end{aligned}$$

From ①,

$$\frac{0.05}{R_P} = \frac{1.8 - V_{GS}}{30000}$$

$$\therefore 1.8 - \left[ 0.051 (V_{GS} - 0.4)^2 - \frac{1.8 - V_{GS}}{15} \right] = V_{GS} - 0.3$$

$$1.85 - 0.051 V_{GS}^2 + 0.0408 V_{GS} - 0.00816 + \frac{1.8 - V_{GS}}{15} = V_{GS}$$

$$29.4276 - 15.388 V_{GS} - 0.765 V_{GS}^2 = 0$$

$$\therefore V_{GS} = 1.76 \text{ V} //$$

$$R_P = \frac{0.05 \times 30000}{1.8 - 1.76}$$

$$\approx 36.3 \text{ k}\Omega$$

(10) For  $M_1$ ,

$$I_x = \frac{1}{2} (200 \times 100^{-6}) \left( \frac{W_1}{0.25} \right) (0.8 - 0.4)^2 \times (1 + 0.1(0.8))$$

$$10^{-3} = 0.16 \times 10^{-4} \left( \frac{W_1}{0.25} \right) (1.08)$$

$$\therefore W_1 = 14.5 \mu \text{m} //$$

For  $M_2$ ,

$$0.5 \times 10^{-3} = 0.16 \times 10^{-4} \left( \frac{W_2}{0.25} \right) (1.08)$$

$$\therefore W_2 = 7.25 \mu \text{m} //$$

Output resistance =  $r_o$

$$= \frac{1}{\lambda} \times \frac{1}{I_D}$$

$$\therefore r_{o1} = \left( \frac{1}{0.1} \right) \left( \frac{1}{10^{-3}} \right)$$

$$= 10 \text{ k}\Omega //$$

$$r_{o2} = \left( \frac{1}{0.1} \right) \left( \frac{1}{0.5 \times 10^{-3}} \right)$$

$$= 20 \text{ k}\Omega //$$

(11)

$$R_{out} = \frac{1}{\eta} \left( \frac{1}{I_D} \right)$$
$$= \frac{1}{0.5 \times 10^{-3} \eta} = 20 \text{ k}\Omega$$

$$\therefore \eta = 0.1 \text{ V}^{-1}$$

(12) For  $M_1$ ,  $\mu = 0.1$

$$0.5 \times 10^{-3} = \frac{1}{2} (200 \times 10^{-6}) \left( \frac{W_1}{0.25} \right) (1 - 0.4)^2$$

$$W_1 \approx 3.47 \text{ mm}$$

For  $M_2$ ,

$$0.5 \times 10^{-3} = \frac{1}{2} (200 \times 10^{-6}) \left( \frac{W_2}{0.25} \right) (1.2 - 0.4)^2$$

$$W_2 \approx 1.95 \text{ mm}$$

$$\frac{r_{o1}}{r_{o2}} = \frac{\frac{1}{\lambda I_x}}{\frac{1}{\lambda I_y}}$$

$$= 1 \quad (\because I_x = I_y)$$

$$\therefore r_{o1} = r_{o2}$$

⑬ Impedance at source of  $M_1$ ,  $Z_s = \frac{1}{f_{mp}}$

$$\begin{aligned} f_{mp} &= \sqrt{2 \mu_p C_{ox} \left(\frac{W}{L}\right) I_D (1 + \lambda) V_{DS}} \\ &= \sqrt{2 \times 100 \times 10^{-6} \left(\frac{10}{0.25}\right) (1 + 0.1 \times 1.2) I_D} \\ &= \sqrt{0.0896 I_D} \end{aligned}$$

$$\begin{aligned} I_D &= \frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{10}{0.25}\right) (V_{B1} - V_x + 0.4)^2 \\ &\quad \times (1 + 0.1 \times 1.2) \\ &\approx 0.806 \text{ mA} \end{aligned}$$

$$\begin{aligned} \therefore f_{mp} &= \sqrt{0.0896 \times 0.806 \times 10^{-3}} \\ &\approx 8.50 \text{ mS} \end{aligned}$$

$$\therefore Z_s \approx 118 \Omega //$$

14

$$I_x = \frac{1}{2} (100 \times 10^{-6}) \left( \frac{20}{0.25} \right) (1 - 1.8 + 0.4)^2$$

$$= 0.64 \text{ mA} //$$

$$I_y = \frac{1}{2} (100 \times 10^{-6}) \left( 2 \times \frac{20}{0.25} \right) (1 - 1.8 + 0.4)^2$$

$$= 1.28 \text{ mA} //$$

$$\therefore r_o \propto \frac{1}{I}$$

and  $I_y = 2 I_x$

$$\therefore r_{out, m_1} = 2 r_{out, m_2} //$$

$$\textcircled{15} \quad |I_{D S 1}| = |I_{D S 2}|,$$

$$\begin{aligned} \frac{1}{2} (200 \times 10^{-6}) \left( \frac{10}{0.18} \right) (V_B - 0.4)^2 (1 + 0.1 \times 0.9) \\ = \frac{1}{2} (100 \times 10^{-6}) (1.8 - V_B - 0.4)^2 (1 + 0.1 \times 0.9) \\ \times \left( \frac{30}{0.18} \right) \end{aligned}$$

$$2 (V_B - 0.4)^2 = 3 (1.4 - V_B)^2$$

$$\sqrt{\frac{2}{3}} (V_B - 0.4) = (1.4 - V_B)$$

$$1.816 V_B = 1.7264$$

$$V_B = 0.95 //$$



⑩ a) For  $M_1$ ,

$$I_{D1} = \frac{1}{2} (200 \times 10^{-6}) \left( \frac{5}{0.18} \right) (V_B - 0.4)^2$$

$$(1 + 0.1 \times 0.9)$$

$$\therefore V_B \approx 0.806 \text{ V}$$

b) There are 3 regions of operation:


For  $V_x < V_B - V_{TH1}$ ,  $M_1$  is in triode.  
and  $|I_{DS2}| > |I_{DS1}|$

For  $|V_x - V_{DD}| > |V_B - V_{DD} - V_{TH2}|$ ,  $M_2$  is in triode  
and  $I_{DS1} > |I_{DS2}|$

For  $V_B - V_{TH1} < V_x$  and  $|V_x - V_{DD}| < |V_B - V_{DD} - V_{TH2}|$   
 $M_1$  and  $M_2$  are in saturation.

and  $I_{DS1} = |I_{DS2}| = 0.5 \text{ mA}$  at  $V_x = 0.9 \text{ V}$

In all cases,  $I_x = I_{DS1} - |I_{DS2}|$

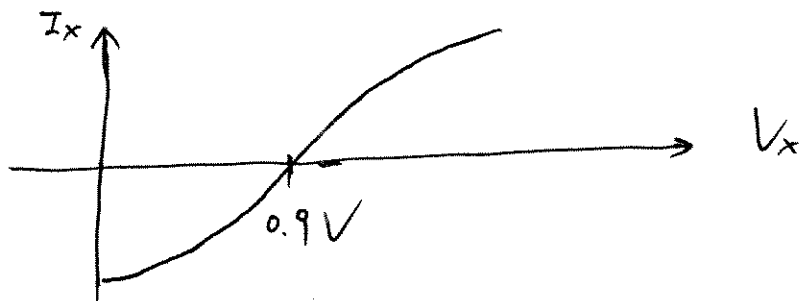

$$\textcircled{17} \quad a) \quad 0.5 \times 10^{-3} = \frac{1}{2} (200 \times 10^{-6}) \left( \frac{30}{0.18} \right) (V_{GS} - V_{TH})^2$$

$$\therefore V_{GS} = 0.573 \text{ V} //$$

$$V_{DS} = 1.8 - 0.5 \times 10^{-3} \times 2000 \\ = 0.8.$$

$$\therefore V_{DS} > V_{GS} - V_{TH},$$

$M_1$  is in saturation.

$$b) \quad \therefore \lambda = 0, \quad r_o = \infty.$$

$$\therefore A_v = g_m R_D$$

$$= \sqrt{2 \times (200 \times 10^{-6}) \times \frac{30}{0.18} \times 0.5 \text{ mA}} \times 2000$$

$$= 11.55 //$$

18

$$a) \quad 0.25 \times 10^{-3} = \frac{1}{2} \times (200 \times 10^{-6}) \left( \frac{20}{0.18} \right) (V_{GS} - 0.4)^2$$

$$\therefore V_{GS} = 0.55 //$$

$$b) \quad V_{DS, \min} = V_{GS} - V_{TH} \\ = 0.15 \text{ V.}$$

$$\text{with } V_{DS} = 0.15 \text{ V,}$$

$$I_{DS, \max} = \frac{1.8 - 0.15}{2000} \\ = 0.825 \text{ mA.}$$

$$\therefore \frac{0.825 \times 10^{-3}}{0.25 \times 10^{-3}} = \frac{\left(\frac{W}{L}\right)'}{\left(\frac{W}{L}\right)},$$

where  $\left(\frac{W}{L}\right)'$  is the new  $\left(\frac{W}{L}\right)$ .

$\therefore \left(\frac{W}{L}\right)$  can be increased by 3.3 times.

$$\therefore A_v \propto I_m \\ \propto \sqrt{\beta I}$$

$\therefore A_v$  is also increased by 3.3 times.

(since both  $\beta$  &  $I$  increase by 3.3 times)

$$(19) \text{ Voltage gain } (A_v) = 5,$$

$$\text{i.e. } f_m R_D = 5.$$

$$\text{Power } (P) = I_{DS} \times V_{DD},$$

$$\therefore P \leq 1 \text{ mW},$$

$$I_{DS} \times 1.8 \leq 1 \text{ mW}.$$

$$I_{DS} \leq 0.556 \text{ mA}.$$

$$f_m = \sqrt{2 \beta I_{DS}}$$

$$\therefore f_{m, \max} = \sqrt{2 \times 200 \times 10^{-6} \times \left(\frac{20}{0.18}\right) \times 0.556 \text{ mA}}$$

$$= 0.00497 \text{ s}^{-1}$$

$$\therefore R_D = \frac{5}{0.00497}$$

$$\approx 1006 \text{ } \Omega$$

$\therefore$  This is minimum value required for  $R_D$ .

20

$$|A_v| = f_{m,} (r_{o1} \parallel r_{o2}) = 10,$$

$$r_{o1} = \frac{1}{\lambda_1 I_1} = \frac{1}{0.1 \times 0.5 \times 10^{-3}}$$

$$= 20 \text{ k}\Omega.$$

$$r_{o2} = \frac{1}{\lambda_2 I_1} = \frac{1}{0.15 \times 0.5 \times 10^{-3}}$$

$$= 13.3 \text{ k}\Omega.$$

$$\therefore f_{m,} = \frac{10}{20 \text{ k} \parallel 13.3 \text{ k}}$$

$$= 0.00138 \Omega^{-1}$$

$$\therefore f_{m,} = \sqrt{2 \beta_1 I_{D5}}$$

$$\beta_1 = 0.00192$$

$$200 \times 10^{-6} \left(\frac{W}{L}\right)_1 = 0.00192$$

$$\therefore \left(\frac{W}{L}\right)_1 = 9.6 //$$

b)

$$0.5 \times 10^{-3} = \frac{1}{2} (100 \times 10^{-6}) (1.8 - V_B - 0.4)^2 \left(\frac{20}{0.18}\right)$$

$$\therefore V_B = 1.1 \text{ V} //$$

(21)

$$|A_v| = g_{m1} (r_{o1} \parallel r_{o2})$$

$$g_{m1} = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{20}{0.18}\right) \times (0.001)}$$

(Since  $V_{ds1}$  is not given, assume  
(if  $\lambda_1 V_{ds1}$ ) has minimal effect on  $g_{m1}$ )

$$= 6.67 \text{ mS.} \quad (S = \Omega^{-1})$$

$$\begin{aligned} r_{o1} &= \frac{1}{\lambda_1 \times I_{D1}} \\ &= \frac{1}{0.1 \times 1 \text{ mA}} \\ &= 10 \text{ k}\Omega. \end{aligned}$$

$$r_{o2} = \infty$$

$$(\because \lambda_2 \ll \lambda_1)$$

$$\therefore |A_v| = 6.67 \times 10^{-3} \times 10^3 \times 10$$

$$= 66.7 //$$

$$(22) a) A_v = \beta_{m_1} (r_{o1} \parallel r_{o2})$$

When length of  $M_1$  and  $M_2$  double,  
 $r_o$  doubles ( $\because r_o \propto \frac{1}{L} \propto L$ )

$$r_{o1} \parallel r_{o2} = \frac{r_{o1} r_{o2}}{r_{o1} + r_{o2}}$$

$$\therefore (r_{o1} \parallel r_{o2}) \propto \frac{L^2}{L},$$

$$\text{i.e. } (r_{o1} \parallel r_{o2}) \propto L.$$

$\beta_{m_1}$  is constant because both  
 $(\frac{W}{L})_{1,2}$  and  $I_{D_3}$  are constant.

$\therefore$  Voltage gain is doubled.

b) When both length and bias current double,  
 $r_o$  remains the same.

$$\therefore \beta_{m_1} \propto \sqrt{I_{D_3}}$$

$\therefore$  Voltage gain increased by  $\sqrt{2}$ .

(23). To get higher voltage gain,

(a) is preferred.

For the same dimensions of transistors  
and same bias current,

(a) has a high " $g_m$ " than (b).

$$\therefore g_{m1} > g_{m2}$$

(since  $\mu_n C_{ox} > \mu_p C_{ox}$ )

while  $(R_{o1} \parallel R_{o2})$  is the same  
for both cases.



(24)

$$A_v = f_{m_2} (r_{o1} // r_{o2})$$

$$r_{o1} = \frac{1}{0.15 \times 0.5 \text{ mA}}$$

$$= 13.3 \text{ k}\Omega$$

$$r_{o2} = \frac{1}{0.05 \times 0.5 \text{ mA}}$$

$$= 40 \text{ k}\Omega$$

$$\therefore r_{o1} // r_{o2} = 10 \text{ k}\Omega$$

$$\therefore 15 = \left[ \sqrt{2 \times (100 \times 10^{-6}) \left( \frac{W}{L} \right)_2 \cdot 0.5 \text{ mA}} \right] \cdot (10 \text{ k}\Omega)$$

$$\left( \frac{W}{L} \right)_2 = 22.5 //$$

(25) From Eq (7.57),

$$3 = \sqrt{\frac{20/0.18}{(w/L)_2}}$$

$$\therefore (w/L)_2 \approx 12.3//.$$

26

a) For  $M_1$ ,

$$0.5 \times 10^{-3} = \frac{1}{2} (200 \times 10^{-6}) \left( \frac{10}{0.18} \right) (V_{GS1} - 0.4)^2$$

$$\therefore V_{GS1} = 0.7 \text{ V}$$

$$\begin{aligned} \therefore V_{DS1, \min} &= V_{GS1} - V_{TH} \\ &= 0.3 \text{ V} \end{aligned}$$

For  $M_2$ ,

$$\begin{aligned} V_{S, \min} &= V_{DS1, \min} \\ &= 0.3 \text{ V} \end{aligned}$$

$$\begin{aligned} V_{GS, \max} &= 1.8 - 0.3 \\ &= 1.5 \text{ V} \end{aligned}$$

$$\begin{aligned} \therefore I_{OS2} &= \frac{1}{2} (200 \times 10^{-6}) \left( \frac{L}{L} \right)_2 (1.5 - 0.4)^2 \\ &= 0.5 \text{ mA} \end{aligned}$$

$$\left( \frac{W}{L} \right)_2 = 4.13 //$$

$$\begin{aligned} \text{b) volt. gain} &= - \sqrt{\frac{(W/L)_1}{(W/L)_2}} \\ &\approx \underline{\underline{3.67}} \end{aligned}$$

c) Because with  $M_1$  at the edge of saturation,  $V_{GS}$  of  $M_2$  is at a maximum ( $V_S$  of  $M_2$  is at a minimum). Thus, a minimum ( $W/L$ ) is required to set up the same bias current. With minimum ( $W/L$ ),  $I_{M_2}$  is at a minimum. Since  $A_v \propto \frac{1}{I_{M_2}}$ ,  $A_v$  is at a maximum.

$$(27) \quad a) \quad A_v = \sqrt{\frac{(w/L)_1}{(w/L)_2}}$$

$$0.5 = \sqrt{\frac{(w/L)_1}{(2/0.18)}}$$

$$\therefore (w/L)_1 \approx 277.8 //$$

b) For  $M_2$ ,

$$I_{D_{S2}} = \frac{1}{2} (200 \times 10^{-6}) \left( \frac{2}{0.18} \right) (1.8 - V_{S2} - 0.4)^2$$

$$I_{D_{S2}} = (0.00111) (1.4 - V_{S2})^2$$

$$\therefore V_{S2} = \quad I_{D_{S2}} = (0.00111) (1.4 - V_{D_{S1}})^2$$

For  $M_1$ ,

$$I_{D_{S1}} = \frac{1}{2} (200 \times 10^{-6}) (277.8) (V_{G_{S1}} - 0.4)^2$$

$$= 0.02778 (V_{G_{S1}} - 0.4)^2$$

$$\therefore I_{D_{S1}} = I_{D_{S2}}$$

$$\therefore (0.02778) (V_{G_{S1}} - 0.4)^2 = (0.00111) (1.4 - V_{D_{S1}})^2$$

$$5 (V_{G_{S1}} - 0.4) = (1.4 - V_{D_{S1}})$$

At edge of saturation,

$$V_{DS1} = V_{GS1} - 0.4,$$

$$\text{Let } m = V_{DS1} = V_{GS1} - 0.4.$$

$$\therefore 5m = 1.4 - m$$

$$m = 0.233$$


$$\begin{aligned} \therefore I_{DS1} &= 0.02778 (V_{GS1} - 0.4)^2 \\ &= I_{Bias}. \end{aligned}$$

$$\begin{aligned} \therefore I_{Bias} &= 0.02778 (0.233)^2 \\ &= 6.48 \text{ mA} // \end{aligned}$$

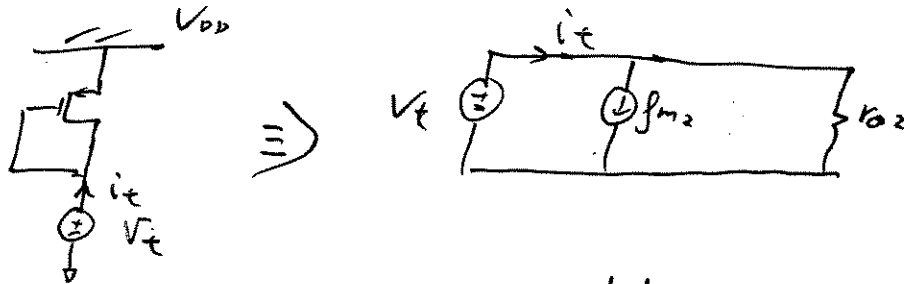(28) a)  $A_v = -g_{m1} r_{o1} \parallel Z_2,$

where  $Z_2$  is the impedance presented by  $M_2$ .

To find  $Z_2$ , apply a test voltage ( $V_t$ ) at the drain of  $M_2$ :



From the small-signal model,

$$i_t = g_{m2} V_t + \frac{V_t}{r_{o2}}$$

$$Z_2 = \frac{V_t}{i_t} = r_{o2} \parallel \frac{1}{g_{m2}}$$

$$\therefore A_v = -g_{m1} (r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}})$$

b)  $A_v = -g_{m1} (r_{o1} \parallel Z_2 \parallel Z_3)$

where  $Z_2$  and  $Z_3$  are impedances presented by  $M_2$  and  $M_3$  respectively.

From (a)  $Z_3 = r_{o3} \parallel \frac{1}{g_{m3}}$

By inspection,  $Z_2 = r_{o2}$

$$\therefore A_v = -g_{m1} (r_{o1} \parallel r_{o2} \parallel r_{o3} \parallel \frac{1}{g_{m3}})$$

$$c) \quad A_v = -\beta_{m1} r_{o1} \parallel Z_2 \parallel Z_3$$

Similar to (b),

$$Z_2 = r_{o2},$$

$$\text{and } Z_3 = r_{o3} \parallel \frac{1}{\beta_{m3}}$$

(the small signal model of  $M_3$  in this case is equivalent to that of  $M_2$  in (a))

$$\therefore A_v = -\beta_{m1} (r_{o1} \parallel r_{o2} \parallel r_{o3} \parallel \frac{1}{\beta_{m3}})$$

d).  $M_2$  is in CS arrangement. (similar to (c))

$$A_v = \beta_{m2} r_{o2} \parallel Z_1 \parallel Z_3$$

$$Z_3 = \frac{1}{\beta_{m3}} \parallel r_{o3}$$

$$Z_1 = r_{o1}$$

$$\therefore A_v = \beta_{m2} (r_{o2} \parallel r_{o1} \parallel \frac{1}{\beta_{m3}} \parallel r_{o3})$$

$$e). \quad A_v = \beta_{m2} (r_{o2} \parallel Z_1 \parallel Z_3)$$

$$Z_1 = r_{o1}$$

$$Z_3 = \frac{1}{\beta_{m3}} \parallel r_{o3}$$


(recall: impedance looking into source =  $\frac{1}{\beta_{m3}}$ )

$$\therefore A_v = \beta_{m2} (r_{o2} \parallel r_{o1} \parallel \frac{1}{\beta_{m3}} \parallel r_{o3})$$




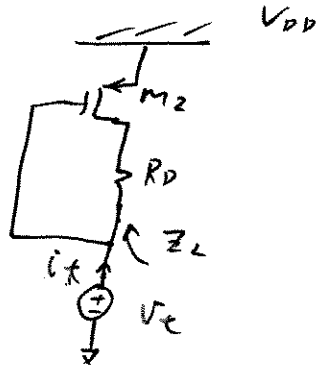(28) f)  $A_v = -\beta m_1 (r_{o1} \parallel Z_L)$

where  $Z_L$  is the impedance depicted as follows:



The equivalent small-signal model is:

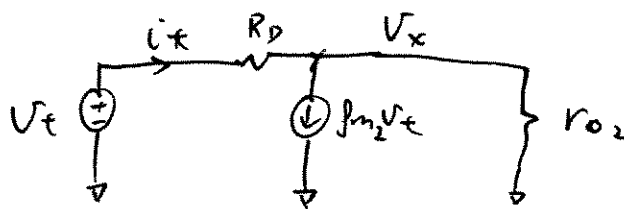

$$i_t = \beta m_2 V_t + \frac{V_x}{r_{o2}}$$

$$V_x = V_t - R_D i_t$$

$$\therefore i_t = \beta m_2 V_t + \frac{V_t - R_D i_t}{r_{o2}}$$

$$i_t \left( 1 + \frac{R_D}{r_{o2}} \right) = V_t \left( \beta m_2 + \frac{1}{r_{o2}} \right)$$

$$\frac{V_t}{i_t} = \frac{r_{o2} + R_D}{\beta m_2 r_{o2} + 1}$$

$$\therefore A_v = -\beta m_1 \left( r_{o1} \parallel \frac{r_{o2} + R_D}{1 + \beta m_2 r_{o2}} \right)$$

30 a) From Eq. (7.67)

$$|A_v| = \frac{R_D}{\frac{1}{g_m} + R_S}$$

$$4 = \frac{1000}{\frac{1}{g_m} + \frac{0.2V}{1mA}}$$

$$\frac{4}{g_m} + 800 = 1000$$

$$\therefore g_m = 20 \text{ mS.}$$

$$\therefore 20 \times 10^{-3} = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L}\right) (1 \times 10^{-3})}$$

$$\therefore \frac{W}{L} = 1000 //$$

To check if  $M_1$  is in saturation:

$$\begin{aligned} V_{DS} &= V_D - V_S \\ &= [1.8 - (10^{-3} \times 1k)] - 0.2 \\ &= 0.6 \text{ V} \end{aligned}$$

$$\text{and } 10^{-3} = \frac{1}{2} (200 \times 10^{-6}) (1000) (V_{GS} - 0.4)^2$$

$$V_{GS} = 0.5$$

$$\therefore V_{DS} > V_{GS} - V_t$$

ie. transistor is in operation.

$$b) \quad f_m = \sqrt{2 \times (200 \times 10^{-6}) \times \left(\frac{50}{0.18}\right) \times 10^{-3}}$$

$$\approx 10.5 \text{ mS}$$

$$|A_v| = \frac{R_D}{\frac{1}{f_m} + R_S}$$

$$4 = \frac{R_D}{\frac{1}{10.5 \times 10^{-3}} + 200}$$

$$\therefore R_D \approx 1179 \Omega$$

To check if  $M_1$  is in saturation:

$$V_{DS} = [1.8 - (1179 \times 10^{-3})] - 0.2$$

$$= 0.421$$

$$\text{and } 10^{-3} = \frac{1}{2} (V_{GS} - 0.4)^2 (200 \times 10^{-6}) \left(\frac{50}{0.18}\right)$$


$$V_{GS} \approx 0.590$$

$$\therefore V_{DS} > V_{GS} - V_{th}$$

Transistor is in saturation.

(31)

The small signal model is:

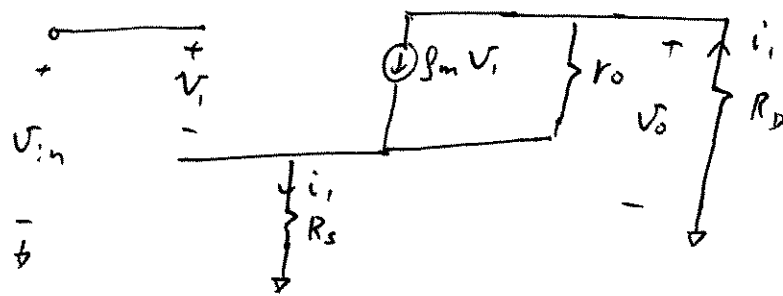

$$v_o = -i_i R_D \quad \text{--- (1)}$$

$$\begin{aligned} i_i &= g_m v_i + \frac{v_o - v_i}{r_o} \\ &= \frac{(g_m r_o - 1) v_i + v_o}{r_o} \end{aligned}$$

$$i_i \approx g_m v_i + \frac{v_o}{r_o}$$

$$-\frac{v_o}{R_D} = g_m v_i + \frac{v_o}{r_o} \quad \text{--- (2)}$$

$$v_{in} = v_i + i_i R_S$$

$$\therefore v_i = v_{in} + \frac{v_o}{R_D} R_S \quad \text{--- (3)}$$

(2) combined with (3):


$$-\frac{v_o}{R_D} = g_m v_{in} + g_m v_o \frac{R_S}{R_D} + \frac{v_o}{r_o}$$

$$-v_o \left[ \frac{1}{R_D} + g_m \frac{R_S}{R_D} + \frac{1}{r_o} \right] = g_m v_{in}$$

$$\therefore \text{Volt. gain} = \frac{v_o}{v_{in}} = - \left[ \frac{g_m}{r_o + g_m R_S + \frac{1}{R_D}} \right] (r_o R_D) //$$

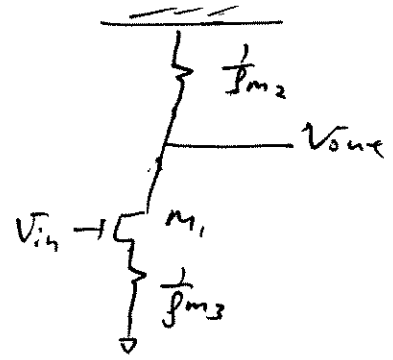32. a) Equivalent circuit is:

$$\therefore A_v = - \frac{\frac{1}{\beta m_2}}{\frac{1}{\beta m_1} + \frac{1}{\beta m_3}}$$




b) Similar to Prob. 28 (f),

Equivalent circuit is:

From Prob. 28 (f),


$$Z_L = \frac{1}{\beta m_2} \quad (\text{as } r_{o2} \rightarrow \infty)$$
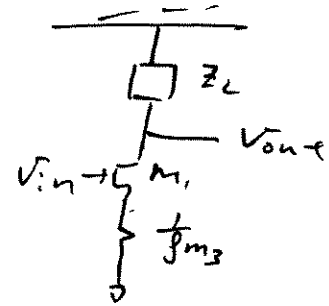
$$\therefore A_v = - \frac{\frac{1}{\beta m_2}}{\frac{1}{\beta m_1} + \frac{1}{\beta m_3}}$$



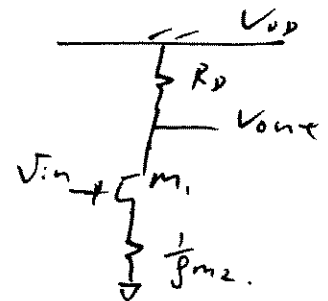
c) Equivalent circuit is:

$$\therefore A_v = - \frac{R_D}{\frac{1}{\beta m_1} + \frac{1}{\beta m_2}}$$



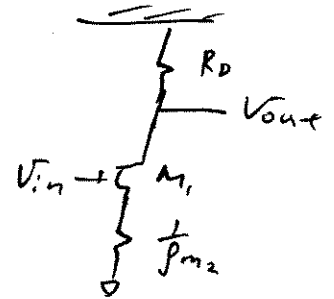
(d) Equivalent circuit is

$$A_V = - \frac{R_D}{\frac{1}{\beta_{m1}} + \frac{1}{\beta_{m2}}}$$



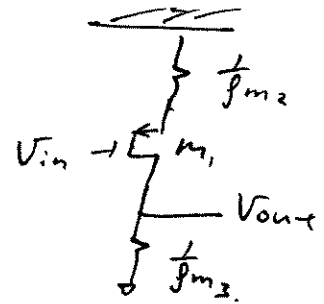(e) Equivalent circuit is

$$A_V = \frac{\frac{1}{\beta_{m3}}}{\frac{1}{\beta_{m1}} + \frac{1}{\beta_{m2}}}$$



33

a) From Eq. (7.71),

$$R_{out} = (1 + \beta_{m1} r_{o1}) \left( \frac{1}{\beta_{m2}} + r_{o1} \right) //$$

b) From Eq. (7.71),

$$R_{out} = (1 + \beta_{m1} r_{o1}) \left( \frac{1}{\beta_{m2}} + r_{o1} \right) //$$

c) From Eq. (7.71),

$$R_{out} = (1 + \beta_{m2} r_{o2}) \left( r_{o1} // \frac{1}{\beta_{m3}} \right) + r_{o2} //$$

d) From Eq. (7.71),

$$R_{out} = (1 + \beta_{m1} r_{o1}) \left( r_{o2} // \frac{1}{\beta_{m3}} \right) + r_{o1} //$$

34. To find  $\left(\frac{W}{L}\right)$

$$10^{-3} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{W}{L}\right) (1 - 0.4)^2 \times (1 + 0.1 V_{DS})$$

$$\text{Where } V_{DS} = 1.8 - 1 \text{ k}\Omega \times 1 \text{ mA} \\ = 0.8 \text{ V}$$

$$\therefore \left(\frac{W}{L}\right) \approx 25.7 //$$

$$\text{Voltage gain, } (A_V) = -f_{m_i} (r_{o_i} // R_D)$$

$$f_{m_i} = \sqrt{2(200 \times 10^{-6}) / (25.7) \times 10^{-3} \times (1 + 0.1 \times 0.8)} \\ = 3.33 \text{ mS}$$

$$r_{o_i} = \frac{1}{0.1 \times 10^{-3}} \\ = 10 \text{ k}\Omega$$

$$\therefore A_V = (-3.33 \times 10^{-3}) / (10 \text{ k}\Omega // 1 \text{ k}\Omega) \\ = -3.03 //$$



(35) With  $\lambda = 0$ ,

$$10^{-3} = \frac{1}{2} (200 \times 10^{-6}) \left( \frac{V}{L} \right) (1 - 0.4)^2$$

$$\therefore \left( \frac{V}{L} \right) \approx 27.8 //$$


$$A_V = -g_m R_D$$

$$= -\sqrt{2(200 \times 10^{-6})(27.8) \times 10^{-3}} \times 1000$$

$$= -3.33 //$$

Without  $r_o$ , gain increases due mainly to increase in load resistance.

36 The small-signal circuit is:

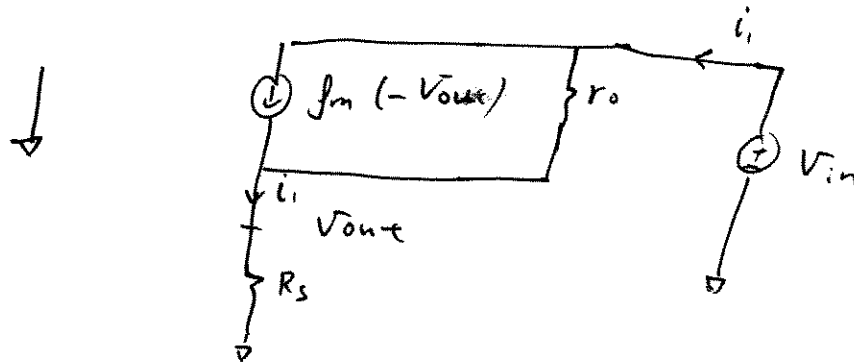

$$i_i = \frac{V_{out}}{R_s} \quad \text{--- (1)}$$

$$i_i = g_m(-V_{out}) + \frac{V_{in} - V_{out}}{r_o} \quad \text{--- (2)}$$

$$\therefore \frac{V_{out}}{R_s} = -g_m V_{out} + \frac{V_{in}}{r_o} - \frac{V_{out}}{r_o}$$

$$V_{out} \left( \frac{1}{R_s} + g_m + \frac{1}{r_o} \right) = \frac{V_{in}}{r_o}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{r_o} \left( \frac{R_s r_o}{r_o + g_m r_o R_s + R_s} \right)$$

$$= \frac{R_s}{g_m r_o R_s + r_o + R_s}$$

Since  $(g_m r_o R_s + r_o) > 0$ , the voltage gain  $< 1$ .

This is expected: Any variation in  $V_{in}$  causes minimal change in the bias current.  
 $\therefore V_{out}$  is determined largely by the amount of bias current ( $\therefore V_{out}$  is set by  $V_{BS1}$ )  
 $\therefore$  There is almost no variation in  $V_{out}$ . (ie.  $\frac{V_{out}}{V_{in}} \ll 1$ )

$$\textcircled{37} \quad a) \quad |Voltage \ gain| = \beta_m R_D$$

$$= 5$$

$$\therefore \beta_m = \frac{5}{500}$$

$$= 10 \text{ mS}$$

$$= \sqrt{2(200 \times 10^{-6}) \left(\frac{W}{L}\right) \times 10^{-3}}$$

$$\therefore \frac{W}{L} = 250 //$$

$$b) \quad V_D = 1.8 - 500 \times 10^{-3}$$

$$= 1.3 \text{ V}$$

$$\text{To obtain } V_{DS} \geq V_{GS} - V_{TH} + 0.2,$$

$$V_D \geq V_G - 0.2$$

$$\therefore V_G \leq 1.5$$

$$\text{Also, } I_{R_1+R_2} = 0.1 \times 10^{-3} \text{ A}$$

$$\therefore R_1 + R_2 = \frac{1.8}{0.1 \times 10^{-3}}$$
$$= 18 \text{ k}\Omega$$

$$\text{choose } R_2 = 15 \text{ k}\Omega \quad \& \quad R_1 = 3 \text{ k}\Omega$$

c) With twice of  $(W/L)$ ,  $M_1$  will go further away from triode. As  $(W/L)$  doubles, &  $I_{bias}$  is fixed by the current source,  $V_{GS}$  is forced to decrease (so  $M_1$  will have same  $I_{DS}$ ). Thus,  $(V_{GS} - V_{TH})$  decreases, and  $V_{DS}$  can be allowed to drop more before  $M_1$  goes into triode.

Gain will be increased by  $\sqrt{2}$ , because  $g_{m1} \propto \sqrt{I_{DS}}$ , and  $f_{m1} \propto \sqrt{W/L}$ .

$$\textcircled{38} \text{ a) } V_G = 1.8 \text{ V.}$$

$$\therefore V_{D, \min} = 1.8 - 0.4 \quad (\text{for } M_1 \text{ stays in saturation})$$
$$= 1.4 \text{ V}$$

$$\therefore R_{D, \max} = \frac{1.4 \text{ V}}{1 \text{ mA}}$$
$$= 1.4 \text{ k}\Omega //$$

$$\text{b) } |\text{Voltage gain}| = g_m R_D$$

$$= 5.$$

$$\therefore g_m = \frac{5}{R_D}$$

$$= 3.57 \text{ mS.}$$

$$= \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L}\right) \times 10^{-3}}$$

$$\therefore \left(\frac{W}{L}\right) = 31.9 //$$

$$\textcircled{39} \quad \text{To get } R_{in} = 50 \Omega,$$

$$\frac{1}{f_m} = 50 \Omega$$

$$\therefore f_m = 20 \text{ mS.}$$

$$\text{voltage gain (Av)} = f_m R_D$$

$$= 4,$$

$$\therefore R_D = \frac{4}{0.02}$$

$$R_D = 200 \Omega //$$

$$\therefore f_m = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L}\right) \times 0.5 \times 10^3}$$

$$\therefore \left(\frac{W}{L}\right) = 2000 //$$

④ To get  $R_{in} = 50 \Omega$ ,

$$f_m = \frac{1}{50}$$
$$= 20 \text{ mS}$$

Voltage gain  $(A_v) = f_m R_D$

$$f_m = \sqrt{2 \times (200 \times 10^{-6}) \cdot \left(\frac{W}{L}\right) \times 0.5 \times 10^{-3}}$$

$$\therefore \frac{W}{L} = 2000$$

$$\therefore V_G = V_E = 1 \text{ V}$$

$$V_{D, \min} = V_G - V_{TH}$$
$$= 0.6 \text{ V}$$

$$\therefore R_{D, \max} = \frac{1.8 - 0.6}{0.5 \times 10^{-3}}$$


$$= 2400$$

$$\therefore \text{max. Voltage gain} = 0.02 \times 2400$$

$$= 48 //$$


(4) Voltage gain ( $A_v$ ) =  $G_m R_{out}$ ,  
 where  $G_m$  and  $R_{out}$  are the transconductance  
 and output resistance of the circuit respectively.

To find  $G_m$ :

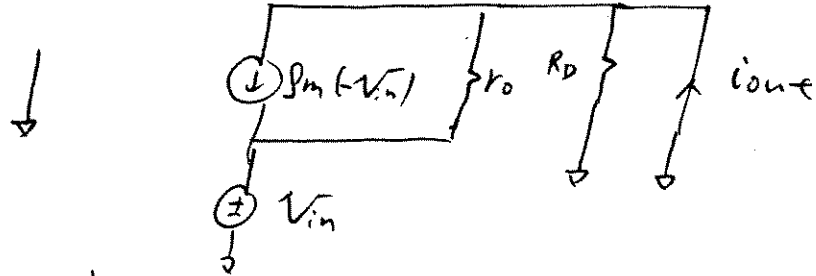

$$G_m = \frac{i_{out}}{V_{in}} = g_m + \frac{1}{r_o} \\ \approx g_m \quad (\because g_m r_o \gg 1)$$

To find  $R_{out}$ :

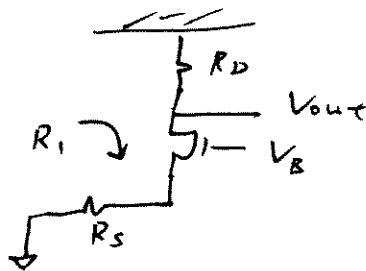

$$R_{out} = R_D \parallel R_i \\ = R_D \parallel [(1 + g_m r_o) R_S + r_o] \\ \text{(from Eq. (7.110))} \\ \approx R_D \parallel (g_m r_o R_S + r_o) \quad (\because g_m r_o \gg 1) \\ = \frac{g_m r_o R_S R_D + r_o R_D}{R_D + g_m r_o R_S + r_o}$$



$$\therefore \text{Voltage gain} = \beta_m \left[ \frac{\beta_m r_o R_D R_S + r_o R_D}{R_D + \beta_m r_o R_S + r_o} \right]$$

(42) a) To get  $R_{in} = 50 \Omega$ ,

$$f_m = \frac{1}{50} \\ = 20 \text{ mS.}$$

To get  $R_{out} = 500 \Omega$ ,

$$R_D = 500 \Omega \quad (\because r_o = \infty)$$

$$\therefore V_{D, \min} = 1.8 - 0.4 = 1.4 \text{ V}$$

$$\therefore I_{D, \max} = \frac{1.8 - 1.4}{500}$$

$$= 0.8 \text{ mA} //$$

$$b) f_m = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L}\right) \times 0.8 \times 10^{-3}}$$

$$\therefore \left(\frac{W}{L}\right) = 1250 //$$

$$c) \text{ Voltage gain} = 0.02 \times 500$$

$$= 10 //$$

43) a) To place  $M_1$  100mV away from triode,

$$\begin{aligned}V_{D, \min} &= V_G - V_{TH} + 0.1V \\ &= 1.5V.\end{aligned}$$

$$\begin{aligned}\therefore R_D &= \frac{(1.8 - 1.5)V}{1mA} \\ &= 300\Omega //\end{aligned}$$

b) Voltage gain =  $g_m R_D$

$$\therefore g_m = \frac{5}{300}$$

$$\therefore g_m = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L}\right) 10^{-3}}$$

$$\therefore \left(\frac{W}{L}\right) \approx 694 //$$

44 a) Voltage gain ( $A_v$ ) =  $\left[ \frac{\frac{1}{\beta_{m1}}}{R_s + \frac{1}{\beta_{m1}}} \right] \frac{\beta_{m1}}{\beta_{m2}}$   
 $= \frac{\beta_{m1}}{\beta_{m2}} \frac{1}{1 + \beta_{m1} R_s}$

b) Voltage gain ( $A_v$ ) =  $\beta_{m1} Z_L$   
 (similar to prob. 32(b))  
 $= \frac{\beta_{m1}}{\beta_{m2}}$

c) Voltage gain =  $\left[ \frac{\frac{1}{\beta_{m1}} \parallel R_i}{R_s + \frac{1}{\beta_{m1}} \parallel R_i} \right] \frac{\beta_{m1}}{\beta_{m2}}$

d) Voltage gain =  $\beta_{m1} [R_D + r_{o3} \parallel \frac{1}{\beta_{m2}}]$

$\therefore r_{o3} = \infty$ ,

gain =  $\beta_{m1} [R_D + \frac{1}{\beta_{m2}}]$

e) Voltage gain =  $\beta_{m1} [R_D + \frac{1}{\beta_{m2}}]$

$$(45) \quad a) \quad \frac{V_x}{V_{in}} = -\beta_{m1} \left[ R_{D1} \parallel \frac{1}{\beta_{m2}} \right]$$

$$\frac{V_{out}}{V_x} = \beta_{m2} R_{D2}$$

$$\therefore \frac{V_{out}}{V_{in}} = -(\beta_{m2} R_{D2}) \left[ \beta_{m1} (R_{D1} \parallel \frac{1}{\beta_{m2}}) \right] //$$

b) if  $R_{D1} \rightarrow \infty$ ,

$$\frac{V_{out}}{V_{in}} = (-\beta_{m2} R_{D2}) \left( \frac{\beta_{m1}}{\beta_{m2}} \right)$$

$$= -\beta_{m1} R_{D2} //$$

This is expected, because the circuit reduces to a cascode stage.

( $\therefore$  gain is the same as that of a cascode stage.)

(46)

$$\frac{V_x}{V_{in}} = (R_{D1} \parallel \frac{1}{\beta m_2}) \beta m_1$$

$$\frac{V_{out}}{V_x} = \beta m_2 R_{D2}$$


$$\therefore \frac{V_{out}}{V_{in}} = \beta m_1 \beta m_2 R_{D2} (R_{D1} \parallel \frac{1}{\beta m_2})$$

Similar to prob. (45), voltage gain approaches that of cascode stage as  $R_{D1}$  approaches infinity. The gain is  $\beta m_1 R_{D2}$ .

47

With  $\lambda = 0$ ,  $M_1$  appears as a diode-connected device.

∴ the circuit becomes :

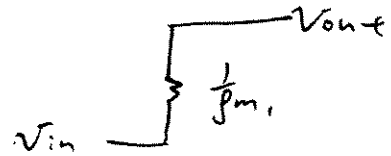


ie.  $\frac{v_{out}}{v_{in}} = 1 //$

This is not a common-gate amplifier, (CG) because the gate is not fixed. (ie. gate is not at an "a.c. ground").

(48)

The small-signal model is:

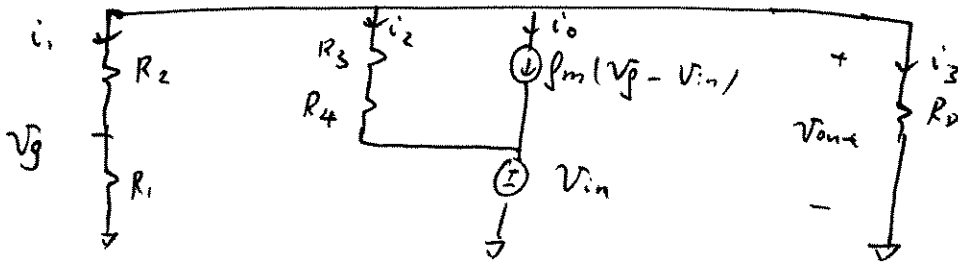

$$\therefore -i_0 = i_1 + i_2 + i_3$$

$$-g_m (V_p - V_{in}) = \frac{V_{out+}}{R_2 + R_1} + \frac{V_{out+} - V_{in}}{R_3 + R_4} + \frac{V_{out+}}{R_D}$$

$$g_m (V_{in} - \frac{R_1}{R_1 + R_2} V_{out+}) = V_{out+} \left( \frac{1}{R_1 + R_2} + \frac{1}{R_3 + R_4} + \frac{1}{R_D} \right) - \frac{V_{in}}{R_3 + R_4}$$

$$V_{in} \left( g_m + \frac{1}{R_3 + R_4} \right) = V_{out+} \left( \frac{g_m R_1 + 1}{R_1 + R_2} + \frac{1}{R_3 + R_4} + \frac{1}{R_D} \right)$$

$$\frac{V_{out+}}{V_{in}} = \frac{\left( g_m + \frac{1}{R_3 + R_4} \right)}{\frac{1}{R_D} + \frac{1}{R_3 + R_4} + \frac{g_m R_1 + 1}{R_1 + R_2}}$$



49

$$\text{Voltage gain } (A_v) = \frac{r_o // R_s}{\frac{1}{g_m} + r_o // R_s}$$

To find  $I_{DS}$ ,

$$I_{DS} = \frac{1}{2} (200 \times 10^{-6}) \left( \frac{20}{0.18} \right) (1.8 - V_s - 0.4)^2$$
$$= 0.0111 (1.4 - I_{DS} \times 1000)^2$$

$$11100 I_{DS}^2 - 32.08 I_{DS} + 0.021756 = 0$$

$$\therefore I_{DS} = 1.80 \text{ mA or } 1.08 \text{ mA.}$$

Reject  $I_{DS} = 1.80 \text{ mA.}$

$$(\because V_s = 1.80 \text{ V} > V_{DD})$$

$$\therefore g_m = \sqrt{2 \times (200 \times 10^{-6}) \times 1.08 \times 10^{-3}}$$

(ignore channel-length modulation)

$$g_m = 0.659 \text{ mS}$$

$$r_o = \frac{1}{0.1 \times 1.08 \times 10^{-3}} \approx 9260 \Omega$$

$$\therefore A_v = \frac{9260 \Omega // 1000 \Omega}{\frac{1}{0.659 \text{ mS}} + 9260 \Omega // 1000 \Omega}$$

$$\approx 0.372 //$$

50

$$A_v = \frac{R}{\frac{1}{f_m} + R}$$

$$\approx 0.8$$

$$\therefore 0.8 = \frac{500}{\frac{1}{f_m} + 500}$$

$$\frac{0.8}{f_m} + 400 = 500$$

$$\therefore f_m = 8 \text{ mS}$$

$$\therefore f_m = \sqrt{2 \times (200 \times 10^{-6}) \times \left(\frac{30}{0.18}\right) I_{DS}}$$

$$\therefore I_{DS} = 0.86 \text{ mA}$$

$$\begin{aligned} \therefore V_S &= 0.86 \times 10^{-3} \times 500 \\ &= 480 \text{ mV} \end{aligned}$$

To find  $V_G$ :

$$0.86 \times 10^{-3} = \frac{1}{2} (200 \times 10^{-6}) / \left(\frac{30}{0.18}\right) (V_G - 0.48 - 0.4)^2$$

$$\therefore V_G = \underline{\underline{1.12 \text{ V}}}$$

(51)

$$A_v = \frac{R_s}{\frac{1}{\beta_m} + R_s}$$
$$= 0.8$$

$$0.8 = \frac{500}{\frac{1}{\beta_m} + 500}$$

$$\therefore \beta_m = 8 \text{ mS.}$$

$$I_{ds} = \frac{1}{2} \beta (V_{gs} - V_t)^2,$$

$$\text{where } \beta = \left(\frac{w}{L}\right) \mu_n C_{ox}$$

$$\text{and } \beta_m = \beta (V_{gs} - V_t).$$

$$\therefore I_{ds} = \frac{1}{2} \beta_m (V_{gs} - V_t)$$

$$= \frac{1}{2} \beta_m (1.8 - I_{ds}(500) - 0.4)$$

$$I_{ds} = 4 \times 10^{-3} (1.4 - 500 I_{ds})$$

$$\therefore I_{ds} = 1.87 \text{ mA.}$$

$$\therefore \beta_m = \sqrt{2(200 \times 10^{-6}) \frac{w}{L} \times 1.87 \times 10^{-3}}$$

$$\therefore \frac{w}{L} \approx 85.7 //$$

52. To get  $R_{out} = 100 \Omega$ ,

$$\frac{1}{g_m} = 100$$

$$\therefore g_m = 10 \text{ mS.}$$

$$\therefore I_{ds} = \frac{1}{2} \beta (V_{gs} - V_{TH})^2$$

$$\text{where } \beta = \mu_n C_{ox} \frac{W}{L}$$

$$\text{and } g_m = \beta (V_{gs} - V_{TH})$$

$$\begin{aligned} \therefore I_{ds} &= \frac{1}{2} g_m (V_{gs} - V_{TH}) \\ &= \frac{1}{2} (10 \times 10^{-3}) (0.8 - 0.4) \end{aligned}$$

$$\therefore I_{ds} = 2.5 \text{ mA.}$$

$$\therefore g_m = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L}\right) (2.5 \times 10^{-3})}$$

$$\therefore \left(\frac{W}{L}\right) = 100 //$$

53. To get  $R_{out} = 50 \Omega$ ,

$$\frac{1}{f_m} = 50 \Omega$$

$$\therefore f_m = 20 \text{ mS}$$

$$\begin{aligned} \text{Power (P)} &= 1.8 \times I_{Ds} \\ &= 2 \times 10^{-3} \text{ W} \end{aligned}$$

$$\therefore I_{Ds} = 1.11 \text{ mA}$$

$$\therefore f_m = \sqrt{2 \times (200 \times 10^{-6}) / \left(\frac{W}{L}\right) / (1.11 \text{ mA})}$$

$$\therefore \frac{W}{L} = 900 //$$

(54)

$$A_v = \frac{R_L}{\frac{1}{\beta_m} + R_L}$$

$$\therefore 0.8 = \frac{50}{\frac{1}{\beta_m} + 50}$$

$$\beta_m = 80 \text{ mS}$$

$$\begin{aligned} \text{Power (P)} &= 1.8 \times I_{DS} \\ &= 3 \text{ mW} \end{aligned}$$

$$\therefore I_{DS} = 1.67 \text{ mA}$$


$$\beta_m = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L}\right) (1.67 \times 10^{-3})}$$

$$\therefore \left(\frac{W}{L}\right) = \underline{\underline{9600}}$$

55

$$a) A_v = \frac{r_{o1} \parallel (R_s + r_{o2})}{\frac{1}{\beta_{m1}} + r_{o1} \parallel (R_s + r_{o2})}$$
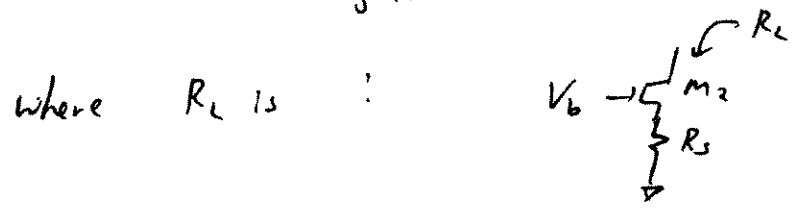
$$b) A_v = \frac{r_{o1} \parallel R_L}{\frac{1}{\beta_{m1}} + (r_{o1} \parallel R_L)}$$




$$R_L = (1 + \beta_{m2} r_{o2}) R_s + r_{o2} \quad \text{Eq. (7.110)}$$

$$\therefore A_v = \frac{r_{o1} \parallel [(1 + \beta_{m2} r_{o2}) R_s + r_{o2}]}{\frac{1}{\beta_{m1}} + r_{o1} \parallel [(1 + \beta_{m2} r_{o2}) R_s + r_{o2}]}$$

$$c) A_v = \frac{r_{o1} \parallel \frac{1}{\beta_{m2}}}{\frac{1}{\beta_{m1}} + (r_{o1} \parallel \frac{1}{\beta_{m2}})}$$


$$d) A_v = \frac{r_{o1} \parallel R_L}{\frac{1}{\beta_{m1}} + (r_{o1} \parallel R_L)}$$

where  $R_L$  is :

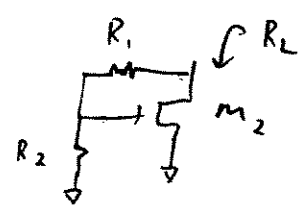

(c) Finding  $R_L$  with small-signal model:

(cont'd)

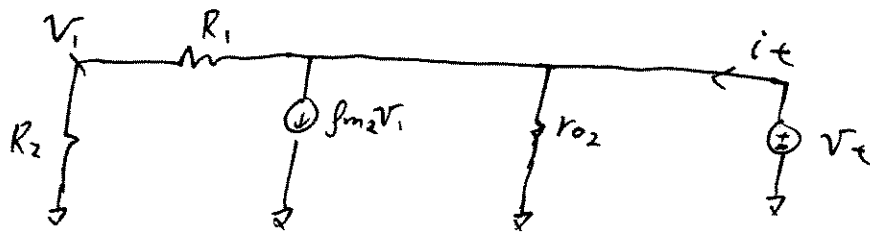

$$R_L = \frac{V_t}{i_t}$$

$$\text{where } i_t = \frac{V_t}{r_{o2}} + \beta_{m2} V_i + \frac{V_t}{R_1 + R_2}$$

$$= \frac{V_t}{r_{o2}} + \frac{\beta_{m2} R_2 V_t}{R_1 + R_2} + \frac{V_t}{R_1 + R_2}$$

$$\therefore R_L = \frac{r_{o2} (R_1 + R_2)}{R_2 + R_1 + r_{o2} + \beta_{m2} r_{o2} R_2}$$

$$\therefore A_v = \frac{r_{o1} \parallel \frac{r_{o2} (R_1 + R_2)}{R_2 + R_1 + r_{o2} + \beta_{m2} r_{o2} R_2}}{\frac{1}{\beta_{m1}} + r_{o1} \parallel \frac{r_{o2} (R_2 + R_1)}{R_2 + R_1 + r_{o2} + \beta_{m2} r_{o2} R_2}}$$

$$e) \quad A_v = \frac{r_{o2} \parallel \left( \frac{1}{\beta_{m1}} \parallel r_{o3} \right)}{\frac{1}{\beta_{m2}} + r_{o2} \left( \frac{1}{\beta_{m1}} \parallel r_{o3} \right)}$$

$$f) \quad A_v = \frac{r_{o1} \parallel \left[ (1 + \beta_{m2} r_{o2}) r_{o3} + r_{o2} \right]}{\frac{1}{\beta_{m1}} + \left\{ r_{o1} \parallel \left[ (1 + \beta_{m2} r_{o2}) r_{o3} + r_{o2} \right] \right\}}$$



$$(56) \quad \frac{v_x}{v_{in}} = \frac{g_{m2}}{\frac{1}{g_{m1}} + g_{m2}}$$

$$\frac{v_{out}}{v_x} = g_{m2} R_D$$

$$\therefore \frac{v_{out}}{v_{in}} = \frac{R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

b) if  $g_{m1} = g_{m2}$ ,

$$\frac{v_{out}}{v_{in}} = \frac{g_{m1} R_D}{2}$$

(57)

$$\therefore R_{out} = 1k\Omega$$

$$\therefore R_D = 1k\Omega$$

$$\begin{aligned}\therefore A_v &= 5 \\ &= g_{m1} R_D\end{aligned}$$

$$\therefore g_{m1} (1000) = 5$$

$$g_{m1} = 5\text{mS}$$

$\therefore M_1$  is 00 mV away from triode,

$$V_D = (V_G - V_{TH}) + 0.1$$

$$V_D = (1.8 - 0.4) + 0.1$$

$$V_D = 1.5\text{V}$$

$$\therefore I_{D1} = \frac{1.8 - 1.5}{R_D} = \frac{0.3}{R_D}$$

$$= 0.3\text{mA}$$

$$\therefore g_{m1} = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L}\right) I_{D1}}$$

$$\therefore \left(\frac{W}{L}\right) \approx 208$$

$$\therefore R_D = 1k\Omega, R_G = 10k\Omega, \left(\frac{W}{L}\right) = 208$$

$$\textcircled{58} \therefore \text{Power (P)} = 2 \text{ mW},$$

$$\therefore I_{DS} = \frac{2 \times 10^{-3}}{1.8}$$

$$= 1.11 \text{ mA}.$$

$$\therefore R_D I = 1$$

$$\therefore R_D = 900 \Omega.$$

$$\therefore |\text{Gain (Av)}| = 5,$$

$$f_m R_D = 5$$

$$f_m = 5.56 \text{ mS}.$$

$$\therefore f_m = \sqrt{2(200 \times 10^{-6}) \left(\frac{\omega}{L}\right) (1.11 \times 10^{-3})}$$

$$\frac{\omega}{L} \approx 69.4 //$$

$$(59) \quad |A_v| = g_m R_L.$$

$\therefore$  To achieve maximum gain, use maximum  $R_L$ .

$$\text{i.e. set } R_D = 500 \Omega.$$

For maximum  $g_m$ , use maximum  $I_{D_s}$ .

(... while keeping  $M_1$  in saturation),

$$\text{i.e. } V_D \geq V_G - V_{TH}$$

$$1.8 - (I_{D_s})(500) \geq 1.8 - 0.4,$$

$$\therefore I_{D_s} \leq \frac{0.4}{500}$$

$$I_{D_s, \max} = 0.8 \text{ mA}.$$

Note: Setting a large  $R_D$  in this case would force  $I_{D_s, \max}$  to be lower (in order to keep  $M_1$  in saturation).

But since  $A_v \propto R_D$ , while  $A_v \propto \sqrt{I_{D_s}}$ , sacrificing  $I_{D_s}$  to get higher  $R_D$  would yield a higher gain.

$$\textcircled{60} \quad \therefore \text{Power (P)} = 2 \text{ mW},$$

$$\therefore I_{DS} = (0.95) \left( \frac{2 \times 10^{-3}}{1.8} \right)$$

(assuming  $(R_1 + R_2)$  consumes 5% of total power)

$$I_{DS} = 1.06 \text{ mA}$$

$$\therefore R_S = \frac{0.2 \text{ V}}{1.06 \text{ mA}}$$

$$\approx 189 \Omega$$

$$\therefore g_m = \beta V_{eff}$$

(where  $\beta = \mu_n C_{ox} \left( \frac{W}{L} \right)$ ;  $V_{eff} = V_{GS} - V_{TH}$ )

$$\text{and } I_{DS} = \frac{1}{2} \beta V_{eff}^2$$

$$\therefore I_{DS} = \frac{1}{2} g_m V_{eff}$$

Set  $V_{eff} = 0.1 \text{ V}$  (< maximum allowable overdrive)

$$1.06 \times 10^{-3} = \frac{1}{2} g_m (0.1)$$

$$g_m = 21.2 \text{ mS}$$

$$\therefore |A_V| = \frac{g_m R_D}{1 + g_m R_S} = 4$$

$$\therefore \frac{21.2 \times 10^{-3} \times R_D}{1 + (21.2 \times 10^{-3}) \times 189} = 4$$

$$R_D \approx 147 \Omega$$

$$\text{With } V_{GS} - V_{TH} = 0.1 \text{ V,}$$

$$V_{GS} = 0.1 + 0.4 \text{ V}$$

$$= 0.5 \text{ V}$$

$$= V_G - V_S$$

$$\therefore V_G - 0.2 \text{ V} = 0.5 \text{ V}$$

$$\therefore V_G = 0.7 \text{ V}$$

To find  $R_1$  &  $R_2$ ,

$$\therefore I_{R_1+R_2} = (0.05) \left( \frac{2 \times 10^{-3}}{1.8} \right)$$

$$= 5.56 \times 10^{-5} \text{ A}$$

$$\therefore R_1 + R_2 = \frac{1.8 \text{ V}}{5.56 \times 10^{-5} \text{ A}}$$

$$= 32.4 \text{ k}\Omega$$

$$V_G = \frac{R_2}{R_1 + R_2} \times 1.8 = 0.7 \text{ V}$$

$$\therefore R_2 = 12.6 \text{ k}\Omega,$$

$$R_1 = (32.4 - 12.6) \text{ k}\Omega = 19.8 \text{ k}\Omega.$$

To find  $(\frac{W}{L})_1$ ,

$$f_m = \sqrt{2 \times 200 \times 10^{-6} \times (\frac{W}{L})_1 \times 1.06 \times 10^{-3}} = 21.2 \text{ ms}$$

$$\therefore (\frac{W}{L})_1 = 1060$$

$$\therefore R_1 = 19.8 \text{ k}, R_2 = 12.6 \text{ k}, R_S = 189 \Omega, R_D = 947 \Omega$$

$$(\frac{W}{L})_1 = 1060, I_{DS} = 1.06 \text{ mA}$$

(61)

$$\text{Power (P)} = 6 \text{ mW}$$

$$\therefore I_{DS} = (0.95) \left( \frac{6 \times 10^{-3}}{1.8} \right) = 3.17 \text{ mA}$$

$$\text{Gain (A}_v) = 5,$$

$$\therefore \frac{g_m R_D}{1 + g_m R_S} = 5$$

$$5 = (R_D - 5R_S) g_m$$

for  $g_m$  to be positive,

$$R_D > 5R_S, \quad \text{ie. } R_S < 50 \Omega$$

$$\text{choose } R_S = 30 \Omega$$

$$\therefore V_{ov} \text{ (over drive voltage)} = V_{R_S}$$

$$\begin{aligned} \therefore V_{ov} &= 3.17 \times 10^{-3} \times 30 \\ &= 95.1 \text{ mV} \end{aligned}$$

$$\text{From } A_v = \frac{g_m R_D}{1 + g_m R_S} = 5,$$

$$g_m = 100 \text{ mS}$$

$$\therefore g_m = (M_n C_{ox}) \left( \frac{W}{L} \right) V_{ov}$$

$$\therefore \left( \frac{W}{L} \right) \approx 5260$$

To find  $R_1$  and  $R_2$ ,

$$I_{R_1 + R_2} = (0.05) \left( \frac{6 \times 10^{-3}}{1.8} \right) = 0.167 \text{ mA}$$

$$\therefore R_1 + R_2 = \frac{1.8}{0.167 \times 10^{-3}} = 10.8 \text{ k}\Omega$$

$$\therefore V_{GS} - V_{TH1} = V_{OV} = 95.1 \text{ mV},$$

$$\text{and } V_S = 95.1 \text{ mV},$$

$$\therefore (V_G - 95.1 \text{ mV}) - 0.4 = 95.1 \text{ mV}$$

$$V_G = 0.5902$$

$$\therefore V_G = \frac{R_2}{R_1 + R_2} \times 1.8$$

$$\therefore R_2 = 3.54 \text{ k}\Omega$$

$$\text{and } R_1 = 10.8 \text{ k}\Omega - 3.54 \text{ k}\Omega \\ = 7.26 \text{ k}\Omega$$

$$\therefore R_1 = 7.26 \text{ k}\Omega, \quad R_2 = 3.54 \text{ k}\Omega, \quad R_S = 30 \Omega$$

$$\left(\frac{W}{L}\right) = 5260 \quad I_{DS} = 3.17 \text{ mA}.$$



$$\textcircled{62} \quad \text{Power } (P) = 2 \text{ mW}$$

$$\therefore I_{DS} = \frac{2 \text{ mW}}{1.8 \text{ V}}$$

$$= 1.11 \text{ mA}$$

$\therefore M_1$  operates 200 mV away from triode

$$V_{DS} = (V_{GS} - V_{TH}) + 0.2$$

$$\therefore V_D = 1.6 \text{ V}$$

$$R_D = \frac{V_{RD}}{I_{DS}} = \frac{(1.8 - 1.6) \text{ V}}{1.11 \times 10^{-3} \text{ A}}$$

$$= 180 \Omega$$

$$\therefore \text{Gain } (A_v) = \frac{g_m R_D}{1 + g_m R_S} = 6$$

$$\therefore 6 = (R_D - 6 R_S) g_m$$

for  $g_m > 0$ ,  $R_D - R_S > 0$ , i.e.  $R_S < 30 \Omega$

See  $R_S = 20 \Omega$ ,

$$g_m = \frac{6}{180 - 6 \times 20} = 100 \text{ mS}$$

$$\therefore g_m = (\mu_n C_{ox}) \left(\frac{W}{L}\right) (V_{GS} - V_{TH})$$

$$0.1 = 200 \times 10^{-6} \left(\frac{W}{L}\right) (1.8 - 1.11 \times 10^{-3} \times 20 - 0.4)$$

$$\therefore \frac{W}{L} \approx 363$$

$$R_{in} = \frac{1}{sC_1} + R_1$$

$\therefore \frac{1}{sC_1}$  is negligible,

$$R_{in} = R_1 = 20 \text{ k}\Omega$$

To make  $\frac{1}{sC_1}$  negligible,

$$\frac{1}{sC_1} \ll R_1$$

$$\frac{1}{2\pi(10^6)C_1} \ll \dots$$

$$\therefore C_1 \ll 7.96 \text{ pF}$$

$$\text{Set } C_1 = 0.796 \text{ pF}$$

To make  $\frac{1}{sC_s}$  negligible,

$$\frac{1}{sC_s} \ll R_s \parallel \frac{1}{\beta m_1}$$

$$\frac{1}{2\pi(10^6)C_s} \ll 20 \parallel \frac{1}{100 \text{ ms}}$$

$$C_s \ll 23.9 \text{ nF}$$

$$\text{Set } C_s = 2.39 \text{ nF}$$

$$\therefore R_D = 180 \Omega, R_s = 20 \Omega, R_1 = 20 \text{ k}\Omega, \frac{W}{L} = 363$$

$$C_1 = 0.796 \text{ pF}, C_s = 2.39 \text{ nF}$$

63. Power  $(P) = 2 \text{ mW}$ ,

$$\therefore I_{DS1} = |I_{DS2}| = \frac{2 \text{ mW}}{1.8 \text{ V}} = 1.11 \text{ mA}$$

$$\begin{aligned} r_{o1} = r_{o2} &= \frac{1}{\lambda I_{DS}} \\ &= \frac{1}{0.1 \times 1.11 \times 10^{-3}} \\ &= 9000 \Omega \end{aligned}$$

$$f_{\text{ain}} (A_v) = f_{m1} (r_{o1} \parallel r_{o2}) = 20,$$

$$f_{m1} \left( \frac{9000}{2} \right) = 20,$$

$$\therefore f_{m1} = 4.44 \text{ mS}$$

$$\text{Set } V_{DS1} \text{ (ie. } V_{out}) = 1.2 \text{ V}$$

$$\text{(which is } < 1.5 \text{ V)}$$

$$\therefore V_{ZV} = V_{GS1} \leq 1.2 + V_{TH}$$

(for  $M_1$  to stay in saturation)

$$\text{Set } V_{GS1} = 1.2 \text{ V}$$

$$\therefore f_{m1} = \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{GS1} - V_{TH})$$

$$\left( \frac{W}{L} \right)_1 = 27.75$$

For  $M_2$ ,  $\therefore M_2$  must be in saturation

for  $V_{out} \leq 1.5 \text{ V}$ .

$$\therefore V_{DD} - V_B \leq V_{DD} - 1.5 \text{ V} + V_{TH}$$

$$\therefore V_B \geq 1.1 \text{ V}$$

$$\text{Set } V_B = 1.2V$$

$$|I_{DS2}| = \frac{1}{2} \mu_p C_{ox} \left( \frac{W}{L} \right)_2 (|V_{GS2}| - V_{TH})^2 \\ (1 + \lambda |V_{DS2}|)$$

$$1.11 \times 10^{-3} = \frac{1}{2} \times 100 \times 10^{-6} \left( \frac{W}{L} \right)_2 (0.6 - 0.2)^2 \\ (1 + 0.1 \times (1.8 - 1.5))$$

$$(\text{assuming } V_{out} = 1.5V)$$

$$\therefore \left( \frac{W}{L} \right)_2 \approx 135$$


$$\therefore \left( \frac{W}{L} \right)_1 = 27.75 \quad \left( \frac{W}{L} \right)_2 = 135$$

$$V_{ZN} = 1.2 \quad V_b = 1.1$$


$$I_{DS1} = I_{DS2} = 1.11 \text{ mA}$$

(64) a) gain  $(A_v) = -g_{m1} r_{o1} \parallel R_L$ ,

where  $R_L$  is:

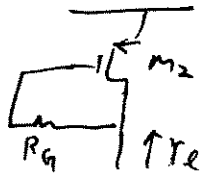

The small-signal model is:

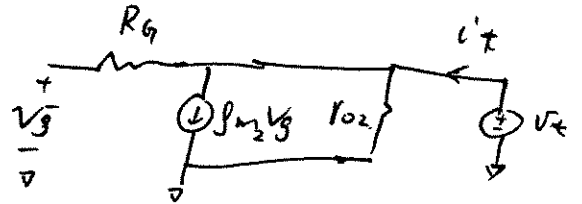

$$R_L = \frac{v_e}{i_e} = r_{o2} \parallel \frac{1}{g_{m2}}$$

$$\therefore A_v = -g_{m1} r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}}$$

b) Power = 3mW

$$\therefore I_{D S1} = |I_{D S2}| = \frac{3\text{mW}}{1.8\text{V}}$$

$$= 1.67\text{mA}$$

$$V_{OUT} = V_{G2} = \frac{V_{DD}}{2}$$

$$\therefore V_{GS2} = -0.9\text{V}$$

$$I_{D S2} = \frac{1}{2} (100 \times 10^{-6}) \left(\frac{W}{L}\right)_2 \times (1 - 0.9 - V_{TH})^2$$

$$\times (1 + 0.1 \times \frac{V_{DD}}{2})$$

$$\therefore \left(\frac{W}{L}\right)_2 \approx 122$$

$$\begin{aligned} f_{m2} &= \mu_p C_{ox} \left( \frac{W}{L} \right)_2 (V_{GS2} - V_{TH}) \\ &= 6.1 \text{ mS} \end{aligned}$$

$$\text{From (a), } |A_d| = \frac{1}{f_{m1}} \times (r_{o1} \parallel r_{o2} \parallel \frac{1}{f_{m2}})$$

$$\therefore r_{o1} = \frac{1}{0.1 \times 1.67 \times 10^{-3}} = 6000 \Omega$$

$$r_{o2} = \frac{1}{0.2 \times 1.67 \times 10^{-3}} = 3000 \Omega$$

$$\therefore 15 = f_{m1} \left( 6000 \parallel 3000 \parallel \frac{1}{6.1 \text{ mS}} \right)$$

$$f_{m1} = 99 \text{ mS}$$

$$f_{m1} = \sqrt{2} \left( \frac{W}{L} \right)_1 \mu_n C_{ox} I_{DS1}$$

$$\therefore \left( \frac{W}{L} \right)_1 = 14672$$

$$\therefore \left( \frac{W}{L} \right)_1 = 14672, \left( \frac{W}{L} \right)_2 = 122, I_{DS1} = |I_{DS2}| = 1.67 \text{ mA}$$

$$\begin{aligned}
 \textcircled{65} \text{ a) Impedance looking into drain of } M_2 & \\
 &= (1 + g_{m_2} r_{o_2}) R_s + r_{o_2} \\
 &= 10 r_{o_1}
 \end{aligned}$$

Assume  $g_{m_2} r_{o_2} \gg 1$ ,

$$\therefore g_{m_2} r_{o_2} R_s + r_{o_2} \approx 10 r_{o_1}$$

$$\therefore r_{o_1} = r_{o_2} \quad (\lambda_1 = \lambda_2 \text{ and } I_{D_1} = |I_{D_2}|)$$

$$\begin{aligned}
 \therefore g_{m_2} R_s + 1 &= 10 \\
 g_{m_2} R_s &= 9 \quad \text{--- (1)}
 \end{aligned}$$

Given  $V_B = 1V$ ,

$$\text{Set } |V_{GS2}| = 0.6V, \quad (\text{ie. } V_{GS2} - V_{TH} = 0.2V)$$

$$\therefore V_{S2} = 1.6V$$

$$\therefore V_{RS} = 1.8V - 1.6V = 0.2V$$

$$\therefore \text{Power} = 2mW$$

$$I_{D_1} = |I_{D_2}| = \frac{2mW}{1.8V} = 1.11mA$$

$$\therefore R_s = \frac{V_{RS}}{1.11 \times 10^{-3}} \approx 180 \Omega //$$

$$\text{From (1), } g_{m_2} = \frac{9}{180} = 50 \text{ mS}$$

$$\therefore g_{m_2} = \left(\frac{W}{L}\right)_2 (100 \times 10^{-6}) (V_{GS2} - V_{TH})$$

$$\therefore \left(\frac{W}{L}\right)_2 = 2500 //$$

$$b). \text{Gain } (A_v) = f_{m_1} (r_{o1} \parallel 10r_{o1})$$

$$30 = f_{m_1} (0.909 r_{o1})$$

$$r_{o1} = \frac{1}{0.1 \times 1.1 \times 10^{-3}}$$

$$= 9009 \Omega$$

$$\therefore f_{m_1} = 3.66 \text{ mS.}$$

$$\therefore f_{m_1} = \sqrt{2} (M_n C_{ox}) \left( \frac{W}{L} \right)_1 \times I_{DS1}$$

$$\therefore \left( \frac{W}{L} \right)_1 \approx 30.2 //$$



66. Power = 1mW

$$\therefore I_{DS1} = I_{DS2} = \frac{1\text{mW}}{1.8\text{V}} = 0.556\text{mA}$$

$$\text{Volt. gain } (A_v) = -\frac{g_{m1}}{g_{m2}} = -\sqrt{\frac{(W/L)_1}{(W/L)_2}}$$

$$= -4$$

See  $V_{GS1} = V_{GS2} = \frac{V_{DD}}{3}$

$$\therefore I_{DS1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{TH})^2$$

$$\therefore \left(\frac{W}{L}\right)_1 = 139 //$$

$$\therefore \left(\frac{W}{L}\right)_2 = \frac{139}{16}$$

$$\approx 8.69 //$$

and  $V_{IN} = \frac{V_{DD}}{3} = 0.6\text{V}$

$$(67) \quad R_{in} = \frac{1}{g_m} = 50 \Omega$$

$$\therefore g_m = 20 \text{ mS}$$

$$\text{Voltage gain } (A_v) = g_m R_D = 5$$

$$\therefore R_D = 250 \Omega$$

$$\text{Power} = 3 \text{ mW}$$

$$\therefore I_{DS} = \frac{3 \text{ mW}}{1.8 \text{ V}}$$

$$= 1.67 \text{ mA}$$

$$\therefore g_m = \sqrt{2 \times \mu_n C_{ox} \times \left(\frac{W}{L}\right)_1 I_{DS}}$$

$$\left(\frac{W}{L}\right)_1 = 600$$

$$\therefore R_D = 250 \Omega, \quad \left(\frac{W}{L}\right)_1 = 600, \quad I_{DS} = 1.67 \text{ mA}$$

(68)

$$\text{Power (P)} = 2 \text{ mW}$$

$$I_{DS} = \frac{2 \text{ mW}}{1.8 \text{ V}} = 1.11 \text{ mA}$$

$\therefore M_1$  operates  $100 \text{ mV}$  away from triode,

$$V_{DS} = V_{GS} - V_{TH} + 0.1$$

$$V_D = 1.8 - 0.4 + 0.1 = 1.5 \text{ V}$$

$$\therefore R_D = \frac{1.8 - 1.5}{1.11 \times 10^{-3}} \approx 270 \Omega$$

$$\text{Volt. gain (A}_v) = g_{m1} R_D = 4$$

$$\therefore g_{m1} = 14.8 \text{ mS}$$

$$\therefore I_{DS} = \frac{1}{2} g_{m1} \times (V_{GS1} - V_{TH})$$

$$V_{GS} \approx 0.550 \text{ V}$$

$$\text{Set } V_G = 0.9 \text{ V}, \quad \therefore V_S = (0.9 - 0.55) \text{ V} = 0.35 \text{ V}$$

$$R_S = \frac{0.35}{1.11 \times 10^{-3}} \approx 315 \Omega$$

$$\text{To find } \left(\frac{W}{L}\right)_1: \quad g_{m1} = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{TH})$$

$$\therefore \left(\frac{W}{L}\right)_1 \approx 135$$

$$\therefore \left(\frac{W}{L}\right)_1 = 135, \quad V_{TH} = 0.9 \text{ V}, \quad R_S = 315 \Omega, \quad R_D = 270 \Omega$$

$$I_{DS} = 1.11 \text{ mA}$$

69

$$\text{Power} = 5 \text{ mW}$$

$$\therefore I_{DS1} = \frac{5 \times 10^{-3}}{1.8} = 2.78 \text{ mA}$$

$$\text{Gain } (A_v) = \beta_m R_D = 5$$

$$V_{GS1} = V_{OUT} = 1.8 - I R_D$$

$$V_{S1} = I R_S$$

$$\text{Let } R_S = \frac{10}{\beta_m}$$

$$\therefore V_{S1} = \frac{10 I}{\beta_m}$$

$$\therefore V_{GS1} = 1.8 - I R_D - \frac{10 I}{\beta_m}$$

$$\therefore I_{DS1} = \frac{1}{2} \beta_m (V_{GS1} - V_{TH1})$$

$$\begin{aligned} 2.78 \times 10^{-3} &= \frac{\beta_m}{2} \left( 1.8 - 2.78 \times 10^{-3} R_D - \frac{2.78 \times 10^{-2}}{\beta_m} \right) \\ &= 0.9 \beta_m - 1.39 \times 10^{-3} \beta_m R_D - 1.39 \times 10^{-2} \end{aligned}$$

$$\therefore \beta_m R_D = A_v = 5$$

$$2.78 \times 10^{-3} = 0.9 \beta_m - 6.95 \times 10^{-3} - 1.39 \times 10^{-2}$$

$$\therefore \beta_m \approx 26.3 \text{ mS}$$

$$\text{and } R_D = \frac{5}{26.3 \times 10^{-3}} \approx 190 \Omega //$$

$$R_S = \frac{10}{26.3 \times 10^{-3}} = 380 \Omega //$$

$$\therefore \beta_m = \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right) I_{DS1}} \Rightarrow \left(\frac{W}{L}\right) \approx 622 //$$

(70)

$$\therefore R_s \approx \frac{10}{\beta_m}$$

$$\therefore R_{in} \approx \frac{1}{\beta_m} = 50 \Omega$$

$$\text{i.e. } \beta_m = 20 \text{ mS} //$$

$$| \text{gain (Av)} | = \frac{\beta_m R_D}{1 + \beta_m R_s} = 4$$

$$\beta_m R_D = 4 + 4 \beta_m R_s$$

$$R_D = \frac{4 + 0.08 R_s}{0.02} = 200 + 4 R_s \quad \text{--- (1)}$$

$$\therefore R_s I_D + V_{GS} - V_{TH} + 0.25 = 1.8 - I_D R_D \quad (\text{given})$$

$$\text{and } I_D = \frac{1}{2} \beta_m (V_{GS} - V_{TH})$$

$$\text{i.e. } V_{GS} - V_{TH} = 100 I_D$$

$$\therefore R_s I_D + 100 I_D + 0.25 = 1.8 - I_D R_D$$

From (1):

$$R_s I_D + 100 I_D + 0.25 = 1.8 - 200 I_D - 4 I_D R_s$$

$$5 R_s I_D + 300 I_D = 1.55$$

$$\text{See } R_s = \frac{10}{\beta_m} = 500 \Omega$$

$$\therefore 2500 I_D + 300 I_D = 1.55$$

$$\therefore I_D = 0.554 \text{ mA} //$$

$$\therefore I_D = \frac{1}{2} \beta_m (V_{GS} - V_{TH})$$

$$0.554 \times 10^{-3} = \frac{1}{2} \times 20 \times 10^{-3} (V_{GS} - 0.4)$$

$$\therefore V_{GS} = 0.455 \text{ V}$$

To find  $(\frac{W}{L})$ :

$$f_m = \sqrt{2 \left( \frac{W}{L} \right) \mu_n C_{ox} I_{D1}}$$

$$\therefore \left( \frac{W}{L} \right) \approx 1805$$

To find  $R_D$ :

$$\therefore R_D = 200 + 4R_S \quad (\text{from (1)})$$

$$R_D = 2200$$

To find  $R_1$  and  $R_2$ ,

$$\therefore R_1 + R_2 = 20 \text{ k}\Omega$$

$$\text{and } V_{GS} = V_G - I_D R_S = 0.455 \text{ V}$$

$$\text{i.e. } V_G = 0.732 \text{ V}$$

$$V_G = \frac{R_2}{R_1 + R_2} \times V_{DD}$$

$$\therefore R_1 = 8133 \Omega$$

$$R_2 \approx 11.9 \text{ k}\Omega.$$

$$\therefore R_1 = 8133 \Omega, R_2 = 11.9 \text{ k}\Omega, R_D = 2200 \Omega, R_S = 500 \Omega$$

$$\left( \frac{W}{L} \right) = 1805 \quad I_{D1} = 0.554 \text{ mA.}$$

(71)

$$R_{in} = R_g = 10 \text{ k}\Omega //$$

$$\text{Power} = 2 \text{ mW}$$

$$\therefore I_{DS} = \frac{2 \text{ mW}}{1.8 \text{ V}} = 1.11 \text{ mA} //$$

$$A_v = \frac{R_s}{\frac{1}{\beta_m} + R_s} = 0.8$$

$$\therefore R_s = \frac{4}{\beta_m} \quad \text{--- (1)}$$

$$\therefore V_{out} = \frac{V_{DD}}{2} = I_{DS} R_s$$

$$I_{DS} R_s = 0.9 \quad \text{--- (2)}$$

$$\therefore V_G = 1.8 \text{ V and } V_s = 0.9$$

$$\therefore V_{GS} = 0.9 \text{ V}$$

$$\text{From (2), } \therefore I_{DS} = 1.11 \text{ mA}$$

$$R_s = \frac{0.9 \text{ V}}{1.11 \text{ mA}} \approx 810 \Omega //$$

$$\text{From (1), } \beta_m = \frac{4}{810 \Omega} \approx 4.94 \text{ mS}$$

$$\therefore \beta_m = \left(\frac{W}{L}\right) (M_n C_{ox}) (V_{GS} - V_{TH})$$

$$\frac{W}{L} \approx 49.4 //$$

72

$$R_{in} = R_g = 20k\Omega$$

$$\therefore \text{Power} = 3\text{mW}$$

$$\therefore I_{DS} = \frac{3\text{mW}}{1.8\text{V}} = 1.67\text{mA}$$


$$V_{x,ac\&dc} = I_{DS} R_s = 0.9\text{V}$$

$$\therefore R_s = 540\Omega$$

$$\text{Load impedance, } Z_L = R_s \parallel \left( \frac{1}{sC_1} + R_L \right)$$

(at 100 MHz)
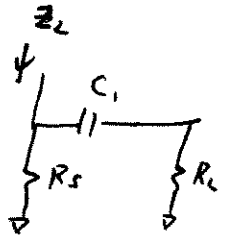
$$= 540 \parallel \left( \frac{1}{2\pi \times 10^8 C_1} + 50 \right)$$



$$\text{Voltage gain } (A_v) = \frac{Z_L}{f_m + Z_L}$$

$$f_m = \frac{2I_{DS}}{V_{GS} - V_{TH}}$$

$$= \frac{2 \times 1.67 \times 10^{-3}}{(1.8 - 0.9) - 0.4}$$

$$= 6.67\text{ms}^{-1}$$

$$\therefore A_v = \frac{Z_L}{f_m + Z_L} = 0.8$$

$$Z_L = 120 + Z_L (0.8)$$

$$\therefore Z_L = 150$$



$$\therefore 150 = 540 \parallel \left( \frac{1}{2\pi \times 10^8 C_1} + 50 \right)$$

$$= 540 \parallel \left[ \frac{1 + 50(2\pi \times 10^8 C_1)}{2\pi \times 10^8 C_1} \right]$$

$$= \frac{540 \times \frac{1 + 50(2\pi \times 10^8 C_1)}{2\pi \times 10^8 C_1}}{540 + \frac{1 + 50(2\pi \times 10^8 C_1)}{2\pi \times 10^8 C_1}}$$

$$\therefore \frac{1 + 50(2\pi \times 10^8 C_1)}{2\pi \times 10^8 C_1} \approx 208$$

$$\therefore C_1 \approx 10.1 \text{ pF} //$$

To find  $\left(\frac{W}{L}\right)$ :

$$\therefore f_m = \left(\frac{W}{L}\right) \mu_n C_{ox} (V_{GS} - V_{TH})$$

$$\frac{W}{L} = 66.7 //$$

$$\therefore \frac{W}{L} = 66.7, C_1 = 10.1 \text{ pF}, R_s = 540 \Omega.$$

(73)

$$\text{Power} = 3 \text{ mW}$$

$$\therefore I_{D_{S_{1,2}}} = \frac{3 \text{ mW}}{1.8 \text{ V}} = 1.67 \text{ mA}$$

$$r_{o2} = \frac{1}{\lambda I_{D_{S_2}}}$$

$$= \frac{1}{0.1 \times 1.67 \times 10^{-3}} \approx 5990 \Omega$$

$$= r_{o1}$$

$$\therefore A_v = \frac{r_{o2} \parallel r_{o1}}{\frac{1}{\beta_{m_1}} + r_{o2} \parallel r_{o1}} = 0.9$$

$$\therefore 0.9 = \frac{2995}{\frac{1}{\beta_{m_1}} + 2995}$$

$$\beta_{m_1} \approx 3 \text{ mS}$$

$\therefore V_{D_{S_2}} \geq 0.3 \text{ V}$  (for  $M_2$  to be in saturation)

Set  $V_{out}$  (i.e.  $V_{D_{S_2}}$ , nominal) = 0.3 V

$$\therefore \beta_{m_1} = \frac{2 I_{D_{S_1}}}{V_{G_{S_1}} - V_{TH}}$$

$$3 \times 10^{-3} = \frac{2 \times 1.67 \times 10^{-3}}{V_G - 0.9 - 0.4}$$


$$\therefore V_{IN} = V_G \approx 1.81 \text{ V}$$

$$I_m = \sqrt{2 \left(\frac{W}{L}\right) \mu_n C_{ox} I_{DS}}$$

$$\therefore \frac{W}{L} \approx 13.5$$


$$\therefore \frac{W}{L} = 13.5, \quad V_{ZM} = 1.81V, \quad I_{DS} = 1.67mA.$$

① a)

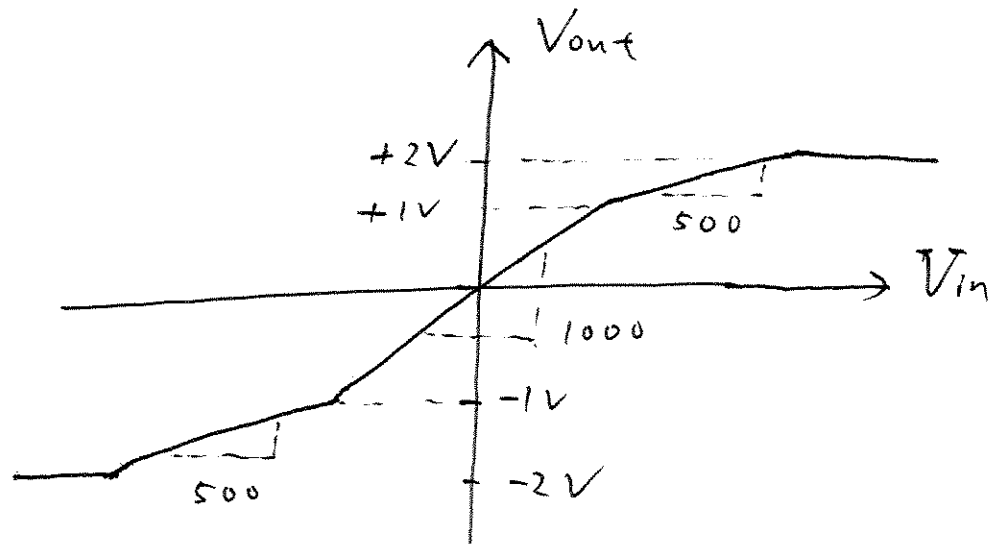

b/ The largest input swing is  $\pm 1mV$ , because gain is constant at  $1000$  over this range of input.
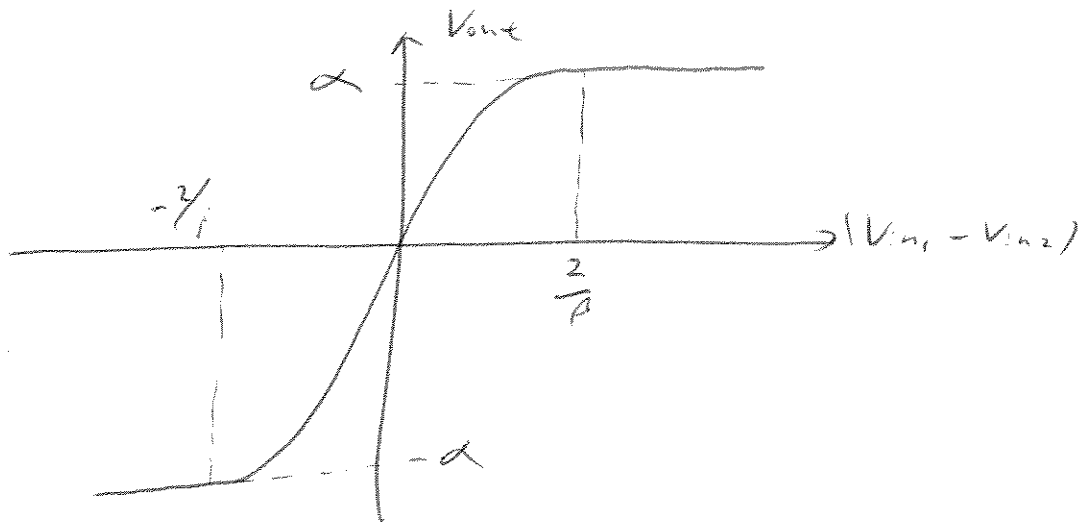
$$(2) \quad V_{out} = \alpha \tanh [\beta (V_{in1} - V_{in2})]$$



To find small-signal gain,

$$\therefore \tanh z = z - \frac{1}{3} z^3 + \frac{2}{15} z^5 + \dots$$

$\therefore$  for  $\beta(V_{in1} - V_{in2}) \approx 0$ ,

$$\frac{dV_{out}}{d(V_{in1} - V_{in2})} \approx \frac{d}{d(V_{in1} - V_{in2})} \alpha \beta (V_{in1} - V_{in2})$$

$$= \underline{\underline{\alpha \beta}}$$

$$\textcircled{3} \text{ closed-loop gain} = \left(1 + \frac{R_1}{R_2}\right)$$

$$= 8$$

$$\text{Gain error} = \left(1 + \frac{R_1}{R_2}\right) (A_0)^{-1}$$

$$= \frac{8}{2000}$$

$$= \underline{\underline{0.4\%}}$$

$$\textcircled{4} \quad \text{closed loop gain} = \left(1 + \frac{R_1}{R_2}\right)$$

$$= 4$$

$$\text{Gain error} = \left(1 + \frac{R_1}{R_2}\right) \left(\frac{1}{A_0}\right)$$

$$= 0.1\%$$

$$\therefore 4/A_0 = 0.1\%$$

$$A_0 = \underline{\underline{4000}}$$

$$\textcircled{5} \quad \text{Let } G_0 = \left(1 + \frac{R_1}{R_2}\right)$$

$$\text{Desired gain} = \alpha_1$$

$$= \frac{A_0}{1 + \frac{R_2}{R_1 + R_2} A_0}$$

$$\therefore \alpha_1 = \frac{A_0}{1 + \frac{A_0}{G_0}}$$

$$1 + \frac{A_0}{G_0} = \frac{A_0}{\alpha_1}$$

$$\frac{1}{G_0} = \frac{1}{\alpha_1} - \frac{1}{A_0}$$

$$G_0 = \frac{A_0 \alpha_1}{A_0 - \alpha_1}$$

$$\therefore \frac{R_2}{R_1 + R_2} = \frac{1}{G_0} = \frac{1}{\alpha_1} - \frac{1}{A_0} //$$

b) if  $A_0$  drops to  $0.6 A_0$ ,

$$\text{Actual gain} = \frac{0.6 A_0}{1 + \left(\frac{1}{\alpha_1} - \frac{1}{A_0}\right) 0.6 A_0}$$

$$= \frac{0.6 A_0}{0.4 + \frac{0.6 A_0}{\alpha_1}}$$



⑤ b) (cont'd)


$$\text{Actual gain} = \frac{\alpha_1}{1 + \frac{0.4}{0.6} \frac{\alpha_1}{A_0}}$$

$$\approx \alpha_1 \left( 1 - \frac{0.4}{0.6} \frac{\alpha_1}{A_0} \right)$$

$$\therefore \text{the gain error} = \frac{0.4}{0.6} \frac{\alpha_1^2}{A_0}$$

$$= \underline{\underline{\frac{2}{3} \frac{\alpha_1^2}{A_0}}}$$

⑥ Using the model in Fig. 8.44,

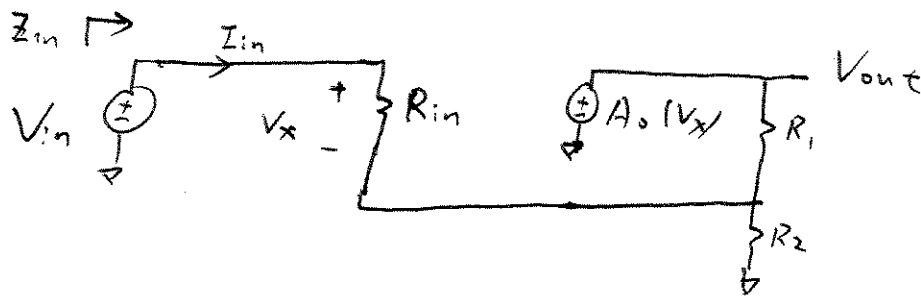

$$V_x = V_{in} - V_{out} \frac{R_1}{R_1 + R_2}$$

$$V_{out} = A_0 V_x$$

$$= A_0 \left( V_{in} - V_{out} \frac{R_1}{R_1 + R_2} \right)$$

$$A_0 V_{in} = V_{out} \left( 1 + A_0 \frac{R_1}{R_1 + R_2} \right)$$

$$\frac{V_{out}}{V_{in}} = \frac{A_0}{1 + A_0 \frac{R_1}{R_1 + R_2}} \quad \text{--- ①}$$

To find input impedance ( $Z_{in}$ ),

$$I_{in} = \frac{V_x}{R_{in}}$$

$$= \frac{1}{R_{in}} \left( V_{in} - V_{out} \frac{R_1}{R_1 + R_2} \right)$$

$$= \frac{V_{in}}{R_{in}} \left( 1 - \frac{V_{out}}{V_{in}} \frac{R_1}{R_1 + R_2} \right)$$

⑥ (cont'd)

$$\begin{aligned} I_{in} &= \frac{V_{in}}{R_{in}} \left( 1 - \frac{A_o}{1 + A_o \frac{R_1}{R_1 + R_2}} \frac{R_1}{R_1 + R_2} \right) \\ &= \frac{V_{in}}{R_{in}} \left( 1 - \frac{1}{\frac{R_1 + R_2}{A_o R_1} + 1} \right) \\ &= \frac{V_{in}}{R_{in}} \left( \frac{\frac{R_1 + R_2}{A_o R_1}}{\frac{R_1 + R_2}{A_o R_1} + 1} \right) \end{aligned}$$


$$\therefore Z_{in} = \frac{V_{in}}{I_{in}} = R_{in} \left[ \frac{1 + \frac{R_1 + R_2}{A_o R_1}}{\frac{R_1 + R_2}{A_o R_1}} \right] \quad \text{--- (2)}$$

As  $A_o \rightarrow \infty$ ,

$$\begin{aligned} \text{Gain} &= \frac{V_{out}}{V_{in}} \Big|_{A_o \rightarrow \infty} \quad [\text{From (1)}] \\ &= 1 + \frac{R_2}{R_1} // \end{aligned}$$

$$\begin{aligned} Z_{in} &= \frac{V_{in}}{I_{in}} \Big|_{A_o \rightarrow \infty} \quad [\text{From (2)}] \\ &= \infty // \end{aligned}$$

7

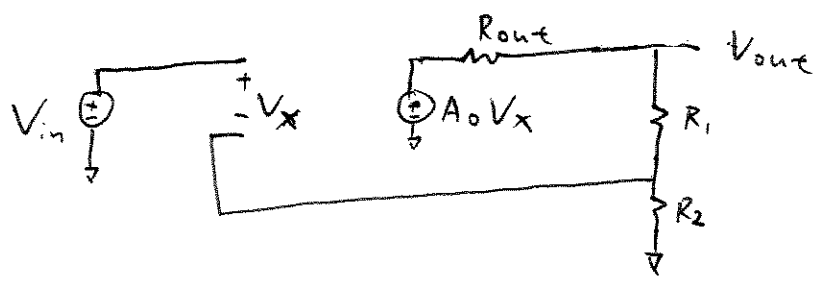

Similar to Prob. (6),

$$\text{Gain} = \frac{V_{out}}{V_{in}}$$

$$V_x = V_{in} - V_{out} \frac{R_2}{R_1 + R_2}$$


$$V_{out} = A_0 V_x \frac{R_1 + R_2}{R_{out} + R_1 + R_2}$$

$$= A_0 \left( V_{in} - V_{out} \frac{R_2}{R_1 + R_2} \right) \frac{R_1 + R_2}{R_{out} + R_1 + R_2}$$

$$V_{in} A_0 \frac{R_1 + R_2}{R_{out} + R_1 + R_2} = V_{out} \left( 1 + \frac{A_0 R_2}{R_{out} + R_1 + R_2} \right)$$

$$\frac{V_{out}}{V_{in}} = \frac{A_0 \frac{R_1 + R_2}{R_{out} + R_1 + R_2}}{1 + \frac{A_0 R_2}{R_{out} + R_1 + R_2}}$$

To find output impedance ( $Z_{out}$ )

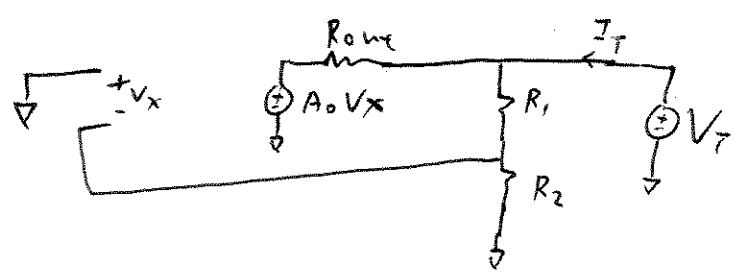

$$(7) \text{ (cont'd)} \quad V_x = \frac{R_2}{R_1 + R_2} V_T$$

$$\begin{aligned} I_T &= \frac{V_T}{R_1 + R_2} + \frac{V_T - A_o V_x}{R_{out}} \\ &= V_T \left[ \frac{R_{out} + R_1 + R_2 - A_o R_2}{(R_{out})(R_1 + R_2)} \right] \end{aligned}$$


$$Z_{out} = \frac{V_T}{I_T} = \frac{(R_{out})(R_1 + R_2)}{R_{out} + R_1 + R_2 - A_o R_2}$$

As  $A_o \rightarrow \infty$ ,

$$\text{gain} = 1 + \frac{R_1}{R_2} //$$

$$Z_{out} = 0 //$$

8

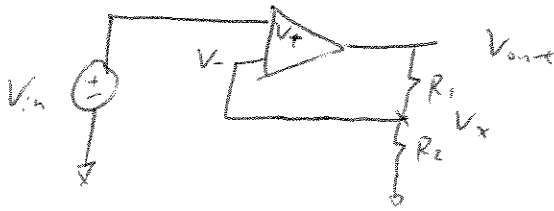

$\Delta R$  for now.

$$V_{out} = A_o (V_x)$$

$$V_x = V_{in} - \frac{R_2}{R_1 + R_2} V_{out}$$

$$\therefore \frac{-V_{out}}{A_o} = V_{in} - \frac{R_1}{R_1 + R_2} V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{A_o (R_1 + R_2)}{A_o R_1 - 1} = \text{nominal gain}$$

$$\text{if } R_2' = \Delta R + R_2$$

$$\left( \frac{V_{out}}{V_{in}} \right)' = \frac{A_o (R_1 + \Delta R + R_2)}{A_o R_1 - 1}$$

$$\therefore \text{gain error} = \frac{\left( \frac{V_{out}}{V_{in}} \right)' - \left( \frac{V_{out}}{V_{in}} \right)}{\frac{V_{out}}{V_{in}}}$$

$$= \frac{\Delta R}{A_o R_1 - 1} \times \frac{A_o R_1 - 1}{A_o (R_1 + R_2)}$$

$$= \frac{\Delta R}{A_o (R_1 + R_2)} //$$

$$\textcircled{9} \quad \text{Closed-loop gain} \approx \left(1 + \frac{R_1}{R_2}\right) \left[1 - \left(1 + \frac{R_1}{R_2}\right) \frac{1}{A_0}\right]$$

$$= 5 \left[1 - \frac{5}{A_0}\right]$$

∴ As  $A_0$  decreases to  $0.8A_0$ , closed-loop gain decreases along. (deviating more from the nominal)

$A_0$  drops to  $0.8A_0$  when  $|V_{in1} - V_{in2}| = 2\text{mV}$ .

$$\therefore V_{in2} = V_{out} \left(\frac{R_2}{R_1 + R_2}\right)$$


$$\text{and } V_{out} = 5 \left(1 - \frac{5}{A_0}\right) V_{in1}$$

$$\therefore V_{in2} = 5 \left(1 - \frac{5}{A_0}\right) \left(\frac{1}{5}\right) V_{in1}$$

$$V_{in1} - V_{in2} = \frac{5}{A_0} V_{in1}$$

$$\text{At } V_{in1} - V_{in2} = 2\text{mV},$$

$$V_{in1} = \frac{A_0}{5} (2\text{mV})$$

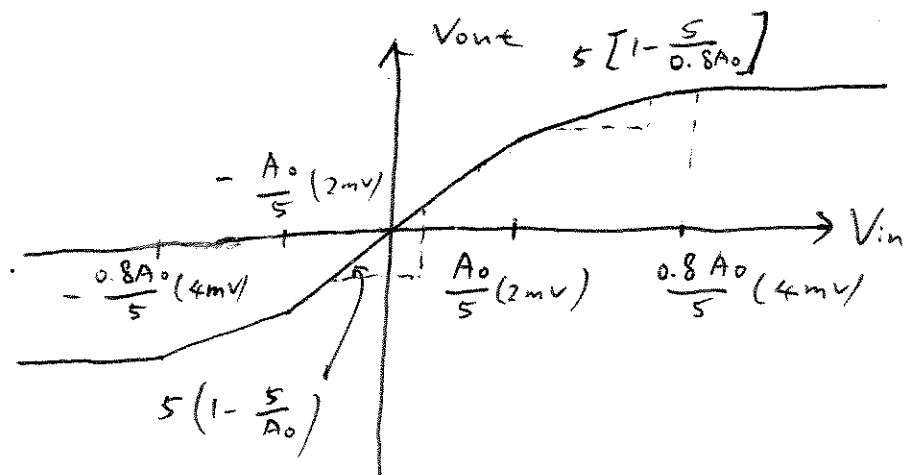

10

$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_1}{R_2}$$

$$\therefore V_{in} = 1V, \quad V_{out} = 1 + \frac{R_1}{R_0 + \Delta W}$$

$$\frac{dV_{out}}{dW} = -R_1 \Delta (R_0 + \Delta W)^{-2}$$

$$= \frac{-R_1 \Delta}{(R_0 + \Delta W)^2}$$



(11) If  $A_o = \infty$ ,

$$V_+ = V_- = V_{in}$$

$$V_- = \left( \frac{R_2}{R_2 + R_3} \right) \left[ \frac{R_4 \parallel (R_2 + R_3)}{R_1 + R_4 \parallel (R_2 + R_3)} \right] V_{out}$$

$\therefore$  closed-loop gain  $\frac{V_{out}}{V_{in}}$

$$= \frac{(R_2 + R_3) [R_1 + R_4 \parallel (R_2 + R_3)]}{R_2 [R_4 \parallel (R_2 + R_3)]}$$

if  $R_1 = 0$ ,

$$G_{R_1=0} = 1 + \frac{R_3}{R_2} //$$

if  $R_3 = 0$ ,

$$G_{R_3=0} = \frac{R_2 [R_1 + R_4 \parallel R_2]}{R_2 [R_4 \parallel R_2]}$$

$$= 1 + \frac{R_1}{R_4 \parallel R_2} //$$

$$\textcircled{12} \quad \text{Gain Error} = \frac{1}{A_0} \left( 1 + \frac{R_1}{R_2} \right)$$


$$= \frac{1}{A_0} (1 + 8)$$

$$= 0.2 \%$$

$$\therefore \frac{1}{A_0} (9) = 0.2 \%$$

$$A_0 = 4500$$

(13)

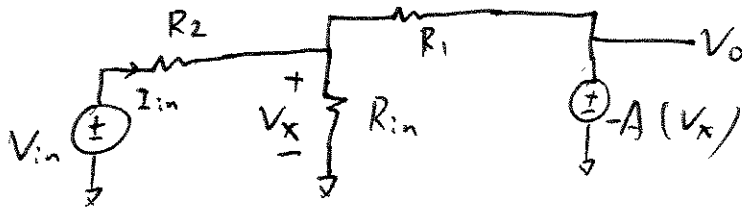

$$V_o = -A V_x \quad \text{--- (1)}$$

$$\frac{V_{in} - V_x}{R_2} + \frac{V_o - V_x}{R_1} = \frac{V_x}{R_{in}} \quad \text{--- (2)}$$

Combining (1) and (2),

$$\frac{V_{in}}{R_2} = -\frac{V_o}{R_1} + \frac{V_o}{(-A)} \left( \frac{1}{R_{in}} + \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\frac{V_{in}}{R_2} = V_o \left[ \frac{A R_{in} R_2 + R_1 R_2 + R_{in} R_2 + R_{in} R_1}{(-A) R_{in} R_1 R_2} \right]$$

$$\frac{V_o}{V_{in}} = - \frac{A R_{in} R_1}{R_1 R_2 + R_{in} R_2 + R_{in} R_1 + A R_{in} R_2}$$

$$\text{Input impedance } (Z_{in}) = \frac{V_{in}}{I_{in}}$$

$$I_{in} - \frac{V_x}{R_{in}} + \frac{(-A)V_x - V_x}{R_1} = 0$$

$$I_{in} = V_x \left[ \frac{1}{R_{in}} + \frac{A+1}{R_1} \right]$$


$$\therefore V_x = V_{in} - I_{in} R_2$$

$$I_{in} = [V_{in} - I_{in} R_2] \left[ \frac{1}{R_{in}} + \frac{A+1}{R_1} \right]$$

$$I_{in} \left[ 1 + \frac{R_2}{R_{in}} + \frac{R_2}{R_1} (A+1) \right] = V_{in} \left( \frac{1}{R_{in}} + \frac{A+1}{R_1} \right)$$

$$I_{in} = \frac{V_{in}}{I_{in}} = \frac{1 + \frac{R_2}{R_{in}} + \frac{R_2}{R_1} (A+1)}{\frac{1}{R_{in}} + \frac{A+1}{R_1}} //$$

14

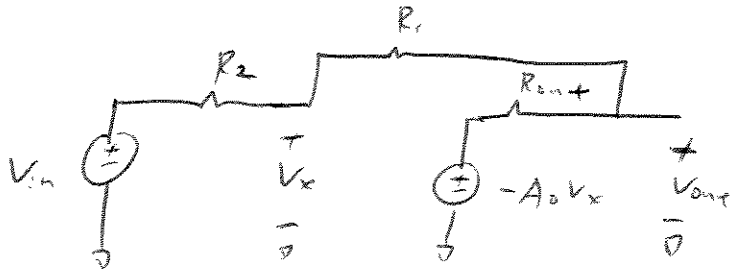

By KCL,

$$\frac{V_{in} - V_x}{R_2} = - \frac{-A_0 V_x - V_x}{R_1 + R_{out}}$$

$$\therefore V_x = - \frac{V_{out}}{A_0}$$

$$\frac{V_{in}}{R_2} = - \frac{V_{out}}{A_0 R_2} - \frac{A_0 + 1}{A_0} \frac{V_{out}}{R_1 + R_{out}}$$

$$\therefore \frac{A_0 + 1}{A_0} \approx 1$$


$$\therefore \frac{V_{in}}{R_2} \approx - \frac{V_{out}}{A_0 R_2} - \frac{V_{out}}{R_1 + R_{out}}$$

$$\frac{V_{in}}{R_2} \approx -V_{out} \left( \frac{R_1 + R_{out} + A_0 R_2}{A_0 R_2 (R_1 + R_{out})} \right)$$

$$\therefore \frac{V_{out}}{V_{in}} \approx - \frac{A_0 (R_1 + R_{out})}{R_1 + R_{out} + A_0 R_2}$$

(14) cont'd:

To find output impedance ( $Z_{out}$ )

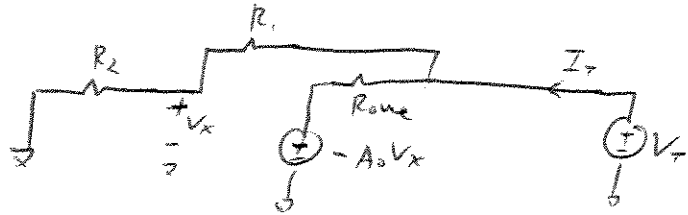

$$Z_{out} = \frac{V_T}{I_T}$$


$$V_x = \frac{R_2}{R_1 + R_2} V_T \quad \text{--- (1)}$$

$$I_T = \frac{V_T}{R_1 + R_2} + \frac{V_T + A_0 V_x}{R_{out}} \quad \text{--- (2)}$$

$$I_T = V_T \left[ \frac{1}{R_1 + R_2} + \frac{1 + \frac{A_0 R_2}{R_1 + R_2}}{R_{out}} \right]$$

$$\frac{V_T}{I_T} = \frac{R_{out} (R_1 + R_2)}{R_{out} + R_1 + (A_0 + 1)R_2} //$$

15

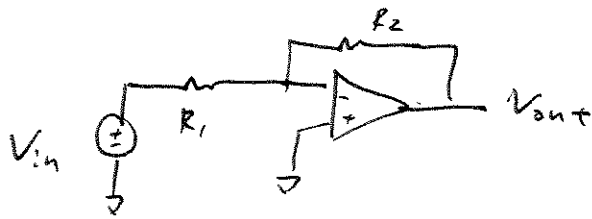

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{R_2}{R_1} = 4 \quad \text{--- (1)}$$

$$\therefore R_2 = 4R_1$$


$$Z_{in} \approx R_1 = 10 \text{ k}\Omega \quad \text{--- (2)}$$

$$\therefore R_2 = 40 \text{ k}\Omega$$

$$A_0 = 1000 \quad \text{--- (3)}$$

$$\begin{aligned} \text{gain error} &= \frac{1}{A_0} \left( 1 + \frac{R_2}{R_1} \right) \\ &= \frac{1}{1000} (1 + 4) \\ &= 0.5\% \end{aligned}$$

(16)

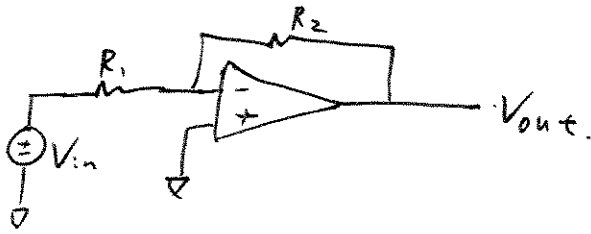

$$\text{Nominal gain} = \frac{R_2}{R_1} = 8 \quad \text{--- (1)}$$

$$R_2 = 8R_1$$

$$\text{Input impedance} \approx R_1 = 1000 \Omega \quad \text{--- (2)}$$

$$\therefore R_2 = 8000 \Omega.$$

$$\text{Gain error} = 0.1\% \quad \text{--- (3)}$$


$$\therefore \frac{1}{A_0} \left( 1 + \frac{R_2}{R_1} \right) = 0.1\%$$

$$\frac{1}{A_0} (9) = \frac{0.1}{100}$$

$$\therefore A_0 = 9000 //$$



(17)

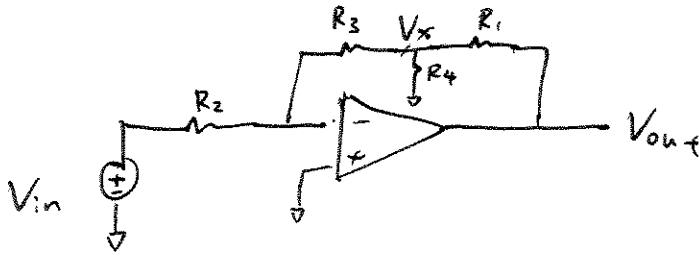

$$V_- = V_+ = 0 \quad (\because A = \infty)$$

$$\frac{V_{in}}{R_2} = - \frac{V_x}{R_3} \quad \text{--- (1)}$$

$$V_x = \frac{R_3 // R_4}{R_1 + R_3 // R_4} V_{out} \quad \text{--- (2)}$$

Combining (1) and (2),

$$\frac{V_{in}}{R_2} = - \frac{R_3 // R_4}{R_3 (R_1 + R_3 // R_4)} V_{out}$$

$$\frac{V_{out}}{V_{in}} = - \frac{R_3}{R_2} \frac{(R_1 + R_3 // R_4)}{R_3 // R_4} //$$


if  $R_1 \rightarrow 0$ ,

$$\frac{V_{out}}{V_{in}} = - \frac{R_3}{R_2} // \quad (\text{typical inverting amplifier})$$

if  $R_3 \rightarrow 0$ ,

$$\frac{V_{out}}{V_{in}} = - \frac{R_1}{R_2} // \quad (\text{typical inverting amplifier})$$

(18)

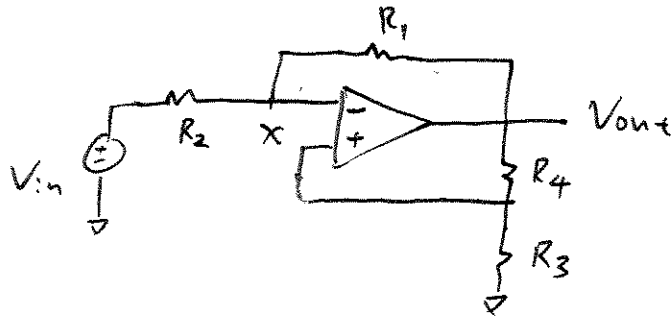

$$\therefore A = \infty$$

$$V_- = V_+$$

$$\therefore V_x = \frac{R_3}{R_3 + R_4} V_{out}$$

$$\frac{V_{in} - V_x}{R_2} = - \frac{V_{out} - V_x}{R_1}$$

$$\frac{V_{in}}{R_2} = V_x \left( \frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{V_{out}}{R_1}$$

$$= \left[ \left( \frac{R_3}{R_3 + R_4} \right) \left( \frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{1}{R_1} \right] V_{out}$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{\frac{1}{R_2}}{\left( \frac{R_3}{R_3 + R_4} \right) \left( \frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{1}{R_1}} //$$

(19)

From eq (8.31),

$$\begin{aligned}V_{out} &= -\frac{1}{R_1 C_1} \int V_{in} dt \\&= -\frac{1}{R_1 C_1} \int V_0 \sin \omega t dt \\&= \frac{V_0}{R_1 C_1 \omega} \cos \omega t\end{aligned}$$

$$\therefore \text{Amplitude of output} = \frac{V_0}{R_1 C_1 \omega} //$$

(20) From prob. (19)

Amplification of the integrator =  $\frac{1}{R_1 C_1 \omega}$

$$\therefore \frac{1}{R_1 C_1 \omega} = 10$$

$$\frac{1}{\omega} = 10 \times 10^{-6} \text{ s}$$

$$\therefore \omega = 10 \text{ MHz}$$

$\therefore$  The frequency of the sinusoid is 10 MHz.

(21)


From Eq. (8.37)

$$S_p = \frac{-1}{2\pi (A_0 + 1) R C} \quad \leq -1 \text{ Hz.}$$

$$\therefore 2\pi (A_0 + 1) (10 \text{ k}\Omega) (1 \text{ nF}) \geq 1$$

$$A_0 \geq \underline{\underline{15915}}$$

(22)

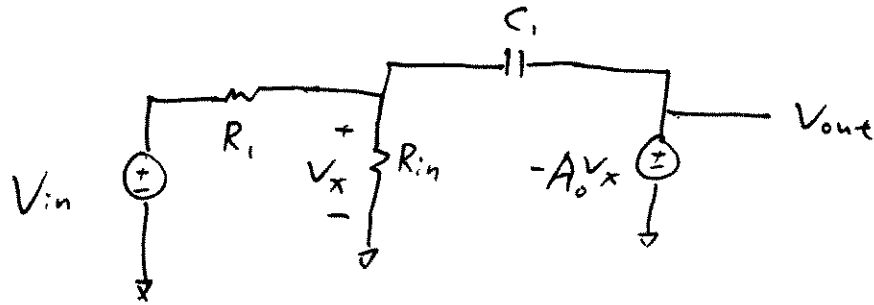

$$\frac{V_{in} - V_x}{R_i} + \frac{V_{out} - V_x}{\frac{1}{sC_f}} = \frac{V_x}{R_{in}}$$

Where  $s = j\omega$

$$\therefore V_{out} = -A_o V_x$$

$$\begin{aligned} \therefore \frac{V_{in}}{R_i} &= (sC_f) \left[ -\frac{V_{out}}{A_o} - V_{out} \right] - \frac{V_{out}}{A_o} \left( \frac{1}{R_{in}} + \frac{1}{R_i} \right) \\ &= -V_{out} \left[ \frac{sC_f}{A_o} + sC_f + \frac{1}{A_o R_{in}} + \frac{1}{A_o R_i} \right] \end{aligned}$$


$$\frac{V_{out}}{V_{in}} = \frac{-1}{\left( \frac{1}{A_o} + \frac{R_i}{A_o R_{in}} \right) + \left( 1 + \frac{1}{A_o} \right) s R_i C_f}$$

To find the pole, equate denominator to zero.

$$s_p = \frac{-1}{(A_o + 1) R_i C_f} \left( 1 + \frac{R_i}{R_{in}} \right)$$

[ $\therefore$  pole shifted out by  $\left( 1 + \frac{R_i}{R_{in}} \right)$ ]

(23)

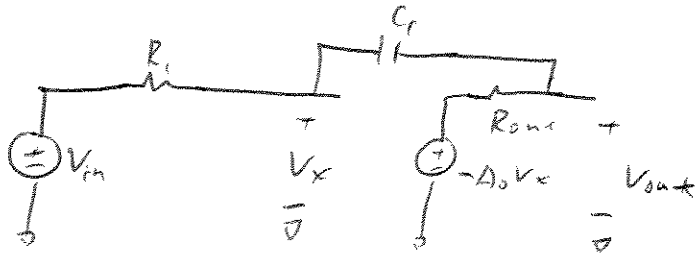

By KCL,

$$\frac{V_{in} - V_x}{R_i} = - \frac{-A_0 V_x - V_x}{R_{out} + \frac{1}{sC_f}}$$

$$\therefore V_x = - \frac{V_{out}}{A_0}$$

$$\frac{V_{in}}{R_i} = - \frac{V_{out}}{A_0 R_i} - \frac{(A_0 + 1)}{A_0} \frac{V_{out}}{R_{out} + \frac{1}{sC_f}}$$

$$\approx - V_{out} \left[ \frac{1}{A_0 R_i} + \frac{1}{R_{out} + \frac{1}{sC_f}} \right]$$

$$\left( \because \frac{A_0 + 1}{A_0} \approx 1 \right)$$

$$\therefore \frac{V_{out}}{V_{in}} = - \frac{A_0 \times (R_{out} + \frac{1}{sC_f})}{(A_0 R_i + R_{out} + \frac{1}{sC_f})}$$

$$\text{pole} = - \frac{1}{C_f (R_{out} + A_0 R_i)}$$

$$(24) \because A_o = \infty$$

$$|A_v| = \frac{R_1}{\frac{1}{\omega C_1}}$$

$$= \omega R_1 C_1$$

$$= 5$$

$$\therefore R_1 C_1 = \frac{5}{\omega}$$

$$= \frac{5}{2\pi \times 10^6}$$

$$= 7.958 \times 10^{-7}$$



(25)

From eq: (8.55)


$$S_p = - \frac{A_0 + 1}{R_1 C_1}$$

$$2\pi \times 100 \times 10^6 = \frac{A_0 + 1}{1000 \times 10^{-9}}$$

(ie.  $R_1$  and  $C_1$  are chosen at minimum)

$$A_0 \approx 627$$

(26)

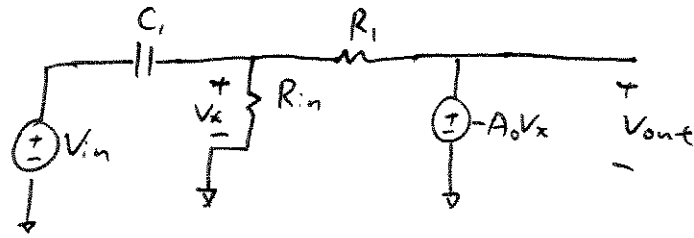

By KCL,

$$(V_{in} - V_x) s C_1 = \frac{V_x}{R_{in}} + \frac{(V_x + A_0 V_x)}{R_f}$$

$$(V_{in}) s C_1 = V_x \left[ s C_1 + \frac{1}{R_{in}} + (A_0 + 1) \frac{1}{R_f} \right]$$


$$\frac{s C_1}{s C_1 + \frac{1}{R_{in}} + (A_0 + 1) \frac{1}{R_f}} = \frac{V_x}{V_{in}}$$

$$\therefore V_{out} = -A_0 V_x,$$

$$\therefore \frac{V_{out}}{V_{in}} = - \frac{A_0 s C_1}{s C_1 + \frac{1}{R_{in}} + (A_0 + 1) \frac{1}{R_f}} //$$

$$\text{As } A_0 \rightarrow \infty, \quad \frac{V_{out}}{V_{in}} \rightarrow - R_f C_1 s. \quad [8.42]$$

(27)

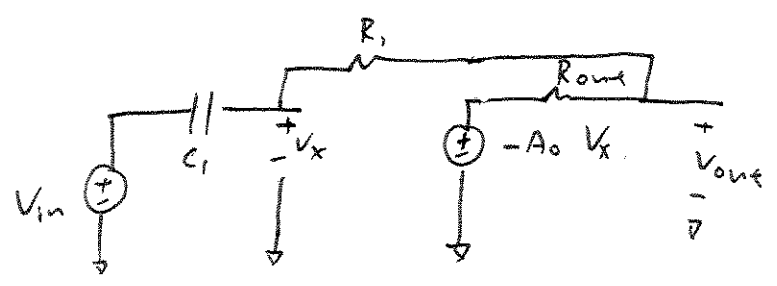

By KCL,

$$(V_{in} - V_x) / s C_i = (V_x + A_o V_x) \frac{1}{R_i + R_{out}}$$

$$(V_{in}) / s C_i = V_x \left[ s C_i + (A_o + 1) \frac{1}{R_i + R_{out}} \right]$$

$$\frac{V_x}{V_{in}} = \frac{s C_i}{s C_i + (A_o + 1) \frac{1}{R_i + R_{out}}}$$

$$V_{out} = (-A_o V_x - V_x) \frac{R_i}{R_i + R_{out}}$$

(resistive divider)

$$= -V_x \frac{(A_o + 1) / R_i}{R_i + R_{out}}$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{(A_o + 1) R_i s C_i}{R_i + R_{out}} \div \frac{s C_i + (A_o + 1) \frac{1}{R_i + R_{out}}}$$

$$\frac{V_{out}}{V_{in}} = -R_i s C_i \quad (\text{as } A_o \rightarrow \infty)$$

[8.42]

(28)

$$\therefore A_o = \infty,$$

$$V_f = V_o = 0$$

By KCL,

$$\frac{V_{in}}{R_1 \parallel \frac{1}{sC_1}} = - \frac{V_{out}}{R_2 \parallel \frac{1}{sC_2}}$$

$$\therefore \frac{V_{out}}{V_{in}} = - \frac{R_2 \parallel \frac{1}{sC_2}}{R_1 \parallel \frac{1}{sC_1}}$$

$$= - \frac{R_2}{R_1} \times \frac{1 + R_1 C_1 s}{1 + R_2 C_2 s}$$

$$\text{For } \left| \frac{V_{out}}{V_{in}} \right| = 1,$$

$$R_2 \parallel \frac{1}{sC_2} = R_1 \parallel \frac{1}{sC_1}$$

That is, choose the components such that the impedance of  $R_2 \parallel \frac{1}{sC_2}$  is equal to  $R_1 \parallel \frac{1}{sC_1}$  at the specific frequency.

(29)

if  $A_0 < \infty$ ,

Let  $V_-$  be the voltage at the negative input terminal of the opamp.

By KCL,

$$\frac{V_{in} - V_-}{R_1 \parallel \frac{1}{sC_1}} = - \frac{V_{out} - V_-}{R_2 \parallel \frac{1}{sC_2}}$$

$$V_{out} = -A_0 V_-$$

$$\frac{V_{in} + \frac{V_{out}}{A_0}}{R_1 \parallel \frac{1}{sC_1}} = - \frac{V_{out} + \frac{V_{out}}{A_0}}{R_2 \parallel \frac{1}{sC_2}}$$

$$V_{in} = - \left[ R_1 \parallel \frac{1}{sC_1} \right] \left[ \frac{\left( R_2 \parallel \frac{1}{sC_2} \right) \frac{V_{out}}{A_0} + V_{out} + \frac{V_{out}}{A_0}}{R_2 \parallel \frac{1}{sC_2}} \right]$$

$$\therefore \frac{V_{out}}{V_{in}} = - \frac{R_2 \parallel \frac{1}{sC_2}}{R_1 \parallel \frac{1}{sC_1}} \left[ \frac{A_0}{(A_0 + 1) + \left( R_2 \parallel \frac{1}{sC_2} \right)} \right]$$

To see  $\left| \frac{V_{out}}{V_{in}} \right| = 1$ ,

Let  $x = R_1 \parallel \frac{1}{sC_1}$  and  $y = R_2 \parallel \frac{1}{sC_2}$ .

$$\therefore \text{For } \left| \frac{V_{out}}{V_{in}} \right| = 1, \quad y A_0 = x \left[ (A_0 + 1) + y \right]$$

$$y (A_0 - 1) = x (A_0 + 1)$$

(29) Cont'd

$$\therefore \frac{x}{y} = \frac{A_0 + 1}{A_0 - 1},$$

ie. we need to set  $\frac{R_1 // \frac{1}{sC_1}}{R_2 // \frac{1}{sC_2}} = \frac{A_0 + 1}{A_0 - 1}$ .

Since  $A_0$  is generally rather large,

$\frac{A_0 + 1}{A_0 - 1}$  is a rational fraction,  
in which the numerator and the  
denominator are large, and differ  
by a small amount.

(e.g. if  $A_0 = 1000$ ,  $\frac{A_0 + 1}{A_0 - 1} = \frac{1001}{999}$ )

Hence, setting  $\left| \frac{V_{out}}{V_{in}} \right|$  to unity is possible  
in principle, although it would be rather  
difficult to precisely control  $A_0$ .


30

From eq. (8.63),

$$V_{out} = -R_F \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

$$\therefore R_1 = R_2,$$
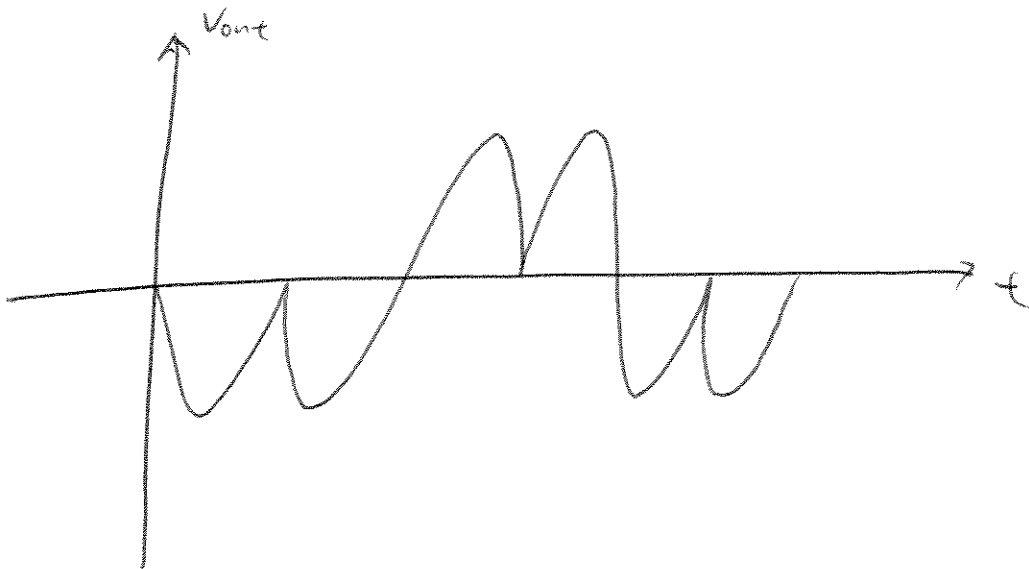
$$V_{out} = -\frac{R_F}{R_1} (V_1 + V_2)$$



(31) - By KCL,

$$\frac{V_1 - V_x}{R_1} + \frac{V_2 - V_x}{R_2} = - \frac{V_{out} - V_x}{R_F}$$

$$\therefore V_{out} = -A_o V_x$$

$$V_x = - \frac{V_{out}}{A_o}$$

$$\left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right) + \frac{V_{out}}{A_o} \left( \frac{1}{R_2} + \frac{1}{R_1} + \frac{1}{R_F} \right) = - \frac{V_{out}}{R_F}$$

$$- \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right) = V_{out} \left[ \frac{1}{R_F} + \frac{1}{A_o} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_F} \right) \right]$$

$$\therefore V_{out} = - \left( \frac{1}{R_F} + \frac{1}{A_o} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_F} \right) \right)^{-1} \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$



32 For  $A_0 = \infty$ ,

$$V_+ = V_- = 0,$$

$\therefore$  No current flows through  $R_F$ ,  
 $\therefore$  No effect due to  $R_F$

$$V_{out} = -R_F \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right) //$$

For  $A_0 \neq \infty$ ,

By KCL


$$\frac{V_1 - V_x}{R_1} + \frac{V_2 - V_x}{R_2} - \frac{V_x}{R_F} = - \frac{V_{out} - V_x}{R_F}$$

$$\therefore V_x = \frac{-V_{out}}{A_0}$$

$$\left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right) + \frac{V_{out}}{A_0} \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_F} + \frac{1}{R_F} \right] = - \frac{V_{out}}{R_F}$$

$$V_{out} = - \left[ \frac{1}{R_F} + \frac{1}{A_0} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_F} + \frac{1}{R_F} \right) \right]^{-1} \\ \times \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right) //$$

33

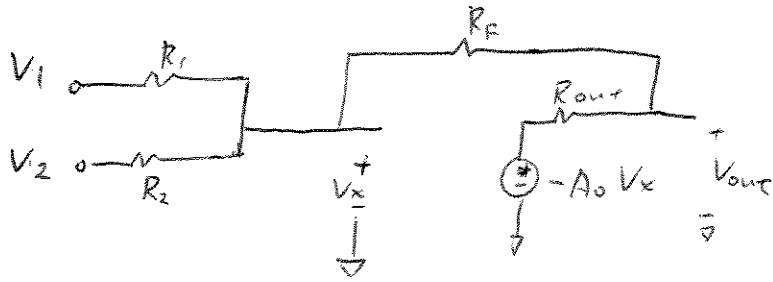

By KCL,

$$\frac{V_1 - V_x}{R_1} + \frac{V_2 - V_x}{R_2} = \frac{V_x (A_0 + 1)}{R_F + R_{out}}$$

$$\left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right) = V_x \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{A_0 + 1}{R_F + R_{out}} \right]$$


$$\begin{aligned} \therefore V_{out} &= (-A_0 V_x - V_x) \frac{R_F}{R_F + R_{out}} \\ &= -V_x (1 + A_0) \frac{R_F}{R_F + R_{out}} \end{aligned}$$

$$\therefore \frac{V_1}{R_1} + \frac{V_2}{R_2} = - \frac{R_F + R_{out}}{R_F (A_0 + 1)} \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{A_0 + 1}{R_F + R_{out}} \right] V_{out}$$

$$V_{out} = - \frac{R_F (A_0 + 1)}{R_F + R_{out}} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{A_0 + 1}{R_F + R_{out}} \right)^{-1}$$

$$\times \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right) //$$

(34)

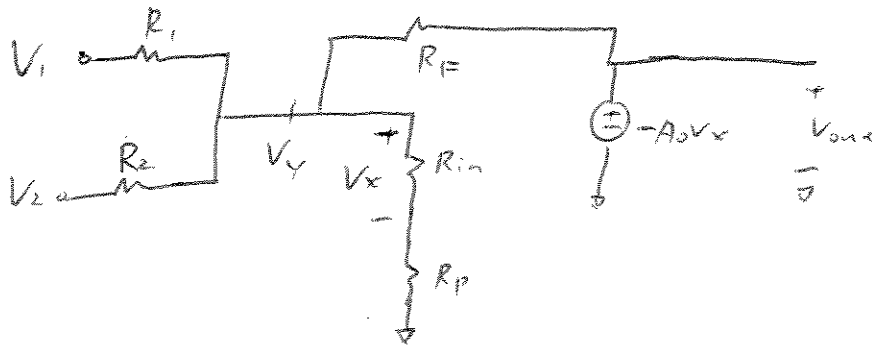

By KCL,

$$\frac{V_1 - V_y}{R_1} + \frac{V_2 - V_y}{R_2} = \frac{V_y + A_0 V_x}{R_F} + \frac{V_y}{R_{in} + R_P}$$

Using voltage divider,

$$V_x = V_y \frac{R_{in}}{R_{in} + R_P}$$

$$V_y = \frac{R_{in} + R_P}{R_P} V_x$$

$$\therefore \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right) = V_y \left( \frac{1}{R_F} + \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_{in} + R_P} \right) + \frac{A_0 V_x}{R_F}$$

$$= \left[ \left( \frac{R_{in} + R_P}{R_P} \right) \left( \frac{1}{R_F} + \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_{in} + R_P} \right) + \frac{A_0}{R_F} \right] \times V_x$$

$$\therefore V_{out} = -A_0 V_x$$

$$\therefore \frac{V_1}{R_1} + \frac{V_2}{R_2} = - \left( \frac{V_{out}}{A_0} \right) \left[ \left( \frac{R_{in} + R_P}{R_P} \right) \left( \frac{1}{R_F} + \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_{in} + R_P} \right) + \frac{A_0}{R_F} \right]$$


$$V_{out} = -A_0 \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right) \times \left[ \left( \frac{R_{in} + R_P}{R_P} \right) \left( \frac{1}{R_F} + \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_{in} + R_P} \right) + \frac{A_0}{R_F} \right]^{-1}$$

35 When  $D_1$  is on, (i.e. when  $V_{in} > 0$ )

$$V_{out} = V_{in} = I_{D_1} R_1,$$

$$\therefore I_{D_1} = \frac{V_{in}}{R_1}$$

When  $D_1$  is off,  $I_{D_1} = 0$ .

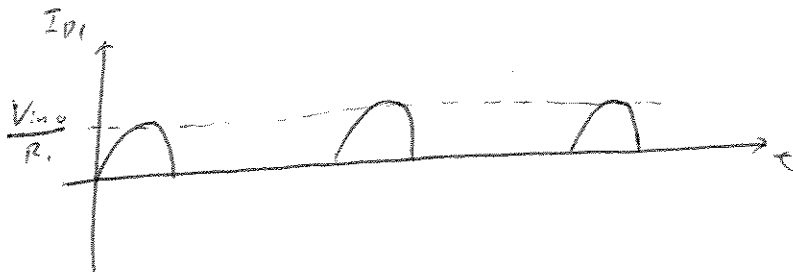


(36) D. is on when  $V_{in} > 0$ ,





$$V_x = 0$$

By KCL ;

$$I_{D1} = \frac{V_{in}}{R_1}$$

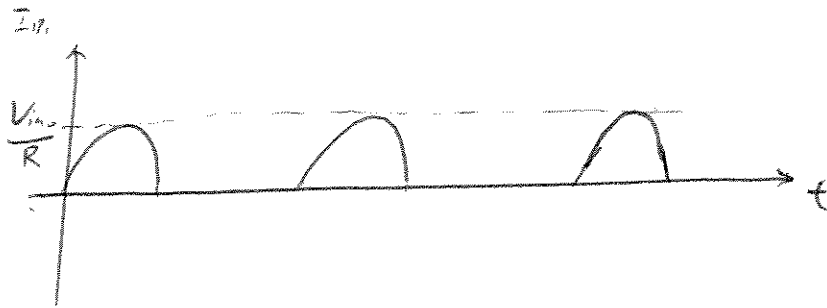

37

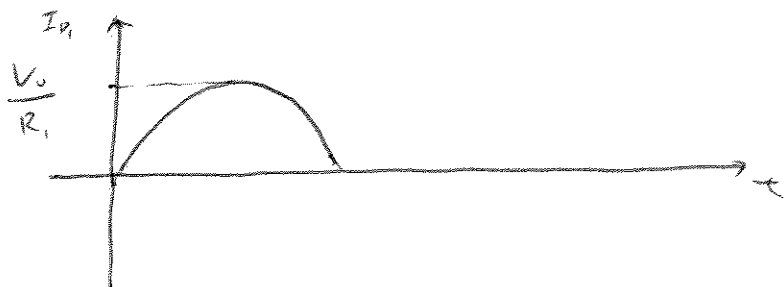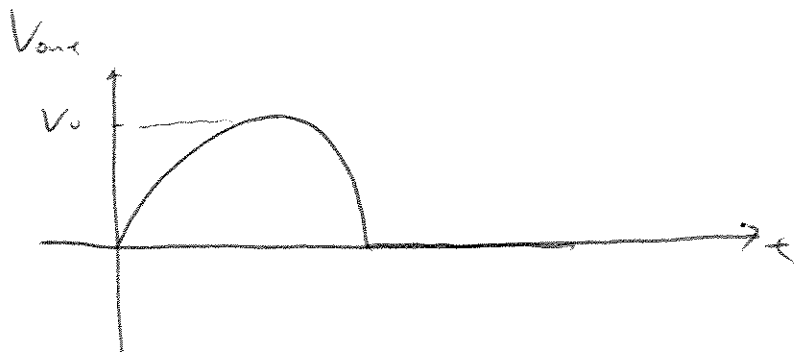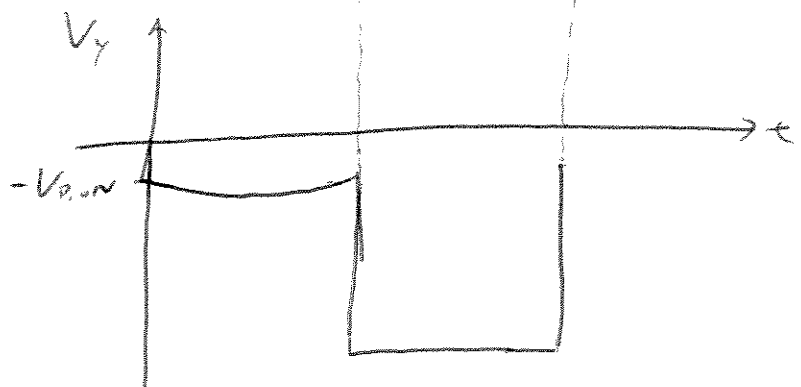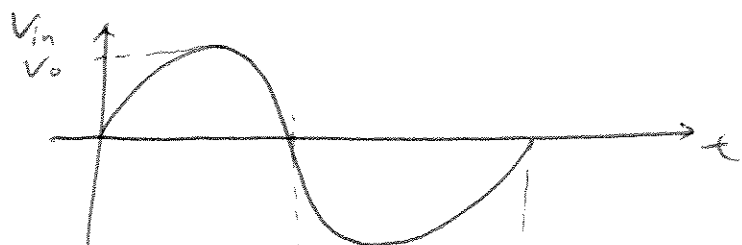

38

$\therefore R_{D, on} \ll R_p$

$\therefore$  when diode is on,  $R_p$  has no effect.


(diode "shorts" nodes X and Y)

when diode is off,  $R_p$  functions as a feedback resistor,

$$\therefore \frac{V_y}{V_{in}} = 1 + \frac{R_1}{R_p}$$


and  $V_{in} = V_{out}$ .

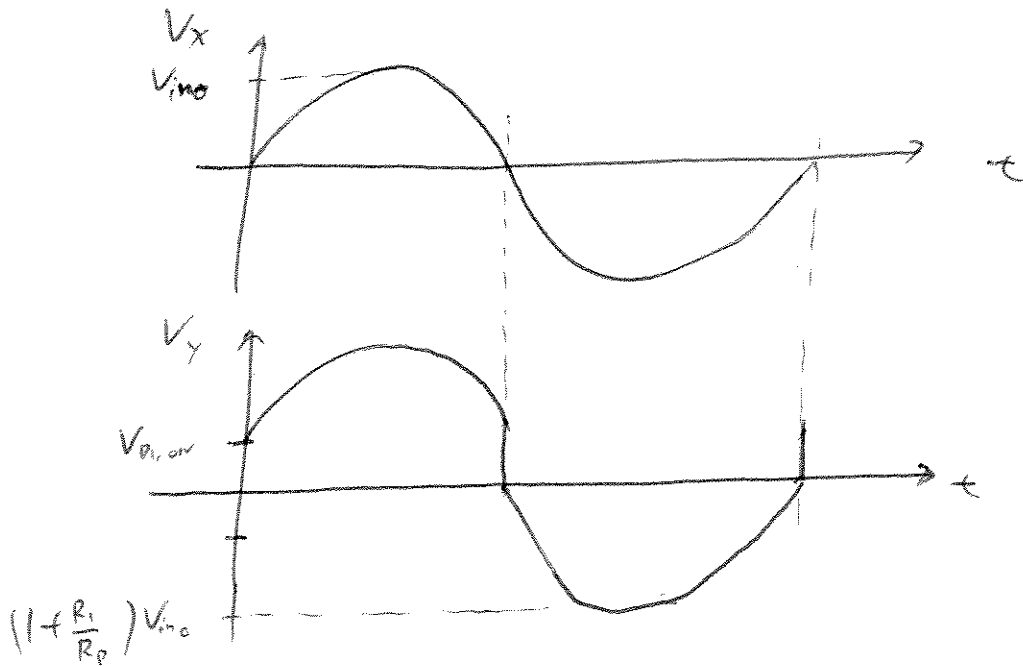$\therefore V_x = V_{in}$  for both  $D_1$  is on and off.




39

Connecting a diode as below:

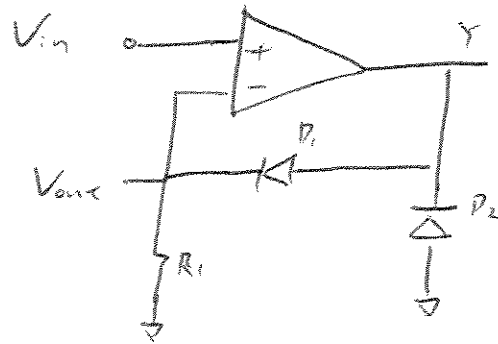

$D_2$  allows the parasitic capacitance to charge up faster, right before  $D_1$  conducts.

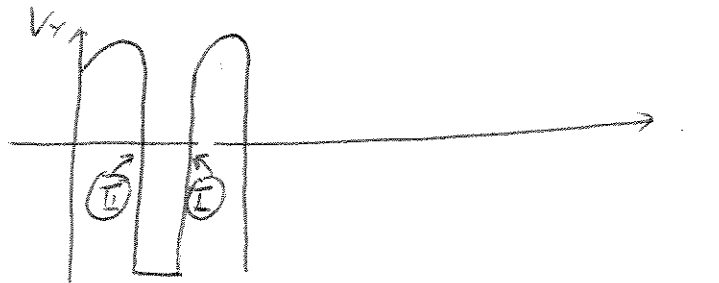
This corresponds to sharpening the transition (I) of  $V_Y$ , as shown below



But it will not speed up transition (II).  
(which is not critical)



(40)

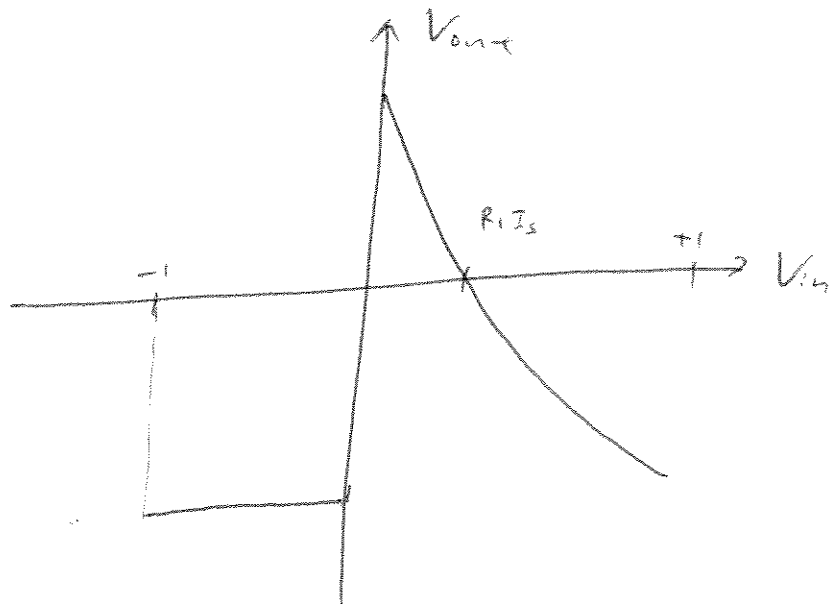

④ By KCL,

$$\frac{V_{in} - V_x}{R_1} = I_{R_1}$$

$$\therefore V_{BE} = V_T \ln \frac{V_{in} - V_x}{R_1 I_s}$$

$$= -V_{out}$$

$$\therefore -A_o V_x = V_{out}$$

$$V_x = -\frac{V_{out}}{A_o}$$

$$\therefore V_{out} = -V_T \ln \frac{V_{in} + \frac{V_{out}}{A_o}}{R_1 I_s}$$



(42). This circuit will not function as a non-inverting opamp:

assuming  $A_0 = \infty$ ,


$$V_+ \approx V_- = V_{in}$$

$$\therefore V_{BE} = V_T \ln \frac{-V_{in}}{R_1 I_S}$$

$$\therefore V_{out} = -V_{BE}$$

$$V_{out} = -V_T \ln \frac{-V_{in}}{R_1 I_S}$$

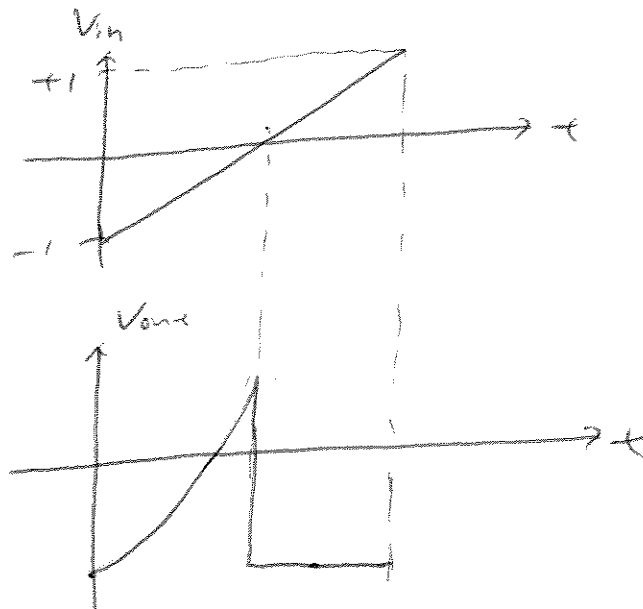
For example, as  $V_{in}$  varies from  $-1V$  to  $+1V$ :



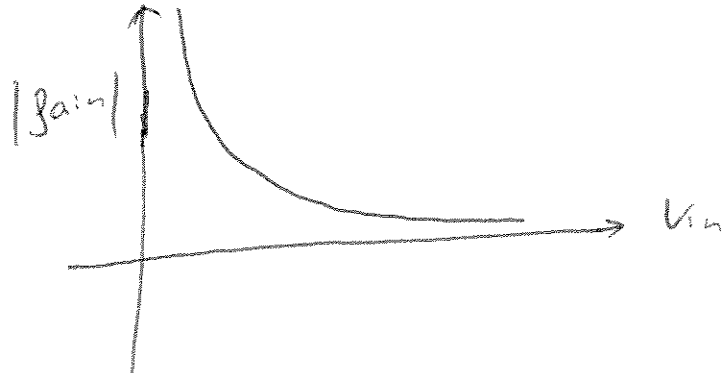(43)

$$V_{out} = -V_T / n \frac{V_{in}}{R_i I_s}$$

$$\frac{dV_{out}}{dV_{in}} = -\frac{V_T}{V_{in}}$$



The gain is compressive, because as  $V_{in}$  increases, the magnitude of the gain decreases.

44 Set  $V_{out} = -0.5V$  when  $V_{in} = 1V$

$$-0.5 = -V_T \ln \frac{1}{R_1 I_S}$$

$$\therefore R_1 I_S = 2.0612 \times 10^{-9}$$

When  $V_{in} = 10V$ ,

$$V_{out} = -V_T \ln \frac{10}{2.0612 \times 10^{-9}}$$

$$= -0.558V > -1V.$$

$\therefore$  setting  $R_1 I_S = 2.0612 \times 10^{-9}$  meets the specification.

$$\text{choose } I_S = 1 \times 10^{-16} A.$$

$$R_1 = 20.61 \text{ M}\Omega //$$

45

Assume  $A_0 = \infty$ ,

$$I_{R_1} = \frac{V_{in} - V_{TH}}{R_1}$$

$$= \frac{1}{2} k' (V_{GS} - V_{TH})^2$$

where  $k' = \frac{W}{L} C_{ox} \mu_n$

$$\therefore V_{GS} = -V_{out}$$

$$\therefore \frac{1}{2} k' (-V_{out} - V_{TH})^2 = \frac{V_{in} - V_{TH}}{R_1}$$

$$(-V_{out} - V_{TH})^2 = \frac{2(V_{in} - V_{TH})}{k' R_1}$$

$$(-V_{out} - V_{TH}) = \sqrt{\frac{2(V_{in} - V_{TH})}{k' R_1}}$$

$$V_{out} = -\sqrt{\frac{2(V_{in} - V_{TH})}{k' R_1}} - V_{TH}$$

$$\text{small signal gain} = -\frac{d}{dV_{in}} \sqrt{\frac{2(V_{in} - V_{TH})}{k' R_1}}$$

$$= \frac{1}{k' R_1} \sqrt{\frac{k' R_1}{2(V_{in} - V_{TH})}}$$

$$= \sqrt{\frac{1}{2k' R_1 (V_{in} - V_{TH})}}$$

46

By KCL,

$$\frac{V_x - V_{in}}{R_1} = I_{sp, m_1}$$

Assume  $A_0 = \infty$ ,  $\therefore V_x = V_+ = 0V$ .

$$\therefore -\frac{V_{in}}{R_1} = \frac{1}{2} k' (V_{GS} - |V_{TH}|)^2$$

where  $k' = \mu_p \frac{W}{L} C_{ox}$ .

$$\therefore V_x = -V_{out}$$

$$\therefore -\frac{V_{in}}{R_1} = \frac{1}{2} k' (-V_{out} - |V_{TH}|)^2$$

$$-\frac{2V_{in}}{R_1 k'} = (V_{out} + |V_{TH}|)^2$$

$$\therefore V_{out} = \sqrt{-\frac{2V_{in}}{R_1 k'}} - |V_{TH}|$$

(47)

Assume  $A_o = \infty$ ,

$$\therefore V_+ = V_- = V_{in}$$

Using voltage divider:

$$V_{in} + V_{os} = V_{out} \frac{R_1}{R_1 + R_2}$$

$$V_{out} = \left( 1 + \frac{R_2}{R_1} \right) (V_{in} + V_{os}) //$$



(48)

In Fig (8.25),


Assuming input is zero,

$$\begin{aligned}V_x &= 10 \times V_{os, A_1} \\ &= 30 \text{ mV}\end{aligned}$$

$$\begin{aligned}\therefore V_{out} &= 10 \times (V_{os, A_2} + V_x) \\ &= 330 \text{ mV}\end{aligned}$$

Thus, the maximum offset error is 330 mV.

(49)

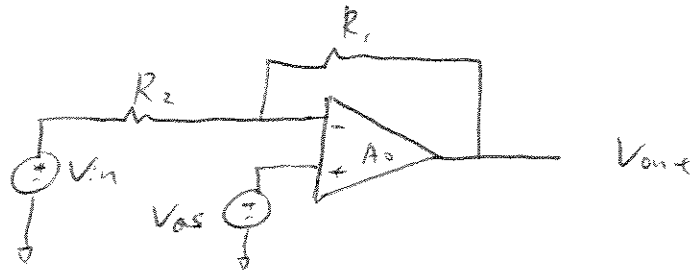

By KCL,

$$\frac{V_{in} - V_{os}}{R_2} = - \frac{V_{out} - V_{os}}{R_1}$$

$$V_{out} = - \frac{R_1}{R_2} (V_{in} - V_{os}) + \underline{\underline{V_{os}}}$$

(50) By eqn (8.72)

$$V_{out} = V_{os} \left( 1 + \frac{R_2}{R_1} \right)$$

$$\therefore 20 \text{ mV} = 3 \text{ mV} \left( 1 + \frac{R_2}{R_1} \right)$$

$$\frac{17}{3} = \frac{R_2}{R_1} \quad \text{--- (1)}$$

$$\therefore \frac{1}{R_2 C_1} \ll 2\pi (1000)$$

and setting  $C_1 = 100 \text{ pF}$ ,

$$\frac{1}{R_2 \times 100 \times 10^{-12}} \ll 2\pi (1000)$$

$$\frac{1}{R_2} \ll 6.283 \times 10^{-7}$$

$$\therefore R_2 \gg 1.59 \text{ M}\Omega$$

choose  $R_2 = 17 \text{ M}\Omega //$

$R_1 = 3 \text{ M}\Omega //$  (From (1))

(51) From eqn (8.44),

$$V_{out} \propto \frac{dV_{in}}{dt}$$

(proportional)

Since offset is static (invariant with time)

$$\text{i.e. } \frac{dV_{os}}{dt} = 0.$$

$\therefore$  offset has no effect to  $V_{out}$ .

(52) From eqn (8.60),

with the presence of offset ( $V_{os}$ ),

$$V_{out} = -V_T \ln \frac{V_{in} + V_{os}}{R \cdot I_s}$$

The effect of offset to  $V_{out}$  is very small, because  $V_{out}$  is proportional to the log. of  $(V_{in} + V_{os})$ .

Thus,  $V_{out}$  is very insensitive to the magnitude of the offset.

(53). From eqn (8.76),

$$V_{out} = R_1 I_{B2}$$


∴  $V_{out}$  is independent of  $I_{B1}$

Also  $I_{B1}$  will not affect  $\frac{V_{out}}{V_{in}}$ .

Thus, the small offset ( $\Delta I$ ) in the input bias currents has no effect on  $V_{out}$ .


54 Using superposition:

(I) turn off  $I_{B1}$ :

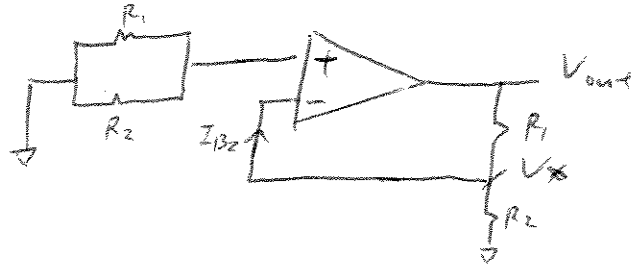


$$\therefore V_+ = V_- = 0, \quad \therefore V_x = 0,$$

The circuit becomes:

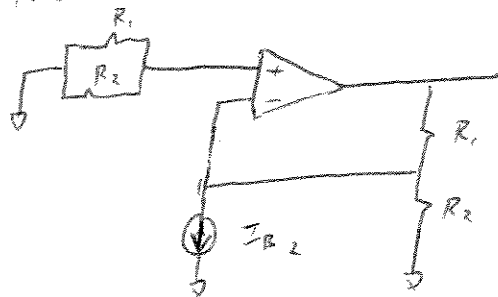

$$\therefore \text{From eqn (8.76), } V_{out, I} = -R_1 I_{B2}$$

(II) turn off  $I_{B2}$ :

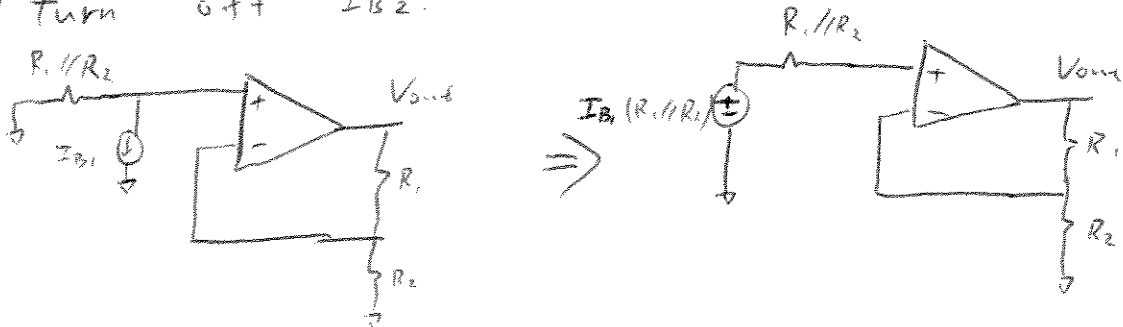

$$\begin{aligned} \therefore V_{out, I_{B1}} &= I_{B1} \left( \frac{R_1 R_2}{R_1 + R_2} \right) \times \left( 1 + \frac{R_1}{R_2} \right) \\ &= I_{B1} R_1 \end{aligned}$$

(54) cont'd

$\therefore$  given  $I_{B1} - I_{B2} = \Delta I$ , and  $V_{out} = I_{B1} + I_{B2}$ ,

$$I_{B1} R_1 - I_{B2} R_1 < \Delta V$$

$$\Delta I R_1 < \Delta V$$

$$\therefore R_1 < \frac{\Delta V}{\Delta I}$$

There is no dependence of output error on  $R_2$ .



(55) Using eqn. (8.84)

$$\text{Gain} = \frac{A_0}{1 + \frac{S}{\omega_c}}$$

For opamp (a); At 100 MHz:

$$\text{Gain}_{(a)} = \frac{1000}{1 + \frac{2\pi \times 100 \times 10^6}{2\pi \times 50}}$$

$$\approx 5 \times 10^{-4}$$


For opamp (b) at 100 MHz,

$$\text{Gain}_{(b)} = \frac{500}{1 + \frac{2\pi \times 100 \times 10^6}{2\pi \times 10}}$$

$$\approx 4.95 > 4$$

$\therefore$  opamp (b) is a possible candidate

(56)

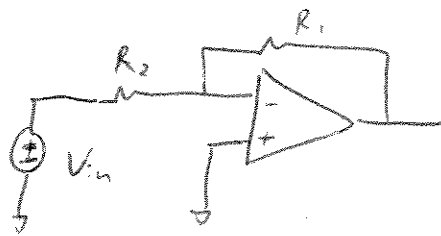

Using eq. (8.20),

$$\frac{V_{out}}{V_{in}} = - \frac{R_2}{R_1} + \frac{1}{A_0} \left(1 + \frac{R_2}{R_1}\right)$$

Here,  $A_0$  becomes  $\frac{A_0}{1 + \frac{s}{\omega_1}}$ ,

$$\begin{aligned} \therefore \frac{V_{out}}{V_{in}} &= \frac{-1}{\frac{R_2}{R_1} + \frac{A_0}{1 + \frac{s}{\omega_1}} \left(1 + \frac{R_2}{R_1}\right)} \\ &= \frac{- \left(1 + \frac{s}{\omega_1}\right)}{\left(1 + \frac{s}{\omega_1}\right) \frac{R_2}{R_1} + A_0 \left(1 + \frac{R_2}{R_1}\right)} \end{aligned}$$


To find the pole, equate denominator to 0.

$$\text{i.e. } \left(1 + \frac{s}{\omega_1}\right) \frac{R_2}{R_1} + A_0 \left(1 + \frac{R_2}{R_1}\right) = 0$$

$$\left(1 + \frac{s}{\omega_1}\right) = - \frac{R_1}{R_2} A_0 \left(1 + \frac{R_2}{R_1}\right)$$

$$\therefore |W_{p, closed}| = \left(1 + \frac{R_1}{R_2} A_0 \left(1 + \frac{R_2}{R_1}\right)\right) \omega_1$$

57.

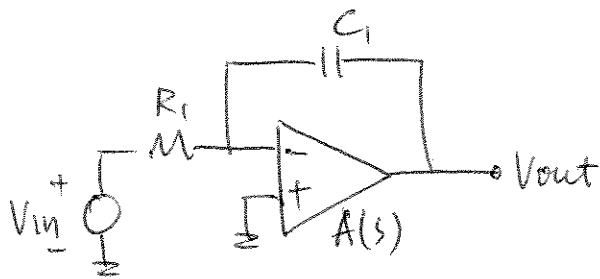

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_0}}$$

$$\omega_0 \gg \frac{1}{RC_f}$$


$$\frac{V_{in} - V(-)}{R_i} = (V(-) - V_{out}) s C_f$$

$$-V(-) \times A(s) = V_{out}$$

Substitute (2) into (1):

$$\begin{aligned} \frac{V_{out}}{V_{in}}(s) &= - \left[ \frac{s C_f R_i + 1}{A(s)} + s C_f R_i \right]^{-1} \\ &= - \left[ \frac{(s C_f R_i + 1) \left(1 + \frac{s}{\omega_0}\right)}{A_0} + s C_f R_i \right]^{-1} \\ &\approx \left\{ \frac{1}{A_0 \omega_0} \left[ s \omega_0 C_f R_i + s^2 C_f R_i + s \right] + s C_f R_i \right\}^{-1} \\ &\approx - \left[ s \left( C_f R_i + \frac{1}{A_0 \omega_0} \right) + s^2 \left( \frac{C_f R_i}{A_0 \omega_0} \right) \right]^{-1} \\ &\approx - \left[ s C_f R_i + s^2 \frac{C_f R_i}{A_0 \omega_0} \right]^{-1} \\ &= \frac{-1}{\left(1 + \frac{s}{A_0 \omega_0}\right) \left(\frac{1}{RC_f}\right)} \end{aligned}$$

58.

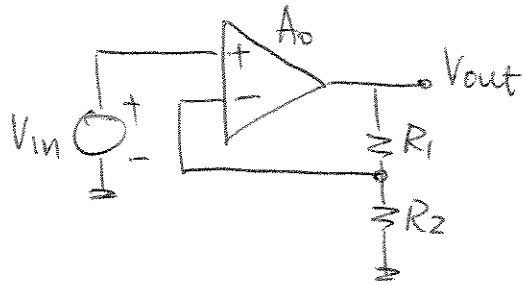

Nominal gain = 4  
Slew Rate = 1V/ns

$V_p = 0.5\text{ V}$

$$V_{in}(t) = 0.5 \sin \omega t \Rightarrow V_{out} = 0.5 \times \overbrace{\left(1 + \frac{R_1}{R_2}\right)}^{=4} \sin \omega t.$$

$$\frac{dV_{out}}{dt} = 0.5 \left(1 + \frac{R_1}{R_2}\right) \omega \cdot \cos \omega t.$$


= Maximum when  $\cos \omega t = 1$

$$\Rightarrow \left. \frac{dV_{out}}{dt} \right|_{\max} = 0.5 \omega \left(1 + \frac{R_1}{R_2}\right) = 2 \omega$$

$\therefore$  Highest frequency  $\Rightarrow 2 \omega = 1\text{ V/ns}$


$$\Rightarrow \omega = 0.5 \text{ rad/ns} \Rightarrow f_{\max} \approx 79.6 \text{ MHz}$$

59.

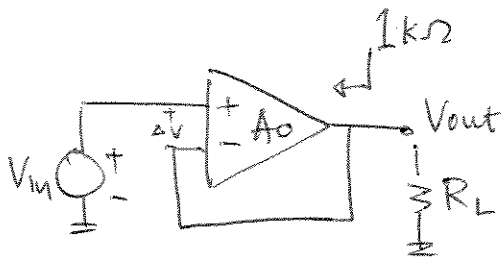

$R_L = 100 \Omega$   
Gain Error = 0.5%
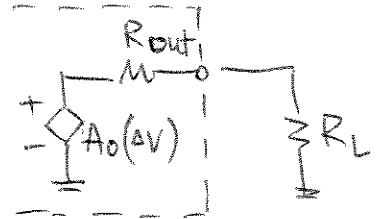
$$(V_{in} - V_{out}) A_0 \times \frac{R_L}{R_{out} + R_L} = V_{out}$$



$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{1}{1 + \frac{R_{out} + R_L}{A_0 R_L}} \approx 1 - \underbrace{\frac{R_{out} + R_L}{A_0 R_L}}_{= \epsilon}$$


$$\therefore \epsilon = \frac{R_{out} + R_L}{A_0 R_L} \Rightarrow A_0 = \frac{R_{out} + R_L}{\epsilon R_L} = \frac{1000 + 100}{0.5\% \times 100} \approx 2200$$

60.

Nominal Gain = 4

Gain Error = 0.2%

$$R_1 + R_2 = 20 \text{ k}\Omega$$

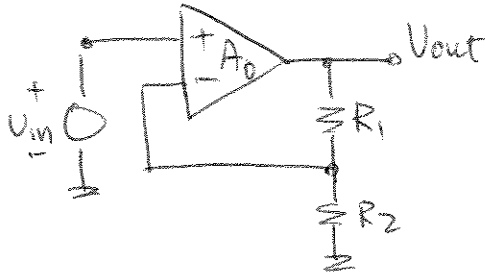

$$\left[ V_{in} - \frac{R_2}{R_1 + R_2} \times V_{out} \right] A_0 = V_{out}$$


$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{A_0}{1 + \frac{R_2}{R_1 + R_2} A_0} \approx \left( 1 + \frac{R_1}{R_2} \right) \left[ 1 - \left( 1 + \frac{R_1}{R_2} \right) \frac{1}{A_0} \right]$$

$$\left( 1 + \frac{R_1}{R_2} \right) = 4 \quad \& \quad (R_1 + R_2) = 20 \text{ k}\Omega$$

$$\Rightarrow R_1 = 15 \text{ k}\Omega, \quad R_2 = 5 \text{ k}\Omega.$$

$$0.2\% = \left( 1 + \frac{R_1}{R_2} \right) \frac{1}{A_0} \Rightarrow A_0 = \left( 1 + \frac{R_1}{R_2} \right) \times \frac{1}{0.2\%}$$
$$= 2000$$

b1.

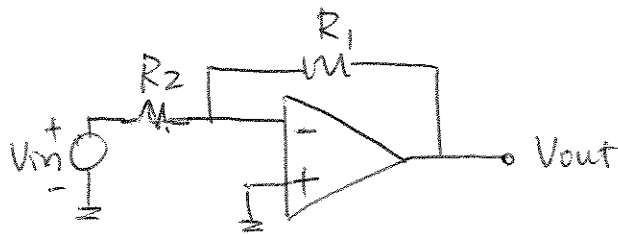

Nominal gain = 8  
 Gain Error = 0.1%  
 $R_{out} = 0.1\%$

$$V_x = V_{in} + (V_{out} - V_{in}) \frac{R_2}{R_1 + R_2} \quad \text{--- (1)}$$

$$\frac{V_{out} - V_{in}}{R_1 + R_2} = \frac{-A_o V_x - V_{out}}{R_{out}} \quad \text{--- (2)}$$

Substitute (2) into (1) gives:

$$\frac{V_{out}}{V_{in}} = \left(-\frac{R_1}{R_2}\right) \frac{A_o - R_{out}/R_1}{\underbrace{1 + \frac{R_{out}}{R_2} + A_o + \frac{R_1}{R_2}}_{(1-\epsilon)}}$$


$$\Rightarrow 8 = R_1/R_2$$

$$0.1\% = 1 - \frac{A_o - 100/R_1}{1 + \frac{100}{R_2} + A_o + (8)}$$

$\Rightarrow$  Choose  $R_1 = 8\text{ k}\Omega$ ,  $R_2 = 1\text{ k}\Omega$

$\Rightarrow A_o \approx 9100$

62.

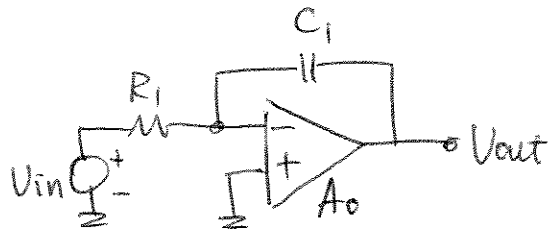

$$= 100 \text{ kHz}$$

$$\text{pole} = 100 \text{ Hz}$$

$$C_{\text{MAX}} = 50 \text{ pF.}$$

$$\frac{V_{in} - V_{(-)}}{R_1} = (V_{(-)} - V_{out}) \leq C_1 \quad \text{--- (1)}$$

$$V_{(-)} \cdot (-A_0) = V_{out} \quad \text{--- (2)}$$

Substitute (2) into (1):

$$\frac{V_{out}}{V_{in}} = \frac{-1}{\frac{1}{A_0} + (1 + \frac{1}{A_0}) R_1 C_1 s}$$

$$\Rightarrow s_p = \frac{-1}{(A_0 + 1) R_1 C_1} = -100 \text{ Hz} \quad \text{--- (1)}$$

Attenuation above 100 kHz  $\Rightarrow \left| \frac{V_{out}}{V_{in}} \right|_{100 \text{ kHz}} = 1$


$$\Rightarrow \frac{A_0}{\sqrt{1 + [(A_0 + 1) R_1 C_1 \omega] ^2}} \Big|_{100 \text{ kHz}} = 1 \quad \text{--- (2)}$$

Substitute (1) into (2):

$$\Rightarrow A_0 \approx 1000. \quad \text{Choose } C = 50 \text{ pF} \Rightarrow R \approx 200 \text{ k}\Omega.$$



63.

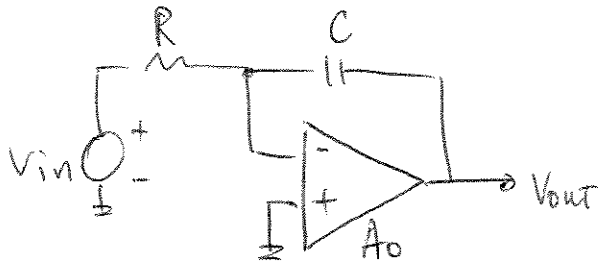

$$V(t) = \alpha t$$


$$0 < V(t) < V_0$$

$$\text{where } \alpha = 10 \text{ V}/\mu\text{s}$$

$$V_0 = 1 \text{ V}$$

$$C_{\text{max}} = 20 \text{ pF}$$

$$\text{Error} < 0.1\%$$

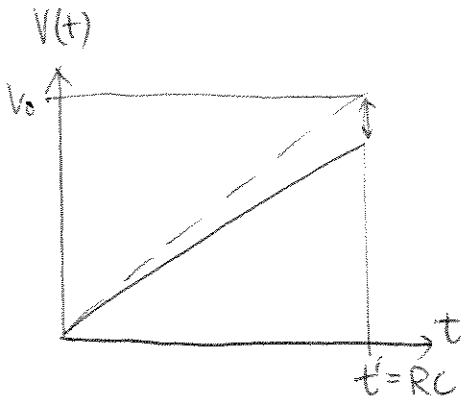

$$V_{\text{out}}(t) = -\frac{V_0}{RC} t, \quad t \in [0, RC]$$

$$V(t) = \alpha t$$

$$\text{At } t = RC, \quad \frac{\Delta V}{V_0} = \frac{V_{\text{out}}(t) - V(t)}{V_0} \Bigg|_{t=RC} < 0.1\%$$


$$\Rightarrow \Delta V = V_0 \times 0.1\% = 0.001 \text{ V}$$

$$\Rightarrow -\frac{V_0}{RC} \times t + \alpha t \Bigg|_{t=RC} = 0.001 \text{ V } (= \Delta V)$$

Choose  $C = 20 \text{ pF}$

$$\therefore R = \frac{V_0 - \Delta V}{\alpha C} = \frac{1 \text{ V} - 0.001 \text{ V}}{10 \text{ V}/\mu\text{s} \times 20 \text{ pF}} = 4995 \Omega$$

64.

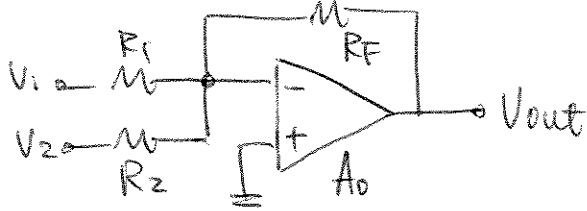

$$V_{out} = \alpha_1 V_1 + \alpha_2 V_2$$

$\uparrow$                      $\uparrow$   
 0.5                    1.5

Error of  $\alpha \leq 0.5\%$   
 $r_{in} \geq 10 \text{ k}\Omega$ .

$$\frac{V_1 - V(-)}{R_1} + \frac{V_2 - V(-)}{R_2} = \frac{V(-) - V_{out}}{R_F} \quad \text{--- (1)}$$

$$V(-) \cdot (-A_0) = V_{out} \quad \text{--- (2)}$$

Substitute (2) into (1) & solve for  $V_{out}$ :

$$V_{out} = - \left( \frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 \right) \cdot \left[ \frac{1}{A_0} \left( \frac{R_F}{R_1} + \frac{R_F}{R_2} + 1 \right) + 1 \right]^{-1}$$


$$\approx - \left( \frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 \right) \cdot \left[ 1 - \frac{1}{A_0} \left( \frac{R_F}{R_1} + \frac{R_F}{R_2} + 1 \right) \right]$$

Choose  $r_{in, V_2} (\approx R_2) = 10 \text{ k}\Omega \Rightarrow R_F = \alpha_2 \times R_2 = 15 \text{ k}\Omega$   
 $\Rightarrow R_1 = R_F / \alpha_1 = 30 \text{ k}\Omega$   
 $\approx r_{in, V_1}$

$$\Rightarrow \epsilon = 0.5\% = \frac{1}{A_0} \left( \frac{R_F}{R_1} + \frac{R_F}{R_2} + 1 \right)$$

$$\Rightarrow A_0 = \frac{1}{0.5\%} (0.5 + 1.5 + 1) = 600 \quad (\text{or larger})$$

65.

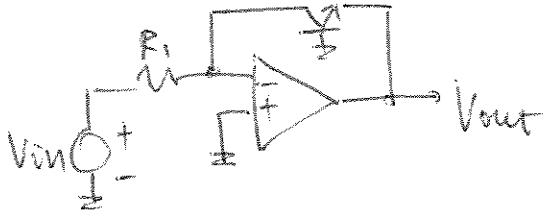

$$[0.1, 2] \text{ V} \mapsto [-0.5, -1] \text{ V}$$

$$V_{out} = -V_T \ln \frac{V_{in}}{I_s R_i}$$

$$-0.5 \text{ V} = -V_T \ln \left[ \frac{(0.1)}{I_s R_i} \right] \Rightarrow I_s R_i = 4.45 \cdot 10^{-10} \text{ V} \quad \text{--- (1)}$$

$$\Rightarrow -V_T \ln \left( \frac{2}{I_s R_i} \right) = -0.026 \text{ V} \ln \left( \frac{2}{4.45 \cdot 10^{-10}} \right) \approx -0.58 \text{ V}$$

∴ input range of  $0.1 \leftrightarrow 2 \text{ V}$  corresponds to output range of  $-0.5 \leftrightarrow -0.58 \text{ V}$

$$\text{Choose } I_s = 1 \times 10^{-16} \text{ A} \Rightarrow R_i = 4.45 \text{ M}\Omega.$$

(6b) No, this is not possible to meet requirements.

$$\frac{\Delta V_{out}}{\Delta V_{in}} = \frac{V_T}{V_{in}}$$


Assuming temperature is fixed,  $V_T$  is a fixed quantity that is both process and design independent.

At  $25^\circ\text{C}$ ,  $V_T \approx 25\text{mV}$ .

$$\therefore \left. \frac{\Delta V_{out}}{\Delta V_{in}} \right|_{V_{in}=1\text{V}} = 25\text{mV/V}$$

$$\left. \frac{\Delta V_{out}}{\Delta V_{in}} \right|_{V_{in}=2\text{V}} = 12.5\text{mV/V}$$

1.

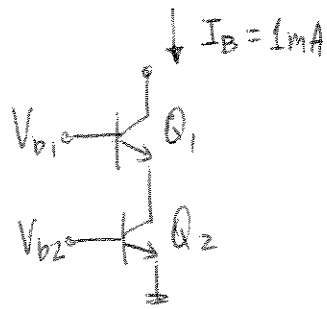

$$I_S = 6 \cdot 10^{-17} \text{ A}$$

$$\beta = 100$$

$$V_A \rightarrow \infty$$

$$V_T = \frac{kT}{q}$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$$(a) \quad V_{b2} = V_T \ln\left(\frac{I_B / \alpha^2}{I_S}\right) = (0.026 \text{ V}) \ln\left(\frac{1.02 \text{ mA}}{6 \cdot 10^{-17} \text{ A}}\right)$$

$$\approx 0.792 \text{ V}$$

(b) From the configuration,


$$V_{b1} = V_{CE2} + V_{BE1} = (V_{BE2} - 300 \text{ mV}) + V_{BE1}$$

$$V_{BE1} = V_T \ln\left(\frac{I_B}{I_S}\right) = (0.026 \text{ V}) \ln\left(\frac{1 \text{ mA}}{6 \cdot 10^{-17} \text{ A}}\right)$$

$$\approx 0.792 \text{ V}$$

$$\therefore V_{b1} = (0.792 - 0.3) + 0.79 = 1.28 \text{ V}$$

2.

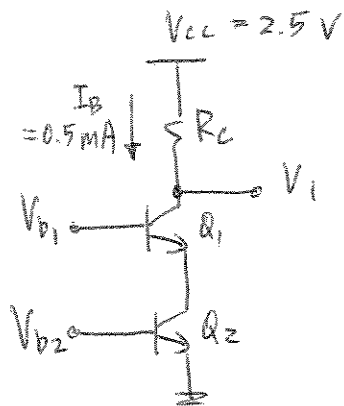

$$(a) \quad V_{b2} = V_{BE2} = V_T \ln\left(\frac{I_B/\alpha^2}{I_s}\right) = (0.026\text{V}) \ln\left(\frac{0.51\text{mA}}{6 \cdot 10^{-17}\text{A}}\right) \\ \approx 0.774\text{V}$$

$$V_{BE1} = V_{b1} - V_{c2} = V_{b1} - (V_{b2} - 300\text{mV})$$


$$\Rightarrow V_{b1} = V_{BE1} + V_{b2} - 0.3\text{V} \\ = (0.026\text{V}) \ln\left(\frac{0.5\text{mA}}{6 \cdot 10^{-17}\text{A}}\right) + (0.774\text{V}) - (0.3\text{V}) \\ \approx 1.25\text{V}$$

$$(b) \quad V_1 = V_{b1} - 0.3\text{V} = 0.95\text{V}$$

$$\therefore R_c = \frac{V_{cc} - V_1}{I_B} = \frac{(2.5 - 0.95)\text{V}}{0.5\text{mA}} \approx 3.1\text{K}\Omega$$

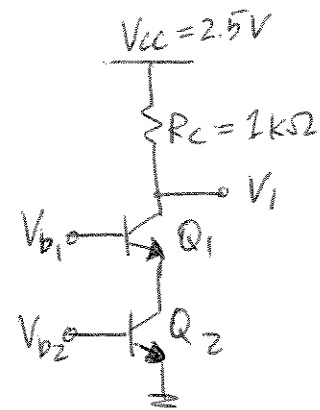3. From previous experience,  
assume both  $V_{BE1}$  &  
 $V_{BE2} = 0.8 \text{ V}$

$$\begin{aligned}\Rightarrow V_1 &= V_{CE1} + V_{CE2} \\ &= (V_{BE1} - 200\text{mV}) + (V_{BE2} - 200\text{mV}) \\ &= 1.2 \text{ V}\end{aligned}$$




\* By KCL, maximum bias current

$$\approx \frac{V_{CC} - V_1}{R_C} = \frac{(2.5 - 1.2) \text{ V}}{1 \text{ k}\Omega} = 1.3 \text{ mA.}$$

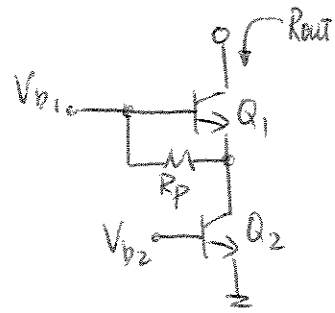
4. (a)  $R_p$  appears in parallel with  $r_{\pi_1}$

$$\therefore R_{out} = [1 + g_{m_1}(r_{o_2} \parallel r_{\pi_1} \parallel R_p)]r_{o_1} + (r_{o_2} \parallel r_{\pi_1} \parallel R_p)$$



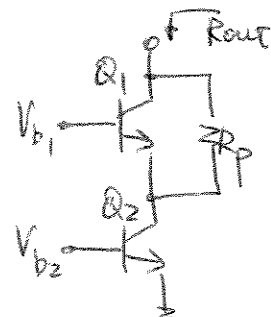
(b)  $R_p$  appears in parallel with  $r_{o_1}$

$$\therefore R_{out} = [1 + g_{m_1}(r_{o_2} \parallel r_{\pi_1})](r_{o_1} \parallel R_p) + (r_{o_2} \parallel r_{\pi_1})$$



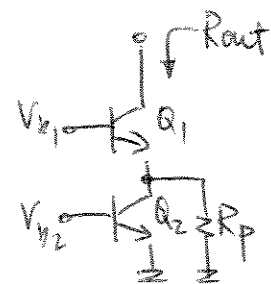
(c)  $R_p$  appears in parallel with  $r_{o_2}$

$$\therefore R_{out} = [1 + g_{m_1}(r_{o_2} \parallel r_{\pi_1} \parallel R_p)]r_{o_1} + (r_{o_2} \parallel r_{\pi_1} \parallel R_p)$$



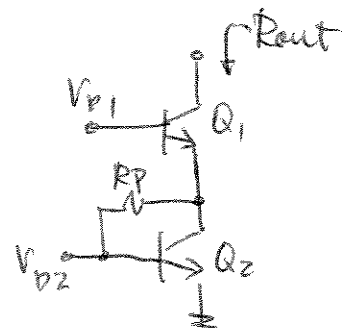
(d)  $R_p$  appears in parallel with  $r_{o_2}$  (in small-signal)  $\therefore V_{b_2}$  is AC GND.

$$\therefore R_{out} = [1 + g_{m_1}(r_{o_2} \parallel r_{\pi_1} \parallel R_p)]r_{o_1} + (r_{o_2} \parallel r_{\pi_1} \parallel R_p)$$





5.

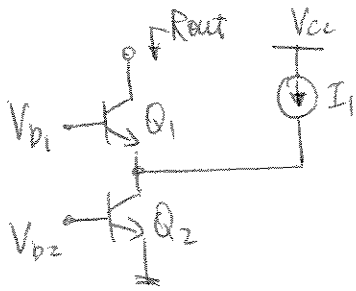

$$I_1 = 0.5 \text{ mA}$$

$$I_{C1} = 0.5 \text{ mA}$$

$$I_{C2} = 1 \text{ mA}$$

$$= 2 I_{C1}$$

$$\beta = 100 \quad V_A = 5 \text{ V}$$

$$R_{out} = g_{m1} r_{o1} (r_{o2} \parallel r_{\pi 1})$$


$$= \frac{I_{C1}}{V_T} \cdot \frac{V_A}{I_{C1}} \cdot \frac{V_{A2}/I_{C2} \cdot \beta V_T / I_{C1}}{V_{A2}/I_{C2} + \beta V_T / I_{C1}}$$

$$= \frac{V_A}{V_T} \cdot \frac{V_{A2}/2}{I_{C1}} \cdot \frac{\beta V_T / I_{C1}}{\frac{V_{A2}/2}{I_{C1}} + \beta V_T / I_{C1}} \approx \frac{1}{I_{C1}} \cdot \frac{V_A}{V_T} \cdot \frac{\beta V_A V_T}{V_A + 2\beta V_T}$$

$$= \frac{1}{0.5 \text{ mA}} \cdot \frac{5 \text{ V}}{0.026 \text{ V}} \cdot \frac{100(5 \text{ V})(0.026 \text{ V})}{(5 \text{ V}) + 2(100)(0.026 \text{ V})}$$


$$\therefore R_{out} \approx 490 \text{ k}\Omega$$

6.

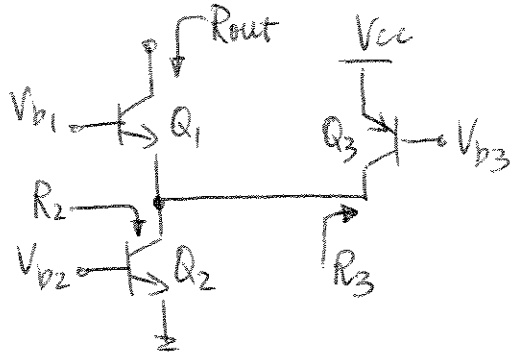

$$R_3 = r_{o3} \quad (V_{cc} \text{ \& } V_{b3} \text{ are AC GND})$$
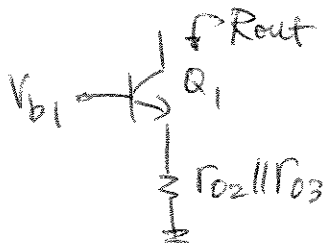
$$R_2 = r_{o2} \quad (V_{b2} \text{ is AC GND})$$




$$\therefore R_{out} = [1 + g_{m1} (r_{o2} \parallel r_{o3} \parallel r_{\pi 1})] r_{o1} + (r_{o2} \parallel r_{o3} \parallel r_{\pi 1})$$

$$\approx g_{m1} r_{o1} (r_{o2} \parallel r_{o3} \parallel r_{\pi 1})$$



7.

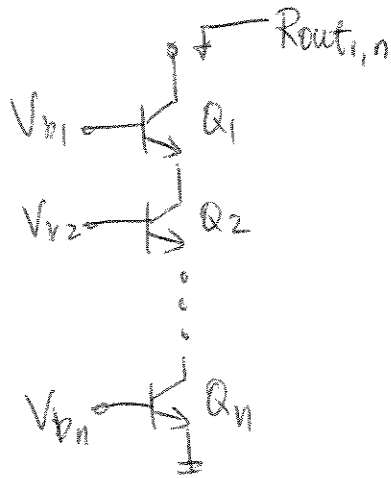

Suppose  $R_{out\ i,j}$  is the output impedance of the cascode circuit with BJTs  $Q_i, Q_{i+1}, Q_{i+2}, \dots, Q_{j-1}, Q_j$ .

$$\begin{aligned}
 R_{out\ n-1,n} &= [1 + g_{m_{n-1}}(r_{on} \parallel r_{\pi_{n-1}})]r_{on-1} + (r_{on} \parallel r_{\pi_{n-1}}) \\
 &\approx g_{m_{n-1}}(r_{on} \parallel r_{\pi_{n-1}})r_{on-1} \approx g_{m_{n-1}}r_{\pi_{n-1}}r_{on-1} \\
 &= \beta r_o \quad (\text{usually, } r_{\pi} \ll r_o)
 \end{aligned}$$

$$\begin{aligned}
 R_{out\ n-2,n} &= [1 + g_{m_{n-2}}(\beta r_o \parallel r_{\pi_{n-2}})]r_o + (\beta r_o \parallel r_{\pi_{n-2}}) \\
 &\approx g_m r_{\pi} r_o + r_{\pi} \approx \beta r_o
 \end{aligned}$$


This means that  $R_{out} \approx \beta r_o$  even if an extra BJT is employed in the cascode configuration.

i.e.  $R_{out\ MAX} \approx \beta r_o$

$$8. (a) R_2 = (r_{\pi_2} \parallel r_{\pi_1})$$

$$\therefore R_{out} = [1 + g_{m_1} R_2] r_{o_1} + R_2$$
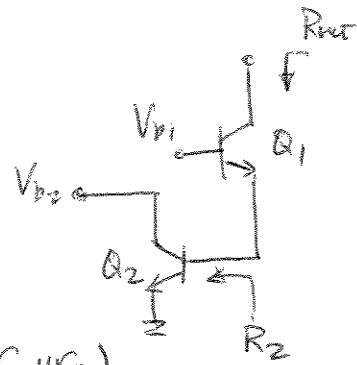
$$= [1 + g_{m_1} (r_{\pi_1} \parallel r_{\pi_2})] r_{o_1} + (r_{\pi_1} \parallel r_{\pi_2})$$



$$(b) \text{ In part (a), } I_{c_2} = \beta I_{c_1} (= I_{B_2})$$

$$\therefore R_{out(a)} = \left[ 1 + g_{m_1} \left( \frac{\beta V_T}{I_{c_1}} \parallel \frac{V_T}{I_{c_1}} \right) \right] r_{o_1} + (r_{\pi_1} \parallel r_{\pi_2})$$

$$\approx \left( 1 + g_{m_1} \frac{V_T}{I_{c_1}} \right) r_{o_1} + \frac{V_T}{I_{c_1}}$$

$$= 2r_{o_1} + V_T/I_{c_1}$$

$$\begin{aligned} R_{out, \text{cascode}} &= [1 + g_{m_1} (r_{o_2} \parallel r_{\pi_1})] r_{o_1} + (r_{o_2} \parallel r_{\pi_1}) \\ &\approx [1 + g_{m_1} r_{\pi_1}] r_{o_1} + r_{\pi_1} \\ &\approx \beta r_{o_1} + r_{\pi_1} = \beta r_{o_1} + V_A/I_{c_1} \end{aligned}$$

Compare term-by-term:


$$\left. \begin{array}{l} 2r_{o_1} \ll \beta r_{o_1} \\ V_T \ll V_A \end{array} \right\} \Rightarrow R_{out(a)} \ll R_{out, \text{cascode}}$$

i.e. using (a) reduces the effect of having a cascode configuration.

$$9. \quad R_{out} = \frac{1}{I_c} \cdot \frac{V_A}{V_T} \cdot \frac{\beta V_A V_T}{V_A + \beta V_T}$$

$$\approx \frac{1}{I_c} \cdot \frac{V_A}{V_T} \cdot \frac{\beta V_A V_T}{V_A} = \beta \frac{V_A}{I_c} = \beta r_o = R_{out, \max}$$

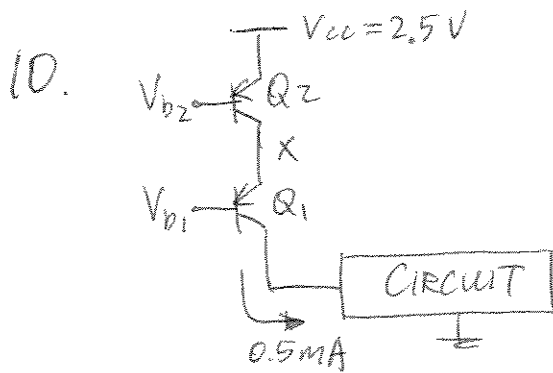This means that  $R_{out, \max}$  is often achieved with 2-BJT cascode.



$$I_S = 10^{-16} \text{ A} \quad \beta = 100$$

$$I_{BIAS} = 0.5 \text{ mA}$$

(a)  $I_{BIAS} \approx I_{C2} = 0.5 \text{ mA}$


$$\begin{aligned} \therefore V_{b2} &= V_{CC} - |V_{BE2}| \\ &= V_{CC} - V_T \ln \left( \frac{0.5 \text{ mA}}{10^{-16} \text{ A}} \right) \\ &= (2.5 \text{ V}) - (0.026 \text{ V}) \ln \left( \frac{0.5 \text{ mA}}{10^{-16} \text{ A}} \right) \approx 1.74 \text{ V} \end{aligned}$$

(b)  $|V_{CB2}| = V_X - V_{b2} = 200 \text{ mV}$   
 $\Rightarrow V_{C2} = V_{b2} + |V_{CB2}| = 1.94 \text{ V}$


$$\begin{aligned} \therefore V_{b1} &= V_{C2} - |V_{BE1}| = V_{C2} - V_T \ln \left( \frac{0.5 \text{ mA}}{10^{-16} \text{ A}} \right) \\ &= (1.94 \text{ V}) - (0.026 \text{ V}) \ln \left( \frac{0.5 \text{ mA}}{10^{-16} \text{ A}} \right) \approx 1.18 \text{ V} \end{aligned}$$

$\Rightarrow$  Maximum allowable  $V_{b1} = 1.18 \text{ V}$

11. (a)

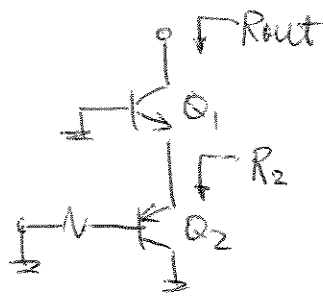

(Ac-small signal)

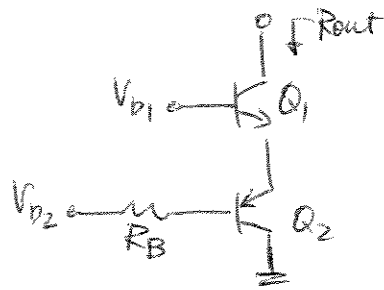


Looking into emitter of  $Q_2$ ,

$$R_2 = \frac{1}{\left( \frac{\beta+1}{R_B + r_{\pi_2}} + \frac{1}{r_{o_2}} \right)}$$

$$\Rightarrow R_{out} = [1 + g_{m_1}(R_2 \parallel r_{\pi_1})] r_{o_1} + (R_2 \parallel r_{\pi_1})$$


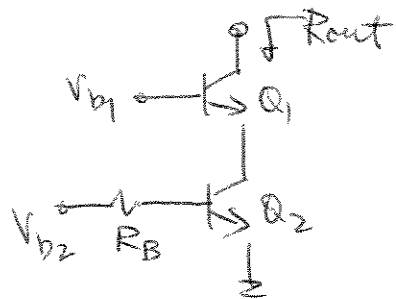
(b)  $R_B$  does not affect  $Q_2$  in small-signal  $R_{out}$ :

$$\therefore R_{out} = [1 + g_{m_1}(r_{o_2} \parallel r_{\pi_1})] r_{o_1} + (r_{o_2} \parallel r_{\pi_1})$$



This is a cascode stage.

(c) Use small-signal analysis:

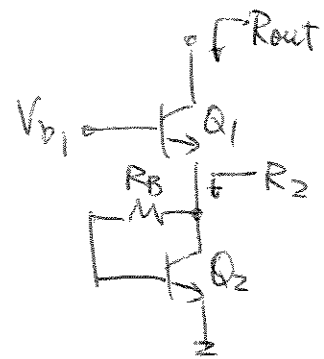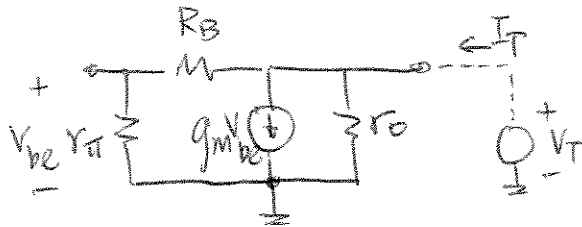

$$\text{By KCL, } I_T = \frac{V_T}{R_B + r_{\pi 2}} + g_{m2} \frac{V_T r_{\pi 2}}{r_{\pi 2} + R_B} + \frac{V_T}{r_{O2}}$$


$$\Rightarrow R_2 = \frac{V_T}{I_T} = \frac{1}{\left( \frac{\beta + 1}{R_B + r_{\pi 2}} + \frac{1}{r_{O2}} \right)} \approx \frac{1}{\beta / (R_B + r_{\pi 2}) + 1/r_{O2}}$$

$$\therefore R_{out} = [1 + g_{m1} (R_2 \parallel r_{\pi 1})] r_{O1} + (R_2 \parallel r_{\pi 1})$$

$$\approx g_{m1} r_{O1} (R_2 \parallel r_{\pi 1})$$



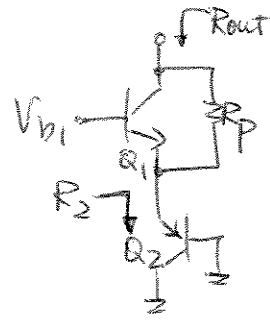(d)  $R_p$  appears in parallel with  $r_{o1}$ .



$$R_2 = r_{o2} \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

$$\approx r_{o2} \parallel \frac{r_{\pi 2}}{\beta} \parallel r_{\pi 2}$$


$$\approx r_{o2} \parallel (r_{\pi 2}/\beta) \approx r_{\pi 2}/\beta$$

$$\therefore R_{out} = [1 + g_{m1}(R_2 \parallel r_{\pi 1})](r_{o1} \parallel R_p) + (R_2 \parallel r_{\pi 1})$$

$$\approx g_{m1}(r_{o1} \parallel R_p)(r_{\pi 1} \parallel R_2)$$

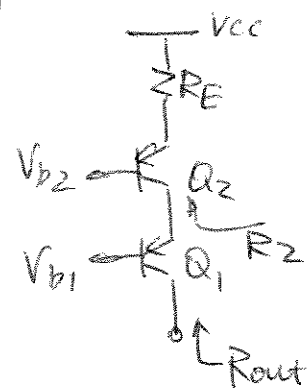(e)  $R_2 = [1 + g_{m2}(R_E \parallel r_{\pi 2})]r_{o2} + (R_E \parallel r_{\pi 2})$

$$\approx g_{m2}(R_E \parallel r_{\pi 2})r_{o2}$$



$$\therefore R_{out} = [1 + g_{m1}(R_2 \parallel r_{\pi 1})]r_{o1} + (R_2 \parallel r_{\pi 1})$$

$$\approx g_{m1}(R_2 \parallel r_{\pi 1})r_{o1}$$


$$= g_{m1} [g_{m2}r_{o2}(R_E \parallel r_{\pi 2}) \parallel r_{\pi 1}] r_{o1}$$

This is a cascode stage.

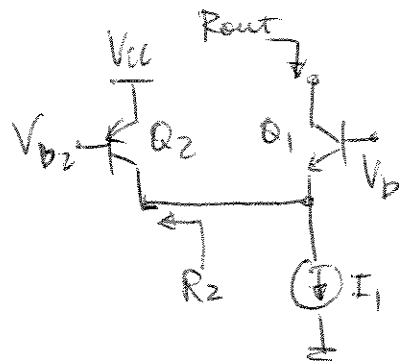(f)  $R_2 = r_{o2}$

$$\therefore R_{out} = [1 + g_{m1}(R_2 \parallel r_{\pi 1})] r_{o1} + (R_2 \parallel r_{\pi 1})$$


$$\approx g_{m1} r_{o1} (R_2 \parallel r_{\pi 1}) = g_{m1} r_{o1} (r_{\pi 1} \parallel r_{o2})$$



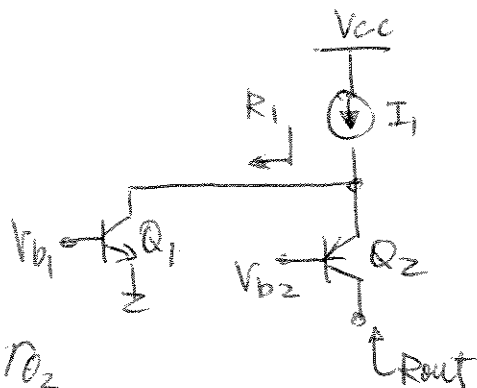
(g)  $R_1 = r_{o1}$   
(output impedance of a common-emitter.)

$$\therefore R_{out} = [1 + g_{m2}(R_1 \parallel r_{\pi 2})] r_{o2} + (R_1 \parallel r_{\pi 2})$$

$$\approx g_{m2} r_{o2} (r_{o1} \parallel r_{\pi 2})$$



12.

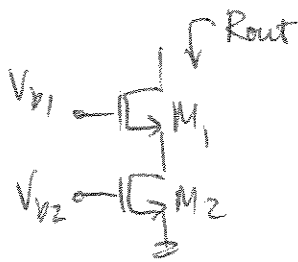

$$I_D = 0.5 \text{ mA} \quad R_{out} \geq 50 \text{ k}\Omega$$

$$\mu_n C_{ox} = 100 \frac{\mu\text{A}}{\text{V}^2} \quad \frac{W}{L} = \frac{20}{0.18}$$

Calculate max  $\lambda$ .Assume  $M_1$  &  $M_2$  in saturation.

$$\Rightarrow R_{out} \approx g_{m1} r_{o1} r_{o2}$$


$$= \sqrt{\frac{2 \mu_n C_{ox} \frac{W}{L} I_D}{\lambda I_D}} \times \frac{1}{\lambda I_D} \times \frac{1}{\lambda I_D} \geq 50 \text{ k}\Omega.$$

(All quantities are known).

Solve for  $\lambda$ :

$$\lambda_{\max} \approx 0.51 \text{ V}^{-1}$$

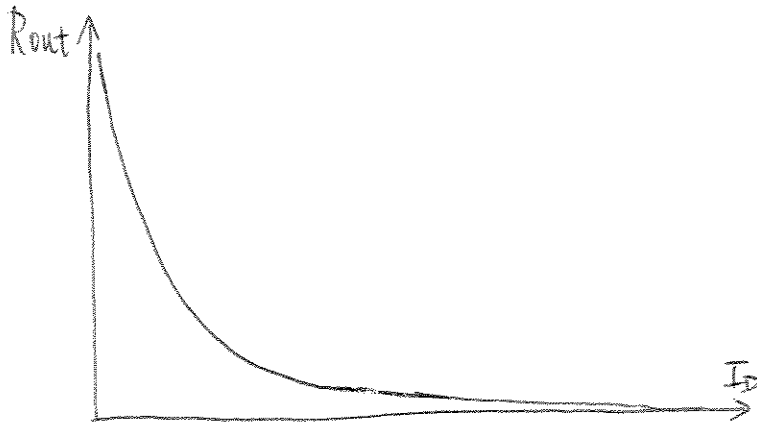
$$\begin{aligned}
 13. (a) \quad R_{out} &= g_{m2} r_{o1} r_{o2} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} \cdot \frac{1}{\lambda I_D} \cdot \frac{1}{\lambda I_D} \\
 &= 2 \mu_n C_{ox} \left(\frac{W}{L}\right) \cdot (I_D)^{-3/2}
 \end{aligned}$$



$$\begin{aligned}
 (b) \quad R_{out} \text{ (BJT)} &\propto I_B^{-1} \\
 R_{out} \text{ (MOS)} &\propto I_B^{-3/2}
 \end{aligned}$$

$\therefore$  MOS cascode is a stronger function of  $I$  in terms of  $R_{out}$ .

14.

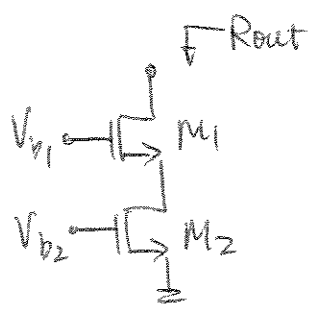

$$\left(\frac{W}{L}\right)_1 = 30/0.18 \quad \left(\frac{W}{L}\right)_2 = 20/0.18$$

$$I_{BIAS} = 0.5 \text{ mA}$$

$$\mu_n C_{ox} = 100 \frac{\mu\text{A}}{\text{V}^2} \quad V_{TH} = 0.4 \text{ V}$$

$$(a) \quad I_{D2} = I_{BIAS} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{b2} - V_{TH})^2$$

$$\begin{aligned} \Rightarrow V_{b2} &= \sqrt{\frac{2 I_{BIAS}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2}} + V_{TH} \\ &= \sqrt{\frac{2 (0.5 \text{ mA})}{100 \frac{\mu\text{A}}{\text{V}^2} \left(\frac{20}{0.18}\right)}} + 0.4 \text{ V} \approx 0.7 \text{ V} \end{aligned}$$

$M_2$  operates in saturation as long as

$$V_{GS2} - V_{TH} \leq V_{DS2} \Rightarrow V_{DS2} \geq 0.3 \text{ V.}$$

Observe that  $V_{GS1} = V_{b1} - V_{DS2}$

$$I_{D1} = I_{BIAS} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{b1} - V_{DS2} - V_{TH})^2$$


$$\begin{aligned} \Rightarrow V_{b1} &\geq \sqrt{\frac{2 I_{BIAS}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} + 0.4 \text{ V} + 0.3 \text{ V} \\ &= \sqrt{\frac{2 (0.5 \text{ mA})}{100 \frac{\mu\text{A}}{\text{V}^2} \left(\frac{30}{0.18}\right)}} + 0.7 \text{ V} \approx 0.95 \text{ V.} \end{aligned}$$

$\therefore$  Minimum  $V_{b1} = 0.95 \text{ V.}$

$$(b) R_{out} = (1 + g_{m1} r_{o2}) r_{o1} + r_{o2}$$

$$= \left( 1 + \sqrt{2 \mu_n C_{ox} \left( \frac{W}{L} \right)_1 I_{BIAS}} \cdot \frac{1}{\lambda I_{BIAS}} \right) \cdot \frac{1}{\lambda I_{BIAS}} + \frac{1}{\lambda I_{BIAS}}$$
$$= \left[ 1 + \sqrt{2 \left( \frac{100 \mu A}{V^2} \right) \left( \frac{30}{0.18} \right) (0.5 \text{ mA})} \cdot \frac{1}{(0.1)(0.5 \text{ m})} \right] \cdot \frac{1}{(0.1)(0.5 \text{ m})}$$
$$+ \frac{1}{(0.1)(0.5 \text{ mA})}$$
$$\approx 1.67 \text{ M}\Omega$$

15.

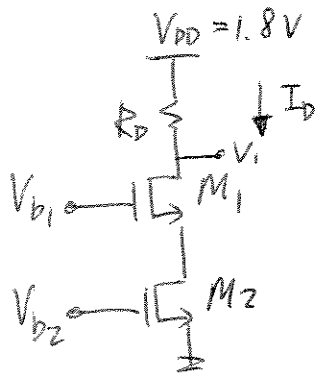

$$\left(\frac{W}{L}\right)_1 = \frac{20}{0.18} \quad \left(\frac{W}{L}\right)_2 = \frac{40}{0.18}$$

$$\mu_n C_{ox} = 100 \frac{\mu A}{V^2} \quad V_{TH} = 0.4 V$$

$$I_D = 1 \text{ mA} \quad R_D = 500 \Omega$$

(a) Both  $M_1$  &  $M_2$  must stay in saturation.

$$\Rightarrow V_i = 1.8 - I_D R_D = 1.8 - (1 \text{ mA})(500 \Omega) = 1.3 \text{ V}$$

Want this value equal to that which makes  $M_1$  operate at the edge of saturation.



$$\therefore V_{b1} = V_i + V_{TH} = 1.3 + 0.4 = 1.7 \text{ V}$$

$$(b) \quad I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \cdot [(V_{b1} - V_x) - V_{TH}]^2 = 1 \text{ mA}$$

$$\begin{aligned} \Rightarrow V_x &= V_{b1} - V_{TH} - \sqrt{\frac{2 I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} \\ &= (1.7 \text{ V}) - (0.4 \text{ V}) - \sqrt{\frac{2(1 \text{ mA})}{(100 \mu A/V^2)(20/0.18)}} \end{aligned}$$

$$\approx 1.276 \text{ V}$$



1b. (a) First compute  $R_x$ :

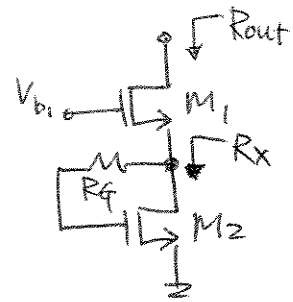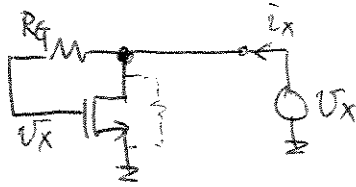

$$I_x = g_{m2}v_x + v_x/r_{o2} \Rightarrow R_x = v_x/i_x = \frac{1}{g_{m2} + 1/r_{o2}}$$

$$\therefore R_{out} = g_{m1}r_{o1}R_x = \frac{g_{m1}r_{o1}}{g_{m2} + 1/r_{o2}}$$


(b) Equivalent circuit:

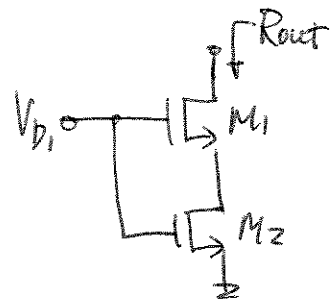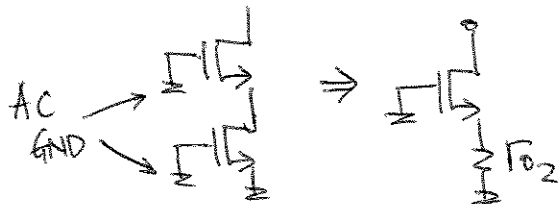

$$\therefore R_{out} = g_{m1}r_{o1}r_{o2}$$



(c) Equivalent Circuit:

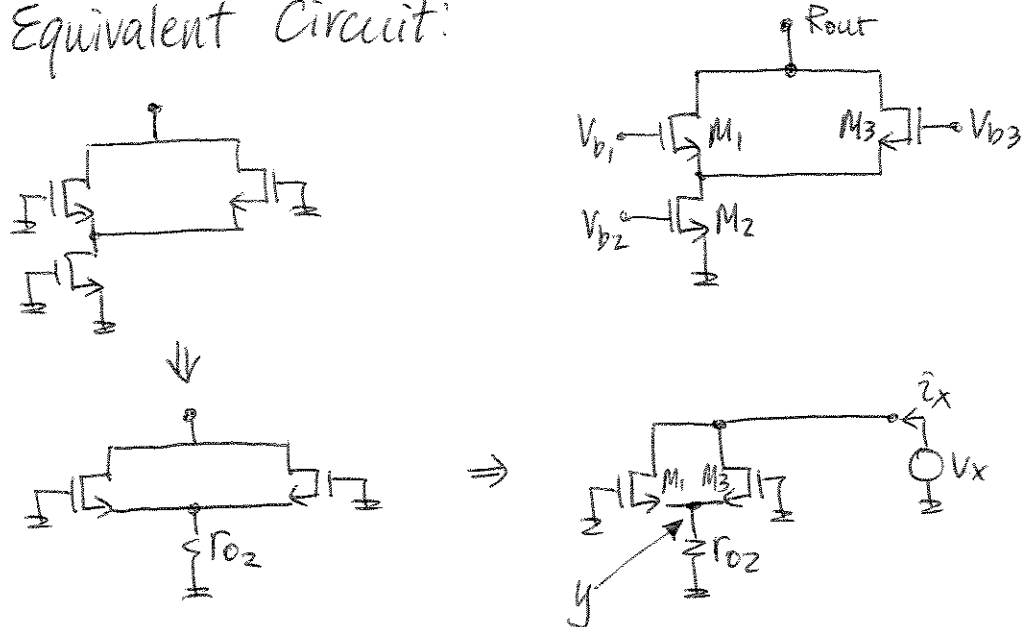

By KCL,  $V_y = \hat{i}_x \cdot r_{o2}$  ①

$$\hat{i}_x = g_{m1}(-V_y) + g_{m3}(-V_y) + (V_x - V_y)\left(\frac{1}{r_{o1}} + \frac{1}{r_{o3}}\right)$$
②



Substitute ① into ② and re-arrange:

$$R_{out} = \frac{V_x}{\hat{i}_x} = (r_{o1} \parallel r_{o3}) + r_{o2}(r_{o1} \parallel r_{o3})(g_{m1} + g_{m3}) + r_{o2}$$

$$\approx r_{o2}(r_{o1} \parallel r_{o3})(g_{m1} + g_{m3})$$

(Intuitively this makes sense because we have 2 NMOSs in parallel —  $\ominus = g_m v_{gs}$  adds up, and  $r_o$ 's are splitting total current,  $\hat{i}_x$ . This is as if an equivalent NMOS replacing  $M_1$  &  $M_3$  with  $g_m = (g_{m1} + g_{m3})$  &  $r_o = (r_{o1} \parallel r_{o3})$ .)

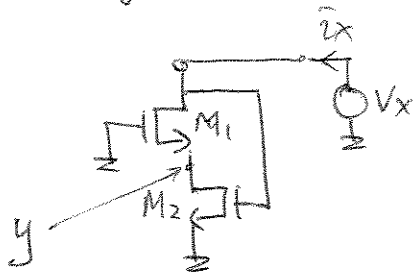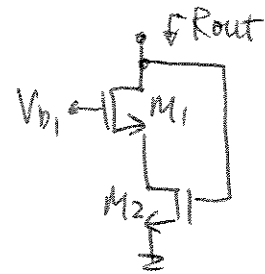(d) Examine the equivalent circuit with a test voltage:




By observation,  $i_x$  must flow through both  $M_1$  &  $M_2$ .

$$\begin{aligned} \text{By KCL, } \bar{i}_x &= g_{m2} V_x + V_y / r_{o2} \\ \bar{i}_x &= g_{m1} (-V_y) + (V_x - V_y) / r_{o1} \end{aligned}$$

Substitute ① into ② and re-arrange:

$$\begin{aligned} R_{out} = \frac{V_x}{\bar{i}_x} &= \frac{g_{m1} r_{o2} + \frac{r_{o2}}{r_{o1}} + 1}{g_{m1} g_{m2} r_{o2} + (g_{m2} r_{o2} + 1) \left( \frac{1}{r_{o1}} \right)} \\ &\approx \frac{r_{o2} \left( g_{m1} + \frac{1}{r_{o1}} \right)}{g_{m2} r_{o2} \left( g_{m1} + \frac{1}{r_{o1}} \right)} \approx \frac{1}{g_{m2}} \end{aligned}$$

17.

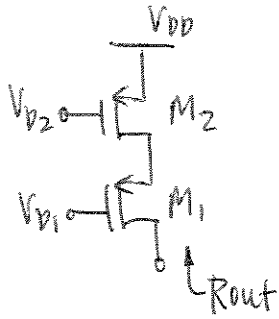

$$I_{BIAS} = 0.5 \text{ mA}$$

$$R_{out} = 40 \text{ k}\Omega$$

$$\mu_p C_{ox} = 50 \text{ mA/V}^2$$

$$\lambda = 0.2 \text{ V}^{-1}$$

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2$$

$$R_{out} = 40 \text{ k}\Omega = (g_{m1} r_{o2} + 1) r_{o1} + r_{o2}$$


$$\Rightarrow g_{m1} = \sqrt{2 \mu_p C_{ox} \left(\frac{W}{L}\right)_1 I_{BIAS}} = \left(\frac{R_{out} - r_{o2}}{r_{o1}} - 1\right) \cdot \frac{1}{r_{o2}}$$

$$\therefore \left(\frac{W}{L}\right)_1 = \left[ \left(\frac{R_{out} - r_{o2}}{r_{o1}} - 1\right) \frac{1}{r_{o2}} \right]^2 \cdot \frac{1}{2 \mu_p C_{ox} I_{BIAS}}$$

$$= \left\{ \left[ \frac{(40 \text{ k}\Omega) - [0.2 \times 0.5 \text{ m}]}{[0.2 \times 0.5 \text{ m}]^{-1}} - 1 \right] \cdot [0.2 \cdot 0.5 \text{ m}] \right\}^2 \cdot \frac{1}{2 (50 \frac{\text{mA}}{\text{V}^2}) (0.5 \text{ mA})}$$

$$\approx 0.8$$

18.

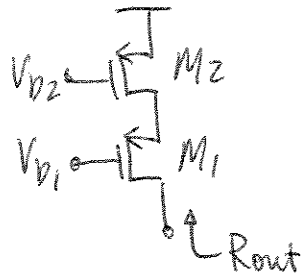


$$R_{out} = g_{m1} r_{o1} r_{o2} = \sqrt{2 \mu_p C_{ox} \left(\frac{W}{L}\right)_1 I_D} \cdot \frac{1}{\lambda I_D} \cdot \frac{1}{\lambda I_D}$$

If  $W_1$  &  $W_2$  increase by  $N$  times and  $L_1, L_2$ , and  $I_D$  remain unchanged:


$$\begin{aligned} R_{out}(\text{new}) &= \sqrt{2 \mu_p C_{ox} \left(\frac{NW}{L}\right) I_D} \cdot \left(\frac{1}{\lambda I_D}\right)^2 \\ &= \sqrt{N} \sqrt{2 \mu_p C_{ox} \frac{W}{L} I_D} \cdot \left(\frac{1}{\lambda I_D}\right)^2 = \sqrt{N} R_{out} \end{aligned}$$

$\therefore R_{out}$  is increased by  $\sqrt{N}$  times.

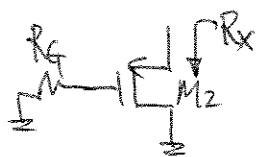19. (a)  $R_x$  is the input impedance of a common-gate configuration:



"Looking into" the source of  $M_2$ ,

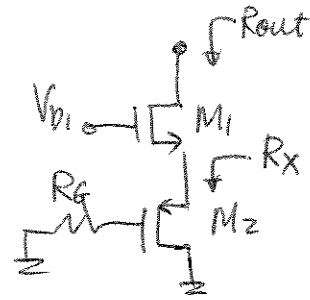


$$R_x = \frac{1}{g_{m2}} \parallel r_{o2}$$

$$\therefore R_{out} = g_{m1} r_{o1} R_x = g_{m1} r_{o1} \left( \frac{1}{g_{m2}} \parallel r_{o2} \right)$$

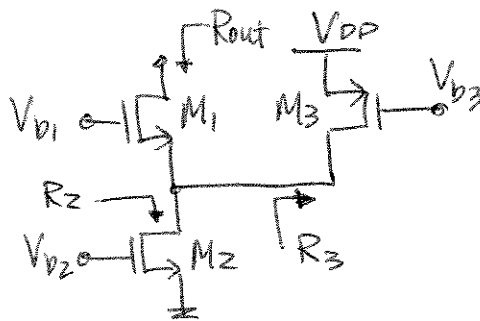(b) From observation,

$$\rightarrow R_3 = r_{o3} \quad (\because V_{sg} = 0 \text{ in AC})$$

$$\rightarrow R_2 = r_{o2} \quad (\because V_{sg} = 0 \text{ in AC})$$




$$\therefore R_{out} = g_{m1} r_{o1} (R_2 \parallel R_3) = g_{m1} r_{o1} (r_{o2} \parallel r_{o3})$$

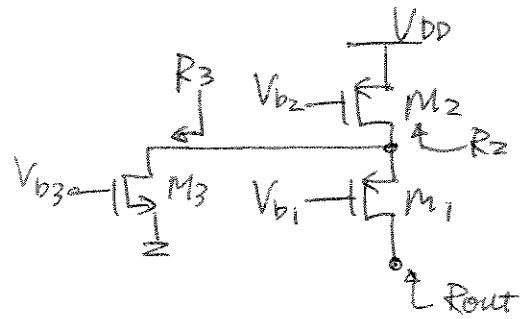(c) By observation,

$$R_2 = r_{o2} \quad (V_s = V_G = \text{AC GND})$$

$$R_3 = r_{o3} \quad (V_s = V_G = \text{AC GND})$$




$$\therefore R_{out} = g_{m1} r_{o1} (R_2 \parallel R_3) = g_{m1} r_{o1} (r_{o2} \parallel r_{o3})$$



(d)  $R_x = g_{m2} r_{o2} r_{o3}$

$$\Rightarrow R_{out} = g_{m1} r_{o1} R_x$$

$$= g_{m1} g_{m2} r_{o1} r_{o2} r_{o3}$$

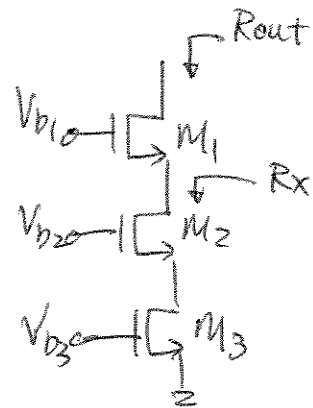

20.(a) Equivalent circuit :

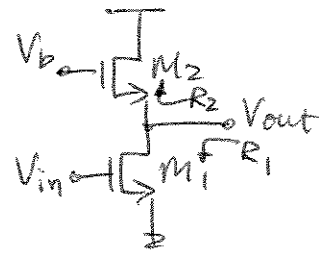
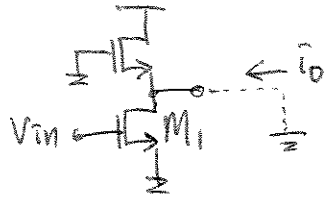


$$\bar{i}_o = G_m V_{in} \Rightarrow G_m = \frac{\bar{i}_o}{V_{in}} = g_{m1}$$

$$R_1 = r_{o1} ; R_2 = \frac{1}{g_{m2}}$$

$$\therefore A_v = -G_m R_{out} = -g_{m1} (r_{o1} \parallel \frac{1}{g_{m2}})$$

(b) Equivalent circuit :

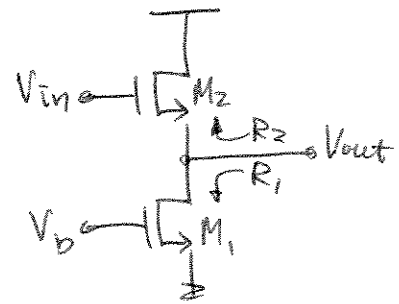
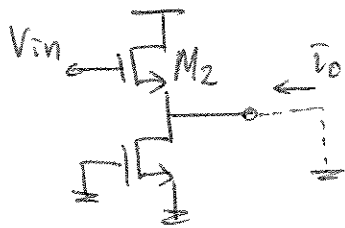


$$-\bar{i}_o = g_{m2} V_{in} \Rightarrow G_m = \frac{\bar{i}_o}{V_{in}} = -g_{m2}$$

$$R_1 = r_{o1} ; R_2 = \frac{1}{g_{m2}}$$

$$\therefore A_v = -G_m R_{out} = g_{m2} (r_{o1} \parallel \frac{1}{g_{m2}})$$

(c) Equivalent circuit:

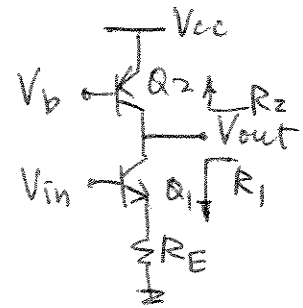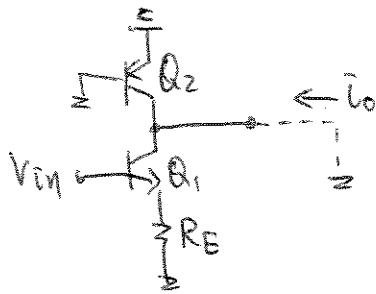

With output node shorted, this is a common-emitter stage with degeneration.

$$\Rightarrow G_m = \frac{g_{m1}}{g_{m1}(R_E \parallel r_{o1}) + 1}$$

$$R_1 = [1 + g_{m1}(R_E \parallel r_{\pi1})] r_{o1} + (R_E \parallel r_{\pi1})$$



$$R_2 = r_{o2}$$

$$\Rightarrow R_{out} = R_1 \parallel R_2$$

$$\therefore A_v = -G_m R_{out} = -\frac{g_{m1}(\{[1 + g_{m1}(R_E \parallel r_{\pi1})] r_{o1} + (R_E \parallel r_{\pi1})\} \parallel r_{o2})}{g_{m1}(R_E \parallel r_{o1}) + 1}$$



(d) Equivalent circuit:

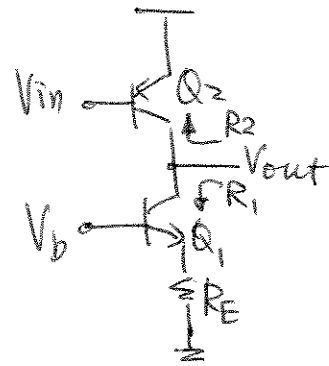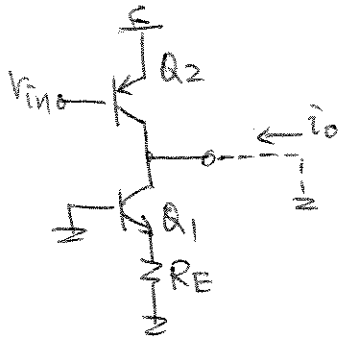

With output shorted to AC GND, circuit becomes a simple common-emitter stage:

$$\Rightarrow G_m = g_{m2}$$



$$R_1 = [1 + g_{m1}(R_E \parallel r_{\pi 1})]r_{o1} + (R_E \parallel r_{\pi 1})$$

$$R_2 = r_{o2}$$

$$\Rightarrow R_{out} = R_1 \parallel R_2$$

$$\therefore A_v = -G_m R_{out} = -g_{m2} \left( [1 + g_{m1}(R_E \parallel r_{\pi 1})]r_{o1} + (R_E \parallel r_{\pi 1}) \right) \parallel r_{o2}$$

(e) Equivalent circuit:

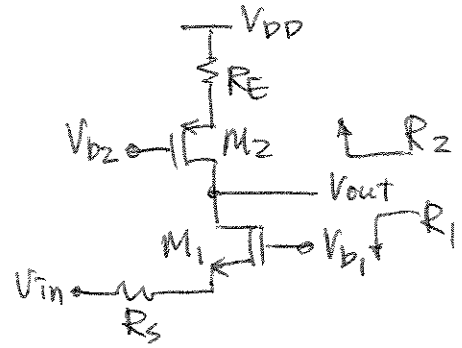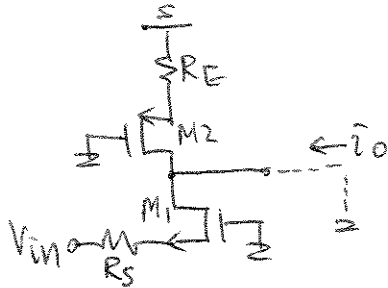

Observing that  $\bar{i}_o$  must flow through  $M_1$  only:

$$\bar{i}_o = g_{m1} \left( -(\overbrace{V_{in} + \bar{i}_o R_s}^{\text{gate voltage of } M_1}) \right)$$

$$\Rightarrow G_m = \frac{\bar{i}_o}{V_{in}} = \frac{-g_{m1}}{1 + g_{m1} R_s}$$

$$R_1 = (1 + g_{m1} R_s) r_{o1} + R_s$$



$$R_2 = (1 + g_{m2} R_E) r_{o2} + R_E$$

$$R_{out} = R_1 \parallel R_2$$

$$\therefore A_v = -G_m R_{out}$$

$$= \frac{g_{m1}}{1 + g_{m1} R_s} \left\{ [(1 + g_{m1} R_s) r_{o1} + R_s] \parallel [(1 + g_{m2} R_E) r_{o2} + R_E] \right\}$$

(f) Equivalent circuit:

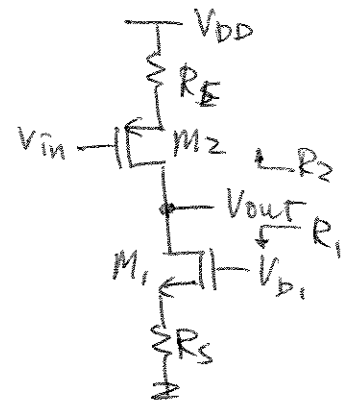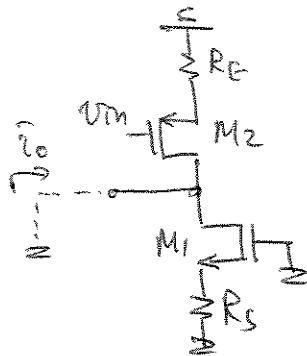

This is a common-source stage with degeneration:

$$\Rightarrow G_m = \frac{g_{m2}}{1 + g_{m2} R_E}$$


$$R_1 = (1 + g_{m1} R_S) r_{o1} + R_S$$

$$R_2 = (1 + g_{m2} R_E) r_{o2} + R_E$$


$$\therefore A_v = -G_m (R_1 \parallel R_2)$$

$$= \frac{g_{m2}}{1 + g_{m2} R_E} \left\{ [(1 + g_{m1} R_S) r_{o1} + R_S] \parallel [(1 + g_{m2} R_E) r_{o2} + R_E] \right\}$$

(g) Equivalent circuit:

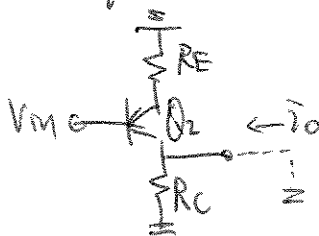
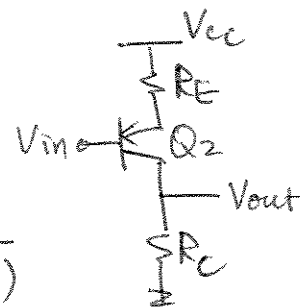
$$\Rightarrow G_m = \frac{g_{m2}}{1 + g_{m2} (R_E \parallel r_{\pi 2})}$$



$$R_{out} = \left\{ [1 + g_{m2} (R_E \parallel r_{\pi 2})] r_{o2} + (R_E \parallel r_{\pi 2}) \right\} \parallel R_L$$


$$\Rightarrow A_v = -G_m R_{out} = \frac{g_{m2} R_{out}}{1 + g_{m2} (R_E \parallel r_{\pi 2})}$$

$$\begin{aligned}
 21. \quad A_v &= -g_{m1} r_{o1} g_{m1} (r_{o1} \parallel r_{\pi 2}) \\
 &= -\frac{I_{c1}}{V_T} \cdot \frac{V_{A1}}{I_{c1}} \cdot \frac{I_{c1}}{V_T} \cdot \frac{1}{\frac{I_{c1}}{V_{A1}} + \frac{I_{c2}}{\beta V_T}}
 \end{aligned}$$

Since  $I_{c1} \approx I_{c2}$ ,

$$A_v \approx -\frac{V_{A1}/V_T^2}{\frac{1}{V_{A1}} + \frac{1}{\beta V_T}} = -\frac{\beta V_A^2}{V_T(V_A + \beta V_T)}$$

22.

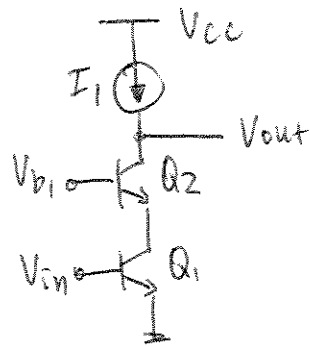

$$A_v = 500$$


$$\beta_1 = \beta_2 = 100$$

$$I_1 = 1\text{mA}$$

Determine minimum  $V_{A_1} = V_{A_2}$ .

Using small-signal analysis,
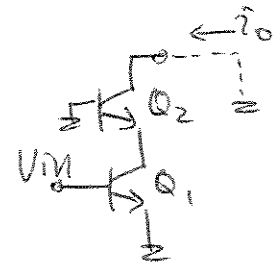
$$G_m = \frac{i_o}{v_{in}} = g_{m1} \left( \frac{\beta+1}{\beta} \right) = \frac{I_1}{V_T} \left( \frac{\beta+1}{\beta} \right)$$



$$R_{out} = [1 + g_{m2}(r_{o1} \parallel r_{\pi 2})] r_{o2} + (r_{o1} \parallel r_{\pi 2})$$

$$\approx g_{m2}(r_{o1} \parallel r_{\pi 2}) r_{o2} = \frac{\beta V_{A_2}^2}{I_C (V_{A_2} + \beta V_T)}$$

$$\Rightarrow A_v = -G_m R_{out}$$

$$= -\frac{I_1}{V_T} \left( \frac{\beta+1}{\beta} \right) \cdot \frac{\beta V_{A_2}^2}{I_C (V_{A_2} + \beta V_T)} = 500$$

$\Rightarrow$  All values are given.  $V_A$  is solved using the quadratic formula:

$$\therefore V_A \approx 0.65\text{ V}$$


23. (a) Even though  $R_{out}$  is independent of where  $V_{in}$  is applied,  $G_m$  changes:



The circuit is a common-emitter with degeneration, which always has  $G_m \leq G_m$  of common-emitter stage without degeneration.

Alternatively, this circuit has less gain because it only has one amplifier stage.


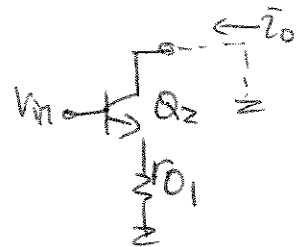
$$(b) \quad G_m = \frac{\bar{i}_o}{V_{in}} = \frac{g_{m2}}{1 + g_{m2}(r_{o1} \parallel r_{o2})}$$



$$R_{out} = [1 + g_{m2}(r_{o1} \parallel r_{o2})] r_{o2} + r_{o1}$$

$$\Rightarrow A_v = -G_m R_{out} = \frac{g_{m2} \{ [1 + g_{m2}(r_{o1} \parallel r_{o2})] [r_{o2} + r_{o1}] \}}{1 + g_{m2}(r_{o1} \parallel r_{o2})}$$

24. Equivalent circuit:

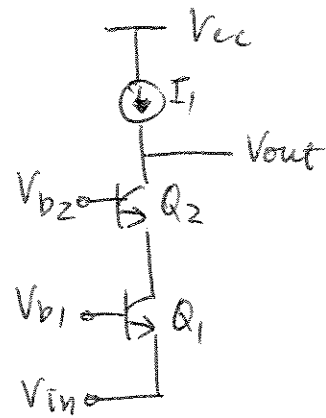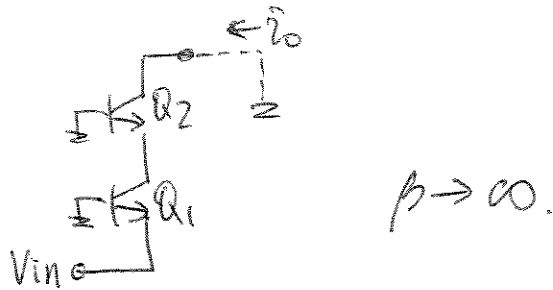


$$G_m = \frac{\bar{i}_o}{V_{in}} \approx -g_{m1}$$

$$R_{out} = [1 + g_{m2}(r_{o1} \parallel r_{\pi 2})] r_{o2} + (r_{o1} \parallel r_{\pi 2})$$

$$\Rightarrow A_v = -G_m R_{out} = g_{m1} \left[ \{1 + g_{m2}(r_{o1} \parallel r_{\pi 2})\} r_{o2} + (r_{o1} \parallel r_{\pi 2}) \right]$$


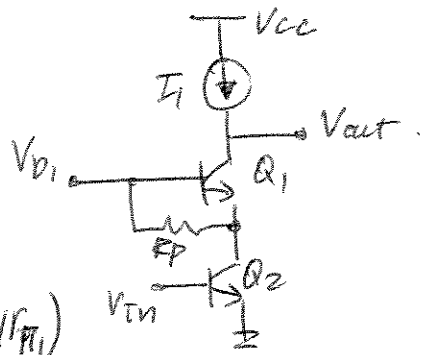
25. (a) From lecture, we know that the voltage gain of a BJT cascode circuit  $\approx -g_{m2} r_{o2} g_{m1} (r_{o2} \parallel r_{\pi 1})$



This circuit resembles such, and the only difference is that  $r_{\pi 1}$  now becomes  $(r_{\pi 1} \parallel R_P)$

$$\therefore A_v \approx -g_{m2}^2 r_{o2} (r_{o2} \parallel r_{\pi 1} \parallel R_P)$$

(b) Equivalent circuit:

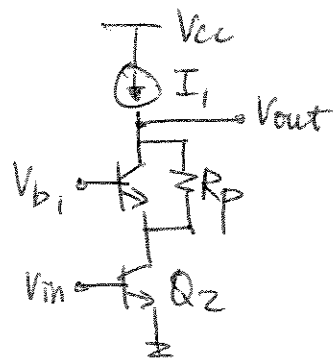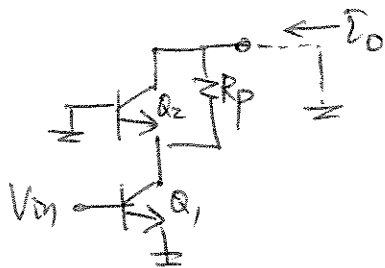



$$G_m = \frac{i_o}{V_{in}} = \frac{\beta + 1}{\beta} g_{m1} \approx g_{m1}$$

$$R_{out} = [1 + g_{m2} (r_{o1} \parallel r_{\pi 2})] (r_{o2} \parallel R_P) + (r_{o1} \parallel r_{\pi 2})$$

$$\therefore A_v = -G_m R_{out} = -g_{m1} \{ [1 + g_{m2} (r_{o1} \parallel r_{\pi 2})] (r_{o2} \parallel R_P) + (r_{o1} \parallel r_{\pi 2}) \}$$



(c) Equivalent circuit:

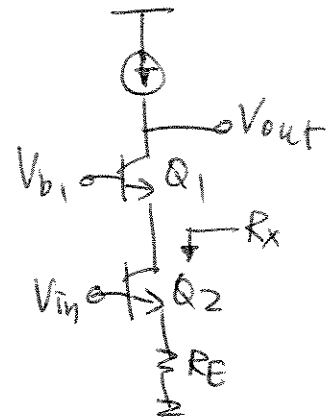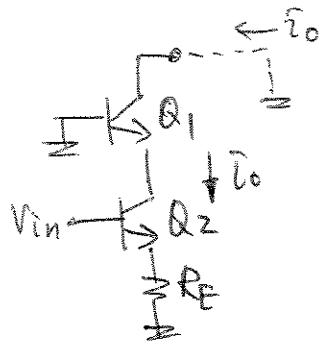



$$G_m = \frac{\bar{i}_o}{V_{in}} = \frac{g_{m2}}{1 + g_{m2}R_E} \quad (\text{small-signal analysis})$$

$$\begin{aligned} R_{out} &= (1 + g_{m1}R_x)r_{o1} + R_x \\ &= [1 + g_{m1}[(1 + g_{m2}R_E)r_{o2} + R_E]]r_{o1} \\ &\quad + [(1 + g_{m2}R_E)r_{o2} + R_E] \end{aligned}$$

$$\therefore A_v = -G_m R_{out}$$

$$= \frac{g_{m2}}{1 + g_{m2}R_E} \left\{ [1 + g_{m1}[(1 + g_{m2}R_E)r_{o2} + R_E]]r_{o1} + [(1 + g_{m2}R_E)r_{o2} + R_E] \right\}$$


(d) Equivalent circuit:

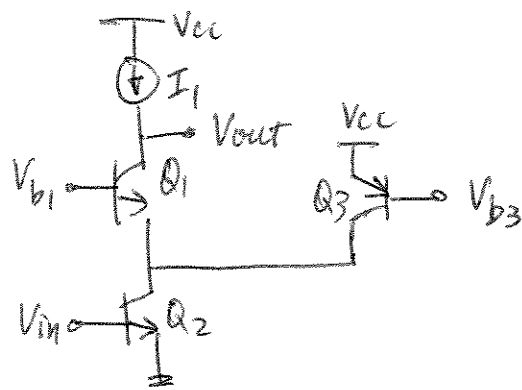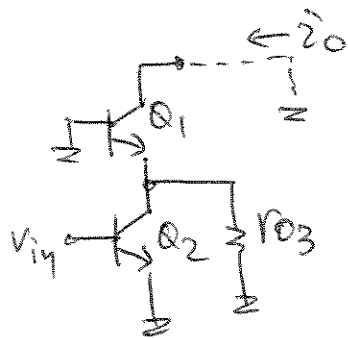

This resembles the BJT cascode topology, only now  $r_{o2}$  becomes  $(r_{o2} || r_{o3})$

$$\Rightarrow A_v \approx -g_{m2}^2 (r_{o2} || r_{o3}) (r_{o2} || r_{o3} || r_{\pi 1})$$
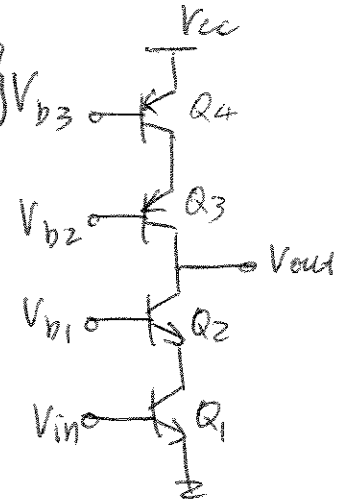
$$2b. A_v = -g_{m1} \left\{ \underbrace{[g_{m2} r_{o2} (r_{o1} \parallel r_{\pi 2})]}_{R_{on}} \parallel \underbrace{[g_{m3} r_{o3} (r_{o4} \parallel r_{\pi 3})]}_{R_{op}} \right\} V_{b3}$$



$$R_{on} = \frac{(V_{AN}/V_T)}{\left(\frac{1}{V_{AN}} + \frac{1}{\beta_n V_T}\right) I_C}$$



$$R_{op} = \frac{(V_{AP}/V_T)}{\left(\frac{1}{V_{AP}} + \frac{1}{\beta_p V_T}\right) I_C}$$

$$g_{m1} = \frac{I_C}{V_T}$$

$$\begin{aligned} \therefore A_v &= \frac{- (I_C/V_T)}{\frac{\left(\frac{1}{V_{AN}} + \frac{1}{\beta_n V_T}\right) I_C}{V_{AN}/V_T} + \frac{\left(\frac{1}{V_{AP}} + \frac{1}{\beta_p V_T}\right) I_C}{V_{AP}/V_T}} \\ &= \frac{V_{AN} \cdot V_{AP}}{V_T^2 \left( \frac{V_{AP}}{V_{AN}} + \frac{V_{AP}}{\beta_n V_T} + \frac{V_{AN}}{V_{AP}} + \frac{V_{AN}}{\beta_p V_T} \right)} \end{aligned}$$

$\therefore A_v$  is independent of bias current,  $I_C$ .

27. Equivalent circuit.

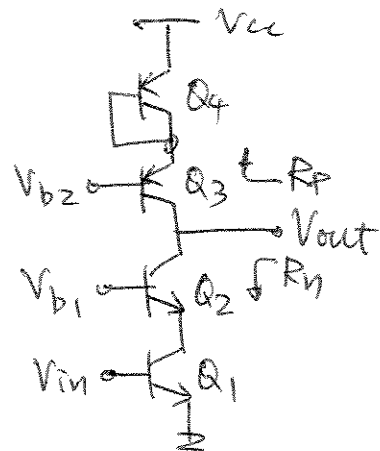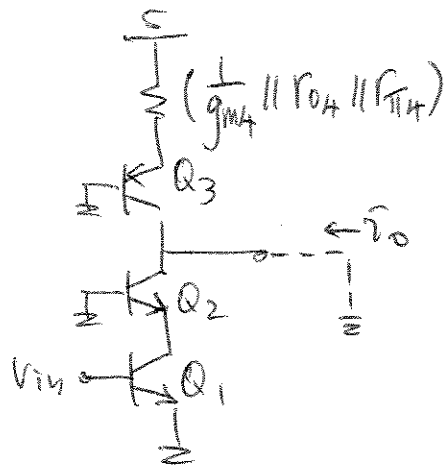

$$G_m = g_{m1} = \frac{\bar{i}_o}{V_{in}} = \frac{\bar{i}_{e1}}{V_{in}}$$


$$R_{out} = R_p \parallel R_n$$

$$R_p = \left[ 1 + g_{m3} \left( \frac{1}{g_{m4}} \parallel r_{o4} \parallel r_{\pi4} \parallel r_{\pi3} \right) \right] r_{o3} + \left[ \frac{1}{g_{m4}} \parallel r_{o4} \parallel r_{\pi4} \parallel r_{\pi3} \right]$$

$$R_n = \left[ 1 + g_{m2} (r_{o1} \parallel r_{\pi2}) \right] r_{o2} + (r_{o1} \parallel r_{\pi2})$$

$$\therefore A_v = -G_m R_{out} = -g_{m1} (R_p \parallel R_n)$$


$$\begin{aligned}
 28. |A_v| &= g_{m1} r_{o1} g_{m2} r_{o2} \\
 &= \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_D} \cdot \frac{1}{\lambda I_D} \cdot \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right)_2 I_D} \cdot \frac{1}{\lambda I_D} \\
 &= 2 \mu_n C_{ox} \sqrt{\left(\frac{W}{L}\right)_1 \left(\frac{W}{L}\right)_2} \cdot \frac{1}{\lambda^2 I_D}
 \end{aligned}$$

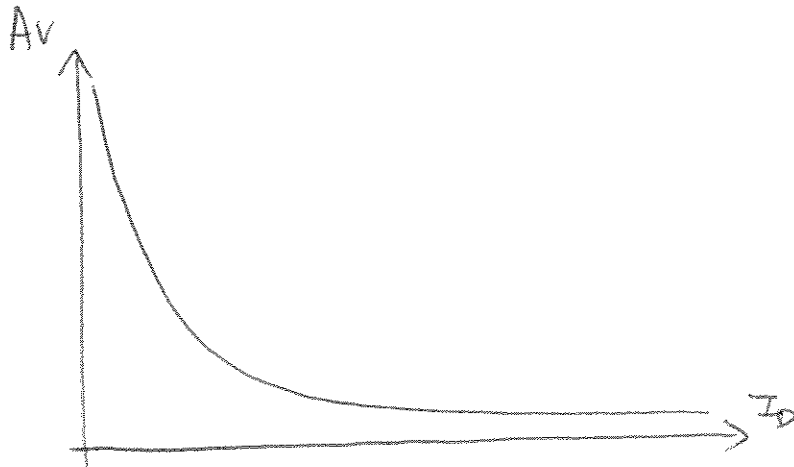

29.  $|A_v| = 200$


$\mu_n C_{ox} = 100 \frac{\mu A}{V^2}$        $\lambda = 0.1 \text{ V}^{-1}$

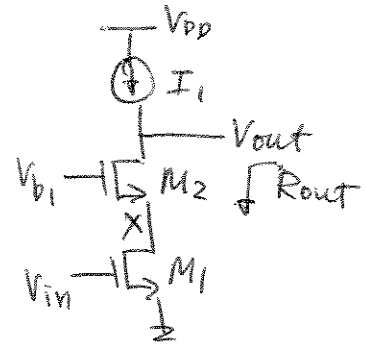Determine  $(\frac{W}{L})_1 = (\frac{W}{L})_2$



$R_{out} = (1 + g_{m2} r_{o1}) r_{o2} + r_{o1}$

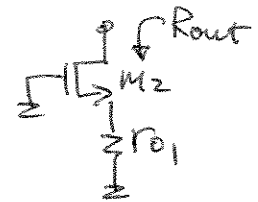$G_m \cong g_{m1}$  (short-circuit current flows through both  $M_1$  &  $M_2$ )



$|A_v| = G_m R_{out} = g_{m1} [(1 + g_{m2} r_{o1}) r_{o2} + r_{o1}]$

$\approx g_{m1} g_{m2} r_{o1} r_{o2} = (g_m r_o)^2 = 200$

( $\because (\frac{W}{L})_1 = (\frac{W}{L})_2$  and  $I_{D1} = I_{D2}$ )


$(g_m r_o)^2 = \left( \frac{2 I_D}{V_{GS} - V_{TH}} \cdot \frac{1}{\lambda I_D} \right)^2 = 200$

$\Rightarrow V_{GS} - V_{TH} = (\sqrt{200} \cdot \lambda / 2)^{-1} = [\sqrt{200} \cdot (0.05 \text{ V}^{-1})]^{-1}$   
 $\approx 1.41 \text{ V}$

$$\Rightarrow I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_{TH})^2$$

$$\begin{aligned} \therefore \left(\frac{W}{L}\right) &= \frac{2 I_D}{\mu_n C_{ox} (V_{GS} - V_{TH})^2} \\ &= \frac{2(1 \text{ mA})}{100 \frac{\mu\text{A}}{\text{V}^2} (1.4 \text{ V})^2} \approx 10 \end{aligned}$$

30.

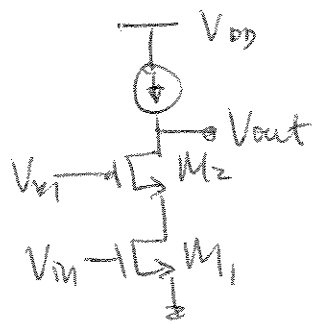

$$\left(\frac{W}{L}\right)_{1, \text{new}} = N \left(\frac{W}{L}\right)_1$$

$$\left(\frac{W}{L}\right)_{2, \text{new}} = N \left(\frac{W}{L}\right)_2$$

$$\lambda_{n,1} = \lambda_{n,2}$$

$$A_{v, \text{new}} \approx -g_{m1} g_{m2} r_{o1} r_{o2}$$

$$= -\sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right)_{1, \text{new}} I_{D1}} \cdot \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right)_{2, \text{new}} I_{D2}} \cdot \frac{1}{\lambda_{I_{D1}}} \cdot \frac{1}{\lambda_{I_{D2}}}$$


$$= -\sqrt{N} \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}} \cdot \sqrt{N} \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right)_2 I_{D2}} \cdot \frac{1}{\lambda_{I_{D1}}} \cdot \frac{1}{\lambda_{I_{D2}}}$$

$$= -N (g_{m1} g_{m2} r_{o1} r_{o2}) = -N \cdot A_{v, \text{old}}$$

Gain is  $N$  times of original value:



31.

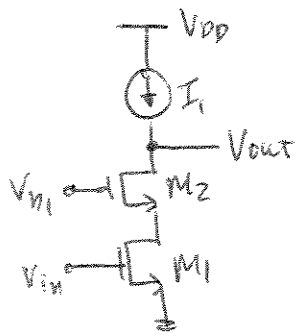

$$\left(\frac{W}{L}\right)_{1, \text{new}} = \frac{1}{N} \left(\frac{W}{L}\right)_1$$

$$\left(\frac{W}{L}\right)_{2, \text{new}} = \frac{1}{N} \left(\frac{W}{L}\right)_2$$

Assume  $\lambda_{n,1} = \lambda_{n,2}$

$$A_{v, \text{new}} \approx -g_{m1} (g_{m2} (r_{o1} r_{o2}))$$


$$= -\sqrt{\frac{1}{N} \cdot 2 \mu_n C_{ox} \left(\frac{W}{L}\right)_{1, \text{new}} \cdot I_{D1}} \cdot \sqrt{\frac{1}{N} \cdot 2 \mu_n C_{ox} \left(\frac{W}{L}\right)_{2, \text{new}} \cdot I_{D1}} \cdot \left(\frac{1}{\lambda I_{D1}}\right)^2$$

$$= -\sqrt{\frac{1}{N} \cdot \frac{1}{N} \cdot 2 \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \cdot I_{D1}} \cdot \sqrt{\frac{1}{N} \cdot \frac{1}{N} \cdot 2 \mu_n C_{ox} \left(\frac{W}{L}\right)_2 \cdot I_{D1}} \cdot \left(\frac{1}{\lambda I_{D1}}\right)^2$$

$$= -\frac{1}{N} g_{m1} g_{m2} r_{o1} r_{o2} = -\frac{1}{N} (A_{v, \text{old}})$$

Gain is  $\frac{1}{N}$  of original value.

32.

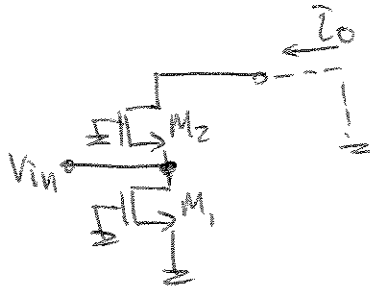


By KCL,

$$\frac{\bar{i}_o}{v_{in}} = -\left(g_{m2} + \frac{1}{r_{o1} \parallel r_{o2}}\right) = G_m$$


$$R_n = r_{o2}$$

$$R_p \approx g_{m3} r_{o3} r_{o4}$$
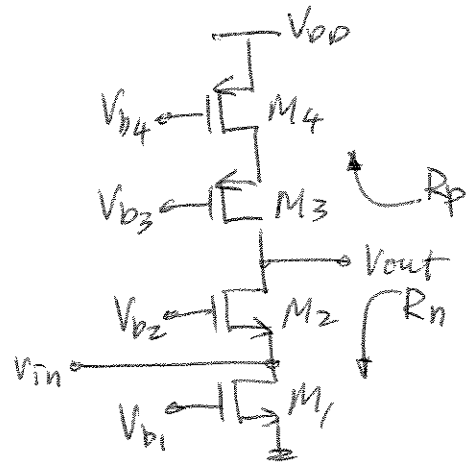
$$\therefore A_v = -G_m (R_n \parallel R_p) = \left(g_m + \frac{1}{r_{o1} \parallel r_{o2}}\right) (r_{o2} \parallel g_{m3} r_{o3} r_{o4})$$



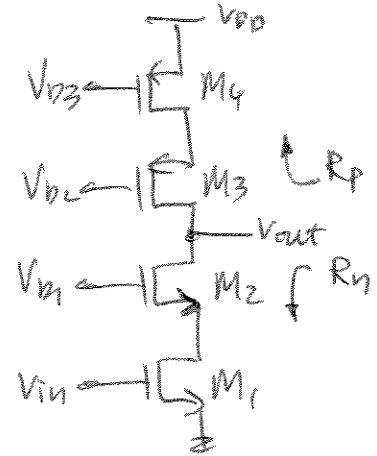33.  $(\frac{W}{L}) = 20/0.18$   
 $\mu_n C_{ox} = 100 \text{ MA/V}^2$   
 $\mu_p C_{ox} = 50 \text{ MA/V}^2$   
 $\lambda_n = 0.1 \text{ V}^{-1}$      $\lambda_p = 0.15 \text{ V}^{-1}$



Calculate  $I_{BIAS}$  such as  
 $A_v = 500$ .



The cascode circuit has gain  
 $\approx -g_{m1} \cdot [g_{m2} r_{o1} r_{o2} \parallel g_{m3} r_{o3} r_{o4}]$

$$\Rightarrow 500 = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D} \left( \frac{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)}}{(\lambda_n)^2 I_D^{3/2}} \parallel \frac{\sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right)}}{(\lambda_p)^2 I_D^{3/2}} \right)$$

All quantities are known. Solving  $I_D$  gives:

$$I_D = I_{BIAS} \approx 1.06 \text{ mA.}$$

34(a) Equivalent circuit:

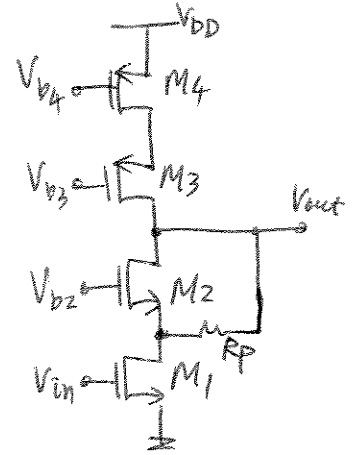
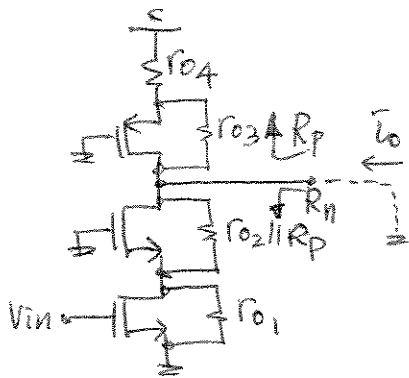


$$G_m = \frac{\bar{i}_o}{V_{in}} \approx g_{m1} \quad (\because g_m r_o \gg 1)$$

$$R_p = g_{m3} r_{o3} r_{o4} \quad R_n = g_{m2} (r_{o2} \parallel R_p) r_{o1}$$

$$\therefore A_v = -G_m R_{out} = -g_{m1} [g_{m3} r_{o3} r_{o4} \parallel g_{m2} (r_{o2} \parallel R_p) r_{o1}]$$

(b) Equivalent circuit

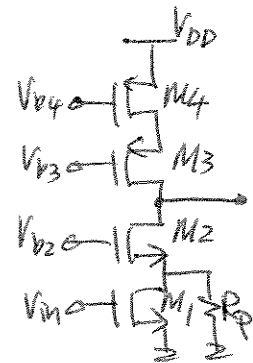
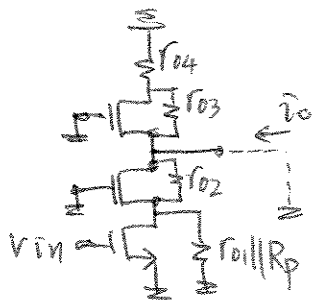


$$G_m = \bar{i}_o / V_{in} \approx g_{m1} \quad (\because g_m r_o \gg 1)$$

$$R_p = g_{m3} r_{o3} r_{o4} \quad R_n = g_{m2} (r_{o1} \parallel R_p) r_{o2}$$

$$\therefore A_v = -G_m R_{out} = -g_{m1} [g_{m3} r_{o3} r_{o4} \parallel g_{m2} (r_{o1} \parallel R_p) r_{o2}]$$

(c) Equivalent circuit:

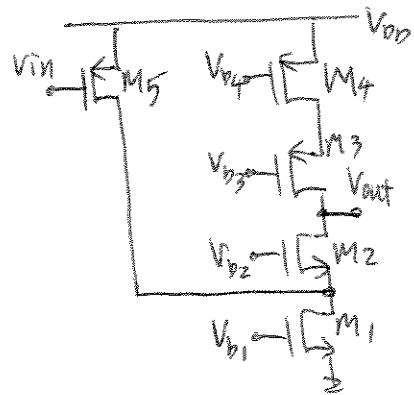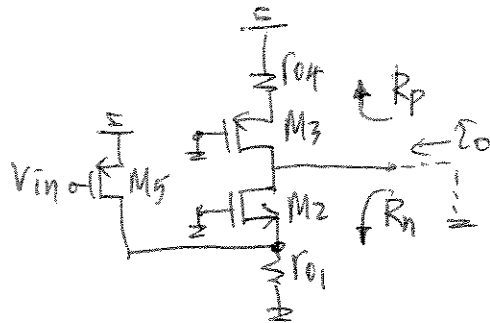



(Realize that  $r_{o1}$  &  $r_{o5}$  are in parallel.)

$$G_m = \frac{i_o}{v_{in}} \approx -g_{m5} \quad (\because g_m r_o \gg 1)$$

$$R_p = g_{m3} r_{o3} r_{o4} \quad R_n = g_{m2} r_{o2} (r_{o1} \parallel r_{o5})$$

$$\therefore A_v = -G_m R_{out} = g_{m5} [g_{m3} r_{o3} r_{o4} \parallel g_{m2} r_{o2} (r_{o1} \parallel r_{o5})]$$

(d) Equivalent circuit:

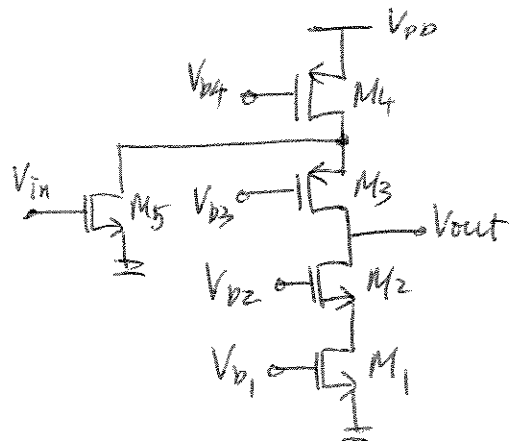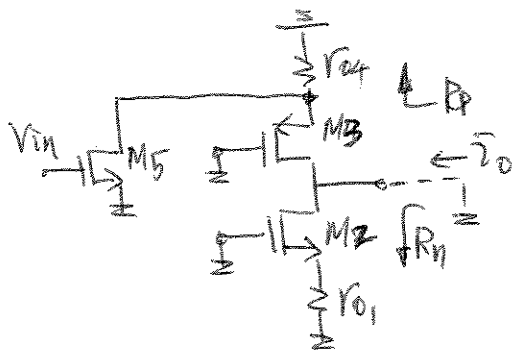

$$G_m = \frac{i_o}{v_{in}} \approx g_{m5}$$

$$R_p = g_{m3} r_{o3} (r_{o4} \parallel r_{o5})$$

$$R_n = g_{m2} r_{o2} r_{o1}$$

$$\therefore A_v = -G_m R_{out} = g_{m5} [g_{m3} r_{o3} (r_{o4} \parallel r_{o5}) \parallel g_{m2} r_{o2} r_{o1}]$$

$$35. \quad \frac{R_2}{R_1 + R_2} V_{CC} = V_T \ln \left( \frac{I_1}{I_S} \right)$$

$$\Rightarrow I_1 = I_S \cdot \exp \left[ \frac{V_{CC}}{V_T} \cdot \frac{R_2}{R_1 + R_2} \right]$$

$$\begin{aligned} \frac{\partial I_1}{\partial V_{CC}} &= \frac{I_S}{V_T} \cdot \frac{R_2}{R_1 + R_2} \cdot \exp \left[ \frac{V_{CC}}{V_T} \cdot \frac{R_2}{R_1 + R_2} \right] \\ &= \frac{I_1}{V_T} \cdot \frac{R_2}{R_1 + R_2} = g_m \left( \frac{R_2}{R_1 + R_2} \right) \end{aligned}$$

Intuitively, we know that an exponential relationship exists between  $I_C$  &  $V_{BE}$ . Its transconductance is also a function (linear) of  $I_C$ . Since  $V_{BE}$  comes from a voltage divider (which is also linear), we expect a linear relationship between  $I_C$  &  $V_{CC}$ .

$$76. \quad I_1 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left( \frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right)^2$$

$$\frac{\partial I_1}{\partial V_{DD}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \cdot 2 \left( \frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right) \cdot \frac{R_2}{R_1 + R_2}$$

$$= \mu_n C_{ox} \frac{W}{L} \left( \frac{R_2}{R_1 + R_2} \right) \left( \frac{R_2 \cdot V_{DD} - V_{TH}}{R_1 + R_2} \right)$$

$$= g_m \cdot \frac{R_2}{R_1 + R_2}$$

Intuitively, the voltage divider gives a linear relationship between  $V_{DD}$  &  $V_{GS1}$ . Since  $g_m$  of MOS is linearly proportional to  $(V_{GS1} - V_{TH})$ , we expect the same relationship between  $V_{DD}$  &  $\frac{\partial I_1}{\partial V_{DD}}$ .


$$37. \quad I_1 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left( \frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right)^2$$

$$\frac{\partial I_1}{\partial V_{TH}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \cdot 2 \left( \frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right) \cdot (-1)$$

$$= - \mu_n C_{ox} \frac{W}{L} \left( \frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right)$$



38.

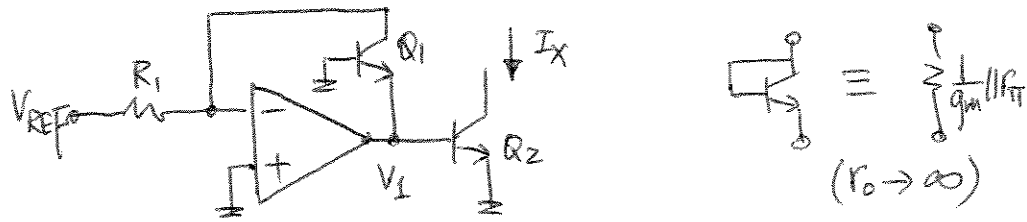


This is a negative feedback circuit.

The inverting input (-) of the op-amp is virtual ground. ( $\because$  of feedback) in DC.  $\Rightarrow Q_1$  becomes diode-connected.

$$\Rightarrow \frac{V_{REF}}{R_1} = \frac{0 - V_1}{\left(\frac{1}{g_{m_1}} \parallel r_{\pi_1}\right)} \Rightarrow V_1 = -\frac{V_{REF} \left(\frac{1}{g_{m_1}} \parallel r_{\pi_1}\right)}{R_1} < 0$$

This implies  $V_{BE_2} < 0 \Rightarrow I_X = 0!$

39.

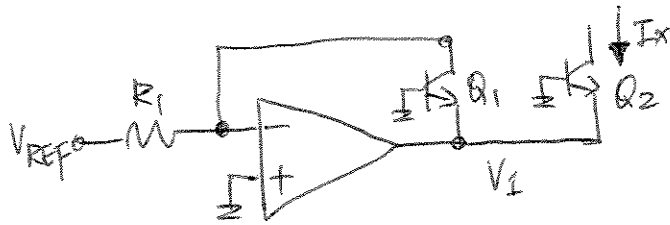


This is a negative feedback circuit.

The inverting input (-) is virtual ground, as a result.  $Q_1$  then becomes diode-connected, and its resistance  $= (\frac{1}{g_{m1}} \parallel r_{\pi 1})$ , assuming  $r_o \rightarrow \infty$ .

$$\Rightarrow \frac{V_{REF}}{R_1} = \frac{-V_1}{(\frac{1}{g_{m1}} \parallel r_{\pi 1})} \Rightarrow V_1 = -\frac{V_{REF} (\frac{1}{g_{m1}} \parallel r_{\pi 1})}{R_1}$$


$$\Rightarrow V_{BE1} = V_{BE2} = -V_1$$

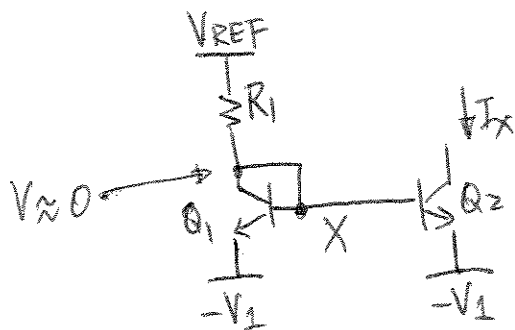This circuit will work if the negative supply voltage of the op-amp allows value of  $-V_1$  or lower.



- An equivalent circuit, (without op-amp). The op-amp guarantees a stable voltage at node X. (i.e. inverting input.)

40.

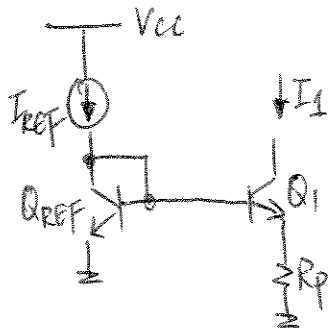

$$Q_{REF} = Q_1$$

$$\beta \rightarrow \infty$$

$$I_1 = \frac{I_{REF}}{2}$$


By KVL,  $V_{BE,REF} = V_{BE2} + I_1 R_p$

$$\Rightarrow V_T \ln\left(\frac{I_{REF}}{I_{S,REF}}\right) = V_T \ln\left(\frac{I_{REF}/2}{I_{S,1}}\right) + \frac{I_{REF} R_p}{2}$$

$$V_T \ln(2) = \frac{I_{REF} R_p}{2}$$

$$R_p = 2 \cdot \ln(2) \cdot (V_T / I_{REF})$$

41.

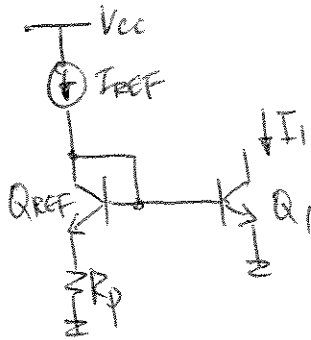

$$Q_{REF} = Q_1$$

$$\beta \rightarrow \infty$$


By KVL,  $V_{BE,REF} + I_{REF} R_P = V_{BE,1}$

$$\Rightarrow V_T \ln \left( \frac{I_{REF}}{I_{S,REF}} \right) + I_{REF} R_P = V_T \ln \left( \frac{2 I_{REF}}{I_{S,1}} \right)$$

$$I_{REF} R_P = V_T \ln(2)$$

$$R_P = \frac{V_T \ln(2)}{I_{REF}}$$


42.

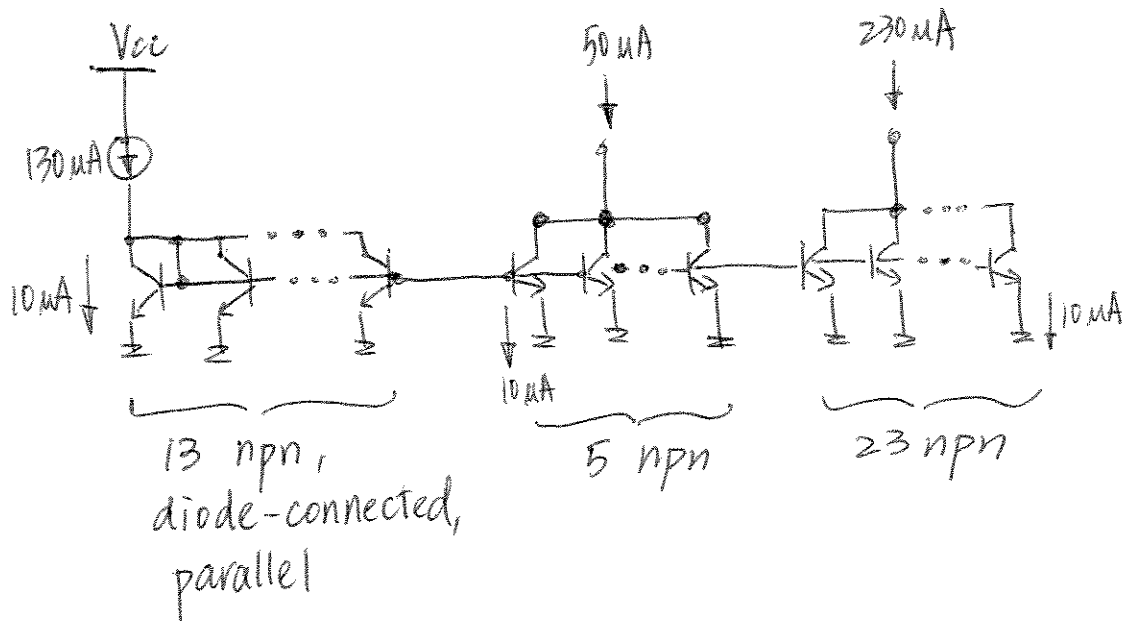


All the bases are the same node.

If the area of BJT is flexible, the 5-npn group can be replaced by one BJT that is 5 times as big in area. Similar concept applies to 23-npn grouping.

43.

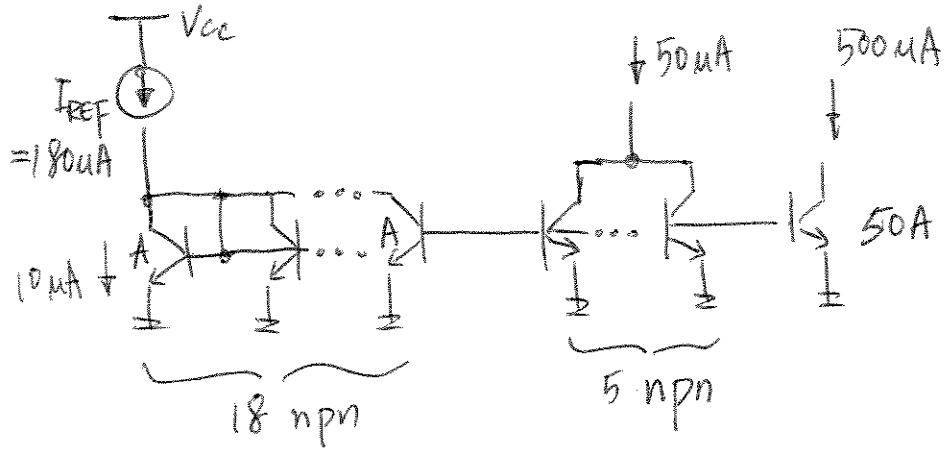

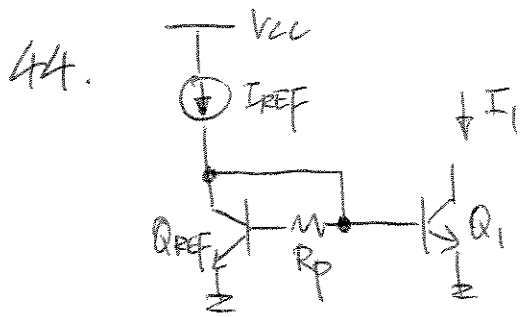

$$Q_{REF} = Q_1$$

$I_1$  10% larger. ( $I_1 = 1.1 I_{C,REF}$ )  
Solve for  $R_P$ .

By KVL,

$$V_{BE,REF} + \frac{I_{C,REF} \cdot R_P}{\beta} = V_{BE,1}$$

$$\Rightarrow V_T \ln\left(\frac{I_1}{I_S}\right) - V_T \ln\left(\frac{I_{C,REF}}{I_S}\right) = \frac{I_{C,REF}}{\beta} \cdot R_P$$

$$V_T \ln\left(\frac{I_1}{I_{C,REF}}\right) = \frac{I_{C,REF}}{\beta} \cdot R_P$$


$$\Rightarrow V_T \ln(1.1) = \frac{I_{C,REF}}{\beta} R_P \quad \Rightarrow I_{C,REF} = \frac{\beta V_T \ln(1.1)}{R_P}$$

By KCL,  $I_{REF} = I_{C,REF} + I_{C,REF}/\beta + I_1/\beta$

$$= \frac{\beta}{R_P} V_T \ln(1.1) \cdot \left(1 + \frac{1}{\beta}\right) + \frac{I_1}{\beta}$$

$$\therefore R_P = \frac{(\beta + 1) V_T \ln(1.1)}{I_{REF} - I_1/\beta}$$

45.

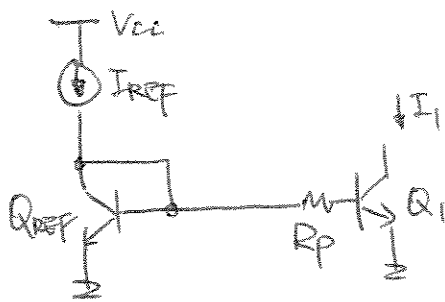

$$I_1 = 0.9 I_{C, REF}$$

By KVL,  $V_{BE, REF} = \frac{I_1}{\beta} R_P + V_{BE, 1}$

$$\Rightarrow V_T \ln\left(\frac{I_{C, REF}}{I_1}\right) = \frac{I_1}{\beta} R_P$$

$$V_T \ln\left(\frac{1}{0.9}\right) = 0.9 I_{C, REF} \frac{R_P}{\beta}$$

$$\Rightarrow I_{C, REF} = \frac{\beta}{0.9 R_P} V_T \ln\left(\frac{1}{0.9}\right)$$

By KCL,


$$I_{REF} = I_{C, REF} + I_{C, REF}/\beta + I_1/\beta$$

$$\therefore I_{REF} - \frac{I_1}{\beta} = \frac{\beta}{0.9 R_P} V_T \ln\left(\frac{1}{0.9}\right) \left(1 + \frac{1}{\beta}\right)$$

$$\Rightarrow R_P = \frac{(\beta + 1) V_T \ln(10/9)}{0.9 (I_{REF} - I_1/\beta)}$$



4b (a)

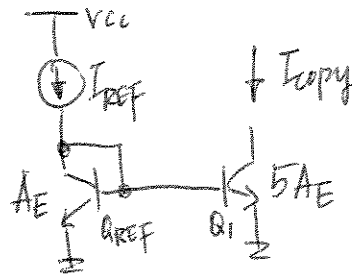

$Q_1$  has  $I_s$  5 times  
as that of  $Q_{REF}$


$$\Rightarrow I_{C_{REF}} = I_{COPY} / 5$$

By KCL,

$$\begin{aligned} I_{REF} &= I_{C_{REF}} + \frac{I_{C_{REF}}}{\beta} + \frac{I_{COPY}}{\beta} \\ &= \frac{I_{COPY}}{5} \left( 1 + \frac{1}{\beta} \right) + \frac{I_{COPY}}{\beta} \end{aligned}$$

$$\therefore I_{COPY} = I_{REF} \left( \frac{5\beta}{\beta+6} \right)$$
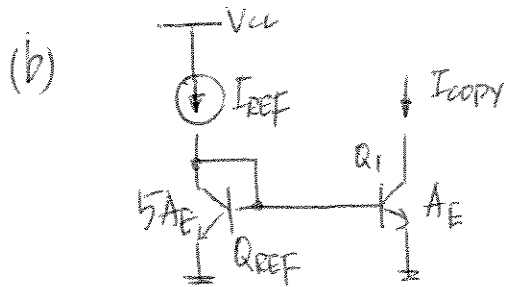
$$\therefore \text{error} = \frac{I_{COPY}}{I_{REF}} = \frac{5\beta}{\beta+6}$$




$Q_1$  &  $Q_{REF}$  have the same  $V_{BE}$ , but area of  $Q_{REF}$  is 5 times larger

$$\Rightarrow I_{C, REF} = 5 \cdot I_{COPY}$$

By KCL,

$$\begin{aligned} I_{REF} &= I_{C, REF} + \frac{I_{C, REF}}{\beta} + \frac{I_{COPY}}{\beta} \\ &= I_{COPY} \cdot 5 + \left(1 + \frac{1}{\beta}\right) + I_{COPY} \left(\frac{1}{\beta}\right) \end{aligned}$$
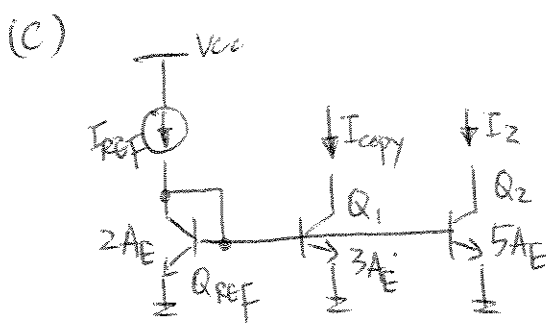
$$\therefore I_{COPY} = I_{REF} \left( \frac{\beta}{5\beta + 6} \right)$$



$Q_1$  &  $Q_{REF}$  have identical  $V_{BE}$ , but area of  $Q_1$  is 1.5 times larger.


$$\Rightarrow 3 I_{C, REF} = 2 I_{COPY}$$

By KCL,

$$\begin{aligned} I_{REF} &= I_{C, REF} + \frac{I_{C, REF}}{\beta} + \frac{I_{COPY}}{\beta} + \frac{I_2}{\beta} \\ &= I_{COPY} \left( \frac{2}{3} \right) \left[ \left(1 + \frac{1}{\beta}\right) + \frac{1}{\beta} + \frac{5}{3} \left(\frac{1}{\beta}\right) \right] \end{aligned}$$

$$\Rightarrow I_{COPY} = \frac{9\beta}{6\beta + 22} I_{REF}$$

47.

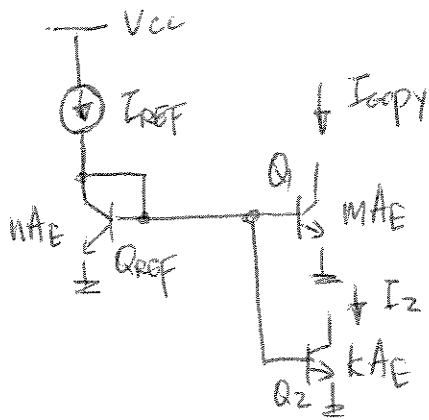


By observing the areas of the BJTs,

$$I_{C,REF} = \left(\frac{n}{m}\right) I_{COPY} = \left(\frac{n}{k}\right) I_2$$

By KCL, 
$$I_{C,REF} = I_{REF} - \frac{I_{C,REF}}{\beta} - \frac{I_{COPY}}{\beta} - \frac{I_2}{\beta}$$

$$\Rightarrow \frac{n}{m} I_{COPY} = I_{REF} - \frac{\left(\frac{n}{m}\right) I_{COPY}}{\beta} - \frac{I_{COPY}}{\beta} - \frac{\left(\frac{k}{m}\right) I_{COPY}}{\beta}$$
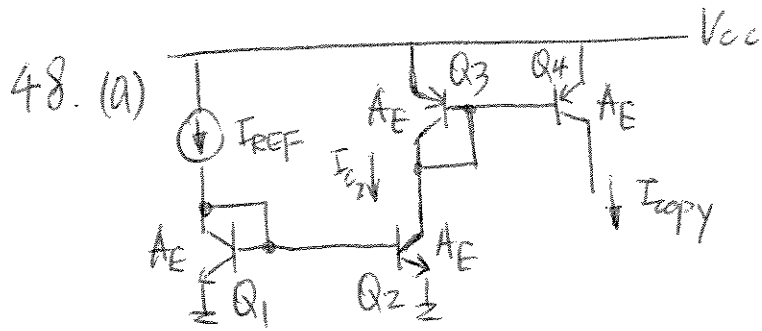
$$\therefore I_{COPY} = I_{REF} \left[ \frac{\beta m}{(\beta+1)n + k + m} \right]$$



$$V_{BE1} = V_{BE2}$$

$$\Rightarrow I_{C1} = I_{C2}$$

$$V_{BE3} = V_{BE4}$$


$$\Rightarrow I_{C3} = I_{C4}$$

First compute  $I_{C1,2}$ :

$$I_{C1} = I_{REF} - \frac{I_{C1}}{\beta} - \frac{I_{C2}}{\beta} \Rightarrow I_{C2} = \frac{\beta}{\beta+2} \cdot I_{REF}$$

View  $I_{C2}$  as the "I<sub>REF</sub>" for the Q<sub>3</sub>-Q<sub>4</sub> current mirror and apply the equation derived.
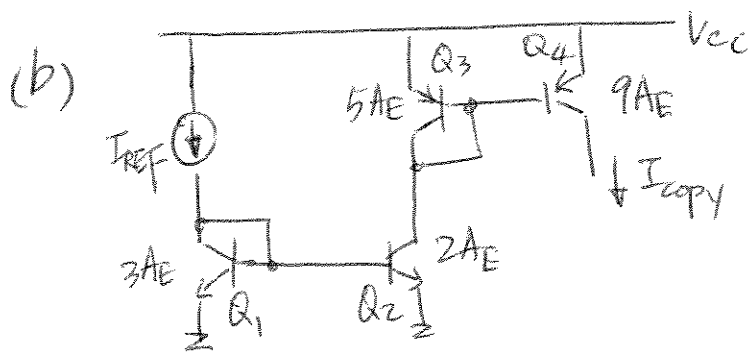
$$\Rightarrow I_{copy} = \frac{\beta}{\beta+2} \left[ \frac{\beta}{\beta+2} \cdot I_{REF} \right] = I_{REF} \left( \frac{\beta}{\beta+2} \right)^2$$



$$V_{BE1} = V_{BE2} \because$$

$$\Rightarrow I_{C1} = \frac{3}{2} I_{C2}$$

$$V_{BE3} = V_{BE4} \because$$

$$\Rightarrow I_{copy} = \frac{9}{5} I_{C3}$$

- By KCL,

$$I_{REF} = I_{C1} + \frac{I_{C1}}{\beta} + \frac{I_{C2}}{\beta}$$

$$\Rightarrow I_{C2} = \frac{2\beta}{3\beta+5} I_{REF} \quad \textcircled{1}$$

- By KCL,


$$I_{C2} = I_{C3} + \frac{I_{C3}}{\beta} + \frac{I_{copy}}{\beta}$$

$$\Rightarrow I_{copy} = \frac{9\beta}{5\beta+14} I_{C2}$$

Substitute  $\textcircled{1}$  into  $I_{copy}$  :

$$\therefore I_{copy} = \frac{9\beta}{5\beta+14} \cdot \frac{2\beta}{3\beta+5} \cdot I_{REF}$$

49.

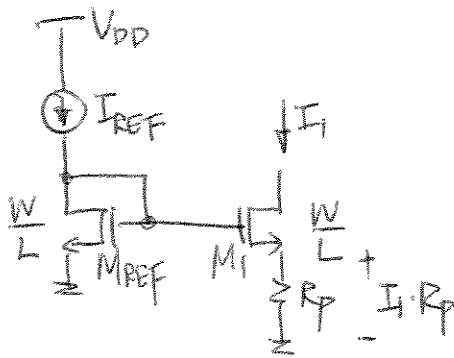

Determine  $R_P$  such that  $I_1 = \frac{I_{REF}}{2}$ .

First calculate  $V_{GS, REF}$ :

$$V_{GS, REF} = \sqrt{\frac{2 I_{REF}}{n \mu_n C_{ox} \frac{W}{L}}} + V_{TH} \quad \text{--- ①}$$

Assuming  $M_1$  in saturation:


$$I_1 = \frac{I_{REF}}{2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [V_{GS1} - V_{TH}]^2$$

$$\Rightarrow \frac{I_{REF}}{2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [V_{GS, REF} - \frac{I_{REF}}{2} R_P - V_{TH}]^2$$

Rearrange, substitute ① into equation above and solve for  $R_P$ :

$$\therefore R_P = \frac{2(\sqrt{2}-1)}{\sqrt{I_{REF} \cdot \mu_n C_{ox} \frac{W}{L}}}$$

50.

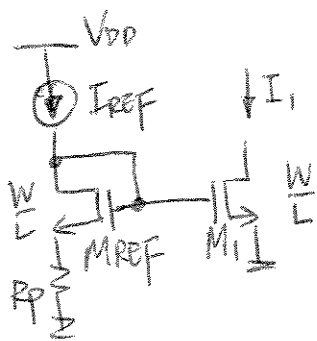

Determine  $R_p$  such that  $I_1 = 2I_{REF}$ .

First calculate  $V_{GS1}$ :

$$V_{GS1} = \sqrt{\frac{2I_1}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} + V_{TH} = 2 \sqrt{\frac{I_{REF}}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} + V_{TH} \quad \text{--- (1)}$$

Assuming  $I_1$  is in saturation:

$$\begin{aligned} I_{REF} &= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS, REF} - V_{TH})^2 \\ &= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) [V_{GS1} - I_{REF} R_p - V_{TH}]^2 \end{aligned}$$


Substitute (1) into  $I_{REF}$ :

$$I_{REF} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) \left[ 2 \sqrt{\frac{I_{REF}}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} - I_{REF} R_p \right]^2 \quad \text{--- (2)}$$

$$\text{Solve for } R_p: \quad R_p = \frac{(2 - \sqrt{2})}{\sqrt{I_{REF}} \cdot \mu_n C_{ox} \left(\frac{W}{L}\right)}$$

From (2), we find that  $R_p$  is independent of any change in  $V_{TH}, \Delta V$  !!

51.

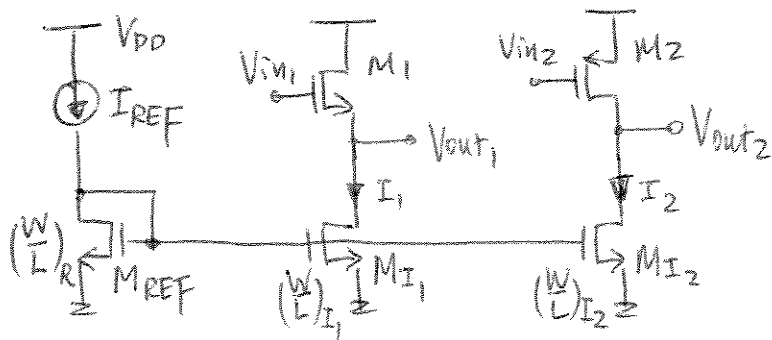

This figure implies that  $V_{GS, REF} = V_{GS, I_1} = V_{GS, I_2}$ .  
 Assuming all devices operate in saturation, with  $(V_{GS} - V_{TH})$  fixed,  $I_D \propto (\frac{W}{L})$


$$\Rightarrow \text{we have } (\frac{W}{L})_R = 7 (\frac{W}{L})$$

$$(\frac{W}{L})_{I_1} = 4 (\frac{W}{L})$$

$$(\frac{W}{L})_{I_2} = 10 (\frac{W}{L})$$



52. (a)

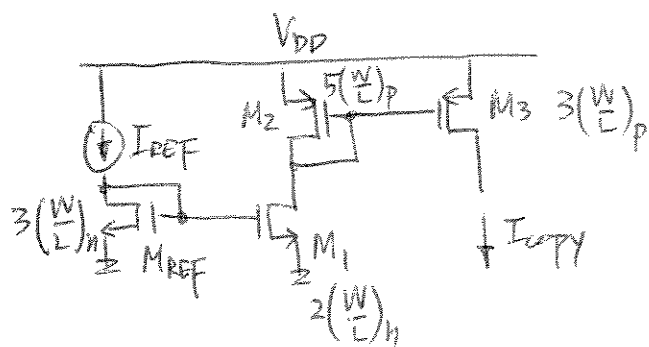


$$V_{GS, REF} = V_{GS, 1} \quad \Rightarrow \quad I_{D, 1} = \frac{2}{3} I_{REF}$$

$$V_{GS, 2} = V_{GS, 3} \quad \Rightarrow \quad I_{COPY} = \frac{3}{5} I_{D, 2} = \frac{3}{5} I_{D, 1}$$

$$= \frac{3}{5} \cdot \left( \frac{2}{3} I_{REF} \right) = \frac{2}{5} I_{REF}$$

(b)

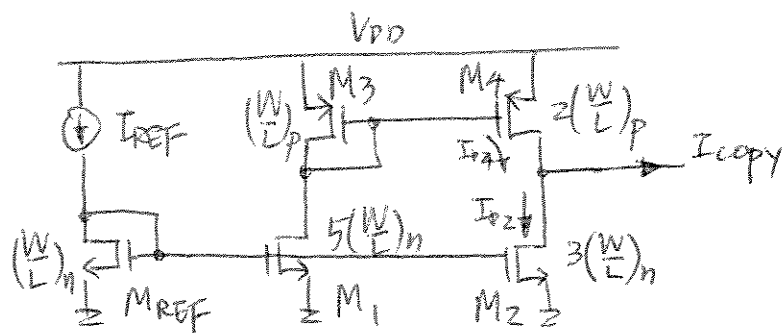


$$V_{GS, REF} = V_{GS, 1} \quad \Rightarrow \quad I_{D, 1} = 5 I_{REF}$$

$$V_{GS, 3} = V_{GS, 4} \quad \Rightarrow \quad I_{D, 4} = 2 I_{D, 3} = 2 I_{D, 1} = 10 I_{REF}$$

$$V_{GS, REF} = V_{GS, 2} \quad \Rightarrow \quad I_{D, 2} = 3 I_{REF}$$

$$\therefore I_{COPY} = I_{D, 4} - I_{D, 2} = 7 I_{REF}$$

53.

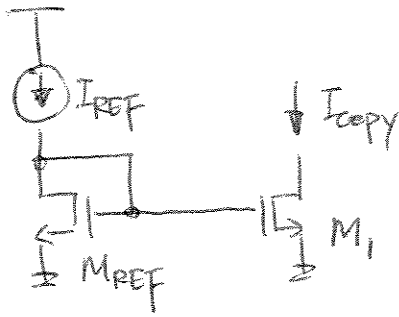

$$V_{GS, REF} = V_{GS, 1} = V_{GS}$$

$$\lambda \neq 0$$

$$(a) \quad I_{REF} = \frac{1}{2} \mu_n C_{OX} \left(\frac{W}{L}\right) (V_{GS} - V_{TH})^2 (1 + \lambda V_{GS})$$



$$I_{COPY} = \frac{1}{2} \mu_n C_{OX} \left(\frac{W}{L}\right) (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS, 1})$$

$$\text{For } I_{REF} = I_{COPY} \Rightarrow V_{DS, 1} = V_{GS}$$

$$(b) \quad \frac{I_{REF}}{I_{COPY}} = \frac{1 + \lambda V_{GS}}{1 + \lambda (V_{GS} - V_{TH})}$$

$$\Rightarrow I_{COPY} = I_{REF} \left( 1 - \frac{\lambda V_{TH}}{1 + \lambda V_{GS}} \right)$$

54.

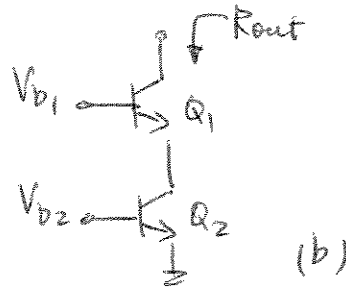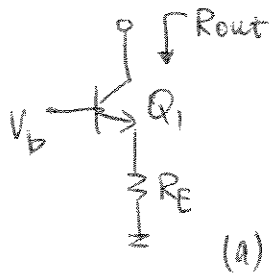

Given  $I_{BIAS} = 1\text{mA}$ ,  $V_{RE} \approx V_{CE,2} \approx 0.5\text{V}$ ,  
design the circuit.

$R_E$  can be readily calculated:

$$R_E = \frac{V_{RE}}{I_{BIAS}/\alpha} = \frac{0.5\text{V}}{1\text{mA}/0.909} = 505\Omega$$

$$V_{be_1} = V_T \ln\left(\frac{I_{BIAS}}{I_{S,1}}\right) = (0.026\text{V}) \ln\left(\frac{1\text{mA}}{6 \cdot 10^{-16}\text{A}}\right) \approx 0.732\text{V}$$

$$\Rightarrow V_b = V_{be_1} + V_{RE} = 0.732\text{V} + 0.5\text{V} = 1.232\text{V}$$


$$R_{out(a)} = [1 + g_{m_1}(R_E \parallel r_{\pi_1})] r_{o_1} + (R_E \parallel r_{\pi_1})$$

$$R_{out(b)} = [1 + g_{m_1}(r_{o_2} \parallel r_{\pi_1})] r_{o_1} + (r_{o_2} \parallel r_{\pi_1})$$

In most cases  $r_o > r_{\pi} > R_E$

$\therefore R_{out(b)}$  is relatively larger than  $R_{out(a)}$

55.

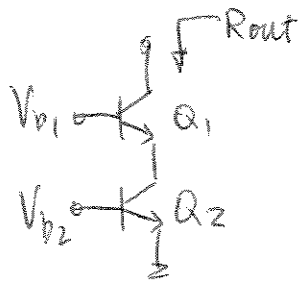

$$I_{BIAS} = 1 \text{ mA}$$

$$\beta = 100$$

Given  $R_{out} = 50 \text{ k}\Omega$ ,  $V_{BC2} = 100 \text{ mV}$ ,  
determine  $V_{b1}$ .

$$R_{out} = [1 + g_{m1} (r_{o2} \parallel r_{\pi 1})] r_{o1} + (r_{o2} \parallel r_{\pi 1})$$

$$\approx g_{m1} (r_{o2} \parallel r_{\pi 1}) r_{o1}$$

$$= \frac{\beta V_A^2}{(V_A + \beta V_T) I_{BIAS}}$$

$$\Rightarrow I_{BIAS} = \left[ \frac{R_{out} (V_A + \beta V_T)}{\beta V_A^2} \right]^{-1} = \left[ \frac{(50 \text{ k}\Omega) (5 \text{ V} + 100 \cdot 0.026 \text{ V})}{100 (5 \text{ V})^2} \right]^{-1}$$

$$\approx 6.6 \text{ mA}$$

$$V_{b2} = V_{BE2} = V_T \ln \left( \frac{I_{BIAS}}{I_S} \right) = (0.026 \text{ V}) \ln \left( \frac{6.6 \text{ mA}}{6 \cdot 10^{-16} \text{ A}} \right)$$


$$\approx 0.78 \text{ V}$$

$$\Rightarrow V_{C2} = V_{BE2} - 100 \text{ mV} = 0.68 \text{ V}$$

$$\therefore V_{b1} = V_{C2} + V_{BE1} = V_{C2} + V_T \ln \left( \frac{I_{BIAS}}{I_S} \right)$$

$$= 0.68 \text{ V} + (0.026 \text{ V}) \ln \left( \frac{6.6 \text{ mA}}{6 \cdot 10^{-16} \text{ A}} \right) \approx 1.46 \text{ V}$$

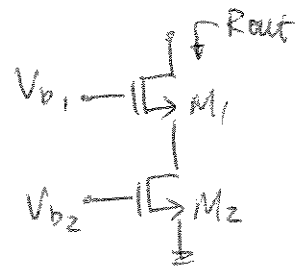5b. Given  $R_{out} = 200 \text{ k}\Omega$   
 $I_{BIAS} = 0.5 \text{ mA}$



(a) Determine  $(W/L)_1 = (W/L)_2$  with  $\lambda = 0.1 \text{ V}^{-1}$

$$R_{out} = (1 + g_{m1} r_{o2}) r_{o1} + r_{o2}$$

$$= \left[ 1 + \sqrt{2 I_{BIAS} \mu_n C_{ox} \left(\frac{W}{L}\right)_1} \cdot \frac{1}{\lambda I_{BIAS}} \right] \frac{1}{\lambda I_{BIAS}} + \frac{1}{\lambda I_{BIAS}}$$

$$\therefore \left(\frac{W}{L}\right)_1 \cong \frac{\left[ \left( R_{out} - \frac{1}{\lambda I_{BIAS}} \right) (\lambda I_{BIAS})^2 \right]^2}{2 I_{BIAS} \mu_n C_{ox}}$$

$$= \frac{\left\{ \left[ 200 \text{ k}\Omega - \frac{1}{(0.1 \text{ V}^{-1})(0.5 \text{ mA})} \right] (0.1 \text{ V}^{-1})^2 (0.5 \text{ mA})^2 \right\}^2}{2 (0.5 \text{ mA}) (100 \frac{\mu\text{A}}{\text{V}^2})}$$


$$\approx 2.0$$

$$(b) I_{BIAS} = 0.5 \text{ mA} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{b2} - V_{TH,n})^2$$

$$\Rightarrow V_{b2} = \sqrt{\frac{2 I_{BIAS}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} + V_{TH}$$

$$= \sqrt{\frac{2 (0.5 \text{ mA})}{(100 \frac{\mu\text{A}}{\text{V}^2}) (2.0)}} + 0.4 \text{ V} \approx 2.62 \text{ V}$$

57. Given  $|A_v| = 500$   
 $\beta = 100$

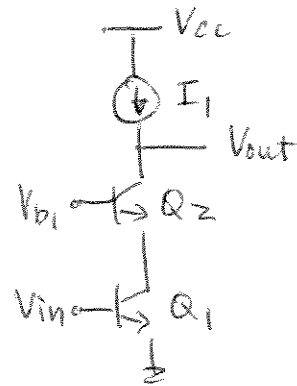

(a)  $A_v = -g_{m1} r_{o1} g_{m2} (r_{o1} \parallel r_{\pi 2})$

$$= -\frac{V_A}{V_T} \times \frac{I_{C2}}{V_T} \left( \frac{V_A}{I_{C1}} \parallel \frac{\beta}{g_{m2}} \right)$$

Assume  $I_{C1} \approx I_{C2}$ . After expanding  $(r_{o1} \parallel r_{\pi 2})$ ,

$$A_v \approx -\frac{V_A/V_T}{\frac{V_T}{V_A} + \frac{1}{\beta}} \Rightarrow V_A^2 + V_A \left( \frac{V_T A_v}{\beta} \right) + (A_v V_T^2) = 0$$

$$\Rightarrow V_A \approx 0.65 \text{ V}$$

(b)  $V_{in} = V_T \ln\left(\frac{I_1}{I_S}\right) = (0.026 \text{ V}) \ln\left(\frac{0.5 \text{ mA}}{6 \cdot 10^{-16} \text{ A}}\right)$   
 $\approx 0.71 \text{ V}$

(c)  $V_{b1} = V_{BE2} + 500 \text{ mV}$   
 $= V_T \ln\left(\frac{I_1}{I_S}\right) + 0.5 \text{ V}$   
 $= 0.71 \text{ V} + 0.5 \text{ V} = 1.21 \text{ V}$

58. Given power budget = 2mW  
 $V_{BC1} = V_{CB4} = 200 \text{ mV}$ ,  
 calculate voltage gain.

$$\alpha_p = \frac{50}{50+1} \approx 0.98$$

$$\alpha_n = \frac{100}{100+1} \approx 0.99$$

$\therefore$  we assume  $I_{C,p} \approx I_{E,p}$  &  $I_{C,n} \approx I_{E,n}$


This implies that 
$$I_{BIAS} = \frac{\text{Power}}{V_{CC}} = \frac{2 \text{ mW}}{2.5 \text{ V}} \approx 0.8 \text{ mA}$$

$$\Rightarrow V_{BE1} = V_{in} = V_T \ln\left(\frac{I_{BIAS}}{I_{S1}}\right) = (0.026 \text{ V}) \cdot \ln\left(\frac{0.8 \text{ mA}}{6 \cdot 10^{-16} \text{ A}}\right) \approx 0.726 \text{ V}$$

$$V_{C11} = V_{BE1} - V_{BC1} = 0.726 \text{ V} - 0.2 \text{ V} = 0.526 \text{ V}$$

$$\therefore V_{b1} = V_{C1} + V_{BE2} = (0.526 \text{ V}) + (0.026 \text{ V}) \ln\left(\frac{0.8 \text{ mA}}{6 \cdot 10^{-16} \text{ A}}\right) \approx 1.252 \text{ V}$$
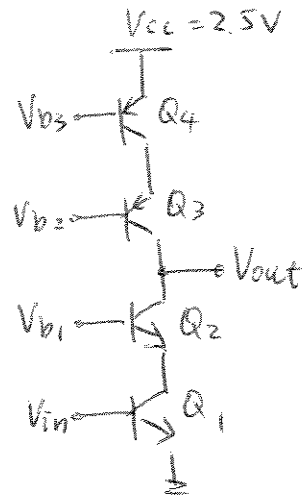
$$\Rightarrow V_{EB4} = V_{CC} - V_{b3} = V_T \ln\left(\frac{I_{BIAS}}{I_{S4}}\right) = 0.026 \text{ V} \cdot \ln\left(\frac{0.8 \text{ mA}}{6 \cdot 10^{-16} \text{ A}}\right) \approx 0.726 \text{ V}$$



$$V_{b3} = V_{cc} - 0.726V = 1.774V$$

$$V_{c4} = V_{D3} + V_{CB4} = 1.774V + 0.2V = 1.974V$$

$$\therefore V_{b2} = V_{c4} - V_{EB3} = (1.974V) - (0.026) \ln\left(\frac{0.8mA}{6 \cdot 10^{-16}A}\right)$$

$$\approx 1.248V$$

$$A_v = -g_{m1} \left\{ [g_{m2} r_{D2} (r_{o1} \parallel r_{\pi2})] \parallel [g_{m3} r_{D3} (r_{o4} \parallel r_{\pi3})] \right\}$$

After simplifying,  $A_v$  is independent of  $I_{BIAS}$ :


$$A_v \approx \frac{V_{AN} \cdot V_{AP}}{V_T^2 \left( \frac{V_{AP}}{V_{AN}} + \frac{V_{AP}}{\beta_N V_T} + \frac{V_{AN}}{V_{AP}} + \frac{V_{AN}}{\beta_P V_T} \right)}$$

$$= \frac{5.5}{(0.026V)^2 \left( \frac{5}{5} + \frac{5}{100 \cdot 0.026} + \frac{5}{5} + \frac{5}{50 \cdot 0.026} \right)}$$

$$\approx 4760$$



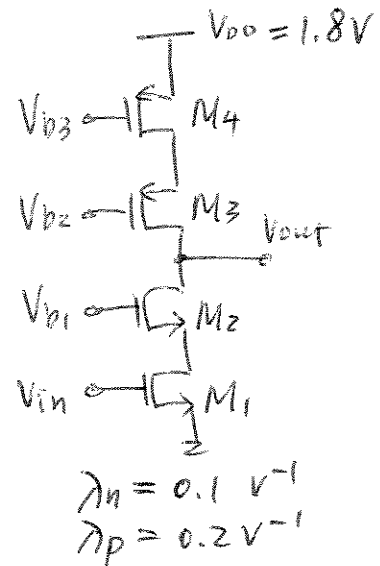59. Given  $A_v = 200$   
 power budget = 2mW  
 all  $(\frac{W}{L}) = \frac{20}{0.18}$   
 $V_{b1} = V_{b2} = 0.9V$



calculate  $V_{in}$  &  $V_{b3}$

$$A_v \approx -g_{m1} (g_{m2} r_{o1} r_{o2} \parallel g_{m3} r_{o3} r_{o4}) = 200$$

$$\text{power} = V_{DD} \times I_{BIAS} \Rightarrow I_{BIAS} = \frac{\text{power}}{V_{DD}} = \frac{2\text{mW}}{1.8V} \approx 1.11\text{mA}$$

$$g_{m2} r_{o1} r_{o2} = \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right) I_{BIAS} \left(\frac{1}{\lambda_n I_{BIAS}}\right)^2}$$

$$= \sqrt{2 \cdot 100\text{MA} \cdot \frac{20}{0.18} \cdot 1.11\text{mA} \cdot \left[\frac{1}{(0.1\text{V}^{-1})(1.11\text{mA})}\right]^2}$$

$$\approx 403\text{K}\Omega$$

$$g_{m3} r_{o3} r_{o4} \approx 71\text{K}\Omega$$

We know that  $\frac{|A_v|}{(g_{m2} r_{o1} r_{o2} \parallel g_{m3} r_{o3} r_{o4})} = g_{m1} = \frac{2I_D}{V_{GS1} - V_{TH}}$

$$\therefore V_{in} = V_{GS1} = V_{TH} + 2I_D \cdot \frac{g_{m2} r_{o1} r_{o2} \parallel g_{m3} r_{o3} r_{o4}}{A_v}$$

$$= (0.4 \text{ V}) + 2(1.11 \text{ mA}) \frac{(403 \text{ k}\Omega \parallel 71. \text{ k}\Omega)}{200}$$

$$\approx 1.07 \text{ V}$$


$$g_{m4} = \frac{2I_D}{V_{DD} - V_{D3} - |V_{THP}|} = \sqrt{2 \mu_p C_{ox} \frac{W}{L} I_D}$$

$$\therefore V_{D3} = V_{DD} - |V_{THP}| - \frac{2I_D}{\sqrt{2 \mu_p C_{ox} \frac{W}{L} I_D}}$$

$$= (1.8 \text{ V}) - (0.5 \text{ V}) - \frac{2(1.11 \text{ mA})}{\sqrt{2 \cdot (50 \frac{\mu\text{A}}{\text{V}^2}) \left(\frac{20}{0.18}\right) (1.11 \text{ mA})}}$$

$$\approx 0.67 \text{ V}$$

60.

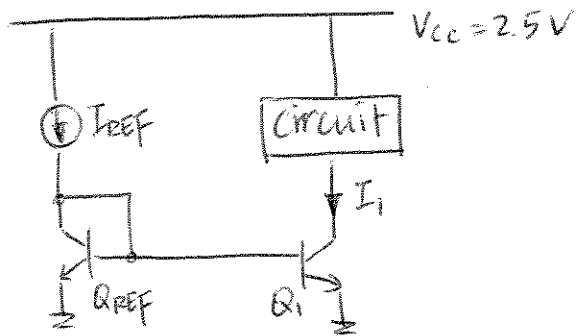

$$I_1 = 0.5 \text{ mA}$$

$$\text{power} = 2 \text{ mW}$$


$$\text{Power} = V_{CC} (I_{REF} + I_1)$$

$$\Rightarrow I_{REF} = \frac{\text{Power}}{V_{CC}} - I_1 = \frac{2 \text{ mW}}{2.5 \text{ V}} - 0.5 \text{ mA} = 0.3 \text{ mA}$$

Therefore, if  $Q_{REF}$  has area  $A_E$ , then  $Q_1$  has area  $\frac{5}{3} A_E$  for the currents specified.

$$\text{i.e. } \frac{A_{REF}}{A_1} = \frac{3}{5}$$

61.

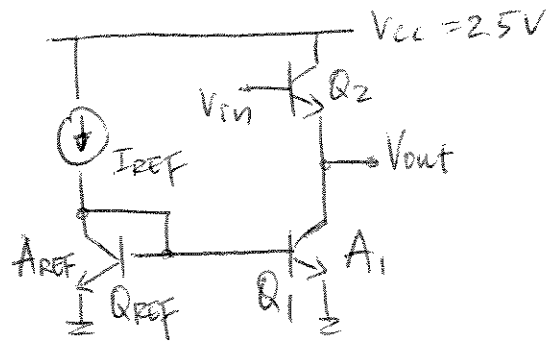

$$\text{power} = 3\text{mW}$$

$$R_{out} = 50\Omega$$

For an emitter follower,  $R_{out} = r_{\pi 2} \parallel \frac{1}{g_{m2}}$

$$\Rightarrow R_{out} = 50\Omega = \frac{1}{\frac{I_{c2}}{V_T} \left(1 + \frac{1}{\beta}\right)}$$

$$\therefore I_{c2} = \frac{V_T}{R_{out}} \cdot \frac{1}{1 + 1/\beta} = \frac{0.026}{50} \frac{1}{1 + 0.01} \approx 0.51\text{mA}$$


Realize that  $V_{cc}$  is providing current through  $I_{REF}$  &  $I_{c2}$ , and we are given

$$\text{power} = V_{cc} (I_{REF} + I_{c2}) = 3\text{mW}$$

$$\Rightarrow I_{REF} = \frac{\text{power}}{V_{cc}} - I_{c2} = \frac{3\text{mW}}{2.5\text{V}} - 0.51\text{mA} \approx 0.69\text{mA}$$

$$\Rightarrow \frac{I_{c2}}{I_{REF}} = \frac{A_1}{A_{REF}} = \frac{0.51}{0.69} \approx \frac{5}{7}$$

62.

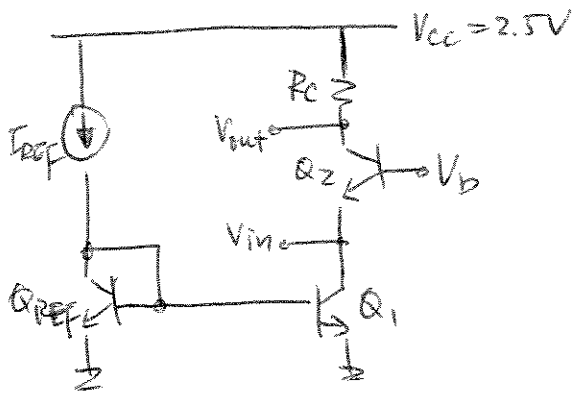

$$R_{out} = 50.5 \Omega$$

$$A_v = 20$$

$$\text{power} = 1.5 \text{ mW}$$

$$\beta \gg 1, V_A \rightarrow \infty$$

$$R_{out} = R_C \Rightarrow R_C = 50.5 \Omega$$

$$A_v = g_m R_C = 20 \Rightarrow g_m = \frac{A_v}{R_C} = \frac{I_{C2}}{V_T}$$


$$\Rightarrow I_{C2} = \frac{A_v V_T}{R_C} = \frac{20 (0.026 \text{ V})}{50.5 \Omega} \approx 10.4 \text{ mA}$$

Realize that  $V_{CC}$  is providing current through  $I_{REF}$  &  $I_{C2}$ :

$$\text{power} = V_{CC} (I_{REF} + I_{C2})$$

$$\Rightarrow I_{REF} = \frac{\text{power}}{V_{CC}} - I_{C2} = \frac{1.5 \text{ mW}}{2.5 \text{ V}} - 10.4 \text{ mA}$$

63.

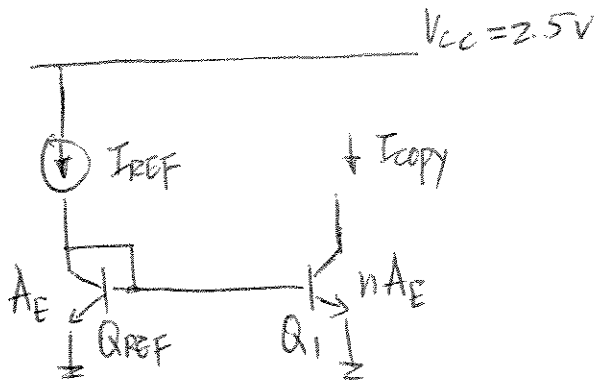Given  $I_{copy} = 0.5 \text{ mA}$ 

$$\begin{aligned} \text{By KCL, } I_{REF} &= I_{C,REF} + \frac{I_{C,REF}}{\beta} + \frac{I_{copy}}{\beta} \\ &= \frac{I_{copy}}{n} + \frac{I_{copy}/n}{\beta} + \frac{I_{copy}}{\beta} \end{aligned}$$

$$\Rightarrow I_{copy} = I_{REF} \cdot \frac{n}{1 + \frac{1}{\beta}(n+1)} = 0.5 \text{ mA}$$


Within 1% implies that :

$$\Rightarrow I_{REF} \geq \frac{0.5 \text{ mA}}{0.99} \approx 0.505 \text{ mA}$$

- For given  $n$  and  $\beta$ ,  $I_{copy} \leq n I_{REF}$ . Since the error term causes  $I_{copy} < n I_{REF}$  (strictly less than), one needs to increase  $I_{REF}$  in order to maintain the desired  $I_{copy}$ . This, however, means an increase of power (i.e.  $\Delta p = V_{CC} \cdot \Delta I_{REF}$ )

$\Rightarrow$  Trade off between accuracy & power dissipation.

64.

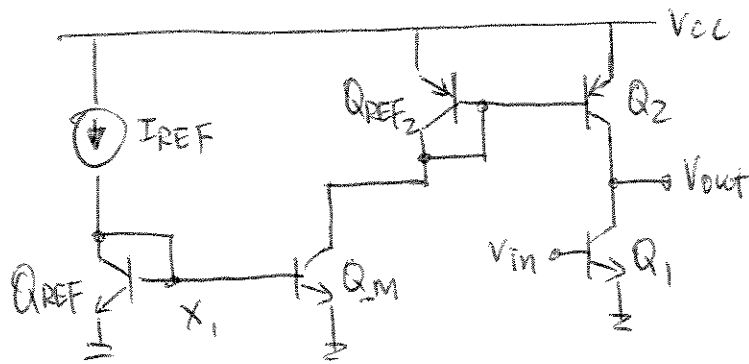

$$I_{C2} = I_{REF} \frac{(A_M/A_{REF})}{1 + \frac{1}{\beta_n} (A_M/A_{REF} + 1)} \cdot \frac{(A_2/A_{REF2})}{1 + \frac{1}{\beta_p} (A_2/A_{REF2} + 1)}$$

X

Given  $I_{C,M} \geq 0.98 I_{REF}$  (less than 2% error)


$$I_{C2} = 1 \text{ mA} = 0.98 I_{REF} \cdot \frac{A_2/A_{REF2}}{1 + \frac{1}{50} (A_2/A_{REF2} + 1)}$$

Suppose  $X = 0.98$  &  $I_{REF} = 2 \text{ mA}$ .

$$\Rightarrow \frac{A_2}{A_{REF2}} \approx 0.5$$

Solution is not unique because no power constraint is present (i.e.  $I_{REF}$  is arbitrary.)

65.

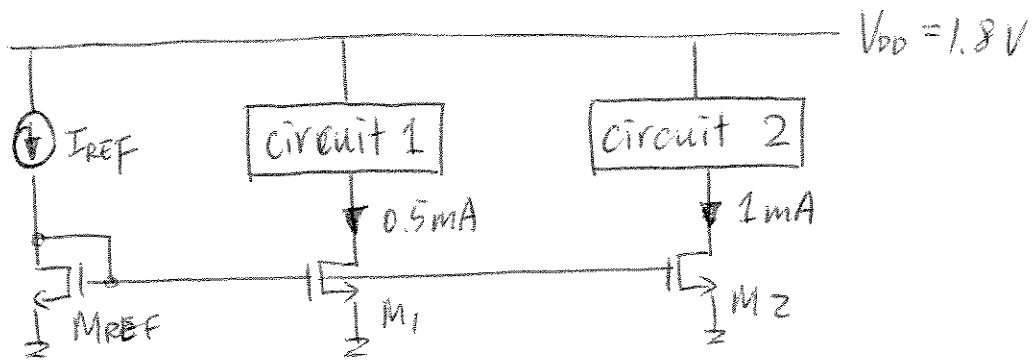

power budget =  $3\text{ mW}$ .

$$\text{power} = V_{DD} (I_{REF} + 0.5\text{ mA} + 1\text{ mA})$$

$$\Rightarrow I_{REF} = \frac{\text{power}}{V_{DD}} - 0.5\text{ mA} - 1\text{ mA} \approx 0.17\text{ mA}$$

Assuming  $M_1$  &  $M_2$  operate in saturation,


If  $M_{REF}$  has  $(\frac{W}{L})_{REF}$ , then

$$\frac{(W/L)_1}{(W/L)_{REF}} = \frac{I_1}{I_{REF}} = \frac{50}{17}$$

$$\frac{(W/L)_2}{(W/L)_{REF}} = \frac{I_2}{I_{REF}} = \frac{100}{17}$$



66.

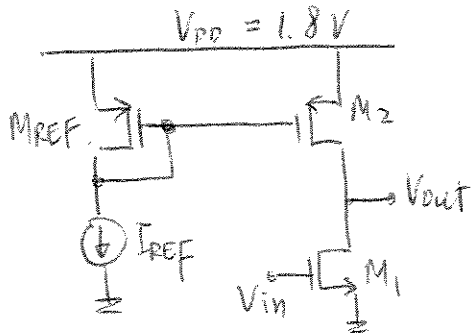

$$A_v = -20$$

$$\text{power} = 2 \text{ mW}$$

$$\left(\frac{W}{L}\right)_1 = \frac{20}{0.18}$$

$$\lambda_n = 0.1 \text{ V}^{-1}$$

$$\lambda_p = 0.2 \text{ V}^{-1}$$

$$R_{out} = r_{o2} \parallel r_{o1} = \frac{1}{\lambda_n I_{D1} + \lambda_p I_{D1}}$$

$$\Rightarrow A_v = -g_{m1} R_{out} = \frac{-g_{m1}}{\lambda_n I_{D1} + \lambda_p I_{D1}} = -\frac{2 I_{D1} / (V_{GS1} - V_{THn})}{I_{D1} (\lambda_n + \lambda_p)}$$

$$\Rightarrow -20 = -\frac{2}{(V_{GS1} - V_{THn})(\lambda_n + \lambda_p)}$$

$$\Rightarrow V_{GS1} = \frac{1}{10(\lambda_n + \lambda_p)} + V_{THn}$$

$$= \frac{1}{10(0.1 + 0.2) \text{ V}^{-1}} + 0.4 \text{ V} \approx 0.73 \text{ V}$$

$$\Rightarrow I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{THn})^2$$

$$= \frac{1}{2} (100 \frac{\mu\text{A}}{\text{V}^2}) \left(\frac{20}{0.18}\right) (0.33 \text{ V})^2 \approx 0.61 \text{ mA}$$

$$\therefore \text{power} = V_{DD} (I_{REF} + I_{D1})$$


$$\Rightarrow I_{REF} = \frac{\text{power}}{V_{DD}} - I_{D1} = \frac{2 \text{ mW}}{1.8 \text{ V}} - 0.61 \text{ mA}$$

$$\approx 0.5 \text{ mA}$$

$\therefore$  if  $M_{REF}$  has  $(\frac{W}{L})_{REF}$ , then

$$\frac{(\frac{W}{L})_2}{(\frac{W}{L})_{REF}} = \frac{I_{D2}}{I_{REF}} = \frac{61}{50} \approx 1.2$$

67.

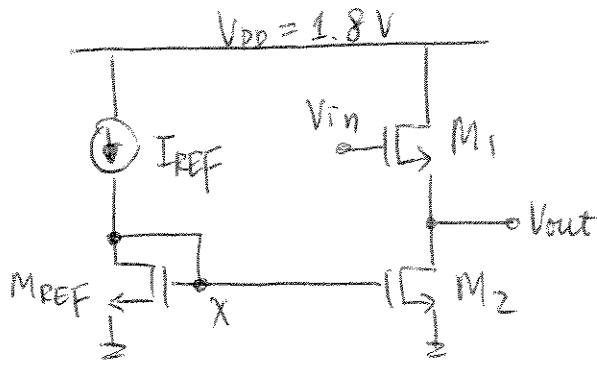

Given:

$$A_v = 0.85$$

$$R_{out} = 100 \Omega$$

$$(W/L)_2 = 10/0.18$$

$$\lambda_n = 0.1 \text{V}^{-1}, \lambda_p = 0.2 \text{V}^{-1}$$

$$R_{out} = r_{o2} \parallel \left( \frac{1}{g_{m1}} \parallel r_{o1} \right) = \frac{1}{g_{m1} + \frac{1}{r_{o2}} + \frac{1}{r_{o1}}} = 100$$

For source follower,

$$A_v = \frac{g_{m1}}{g_{m1} + \frac{1}{r_{o2}} + \frac{1}{r_{o1}}} = 0.85$$

$$\Rightarrow g_{m1} = \frac{0.85}{100} = 8.5 \cdot 10^{-3} \text{S}$$

$$R_{out} = \frac{1}{g_{m1} + \frac{2}{r_o}} = 100$$

$$\Rightarrow r_o = \frac{200}{1 - 100g_{m1}} = \frac{200}{1 - 100(8.5 \cdot 10^{-3})} \approx 1333 \Omega$$

$$\Rightarrow I_{D1} = \frac{1}{\lambda_p r_{o1}} = 7.5 \text{mA}$$


Assume  $V_x \approx 1 \text{V}$ 

$$\left( \frac{W}{L} \right)_2 = \frac{2I_{D1}}{\mu_n C_{ox} (V_x - V_{TH})^2} \approx 416$$

Set  $I_{REF} \approx 0.75 \text{ mA}$ .

$$\Rightarrow \left(\frac{W}{L}\right)_{REF} = \left(\frac{W}{L}\right)_2 \frac{I_{REF}}{I_{D2}} \approx 42.$$

68.

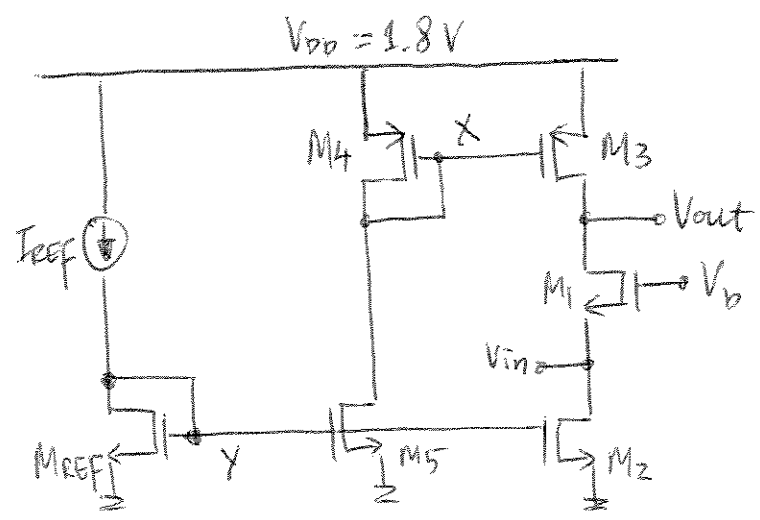

$$\left. \begin{aligned} \left(\frac{W}{L}\right)_3 &= 20/0.18 \\ \lambda_n &= 0.1 \text{ V}^{-1} \\ \lambda_p &= 0.2 \text{ V}^{-1} \end{aligned} \right\} \begin{aligned} A_v &= 20 \\ R_{in} &= 50 \Omega \end{aligned}$$

$$R_{in} = 50 \Omega = r_{o2} \parallel \frac{1}{g_{m1}} = \frac{1}{\lambda_n I_{D1} + g_{m1}} \quad \text{--- (1)}$$

$$R_{out} = r_{o3}$$

$$A_v = g_{m1} r_{o3} = \frac{g_{m1}}{\lambda_p I_{D1}} \quad \text{--- (2)}$$

Solve for  $g_{m1}$  in (2) and substitute it into (1):

$$50 = \frac{1}{\lambda_n I_{D1} + A_v \lambda_p I_{D1}}$$

$$\Rightarrow I_{D1} = \frac{1}{(\lambda_n + A_v \lambda_p)(50 \Omega)} = \frac{1}{(0.1 + 20(0.2))(50 \Omega)} \approx 4.88 \mu\text{A}$$

$$|V_{GS3}| = \sqrt{\frac{2I_{D1}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_3}} + |V_{THP}| \approx 1.44 \text{ V}$$

$$g_{m1} = A_v \lambda_p I_{D1} \Rightarrow \left(\frac{W}{L}\right)_1 = \left[ \frac{A_v \lambda_p I_{D1}}{\sqrt{2\mu_n C_{ox} I_{D1}}} \right]^2$$

$$\approx 390.$$

Since  $V_x \approx 0.4 \text{ V}$ , size up other transistors to allow them to operate in saturation.

$$\text{Suppose } I_{D4} = 1.2 \text{ mA} \Rightarrow \left(\frac{W}{L}\right)_4 = \frac{2I_{D4}}{\mu_p C_{ox} (|V_{GS3}| - |V_{THP}|)^2}$$

$$\approx 10/0.18$$

$$I_{D5} = I_{D4} \Rightarrow \left(\frac{W}{L}\right)_5 = \frac{2I_{D5}}{\mu_n C_{ox} (V_y - V_{THN})^2} \approx \frac{100}{0.18}$$

(Assume  $V_y = 0.6$ ; this is arbitrary, but must ensure  $M_5$  in saturation.)


$$\text{Set } I_{REF} = I_{D5} \Rightarrow \left(\frac{W}{L}\right)_{REF} \approx \frac{100}{0.18}$$

$$I_{D2} \approx I_{D3} \Rightarrow \left(\frac{W}{L}\right)_2 = \frac{2I_{D2}}{\mu_n C_{ox} (V_y - V_{THN})^2} \approx \frac{45}{0.18}$$


$$\text{Total power} = V_{DD} (I_{REF} + I_{D4} + I_{D3})$$

$$= 1.8 (7.3) \text{ mW} \approx 13 \text{ mW}$$

(1)

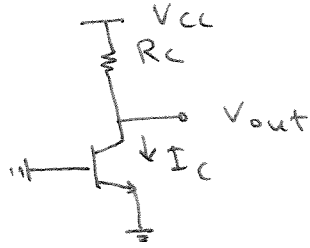


the small signal model is as follows:

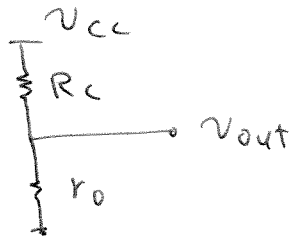


$$\frac{v_{out}}{v_{cc}} = \frac{r_o}{r_o + R_c} = \frac{\frac{V_A}{I_c}}{\frac{V_A}{I_c} + R_c} = \frac{V_A}{V_A + R_c I_c}$$

(2)

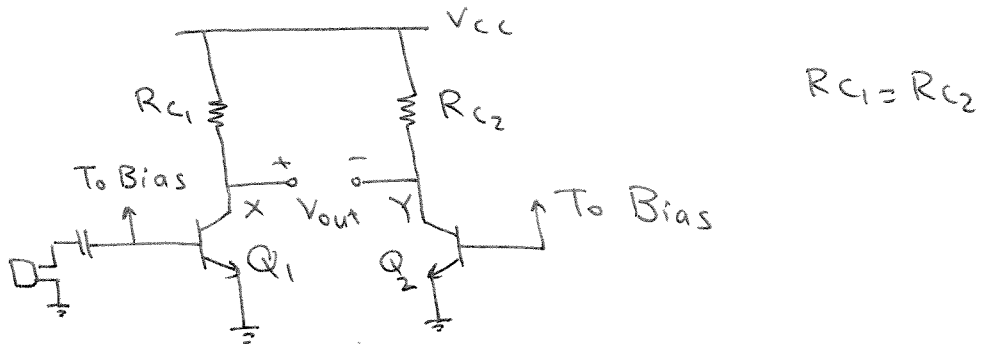

The small signal model is:

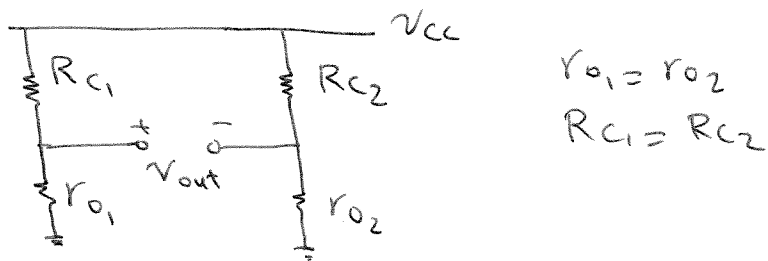


$$\frac{V_{out}}{V_{cc}} = \frac{1}{V_{cc}} \left( \frac{r_{o1}}{R_{C1} + r_{o1}} - \frac{r_{o2}}{R_{C2} + r_{o2}} \right) V_{cc} = 0$$




(3)

(a)


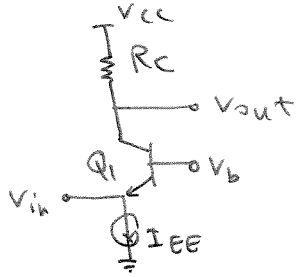


The small signal model is:

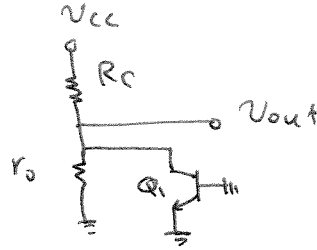




$$\frac{V_{out}}{V_{CC}} = \frac{r_o}{r_o + R_C} = \frac{V_A}{V_A + R_C I_{EE}}$$

(b)

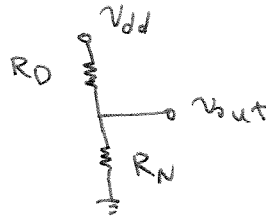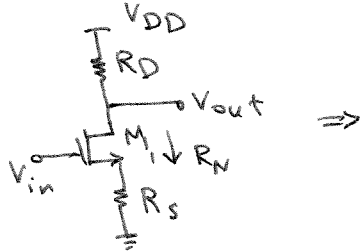

$$R_N = g_{m1} r_{o1} R_S + r_{o1} + R_S, \quad \frac{V_{out}}{V_{DD}} = \frac{R_N}{R_N + R_D}$$



(c)

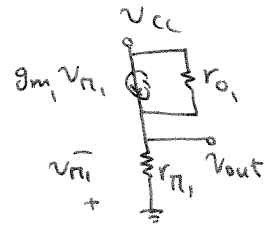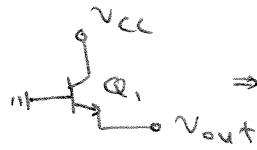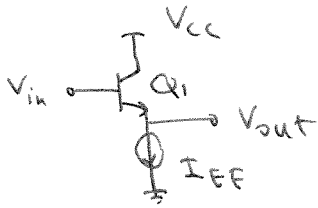

$$\frac{V_{out}}{r_{\pi_1}} + \frac{V_{out} - V_{CC}}{r_{o_1}} + g_{m_1} V_{out} = 0 \rightarrow (r_{\pi_1} + r_{o_1} + g_{m_1} r_{o_1} r_{\pi_1}) V_{out} = \frac{r_{\pi_1}}{r_{\pi_1}} V_{CC}$$

$$\Rightarrow \frac{V_{out}}{V_{CC}} = \frac{r_{\pi_1}}{\beta r_{o_1} + r_{o_1} + r_{\pi_1}}$$

(3) (d)

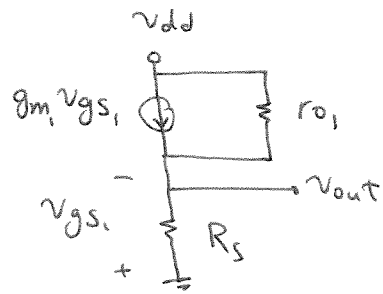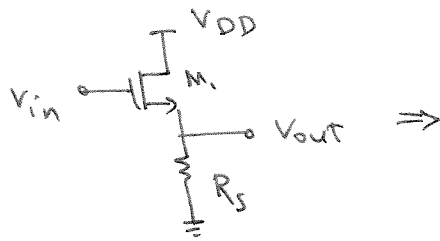


$$\frac{V_{out}}{R_S} + \frac{V_{out} - V_{DD}}{r_{o1}} + g_m V_{out} = 0$$

$$\Rightarrow (r_{o1} + R_S + g_m r_{o1} R_S) V_{out} = R_S V_{DD}$$


$$\Rightarrow \frac{V_{out}}{V_{DD}} = \frac{R_S}{g_m r_{o1} R_S + R_S + r_{o1}}$$

④

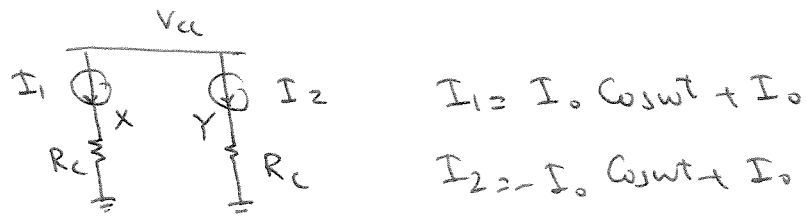

$$V_X = R_C I_1 = R_C I_0 (1 + \cos \omega t)$$

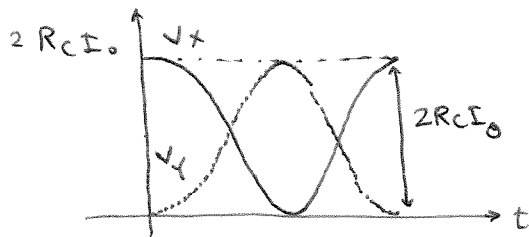
$$V_Y = R_C I_2 = R_C I_0 (1 - \cos \omega t)$$



$$V_{X,P-P} = V_{Y,P-P} = 2R_C I_0$$

$$V_{X,CM} = V_{Y,CM} = R_C I_0$$

⑤

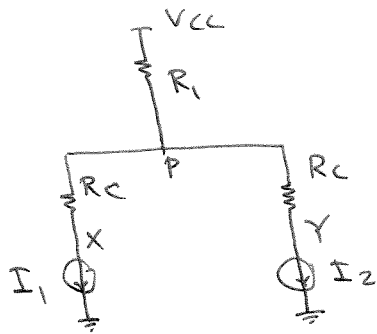

$$I_1 = I_0 \cos \omega t + I_0$$


$$I_2 = -I_0 \cos \omega t + I_0$$

$$V_P = V_{CC} - R_1 (I_1 + I_2) = V_{CC} - 2R_1 I_0$$

$$V_X = V_P - R_C I_1 = V_{CC} - 2R_1 I_0 - R_C I_0 - R_C I_0 \cos \omega t$$

$$\Rightarrow V_X = V_{CC} - (2R_1 + R_C) I_0 - R_C I_0 \cos \omega t$$

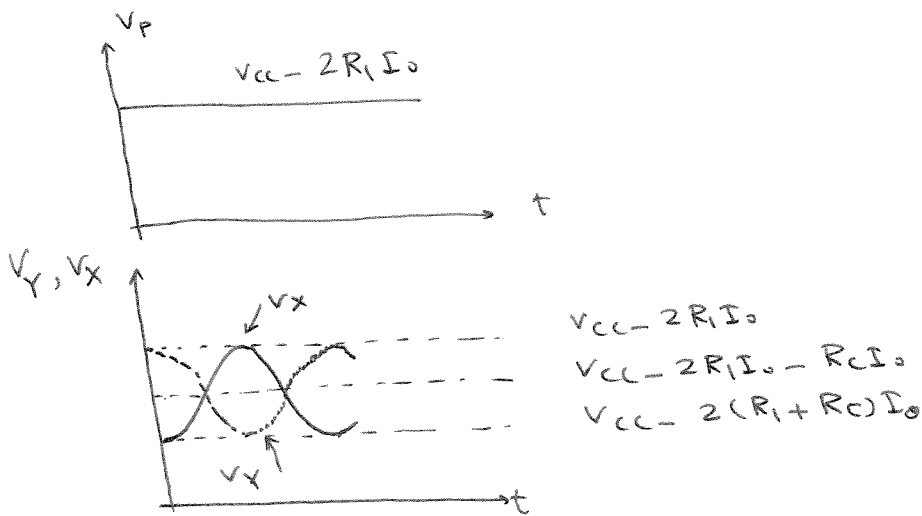
$$V_Y = V_P - R_C I_2 = V_{CC} - (2R_1 + R_C) I_0 + R_C I_0 \cos \omega t$$



$$V_{X,CM} = V_{Y,CM} = V_{CC} - (2R_1 + R_C) I_0$$

$$V_{X,P-P} = V_{Y,P-P} = 2R_C I_0$$

6

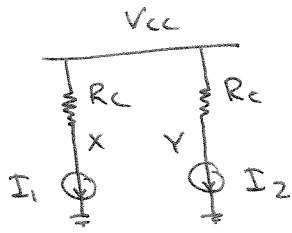


$$I_1 = I_0 \cos \omega t + I_0$$

$$I_2 = -I_0 \cos \omega t + I_0$$

$$V_X = V_{CC} - R_C I_1 = V_{CC} - R_C I_0 (1 + \cos \omega t)$$

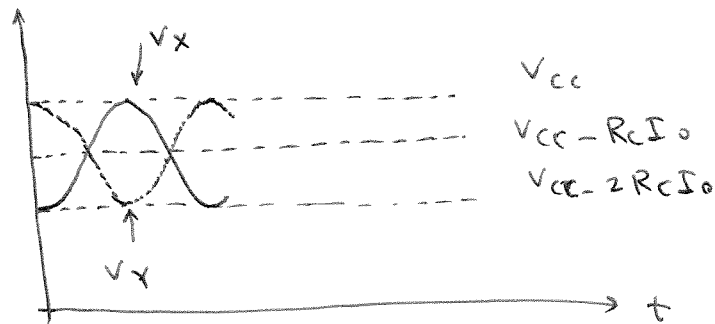
$$V_Y = V_{CC} - R_C I_2 = V_{CC} - R_C I_0 (1 - \cos \omega t)$$



$$V_{X,CM} = V_{Y,CM} = V_{CC} - R_C I_0$$

$$V_{X,P-P} = V_{Y,P-P} = 2 R_C I_0$$

⑦

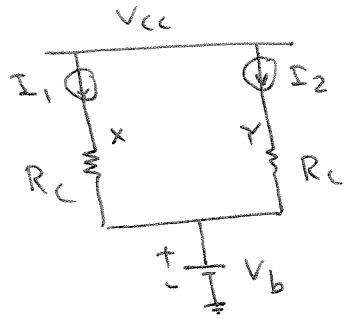


$$I_1 = I_0 \cos \omega t + I_0$$

$$I_2 = -I_0 \cos \omega t + I_0$$

$$V_X = R_C I_1 + V_b = R_C I_0 (1 + \cos \omega t) + V_b$$

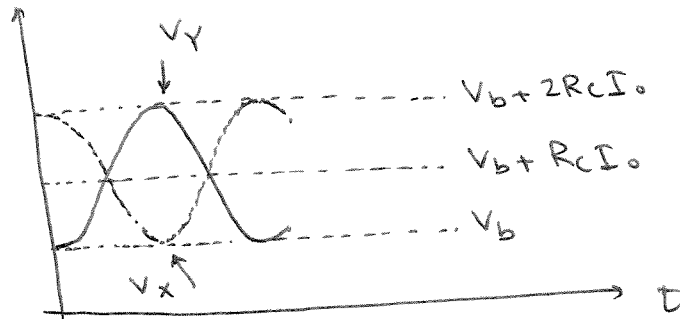
$$V_Y = R_C I_2 + V_b = R_C I_0 (1 - \cos \omega t) + V_b$$



$$V_{X,CM} = V_{Y,CM} = V_b + R_C I_0$$

$$V_{X,P-P} = V_{Y,P-P} = 2R_C I_0$$

(8)

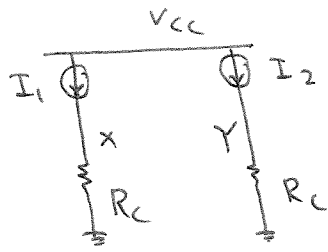


$$I_1 = I_0 \cos \omega t + I_0$$

$$I_2 = -I_0 \cos \omega t + 0.8 I_0$$

$$V_x = R_c I_1 = R_c I_0 (1 + \cos \omega t)$$
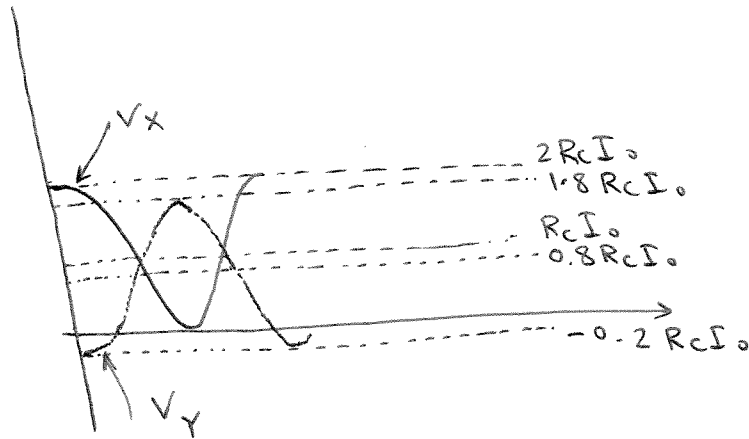
$$V_y = R_c I_2 = R_c I_0 (0.8 - \cos \omega t)$$



$$V_{x,CM} = R_c I_0 \quad V_{y,CM} = 0.8 R_c I_0$$

$$V_{x,P-P} = 2 R_c I_0 \quad V_{y,P-P} = 2 R_c I_0$$


X and Y are true differential signals.

9)

$$I_1 = I_0 \cos \omega t + I_0$$

$$I_2 = -I_0 \cos \omega t + I_0$$



(a)

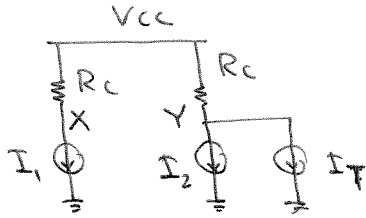


$$V_x = R_c I_1 = R_c I_0 (1 + \cos \omega t)$$

$$V_y = R_c (I_2 + I_T) =$$
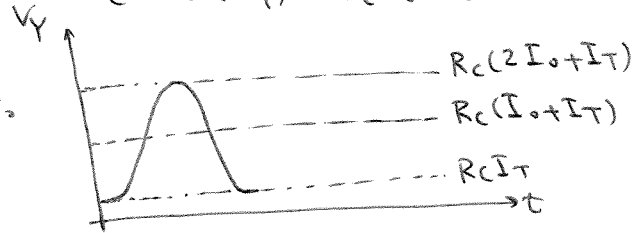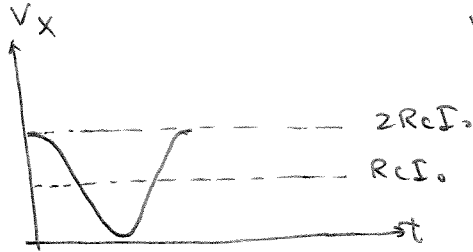
$$R_c (I_0 + I_T) - R_c I_0 \cos \omega t$$





(b)

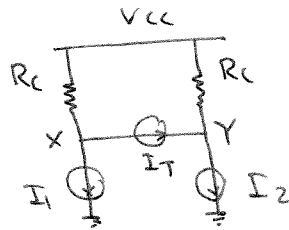


$$V_x = V_{cc} - R_c (I_1 + I_T) = V_{cc} - R_c (I_0 + I_T) - R_c I_0 \cos \omega t$$
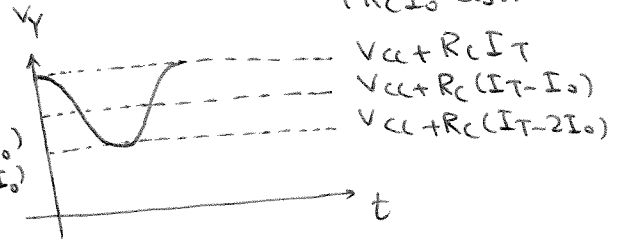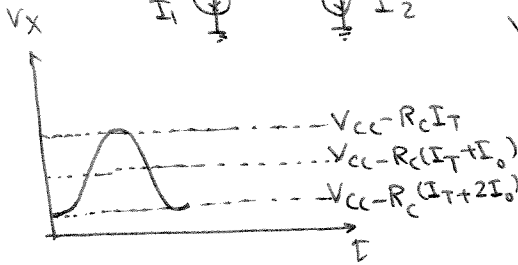
$$V_y = V_{cc} - R_c (I_2 - I_T) = V_{cc} - R_c (I_0 - I_T) + R_c I_0 \cos \omega t$$



(c)

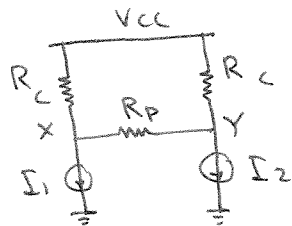


$$\begin{cases} \frac{V_x - V_{cc}}{R_c} + \frac{V_x - V_y}{R_p} + I_1 = 0 \\ \frac{V_y - V_{cc}}{R_c} + \frac{V_y - V_x}{R_p} + I_2 = 0 \end{cases} \Rightarrow$$


$$V_x = V_{cc} - R_c I_0 - \frac{R_c R_p}{2R_c + R_p} I_0 \cos \omega t$$
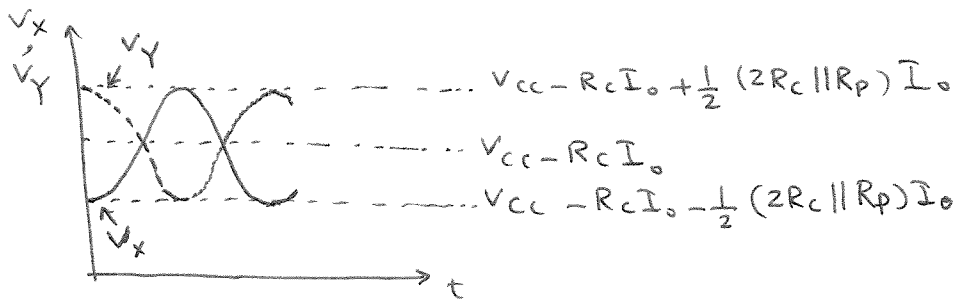
$$V_y = V_{cc} - R_c I_0 + \frac{R_c R_p}{2R_c + R_p} I_0 \cos \omega t$$







(d)

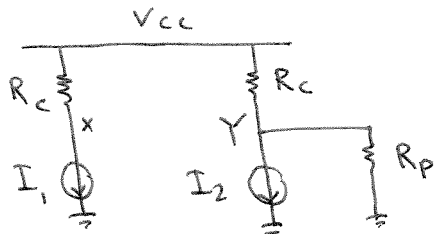

$$V_x = V_{CC} - R_c I_1 = V_{CC} - R_c I_0 (1 + \cos \omega t)$$

$$V_Y = \frac{R_p}{R_p + R_c} V_{CC} - (R_c || R_p) I_2 =$$

$$\frac{R_p}{R_p + R_c} V_{CC} - (R_c || R_p) I_0 (1 - \cos \omega t)$$

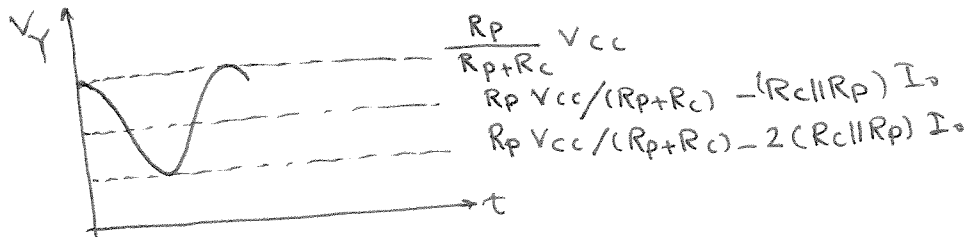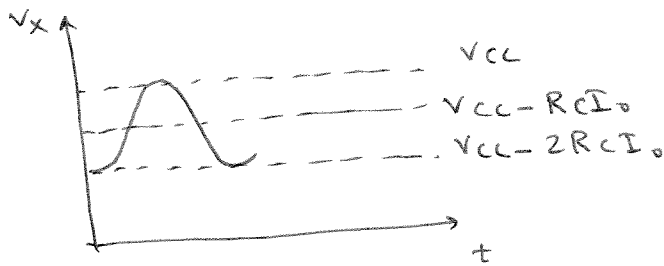


(10)

$$V_1 = V_0 \cos \omega t + V_0$$

$$V_2 = -V_0 \cos \omega t + V_0$$


(a)

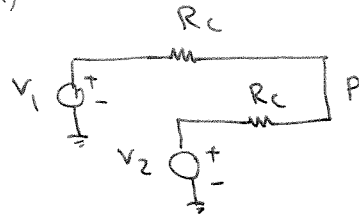

$$V_p = \frac{V_1 + V_2}{2} = V_0$$




(b)

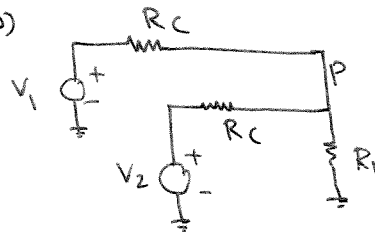


$$\frac{2V_p - V_1 - V_2}{R_c} + \frac{V_p}{R_i} = 0 \Rightarrow$$

$$\frac{2V_p - 2V_0}{R_c} + \frac{V_p}{R_i} = 0 \Rightarrow (2R_i + R_c)V_p = 2V_0 R_i$$
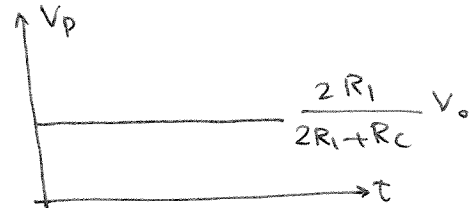
$$\rightarrow V_p = \frac{2R_i}{2R_i + R_c} V_0$$



(c)

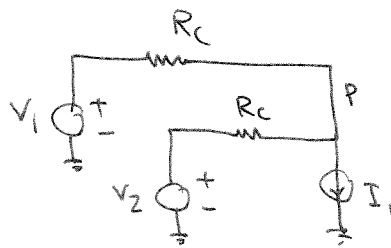


$$\frac{2V_p - V_1 - V_2}{R_c} + I_1 = 0 \Rightarrow$$

$$\frac{2V_p - 2V_0}{R_c} = -I_1 \Rightarrow$$

$$V_p = V_0 - \frac{R_c I_1}{2}$$



(11)

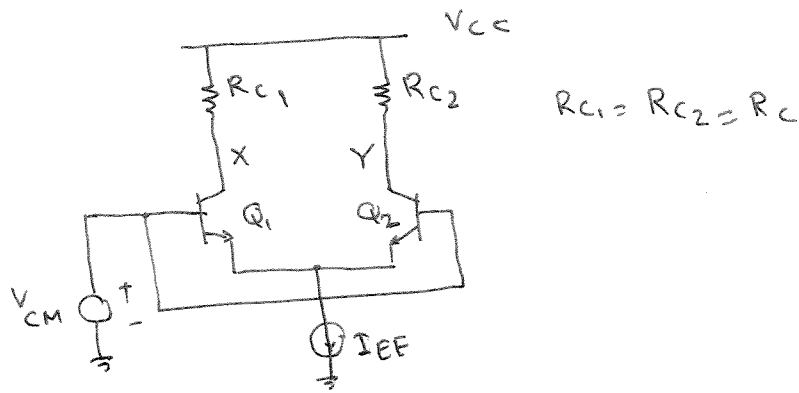


if  $V_{CC}$  changes by  $\Delta V$  then:

$$\Delta V_X = \Delta V, \quad \Delta V_Y = \Delta V \Rightarrow$$

$$\Delta (V_X - V_Y) = 0$$

Since both  $V_X$  and  $V_Y$  response to the supply changes similarly, the circuit rejects supply noise.

12

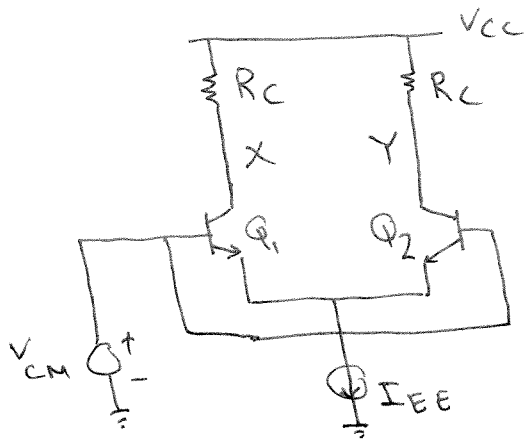


$$\Delta V_X = - \frac{R_C \Delta I_{EE}}{2} = - \frac{R_C \Delta I}{2}$$

$$\Delta V_Y = - \frac{R_C \Delta I_{EE}}{2} = - \frac{R_C \Delta I}{2}$$

$$\Rightarrow \Delta(V_X - V_Y) = 0$$

(13)

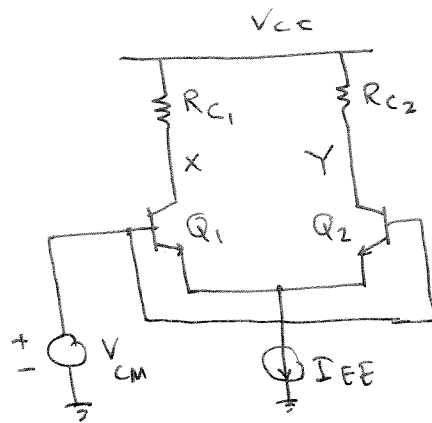


$$R_{C1} = R_{C2} + \Delta R$$

$$\Delta V_X = - \frac{R_{C1} \Delta I}{2} = - \frac{(R_{C2} + \Delta R) \Delta I}{2}$$

$$\Delta V_Y = - \frac{R_{C2} \Delta I}{2} \Rightarrow$$

$$\Delta(V_X - V_Y) = - \frac{\Delta R \Delta I}{2}$$


14

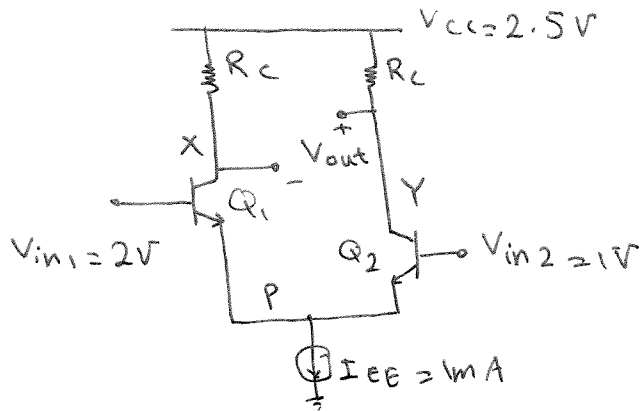

$$V_X \geq V_{in1} \Rightarrow V_X \geq 2 \Rightarrow V_{CC} - R_C I_{EE} \geq 2$$

$$\Rightarrow 2.5 - R_C^{(k\Omega)} \geq 2 \Rightarrow R_C \leq 0.5 \text{ k}\Omega$$


15

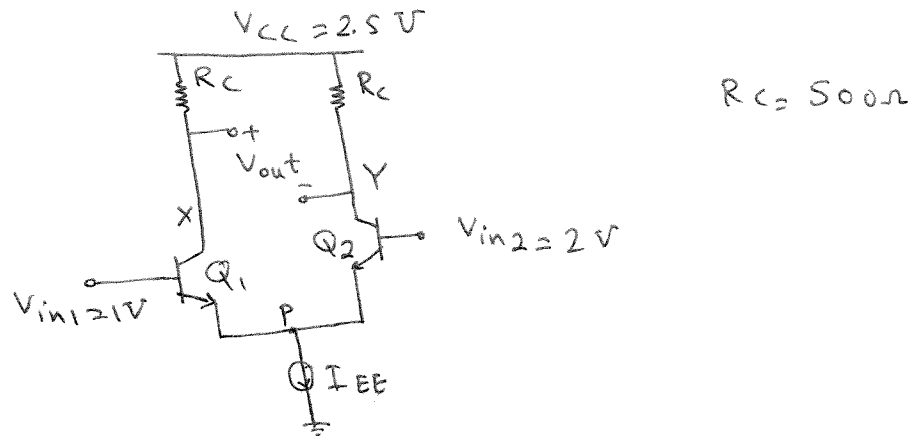

$$V_Y \geq V_{in2} \Rightarrow V_{CC} - R_C I_{EE} \geq 2 \Rightarrow$$

$$2.5 - 500 I_{EE} \geq 2 \Rightarrow I_{EE} \leq 1\text{ mA}$$

16

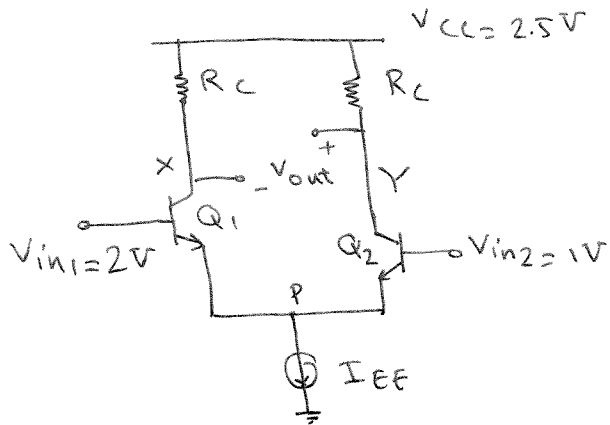

$$I_{EE} = 1\text{mA}$$

$$R_C = 800\ \Omega$$



$$V_X = V_{CC} - R_C \bar{I}_{EE} = 2.5 - 0.8 = 1.7\text{V}$$

$\Rightarrow V_X < V_{in1} \Rightarrow Q_1$  is in saturation region.





(17)



(a)

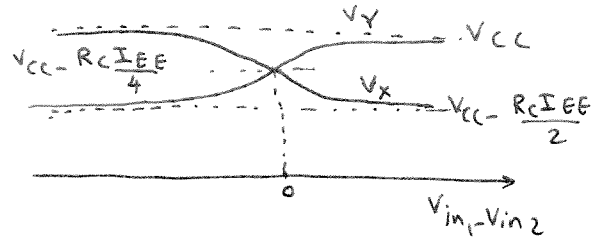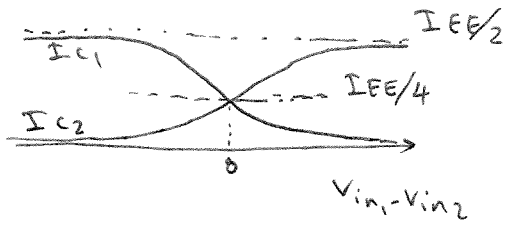


(b)

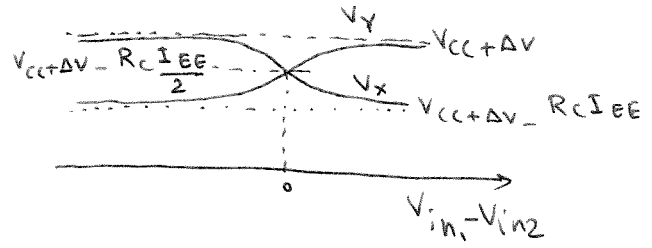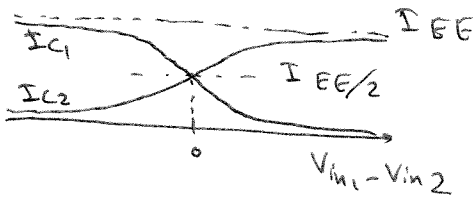

(c)

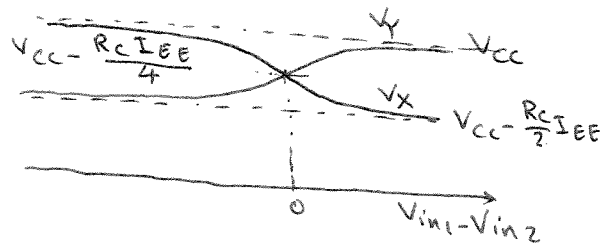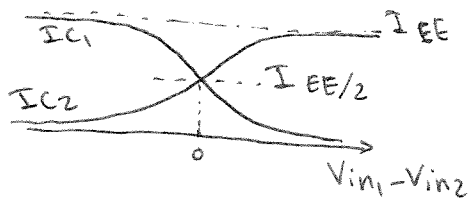

18

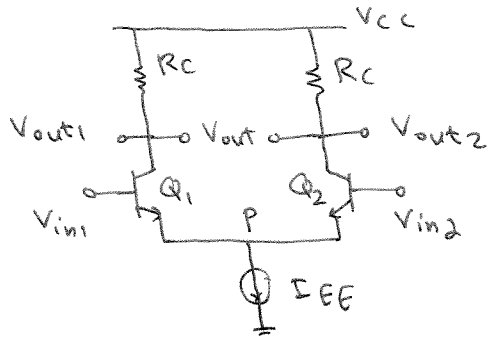

$$\frac{I_{C1}}{I_{C2}} = 5$$

$$V_{in1} - V_{in2} = V_T \ln \frac{I_{C1}}{I_{C2}} = 0.026 \ln 5 = 41.845 \text{ mV}$$

at  $27^\circ$ ,  $V_T = 26 \text{ mV} \Rightarrow$  at  $100^\circ$ ,

$$V_T = \frac{(273 + 100)}{273 + 27} 26^{\text{mV}} = 32.33 \text{ mV}$$

$$\Rightarrow \frac{41.845 \text{ mV}}{\text{mV}} = \frac{32.33 \text{ mV}}{\text{mV}} \ln \frac{I_{C1}}{I_{C2}} \Rightarrow \frac{I_{C1}}{I_{C2}} = 3.65$$

(19)

$$I_{C2} = I_{C1} = \frac{I_{EE}}{2}$$

if  $I_{C2}$  changes by 10% then


$$1.1 \times I_{C2 \text{ bias}} = \frac{I_{EE}}{1 + \exp \frac{V_{in1} - V_{in2}}{V_T}} \Rightarrow$$

$$1.1 \times \frac{I_{EE}}{2} = \frac{I_{EE}}{1 + \exp \frac{V_{in1} - V_{in2}}{V_T}} \Rightarrow$$

$$V_{in1} - V_{in2} = V_T \ln \frac{0.9}{1.1} = -0.2 V_T = -5.217 \text{ mV}$$

So the input differential voltage should change by no more than 5.2 mV.

(20)

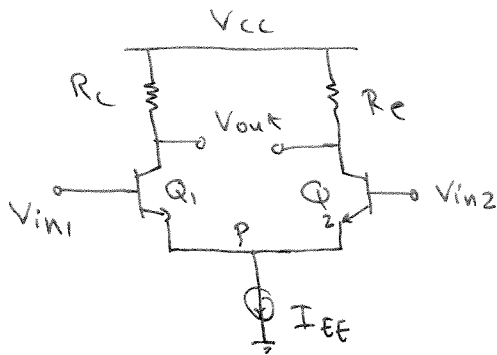

$$I_{C2} = \frac{I_{EE}}{1 + \exp\left(\frac{V_{in1} - V_{in2}}{V_T}\right)}$$

$$I_{C2 \text{ bias}} = \frac{I_{EE}}{2}$$

if the transconductance of  $Q_2$  drops by a factor of 2, then  $I_{C2} = \frac{I_{EE}}{4}$

$$\Rightarrow \frac{I_{EE}}{4} = \frac{I_{EE}}{1 + \exp\left(\frac{V_{in1} - V_{in2}}{V_T}\right)} \Rightarrow$$


$$V_{in1} - V_{in2} = V_T \ln 3 = 1.0986 V_T = 28.564 \text{ mV}$$

$$(21) \quad v_{in1} - v_{in2} = \Delta v_{in}$$

$$I_{C1} - I_{C2} = \frac{I_{EE} \exp \frac{\Delta v_{in}}{V_T}}{1 + \exp \frac{\Delta v_{in}}{V_T}} - \frac{I_{EE}}{1 + \exp \frac{\Delta v_{in}}{V_T}}$$

$$\Rightarrow \frac{\partial (I_{C1} - I_{C2})}{\partial (\Delta v_{in})} = I_{EE} \left[ \frac{\frac{1}{V_T} \exp \left( \frac{\Delta v_{in}}{V_T} \right) (1 + \exp \frac{\Delta v_{in}}{V_T}) - \frac{(\exp \frac{\Delta v_{in}}{V_T})^2}{V_T}}{(1 + \exp \frac{\Delta v_{in}}{V_T})^2} + \frac{\frac{1}{V_T} \exp \frac{\Delta v_{in}}{V_T}}{(1 + \exp \frac{\Delta v_{in}}{V_T})^2} \right]$$
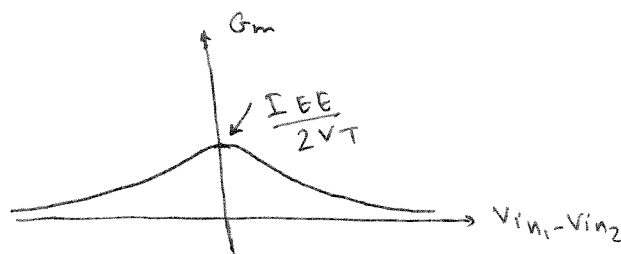
$$= \frac{2 I_{EE}}{V_T} \frac{\exp \left( \frac{v_{in1} - v_{in2}}{V_T} \right)}{\left( 1 + \exp \left( \frac{v_{in1} - v_{in2}}{V_T} \right) \right)^2}$$



$$\begin{cases} \max G_m = \frac{I_{EE}}{2V_T} \\ \text{At } v_{in1} - v_{in2} = 0 \end{cases}$$

$$\text{if } G_m = \frac{1}{2} G_{m_{\max}} = \frac{I_{EE}}{4V_T} \Rightarrow$$

$$\frac{\exp \left( \frac{v_{in1} - v_{in2}}{V_T} \right)}{\left( 1 + \exp \left( \frac{v_{in1} - v_{in2}}{V_T} \right) \right)^2} = \frac{1}{8} \Rightarrow v_{in1} - v_{in2} = \pm 1.763 V_T = \pm 45.838 \text{ mV}$$

Q2)

$$V_{out1} - V_{out2} = -R_C I_{EE} \tanh \frac{V_{in1} - V_{in2}}{2V_T}$$

$$A_V = \frac{\partial (V_{out1} - V_{out2})}{\partial (V_{in1} - V_{in2})} = -\frac{2R_C I_{EE}}{V_T} \frac{\exp\left(\frac{V_{in1} - V_{in2}}{V_T}\right)}{\left[1 + \exp\left(\frac{V_{in1} - V_{in2}}{V_T}\right)\right]^2}$$


if  $V_{in1} - V_{in2} = 30 \text{ mV} \Rightarrow$

$$A_V = -14.02 R_C I_{EE}$$

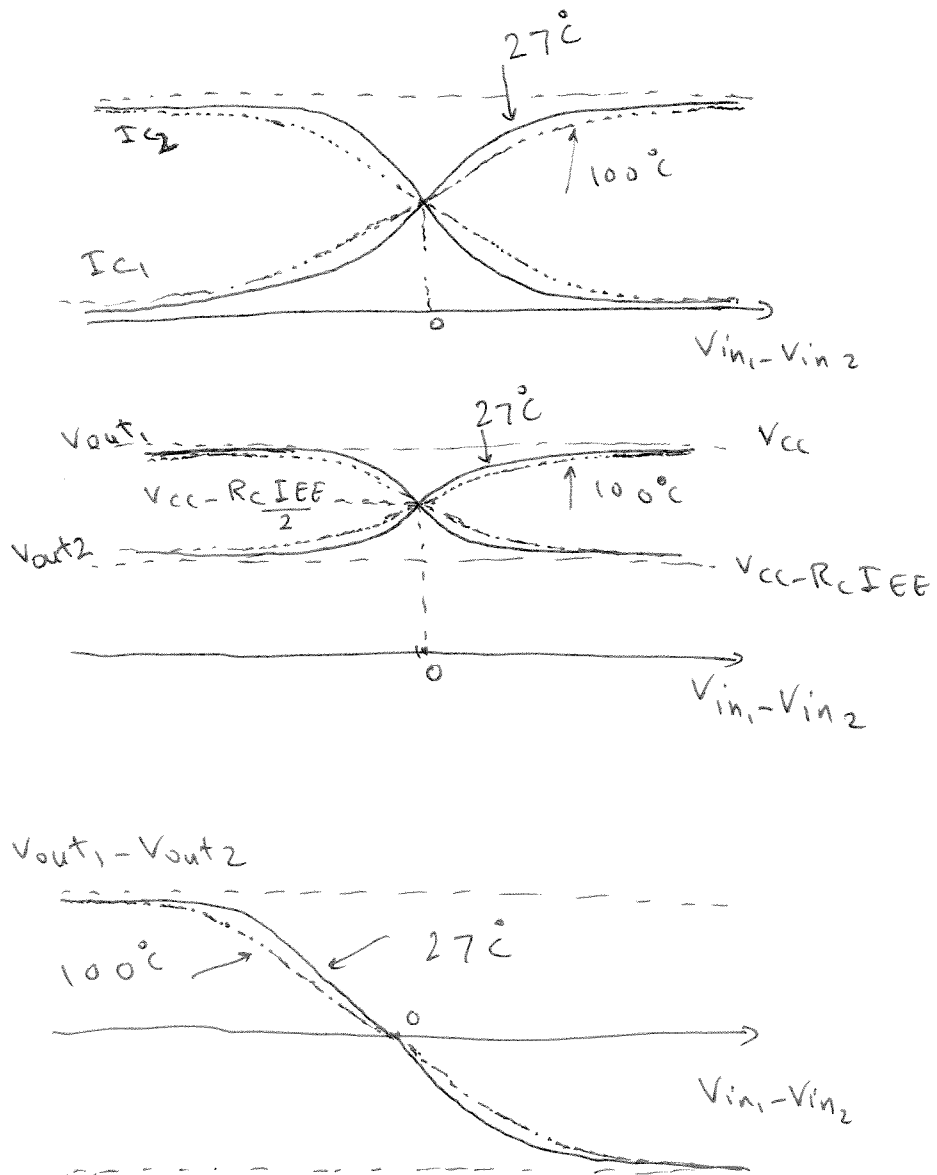
(23)

if the ambient temperature goes from  $27^{\circ}\text{C}$  to  $100^{\circ}\text{C}$ ,  $V_T$  will change from  $26\text{mV}$  to  $32.33\text{mV}$ .

Therefore the curves stretch out as shown below to the sides:



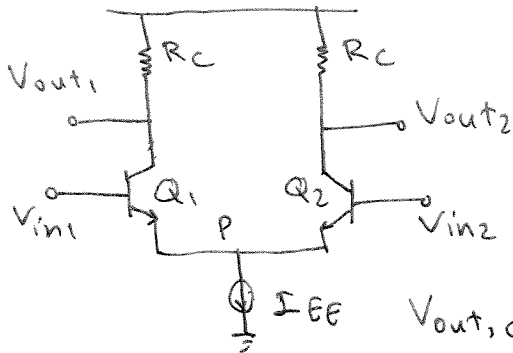(24)  $R_C = 500 \Omega$ ,  $I_{EE} = 1 \text{ mA}$ ,  $V_{CC} = 2.5 \text{ V}$   
 $V_{in1} = V_0 \sin \omega t + V_{CM}$   $V_{in2} = -V_0 \sin \omega t + V_{CM}$ ,  $V_{CM} = 1 \text{ V}$   
 $V_{CC}$




$$A_v = -g_m R_C = -\frac{I_{EE}}{2V_T} R_C =$$

$$= -\frac{10^{-3} \times 500}{2 \times 0.026} = -9.615$$

$$V_{out, CM} = V_{CC} - R_C \frac{I_{EE}}{2} = 2.5 - 0.5 \times 0.5 \Rightarrow$$

$$V_{out, CM} = 2.25$$

(a)  $|V_{out}| = |A_v V_{in}| = 9.615 \times 2 \text{ m} = 19.23 \text{ mV}$

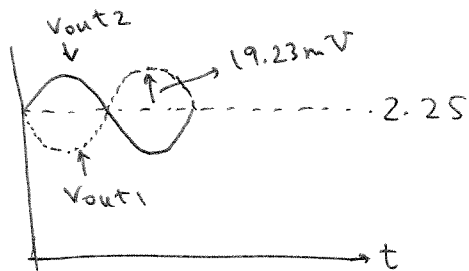


(b)  $I_{C1} = 0.95 I_{EE}$ ,  $I_{C2} = 0.05 I_{EE}$ ,  $\frac{I_{C1}}{I_{C2}} = 19$

$$V_{in1} - V_{in2} = V_T \ln \frac{I_{C1}}{I_{C2}} = 76.555 \text{ mV}$$


$$\frac{V_{in1} - V_{in2}}{2} = \frac{50 \text{ mV}}{2} \sin \omega t_1 \Rightarrow 38.278 = \frac{50 \text{ mV}}{2} \sin \omega t_1 \Rightarrow$$

$$t_1 = \frac{0.872}{\omega}$$

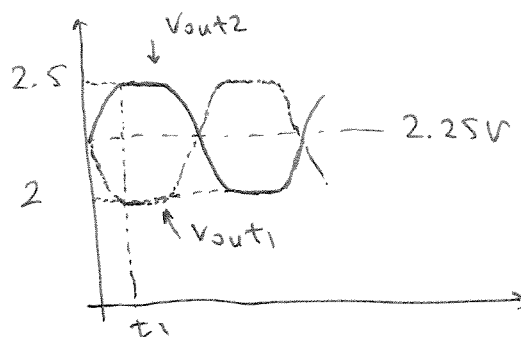



(25)

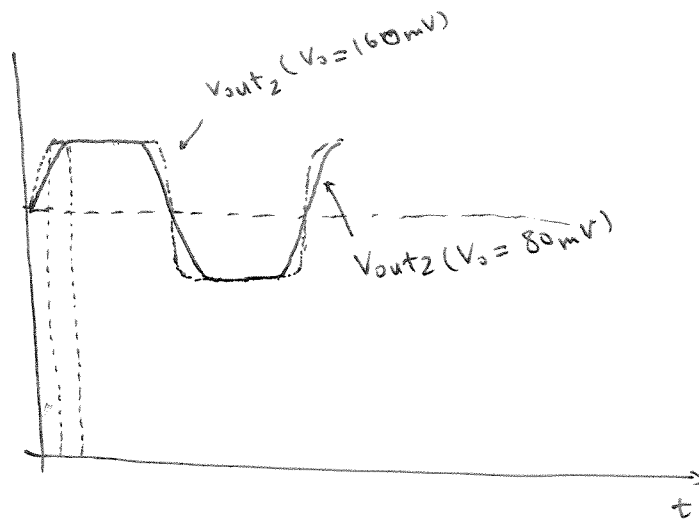

The time at which one transistor takes 95% of the tail current source is achievable through:

$$\frac{I_{C1}}{I_{C2}} = 19 \Rightarrow V_{in1} - V_{in2} = V_T \ln \frac{I_{C1}}{I_{C2}} = 76.555 \text{ mV}$$

$$\frac{V_{in1} - V_{in2}}{2} = V_0 \sin \omega t_1 \Rightarrow t_1 = \frac{\text{Arc Sin } \frac{38.278}{V_0}}{\omega}$$

evidently as  $V_0$  increases,  $t_1$  decreases and the output waveform becomes sharper.

$$t_1 (V_0 = 80 \text{ mV}) = \frac{0.499}{\omega}$$

$$t_1 (V_0 = 160 \text{ mV}) = \frac{0.242}{\omega}$$


$$(26) \quad \omega = 2\pi \times (100 \text{ MHz})$$

$$\text{Slope} \approx \frac{V_{CC} - V_{CM}}{t_1} = \frac{0.25 \text{ V}}{\text{Arc Sin}\left(\frac{38.278}{V_o \text{ (mV)}}\right)}$$


$$\Rightarrow \text{if } V_o = 80 \text{ mV} \Rightarrow \text{slope} = 3.148 \times 10^8 \text{ V/s}$$

$$\text{if } V_o = 160 \text{ mV} \Rightarrow \text{slope} = 6.491 \times 10^8 \text{ V/s}$$

(27)

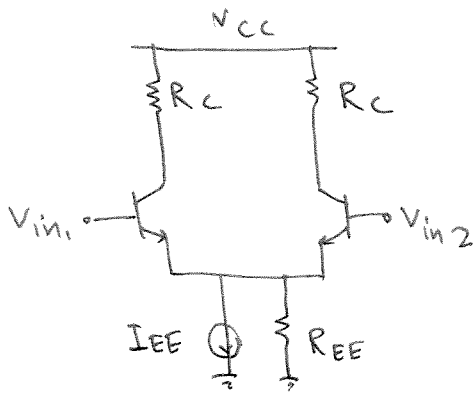

The small signal model is,

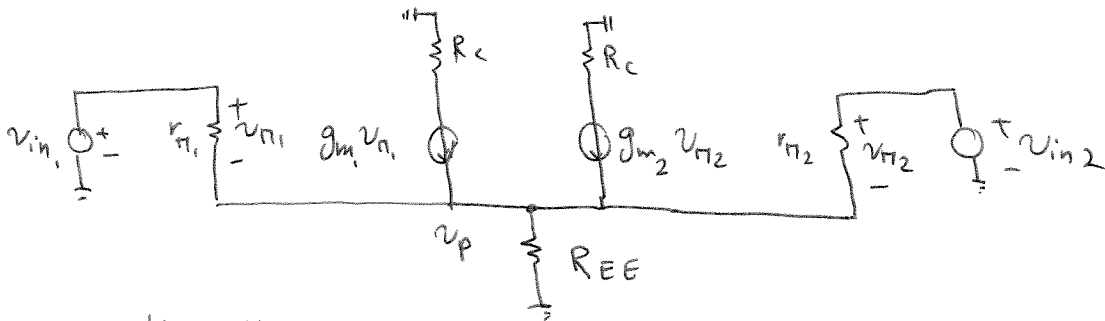


writing the node equation at P we have:

$$\frac{v_P}{R_{EE}} + \frac{v_P - v_{in1}}{r_{\pi 1}} + g_{m1}(v_P - v_{in1}) + \frac{v_P - v_{in2}}{r_{\pi 2}} + g_{m2}(v_P - v_{in2}) = 0$$


Since  $v_{in1} = -v_{in2}$  and  $\begin{cases} r_{\pi 1} = r_{\pi 2} \\ g_{m1} = g_{m2} \end{cases}$ , the above equation simplifies to:
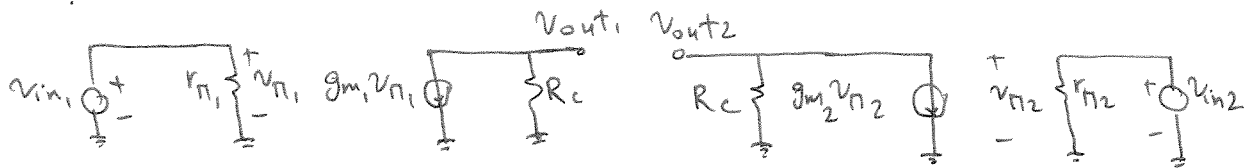
$$\frac{v_P}{R_{EE}} + \frac{2v_P}{r_{\pi 1}} + 2g_{m1}v_P = 0 \Rightarrow v_P = 0 \Rightarrow \text{the small signal model is:}$$



$$A_v = \frac{v_{out1} - v_{out2}}{v_{in1} - v_{in2}} = \frac{-g_{m1}v_{in1}R_C + g_{m2}v_{in2}R_C}{v_{in1} - v_{in2}} = -g_{m1}R_C$$

(28)

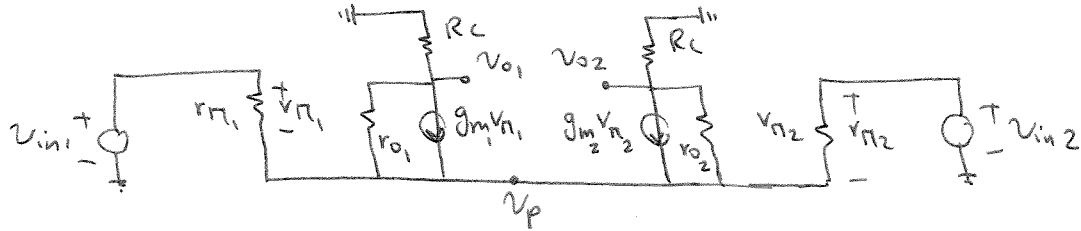

$$V_{in1} = -V_{in2} \rightarrow V_{in1} + V_{in2} = 0$$
$$g_{m1} = g_{m2}, r_{\pi1} = r_{\pi2}, r_{o1} = r_{o2}$$

Writing the node equation at  $V_p$ :

$$\frac{V_p - V_{in1}}{r_{\pi1}} + \frac{V_p - V_{o1}}{r_{o1}} + g_{m1}(V_p - V_{in1}) + g_{m2}(V_p - V_{in2}) +$$
$$\frac{V_p - V_{in2}}{r_{\pi2}} + \frac{V_p - V_{o2}}{r_{o2}} = 0 \Rightarrow 2g_{m1} V_p + \frac{2V_p - V_{o1} - V_{o2}}{r_{o1}} + \frac{2V_p \times 2}{r_{\pi1}} = 0 \quad (1)$$

Now the node equations at nodes  $V_{o1}$  and  $V_{o2}$  leads to:


$$\begin{cases} \frac{V_{o1}}{R_c} + \frac{V_{o1} - V_p}{r_{o1}} + g_{m1}(V_{in1} - V_p) = 0 & (2) \\ \frac{V_{o2}}{R_c} + \frac{V_{o2} - V_p}{r_{o2}} + g_{m2}(V_{in2} - V_p) = 0 & (3) \end{cases} \Rightarrow (2) + (3) =$$

$$(V_{o1} + V_{o2}) \left( \frac{1}{R_c} + \frac{1}{r_{o1}} \right) = \frac{2V_p}{r_{o1}} + 2g_{m1} V_p \quad (4)$$

placing 4 in (1)  $\Rightarrow$

$$2g_{m1} V_p + \frac{1}{r_{o1}} \left( 2V_p - \frac{1}{\frac{1}{R_c} + \frac{1}{r_{o1}}} \left( \frac{2V_p}{r_{o1}} + 2g_{m1} V_p \right) \right) + \frac{2V_p \times 2}{r_{\pi1}} = 0$$
$$\Rightarrow \underline{V_p = 0}$$


(29)

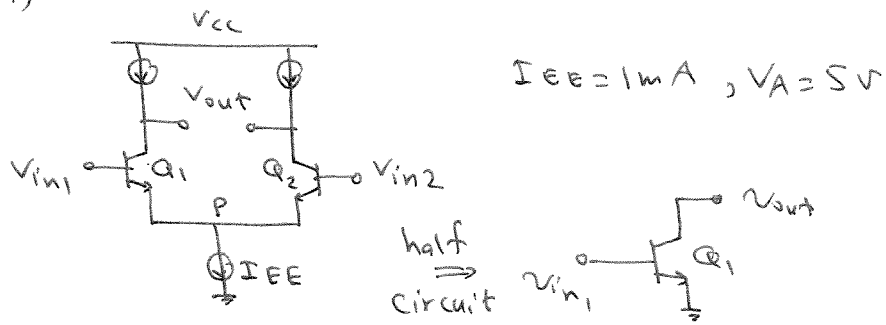


$$A_v = -g_{m1} \cdot r_{o1} = -\frac{I_{EE}}{2V_T} \cdot \frac{V_A}{\frac{I_{EE}}{2}} = -\frac{V_A}{V_T} = \frac{-5}{0.026}$$

$$\rightarrow A_v = -192.31$$

(30)

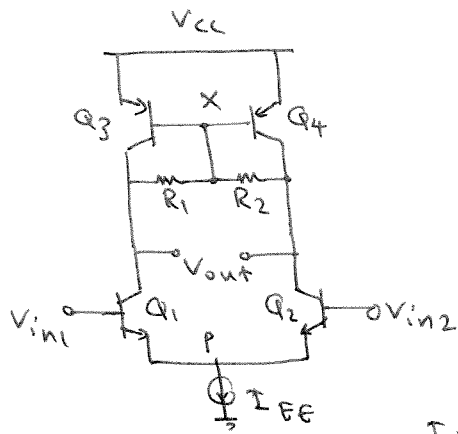

half  
=>  
circuit

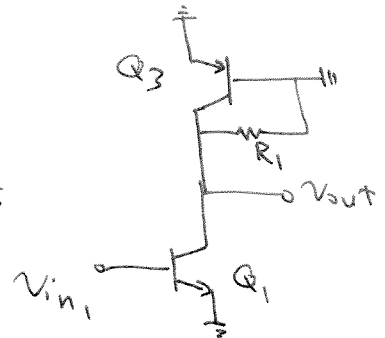

$$I_{EE} = 2\text{mA}, V_{A,n} = 5\text{V}, V_{A,p} = 4\text{V}$$

$$A_v = -g_{m1} (r_{o1} \parallel r_{o3} \parallel R_1)$$

$$\Rightarrow 50 = \frac{I_{EE}}{2V_T} \left( \frac{V_{A,n}}{\frac{I_{EE}}{2}} \parallel \frac{V_{A,p}}{\frac{I_{EE}}{2}} \parallel R_1 \right) \Rightarrow$$

$$50 = \frac{2}{2 \times 26} \left( \frac{5}{10^{-3}} \parallel \frac{4}{10^{-3}} \parallel R_1 \right) \rightarrow$$

$$R_1 = 3132.53 \Omega$$

(31)

The half circuit is:

$$A_v = -g_{m1} (r_{o1} \parallel r_{o3} \parallel R_1)$$


$\Rightarrow$

$$S_0 = \frac{I_{EE}}{2 \times 0.026} \left( \frac{5}{\frac{I_{EE}}{2}} \parallel \frac{4}{\frac{I_{EE}}{2}} \parallel 5K \right) \Rightarrow$$


$$S_0 = \frac{1}{0.052} (10 \parallel 8 \parallel 5I_{EE}) \Rightarrow$$

$\downarrow$        $\downarrow$   
10K      5mA


$$I_{EE} = 1.253 \text{ mA}$$

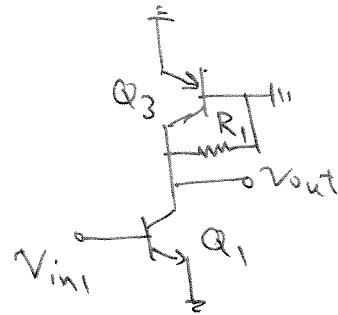


32

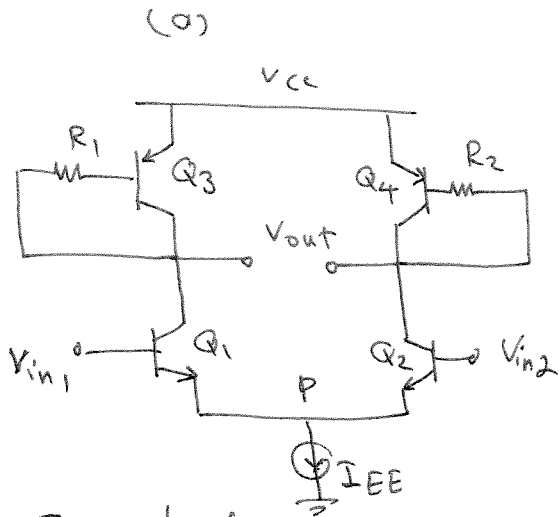

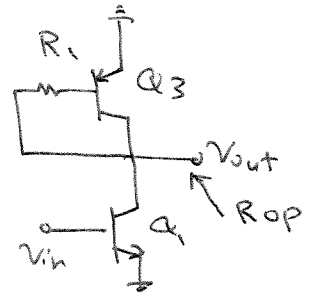From half circuit concept we have:  $A_v = -g_{m1}(r_{o1} \parallel R_{op})$



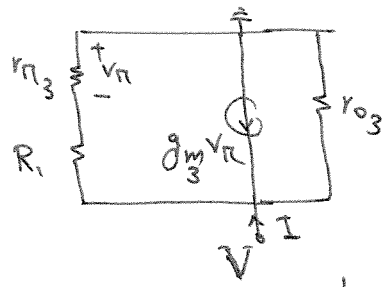To calculate  $R_{op}$ , from small signal model we have:



$$I = \frac{V}{r_{o3}} - g_{m3}V_{\pi} + \frac{V}{R_1 + r_{\pi 3}} = V \left[ \frac{1}{r_{o3}} + \frac{1}{R_1 + r_{\pi 3}} \right] + g_{m3} \frac{r_{\pi 3}}{R_1 + r_{\pi 3}} V$$


$$\rightarrow R_{op} = \frac{V}{I} = r_{o3} \parallel (R_1 + r_{\pi 3}) \parallel \left( \left( 1 + \frac{R_1}{r_{\pi 3}} \right) \frac{1}{g_{m3}} \right)$$

$$\rightarrow A_v = -g_{m1} \left[ r_{o1} \parallel r_{o3} \parallel (R_1 + r_{\pi 3}) \parallel \left( \left( 1 + \frac{R_1}{r_{\pi 3}} \right) \frac{1}{g_{m3}} \right) \right]$$




32


b)

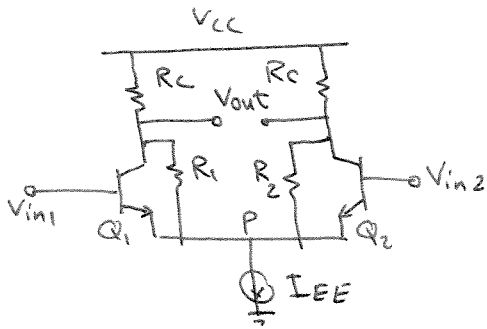


From half circuit concept:

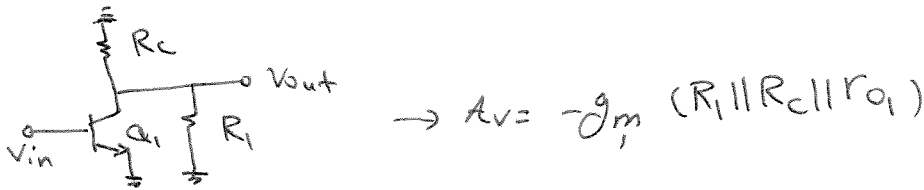

(c)

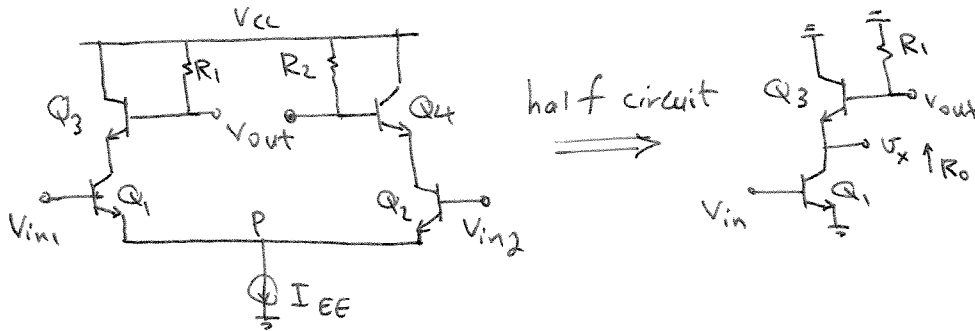

To calculate  $R_o$  we have:

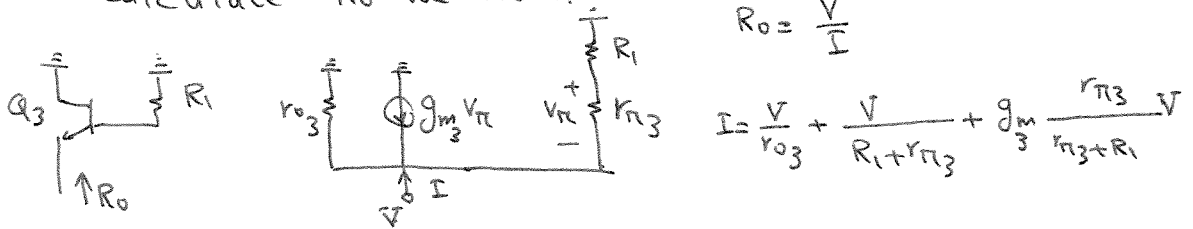


$$\Rightarrow R_o = r_{o3} \parallel (R_1 + r_{\pi 3}) \parallel \left(1 + \frac{R_1}{r_{\pi 3}}\right) \frac{1}{g_{m3}}$$


$$A_v = \frac{v_{out}}{v_{in}} = \frac{v_x}{v_{in}} \frac{v_{out}}{v_x} = -g_{m1} (r_{o1} \parallel R_o) \frac{R_1}{R_1 + r_{\pi 3}}$$

32

(d)

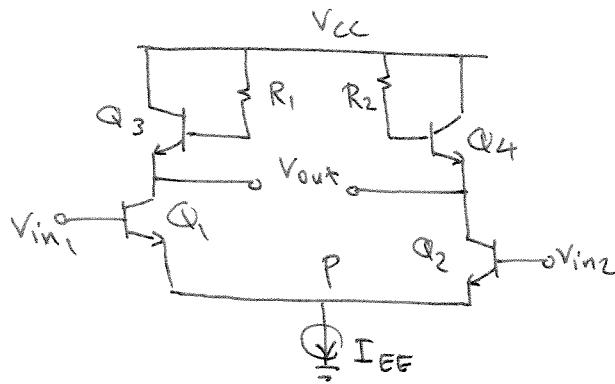

From half circuit concept :

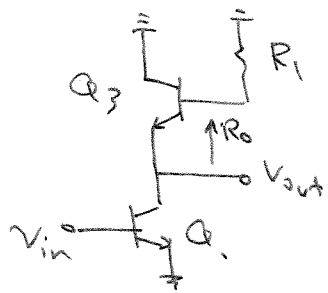


we already proved in part (c) that

$$R_o = r_{o3} \parallel (R_1 + r_{\pi 3}) \parallel \left(1 + \frac{R_1}{r_{\pi 3}}\right) \frac{1}{g_{m3}}$$


$$\rightarrow A_v = \frac{v_{out}}{v_{in}} = -g_{m1} (r_{o1} \parallel R_o)$$

(33)

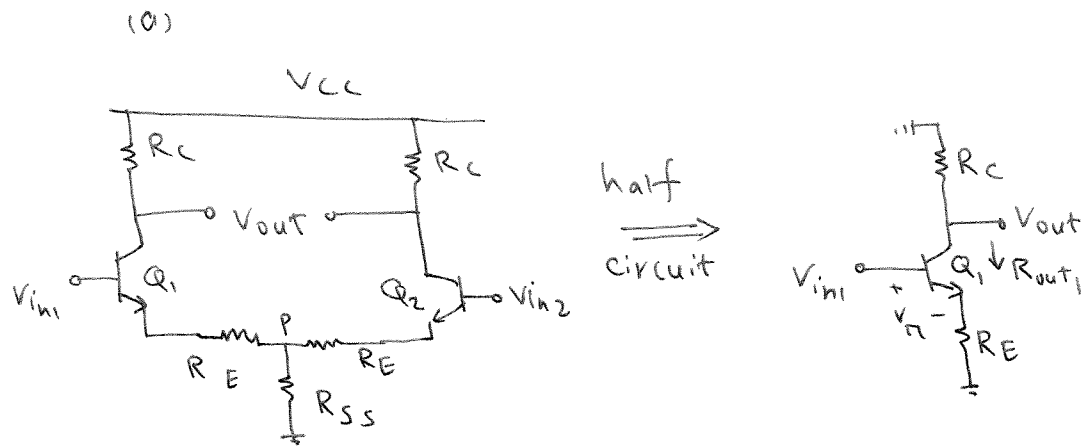

$$R_{out} = R_C \parallel R_{out1} = R_C \parallel (g_{m1} r_{o1} (R_E \parallel r_{\pi1}) + r_{o1} + (R_E \parallel r_{\pi1}))$$

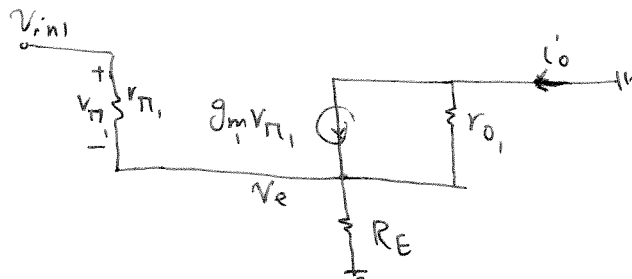To calculate  $G_m$ , the small signal model is:



writing node equation at node  $v_e$ :

$$\frac{v_e}{R_E \parallel r_{o1}} = (g_{m1} + \frac{1}{r_{\pi1}}) v_{\pi1} = \underbrace{(g_{m1} + \frac{1}{r_{\pi1}})}_{g_{m1}} (v_{in1} - v_e)$$


$$\Rightarrow v_e = \frac{g_{m1}}{g_{m1} + \frac{1}{R_E \parallel r_{o1}}} v_{in1} \Rightarrow i_o = \frac{v_e}{r_{o1}} - g_{m1} v_{\pi1}$$

$$= \frac{v_e}{r_{o1}} + g_{m1} (v_e - v_{in1}) \Rightarrow G_m = \frac{i_o}{v_{in1}} = + \frac{g_{m1} r_{o1}}{g_{m1} r_{o1} R_E + r_{o1} + R_E}$$

$$\Rightarrow A_v = -G_m R_{out}$$

(33)

(b)

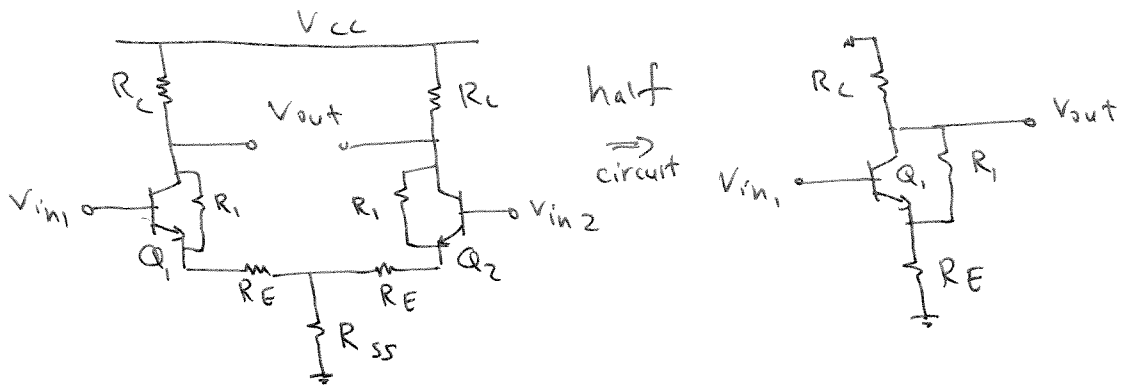


$$R_{out} = R_C \parallel \left( g_{m_1} (r_{o_1} \parallel R_1) (R_E \parallel r_{\pi_1}) + (r_{o_1} \parallel R_1) + (R_E \parallel r_{\pi_1}) \right)$$

Similar to the approach in part (a)


$$G_m = + \frac{g_{m_1} (r_{o_1} \parallel R_1)}{g_{m_1} (r_{o_1} \parallel R_1) R_E + (r_{o_1} \parallel R_1) + R_E}$$

$$\Rightarrow A_v = -G_m R_{out}$$

34

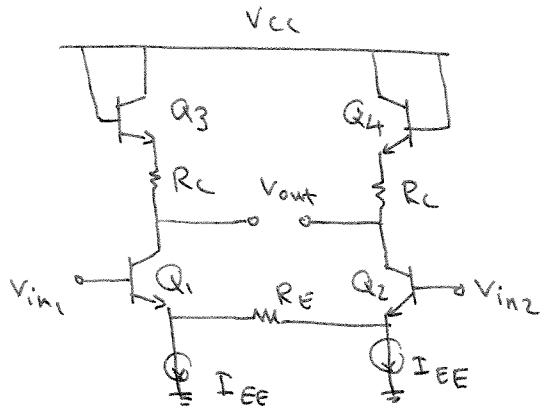

The half circuit is shown as:

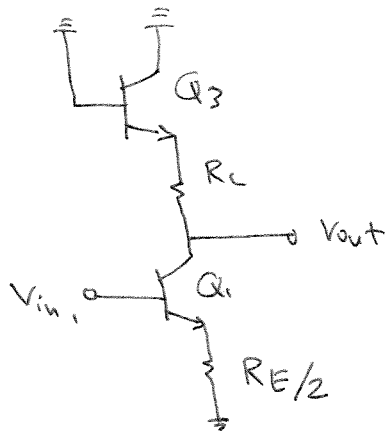


$$a) \quad A_v = \frac{v_{out}}{v_{in1}} = - \frac{R_C + 1/g_{m3}}{R_E/2 + 1/g_{m1}}$$

$$b) \quad \text{if } \frac{R_C}{R_E/2} = A, \text{ then if } \frac{1/g_{m3}}{1/g_{m1}} = A$$

we conclude  $A_v = -A$ . So the circuit is very linear.

35

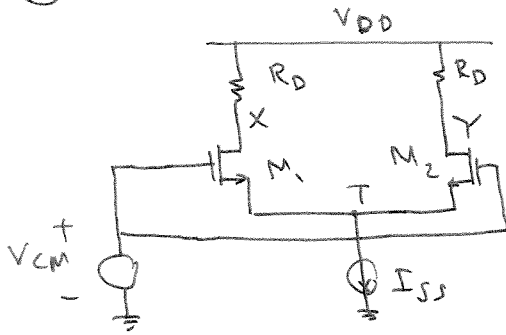

$$V_T = V_{CM} - V_{GS1} = V_{CM} - V_{TH} - \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

(a)  $V_T = V_{CM} - V_{TH} - \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{2W}{L}}}$

The tail voltage increases


(b)  $V_T = V_{CM} - V_{TH} - \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$

The tail voltage decreases

(c)  $V_T = V_{CM} - V_{TH} - \sqrt{\frac{I_{SS}}{\mu_n \frac{C_{ox}}{2} \frac{W}{L}}}$

The tail voltage decreases

36

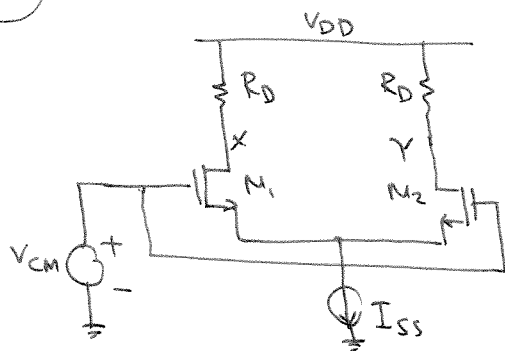

$$\begin{aligned}V_{CM} &= 1V \\ I_{SS} &= 1mA \\ R_D &= 1k\Omega\end{aligned}$$


$$V_X = V_{DD} - R_D \frac{I_{SS}}{2} = V_{DD} - 0.5$$

To ensure that the devices work in saturation

$$V_{CM} \leq V_X - V_{TH} \rightarrow V_{DD} - 0.5 - V_{TH} \geq 1$$

$$\text{if } V_{TH} = 0.5 \rightarrow V_{DD} > 2$$

37

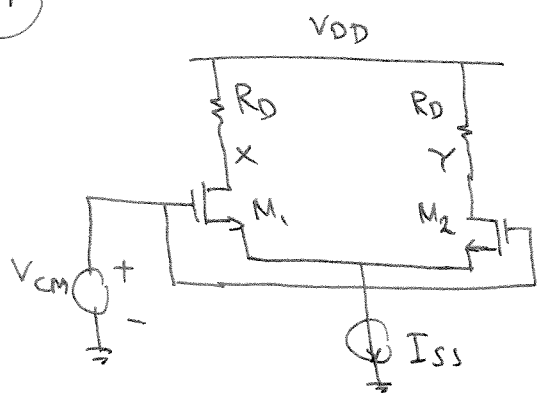


$$V_{GS} - V_{TH} = 200 \text{ mV}$$
$$\mu_n C_{ox} = 100 \text{ } \mu\text{A/V}^2$$
$$\frac{W}{L} = 20/0.18$$

$$(V_{GS} - V_{TH})_{\text{equil}} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \rightarrow$$

$$0.2 = \sqrt{\frac{I_{SS}}{10^{-4} \times \frac{20}{0.18}}} \rightarrow I_{SS} = 0.44 \text{ mA}$$



38

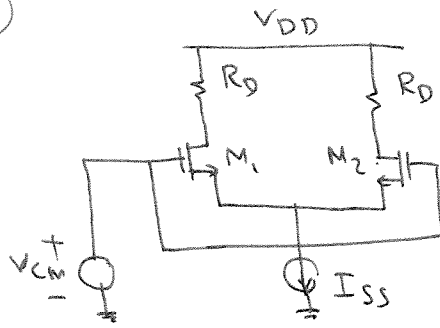


$$\frac{I_{D1}}{W} = \frac{I_{SS}}{2W} = J$$

current density


$$(V_{GS} - V_{TH})_{\text{equil}} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} =$$

$$\sqrt{\frac{2J}{\mu_n C_{ox} \frac{1}{L}}}$$

(39)

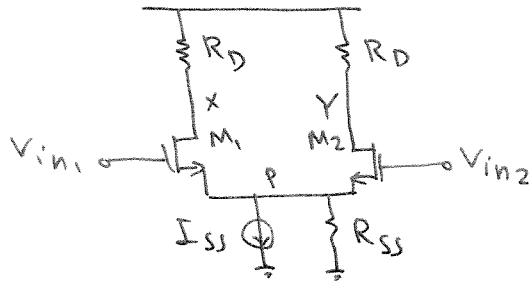

$$g_{m1} = g_{m2} = g_m$$

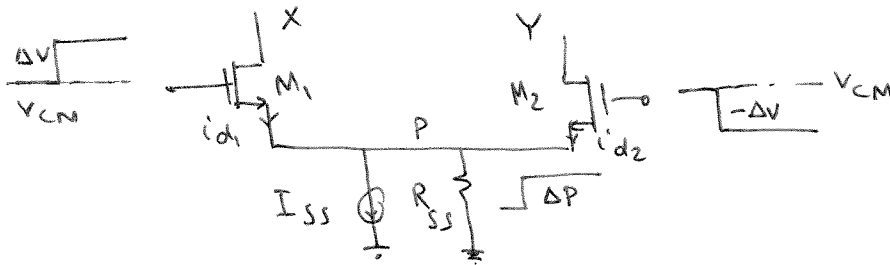


if  $V_{in1}$  and  $V_{in2}$  change by  $\Delta V$  and  $-\Delta V$  we have:

node equation at P:  $i_{d1} + i_{d2} + \frac{\Delta P}{R_{SS}} = 0 \Rightarrow$

$$g_m (\Delta V - \Delta P) + g_m (-\Delta V - \Delta P) + \frac{\Delta P}{R_{SS}} = 0 \Rightarrow$$

$$-g_m \Delta P - g_m \Delta P + \frac{\Delta P}{R_{SS}} = 0 \Rightarrow \Delta P = 0$$

40

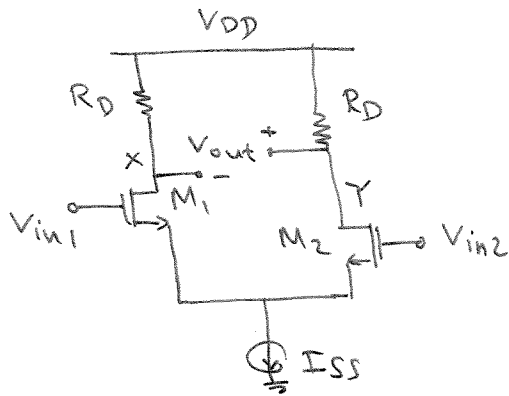

$$V_{in1} = 1.5$$
$$V_{in2} = 0.3$$

$$V_x - V_{TH} > V_{in1} \rightarrow V_{DD} - R_D I_{SS} - V_{TH} > 1.5$$

41

$$P = 2 \text{ mW}$$

$$V_{DD} = 2 \text{ V} \rightarrow I_{SS} = 1 \text{ mA}$$

$$V_{CM, out} = V_{DD} - R_D \frac{I_{SS}}{2} = 2 - 0.5 R_D \rightarrow$$

$$R_D = \frac{2 - V_{CM, out}}{0.5} \text{ (k}\Omega\text{)}$$

$$g_m R_D = 5 \rightarrow \sqrt{2 \mu_n C_{ox} \frac{W}{L} \frac{I_{SS}}{2}} \cdot \frac{2 - V_{CM, out}}{0.5} = 5$$

$\downarrow$  k $\Omega$

$$\rightarrow \sqrt{2 \times 10^{-4} \frac{W}{L} \frac{10^{-3}}{2}} \cdot 2 \times 10^3 (2 - V_{CM, out}) = 5$$

$$\text{if } V_{CM, out} = 1.6 \rightarrow \frac{W}{L} = 390.625$$


To formulate the trade off we have:

$$I_{SS} = \frac{2}{V_{DD}} \text{ mA} \Rightarrow R_D = \frac{V_{DD} - V_{CM, out}}{1} \times V_{DD} \text{ (k}\Omega\text{)}$$

$$\Rightarrow |g_m R_D| = 5 \Rightarrow$$

$$\sqrt{2 \times 10^{-4} \left(\frac{W}{L}\right) \frac{1}{V_{DD}} \times 10^{-3}} (V_{DD} - V_{CM, out}) V_{DD} = 5$$

(42)

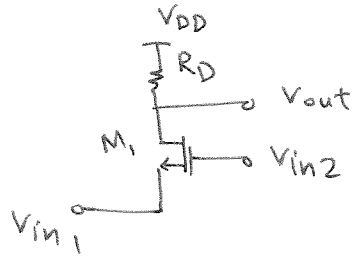

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{in2} - V_{in1} - V_{TH})^2$$

- (1) The current is not an odd function of  $(V_{in2} - V_{in1})$ . Therefore it is not symmetric around  $V_{in1} = V_{in2} [(V_{in1} - V_{in2}) = 0]$ .
- (2) The input impedance seen at  $V_{in1}$  and  $V_{in2}$  are different
- (3) The circuit cannot suppress the supply noise because there is no differential output available.

(43)

$$(V_{in1} - V_{in2})^2 = \frac{2}{\mu_n C_{ox} \frac{W}{L}} (I_{SS} - 2\sqrt{I_{D1} I_{D2}})$$

(a)

$$I_{D1} = 0 \Rightarrow$$

$$(V_{in1} - V_{in2})^2 = \frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}} \rightarrow V_{in1} - V_{in2} = \sqrt{\frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

This is the minimum differential input voltage to turn  $M_1$  off.

$$(b) \quad I_{D1} = \frac{I_{SS}}{2} \Rightarrow I_{D2} = \frac{I_{SS}}{2}$$

$$(V_{in1} - V_{in2})^2 = \frac{2}{\mu_n C_{ox} \frac{W}{L}} (I_{SS} - I_{SS}) = 0 \rightarrow V_{in1} - V_{in2} = 0$$

This is the equilibrium input case.

$$(c) \quad I_{D1} = I_{SS} \rightarrow I_{D2} = 0$$

$$(V_{in1} - V_{in2})^2 = \frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}} \rightarrow V_{in1} - V_{in2} = \sqrt{\frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

This is the minimum input differential

voltage to turn  $M_2$  off.

(44)

$$I_{D1} = \frac{I_{SS}}{2} - \frac{1}{4} \sqrt{4I_{SS}^2 - \left[ \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 - 2I_{SS} \right]}$$

The analyses which led to the above equation assume that the transistors work in saturation region.

So,

$$-(V_{in1} - V_{in2})_{\max} \leq V_{in1} - V_{in2} \leq (V_{in1} - V_{in2})_{\max}$$

$$(V_{in1} - V_{in2})_{\max} = \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \Rightarrow$$

$$\mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 \leq 2I_{SS} \Rightarrow$$


$$- \left[ \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 - 2I_{SS} \right] \geq 0 \Rightarrow$$

$$\frac{1}{4} \sqrt{4I_{SS}^2 - \left[ \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 - 2I_{SS} \right]} \geq \frac{1}{2} I_{SS}$$

$$\Rightarrow I_{D1} < 0$$

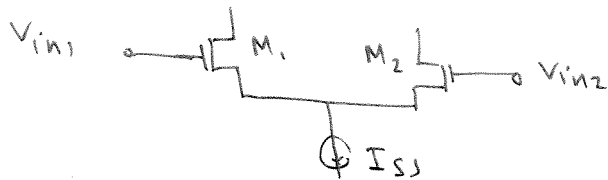(45)

$$I_{D1} - I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}$$



The equilibrium overdrive voltage is:

$$(V_{GS1} - V_{TH})_{\text{equil}} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} = V_{OV} \Rightarrow$$

$$\mu_n C_{ox} \frac{W}{L} = \frac{I_{SS}}{V_{OV}^2} \quad \text{therefore}$$

$$I_{D1} - I_{D2} = \frac{I_{SS}}{2} \frac{(V_{in1} - V_{in2})}{V_{OV}^2} \sqrt{\frac{4I_{SS}}{\frac{I_{SS}}{V_{OV}^2}} - (V_{in1} - V_{in2})^2} \Rightarrow$$

$$I_{D1} - I_{D2} = I_{SS} \Rightarrow$$

$$I_{SS} = \frac{I_{SS}}{2} \frac{(V_{in1} - V_{in2})}{V_{OV}^2} \sqrt{4V_{OV}^2 - (V_{in1} - V_{in2})^2}$$

$$\Rightarrow (V_{in1} - V_{in2})^4 - 4V_{OV}^2 (V_{in1} - V_{in2})^2 + 4V_{OV}^4 = 0$$

$$\Rightarrow ((V_{in1} - V_{in2})^2 - 2V_{OV}^2)^2 = 0 \Rightarrow$$

$$V_{in1} - V_{in2} = \sqrt{2} V_{OV} = \sqrt{2} \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$



(46)

$$I_{D1} - I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}$$

$$V_{ov} = (V_{GS} - V_{TH})_{\text{equil}} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \Rightarrow \mu_n C_{ox} \frac{W}{L} = \frac{I_{SS}}{V_{ov}^2}$$

$$\Rightarrow I_{D1} - I_{D2} = \frac{I_{SS}}{2} \frac{(V_{in1} - V_{in2})}{V_{ov}^2} \sqrt{4V_{ov}^2 - (V_{in1} - V_{in2})^2}$$

$$\Rightarrow G_m = \frac{\partial(I_{D1} - I_{D2})}{\partial(V_{in1} - V_{in2})} =$$


$$\frac{I_{SS}}{2V_{ov}^2} \left[ \frac{\sqrt{4V_{ov}^2 - (V_{in1} - V_{in2})^2}}{\sqrt{4V_{ov}^2 - (V_{in1} - V_{in2})^2}} - \frac{(V_{in1} - V_{in2})^2}{\sqrt{4V_{ov}^2 - (V_{in1} - V_{in2})^2}} \right] =$$

$$\frac{I_{SS}}{2V_{ov}^2} \frac{4V_{ov}^2 - 2(V_{in1} - V_{in2})^2}{\sqrt{4V_{ov}^2 - (V_{in1} - V_{in2})^2}} =$$

$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} \frac{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - 2(V_{in1} - V_{in2})^2}{\sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}}$$

$$V_{in1} - V_{in2} = 0 \Rightarrow$$
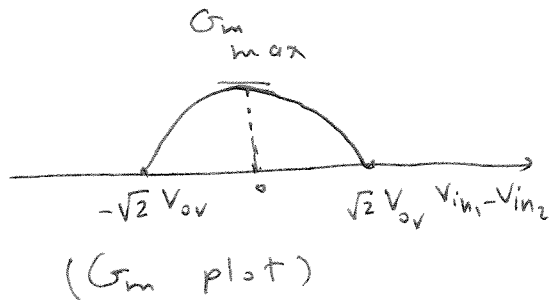
$$G_{m \max} = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}}$$



47

From problem 46:

$$G_{m \max} = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} = \sqrt{\frac{I_{SS}}{V_{ov}^2} I_{SS}} = \frac{I_{SS}}{V_{ov}}$$

$$\Rightarrow \text{if } G_m = \frac{1}{2} \frac{I_{SS}}{V_{ov}} \text{ we have}$$

$$\frac{1}{2} \frac{I_{SS}}{V_{ov}} = \frac{I_{SS}}{2 V_{ov}^2} \frac{4V_{ov}^2 - 2(V_{in1} - V_{in2})^2}{\sqrt{4V_{ov}^2 - (V_{in1} - V_{in2})^2}} \Rightarrow$$

$$V_{ov} = \frac{4V_{ov}^2 - 2(V_{in1} - V_{in2})^2}{\sqrt{4V_{ov}^2 - (V_{in1} - V_{in2})^2}} \Rightarrow$$

$$(4V_{ov}^2 - (V_{in1} - V_{in2})^2) V_{ov}^2 = 16V_{ov}^4 + 4(V_{in1} - V_{in2})^4 - 16V_{ov}^2 (V_{in1} - V_{in2})^2$$

$$\Rightarrow 4(V_{in1} - V_{in2})^4 - 15V_{ov}^2 (V_{in1} - V_{in2})^2 + 12V_{ov}^4 = 0$$

$$\Rightarrow (V_{in1} - V_{in2})^2 = \frac{15V_{ov}^2 \pm \sqrt{225V_{ov}^4 - 192V_{ov}^4}}{8} =$$

$$\frac{15V_{ov}^2 \pm \sqrt{33} V_{ov}^2}{8}$$


positive sign is not accepted

$$\text{because } (V_{in1} - V_{in2})^2 \leq 2V_{ov}^2 \Rightarrow$$


$$V_{in1} - V_{in2} = \pm \sqrt{\frac{15 - \sqrt{33}}{8}} V_{ov} = \pm 1.0756 V_{ov}$$

48-

$$I_D = \gamma (V_{GS} - V_{TH})^3$$

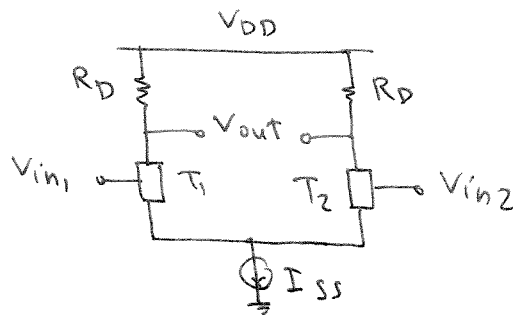

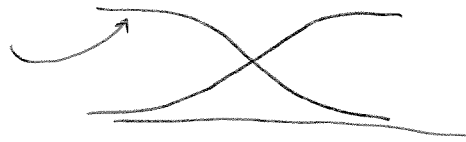(a) The characteristic of  $I_{D1} - I_{D2}$  vs.  $V_{in1} - V_{in2}$  is similar to the standard CMOS differential pair, because it has saturation part.



(b)  $I_D = \frac{I_{SS}}{2} = \gamma (V_{GS} - V_{TH})^3 \Rightarrow$

$$(V_{GS} - V_{TH})_{\text{equil}} = \sqrt[3]{\frac{I_{SS}}{2\gamma}}$$

(c)  $I_{D1} = I_{SS} = \gamma (V_{GS1} - V_{TH})^3 \Rightarrow V_{GS1} - V_{TH} = \sqrt[3]{\frac{I_{SS}}{\gamma}}$

$I_{D2} = 0 = \gamma (V_{GS2} - V_{TH})^3 \Rightarrow V_{GS2} - V_{TH} = 0$

$\Rightarrow V_{GS1} - V_{GS2} = V_{in1} - V_{in2} = \sqrt[3]{\frac{I_{SS}}{\gamma}} =$


$$\sqrt[3]{2} (V_{GS} - V_{TH})_{\text{equil}}$$

(49)

(a)

gate oxide thickness is doubled  $\Rightarrow C_{ox}$  is halved  $\Rightarrow$

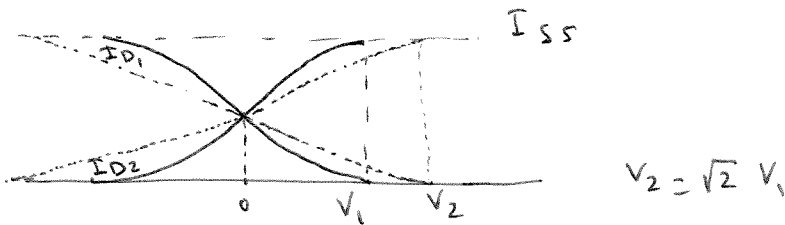
$(V_{in1} - V_{in2})_{max}$  scales up by  $\sqrt{2}$ .



so all the curves stretch out to the sides by  $\sqrt{2}$  times.

(b) if threshold voltage is halved, nothing will change in the curves. The reason is that the curves depend on  $V_{in1} - V_{in2}$ .

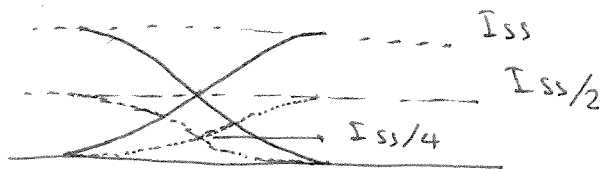
(c) In this case,  $(V_{in1} - V_{in2})_{max}$  does not change so all the curves scale half downward because  $I_{SS}$  is halved.




(50)

if mobility falls then  $(V_{in1} - V_{in2})_{max}$  will increase because  $(V_{in1} - V_{in2})_{max} = \sqrt{\frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$


So the curves stretch out to the sides.

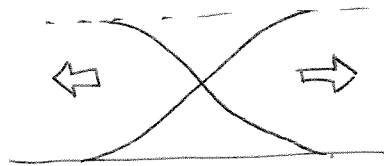

(51)

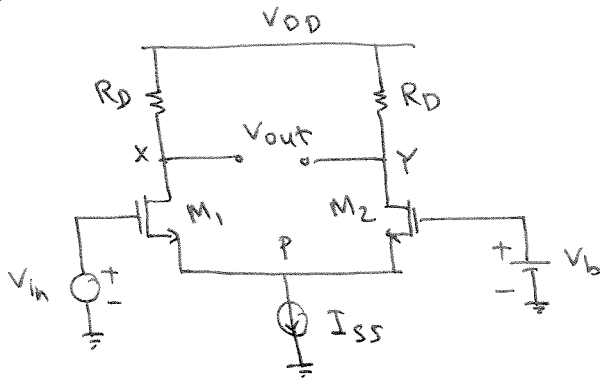


$$g_{m1} = g_{m2} = g_m$$

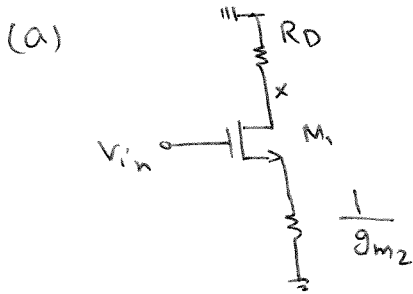

$$v_x = -g_{m1} v_{gs1} R_D =$$

$$-g_{m1} \frac{\frac{1}{g_{m1}}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} v_{in} R_D =$$
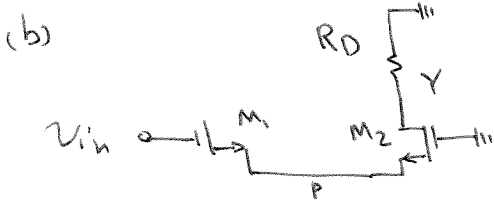
$$-\frac{g_{m1} g_{m2}}{g_{m1} + g_{m2}} R_D v_{in} = -\frac{g_m}{2} R_D v_{in}$$



$$v_p = \frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} v_{in}$$

$$\Rightarrow v_p = \frac{g_{m1}}{g_{m1} + g_{m2}} v_{in} \Rightarrow$$

$$v_y = -g_{m2} v_{gs2} R_D = g_{m2} v_p R_D = \frac{g_{m1} g_{m2}}{g_{m1} + g_{m2}} R_D v_{in}$$


$$\rightarrow v_y = \frac{g_m}{2} R_D v_{in}$$

(c)  $\frac{v_x - v_y}{v_{in}} = -g_m R_D$

This value is equal to the gain of the differential amplifier.


(52)

(a)

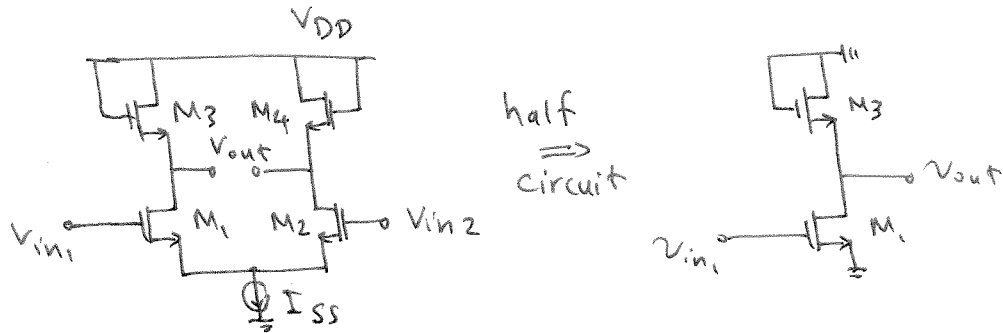


$$A_v = -g_{m1} (r_{o1} \parallel r_{o3} \parallel \frac{1}{g_{m3}})$$

(b)

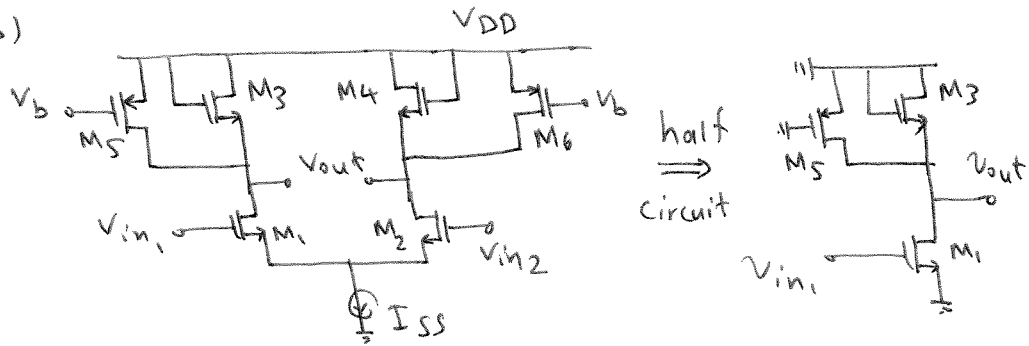


$$A_v = -g_{m1} (r_{o1} \parallel r_{o5} \parallel \frac{1}{g_{m3}} \parallel r_{o3})$$

(c)

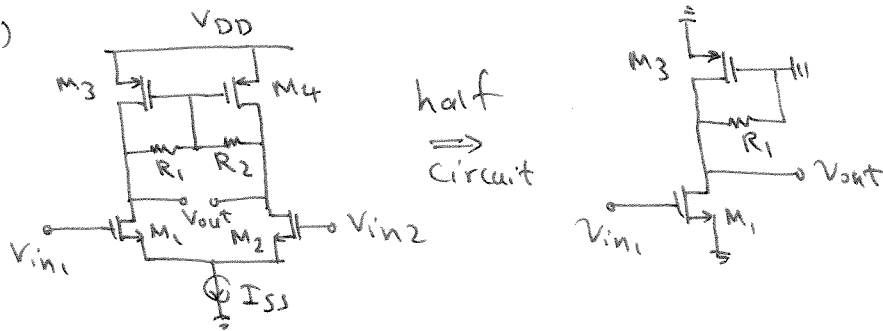


$$A_v = -g_{m1} (r_{o1} \parallel r_{o3} \parallel R_1)$$

(53)

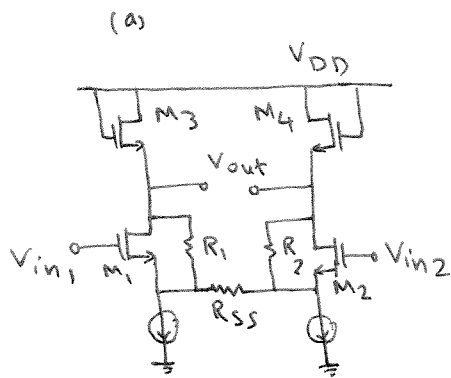


half  
⇒  
circuit

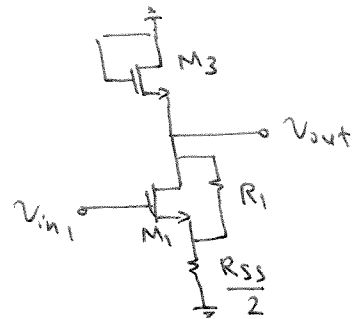

$$R_{out} = (r_{o3} \parallel \frac{1}{g_{m3}}) \parallel (g_{m1} (R_1 \parallel r_{o1}) \frac{R_{SS}}{2} + \frac{R_{SS}}{2} + R_1 \parallel r_{o1})$$

To calculate  $G_m$ :

$$v_{gs1} = v_{in} - v_s$$

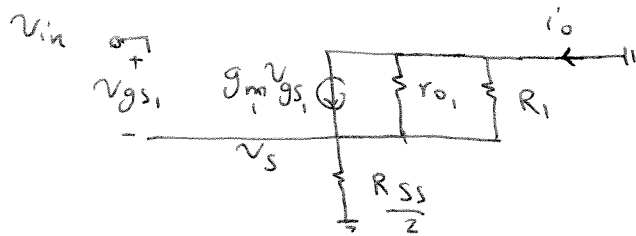

$$\frac{v_s}{\frac{R_{SS}}{2} \parallel R_1 \parallel r_{o1}} + g_{m1} v_s = g_{m1} v_{in} \Rightarrow v_s = \frac{g_{m1} v_{in}}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel R_1 \parallel r_{o1}}}$$

$$i_o = + \frac{v_s}{\frac{R_{SS}}{2}} = + \frac{1}{\frac{R_{SS}}{2}} \frac{g_{m1} v_{in}}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel R_1 \parallel r_{o1}}} \Rightarrow$$


$$G_m = \frac{i_o}{v_{in}} = + \frac{2 g_{m1}}{R_{SS}} \frac{1}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel R_1 \parallel r_{o1}}}$$

$$A_v = -G_m R_{out}$$




53

(b)

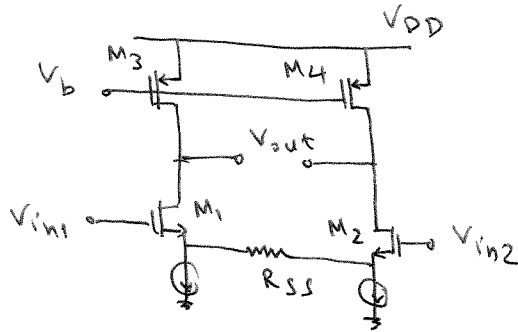


half  
 $\Rightarrow$   
 circuit

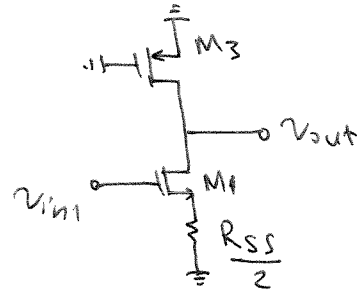

$$R_{out} = r_{o3} \parallel \left( g_{m1} r_{o1} \frac{R_{SS}}{2} + r_{o1} + \frac{R_{SS}}{2} \right)$$


To calculate  $G_m$ :

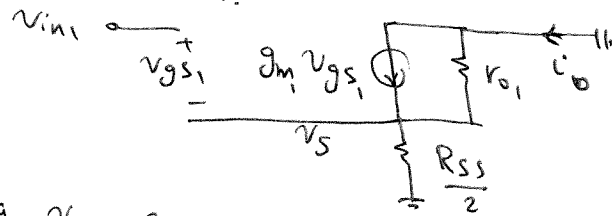


$$\frac{v_s}{r_{o1} \parallel \frac{R_{SS}}{2}} + g_{m1} v_s = g_{m1} v_{in} \Rightarrow v_s = \frac{g_{m1} v_{in}}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel r_{o1}}}$$

$$G_m = \frac{i_o}{v_{in}} = + \frac{v_s}{\frac{R_{SS}}{2}} \frac{1}{v_{in}} = + \frac{2g_{m1}}{R_{SS}} \frac{1}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel r_{o1}}}$$

$$\rightarrow A_{v3} = -G_m R_{out}$$

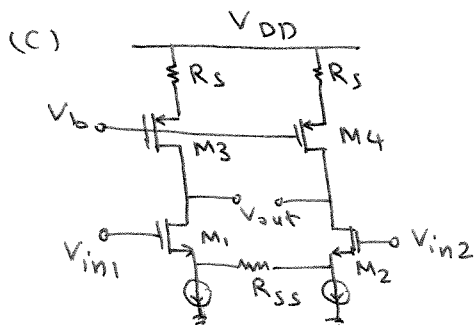

half  
 $\Rightarrow$   
 circuit

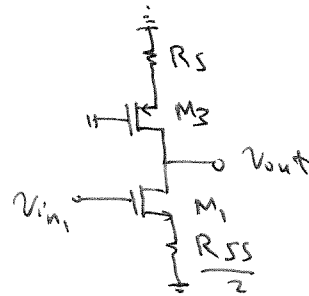


$$R_{out} = (g_{m3} r_{o3} R_s + r_{o3} + R_s) \parallel \left( g_{m1} r_{o1} \frac{R_{SS}}{2} + r_{o1} + \frac{R_{SS}}{2} \right)$$


$G_m$  for this circuit is equal to the one for part (b) so:

$$G_m = + \frac{2g_{m1}}{R_{SS}} \frac{1}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel r_{o1}}} \Rightarrow A_{v2} = -G_m R_{out}$$

(54)

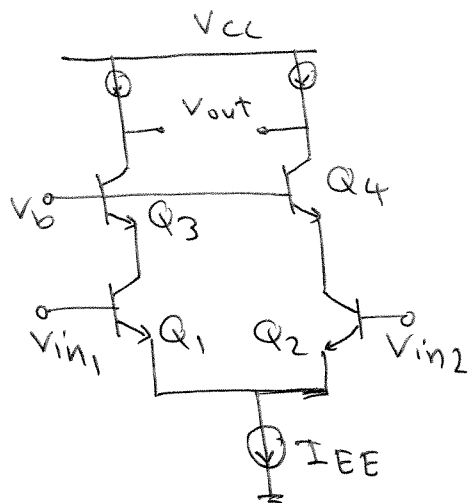

half  
=>  
circuit

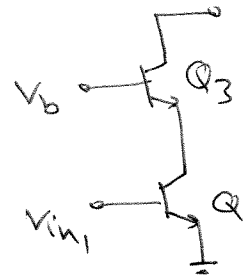

$$A_v = 4000$$
$$\beta = 100$$

$$A_v = -g_{m1} \left[ g_{m3} (r_{o1} \parallel r_{\pi 3}) r_{o3} + r_{o3} + r_{o1} \parallel r_{\pi 3} \right]$$

$$g_{m_{1-4}} = \frac{I_{EE}}{2V_T} \quad r_{o_{1-4}} = \frac{2V_A}{I_{EE}} \quad r_{\pi 3} = \frac{2V_T \beta}{I_{EE}}$$

$$4000 = \frac{I_{EE}}{2V_T} \left[ \frac{I_{EE}}{2V_T} \left( \frac{2V_A}{I_{EE}} \parallel \frac{2V_T \beta}{I_{EE}} \right) \frac{2V_A}{I_{EE}} + \frac{2V_A}{I_{EE}} + \left( \frac{2V_A}{I_{EE}} \parallel \frac{2V_T \beta}{I_{EE}} \right) \right]$$

$$\Rightarrow 4000 = \frac{1}{2V_T} \left[ \frac{V_A}{V_T} (2V_A \parallel 2V_T \beta) + 2V_A + (2V_A \parallel 2V_T \beta) \right] \Rightarrow$$


$$4000 = \frac{1}{V_T} \left[ \frac{V_A}{V_T} (V_A \parallel \beta V_T) + V_A + (V_A \parallel \beta V_T) \right] \Rightarrow$$

$$4000 = \frac{1}{V_T} \left[ \frac{\beta V_A^2}{\beta V_T + V_A} + V_A + \frac{\beta V_A V_T}{\beta V_T + V_A} \right] \Rightarrow$$


$$4000 = \frac{1}{0.026} \left[ \frac{100 V_A^2}{2.6 + V_A} + V_A + \frac{2.6 V_A}{2.6 + V_A} \right] \Rightarrow$$

$$V_A = 2.197$$

(55)

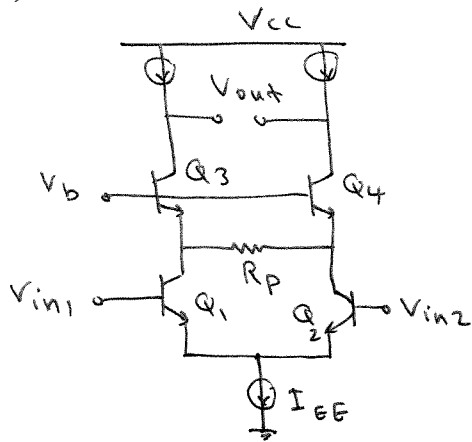

half  
 $\Rightarrow$   
 circuit

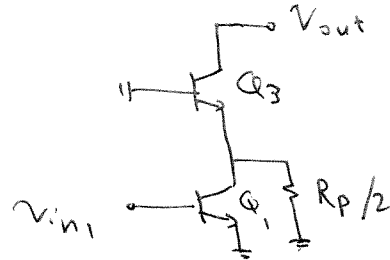


$$R_{out} = g_{m3} r_{o3} \left( \frac{R_p \parallel r_{o1} \parallel r_{o3}}{2} \right) + r_{o3} + \frac{R_p \parallel r_{o1} \parallel r_{o3}}{2}$$

To calculate  $G_m$


$$G_m = \frac{i_o}{v_{in}}$$
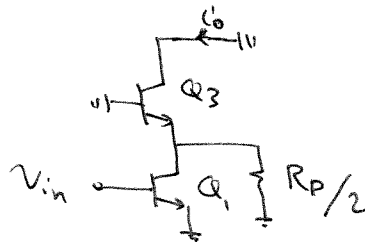
$$\frac{i_o}{v_{in}} = +g_{m1} \frac{g_{m3} \left( \frac{R_p \parallel r_{o1}}{2} \right)}{g_{m3} \left( \frac{R_p \parallel r_{o1}}{2} \right) + 1}$$




$$A_v = -G_m R_{out}$$

(56)

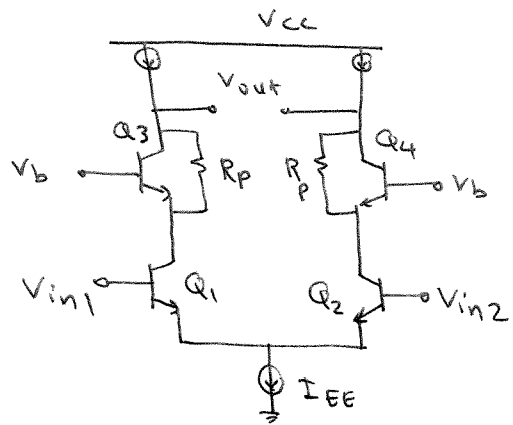


half  
 $\Rightarrow$   
circuit

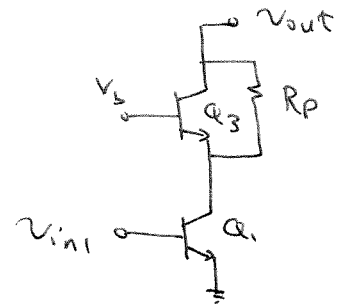


$$A_V = -g_{m_1} ( g_{m_3} (r_{o_3} \parallel R_P) (r_{o_1} \parallel r_{\pi_3}) + (r_{o_3} \parallel R_P) + (r_{o_1} \parallel r_{\pi_3}) )$$

(57)

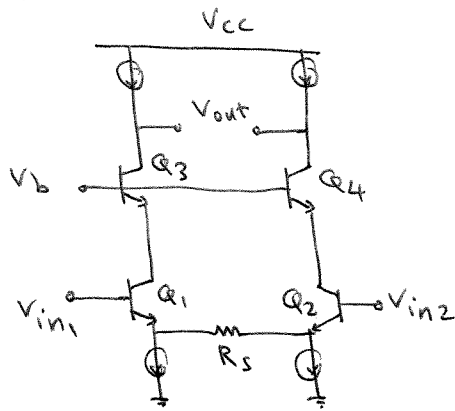

half  
⇒  
circuit

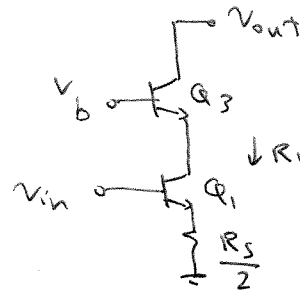


$$R_i = g_{m1} r_{o1} \left( \frac{R_s}{2} \parallel r_{\pi 1} \right) + r_{o1} + \frac{R_s}{2} \parallel r_{\pi 1}$$

$$R_{out} = g_{m3} r_{o3} (R_i \parallel r_{\pi 3}) + r_{o3} + (R_i \parallel r_{\pi 3})$$

To calculate  $G_m$ :

$$v_{\pi 1} \approx \frac{1}{\frac{1}{g_{m1}} + \frac{R_s}{2}} v_{in}$$

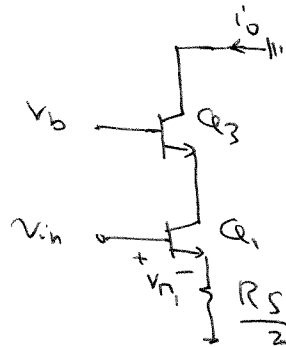
$$= \frac{1}{1 + g_{m1} \frac{R_s}{2}} v_{in}$$




$$G_m = \frac{i_o}{v_{in}} = \frac{+g_{m1} v_{\pi 1}}{v_{in}} = \frac{+g_{m1}}{1 + g_{m1} \frac{R_s}{2}}$$

$$A_v = -G_m R_{out}$$

(58)

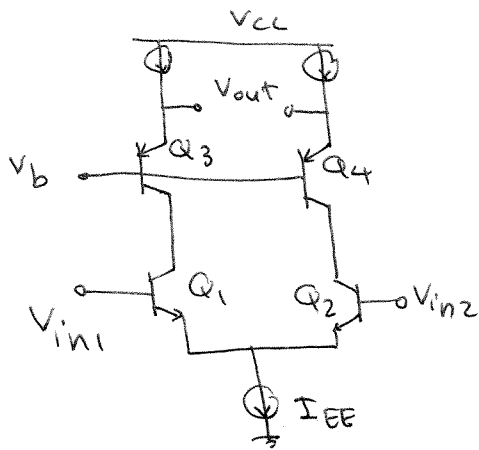


half  
=>  
Circuit

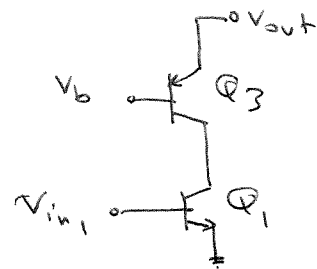

To calculate Rout

$$v_{n3} = v_t$$

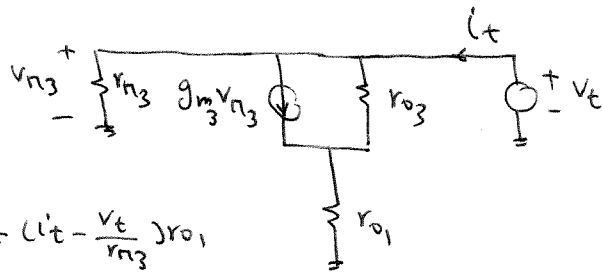

$$v_t = (i_t - g_{m3} v_t - \frac{v_t}{r_{n3}}) r_{o3} + (i_t - \frac{v_t}{r_{n3}}) r_{o1}$$

$$\rightarrow v_t \left( 1 + g_{m3} r_{o3} + \frac{r_{o3}}{r_{n3}} + \frac{r_{o1}}{r_{n3}} \right) = i_t (r_{o1} + r_{o3})$$


$$\rightarrow \frac{v_t}{i_t} = \frac{r_{o1} + r_{o3}}{1 + g_{m3} r_{o3} + \frac{g_{m3} r_{o3}}{\beta_3} + \frac{g_{m3} r_{o1}}{\beta_3}} = R_{out} \rightarrow$$

$$R_{out} \approx \frac{r_{o1} + r_{o3}}{g_{m3} r_{o3}}$$


$$G_m = +g_{m1} \Rightarrow$$

$$A_v \approx -G_m R_{out} \approx -g_{m1} \frac{r_{o1} + r_{o3}}{g_{m3} r_{o3}}$$

(59)

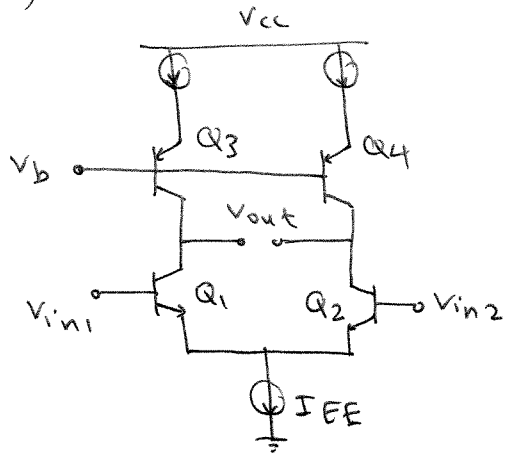


half  
 $\Rightarrow$   
circuit

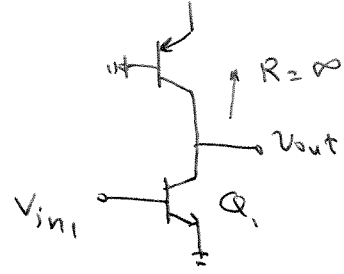


$$A_v = -g_{m1} R_{o1}$$

60

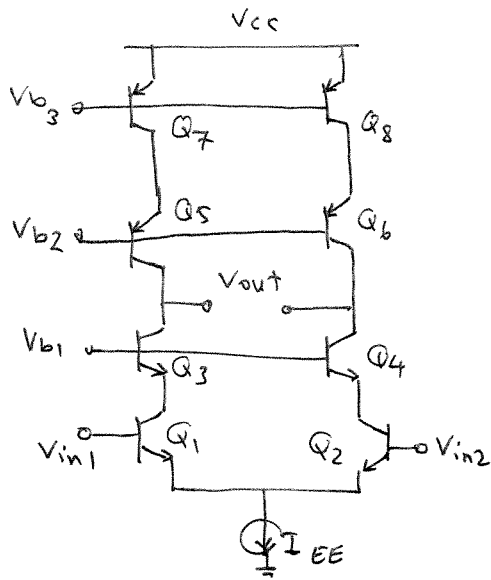

half circuit  
 $\Rightarrow$

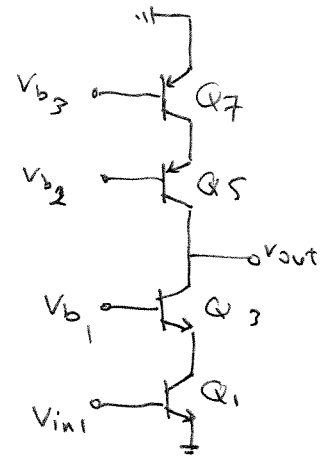

$$A_V = 800, \quad \beta_n = 2\beta_p = 100, \quad V_{A,n} = 2V_{A,p}$$

$$A_V \approx -g_{m1} \left[ g_{m3} r_{o3} (r_{o1} \parallel r_{\pi3}) \right] \parallel \left[ g_{m5} r_{o5} (r_{o7} \parallel r_{\pi5}) \right] =$$

$$- \frac{I_{EE}}{2V_T} \left[ \frac{I_{EE}}{2V_T} \frac{V_{A,n}}{I_{EE}} \left( \frac{V_{A,n}}{I_{EE}} \parallel \frac{\beta_n V_T}{I_{EE}} \right) \right] \parallel \left[ \frac{I_{EE}}{2V_T} \frac{V_{A,p}}{I_{EE}} \left( \frac{V_{A,p}}{I_{EE}} \parallel \frac{\beta_p V_T}{I_{EE}} \right) \right]$$

$$= - \frac{1}{V_T^2} \left[ V_{A,n} (V_{A,n} \parallel \beta_n V_T) \right] \parallel \left[ V_{A,p} (V_{A,p} \parallel \beta_p V_T) \right] =$$


$$- \frac{1}{V_T^2} \left[ V_{A,n} (V_{A,n} \parallel \beta_n V_T) \right] \parallel \left[ \frac{V_{A,n}}{2} \left( \frac{V_{A,n}}{2} \parallel \frac{\beta_n V_T}{2} \right) \right] \Rightarrow$$

$$800 = \frac{1}{5V_T^2} (V_{A,n} (V_{A,n} \parallel 2.6)) \Rightarrow V_{A,n} = 2.245 \text{ V}$$


$$\Rightarrow V_{A,p} = 1.225 \text{ V}$$



61

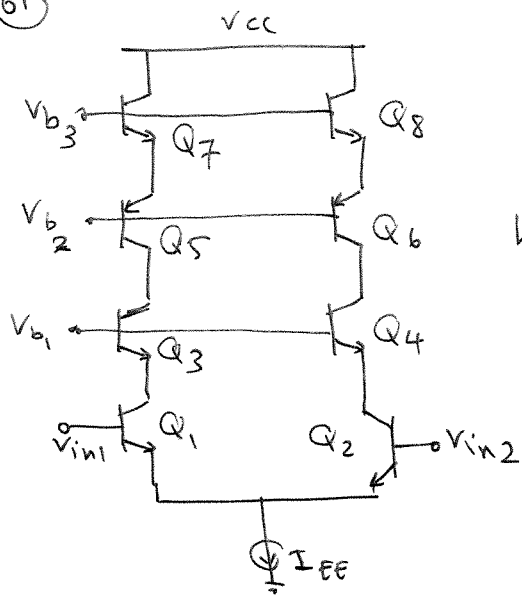

half circuit  
 $\Rightarrow$

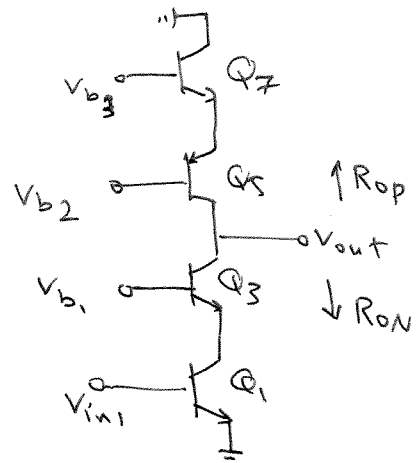



$$R_{oN} = (r_{o1} \parallel r_{\pi 3}) + r_{o3} + g_{m3} r_{o3} (r_{o1} \parallel r_{\pi 3})$$

$$R_{oP} = \frac{1}{g_{m7}} \parallel r_{o7} \parallel r_{\pi 5} + r_{o5} + g_{m5} r_{o5} \left( \frac{1}{g_{m7}} \parallel r_{o7} \parallel r_{\pi 5} \right) \approx$$

$$\frac{1}{g_{m7}} \parallel r_{\pi 5} + r_{o5} + g_{m5} r_{o5} \left( \frac{1}{g_{m7}} \parallel r_{\pi 5} \right)$$

$$A_v = -g_{m1} (R_{oN} \parallel R_{oP})$$

(62)

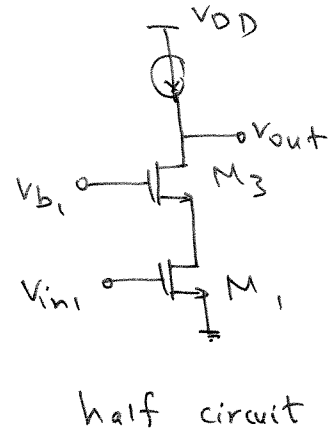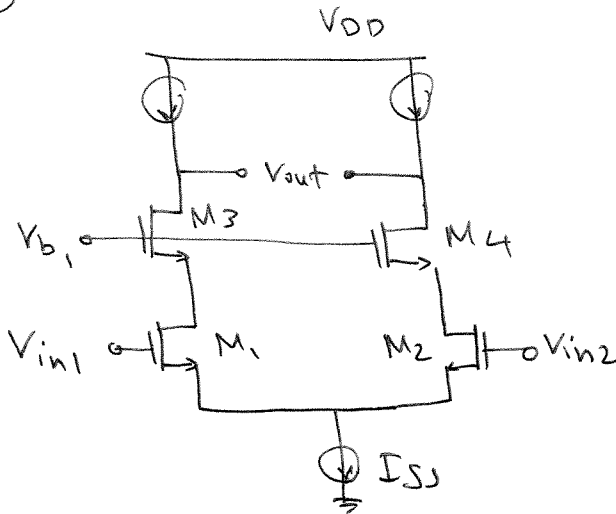

$$A_v = 300, \quad W/L = \frac{20}{0.18}, \quad \mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$$
$$\lambda = 0.1 \text{ V}^{-1}$$

$$A_v \approx -g_{m3} r_{o3} g_{m1} r_{o1}$$

$$g_{m1} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 \frac{I_{SS}}{2}} \quad g_{m3} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_3 \frac{I_{SS}}{2}}$$

$$\rightarrow g_{m1} = g_{m3} = \sqrt{10^{-4} \frac{20}{0.18} I_{SS}}$$



$$r_{o1} = \frac{1}{\lambda \frac{I_{SS}}{2}}, \quad r_{o3} = \frac{1}{\lambda \frac{I_{SS}}{2}} \rightarrow r_{o1} = r_{o3} = \frac{20}{I_{SS}}$$

So:

$$300 = \left(10^{-4} \frac{20}{0.18} I_{SS}\right) \frac{400}{I_{SS}} \Rightarrow$$

$$I_{SS} = 14.815 \text{ mA}$$

63

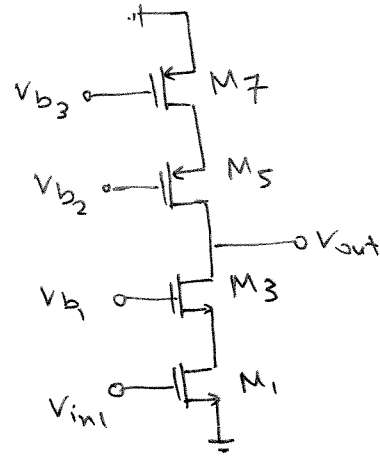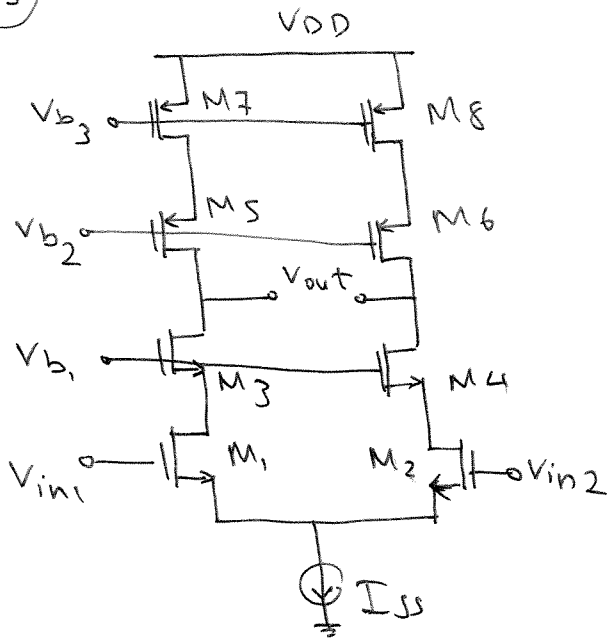

$A_v = 200$ ,  $I_{SS} = 1\text{mA}$ ,  $\mu_n C_{ox} = 100 \mu\text{A/V}^2$   
 $\mu_p C_{ox} = 50 \mu\text{A/V}^2$ ,  $\lambda_n = 0.1\text{V}^{-1}$ ,  $\lambda_p = 0.2\text{V}^{-1}$

$(\frac{W}{L})_1 = \dots = (\frac{W}{L})_8 = ?$



$A_v \approx -g_{m1} [(g_{m3} r_{o3} r_{o1}) || (g_{m5} r_{o5} r_{o7})] \Rightarrow$

$$200 = \sqrt{\mu_n C_{ox} (\frac{W}{L})_1 I_{SS}} \left[ \left( \sqrt{\mu_n C_{ox} (\frac{W}{L})_3 I_{SS}} \left( \frac{2}{\lambda_n I_{SS}} \right)^2 \right) || \left( \sqrt{\mu_p C_{ox} (\frac{W}{L})_5 I_{SS}} \left( \frac{2}{\lambda_p I_{SS}} \right)^2 \right) \right]$$

$$\Rightarrow 200 = \sqrt{10^{-4} (\frac{W}{L})_1 10^{-3}} \left[ \left( \sqrt{10^{-4} (\frac{W}{L})_3 10^{-3}} \left( \frac{20}{10^{-3}} \right)^2 \right) || \left( \sqrt{0.5 \times 10^{-4} (\frac{W}{L})_5 10^{-3}} \left( \frac{10}{10^{-3}} \right)^2 \right) \right]$$


$\Rightarrow \frac{W}{L} = 33.28$

(64)

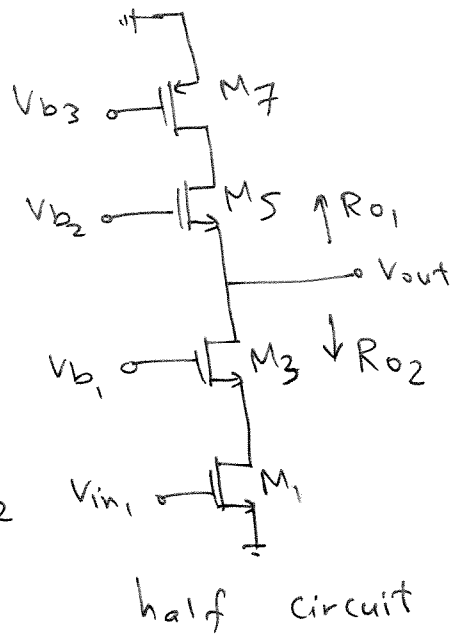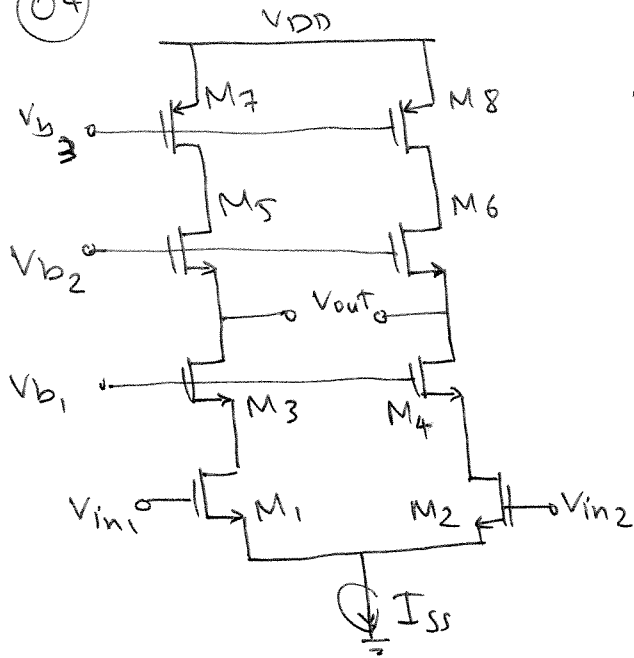

$$R_{o2} = g_{m3} r_{o3} r_{o1} + r_{o1} + r_{o3}$$

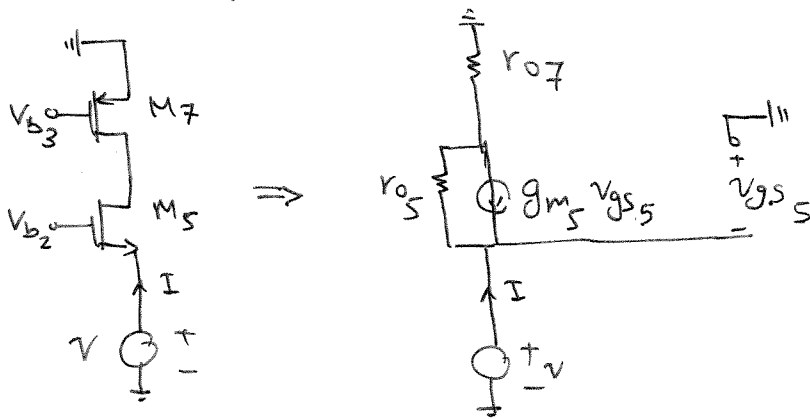To calculate  $R_{o1}$ , using the small signal model we have:






$$v_{gs5} = -v \rightarrow g_{m5} v_{gs5} = -g_{m5} v$$

From KVL: 
$$v = r_{o5} (I - g_{m5} v) + r_{o7} I$$

$$\rightarrow \frac{v}{I} = R_{o1} = \frac{r_{o5} + r_{o7}}{1 + g_{m5} r_{o5}} \Rightarrow A_v = -g_{m1} (R_{o1} \parallel R_{o2})$$


(65)

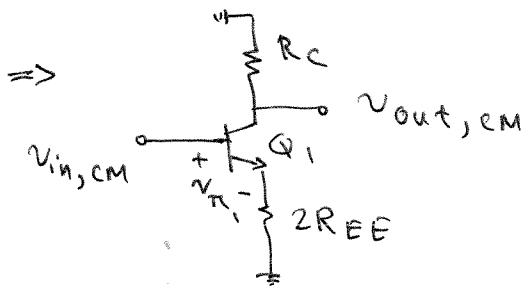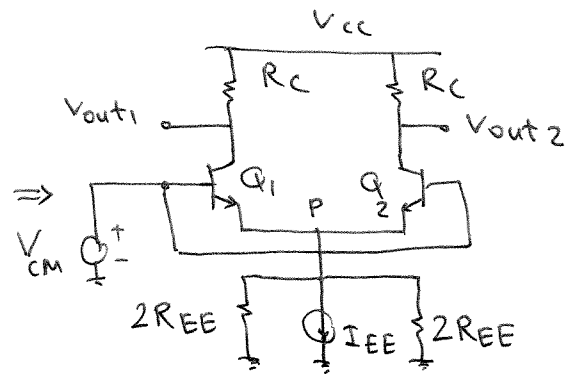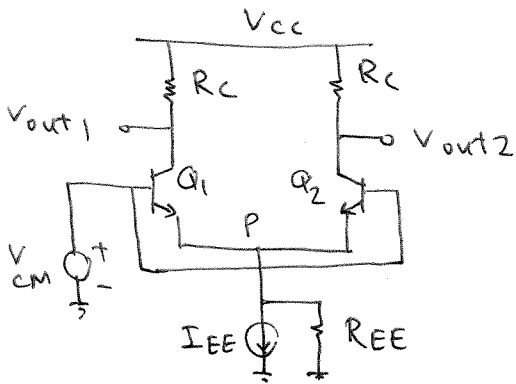

$$v_{out,cm} = -g_{m1} v_{\pi 1} R_c = -g_{m1} R_c \frac{\frac{1}{g_{m1}}}{\frac{1}{g_{m1}} + 2R_{EE}} v_{in,cm}$$

$$\Rightarrow \frac{v_{out,cm}}{v_{in,cm}} = -\frac{g_{m1} R_c}{1 + 2R_{EE} g_{m1}} = -\frac{\frac{R_c}{2}}{R_{EE} + \frac{1}{2g_{m1}}}$$

66

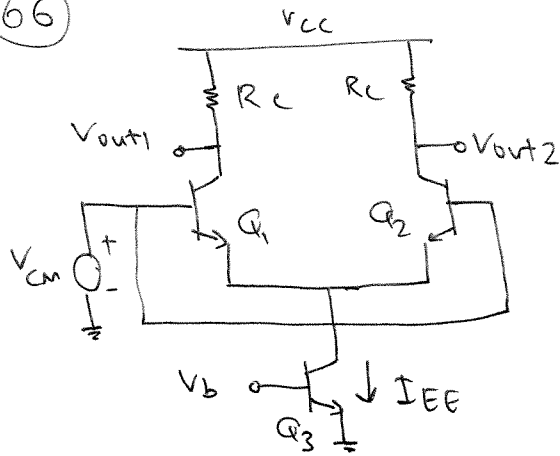


$$A_{cm} = \frac{\Delta V_{out, CM}}{\Delta V_{in, CM}} = \frac{R_c/2}{\frac{1}{2g_m} + r_{o3}} \Rightarrow$$


$$A_{cm} \leq 0.01 \Rightarrow \frac{R_c/2}{\frac{1}{2 \frac{I_{EE}}{2V_T}} + \frac{V_A}{I_{EE}}} < 0.01 \Rightarrow$$

$$\frac{R_c I_{EE}}{2(V_A + V_T)} < 0.01 \Rightarrow R_c I_{EE} < 0.02(V_A + V_T)$$

67

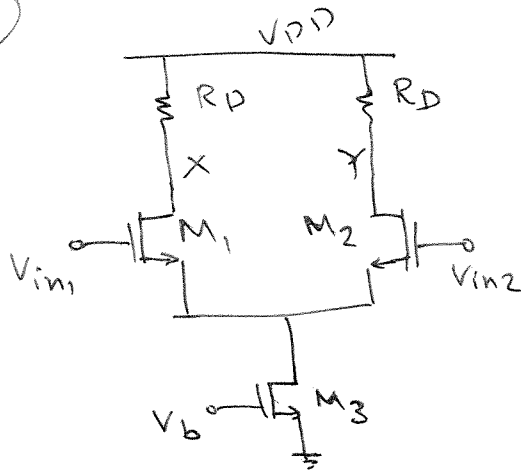

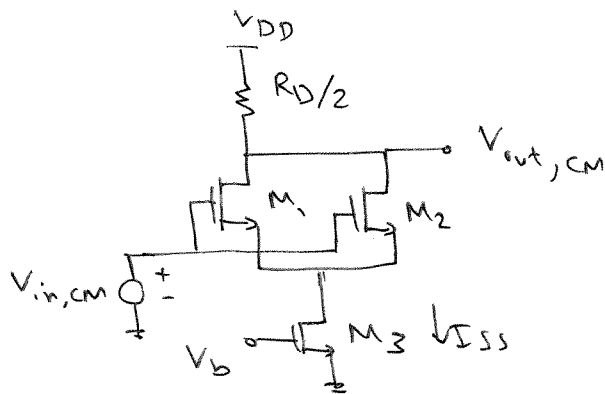The same value for the inputs common-mode leads to the following circuit:



$$g_{m1} = g_{m2} = \frac{2 I_{SS}/2}{(V_{GS} - V_{TH})_{eq}}$$


$$= \frac{I_{SS}}{(V_{GS} - V_{TH})_{eq}}$$

$$\frac{\Delta V_{out, CM}}{\Delta V_{in, CM}} = - \frac{R_D/2}{\frac{1}{2g_{m1}} + r_{o3}}$$

$$= \frac{- R_D}{\frac{1}{g_{m1}} + 2r_{o3}} = \frac{- R_D}{\frac{(V_{GS} - V_{TH})_{eq}}{I_{SS}} + \frac{2}{\lambda I_{SS}}} \Rightarrow$$

$$A_{CM} = - \frac{R_D I_{SS}}{\frac{2}{\lambda} + (V_{GS} - V_{TH})_{eq}}$$

(68)

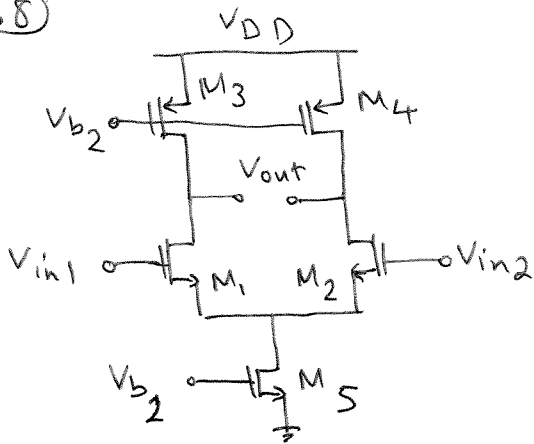


$$\lambda > 0, g_m r_o \gg 1$$

$$r_{o3} = r_{o4}$$

$$r_{o1} = r_{o2}$$

$$g_{m1} = g_{m2}$$

For the common mode input we have:

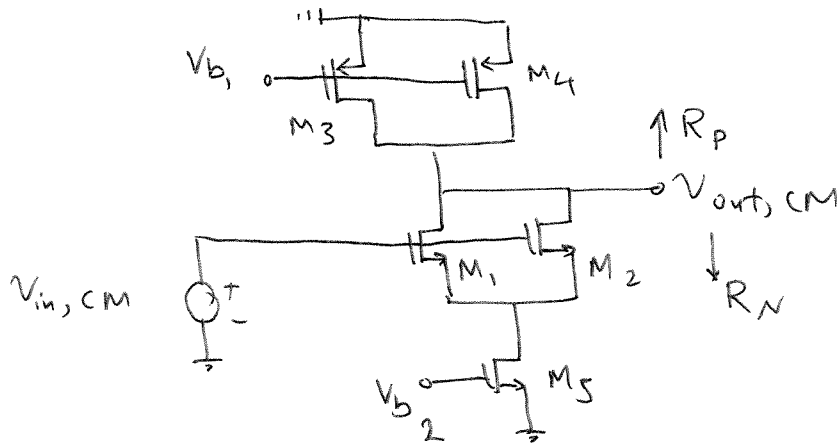


$$R_P = r_{o3} \parallel r_{o4} = \frac{r_{o3}}{2} = \frac{r_{o4}}{2}$$

$$R_N = r_{o5} + \frac{r_{o1}}{2} + 2g_{m1} \frac{r_{o1}}{2} r_{o5} =$$

$$g_{m1} r_{o1} r_{o5} + r_{o5} + \frac{r_{o1}}{2}$$

$$\frac{i_o}{v_{in,CM}} = G_m = \frac{2g_{m1} v_{gs1}}{v_{in,CM}} = 2g_{m1} \frac{\frac{1}{2g_{m1}}}{\frac{1}{2g_{m1}} + r_{o5}}$$
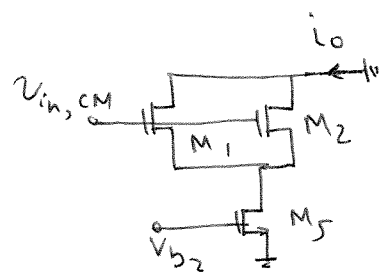
$$\rightarrow G_m = \frac{2g_{m1}}{1 + 2g_{m1} r_{o5}} \approx \frac{1}{r_{o5}}$$





$$\Rightarrow A_{CM} = -G_m R_o$$


$$R_o = R_P \parallel R_N = \frac{r_{o4}}{2} \parallel (g_{m1} r_{o1} r_{o5} + r_{o5} + \frac{r_{o1}}{2})$$

$$\approx \frac{r_{o4}}{2} \parallel g_{m1} r_{o1} r_{o5} \approx \frac{r_{o4}}{2}$$


$$\rightarrow A_{CM} = -\frac{1}{r_{o5}} \frac{r_{o4}}{2} = -\frac{r_{o4}}{2 r_{o5}}$$

(69)

(a)

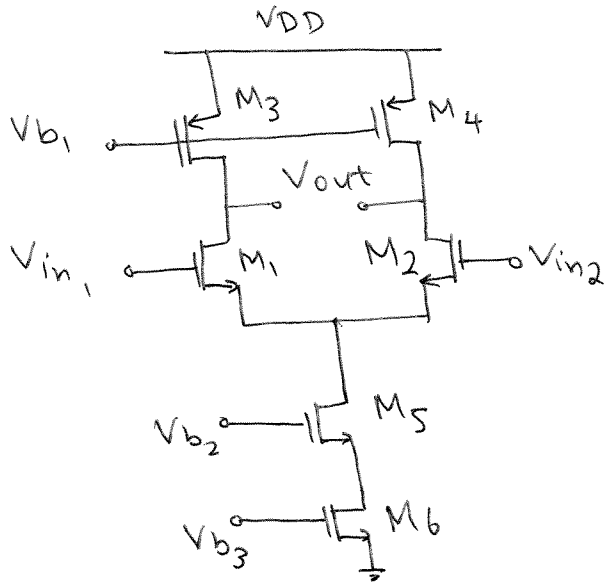

For the common mode input :

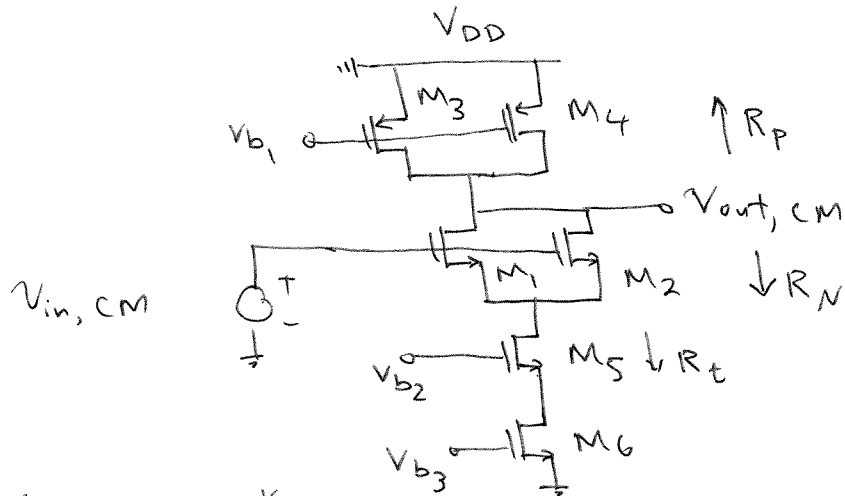

$$R_P = r_{o3} \parallel r_{o4} = \frac{r_{o3}}{2}$$

$$R_N = \frac{r_{o1}}{2} + R_t + 2g_{m1} \frac{r_{o1}}{2} R_t \approx g_{m1} r_{o1} R_t \approx$$


$$g_{m1} r_{o1} g_{m5} r_{o5} r_{o6}$$

$$R_{out} = R_P \parallel R_N = \frac{r_{o3}}{2} \parallel g_{m1} g_{m5} r_{o1} r_{o5} r_{o6} \approx \frac{r_{o3}}{2}$$

To calculate  $G_m$ :

$$G_m = \frac{i_o}{v_{in, CM}} = \frac{2g_{m1} v_{gs1}}{v_{in, CM}}$$
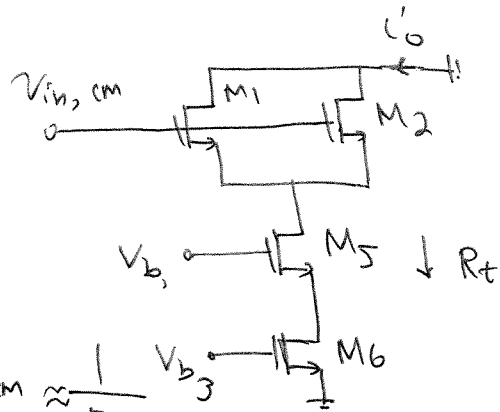
$$= \frac{2g_{m1}}{v_{in, CM}} \frac{\frac{1}{2g_{m1}}}{\frac{1}{2g_{m1}} + R_t} v_{in, CM} \approx \frac{1}{R_t}$$




$$\rightarrow A_{CM} = -G_m R_{out} = -\frac{r_{o3}}{2R_t} =$$

$$\frac{r_{o3}}{2g_{m5} r_{o5} r_{o6}}$$

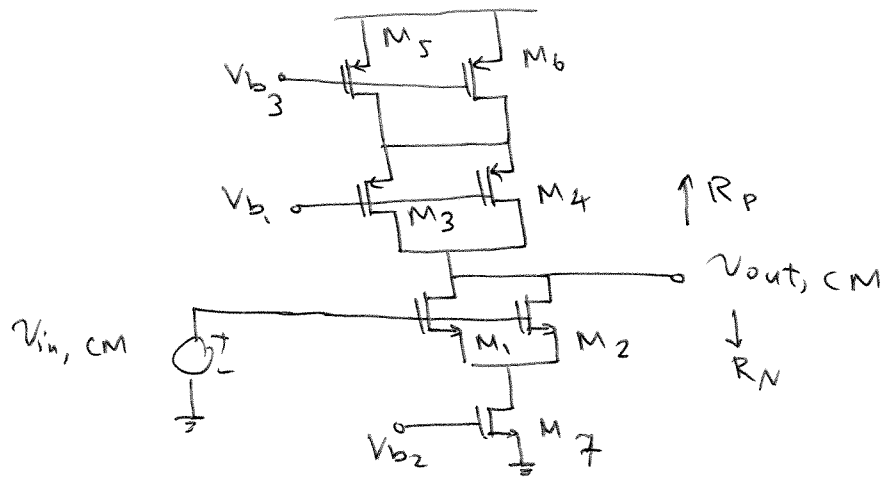(69) (b)

For the common mode input, the circuit is:




$$R_P = 2g_{m3} \frac{r_{o3}}{2} \frac{r_{o5}}{2} + \frac{r_{o3}}{2} + \frac{r_{o5}}{2} \approx \frac{g_{m3} r_{o3} r_{o5}}{2}$$

$$R_N = 2g_{m1} \frac{r_{o1}}{2} r_{o7} + \frac{r_{o1}}{2} + r_{o7} \approx g_{m1} r_{o1} r_{o7}$$

$$R_{out} = R_N \parallel R_P$$

To calculate  $G_m$ :

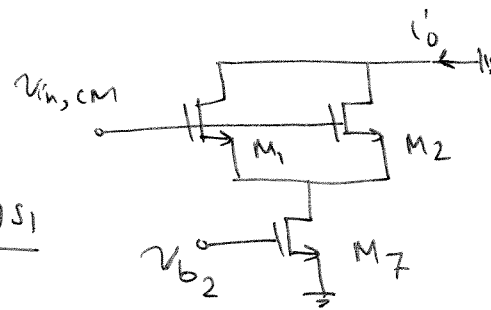


$$G_m = \frac{i'_o}{v_{in,CM}} = \frac{2g_{m1} v_{gs1}}{v_{in,CM}}$$

$$= \frac{2g_{m1}}{v_{in,CM}} \frac{\frac{1}{2g_{m1}}}{\frac{1}{2g_{m1}} + r_{o7}} v_{in,CM} \approx \frac{1}{r_{o7}}$$


$$\rightarrow A_{cm} = -G_m R_{out}$$

(70)


(a)

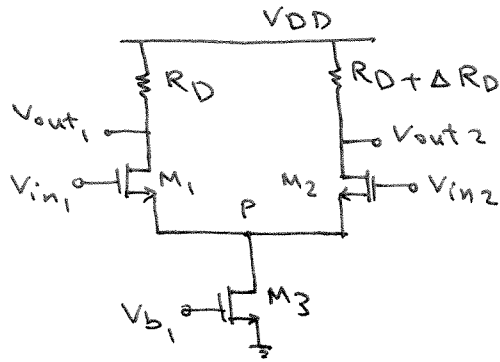

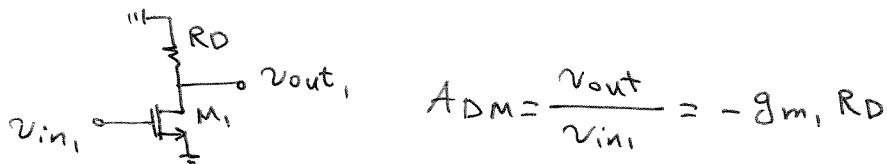To calculate  $A_{DM}$ , using the half circuit:



To calculate  $A_{CM-DM}$  we have:

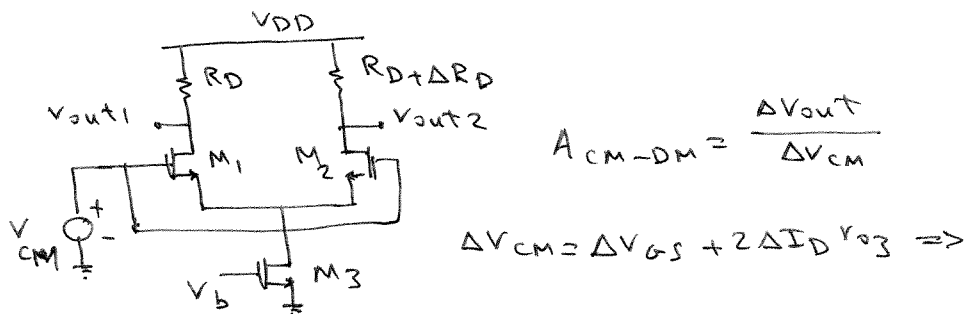


$$\Delta V_{cm} = \Delta I_D \left( \frac{1}{g_{m1}} + 2r_{o3} \right)$$

$$\Delta V_{out} = \Delta V_{out1} - \Delta V_{out2} = -\Delta R_D \Delta I_D \Rightarrow$$

$$A_{CM-DM} = - \frac{\Delta R_D}{\frac{1}{g_{m1}} + 2r_{o3}} \Rightarrow$$

$$CMRR = \frac{A_{DM}}{A_{CM-DM}} = \frac{g_{m1} R_D}{\frac{\Delta R_D}{\frac{1}{g_{m1}} + 2r_{o3}}} = (1 + 2g_{m1} r_{o3}) \frac{R_D}{\Delta R_D}$$

(70) (b)

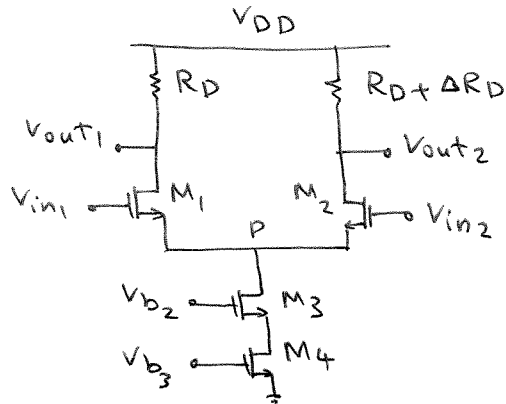

To calculate  $A_{DM}$ , using the half circuit, we have

$$A_{DM} = \frac{V_{out1}}{V_{in1}} = -g_{m1} R_D$$


Similar to part (a) we have:

$$A_{CM-DM} = - \frac{\Delta R_D}{\frac{1}{g_{m1}} + 2 [g_{m3} r_{o3} r_{o4} + r_{o3} + r_{o4}]}$$

$$\Rightarrow CMMR = \frac{A_{DM}}{A_{CM-DM}} = (1 + 2g_{m1} [g_{m3} r_{o3} r_{o4} + r_{o3} + r_{o4}]) \frac{R_D}{\Delta R_D}$$

Notice that CMMR of part (b) is much higher than the one for part (a).

71

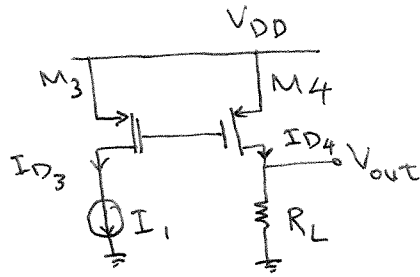


$$\left(\frac{W}{L}\right)_3 = N \left(\frac{W}{L}\right)_4$$

$$\left(\frac{W}{L}\right)_3 = N \left(\frac{W}{L}\right)_4 \Rightarrow I_{D3} = N I_{D4} \Rightarrow \underbrace{i_{d3} = N i_{d4}}_{\text{small signal}}$$

$$\left. \begin{array}{l} i_{d3} = i_i \\ v_{out} = R_L i_{d4} = \frac{R_L}{N} i_{d3} = \frac{R_L}{N} i_i \Rightarrow \end{array} \right\}$$

$$\frac{v_{out}}{i_i} = \frac{R_L}{N}$$

72

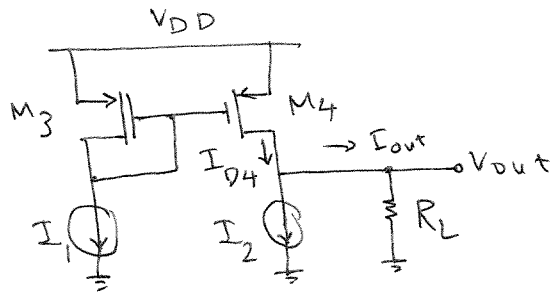

$$(a) \left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4$$

if  $I_1 = I_2 = I_0$   $\Rightarrow \begin{cases} V_{out} = I_{out} \times R_L = 0 & \text{because} \\ I_{out} = I_{D4} - I_2 = I_1 - I_2 = 0 \end{cases}$

$$\text{if } I_1 = I_0 + \Delta I \Rightarrow I_{D4} = I_{D3} = I_1 = I_0 + \Delta I$$

$$I_2 = I_0 - \Delta I \Rightarrow I_{out} = I_{D4} - I_2 = 2\Delta I$$

$$V_{out} = I_{out} R_L = 2 R_L \Delta I$$

$$(b) \left(\frac{W}{L}\right)_3 = 2\left(\frac{W}{L}\right)_4$$

$$\Rightarrow I_{D3} = 2 I_{D4}$$

$$\text{if } I_1 = I_2 = I_0 \text{ then } I_{D3} = I_1 = I_0 \Rightarrow I_{D4} = \frac{I_{D3}}{2}$$

$$\Rightarrow I_{D4} = \frac{I_0}{2} \Rightarrow I_{out} = I_{D4} - I_2 = -\frac{I_0}{2}$$

$$\Rightarrow V_{out} = R_L I_{out} = -\frac{R_L I_0}{2}$$


$$\text{if } I_1 = I_0 + \Delta I \Rightarrow I_{D4} = \frac{I_{D3}}{2} = \frac{I_1}{2} = \frac{I_0 + \Delta I}{2}$$

$$I_2 = I_0 - \Delta I \Rightarrow I_{out} = I_{D4} - I_2 = -\frac{I_0}{2} + \frac{3\Delta I}{2}$$

$$\Rightarrow V_{out} = R_L I_{out} = +R_L \left(-\frac{I_0}{2} + \frac{3\Delta I}{2}\right)$$



(73)

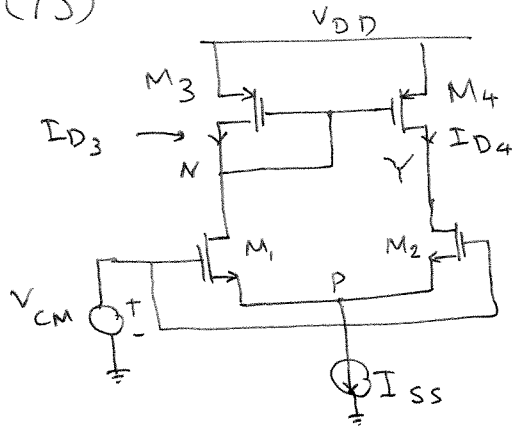

$$V_{TH3} = |V_{TH,P}|$$

$$(a) \quad I_{D3} = \frac{I_{SS}}{2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_3 (V_{SG3} - V_{TH})^2 \Rightarrow$$

$$V_{SG3} = V_{TH3} + \sqrt{\frac{I_{SS}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_3}}$$


$$V_N = V_{DD} - V_{SG3} = V_{DD} - V_{TH} - \sqrt{\frac{I_{SS}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_3}}$$

(b) Since the circuit is symmetric:

$$\begin{cases} I_{D3} = I_{D4} \\ V_{SG3} = V_{SG4} \end{cases} \Rightarrow V_{SD3} = V_{SD4} \Rightarrow V_Y = V_N$$

(c) if  $V_{DD}$  changes by a small amount  $\Delta V$ , both  $V_N$  and  $V_Y$  will change by  $\Delta V$ .

74

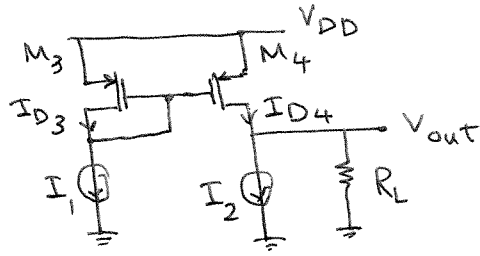


$$I_{D3} = I_{D4} = I_1$$

$$V_{out} = (I_{D4} - I_2) R_L = (I_1 - I_2) R_L$$

$$\begin{matrix} \text{small} \\ \Rightarrow \\ \text{signal} \end{matrix} \frac{V_{out}}{i_1} = R_L, \quad \frac{V_{out}}{i_2} = -R_L$$

(75)

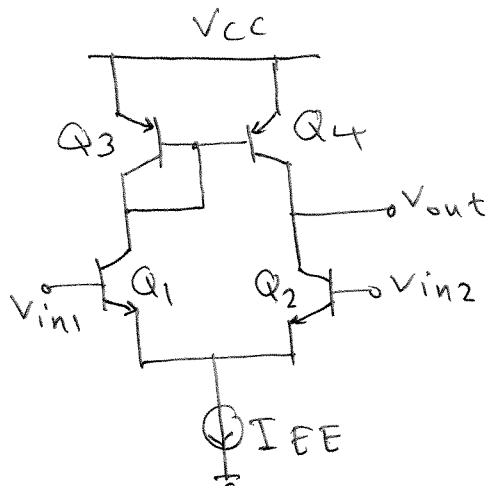

$$V_{A,n} = 5V$$


$$A_v = 100$$

$$\frac{v_{out}}{v_{in1} - v_{in2}} = g_{mN} (r_{oN} || r_{oP}) =$$


$$\frac{I_{EE}/2}{V_T} \left( \frac{V_{A,n}}{I_{EE}/2} || \frac{V_{A,p}}{I_{EE}/2} \right) = \frac{V_{A,n} V_{A,p}}{(V_{A,n} + V_{A,p}) V_T}$$

$$\Rightarrow 100 = \frac{5 V_{A,p}}{(5 + V_{A,p}) 0.026} \Rightarrow V_{A,p} = 5.417V$$

(76)

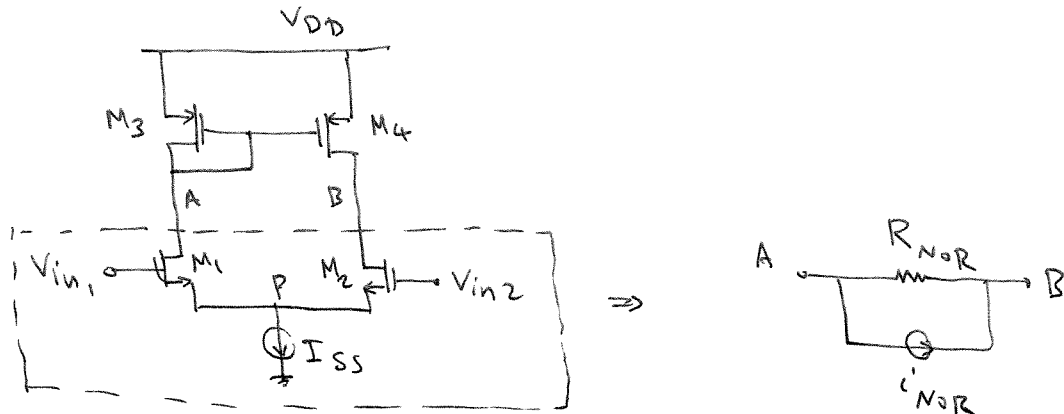

To calculate  $i_{NOR}$  we have:

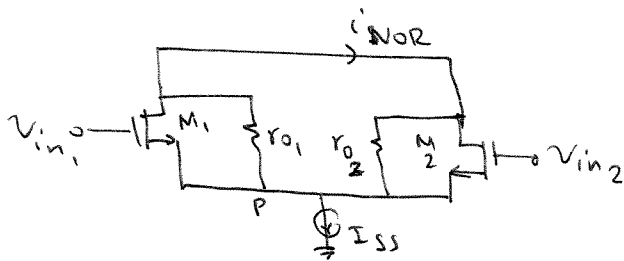


$$r_{o1} (i_{NOR} + g_{m1} v_{in1}) + r_{o2} (i_{NOR} - g_{m2} v_{in2}) = 0$$

$$\rightarrow 2 r_{oN} i_{NOR} = -g_{m1} r_{o1} v_{in1} + g_{m2} r_{o2} v_{in2} \Rightarrow$$

$$i_{NOR} = -\frac{g_{mN}}{2} (v_{in1} - v_{in2})$$

To calculate  $R_{NOR}$ :

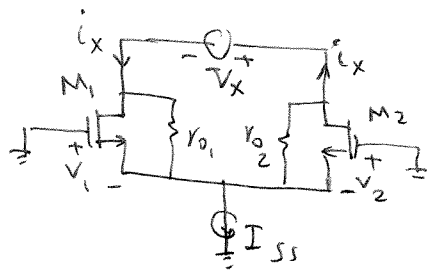


$$v_1 = v_2$$

$$(i_x - g_{m1} v_1) r_{o1} + (i_x + g_{m2} v_2) r_{o2} = v_x$$

$$\Rightarrow R_{NOR} = \frac{v_x}{i_x} = 2 r_{oN}$$

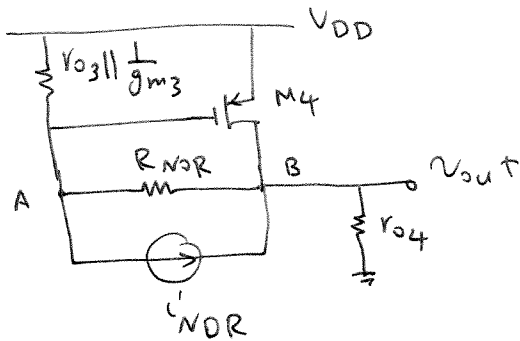Therefore, utilizing the Norton model we have:



$$\begin{cases} \frac{V_A - V_B}{R_{NOR}} + \frac{V_A}{r_{o3} \parallel \frac{1}{g_{m3}}} + i_{NOR} = 0 \Rightarrow V_A = \frac{\frac{V_B}{R_{NOR}} - i_{NOR}}{\frac{1}{R_{NOR}} + \frac{1}{r_{o3} \parallel \frac{1}{g_{m3}}}} \\ \frac{V_B - V_A}{R_{NOR}} + \frac{V_B}{r_{o4}} - i_{NOR} + g_{m4} V_A = 0, V_B = v_{out} \end{cases}$$

$$\Rightarrow v_{out} \left( \frac{1}{R_{NOR}} + \frac{1}{r_{o4}} \right) + \left( g_{m4} - \frac{1}{R_{NOR}} \right) \frac{\frac{v_{out}}{R_{NOR}} - i_{NOR}}{\frac{1}{R_{NOR}} + \frac{1}{r_{o3} \parallel \frac{1}{g_{m3}}}} = i_{NOR}$$

$\frac{1}{g_{m3}} \ll r_{o3}, \frac{1}{g_{m3}} \ll R_{NOR}, g_{m3} = g_{m4} = g_m, r_{o3} = r_{o4} = r_{op}$


$$\Rightarrow v_{out} \left( \frac{1}{R_{NOR}} + \frac{1}{r_{op}} \right) + g_{m4} \frac{\frac{v_{out}}{R_{NOR}} - i_{NOR}}{g_{m3}} = i_{NOR}$$

$$\Rightarrow v_{out} \left( \frac{1}{R_{NOR}} + \frac{1}{r_{op}} \right) + \frac{v_{out}}{R_{NOR}} = 2 i_{NOR} \Rightarrow$$

$$\frac{2 v_{out}}{R_{NOR}} + \frac{v_{out}}{r_{op}} = 2 i_{NOR} \Rightarrow v_{out} \left( \frac{1}{r_{on}} + \frac{1}{r_{op}} \right) = -g_{mN} (v_{in1} - v_{in2})$$

$$\Rightarrow \frac{v_{out}}{v_{in1} - v_{in2}} = -g_{mN} (r_{on} \parallel r_{op})$$


77

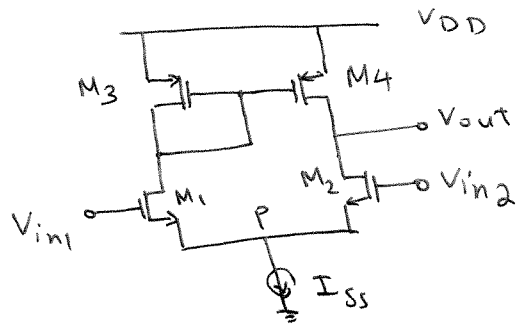

$$g_m r_o \gg 1$$


$$g_{m1} = g_{m2}$$

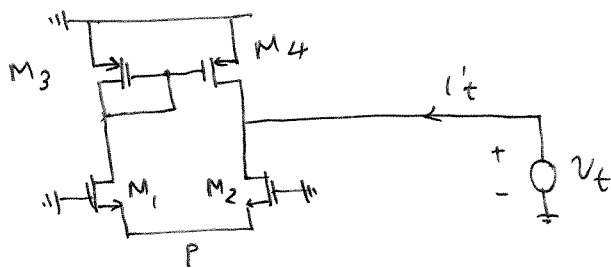To calculate the output impedance we have the following circuit:



$$R_{out} = \frac{v_t}{i_t}$$

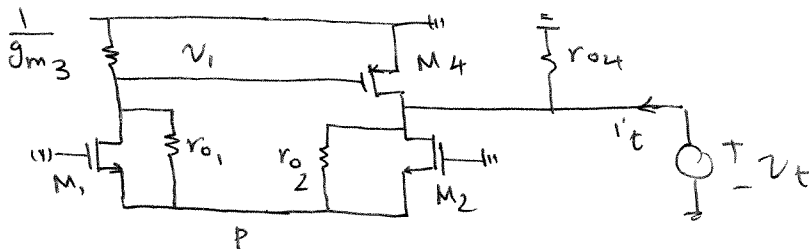↓ neglecting  $r_{o3}$  ( $r_{o3} \gg \frac{1}{g_{m3}}$ )




writing node equations of  $v_i$  and  $v_p$ :

$$\begin{cases} g_{m3} v_i + \frac{v_i - v_p}{r_{o1}} - g_{m1} v_p = 0 \\ 2g_{m1} v_p + \frac{v_p - v_i}{r_{o1}} + \frac{v_p - v_t}{r_{o2}} = 0 \end{cases} \xrightarrow{g_m r_o \gg 1} \begin{cases} g_{m3} v_i \approx g_{m1} v_p \\ 2g_{m1} v_p \approx 0 \end{cases}$$

$$\Rightarrow v_p \approx v_i = 0 \Rightarrow R_{out} = \frac{v_t}{i_t} = r_{o4} \parallel r_{o2} = r_{oN} \parallel r_{oP}$$

78


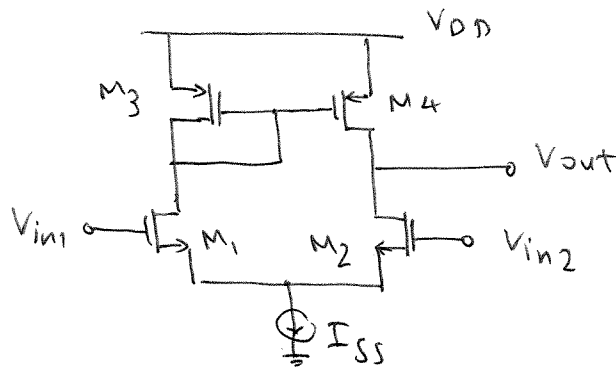


$$g_m r_o \gg 1$$

$$g_{m1} = g_{m2}$$

$$g_{m3} = g_{m4}$$

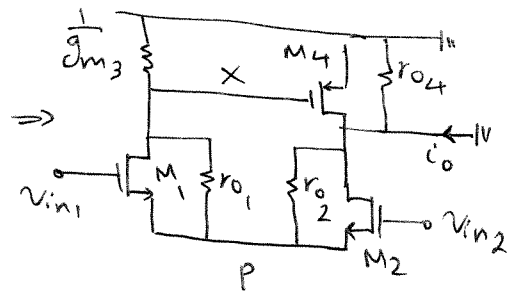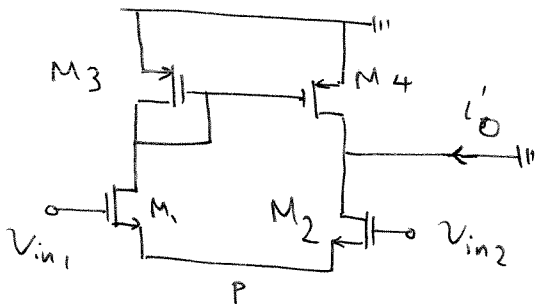To calculate  $G_m$  we have from small signal model:



writing node equations of nodes P and X we have:

$$\begin{cases} g_{m1}(v_p - v_{in1}) + g_{m2}(v_p - v_{in2}) + \frac{v_p - v_x}{r_{o1}} + \frac{v_p}{r_{o2}} = 0 \\ g_{m3} v_x + g_{m1}(v_{in1} - v_p) + \frac{v_x - v_p}{r_{o1}} = 0 \end{cases}$$

Since  $g_m r_o \gg 1$  we have

$$\begin{cases} g_{m1}(v_p - v_{in1}) + g_{m2}(v_p - v_{in2}) = 0 \Rightarrow v_p = \frac{v_{in1} + v_{in2}}{2} \\ v_x = -\frac{g_{m1}}{g_{m3}}(v_{in1} - v_p) = -\frac{g_{m1}}{g_{m3}}\left(\frac{v_{in1} - v_{in2}}{2}\right) \end{cases}$$

$$i_o = -\frac{v_p}{r_{o2}} + g_{m2}(v_{in2} - v_p) - g_{m4}(-v_x)$$

$$\Rightarrow i_o \approx -g_{m4}(-v_x) + g_{m2} \left( v_{in2} - \frac{v_{in1} + v_{in2}}{2} \right)$$

$$= - \left[ g_{m4} \frac{g_{m1}}{g_{m3}} \left( \frac{v_{in1} - v_{in2}}{2} \right) + g_{m2} \left( \frac{v_{in1} - v_{in2}}{2} \right) \right]$$


$$= -g_{m1} (v_{in1} - v_{in2})$$

$$G_m = \frac{i_o}{v_{in1} - v_{in2}} = -g_{m1} = -g_{mN}$$

$$\rightarrow A_v = -G_m R_{out} = g_{mN} (r_{oN} \parallel r_{op})$$



79

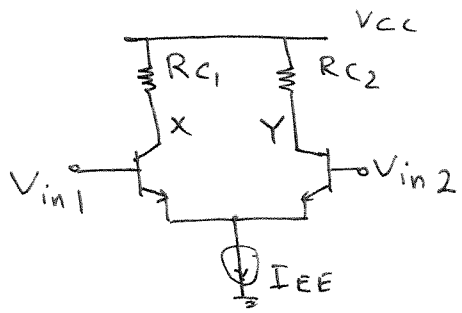


$$\begin{aligned}A_v &= 10, \\ P &= 2 \text{ mW} \\ V_{CC} &= 2.5 \text{ V} \\ V_A &= \infty\end{aligned}$$

$$P = V_{CC} I_{EE} \Rightarrow 2 \times 10^{-3} = 2.5 I_{EE} \Rightarrow I_{EE} = 0.8 \text{ mA}$$

$$A_v = \frac{v_{XY}}{v_{in1} - v_{in2}} = -g_m R_C = -\frac{I_{EE}/2}{V_T} R_C$$

$$\Rightarrow 10 = \frac{0.4 \times 10^{-3}}{0.026} R_C \Rightarrow R_C = 650 \Omega$$

(80)

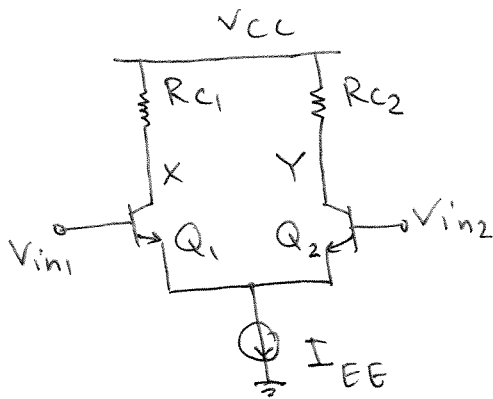

$$V_{in, CM} = 1.2 \text{ V}$$

$$P = 3 \text{ mW}$$

$$V_{CC} = 2.5 \text{ V}$$

$$P = I_{EE} V_{CC} \Rightarrow 3 \times 10^{-3} = 2.5 I_{EE} \Rightarrow I_{EE} = 1.2 \text{ mA}$$

$$A_v = -g_m R_C = -\frac{I_{EE}/2}{V_T} R_C = -\frac{R_C I_{EE}}{2 V_T}$$


To maximize gain,  $R_C I_{EE}$  and therefore  $R_C$  should be maximum. However, the upper bound of  $R_C$  value is limited by the voltage value of  $X$ . because:

$$V_{in, CM} \leq V_X \Rightarrow 1.2 \leq V_{CC} - R_C I_{EE}/2 \Rightarrow$$

$$R_C \leq 2 \frac{V_{CC} - 1.2}{I_{EE}} \Rightarrow R_C \leq 2 \frac{2.5 - 1.2}{1.2 \times 10^{-3}} \Rightarrow$$

$$R_C \leq 2.167 \text{ k}\Omega \Rightarrow R_C = 2.167 \text{ k}\Omega$$

81

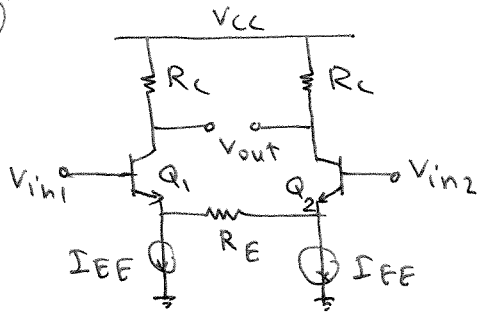


$$A_v = 5$$

$$P = 4 \text{ mW}$$

$$V_{CC} = 2.5 \text{ V}$$

$$V_A = \infty$$

The half circuit is:

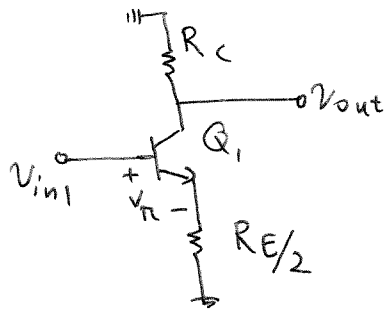

$$A_v = \frac{v_{out}}{v_{in1}} \approx \frac{-g_m v_{\pi} R_c}{v_{in1}} = -\frac{g_m R_c}{\frac{1}{g_m} + \frac{R_E}{2}}$$

$$= -\frac{R_c}{\frac{R_E}{2} + \frac{1}{g_m}}$$

$$P = 4 \text{ mW} = 2 I_{EE} V_{CC} = 5 I_{EE} \Rightarrow I_{EE} = 0.8 \text{ mA}$$

$$g_m = \frac{I_{EE}}{V_T} = 0.03077$$

$$A_v = 5 \Rightarrow \frac{R_c}{\frac{R_E}{2} + 32.5} = 5 \quad (1)$$

if  $I_{EE}$  increases by 10%, the gain will be:

$$A_v = \frac{R_c}{\frac{R_E}{2} + \frac{32.5}{1.1}} \Rightarrow 5 < \frac{R_c}{\frac{R_E}{2} + \frac{32.5}{1.1}} < 5 \times 1.02 \quad (2)$$

if  $I_{EE}$  decreases by 10% then:

$$5 \times 0.98 < \frac{R_c}{\frac{R_E}{2} + \frac{32.5}{0.9}} < 5 \quad (3)$$

The worse case is:

$$\left\{ \begin{array}{l} \frac{R_C}{\frac{R_E}{2} + \frac{32.5}{1.1}} = 5 \times 1.02 \quad (4) \\ \frac{R_C}{\frac{R_E}{2} + \frac{32.5}{0.9}} = 5 \times 0.98 \quad (5) \end{array} \right.$$


dividing (4) and (5) to (1) leads to:

$$\left\{ \begin{array}{l} \frac{\frac{R_E}{2} + 32.5}{\frac{R_E}{2} + \frac{32.5}{1.1}} = 1.02 \Rightarrow R_E = 236.36 \Omega \\ \frac{\frac{R_E}{2} + 32.5}{\frac{R_E}{2} + \frac{32.5}{0.9}} = 0.98 \Rightarrow R_E = 288.89 \Omega \end{array} \right.$$

To ensure less than 2% gain variation for 10% current variation  $R_E = 288.89 \Omega$

$$\text{From (1)} \quad R_C = 5 \left( \frac{R_E}{2} + 32.5 \right) = 884.72 \Omega$$

(82)

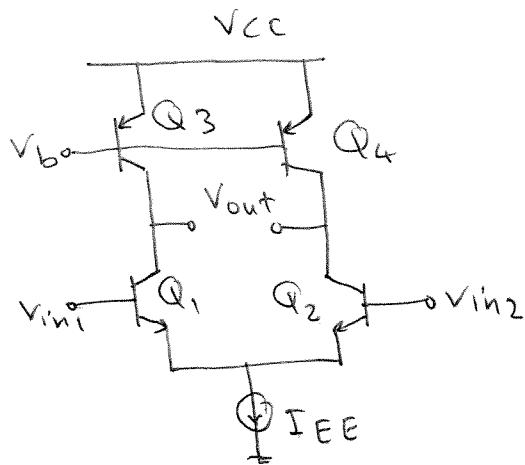

$$A_v = 100$$

$$P = 1 \text{ mW}$$

$$V_{A, n} = 6$$

$$V_{CC} = 2.5 \text{ V}$$

$$P = 1 \text{ mW} = I_{EE} V_{CC} \Rightarrow I_{EE} = \frac{10^{-3}}{2.5} = 0.4 \text{ mA}$$


$$r_{oN} = \frac{V_{A, n}}{I_{EE}/2} = \frac{6}{0.2 \times 10^{-3}} = 30 \text{ k}\Omega, \quad g_{mN} = \frac{I_{EE}/2}{V_T} = \frac{0.2}{26} \text{ S}$$

$$A_v = -g_{mN} (r_{oN} \parallel r_{op}) \Rightarrow$$

$$100 = \frac{0.2}{26} (30 \times 10^3 \parallel r_{op}) \Rightarrow r_{op} = 22.94 \text{ k}\Omega$$


$$\Rightarrow V_{A, P} = r_{op} \frac{I_{EE}}{2} = 4.588 \text{ V}$$

83

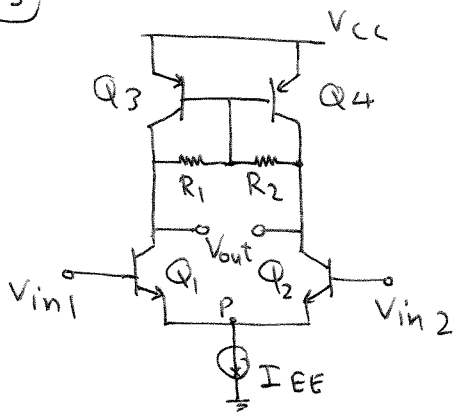

$$\begin{aligned}
 A_v &= 50 \\
 P &= 1 \text{ mW} \\
 V_{A,n} &= 10 \text{ V} \\
 V_{A,p} &= 5 \text{ V} \\
 V_{CC} &= 2.5 \text{ V} \\
 R_1 &= R_2
 \end{aligned}$$

The half circuit is:

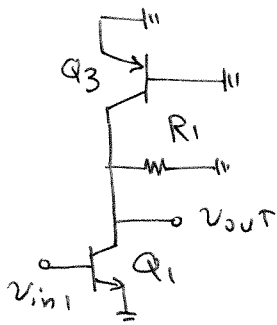

$$A_v = -g_{m_1} (R_1 \parallel r_{o_1} \parallel r_{o_3})$$

$$g_{m_1} = \frac{I_{EE}}{2V_T} \quad r_{o_1} = \frac{2V_{A,n}}{I_{EE}} \quad r_{o_3} = \frac{2V_{A,p}}{I_{EE}}$$

$$\Rightarrow 50 = \frac{1}{2V_T} \left( (R_1 I_{EE}) \parallel \underbrace{(2V_{A,n})}_{20} \parallel \underbrace{(2V_{A,p})}_{10} \right) \Rightarrow$$


$$R_1 I_{EE} = 4.262$$

$$P = 1 \text{ mW} = I_{EE} V_{CC} \Rightarrow I_{EE} = \frac{10^{-3}}{2.5} = 0.4 \text{ mA}$$

$$\rightarrow R_1 = \frac{4.262}{I_{EE}} = 10.655 \text{ k}\Omega$$

Notice that larger value of  $R_1$ , requires smaller  $I_{EE}$  and saves power.

84

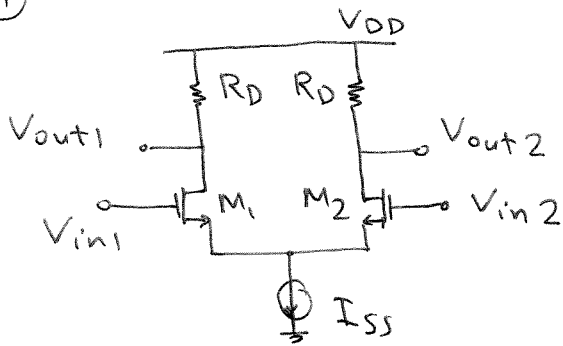

$$\Delta V_{in, \max} = 0.3 \text{ V}$$

$$P = 3 \text{ mW}$$

$$R_D = 500 \Omega$$

$$\lambda = 0, \mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$$

$$V_{DD} = 1.8 \text{ V}$$


$$P = V_{DD} I_{SS} \Rightarrow 3 \times 10^{-3} = 1.8 I_{SS} \Rightarrow$$

$$I_{SS} = 1.67 \text{ mA}$$

$$\Delta V_{in, \max} = \sqrt{\frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \Rightarrow$$

$$0.3 = \sqrt{\frac{2 \times 1.67 \times 10^{-3}}{10^{-4} \times \frac{W}{L}}} \Rightarrow \frac{W}{L} = 370.37$$

(85)

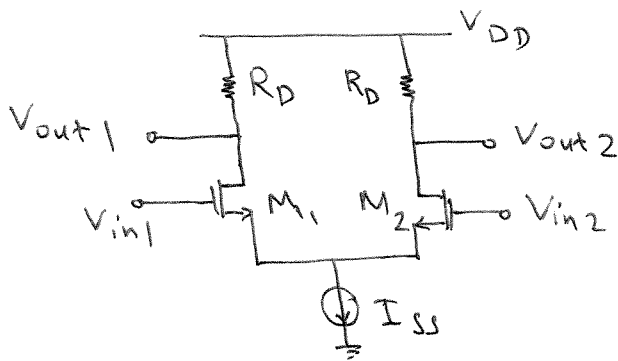

$$\begin{aligned} P &= 2 \text{ mW} \\ \text{overdrive} &= 100 \text{ mV} \\ V_{CM} &= 1 \text{ V} \\ \lambda &= 0, \mu_n C_{ox} = 100 \mu\text{A/V}^2 \\ V_{DD} &= 1.8 \text{ V} \\ V_{TH,n} &= 0.5 \end{aligned}$$

$$P = I_{SS} V_{DD} \Rightarrow 2 \times 10^{-3} = 1.8 I_{SS} \Rightarrow I_{SS} = 1.11 \text{ mA}$$

$$V_{GS1} - V_{TH} = \sqrt{\frac{2 I_{D1}}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \Rightarrow$$

$$0.1^2 = \frac{1.11 \times 10^{-3}}{10^{-4} \times \frac{W}{L}} \Rightarrow \frac{W}{L} = 1111.11$$

$$g_m = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} = \sqrt{10^4 \times 1111.11 \times 1.11 \times 10^{-3}} = 0.011$$

To place the transistor at the edge of triode region:

$$V_{in,CM} = V_{out1} + V_{TH,n}$$


$$1 = V_{DD} - R_D \frac{I_{SS}}{2} + 0.5 \Rightarrow$$

$$1 = 1.8 - R_D \frac{1.11 \times 10^{-3}}{2} + 0.5 \Rightarrow R_D = 2.34 \text{ k}\Omega$$

$$A_V = -g_m R_D = -25.74$$



86

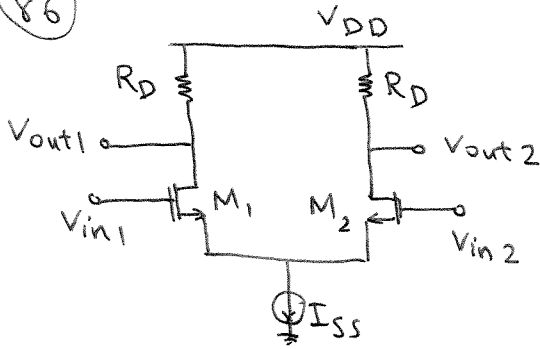

$$A_v = 5$$

$$P = 1 \text{ mW}$$

$$(V_{GS} - V_{TH})_{\text{equil}} = 150 \text{ mV}$$

$$\lambda = 0, \mu_n C_{ox} = 100 \mu\text{A/V}^2$$

$$V_{DD} = 1.8 \text{ V}$$

$$P = 1 \text{ mW} = V_{DD} I_{SS} = 1.8 I_{SS} \Rightarrow I_{SS} = 0.556 \text{ mA}$$

$$g_{m1} = \frac{2 I_{D1}}{(V_{GS} - V_{TH})_{\text{equil}}} = \frac{I_{SS}}{(V_{GS} - V_{TH})_{\text{equil}}} = \frac{0.556 \times 10^{-3}}{0.15}$$


$$= 3.704 \text{ mS}$$

$$A_v = -g_{m1} R_D \Rightarrow 5 = 3.704 \times 10^{-3} \times R_D \Rightarrow R_D = 1.35 \text{ k}\Omega$$

$$(V_{GS} - V_{TH})_{\text{equil}} = \sqrt{\frac{2 I_{D1}}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \Rightarrow$$

$$0.15 = \sqrt{\frac{0.556 \times 10^{-3}}{10^{-4} \times \frac{W}{L}}} \Rightarrow \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 246.91$$

(87)

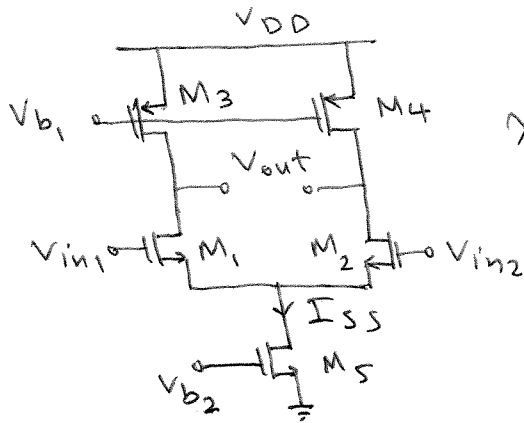

$$A_V = 40$$

$$(V_{GS} - V_{TH})_{\text{equil}} = ?$$

$$\lambda_n = 0.1 \text{ V}^{-1} \quad \lambda_p = 0.2 \text{ V}^{-1}$$

$$\mu_n C_{ox} = 100 \text{ MA/V}^2$$

$$\mu_p C_{ox} = 50 \text{ MA/V}^2$$

$$V_{DD} = 1.8$$

$$P = 2 \text{ mW}$$

$$A_V = -g_{m_N} (r_{op} \parallel r_{oN}) = -\frac{I_{SS}}{(V_{GS1} - V_{TH})_{\text{equil}}} \left( \frac{1}{\frac{I_{SS} \lambda_n}{2}} \parallel \frac{1}{\frac{I_{SS} \lambda_p}{2}} \right)$$

$$= -\frac{2}{(V_{GS1} - V_{TH})_{\text{equil}}} \left( \frac{1}{\lambda_n} \parallel \frac{1}{\lambda_p} \right) \Rightarrow$$

$$\frac{2}{(V_{GS1} - V_{TH})_{\text{equil}}} (10 \parallel 5) = 40 \Rightarrow (V_{GS1} - V_{TH})_{\text{equil}} = 166.67 \text{ mV}$$


$$P = 2 \times 10^{-3} = V_{DD} I_{SS} \Rightarrow I_{SS} = \frac{2 \times 10^{-3}}{1.8} = 1.11 \text{ mA}$$

$$\left( \frac{W}{L} \right)_{1,2} = \frac{I_{SS}}{\mu_n C_{ox} (V_{GS1} - V_{TH})_{\text{equil}}^2} = \frac{1.11 \times 10^{-3}}{10^{-4} \times (0.16667)^2} = 400$$

$$\left( \frac{W}{L} \right)_{3,4} = \frac{I_{SS}}{\mu_p C_{ox} (V_{GS1} - V_{TH})_{\text{equil}}^2} = \frac{1.11 \times 10^{-3}}{0.5 \times 10^{-4} \times (0.16667)^2} = 800$$

$$\left( \frac{W}{L} \right)_5 = \frac{2 I_{SS}}{\mu_n C_{ox} (V_{GS1} - V_{TH})_{\text{equil}}^2} = \frac{2 \times 1.11 \times 10^{-3}}{10^{-4} \times (0.16667)^2} = 800$$

(88)

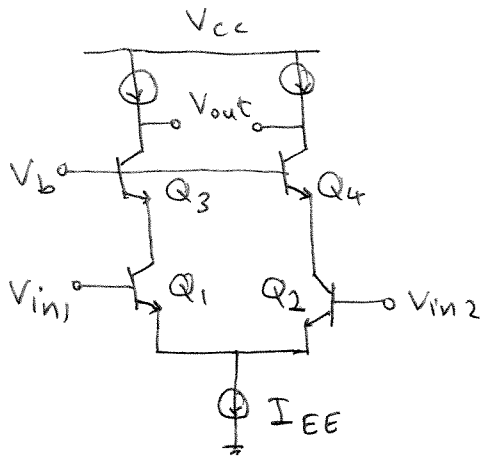

$$A_v = 4000$$

$$\beta = 100$$

$$V_{CC} = 2.5 \text{ V}$$

$$P = 1 \text{ mW}$$

$$P = I_{EE} V_{CC} = 10^{-3} \Rightarrow I_{EE} = \frac{10^{-3}}{2.5} = 0.4 \text{ mA}$$

$$g_{m_{1-4}} = \frac{I_{EE}}{2V_T} = \frac{0.2}{26} = 7.692 \text{ mS}$$

$$r_{\pi_{1-4}} = \frac{\beta}{g_{m_i}} = 13 \text{ k}\Omega$$


$$r_{o_{1-4}} = \frac{V_A}{\frac{I_{EE}}{2}} = 5 \times 10^3 \text{ V}_A$$

$$A_v = -g_{m_1} [g_{m_3} (r_{o_1} \parallel r_{\pi_3}) r_{o_3} + (r_{o_1} \parallel r_{\pi_3}) + r_{o_3}] \Rightarrow$$

$$4000 = \frac{0.2}{26} \left[ \frac{0.2}{26} (5 \times 10^3 \text{ V}_A \parallel 13 \times 10^3) 5 \times 10^3 \text{ V}_A + (5 \times 10^3 \text{ V}_A) \parallel 13 \times 10^3 + 5 \times 10^3 \text{ V}_A \right]$$

$$\Rightarrow V_A = 2.197$$

(89)

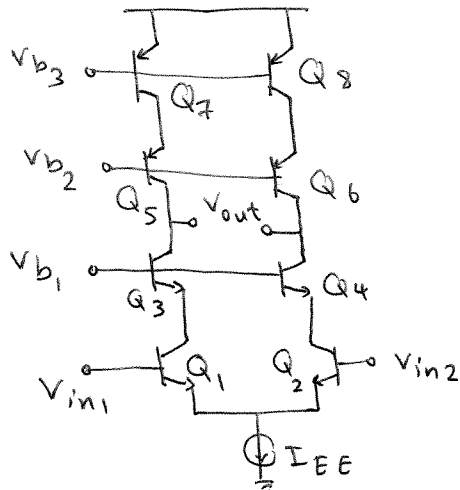

$$A_v = 2000$$

$$\beta_n = 100$$

$$\beta_p = 50$$

$$V_{A,n} = 5V$$

$$V_{CC} = 2.5V$$

$$P = 2mW$$

$$P = I_{EE} V_{CC} = 2 \times 10^{-3} \Rightarrow I_{EE} = \frac{2 \times 10^{-3}}{2.5} = 0.8mA$$

$$g_{m_{1-8}} = \frac{I_{EE}}{2V_T} = \frac{0.4}{26} = 0.0154 \Rightarrow$$

$$r_{\pi_{1-4}} = \frac{\beta_n}{g_{m_1}} = 6.5k\Omega \quad r_{\pi_{5-8}} = \frac{\beta_p}{g_{m_5}} = 3.25k\Omega$$


$$r_{o_{1-4}} = \frac{V_{A,n}}{I_{EE}/2} = 12.5k\Omega \quad r_{o_{5-8}} = \frac{V_{A,p}}{I_{EE}/2}$$

$$A_v \approx -g_{m_1} \left[ g_{m_3} r_{o_3} (r_{o_1} \parallel r_{\pi_3}) \right] \parallel \left[ g_{m_5} r_{o_5} (r_{o_7} \parallel r_{\pi_5}) \right]$$

$$\Rightarrow \frac{0.4}{26} \left[ \frac{0.4}{26} \times 12.5 \times 10^3 (12.5 \times 10^3 \parallel 6.5 \times 10^3) \right] \parallel \left[ \frac{0.4}{26} \frac{V_{A,p}}{I_{EE}/2} \left( \frac{V_{A,p}}{I_{EE}/2} \parallel 3250 \right) \right] = 2000$$

$$\Rightarrow V_{A,p} = 2.027V$$

(90)

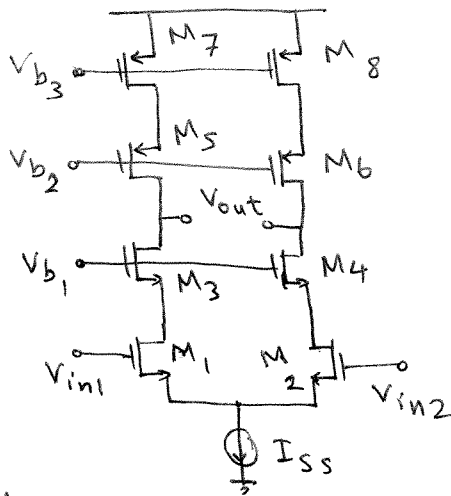

$$A_v = 600$$

$$P = 4 \text{ mW}$$

$$(V_{GS} - V_{TH})_{NMOS} = 100 \text{ mV}$$

$$(V_{GS} - V_{TH})_{PMOS} = 150 \text{ mV}$$

$$\mu_n C_{ox} = 100 \text{ } \mu\text{A/V}^2$$

$$\mu_p C_{ox} = 50 \text{ } \mu\text{A/V}^2$$

$$\lambda_n = 0.1 \text{ V}^{-1}$$

$$A_v \approx -g_{m1} [(g_{m3} r_{o3} r_{o1}) \parallel (g_{m5} r_{o5} r_{o7})] = -600$$

$$P = 4 \text{ mW} = I_{SS} V_{DD} \Rightarrow I_{SS} = \frac{4 \times 10^{-3}}{1.8} = 2.22 \text{ mA}$$

$$g_{m_{1-4}} = \frac{2I_{D1}}{(V_{GS} - V_{TH})_{NMOS}} = \frac{I_{SS}}{(V_{GS} - V_{TH})_{NMOS}} = \frac{2.22 \times 10^{-3}}{0.1} = 22.22 \text{ mS}$$

$$g_{m_{5-8}} = \frac{2I_{D5}}{(V_{GS} - V_{TH})_{PMOS}} = \frac{I_{SS}}{(V_{GS} - V_{TH})_{PMOS}} = \frac{2.22 \times 10^{-3}}{0.15} = 14.815 \text{ mS}$$

$$r_{o_{1-4}} = \frac{1}{\lambda_n \frac{I_{SS}}{2}} = \frac{1}{0.1 \times \frac{2.22}{2} \times 10^{-3}} = 9 \text{ k}\Omega$$

$$r_{o_{5-8}} = \frac{1}{\lambda_p \frac{I_{SS}}{2}} = \frac{1}{\lambda_p \times \frac{2.22 \times 10^{-3}}{2}} = \frac{0.9 \times 10^3}{\lambda_p}$$

in  $A_v$   
 $\Rightarrow$  equation


$$22.22 \times 10^{-3} \left[ (22.22 \times 10^{-3} \times 81 \times 10^6) \parallel (14.815 \times 10^{-3} \times \frac{0.81 \times 10^6}{\lambda_p^2}) \right] = 600 \Rightarrow$$

$$\lambda_p = 0.66 \text{ V}^{-1}$$

$$\left(\frac{W}{L}\right)_{NMOS} = I_{SS} / (\mu_n C_{ox} (V_{GS} - V_{TH})_{NMOS}^2) = 2222.2$$

$$\left(\frac{W}{L}\right)_{PMOS} = I_{SS} / (\mu_p C_{ox} (V_{GS} - V_{TH})_{PMOS}^2) = 1975.31$$

(91)

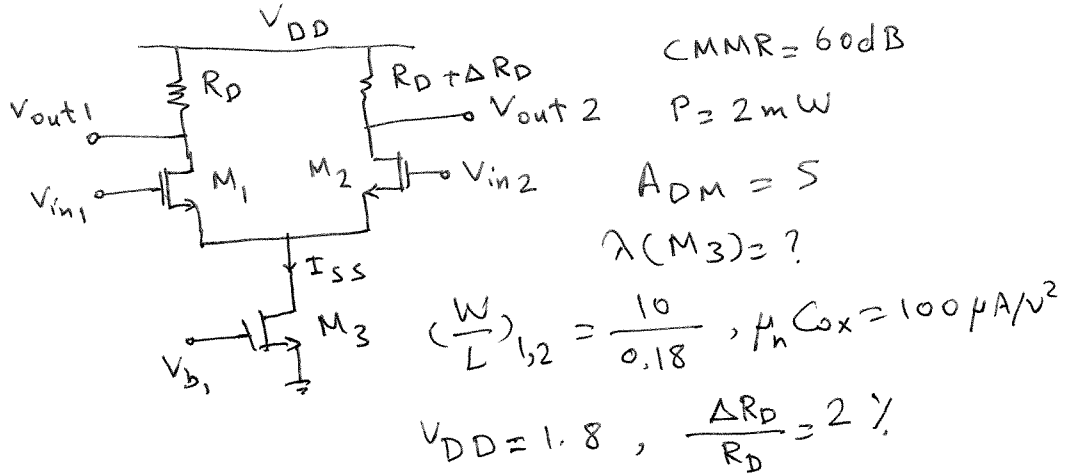


$$P = 2 \text{ mW} = I_{SS} V_{DD} \Rightarrow I_{SS} = \frac{2 \times 10^{-3}}{1.8} = 1.11 \text{ mA}$$

$$A_{DM} = -g_{m1} R_D$$

$$g_{m1} = \sqrt{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_{SS}} = \sqrt{10^{-4} \times \frac{10}{0.18} \times 1.11 \times 10^{-3}} = 2.4845 \text{ mS}$$

$$\Rightarrow R_D = \frac{|A_{DM}|}{g_{m1}} = \frac{5}{2.4845 \times 10^{-3}} = 2.012 \text{ k}\Omega$$

To calculate  $A_{CM,DM}$  we have:

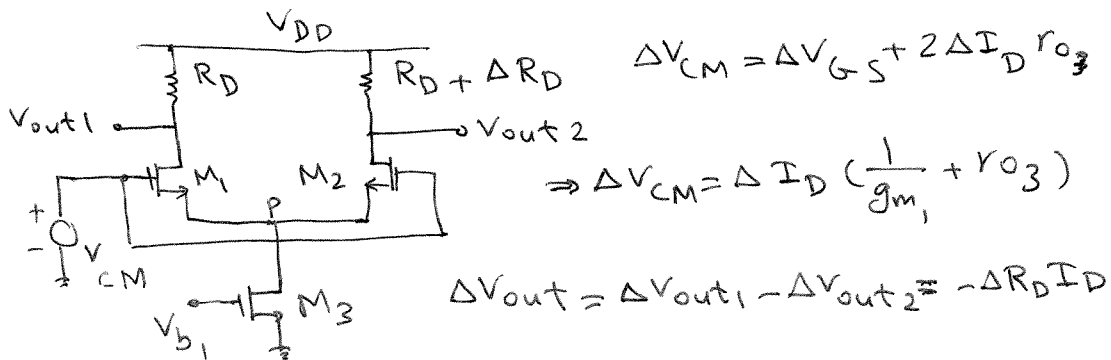


$$\Rightarrow A_{CM,DM} = \frac{\Delta V_{out}}{\Delta V_{CM}} = - \frac{\Delta R_D / 2}{\frac{1}{2g_{m1}} + r_{O3}}$$

$$\Rightarrow CMMR = \frac{A_{DM}}{A_{CM,DM}} = (1 + 2g_{m1} r_{O3}) \frac{R_D}{\Delta R_D}, \quad r_{O3} = \frac{1}{\lambda_3 I_{SS}}$$

$$\Rightarrow \text{CMRR} = 60\text{dB} = 10^3 = \left(1 + 2 \times 2.4845 \times 10^{-3} \frac{1}{\lambda_3 \times 1.11 \times 10^{-3}}\right) 50$$

$$\Rightarrow \lambda_3 = 0.2354$$

92

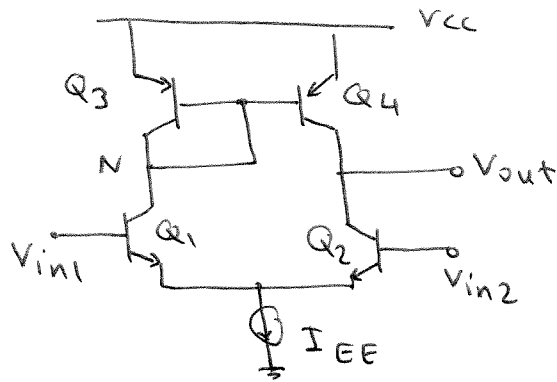

$$A_v = 200$$

$$P = 3 \text{ mW}$$

$$V_{cc} = 2.5 \text{ V}$$

$$V_{A,n} = 2 V_{A,p}$$

$$P = V_{cc} I_{EE} \Rightarrow I_{EE} = \frac{3 \times 10^{-3}}{2.5} = 1.2 \text{ mA}$$

$$g_{m_{1-4}} = \frac{I_{EE}}{2V_T} = \frac{0.6}{26} = 23.077 \text{ mS}$$

$$r_{o1} = r_{o2} = \frac{V_{A,n}}{\frac{I_{EE}}{2}} = \frac{V_{A,n}}{0.6 \times 10^{-3}}$$


$$r_{o3} = r_{o4} = \frac{V_{A,p}}{\frac{I_{EE}}{2}} = \frac{V_{A,n}}{1.2 \times 10^{-3}}$$

$$A_v = g_{m_i} (r_{o2} \parallel r_{o4}) \Rightarrow \frac{0.6}{26} \left( \frac{V_{A,n}}{0.6 \times 10^{-3}} \parallel \frac{V_{A,n}}{1.2 \times 10^{-3}} \right) = 200$$

$$\Rightarrow V_{A,n} = 15.6 \text{ V}$$



93

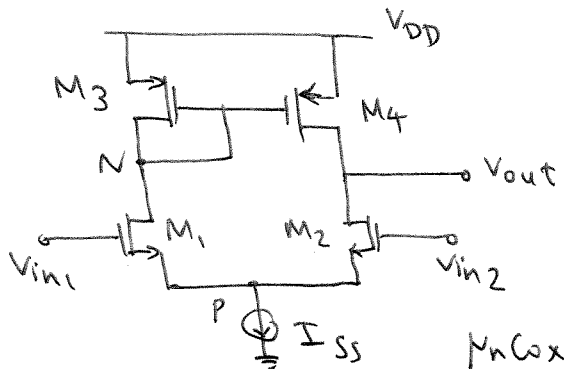

$A_V = 20$   
 $P = 1 \text{ mW}$   
 $V_{DD} = 1.8 \text{ V}$   
 $V_{in,cm} = 1 \text{ V}$

$\mu_n C_{ox} = 2 \mu_p C_{ox} = 100 \mu\text{A/V}^2$   
 $V_{TH,n} = 0.5 \text{ V}, V_{TH,p} = -0.4 \text{ V}$   
 $\lambda_n = \frac{\lambda_p}{2} = 0.1 \text{ V}^{-1}$

$$P = V_{DD} I_{SS} \Rightarrow I_{SS} = \frac{10^{-3}}{1.8} = 0.556 \text{ mA}$$

$$A_V = + g_{m_N} (r_{o_N} \parallel r_{o_P}) = 20$$

$$r_{o_N} = \frac{1}{\lambda_n \frac{I_{SS}}{2}} = \frac{1}{0.1 \frac{0.556 \times 10^{-3}}{2}} = 36 \text{ k}\Omega$$

$$r_{o_P} = \frac{1}{\lambda_p \frac{I_{SS}}{2}} = 18 \text{ k}\Omega$$

$$g_{m_N} (36 \text{ k} \parallel 18 \text{ k}) = 20 \Rightarrow g_{m_N} = 1.667 \text{ mS}$$

$$\Rightarrow g_{m_N} = \frac{2 I_{D_N}}{(V_{GS} - V_{TH})_{NMOS}} = \frac{I_{SS}}{(V_{GS} - V_{TH})_{NMOS}} \Rightarrow$$

$$(V_{GS} - V_{TH})_{NMOS} = 0.333 \text{ V}$$

$$(V_{GS} - V_{TH})_{NMOS} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_{NMOS}}} \Rightarrow \left(\frac{W}{L}\right)_{1/2} = 50$$


$$V_N = V_{in,CM} - V_{TH,n} = 1 - 0.5 = 0.5 \text{ V}$$

$$\rightarrow |V_{G_3}| - V_{TH,p} = 1.3 - 0.4 = 0.9 \text{ V}$$

$$\rightarrow 0.9 = \sqrt{\frac{I_{SS}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_{PMOS}}} \Rightarrow$$

$$\left(\frac{W}{L}\right)_{3,4} = 13.717$$

1)

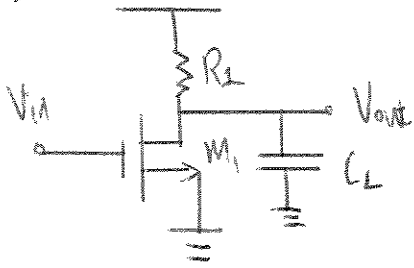

$$R_1 = 1 \text{ k}\Omega$$

$$C_L = 1 \text{ pF}$$


$$V_{out} = -g_{m_1} R_1 \parallel \frac{1}{C_L s} V_{in} \Rightarrow \frac{V_{out}}{V_{in}} = -g_m R_1 \parallel \frac{1}{C_L s}$$

$$\frac{V_{out}}{V_{in}} = -g_{m_1} \left( \frac{R_1}{R_1 C_L s + 1} \right), \quad s \rightarrow j\omega, \quad \frac{V_{out}}{V_{in}}(j\omega) = -g_{m_1} \left( \frac{R_1}{R_1 C_L j\omega + 1} \right)$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{g_m R_1}{\sqrt{1 + (\omega R_1 C_L)^2}}, \quad \text{Fall by } 10\% = \left| \frac{V_{out}}{V_{in}} \right| = g_m R_1 \cdot 0.9$$

$$\Rightarrow \frac{g_m R_1}{\sqrt{1 + (\omega R_1 C_L)^2}} = g_m R_1 \cdot 0.9 \Rightarrow \omega_{-10\%} = 4.84 \times 10^9 \text{ rad/s}$$
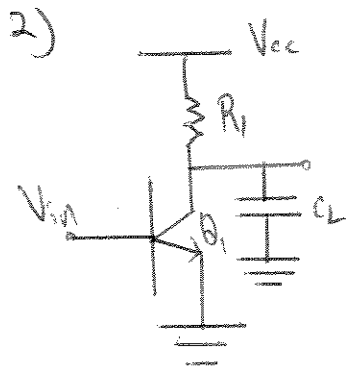
$$2\pi f = 4.84 \times 10^9 \Rightarrow f = 7.708 \times 10^8 \text{ Hz}$$



-3dB bandwidth = 1 GHz

$$C_L = 2 \text{ pF}$$

$$\text{Power} = 2 \text{ mW}$$

Low freq gain?

$$\text{Power} = 2.5 \text{ V } I_c, \quad I_c = 0.8 \text{ mA}$$


$$\text{Dominant Pole at the output} = \frac{1}{R_L C_L} = 2\pi (1 \text{ GHz})$$

$$R_L = 79.58 \text{ Ohm}$$

$$\text{Low Freq gain: } -g_m R_L = \frac{-I_c R_L}{V_T} = \frac{(79.58)(0.8)}{26}$$


$$A_v \Big|_{\text{low freq}} = -2.45$$

3)

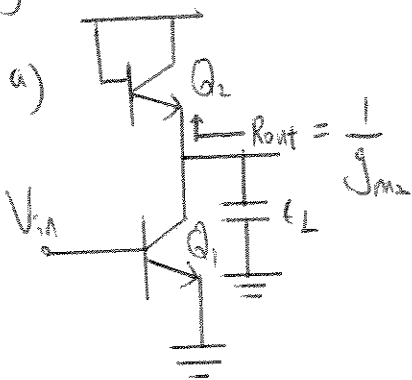


Assume  $\beta \gg 1$

$$-3dB = \frac{g_{m2}}{C_L}$$

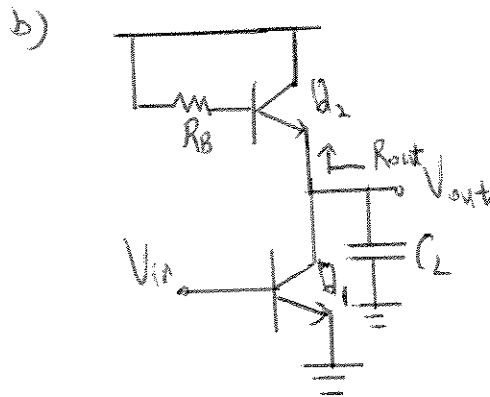


$$R_{out} = \frac{1}{g_{m2}} + \frac{R_B}{\beta + 1}$$
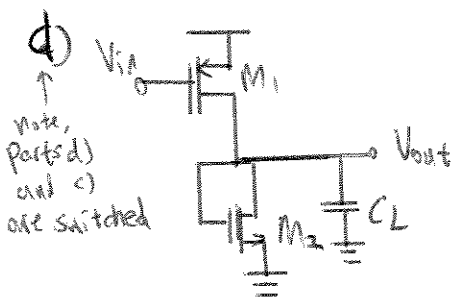
$$-3dB = \frac{(\beta + 1) g_{m2}}{C_L [\beta + R_B g_{m2}]}$$



$$R_{out} = \frac{1}{g_{m2} \parallel Y_{o2} \parallel Y_{o1}} \approx \frac{1}{g_{m2}}$$


$$-3dB = \frac{g_{m2}}{C_L}$$

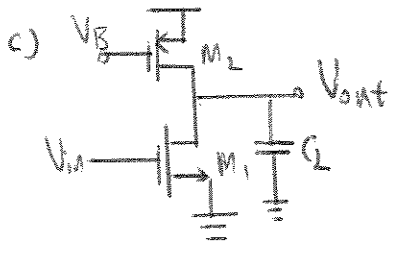


$$R_{out} = Y_{o1} \parallel Y_{o2}$$

$$-3dB = \frac{1}{(Y_{o1} \parallel Y_{o2}) C_L}$$


4)

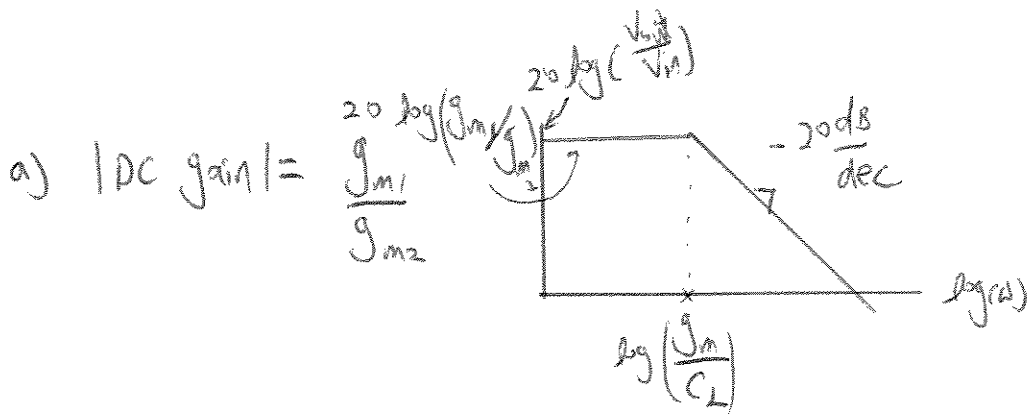


b)  $|DC \text{ gain}| = g_{m1} \left( \frac{1}{g_{m2}} + \frac{R_B}{\beta + 1} \right)$

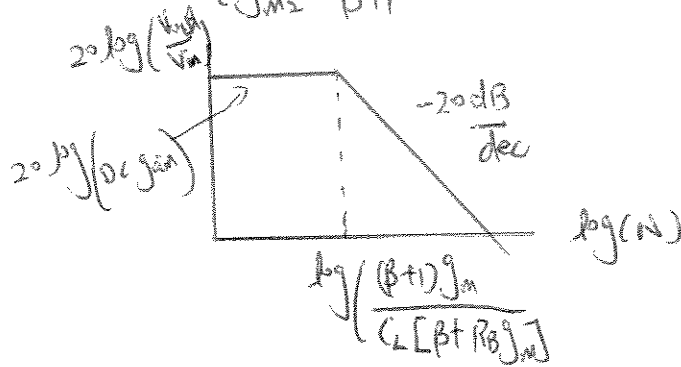


c)  $|DC \text{ gain}| = g_m (v_{o1}/v_{o2})$

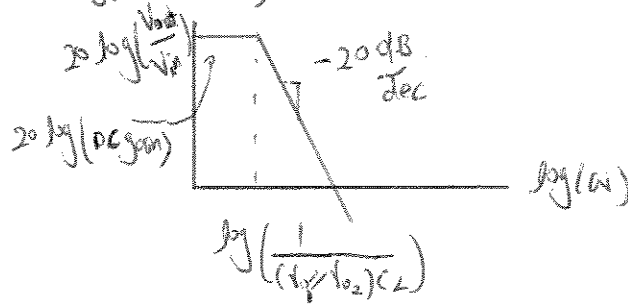

d)  $|DC \text{ gain}| = g_{m1}/g_{m2}$

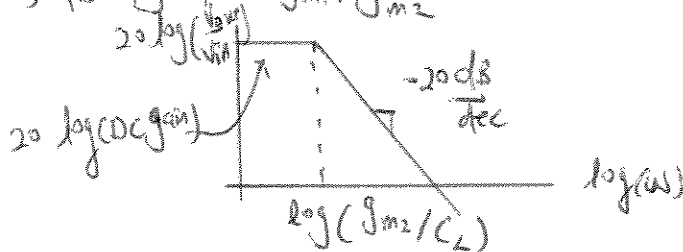

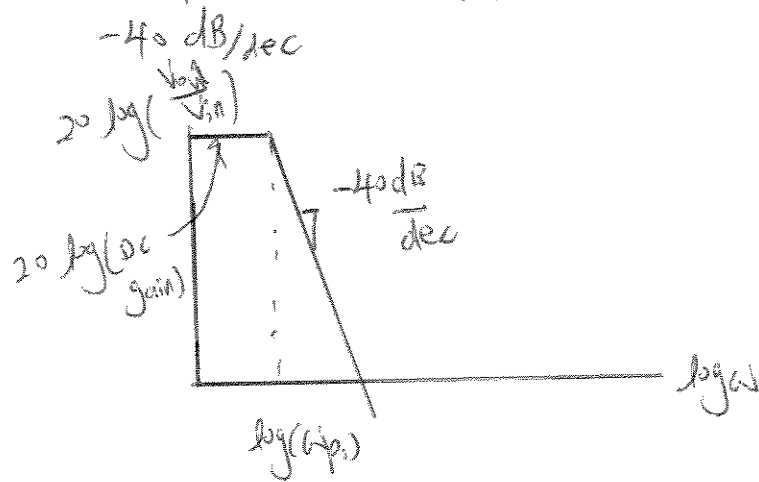
5) 2 poles at  $\omega_p$ , means slope is



\* Assuming transfer function is in the form  
of

$$\frac{A}{\left(\sqrt{\left(\frac{\omega}{\omega_p}\right)^2 + 1}\right)^2}$$

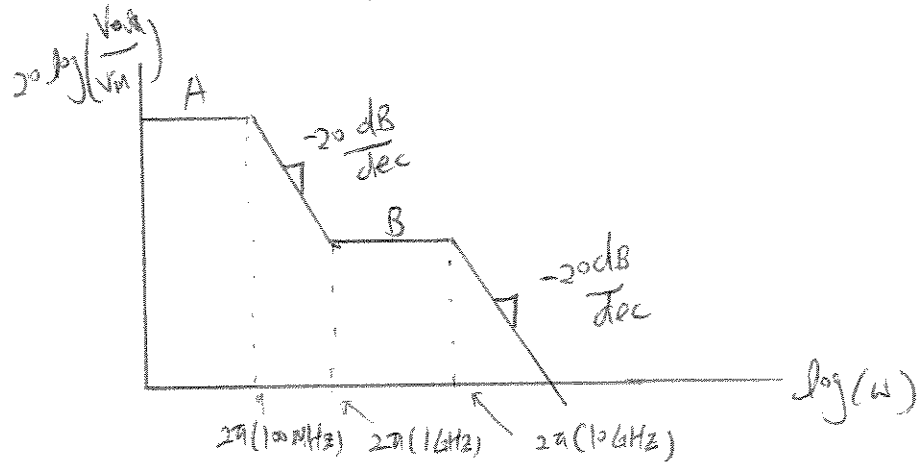6) Poles at 100 MHz, 10 GHz  
Zero at 1 GHz.




$$A(100MHz) = B(1GHz)$$

$$B = 0.1A$$




7) Ideal Integrator:  $\frac{V_{out}(s)}{V_{in}} = \frac{1}{s}$

$$\left| \frac{V_{out}(\omega)}{V_{in}} \right| = \frac{1}{\omega}$$

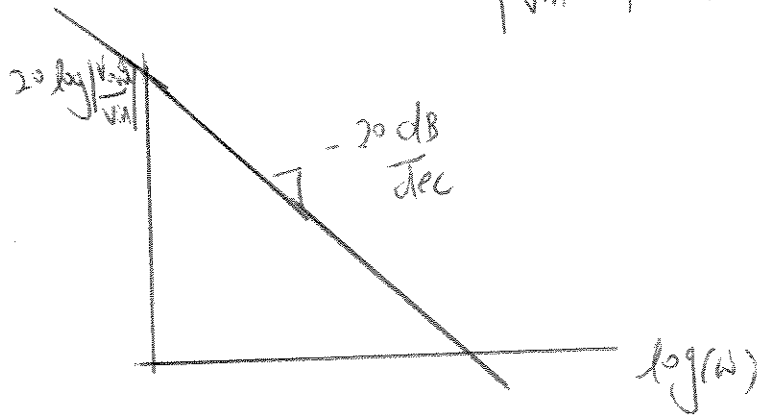


For an integrator, the gain at arbitrary low freq approaches infinity.

8) Ideal differentiator:  $S = \frac{V_{out}}{V_{in}}$ ,  $\left| \frac{V_{out}}{V_{in}}(j\omega) \right| = \omega$   
 $20 \log \left| \frac{V_{out}}{V_{in}} \right|$   
 $\omega_z = 0$

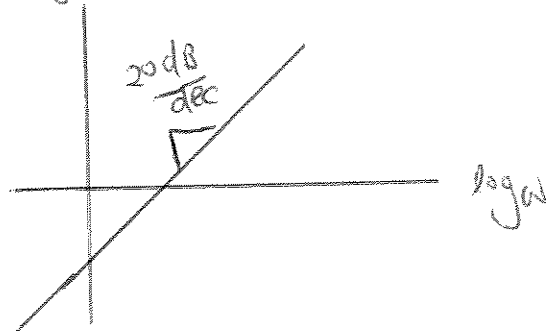

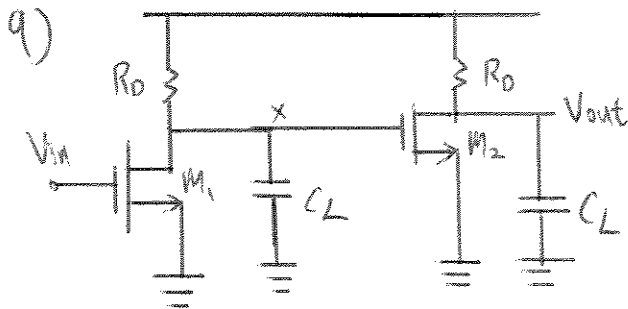For an ideal differentiator, gain at arbitrary high freq approaches infinity.





$\lambda = 0$ , ↓ neglect other caps.

DC gain:  $\frac{V_x}{V_{in}} = -g_m R_o$ ,  $\frac{V_{out}}{V_x} = -g_m R_o$

$$\frac{V_{out}}{V_{in}} = (g_m R_o)^2 \quad (\text{At DC})$$

2 poles at  $\frac{1}{R_o C_L}$

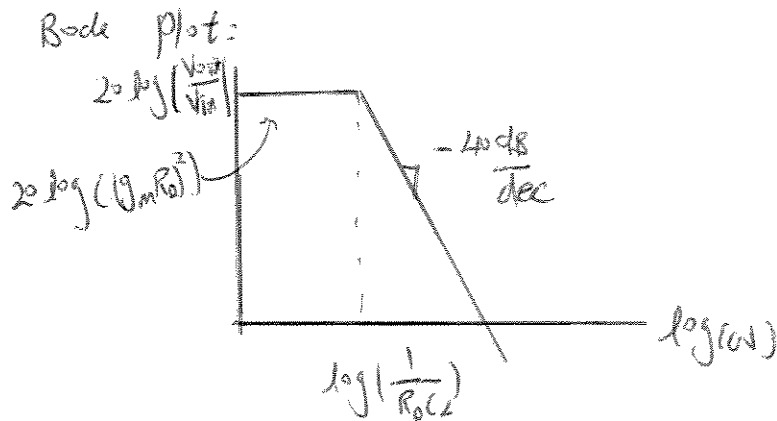

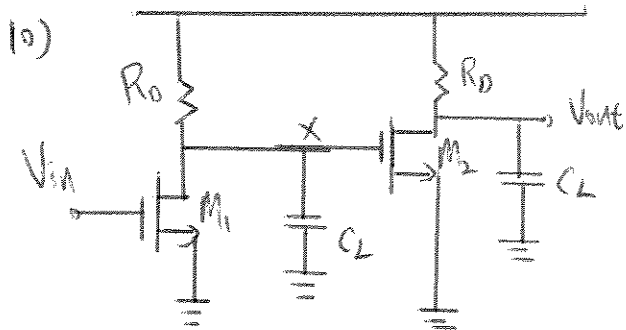

$$\frac{V_x(s)}{V_{in}} = -g_m \left( R_D \parallel \frac{1}{C_L s} \right), \quad \frac{V_{out}(s)}{V_x} = -g_m \left( \frac{R_D}{R_D C_L s + 1} \right)$$

$$= -g_m \left( \frac{R_D}{R_D C_L s + 1} \right)$$

$$H(s) = \frac{V_x(s)}{V_{in}} \frac{V_{out}(s)}{V_x} = \left( \frac{g_m R_D}{R_D C_L s + 1} \right)^2$$

$$s \rightarrow j\omega, \quad H(j\omega) = \left( \frac{g_m R_D}{1 + R_D C_L j\omega} \right)^2$$

$$|H(j\omega)| = \frac{(g_m R_D)^2}{1 + (R_D C_L \omega)^2}$$

-3dB Bandwidth:


$$\frac{(g_m R_D)^2}{1 + (R_D C_L \omega)^2} = \frac{(g_m R_D)^2}{\sqrt{2}}$$

$$\Rightarrow (R_D C_L \omega)^2 + 1 = \sqrt{2}$$

$$\Rightarrow \omega = \frac{\sqrt{\sqrt{2}-1}}{R_D C_L} = \frac{0.6436}{R_D C_L} \text{ (rad/s)}$$

$$2\pi f = \frac{0.6436}{R_D C_L} \Rightarrow f = \frac{0.10243}{R_D C_L} \text{ (Hz)}$$

11)

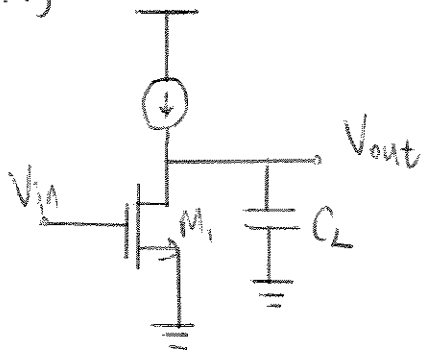

$$\lambda > 0$$

Since  $\lambda > 0$ , and we have an ideal current source, the impedance looking from out to ground is  $r_o \parallel \frac{1}{C_2 s}$


$$\text{So, } V_{out} = -g_m V_{in} \left( r_o \parallel \frac{1}{C_2 s} \right)$$

$$H(s) = -g_m \left( \frac{r_o}{r_o C_2 s + 1} \right), \quad |H(j\omega)| = \frac{g_m r_o}{\sqrt{(r_o C_2 \omega)^2 + 1}}$$

$$\text{For } \lambda \rightarrow 0, r_o \rightarrow \infty \Rightarrow H(s) \rightarrow \frac{-g_m r_o}{r_o C_2 s}$$

$H(s) = \frac{-g_m}{C_2 s}$ , A pole at origin, thus operating as an ideal integrator.

12)

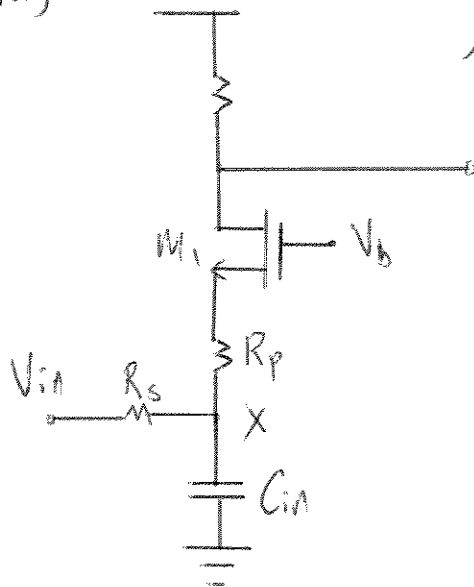


To find input pole,  
let  $V_{in} = 0$  and  
find the equivalent  
resistance and capacitance  
from node X to  
ground.

$$R_x = R_s \parallel \left( R_p + \frac{1}{g_{m_1}} \right), \quad C_x = C_{in}$$

$$\omega_{p.in} = \frac{1}{C_{in} \left[ R_s \parallel \left( R_p + \frac{1}{g_m} \right) \right]}$$

$$\omega_{p.out} = \frac{1}{R_o C_L}$$

13)

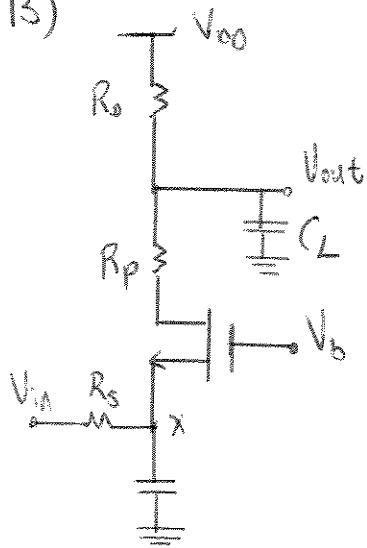

$\lambda=0$ , neglect all other caps.

$$R_x = R_s // \frac{1}{g_m}$$

$$C_x = C_{in}$$


$$R_{out} = R_o \quad (\text{since } V_o = \infty)$$

$$C_{out} = C_L$$

$$\omega_{pin} = \frac{1}{(R_s // \frac{1}{g_m}) C_{in}}$$

$$\omega_{pout} = \frac{1}{R_o C_L}$$

(4)

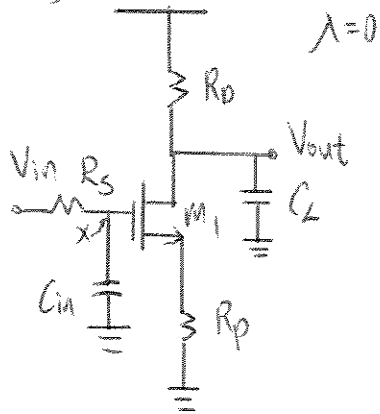


$$R_x = R_s, \quad R_{out} = R_D$$

$$C_x = C_{in}, \quad C_{out} = C_L$$
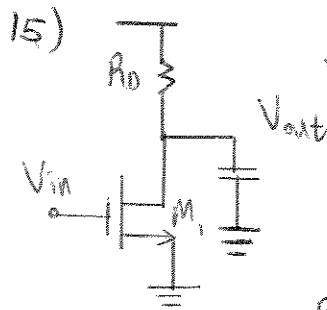
$$\omega_{pin} = \frac{1}{R_s C_{in}}, \quad \omega_{pout} = \frac{1}{R_D C_L}$$





DC Gain:  $g_m R_D = \frac{2I_D R_D}{V_{eff}}$

where  $V_{eff} = V_{GS} - V_{th}$

Band Width:  $\frac{1}{R_D C_L}$

Power Consumption:  $V_{DD} I_D$


F.O.M. (11.5) =  $\frac{\text{Gain} \times \text{Band Width}}{\text{Power Consumption}}$

$$= \frac{\left( \frac{2I_D R_D}{V_{eff}} \right) \left( \frac{1}{R_D C_L} \right)}{V_{DD} I_D}$$

$$= \frac{2}{V_{eff} V_{DD} C_L}$$


For practical design,  $V_{eff} > V_t$ , thus bipolar has a larger F.O.M. than MOS.

16)

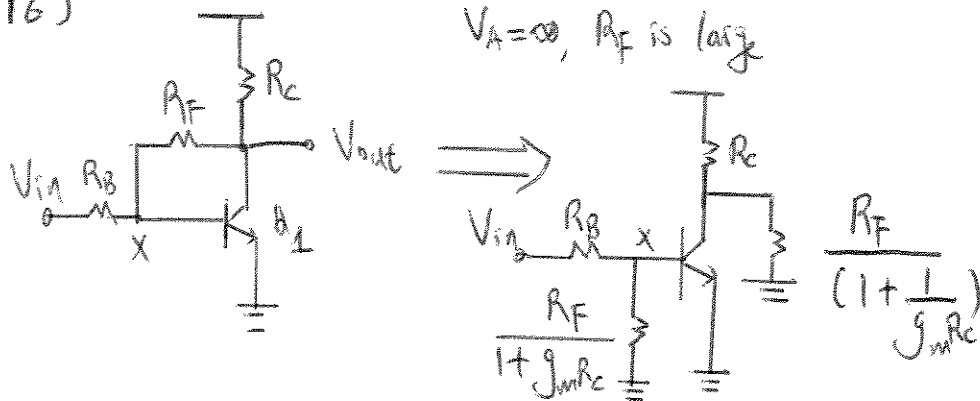

$$R_x = R_B \parallel \left( \frac{R_F}{1 + g_m R_c} \right), \quad R_{out} = R_c \parallel \left( \frac{R_F}{1 + \frac{1}{g_m R_c}} \right)$$

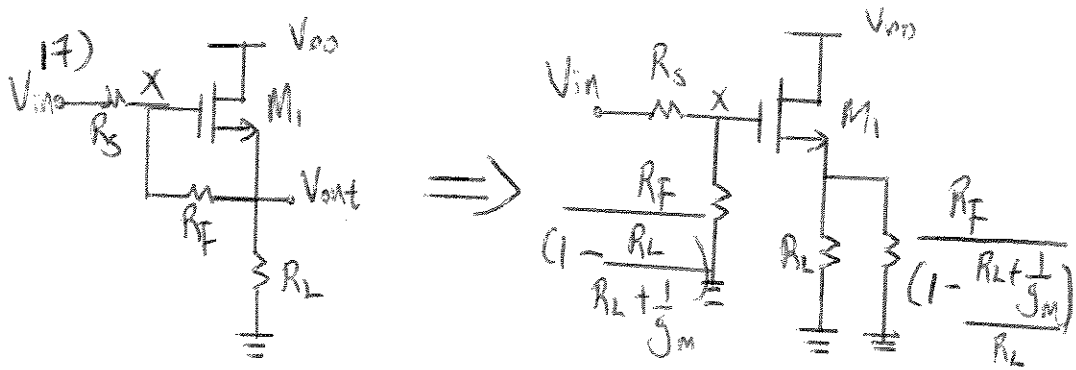
$$\frac{V_{out}}{V_{in}} = \frac{-R_{out}}{\frac{1}{g_m} + \frac{R_x}{\beta + 1}} = \frac{-R_c \parallel \left( \frac{R_F}{1 + 1/g_m R_c} \right)}{\frac{1}{g_m} + \frac{R_B \parallel \left( \frac{R_F}{1 + g_m R_c} \right)}{\beta + 1}}$$



$$R_{out} = R_L \parallel \frac{R_F}{1 - \frac{R_L + \frac{1}{g_m}}{R_L}} = R_L \parallel \frac{R_F}{-\frac{1}{g_m R_L}}$$

$$R_{out} = R_L \parallel -R_F g_m R_L \quad (\text{note that } R_{out} \text{ may be negative})$$

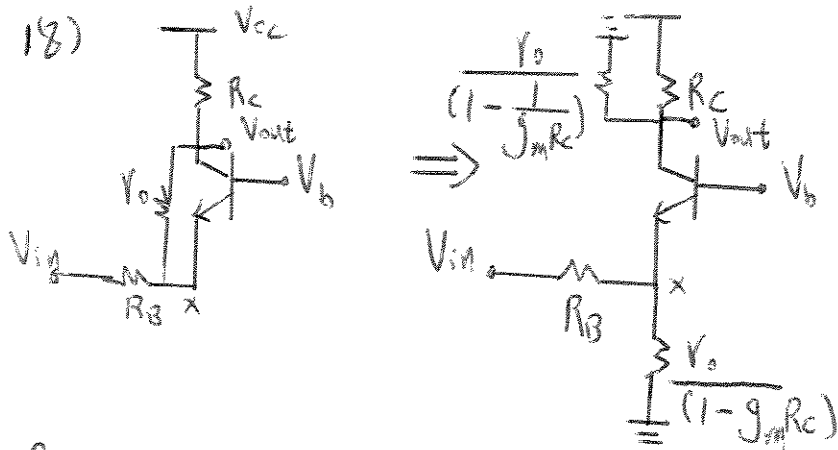
$$\frac{V_{out}}{V_{in}} = \frac{R_L \parallel -R_F g_m R_L}{R_L \parallel (-R_F R_L g_m) + \frac{1}{g_m}}$$




$$R_{out} = R_C \parallel \left( \frac{V_o}{1 - \frac{1}{\beta g_m R_C}} \right)$$

$$R_x = R_B \parallel \left( \frac{V_o}{1 - \beta g_m R_C} \right)$$
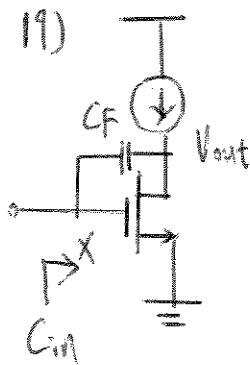
$$\frac{V_{out}}{V_{in}} = \frac{R_{out}}{R_x + \frac{1}{g_m}} = \frac{R_C \parallel \left( \frac{V_o}{1 - \frac{1}{\beta g_m R_C}} \right)}{R_B \parallel \left( \frac{V_o}{1 - \beta g_m R_C} \right) + \frac{1}{g_m}}$$



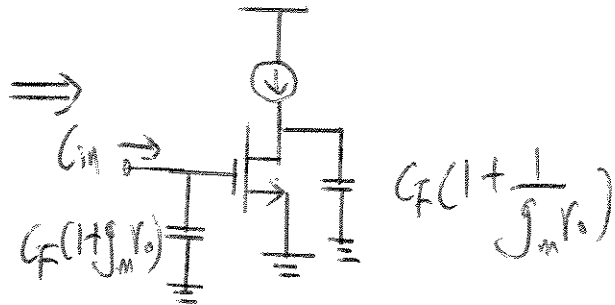
$$\lambda > 0, \text{ DC gain} = -\beta_m r_o$$



$$C_{in} = C_F (1 + \beta_m r_o), \text{ neglecting other caps.}$$

$$\text{As } \lambda \rightarrow 0, r_o \rightarrow \infty, \text{ DC gain} \rightarrow \infty,$$

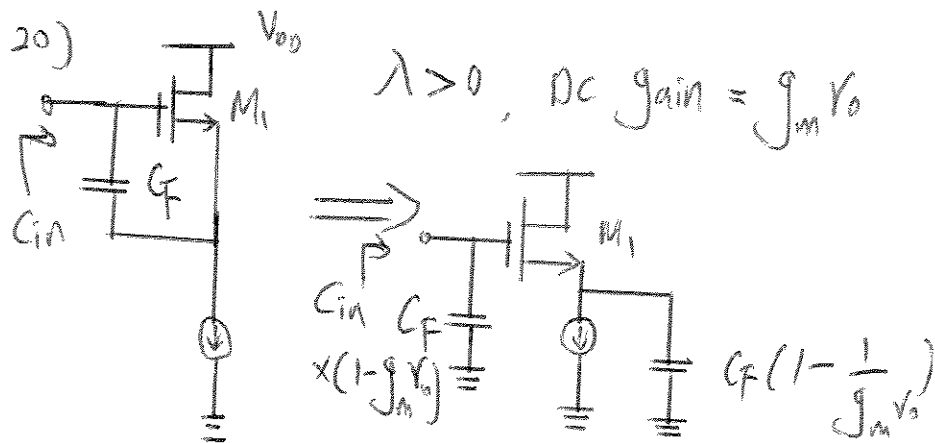
$$C_{in} \rightarrow \infty, \text{ this bandwidth will } \rightarrow 0.$$




$$C_{in} = C_f \left(1 - g_m r_o\right)$$

As  $\lambda \rightarrow 0$ ,  $r_o \rightarrow \infty$ ,  $g_m r_o \rightarrow \infty$ ,  $C_{in} = -\infty$

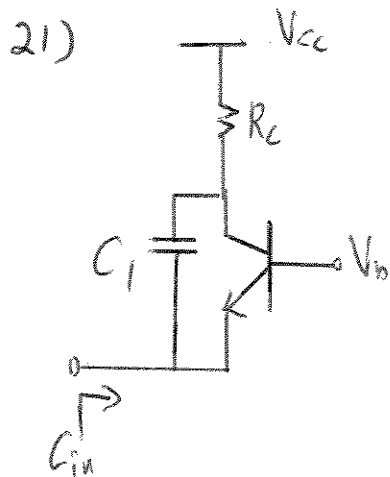When  $C \rightarrow$  negative in value, we have inductive activity. So right here, we have an effective infinite inductor.




DC gain:  $g_m R_c$

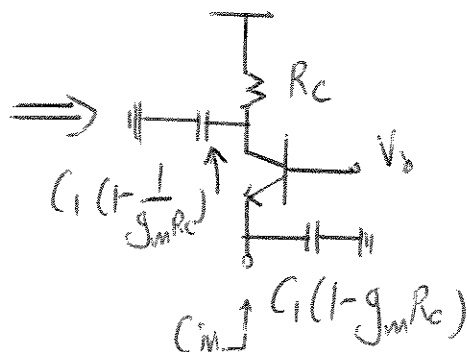


$$C_{in} = C_1 (1 - g_m R_c)$$

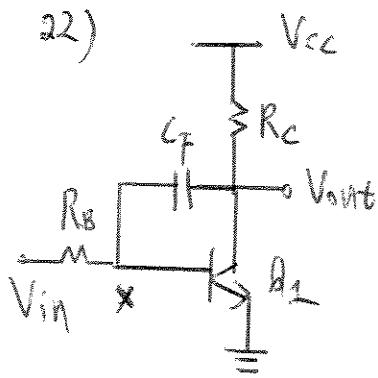If  $g_m R_c$  is designed to be larger than 1, as it normally would, we will have inductive action.



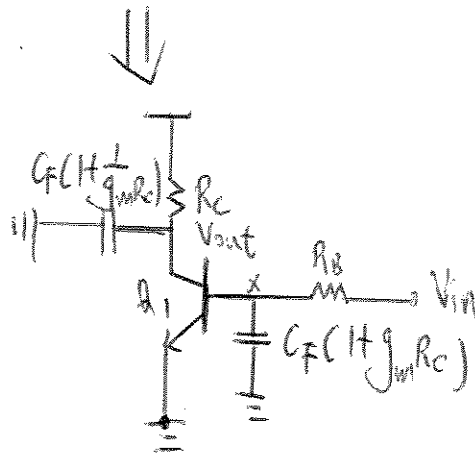DC gain (from  $x$  to out):  
 $-g_m R_c$



$$C_{in} = C_F (1 + g_m R_c)$$

$$R_{in} = R_B \parallel Y_{\pi}$$

$$C_{out} = C_F (1 + \frac{1}{g_m R_c})$$

$$R_{out} = R_c$$


$$\omega_{p1} = \frac{1}{R_B \parallel Y_{\pi} [C_F (1 + g_m R_c)]}$$

$$\omega_{pout} = \frac{1}{R_c C_F (1 + \frac{1}{g_m R_c})} \approx \frac{1}{R_c C_F}$$


(If  $g_m R_c \gg 1$ )



23)

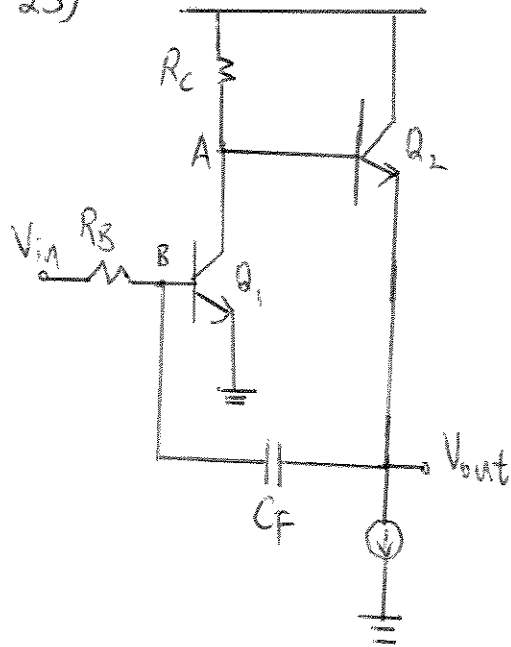

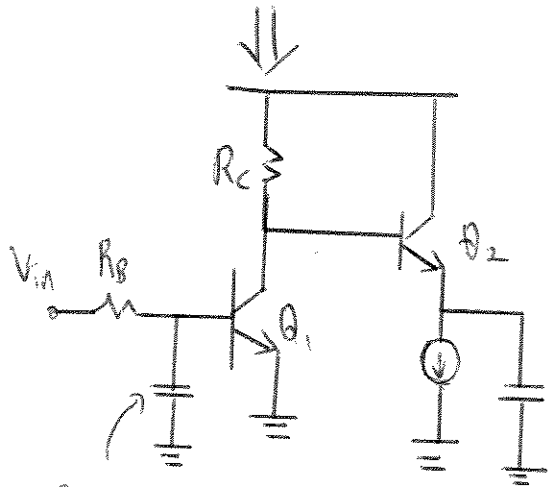The gain from B to A is  $-g_m R_C$ , from A to out is 1 (since we have an ideal current source). So the gain from B to out is  $-g_m R_C$ .



$$R_{in} = R_B \parallel r_{\pi}$$

$$C_{in} = C_F (1 + g_m R_C)$$


$$R_{out} = \frac{1}{g_m} + \frac{R_C}{\beta + 1}$$

$$C_F \left(1 + \frac{1}{g_m R_C}\right)$$

$$C_{out} = C_F \left(1 + \frac{1}{g_m R_C}\right)$$

$$\omega_{pin} = \frac{1}{R_B \parallel r_{\pi} [C_F (1 + g_m R_C)]}$$

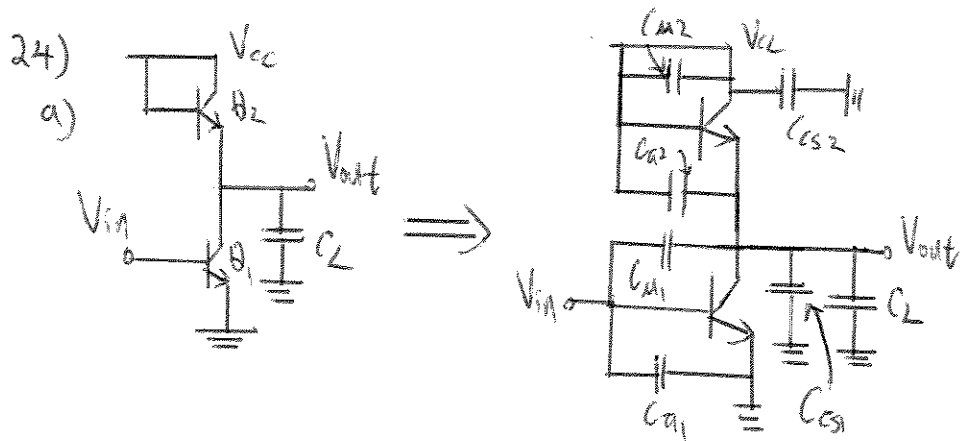
$$\omega_{pout} = \frac{1}{\left(\frac{1}{g_m} + \frac{R_C}{\beta + 1}\right) C_F \left(1 + \frac{1}{g_m R_C}\right)} \approx \frac{1}{\left(\frac{1}{g_m} + \frac{R_C}{\beta + 1}\right) C_F}, \quad (g_m R_C \gg 1)$$



$C_{M2}$ ,  $C_{S1}$ ,  $C_L$  are in parallel

$C_{M1}$ ,  $C_{S2}$  are grounded on both ends.



(and technically in parallel as well)

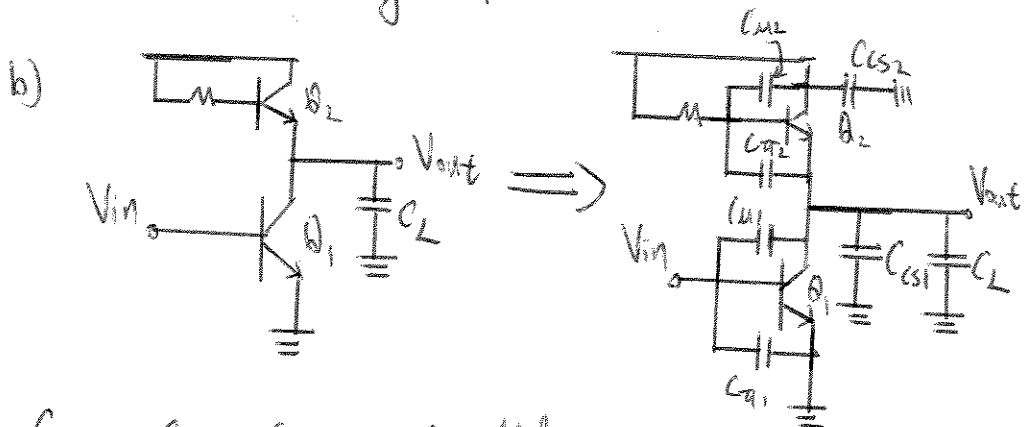


$C_{S1}$ ,  $C_L$  are in parallel

$C_{S2}$  is grounded on both ends


24)

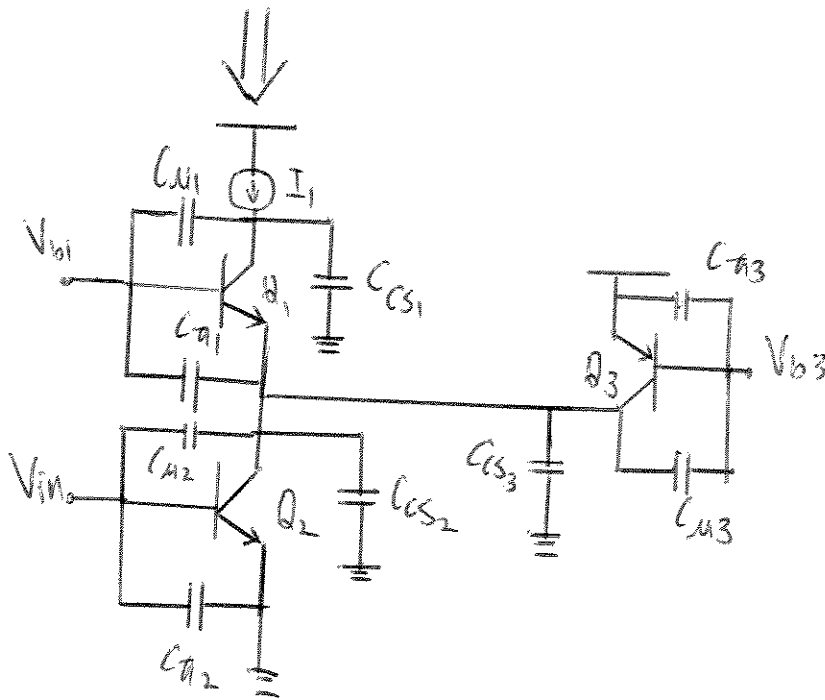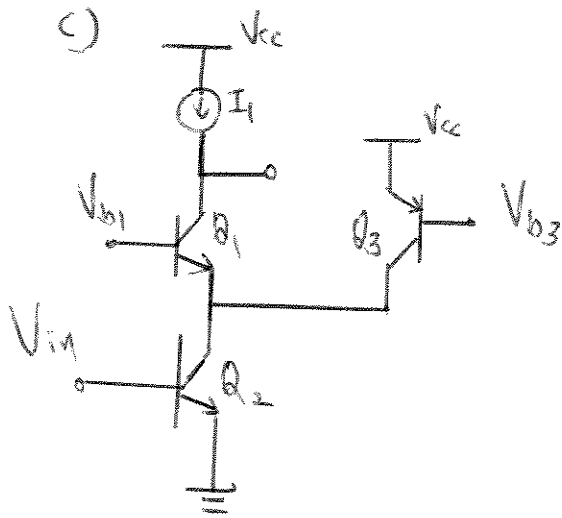

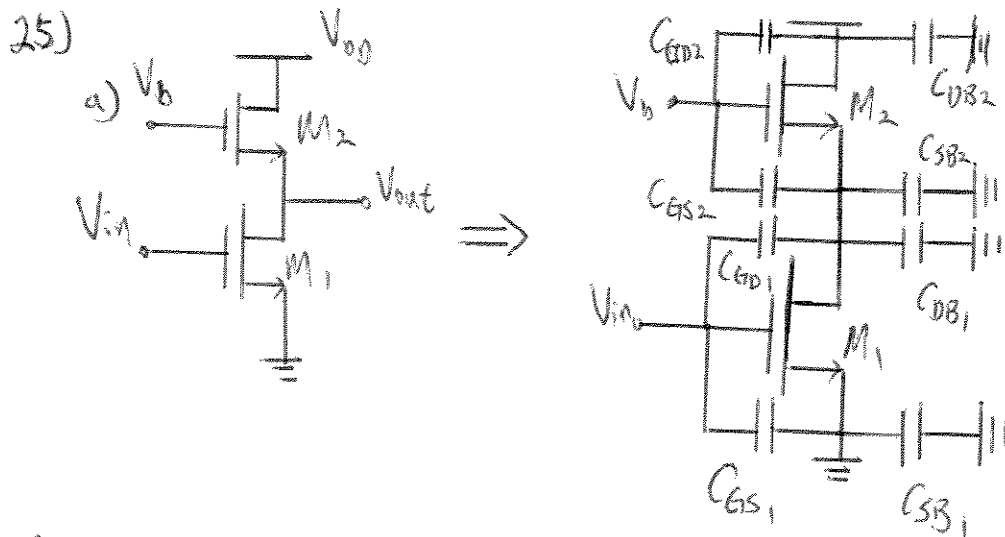$C_{\mu 1}, C_{cs 2}, C_{cs 3}, C_{\mu 3}$  are in parallel  
 $C_{\mu 1}, C_{cs 1}$  are also in parallel  
 $C_{\mu 3}$  is grounded on both ends



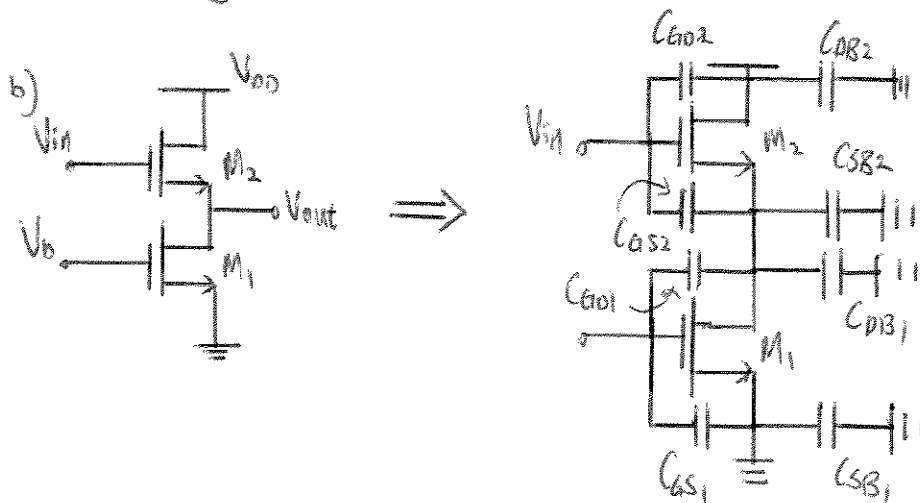$C_{GS2}$ ,  $C_{SB2}$ ,  $C_{DB1}$  are in parallel  
 $C_{GD2}$ ,  $C_{DB2}$  are in parallel and grounded on both ends  
 $C_{SB1}$  is grounded on both ends.




$C_{GD1}$ ,  $C_{DB1}$ ,  $C_{SB2}$  are in parallel

$C_{GS1}$ ,  $C_{SB1}$  are in parallel and grounded on both ends

$C_{DB2}$  is grounded on both ends.

25)

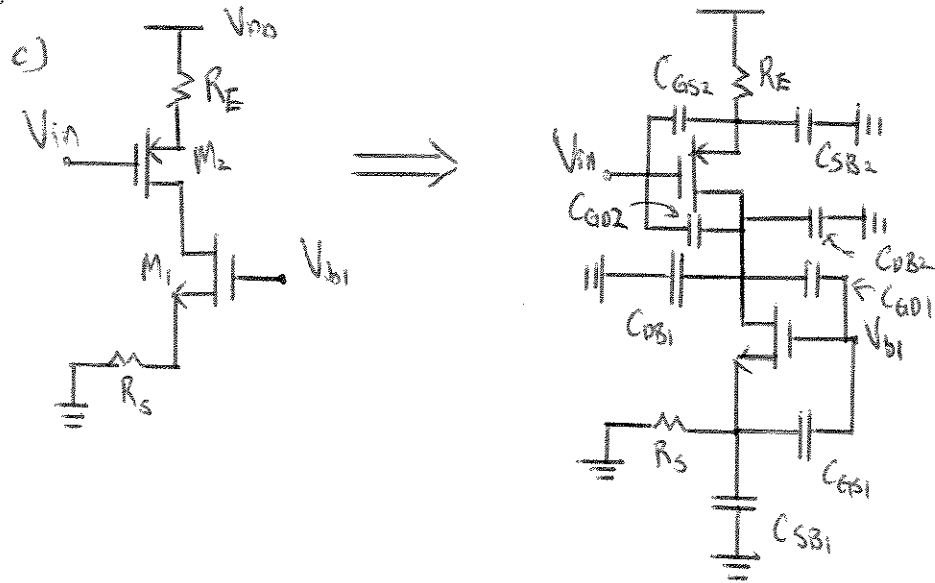


$C_{DB2}$ ,  $C_{GD1}$ ,  $C_{DB1}$ , are in parallel

$C_{SB1}$ ,  $C_{GS1}$  are also in parallel.

26)

Bipolar

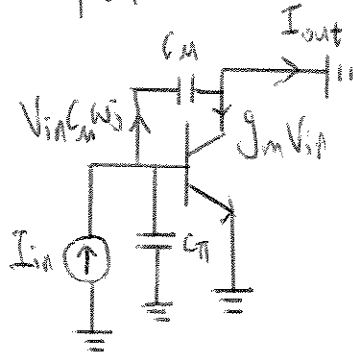


$$V_{in} = (I_{in}) \left( \frac{1}{[C_M + C_\pi] \omega j} \right) \quad (\text{Assuming we are at freq, and } V_A \text{ can be neglected})$$

$$I_{out} = V_{in} C_M \omega j - g_m I_{in} \left( \frac{1}{[C_M + C_\pi] \omega j} \right)$$

$$\frac{I_{out}}{I_{in}} = \frac{C_M \omega j - g_m}{[C_M + C_\pi] \omega j} \Rightarrow \left| \frac{I_{out}}{I_{in}} \right| = \frac{\sqrt{(g_m)^2 + (C_M \omega)^2}}{[C_M + C_\pi] \omega} = 1$$
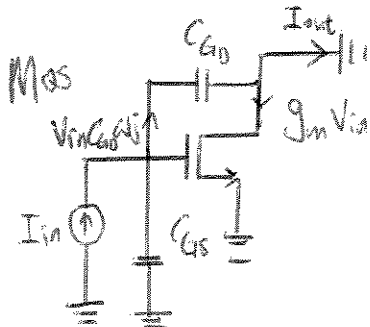
$$\omega_T^2 = \frac{g_m^2}{2 C_M C_\pi + C_\pi^2} \Rightarrow \omega_T = 2\pi f_T = \frac{g_m}{\sqrt{2 C_M C_\pi + C_\pi^2}}$$



Similarly for MOS, with  $C_M$  and  $C_\pi$  replaced by  $C_{gd}$  and  $C_{gs}$  respectively.

$$\omega_T = 2\pi f_T = \frac{g_m}{\sqrt{2 C_{gd} C_{gs} + C_{gs}^2}}$$


27)

$$C_{\pi} = g_m \tau_F + C_{je}$$

$$2\pi f_T = \frac{g_m}{C_{\pi}} = \frac{g_m}{g_m \tau_F + C_{je}}$$

Assume  $C_{je}$  to be independent  
of  $I_c$ .
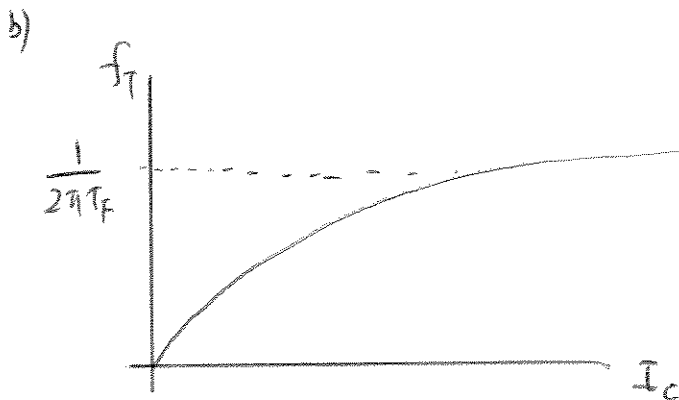
$$a) \quad 2\pi f_T = \frac{\frac{I_c}{V_T}}{\frac{I_c}{V_T} \tau_F + C_{je}} \Rightarrow f_T = \frac{I_c}{2\pi (I_c \tau_F + V_T C_{je})}$$



As  $I_c \rightarrow \infty$ ,  $f_T \rightarrow \frac{1}{2\pi \tau_F}$

28)

$$C_{GS} \approx \left(\frac{2}{3}\right) WL C_{ox}$$

$$2\pi f_T = \frac{g_m}{C_{GS}} = \frac{\frac{W}{L} \mu_n C_{ox} (V_{GS} - V_{TH})}{\frac{2}{3} WL C_{ox}}$$

$$2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$$



29)

$$2\pi f_T = \frac{3}{2} \frac{2I_D}{WLC_{ox}} \frac{1}{(V_{GS} - V_{TH})}$$

Apparently,  $f_T$  decreases with the overdrive.

However, when we look closely,  $I_D$  is

actually proportional to  $(V_{GS} - V_{TH})^2$  (in

saturation), so  $f_T$  is proportional to

$(V_{GS} - V_{TH})$ .


30)

a) As  $W \uparrow$ ,  $(V_{GS} - V_{TH})$  has to  $\downarrow$  by

$\frac{1}{\sqrt{W}}$  in order to maintain  $I_D$  constant

Using equation  $2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$


$$2\pi f_T \propto \frac{1}{\sqrt{W}}$$

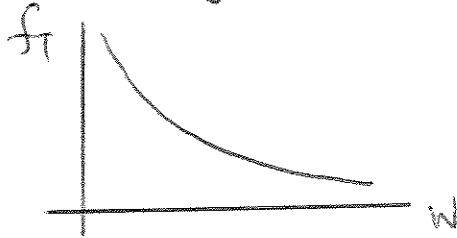

b)  $I_D \uparrow$ ,  $W$  constant it means  $V_{GS} - V_{TH} \uparrow$

With  $\sqrt{I_D}$ . Using equation  $2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$


$$2\pi f_T \propto \sqrt{I_D}$$

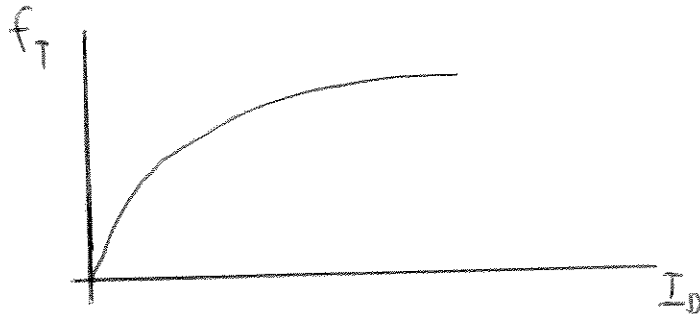

31)


Using equation  $2\pi f_T = \frac{3\mu_n}{2L^2} (V_{GS} - V_{TH})$

a)  $2\pi f_T \propto (V_{GS} - V_{TH})$

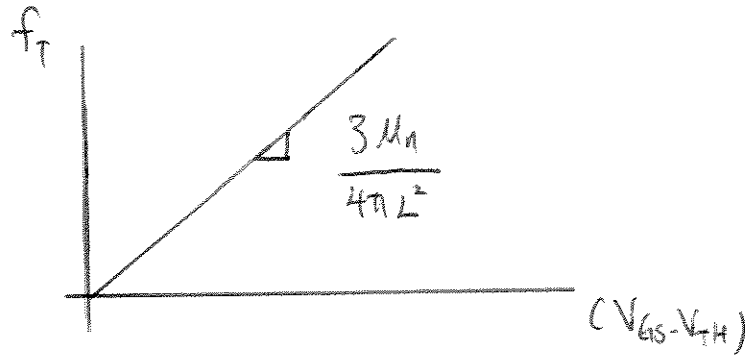

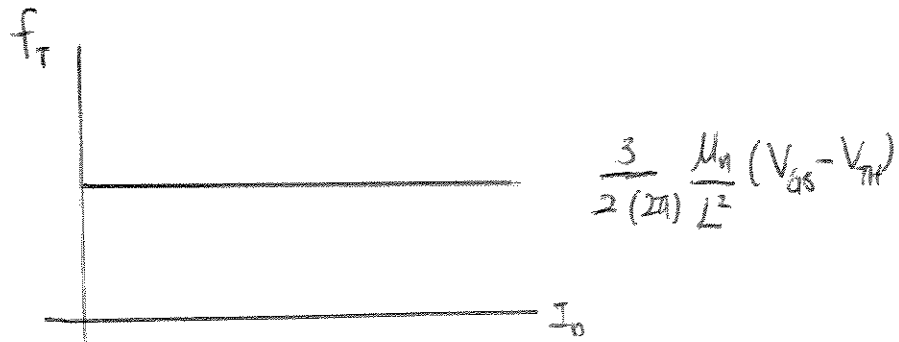b) Using equation  $2\pi f_T = \frac{3\mu_n}{2L^2} (V_{GS} - V_{TH})$


$2\pi f_T = \text{constant for all } I_D$



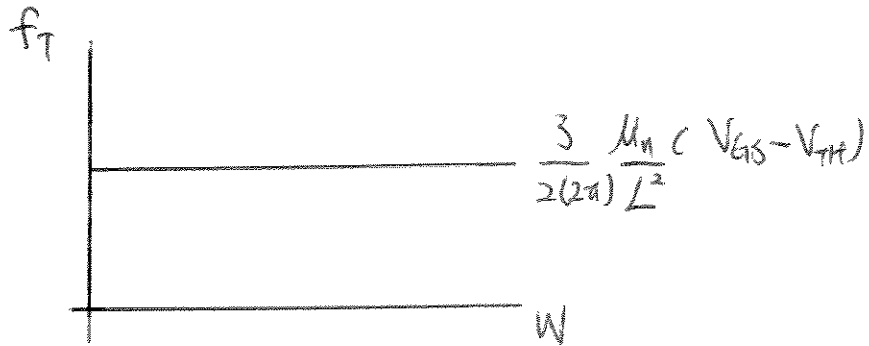32) a)


Using equation  $2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$

We know that  $2\pi f_T$  is constant for all  $W$ .



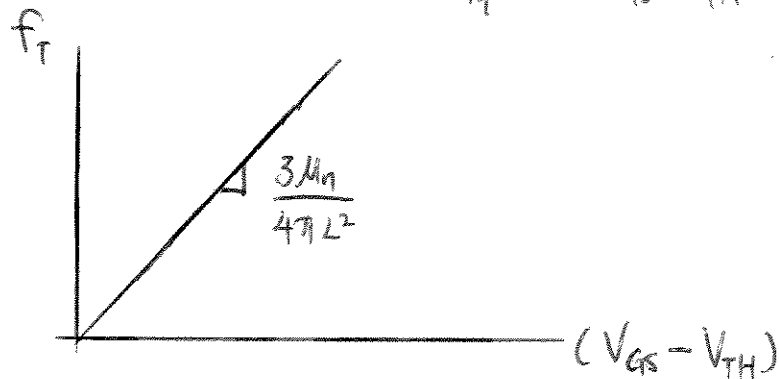b) Using equation  $2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$ ,

we know that  $2\pi f_T \propto (V_{GS} - V_{TH})$ .



33)

$$a) I_D = \frac{1}{2} \frac{W}{L} \mu_n C_{ox} (V_{GS} - V_{TH})^2$$

As  $L \uparrow$ , to maintain the same current and overdrive voltage,  $W \uparrow$  as well.

So  $W$  also  $2X$ .

$$b) \text{ Since } 2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH}), \text{ and}$$

$L$   $2X$  while  $(V_{GS} - V_{TH})$  is constant,

$$f_T \downarrow \text{ by } \frac{3}{4} \text{ or } f_{T_{\text{new}}} = \frac{1}{4} f_{T_{\text{old}}}.$$

34)

$$a) V_{GS} - V_{TH} \rightarrow \frac{1}{2} (V_{GS} - V_{TH})$$

Constant  $I_D$  and  $W \uparrow$  ( $L$  constant)

$$2\pi f_T = \frac{3}{2} \frac{M_n}{L^2} (V_{GS} - V_{TH})$$

$$f_{T, \text{new}} = \frac{f_{T, \text{old}}}{2}$$


$$b) V_{GS} - V_{TH} \rightarrow \frac{1}{2} (V_{GS} - V_{TH})$$

Constant  $W$  and  $I_D \downarrow$  ( $L$  constant)

$$2\pi f_T = \frac{3}{2} \frac{M_n}{L^2} (V_{GS} - V_{TH})$$

$$f_{T, \text{new}} = \frac{f_{T, \text{old}}}{2}$$


35)  
Bipolar CE Stage

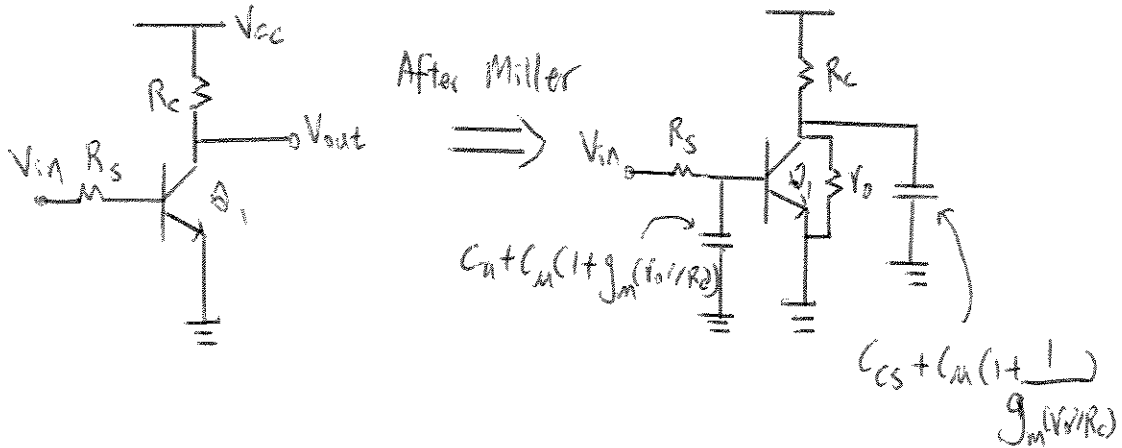

$$\omega_{p_{in}} = \frac{1}{(R_s // R_{in}) [C_i + C_\mu(1 + g_m(V_o/R_L))]}$$

$$\omega_{p_{out}} = \frac{1}{(R_c // R_o) [C_{o3} + C_\mu(1 + 1/g_m(V_o/R_L))]}$$


MOS CS Stage

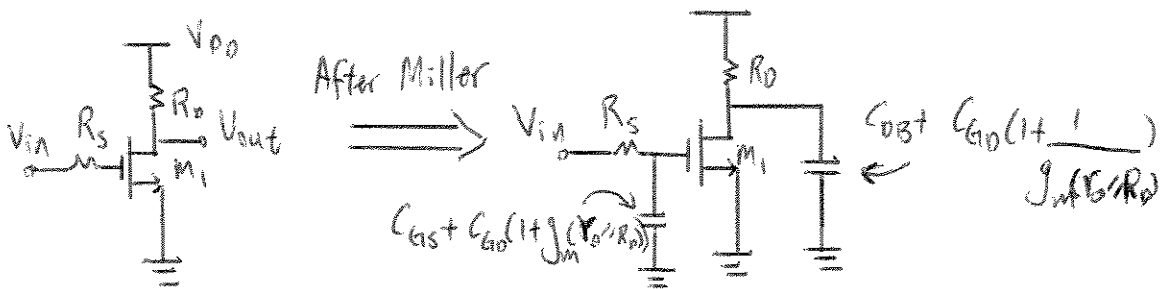

$$\omega_{p_{in}} = \frac{1}{R_s [C_{i3} + C_{gd}(1 + g_m(V_o/R_L))]}$$

$$\omega_{p_{out}} = \frac{1}{(R_D // R_o) [C_{o3} + C_{gd}(1 + 1/g_m(V_o/R_L))]}$$

36)

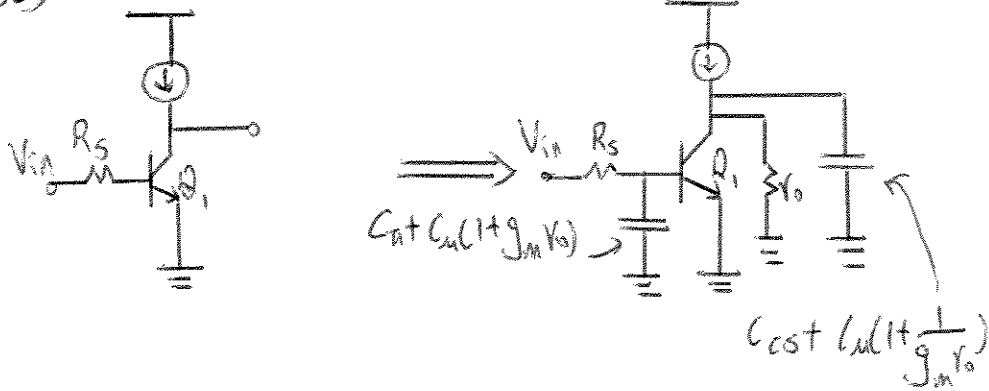


$$\omega_{p1} = \frac{1}{(R_s \parallel r_{\pi}) [C_{\pi} + C_{\mu}(1 + g_m r_o)]}$$

$$\omega_{p2} = \frac{1}{r_o [C_{cs} + C_{\mu}(1 + 1/g_m r_o)]}$$

$$H(s) = \frac{\text{DC gain}}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$
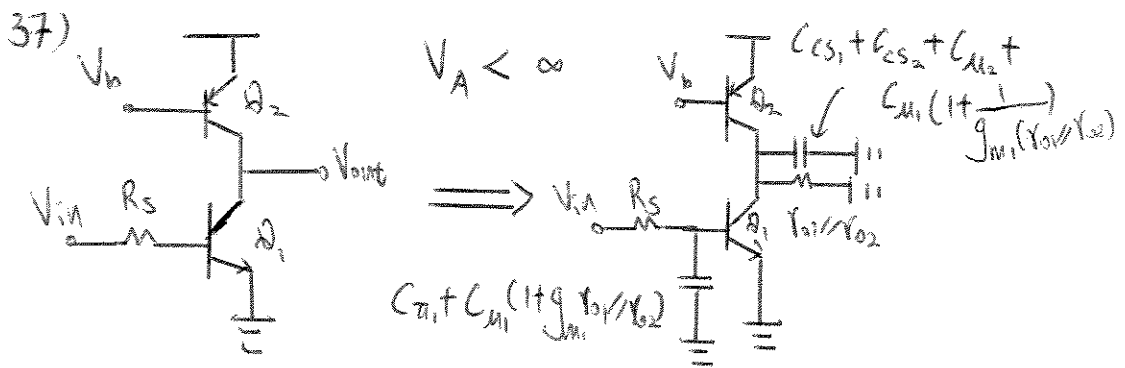
$$H(s) = \frac{g_m r_o (r_{\pi} / (r_{\pi} + R_s))}{\left(1 + \frac{s}{1 / (R_s \parallel r_{\pi}) [C_{\pi} + C_{\mu}(1 + g_m r_o)]}\right) \left(1 + \frac{s}{1 / (r_o [C_{cs} + C_{\mu}(1 + 1/g_m r_o)])}\right)}$$





$$\omega_{pin} = \frac{1}{(R_s/V_{in}) [C_{\pi1} + C_{\mu1} (1 + g_{m1} (V_{o1}/V_{o2}))]}$$



$$\omega_{pout} = \frac{1}{(V_{o1}/V_{o2}) [C_{cs1} + C_{cs2} + C_{\mu2} + C_{\mu1} (1 + 1/(g_{m1} (V_{o1}/V_{o2})))]}$$

$$g_m V_o \gg 1$$

$$H(s) = \frac{g_m (V_{o1}/V_{o2}) (V_{in}/V_{in} + R_s)}{(1 + R_s [C_{\pi1} + C_{\mu1} (g_m (V_{o1}/V_{o2}))] s) (1 + (V_{o1}/V_{o2}) [C_{cs1} + C_{cs2} + C_{\mu2} + C_{\mu1}] s)}$$

3B)

a)

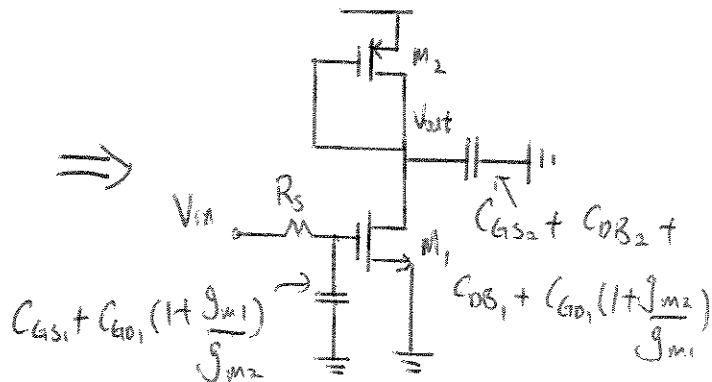
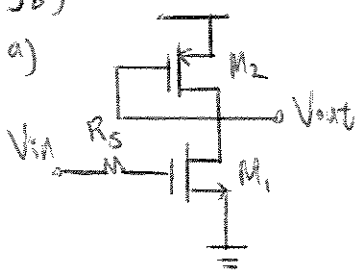


$$\text{DC gain} = -g_{m1} (V_{o1} // V_{o2} // \frac{1}{g_{m2}}) \approx -\frac{g_{m1}}{g_{m2}}$$

$$\omega_{p_{in}} = \frac{1}{R_s (C_{gs1} + C_{gd1} (1 + \frac{g_{m1}}{g_{m2}}))}$$

$$\omega_{p_{out}} = \frac{g_{m2}}{C_{gs2} + C_{db2} + C_{db1} + C_{gd1} (1 + \frac{g_{m2}}{g_{m1}})}$$

b)

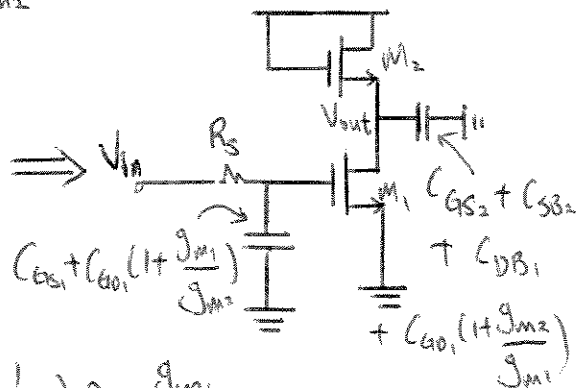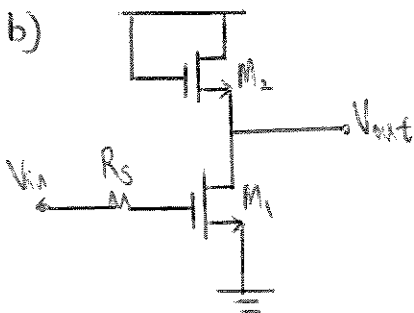


$$\text{DC gain} = -g_{m1} (V_{o1} // V_{o2} // \frac{1}{g_{m2}}) \approx -\frac{g_{m1}}{g_{m2}}$$

$$\omega_{p_{in}} = \frac{1}{R_s (C_{gs2} + C_{gd2} (1 + \frac{g_{m2}}{g_{m1}}))}$$

$$\omega_{p_{out}} = \frac{g_{m2}}{C_{db2} + C_{gs2} + C_{db1} + C_{gd1} (1 + \frac{g_{m2}}{g_{m1}})}$$

38)

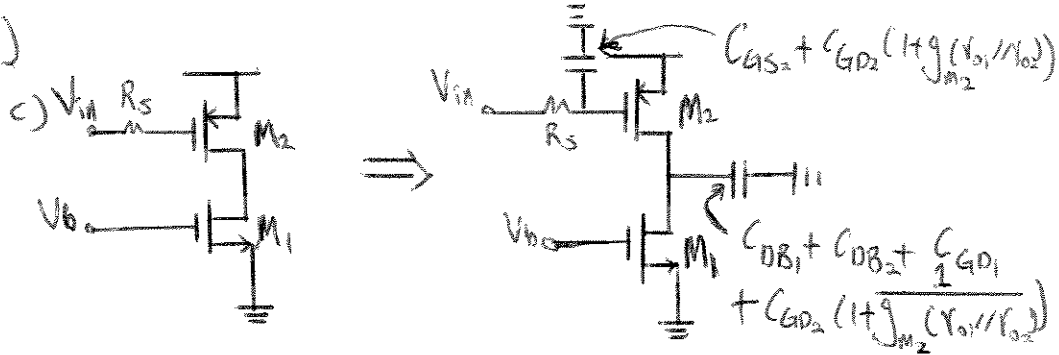

DC gain:  $-g_{m2} (V_{o1} // V_{o2})$


$$\omega_{pin} = \frac{1}{R_S (C_{gs2} + C_{GD2} (1 + g_{m2} (V_{o1} // V_{o2})))}$$

$$\omega_{pout} = \frac{1}{(V_{o1} // V_{o2}) [C_{DB1} + C_{DB2} + C_{GD1} + C_{GD2} (1 + \frac{1}{g_{m2} (V_{o1} // V_{o2})})]}$$

$$\omega_{pout} \approx \frac{1}{(V_{o1} // V_{o2}) [C_{DB1} + C_{DB2} + C_{GD1} + C_{GD2}]}$$

Since  $g_{m2} (V_{o1} // V_{o2}) \gg 1$

39)

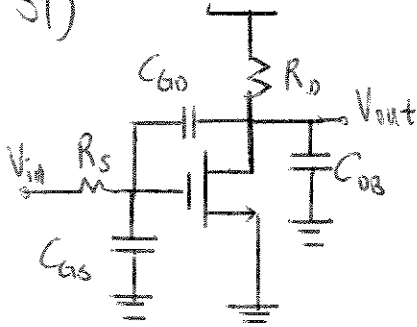


$$R_S = 200 \Omega \quad C_{GS} = 5 \text{ fF}$$

$$R_D = 1 \text{ k}\Omega \quad C_{GD} = 10 \text{ fF}$$

$$I_D = 1 \text{ mA} \quad C_{DB} = 15 \text{ fF}$$

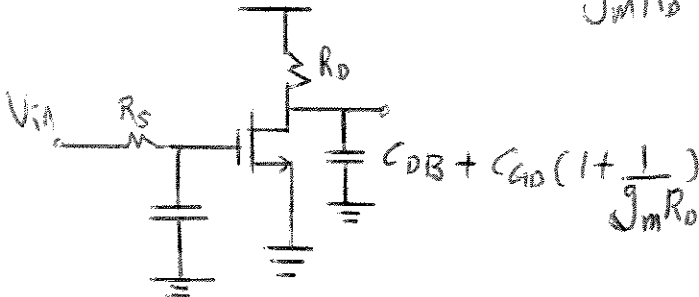a) Miller's approximation:

$$-g_m R_D = \frac{-(1)(2)(1)}{(0.2)} = -10$$



$$C_{GS} + (1 + g_m R_D) C_{GD}$$

$$\omega_{p_{in}} = \frac{1}{R_S (C_{GS} + (1 + g_m R_D) C_{GD})} = \frac{1}{200 (5 \text{ fF} + (11)(10 \text{ fF}))} = 31.25 \text{ GHz}$$

$$\omega_{p_{out}} = \frac{1}{R_D (C_{DB} + (1 + \frac{1}{10}) C_{GD})} = \frac{1}{1000 (15 \text{ fF} + (1 + 0.1) 10 \text{ fF})} = 38.46 \text{ GHz}$$

39)

$$b) \text{ Equation } \frac{V_{out}(s)}{V_{Thev}} = \frac{(C_{XY}S - g_m)R_L}{as^2 + bs + 1}$$

$$a = R_{Thev}R_L(C_{in}C_{XY} + C_{out}C_{XY} + C_{in}C_{out})$$

$$R_{Thev} = R_S, C_{in} = C_{GS}, C_{out} = C_{OB}, R_L = R_O, C_{XY} = C_{GD}$$

$$a = (200 \times 1000) [(50 \times 10^{-15})(10 \times 10^{-15}) + (15 \times 10^{-15})(10 \times 10^{-15}) + (50 \times 10^{-15})(15 \times 10^{-15})] = 2.8 \times 10^{-22}$$

$$b = (1 + g_m R_L)C_{XY}R_{Thev} + R_{Thev}C_{in} + R_L(C_{XY} + C_{out})$$

$$b = (1 + 10)(10 \times 10^{-15})(200) + (200)(50 \times 10^{-15}) + (1000)(10 \times 10^{-15}) + 1000(15 \times 10^{-15})$$

$$b = 5.7 \times 10^{-11}$$

$$\text{So denominator} = (2.8 \times 10^{-22} s^2 + 5.7 \times 10^{-11} s + 1)$$

$$s = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$s = -1.93909 \times 10^{10}, -1.84181 \times 10^{11}$$

$$\omega_{p1} = 19.39 \text{ GHz}, \omega_{p2} = 184.2 \text{ GHz}$$

Which one is  $\omega_{pin}$ , and which one is  $\omega_{pout}$ ?

This can be seen from inspection, at output and high frequency  $C_{GD}$  starts to become a short and thus the output resistance collapses to  $1/g_m$ , and pushes the output pole out. Whereas at the input the pole location does not change too much because  $R_S$  is small and  $C_{GS}$  is large.

Therefore, we conclude that when solving the transfer function directly, the  $\omega_{pin}$  is 19.39 GHz (on the same order as

39)

b). that obtained from Miller's approximation), while  $\omega_{\text{pout}}$  is pushed out significantly, 184.2 GHz (when compared to that obtained from Miller's approximation).

Miller Approximation

$$\omega_{\text{pin}} = 31.25 \text{ GHz}$$


$$\omega_{\text{pout}} = 38.46 \text{ GHz}$$

Transfer Function


$$\omega_{\text{pin}} = 19.39 \text{ GHz}$$

$$\omega_{\text{pout}} = 184.2 \text{ GHz}$$

40)

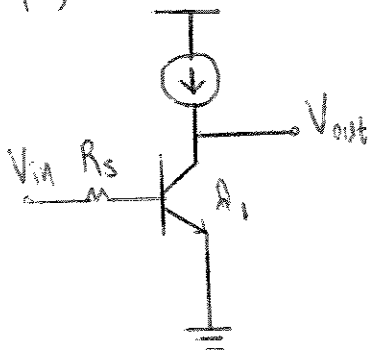

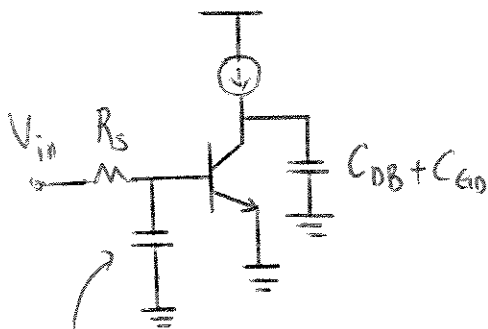a) Miller's Approximation: DC gain:  $-\infty$



$C_{GS} + \infty$

$$\omega_{pin} = \frac{1}{R_s(\infty)} = 0, \quad \omega_{part} = \frac{1}{\infty(C_{OB} + C_{GD})} = 0$$

b) Transfer Function:

$$\frac{V_{out}(s)}{V_{thv}} = \frac{(C_{xy}s - g_m)R_L}{as^2 + bs + 1}$$

$$a = R_{Thev}R_L(C_{in}C_{xy} + C_{out}C_{xy} + C_{in}C_{out})$$

$$b = (1 + g_mR_L)C_{xy}R_{Thev} + R_{Thev}C_{in} + R_L(C_{xy} + C_{out})$$

40)

b)  $R_2 \rightarrow \infty$

$$\frac{V_{out}}{V_{thv}} = \frac{C_{xy} S - g_m}{S [R_{thv} (C_{in} C_{xy} + C_{out} C_{xy} + C_{in} C_{out}) S + g_m C_{xy} R_{thv} + (C_{xy} + C_{out})]}$$

so  $\omega_{p1} = 0$

$$\omega_{p2} = \frac{(g_m C_{xy} R_{thv} + (C_{xy} + C_{out}))}{R_{thv} [C_{in} C_{xy} + C_{out} C_{xy} + C_{in} C_{out}]}$$

$$\omega_{p2} = \frac{g_m C_u R_S / R_{th} + C_u + C_{cs}}{R_S / R_{th} [C_{in} C_u + C_{cs} C_u + C_{in} C_{cs}]}$$

$\omega_{p1} = \omega_{pin}, \quad \omega_{p2} = \omega_{pout}.$

Miller:

$\omega_{pin} = 0, \quad \omega_{pout} = 0$

Again, the output pole predicted by the transfer function is pushed out, and the input poles are similar. (In fact, they are the same this time.)

This shows one of the short-comings of Miller's approximation.



4) Dominant-pole approximation:

$$\omega_{p1} = \frac{1}{(1 + g_m R_L) C_{xy} R_{Thev} + R_{Thev} C_{in} + R_L (C_{xy} + C_{out})}$$

$$\omega_{p1} = 0 \quad (\text{Since } R_L = \infty)$$

$$\omega_{p2} = \frac{(1 + g_m R_L) C_{xy} R_{Thev} + R_{Thev} C_{in} + R_L (C_{xy} + C_{out})}{R_{Thev} R_L (C_{in} C_{xy} + C_{out} C_{xy} + C_{in} C_{out})}$$


Since  $R_L = \infty$

$$\omega_{p2} = \frac{g_m C_{xy} R_{Thev} + C_{xy} + C_{out}}{R_{Thev} (C_{in} C_{xy} + C_{out} C_{xy} + C_{in} C_{out})}$$

$$\omega_{p2} = \frac{g_m C_M R_S' R_{\pi} + C_M + C_{CS}}{R_S (C_{\pi} C_M + C_{CS} C_M + C_{\pi} C_{CS})}$$

Dominant-pole approximation gives the same result as the transfer function method.

42)

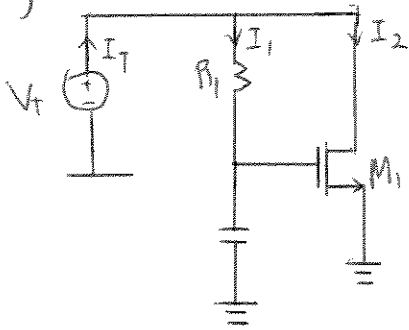

$\lambda=0$ , and neglect other capacitances.

$$I_T = I_1 + I_2$$


$$I_1 = \frac{V_T}{(R_1 + \frac{1}{C_1 s})}, \quad I_2 = \frac{g_m V_T}{C_1 R_1 s + 1}$$

$$I_T = \frac{C_1 s V_T}{C_1 R_1 s + 1} + \frac{g_m V_T}{C_1 R_1 s + 1} \Rightarrow \frac{V_T}{I_T} = \frac{C_1 R_1 s + 1}{C_1 s + g_m}$$

$$s \rightarrow j\omega \Rightarrow \frac{C_1 R_1 (j\omega) + 1}{C_1 j\omega + g_m} = Z_T(j\omega)$$


$$|Z_T| = |Z_{in}| = \frac{\sqrt{(C_1 R_1 \omega)^2 + 1}}{\sqrt{C_1^2 \omega^2 + g_m^2}} = \frac{\sqrt{C_1 R_1 \omega^2 + 1}}{g_m \sqrt{\left(\frac{C_1 \omega}{g_m}\right)^2 + 1}}$$

At  $\omega = \frac{1}{C_1 R_1}$ , we have a zero, at  $\omega = \frac{g_m}{C_1}$ , we have a pole. If  $R_1 > \frac{1}{g_m}$ , the zero  $C_1$  is at a lower frequency than the pole, and the bode-plot for magnitude would look like the following.

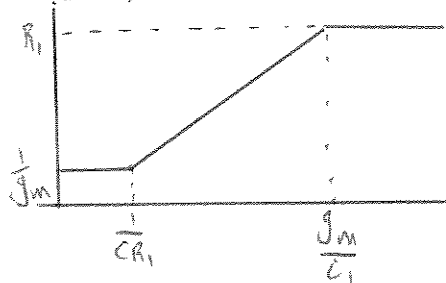 $20 \log(Z_{in})$ 


The bode-plot shows an impedance that increases with frequency, an inductive behavior.

43)

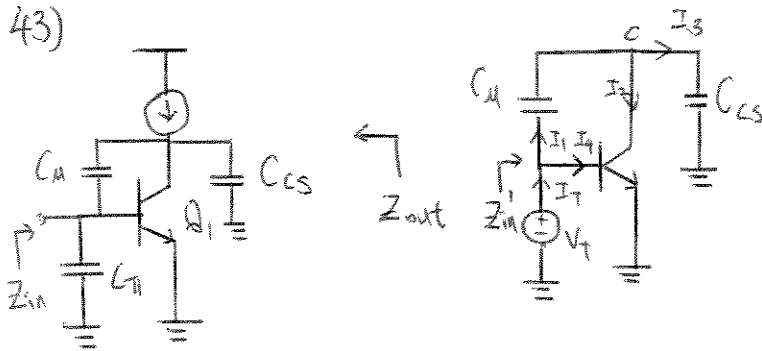

$$Z_{in} = Z_{in}' \parallel \frac{1}{C_{in} s}, \quad I_T = I_1 + I_4 = C_{in} s V_{bc} + \frac{g_m V_T}{\beta}$$

$$V_{bc} = V_T - V_c, \quad V_c = (I_1 - g_m V_T) \frac{1}{C_{CS} s}$$

$$I_1 = \left[ V_T - (I_1 - g_m V_T) \frac{1}{C_{CS} s} \right] C_{in} s$$

$$I_1 = V_T \left[ C_{in} s + \frac{g_m C_{in}}{C_{CS}} \right] / \left( 1 + \frac{C_{in}}{C_{CS}} \right)$$


$$I_T = V_T \left[ C_{in} s + \frac{g_m C_{in}}{C_{CS}} \right] / \left( 1 + \frac{C_{in}}{C_{CS}} \right) + \frac{g_m V_T}{\beta}$$

$$Z_{in}' = \frac{V_T}{I_T} = \frac{1}{\frac{g_m}{\beta} + \frac{C_{in} s}{\left( 1 + \frac{C_{in}}{C_{CS}} \right)} + \frac{g_m C_{in}}{\left( 1 + \frac{C_{in}}{C_{CS}} \right) C_{CS}}}$$

$$Z_{in} = Z_{in}' \parallel \frac{1}{C_{in} s} = r_{\pi} \parallel \frac{1}{\frac{C_{CS} C_{in} s}{C_{CS} + C_{in}}} \parallel \frac{1}{C_{in} s} \parallel \frac{C_{CS} + C_{in}}{g_m C_{in}}$$

$$Z_{out} = \frac{1}{(C_{out} + C_{CS}) s}$$

44)

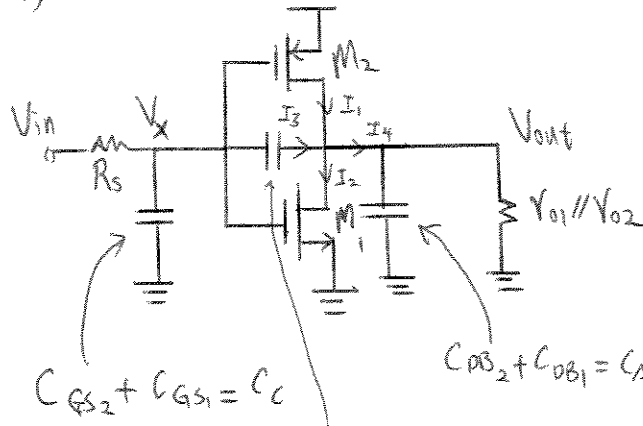 $\lambda > 0$ 

$$C_{GS2} + C_{GS1} = C_C$$

$$C_{GD1} + C_{GD2} = C_B$$

$$C_{DB2} + C_{DB1} = C_A$$

$$V_{out} = I_4 \left( Y_{01} // Y_{02} // \frac{1}{[C_{DB2} + C_{DB1}]s} \right) \xrightarrow{Z_{out}}$$

$$I_4 = I_1 + I_3 - I_2$$

$$I_1 = (0 - V_x) g_{m2}$$

$$I_2 = V_x g_{m1}$$

$$I_3 = (V_x - V_{out}) (C_{GD1} + C_{GD2}) s$$

$$I_4 = -V_x g_{m2} + (V_x - V_{out}) C_B s - V_x g_{m1}$$

$$V_{out} = Z_{out} [-V_x (g_{m2} + g_{m1}) + (V_x - V_{out}) C_B s]$$

Writing a node equation at X.

$$\frac{V_x - V_{in}}{R_s} + V_x C_C s + (V_x - V_{out}) C_B s = 0$$

$$V_x = \frac{V_{out} C_B s + V_{in}/R_s}{(1/R_s + C_C s + C_B s)}$$

$$(1/R_s + C_C s + C_B s)$$

44)

Substitute everything and we get

$$V_{out} = Z_{out} \left[ -(g_{m1} + g_{m2}) \left( \frac{V_{out} C_B s + V_{in} / R_s}{1/R_s + C_c s + C_B s} \right) + \left( \frac{V_{out} C_B s + V_{in} / R_s}{1/R_s + C_c s + C_B s} - V_{out} \right) C_B s \right]$$

Collect all the  $V_{out}$ 's on one-side and likewise for  $V_{in}$ 's,  
we will get

$$\frac{V_{out}}{V_{in}} = \frac{Z_{out}}{R_s} (C_B s - (g_{m1} + g_{m2}))$$


$$\frac{1}{R_s + (C_c + C_B) s} + Z_{out} C_B s (g_{m1} + g_{m2}) + Z_{out} C_B s \left( \frac{1}{R_s} + (C_c + C_B) s \right) - Z_{out} C_B^2 s^2$$

$$\text{where } Z_{out} = Y_{o1} // Y_{o2} // \frac{1}{[C_{DB1} + C_{DB2}] s}$$

$$C_B = C_{GD1} + C_{GD2}$$

$$C_c = C_{GS1} + C_{GS2}$$

45)

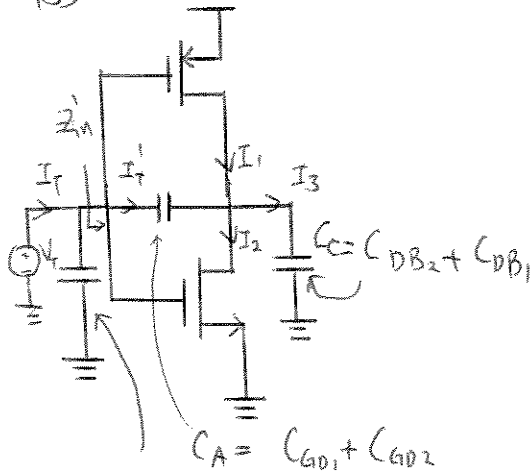

$$Z_{in} = \frac{V_T}{I_T} = \frac{1}{C_B} \parallel Z_{in}'$$

$$Z_{in}' = \frac{V_T}{I_T'}$$

$$C_B = C_{GS1} + C_{GS2}$$

$$I_T' = [V_T - (I_3 \frac{1}{C_{CS}})] C_{AS}$$

$$I_3 = I_T' - V_T g_{m2} - g_{m1} V_T$$


$$\text{We get } \Rightarrow I_T' (1 + \frac{C_A}{C_C}) = V_T [C_{AS} + (g_{m1} + g_{m2}) \frac{C_A}{C_C}]$$

$$Z_{in}' = \frac{V_T}{I_T'} = \frac{(1 + \frac{C_A}{C_C})}{[C_{AS} + (g_{m1} + g_{m2}) \frac{C_A}{C_C}]}$$

$$Z_{in} = \frac{1}{[C_{GS1} + C_{GS2}]s} \parallel \frac{(1 + \frac{C_{GD1} + C_{GD2}}{C_{DB1} + C_{DB2}})}{[ (C_{GD1} + C_{GD2})s + (g_{m1} + g_{m2}) \frac{C_{GD1} + C_{GD2}}{C_{DB2} + C_{DB1}} ]}$$

46)

a)

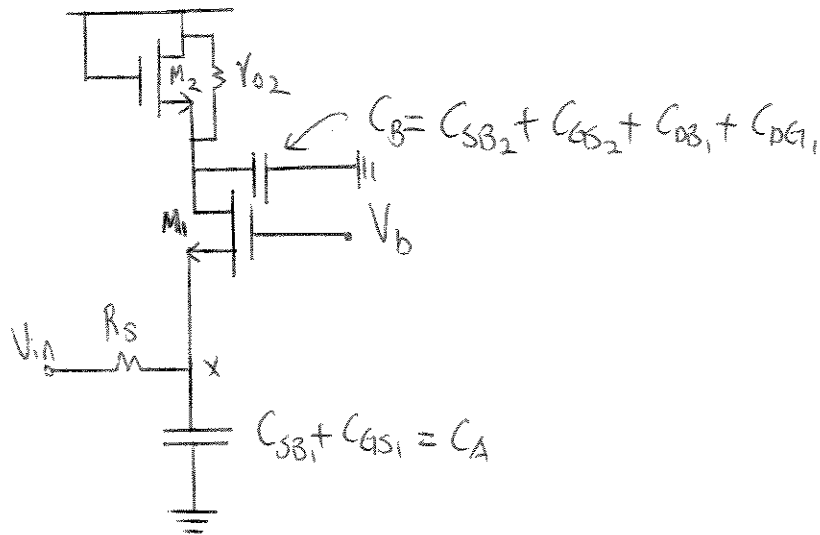

$$V_{out} = -(0 - V_x) g_{m1} \left[ \frac{1}{g_{m2}} \parallel \frac{1}{C_B s} \right] = V_x g_{m1} \left[ \frac{1}{g_{m2}} \parallel \frac{1}{C_B s} \right]$$

Node equation at X,  $\frac{V_x - V_{in}}{R_s} + V_x C_A s - g_m (0 - V_x) = 0$

$$V_x \left( \frac{1}{R_s} + C_A s + g_m \right) = \frac{V_{in}}{R_s} \Rightarrow V_x = \frac{V_{in}}{(1 + R_s C_A s + R_s g_m)}$$

substitute in  $V_x$  and solving for  $V_{out}/V_{in} \Rightarrow$


$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} \left[ \frac{1}{g_{m2}} \parallel \frac{1}{C_B s} \right]}{(1 + R_s C_A s + R_s g_m)}$$

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} (1/g_{m2})}{(C_B (1/g_{m2}) s + 1) (1 + R_s C_A s + R_s g_m)}$$

Where  $C_B = C_{SB2} + C_{CS2} + C_{DB1} + C_{DB2}$

$$C_A = C_{SB1} + C_{CS1}$$

46)

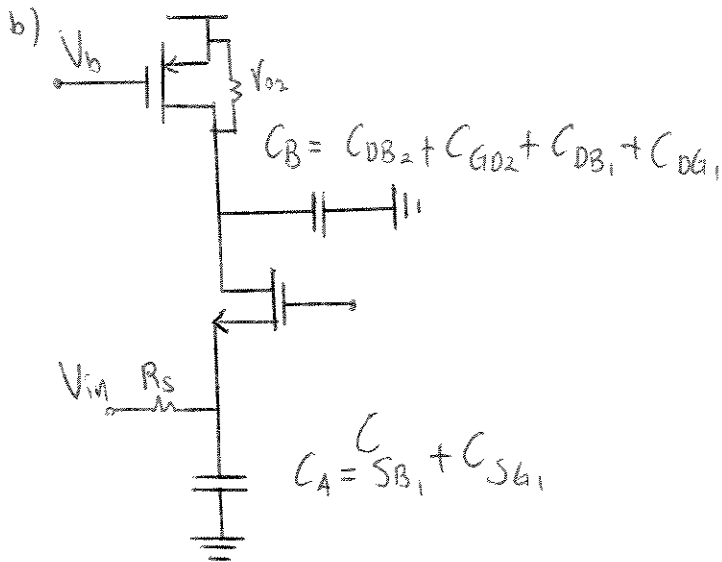

Similar to part a), with  $\frac{1}{g_{m2}}$  replaced by  $V_{o2}$ ,  
and different  $C_B$

$$\text{So } \frac{V_{out}}{V_{in}} = \frac{g_{m1} V_{o2}}{(C_B V_{o2} s + 1)(1 + R_S C_A s + R_S g_{m1})}$$


Where  $C_B = C_{DB2} + C_{GO2} + C_{DB1} + C_{DG1}$

$$C_A = C_{SB1} + C_{SE1}$$



46)

c)

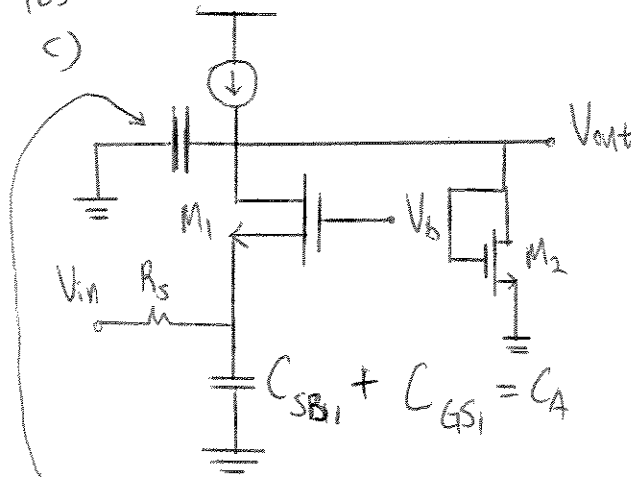

$$C_B = C_{DB1} + C_{GD1} + C_{DB2} + C_{GS2}$$


AC-wise, this circuit is very similar to part a), Its transfer function is the same as part a), except for  $C_B$ .

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} (1/g_{m2})}{(C_B (V_{g_{m2}})^2 s + 1) (1 + R_S C_A s + R_S g_{m1})}$$

Where  $C_B = C_{DB1} + C_{GD1} + C_{DB2} + C_{GS2}$

$$C_A = C_{SB1} + C_{GS1}$$

47)

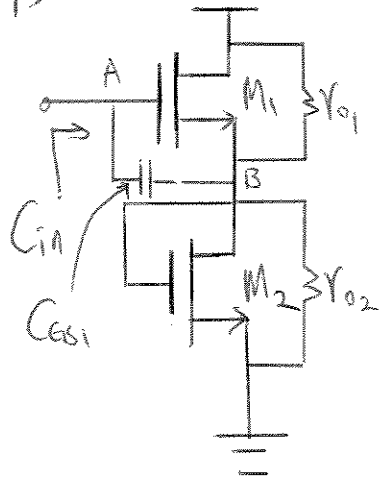

DC gain from A to B:

$$A_V = \frac{\frac{1}{g_{m2}} \parallel R_{O1} \parallel R_{O2}}{\frac{1}{g_{m2}} \parallel R_{O1} \parallel R_{O2} + \frac{1}{g_{m1}}}$$

$$A_V \approx \frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m2}} + \frac{1}{g_{m1}}} = \frac{g_{m1}}{g_{m1} + g_{m2}}$$


since  $g_{m1} r_{O1} \gg 1$

Using Miller's Capacitance:

$$C_{in} = C_{GS1} (1 - A_V) = C_{GS1} \left( 1 - \frac{g_{m1}}{g_{m1} + g_{m2}} \right)$$

$$C_{in} = C_{GS1} \left( \frac{g_{m2}}{g_{m2} + g_{m1}} \right)$$

48)

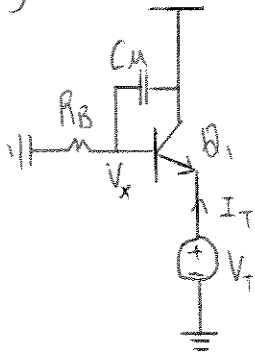

$V_A = \infty$ ,

$\frac{\beta}{\beta+1} \approx 1$ , if  $\beta \gg 1$

$$I_T = -(V_x - V_T) g_m \approx -(V_x - V_T) g_m$$

$$V_x = \frac{I_T}{\beta} \left( R_B \parallel \frac{1}{C_{\mu} s} \right)$$

$$I_T = \left( V_T - \frac{I_T}{\beta} \left( R_B \parallel \frac{1}{C_{\mu} s} \right) \right) g_m$$

$$I_T = g_m V_T - \frac{g_m}{\beta} \left( R_B \parallel \frac{1}{C_{\mu} s} \right) I_T$$


$$I_T \left( 1 + \frac{g_m}{\beta} \left( R_B \parallel \frac{1}{C_{\mu} s} \right) \right) = g_m V_T$$


$$\frac{V_T}{I_T} = \frac{1}{g_m} + \frac{R_B \parallel \frac{1}{C_{\mu} s}}{\beta} = \frac{\beta C_{\mu} R_B \left( s + \frac{\beta + R_B g_m}{\beta C_{\mu} R_B} \right)}{g_m \beta (1 + C_{\mu} R_B s)}$$

Zero:  $\frac{\beta + R_B g_m}{\beta C_{\mu} R_B}$ , Pole:  $\frac{1}{C_{\mu} R_B}$

At DC,  $|Z_{out}| = \frac{1}{g_m} + \frac{R_B}{\beta}$

At very high freq:  $|Z_{out}| = \frac{1}{g_m}$

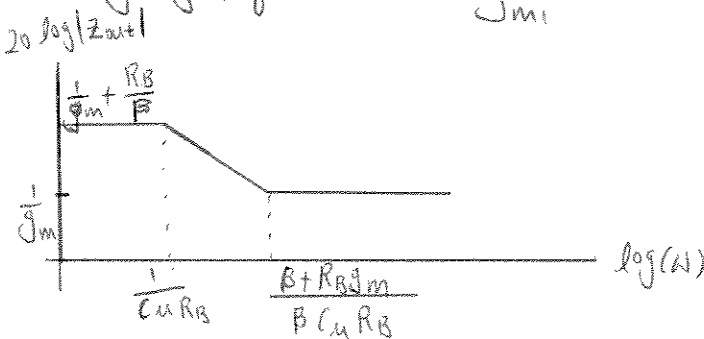

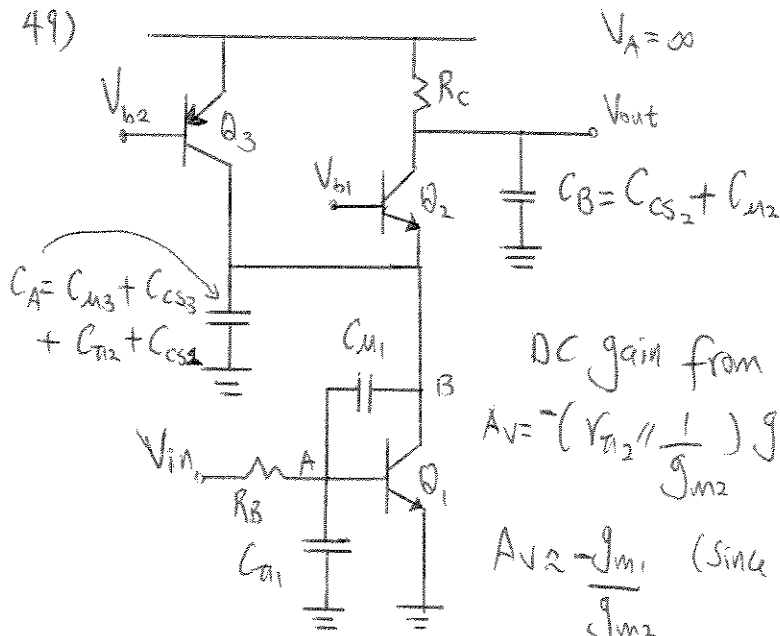

We have  $I_{C2} = 0.25 I_{C1}$ ,  $g_m = \frac{I_C}{V_T} \Rightarrow g_{m2} = 0.25 g_{m1}$

$A_V = -\frac{g_{m1}}{g_{m2}} = -4$ . (If  $I_{C2} = I_{C1}$ ,  $A_V = -1$ )

Applying Miller's Theorem:  $C_{in} = C_{\mu1} + C_{\mu1}(1+4) = C_{\mu1} + 5C_{\mu1}$   
 $C_B = C_A + C_{\mu1}(1+\frac{1}{4}) = C_A + C_{\mu1}(\frac{5}{4})$


$\omega_{p1} (\omega_{pA}) = \frac{1}{(R_B \parallel R_{\mu1}) [C_{\mu1} + 5C_{\mu1}]}$ ,  $\omega_{pB} = \frac{0.25 g_{m1}}{[C_A + \frac{5}{4} C_{\mu1}]}$

$\omega_{pB} = \frac{g_{m2}}{[C_A + \frac{5}{4} C_{\mu1}]}$ ,  $\omega_{pout} = \frac{1}{R_C [C_{CS2} + C_{\mu2}]}$

Where  $C_A = C_{\mu3} + C_{CS3} + C_{\mu2} + C_{CS4}$ .

Since the DC gain is increased, Miller effect is more significant.  
 (In magnitude)

50)

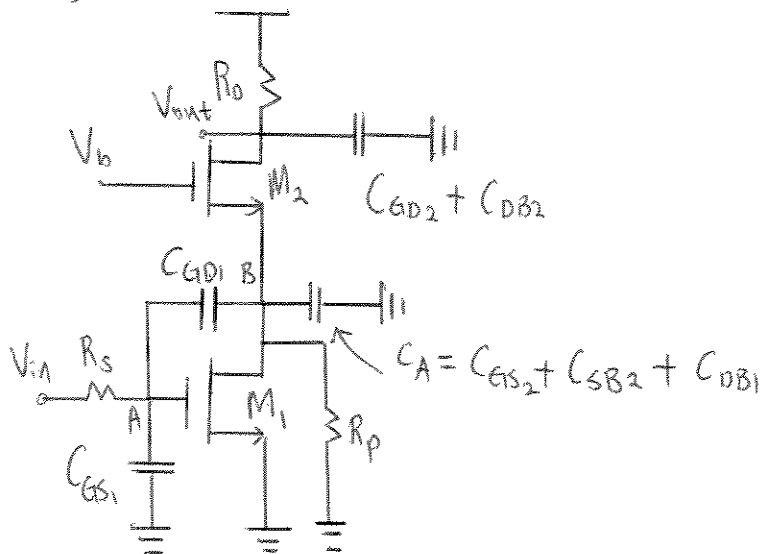

DC gain from A to B is  $-g_{m1} (R_p \parallel \frac{1}{g_{m2}})$


Applying Miller's Theorem:

$$\omega_{pin} (\omega_{pA}) = \frac{1}{R_s (C_{GS1} + C_{GD1} (1 + g_{m1} (R_p \parallel \frac{1}{g_{m2}})))}$$

$$\omega_{pB} = \frac{1}{R_p \parallel \frac{1}{g_{m2}} [C_{GS2} + C_{SB2} + C_{DB1} + C_{GD1} (1 + 1/g_{m1} (R_p \parallel \frac{1}{g_{m2}}))]}$$

$$\omega_{pout} = \frac{1}{R_o (C_{GD2} + C_{DB2})}$$

51)

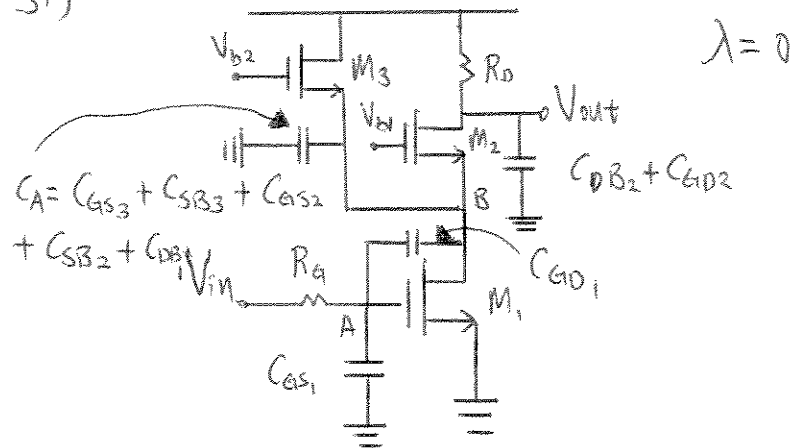

DC gain from A to B:  $-g_{m1} \left( \frac{1}{g_{m3}} \parallel \frac{1}{g_{m2}} \right) = -g_{m1} \left( \frac{1}{g_{m2} + g_{m3}} \right)$

Applying Miller's Theorem:


$$\omega_{p1} (\omega_{pa}) = \frac{1}{R_A \left( C_{as1} + C_{GD1} \left( \frac{g_{m1} + g_{m2} + g_{m3}}{g_{m2} + g_{m3}} \right) \right)}$$

$$\omega_{pB} = \frac{g_{m3} + g_{m2}}{\left( C_A + C_{GD1} \left( \frac{g_{m1} + g_{m2} + g_{m3}}{g_{m1}} \right) \right)}$$

$$\omega_{pout} = \frac{1}{R_D (C_{DB2} + C_{GD2})}$$

Where  $C_A = C_{as3} + C_{sb3} + C_{as2} + C_{sb2} + C_{DB1}$

52)

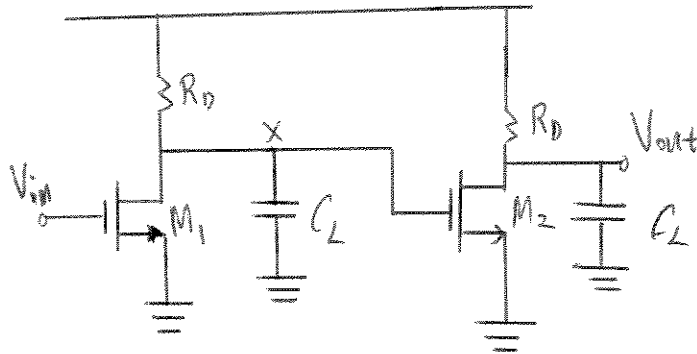

Bias Current = 1mA (each stage)

$$C_L = 50 \text{ fF}$$

$$\mu_n C_{ox} = 100 \mu\text{A/V}^2, A_V = 20, -3\text{dB}: 1\text{GHz}$$

$$\text{DC gain: } (g_m R_D)^2 = 20$$

$$\text{-3dB bandwidth: } 0.10243 / (R_D C_L) = 1\text{GHz}$$

$$\text{Since } C_L = 50 \text{ fF}, R_D = 2048.6 \Omega$$

$$(g_m R_D)^2 = 20 \Rightarrow g_m = 0.002183 = \frac{2I_D}{V_{eff}} \Rightarrow V_{eff} = 0.916\text{V}$$


$$V_{eff} = V_{GS} - V_{th} = 0.916\text{V}$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{eff}) \Rightarrow \frac{W}{L} = \frac{g_m}{\mu_n C_{ox} (V_{eff})} = 23.83$$

$$\text{So } R_D = 2.05\text{K}, C_L = 50\text{fF}$$

$$V_{GS} - V_{th} = 0.916\text{V}, W/L = 23.83$$

53)

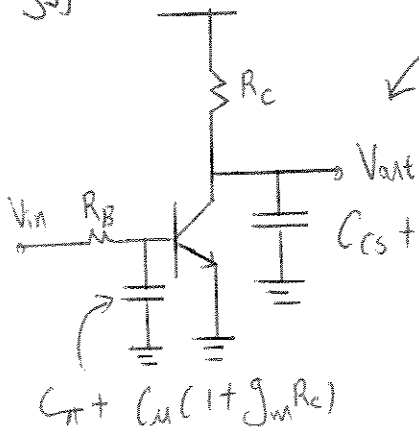

After apply Miller's theorem

$$\omega_{pin} = (2\pi)(500\text{MHz})$$

$$\omega_{pout} = (2\pi)(2\text{G})$$

$$I_c = 1\text{mA}, C_{\pi} = 2\text{pF},$$

$$C_{\mu} = 5\text{fF}, C_{cs} = 1\text{pF}$$

$$V_A = \infty$$

Low frequency Voltage gain: 
$$\frac{V_{out}}{V_{in}} = \frac{-R_c}{\frac{1}{g_m} + \frac{R_B}{\beta + 1}}$$

$$\omega_{pin} = \frac{1}{(R_B // r_{\pi})(C_{\pi} + C_{\mu}(1 + g_m R_c))} = (2\pi)(500\text{MHz})$$

$$\omega_{pout} = \frac{1}{R_c [C_{cs} + (1 + 1/(g_m R_c))C_{\mu}]} = (2\pi)(2\text{G})$$

$$\Rightarrow g_m = 2\pi(2\text{G}) [g_m R_c C_{cs} + g_m R_c C_{\mu} + C_{\mu}]$$

$$\Rightarrow R_c = \left( \frac{g_m}{(2\pi)(2\text{G})} - C_{\mu} \right) / (g_m (C_{cs} + C_{\mu}))$$

$$g_m = \frac{I_c}{V_T} = 0.0386 \frac{1}{\Omega}, R_c = 5296.53 \Omega$$



53)

In order to maximize low frequency gain  $V_{out}/V_{in}$ ,  $R_B$  should be as small as possible (restricted by the input pole location). So  $R_B \approx R_{\pi} \approx R_B$ .

$$\omega_{pin} \approx \frac{1}{R_B (C_{\pi} + C_{\mu} (1 + g_m R_c))} = (2\pi \times 500 \times 10^6)$$

$$g_m R_c = 204.446$$


$$R_B = \frac{1}{\omega_{pin} (C_{\pi} + C_{\mu} (1 + g_m R_c))} \approx 303.95 \Omega$$

So

$$R_B = 303.95 \Omega$$

$$R_c = 5296.53 \Omega$$

54)

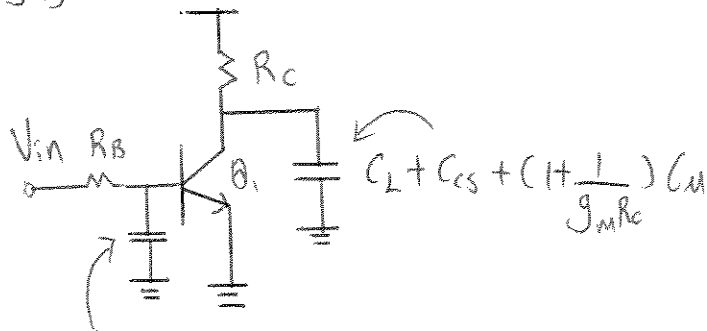

$$C_{\pi} + (1 + g_m R_c) C_M$$

Low freq Voltage gain: 
$$\frac{V_{out}}{V_{in}} = \frac{-R_c}{\frac{1}{g_m} + \frac{R_B}{\beta + 1}}$$

$$\omega_{pout} = \frac{1}{R_c [C_L + C_{CS} + (1 + \frac{1}{g_m R_c}) C_M]} = (2\pi)(2 \text{ GHz})$$

$$g_m = \frac{I_c}{V_T} = 0.0386 \frac{1}{\Omega}$$

$$g_m = (2\pi)(2 \text{ GHz}) [g_m R_c [C_L + C_{CS}] + g_m R_c (C_M + C_{\pi})]$$

$$R_c = \left[ \frac{g_m}{(2\pi)(2 \text{ GHz})} - C_M \right] / (g_m [C_L + C_{CS} + C_{\pi}])$$

$$R_c = 2269.94 \Omega \approx 2.27 \text{ K}\Omega$$


Again, to maximize low freq gain,  $R_B$  should be as small as possible, so  $R_B / (\beta + 1) \approx R_B$

$$\omega_{pin} \approx \frac{1}{R_B (C_{\pi} + C_M (1 + g_m R_c))} = (2\pi)(500 \times 10^6), g_m R_c = 87.62$$

$$R_B = 687.35 \Omega$$

So,  $R_c = 2.27 \text{ K}\Omega, R_B = 687.35 \Omega$

55)

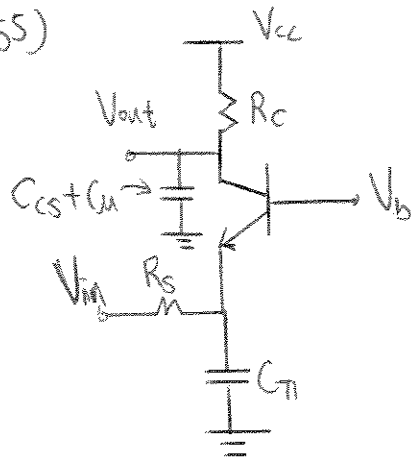

$$V_A = \infty, I_C = 1 \text{ mA}, R_S = 50 \Omega,$$

$$C_{\pi} = 20 \text{ fF}, C_{cs} = 20 \text{ fF}, C_u = 5 \text{ fF}$$

$$-3 \text{ dB bandwidth} = 10 \text{ GHz}$$

Since the output node sees a larger capacitance and resistance than the input, ( $R_C$  usually large for large gain), dominant pole and thus  $-3 \text{ dB}$  bandwidth occurs at the output.


$$\omega_{\text{pout}} = \frac{1}{R_C [C_u + C_{cs}]} = (2\pi)(10 \text{ GHz})$$

$$R_C = 636.62 \Omega, \quad \frac{1}{g_m} = 25.9 \text{ mV} / 1 \text{ mA}$$

$$\text{Maximum achievable gain} = \frac{R_C}{R_S + \frac{1}{g_m}} = 8.4$$

Here we have a tradeoff between gain and bandwidth.

36)

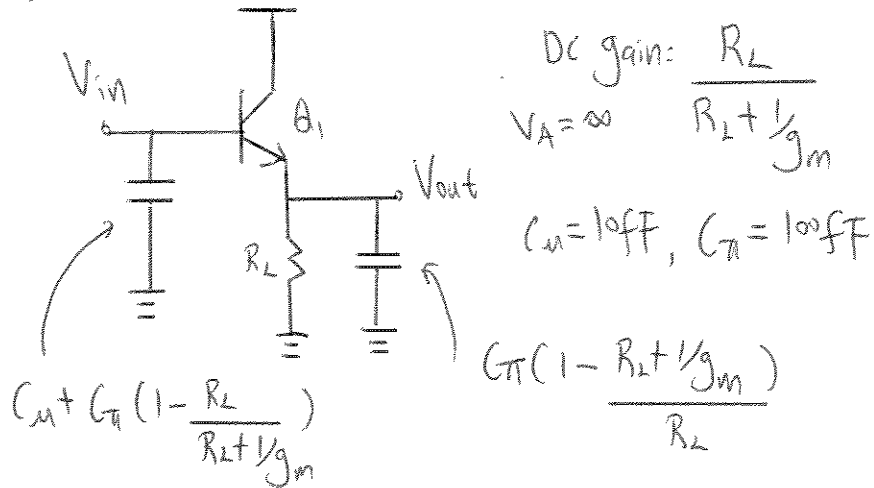

$$C_{in} < 50 \text{ fF} \Rightarrow C_n + C_{\pi} \left(1 - \frac{R_L}{R_L + 1/g_m}\right) < 50 \text{ fF}$$


$$10 \text{ fF} + 100 \text{ fF} \left(1 - \frac{R_L}{R_L + 1/g_m}\right) < 50 \text{ fF}$$

$$100 \text{ fF} \left(1 - \frac{R_L}{R_L + 1/g_m}\right) < 40 \text{ fF}$$

$$\left(\frac{1/g_m}{R_L + 1/g_m}\right) < 0.4$$

$$R_L > \frac{3}{2g_m} = 38.85 \Omega$$

57)

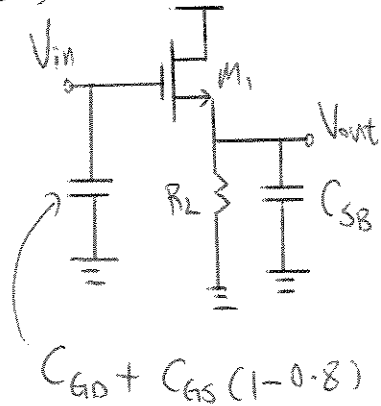

$$R_L = 100\Omega, \quad I_D = 1\text{mA}$$

$$A_V = \frac{V_{out}}{V_{in}} = 0.8 \quad \mu_n C_{ox} = 100 \mu\text{A/V}^2$$

$$L = 0.18 \mu\text{m}, \quad \lambda = 0, \quad C_{GD} \approx 0,$$

$$C_{SB} \approx 0, \quad C_{GS} = \left(\frac{2}{3}\right) WL C_{ox}$$

$$C_{ox} = 12 \text{ fF}/\mu\text{m}^2$$

$$C_{in} = C_{GD} + C_{GS}(0.2), \quad C_{in} = C_{GS}(0.2) = C_{in, \min}$$


$$A_V = \frac{R_L}{R_L + 1/g_m} = 0.8, \quad \frac{1}{g_m} = 25 = \frac{V_{eff}}{2I_D}$$

$$V_{eff} = 50 \text{ mV}, \quad I_D = \frac{1}{2} \frac{W}{L} \mu_n C_{ox} (V_{eff})^2 \Rightarrow W = 1440$$

$$C_{in, \min} = 0.2 C_{GS} = 0.2 \left(\frac{2}{3}\right) WL C_{ox} = 414.72 \text{ fF}$$

$$\text{or } C_{in, \min} = 0.415 \text{ pF}$$

58)

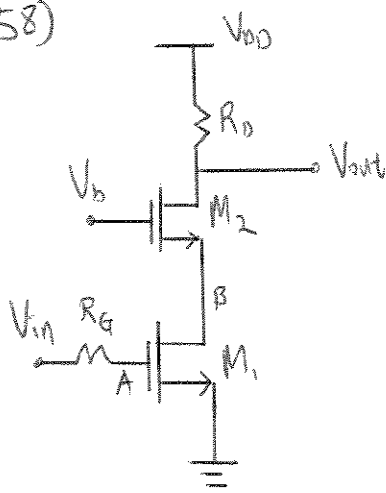

$$\omega_{pin} = 5 \text{ GHz}, \omega_{pout} = 10 \text{ GHz}$$

$$V_{eff} = 200 \text{ mV} (V_{GS} - V_{th}), I_D = 0.5 \text{ mA}$$

$$\lambda = 0, C_{GS} = (2/3) W L C_{ox}$$

$$L = 0.18 \mu\text{m}, \mu_n C_{ox} = 100 \mu\text{A/V}^2$$

$$C_{GD} = W C_o, C_o = 0.2 \text{ fF}/\mu\text{m}$$

$$C_{ox} = 12 \text{ fF}/\mu\text{m}^2$$

$$\text{DC gain from A to B: } -\frac{g_{m1}}{g_{m2}} = 1$$

$$C_{in} = C_{GS} + C_{GD} (1 + g_{m1}/g_{m2}) = C_{GS} + 2 C_{GD}$$

$$I_D = \frac{1}{2} \frac{W}{L} \mu_n C_{ox} (V_{eff})^2 = 0.5 \text{ mA} \Rightarrow \frac{W}{L} = 250$$

$$L = 0.18 \mu\text{m}, W = 45 \mu\text{m}$$

$$\omega_{pin} = (2\pi)(5 \times 10^9) = \frac{1}{R_D \left[ \frac{2}{3} (45)(0.18)(12 \text{ fF}/\mu\text{m}^2) + (0.2)(45)(2) \right]}$$

$$R_D = 384.43 \Omega$$

$$\omega_{pout} = \frac{1}{R_D [0.2 W]} = (10 \times 10^9)(2\pi), W = 45 \mu\text{m}$$

$$\Rightarrow R_D = 1.8 \text{ k}\Omega \quad (1768.4 \Omega) \text{ exact value}$$

$$\text{Gain} = |g_m R_D| = \frac{2 I_D R_D}{V_{eff}} = 8.842$$

59)

$$W_2 = 4W_1, \quad V_{eff2} = \frac{V_{eff1}}{2} \quad (\text{To maintain the current constant})$$

$$V_{eff1} = 200 \text{ mV}, \quad V_{eff2} = 100 \text{ mV} \quad (\text{Assume } V_{eff1} \text{ is not changed})$$

$$\text{DC gain: } -\frac{g_{m1}}{g_{m2}} = -\frac{g_{m1}}{2g_{m1}} = -\frac{1}{2}$$

$$\omega_{pin} = \frac{1}{R_G \left[ \frac{2}{3} W L (C_x + (0.2) W \left( \frac{1}{2} \right) \right]} = (5 \times 10^9) (2\pi)$$


$$W = 45 \mu\text{m}$$

$$\Rightarrow R_G = 459.32 \Omega$$

$$R_0 = \frac{1}{(10 \times 10^9) (2\pi) (0.2) (4) (45)} = 442.097 \Omega$$

$$\text{DC gain: } |g_{m1} R_0| = \frac{2I_D R_0}{V_{eff1}} = 2.2105$$

1. (a)

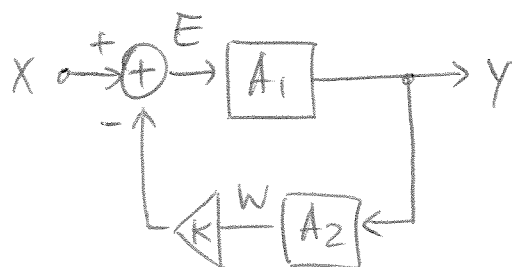


$$Y = A_1 E_1$$

$$= A_1 [X - Y A_2 k]$$

$$\Rightarrow \frac{Y}{X} = \frac{A_1}{1 + k A_1 A_2}$$

(b)

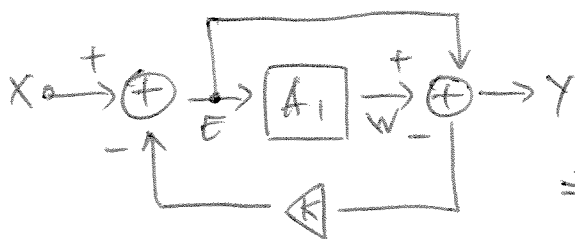


$$Y = E - A_1 W$$

$$= (X - kY) - A_1 (X - kY)$$

$$\Rightarrow \frac{Y}{X} = \frac{1 - A_1}{1 + (1 - A_1)k}$$

(c)

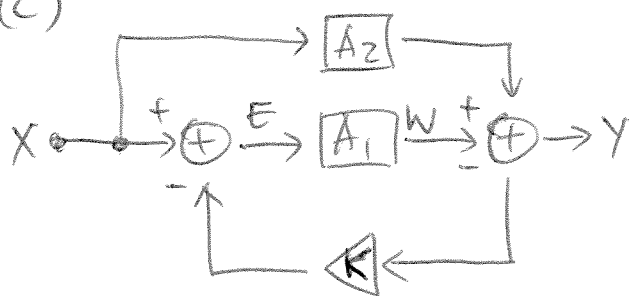


$$Y = X A_2 - W$$

$$= X A_2 - A_1 (X - Y k)$$

$$\Rightarrow \frac{Y}{X} = \frac{A_2 - A_1}{1 - A_1 k}$$

(d)

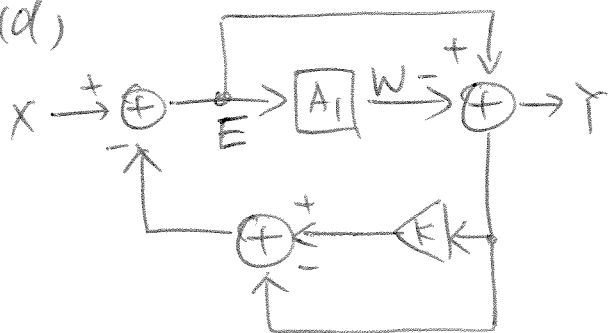

$$Y = E - W$$

$$= (X - (kY - Y)) - A_1 [X - (kY - Y)]$$

$$\Rightarrow \frac{Y}{X} = \frac{(1 - A_1)}{1 + (k - 1)(1 - A_1)}$$



$$2. \quad (a) \quad W = A_2 Y = A_2 [(X - kW)A_1]$$

$$\Rightarrow \frac{W}{X} = \frac{A_1 A_2}{1 + A_1 A_2 k}$$

$$(b) \quad W = A_1 X E = A_1 [X - k(\frac{W}{A_1} - W)]$$

$$\Rightarrow \frac{W}{X} = \frac{A_1}{1 + k(1 - A_1)}$$

$$(c) \quad W = A_1 E = A_1 [X - (A_2 X - W)k]$$

$$\Rightarrow \frac{W}{X} = \frac{A_1 (1 - A_2 k)}{(1 - A_1 k)}$$

$$(d) \quad W = A_1 E = A_1 [X - \left\{ \left( \frac{W}{A_1} - W \right) k - \left( \frac{W}{A_1} - W \right) \right\}]$$

$$\Rightarrow \frac{W}{X} = \frac{A_1}{1 + (k-1)(1-A_1)}$$

$$3. (a) E = X - kA_2A_1E$$
$$\Rightarrow \frac{E}{X} = \frac{1}{1 + kA_2A_1}$$

$$(b) E = X - k[E - A_1E]$$

$$\Rightarrow \frac{E}{X} = \frac{1}{1 + k(1 - A_1)}$$

$$(c) E = X - k[A_2X - A_1E]$$


$$\Rightarrow \frac{E}{X} = \frac{1 - A_2k}{1 - A_1k}$$

$$(d) E = X - \{k[E - A_1E] - [E - A_1E]\}$$

$$\Rightarrow \frac{E}{X} = \frac{1}{1 + (k-1)(1-A_1)}$$

4.

(a)

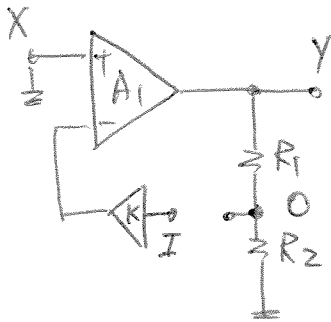


(X is grounded  
in loop-gain calculation)

$$0 = Y \frac{R_2}{R_1 + R_2} = (-IK)A_1 \left( \frac{R_2}{R_1 + R_2} \right)$$

$$\Rightarrow -\frac{0}{I} = \text{Loop Gain} = +KA_1 \left( \frac{R_2}{R_1 + R_2} \right)$$

(b)

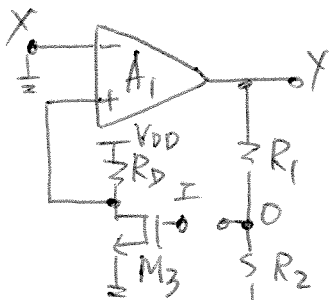


(X is grounded)

$$0 = Y \left( \frac{R_2}{R_1 + R_2} \right) = -I g_{m3} R_D A_1 \left( \frac{R_2}{R_1 + R_2} \right)$$

$$\Rightarrow -\frac{0}{I} = \text{Loop Gain} = +g_{m3} R_D A_1 \left( \frac{R_2}{R_1 + R_2} \right)$$

(c)

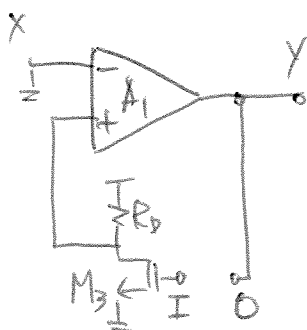


(X is grounded)

$$0 = Y = -I g_{m3} R_D A_1$$

$$\Rightarrow -\frac{0}{I} = \text{Loop Gain} = +g_{m3} R_D A_1$$

(d)

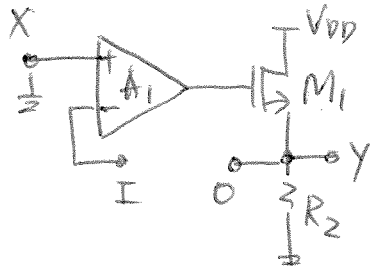

(X is grounded)

$$0 = Y = -I \times \frac{g_{m1} R_2}{1 + g_{m1} R_2} \times A_1$$

$$\Rightarrow -\frac{0}{I} = \text{Loop Gain}$$
$$= + A_1 \frac{g_{m1} R_2}{1 + g_{m1} R_2}$$

5. (a)  $\frac{Y}{X} = \frac{A_{o.l.}}{1 + \text{Loop Gain}} = \frac{A_1}{1 + A_1 K \left( \frac{R_2}{R_1 + R_2} \right)}$

(b)  $\frac{Y}{X} = \frac{A_1}{1 + g_{m3} R_D A_1 \left( \frac{R_2}{R_1 + R_2} \right)}$

(c)  $\frac{Y}{X} = \frac{A_1}{1 + g_{m3} R_D A_1}$

(d)  $\frac{Y}{X} = \frac{A_1}{1 + A_1 \left( \frac{g_{m1} R_2}{1 + g_{m1} R_2} \right)}$

b.  $A_1 = 500$   
 $R_1/R_2 = 7$


$$\frac{Y}{X} \approx 1 + \frac{R_1}{R_2} = 8$$

$$\Rightarrow \frac{R_2}{R_1 + R_2} = \frac{1}{8} = K$$

$$E = \frac{X}{1 + KA_1} = \frac{2 \text{ mV}}{1 + 500/8} \approx 0.031 \text{ mV}$$

$\therefore$  Amplitude of feedback waveform  
 $= X - E \approx 1.969 \text{ mV}$

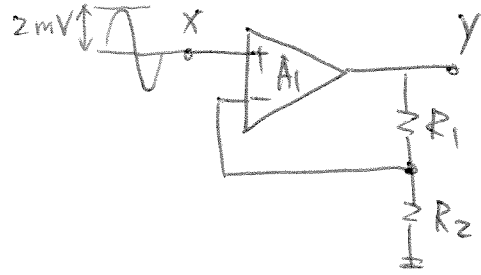Amplitude of output waveform  
 $= X \frac{A_1}{1 + KA_1} \approx 15.75 \text{ mV}$



$$1. \quad A_{CL} = \frac{A_1}{1+A_1K}$$

$$\frac{dA_{CL}}{dA_1} = \frac{1}{(1+A_1K)^2} \Rightarrow dA_{CL} = \frac{dA_1}{(1+A_1K)^2}$$

$$\begin{aligned} \Rightarrow \frac{dA_{CL}}{A_{CL}} &= \frac{dA_{CL}}{\left(\frac{A_1}{1+A_1K}\right)} = dA_1 \left(\frac{1+A_1K}{A_1}\right) \left(\frac{1}{(1+A_1K)^2}\right) \\ &= \frac{(dA_1/A_1)}{(1+A_1K)} \end{aligned}$$

This equation implies that for a fractional change in  $A_{CL}$ , it is reduced by  $(1+A_1K)$  compared to a fractional change in  $A_1$ .

$$\Rightarrow 0.01 > \frac{0.2}{1+A_1K} \Rightarrow A_1K > 19$$

$$8. A_{OL} = -g_m r_{o1} \quad (\text{max gain})$$

$$= -\frac{2}{\lambda V_{eff}}$$

$$A_{CL} = \frac{A_{OL}}{1 + A_{OL}K}$$

$$\frac{dA_{CL}}{d\lambda} = \frac{d}{d\lambda} \left( \frac{A_{OL}}{1 + A_{OL}K} \right) = \frac{\frac{2}{\lambda^2 V_{eff}}}{(1 + A_{OL}K)^2} = \frac{-A_{OL} \times \frac{1}{\lambda}}{(1 + A_{OL}K)^2}$$

$$\Rightarrow \frac{dA_{CL}}{A_{CL}} = \frac{-A_{OL} \times \frac{d\lambda}{\lambda}}{(1 + A_{OL}K)^2} \times \frac{(1 + A_{OL}K)}{A_{OL}} = \frac{-\frac{d\lambda}{\lambda}}{(1 + A_{OL}K)}$$

$\Rightarrow$  This implies a change in  $\lambda$  ( $\frac{d\lambda}{\lambda}$ ) leads to a change in  $A_{CL}$  ( $\frac{dA_{CL}}{A_{CL}} = \frac{d\lambda}{\lambda} \cdot \frac{1}{(1 + \text{Loop Gain})}$ ) in the opposite direction (i.e. the sign)

$$590 > \frac{20\%}{1 + A_{OL}K} \Rightarrow \text{Loop Gain} = A_{OL}K > 3$$



9. From the question,

$$(1-10\%)A_0 = |A(j\omega')| \quad \text{where } \omega' = \text{-1-dB bandwidth frequency}$$

$$0.9A_0 = \frac{A_0}{|1+j\frac{\omega'}{\omega_0}|} = \frac{A_0}{\sqrt{1+(\frac{\omega'}{\omega_0})^2}}$$

$$\Rightarrow \omega' \cong 0.48\omega_0$$

$\Rightarrow$  This is the open-loop -1dB bandwidth.

Similarly,

$$0.9 \frac{A_0}{1+LG} = \left| \frac{Y}{X}(j\omega'') \right| \quad \text{where } \omega'' = \text{-1dB bandwidth frequency}$$



$$0.9 \frac{A_0}{1+LG} = \frac{\frac{A_0}{1+LG}}{\left| 1 + j \frac{\omega''}{\omega_0(1+LG)} \right|} = \frac{\frac{A_0}{1+LG}}{\sqrt{1 + \left[ \frac{\omega''}{\omega_0(1+LG)} \right]^2}}$$

L.G = Loop Gain

$$\Rightarrow \omega'' \cong 0.48\omega_0(1+LG)$$

$\therefore$  -1dB bandwidth is boosted (expected) by  $(1+LG)$  in closed-loop measurement.

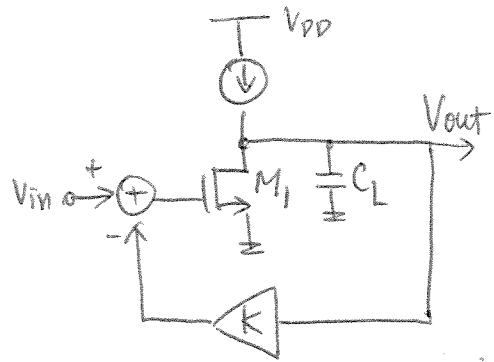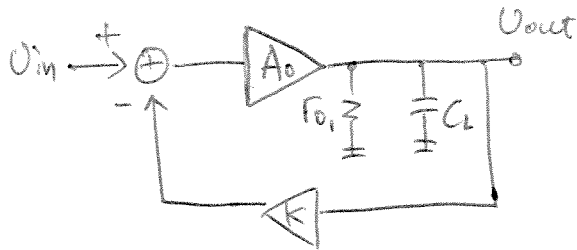10. An equivalent circuit is shown below:



Open-loop transfer function (without feedback):

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_p}} = \frac{-g_{m1} r_{o1}}{1 + \frac{s}{r_{o1} C_L}}$$

$$\text{Loop Gain} = A_0 k = g_{m1} r_{o1} k$$

⇒ Closed-loop -3dB bandwidth


$$= B = (r_{o1} C_L)(1 + A_0 k) = r_{o1} C_L (1 + g_{m1} r_{o1} k)$$

$$\therefore k = \left( \frac{B}{r_{o1} C_L} - 1 \right) \times \frac{1}{g_{m1} r_{o1}}$$

11.

## Feedforward System

$M_1$  &  $R_D$  (common-gate stage)

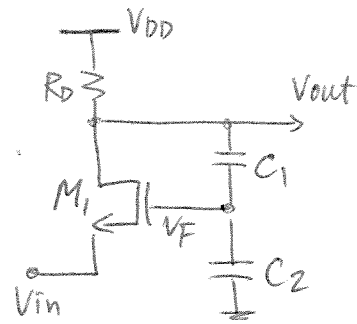

## Sense Mechanism (Feedback):

$C_1 + C_2$  (capacitive divider)

$$\Rightarrow V_F = \frac{C_1}{C_2 + C_1} \times V_{out}$$

Comparison Mechanism:  $M_1$  itself.

$$\text{Open-loop gain} = A_o = g_m R_D$$

$$\begin{aligned} \text{Closed-loop gain} &= \frac{V_{out}}{V_{in}} = \frac{A_o}{1 + K A_o} \\ &= \frac{g_m R_D}{1 + \frac{C_1}{C_1 + C_2} g_m R_D} \end{aligned}$$

$$\text{Open-loop } r_{in} = \frac{1}{g_m}$$


$$r_{out} = R_D$$

$$\begin{aligned} \text{Closed-loop } r_{in} &= r_{in,ol} \times (1 + K A_o) \\ &= \frac{1}{g_m} \left( 1 + \frac{C_1}{C_1 + C_2} g_m R_D \right) \end{aligned}$$

$$r_{out} = \frac{r_{out,ol}}{(1 + K A_o)} = \frac{R_D}{1 + \frac{C_1}{C_1 + C_2} g_m R_D}$$

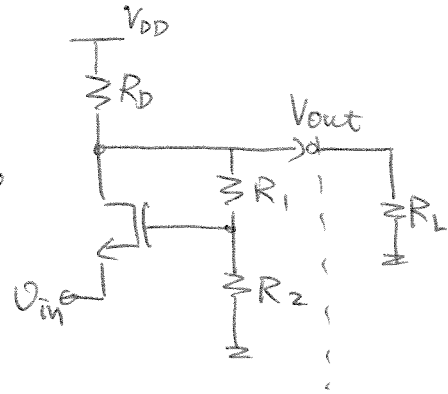12.

Given:  $\frac{\text{Gain}_{\text{loaded}} - \text{Gain}_{\text{unloaded}}}{\text{Gain}_{\text{unloaded}}} = 10\%$   
 $= 0.1$



$$\text{Gain}_{\text{unloaded}} \cong \frac{g_m R_D}{1 + \frac{R_2}{R_1 + R_2} g_m R_D} \quad (\text{assume } R_1 + R_2 \gg R_D)$$

$$\text{Gain}_{\text{loaded}} = \frac{g_m (R_D \parallel R_L)}{1 + \frac{R_2}{R_1 + R_2} g_m (R_D \parallel R_L)}$$

$$\therefore 0.1 = \frac{\frac{g_m R_D}{1 + \frac{R_2}{R_1 + R_2} g_m R_D} - \frac{g_m (R_D \parallel R_L)}{1 + \frac{R_2}{R_1 + R_2} g_m (R_D \parallel R_L)}}{\frac{g_m R_D}{1 + \frac{R_2}{R_1 + R_2} g_m R_D}}$$

After solving for  $R_L$ :

$$R_L = \frac{g_m R_D}{1 + \left(\frac{R_2}{R_1 + R_2}\right) g_m R_D}$$

$$13. \text{ Gain at } x_1 = \frac{500}{1+500K}$$

$$\text{Gain at } x_2 = \frac{420}{1+420K}$$

$$\Rightarrow \frac{\frac{500}{1+500K} - \frac{420}{1+420K}}{\frac{500}{1+500K}} < 0.05$$

$$\Rightarrow K > \frac{11}{2100}$$

$$A_{x_1} = \frac{500}{1+500(K)} = \frac{2625}{19} \approx 138.16$$

$$A_{x_2} = \frac{420}{1+420(K)} = \frac{525}{4} \approx 131.25$$

$$14. \quad y = \alpha_1 x - \alpha_3 x^3$$

$$(a) \quad \frac{\partial y}{\partial x} = \alpha_1 - 3\alpha_3 x^2$$

$$\left. \frac{\partial y}{\partial x} \right|_{x=0} = \alpha_1$$



$$\left. \frac{\partial y}{\partial x} \right|_{x=\Delta x} = \alpha_1 \quad (\text{around } x=0)$$

$$(b) \quad \text{Closed-loop } \left. \right|_{x=0} = \frac{\alpha_1}{1 + \alpha_1 k}$$




$$\text{Closed-loop } \left. \right|_{x=\Delta x} = \frac{\alpha_1}{1 + \alpha_1 k} \quad (\text{around } x=0)$$

15.




(a)

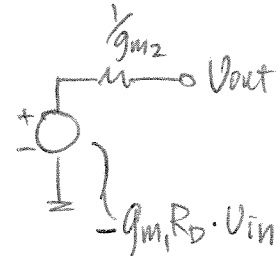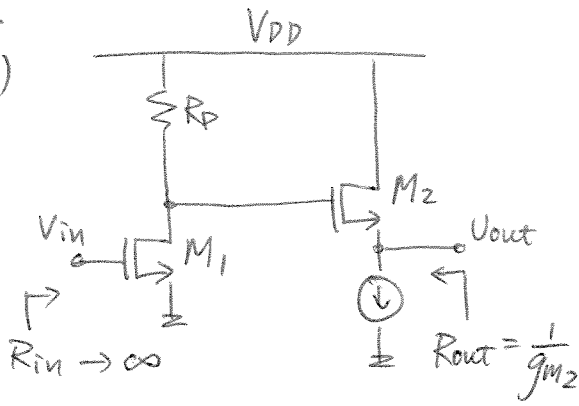




(b)

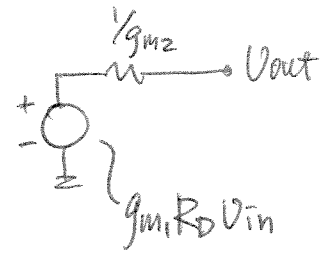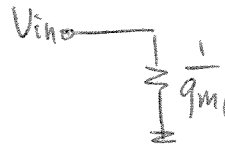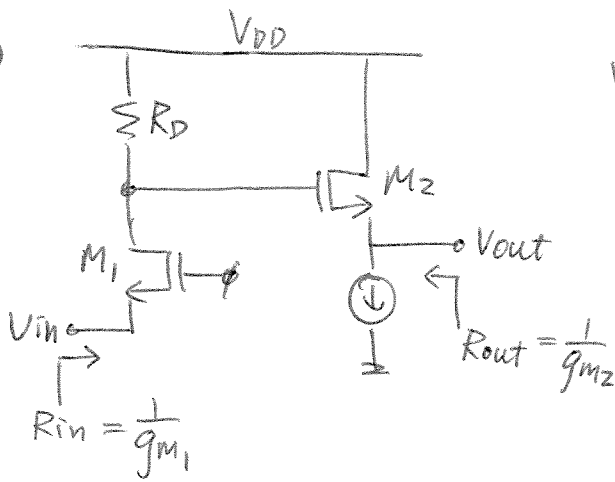

(c)

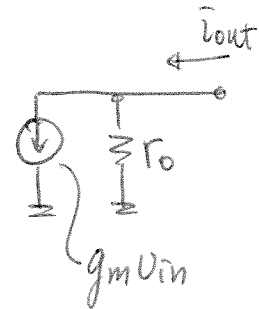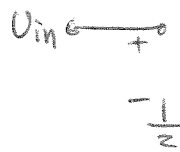
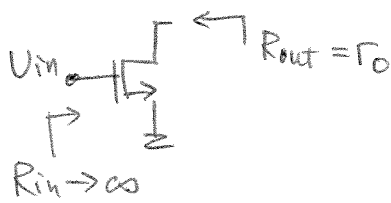


(d)

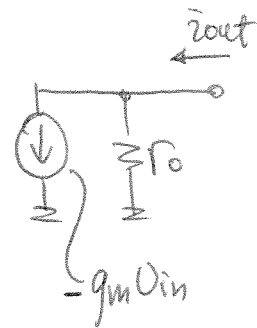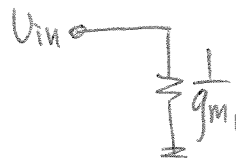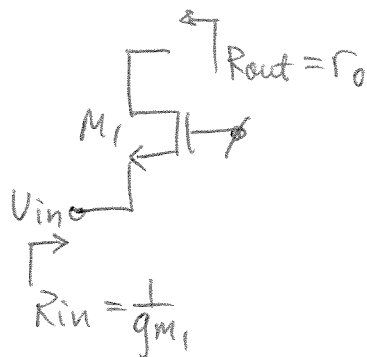


16.

$\lambda > 0$

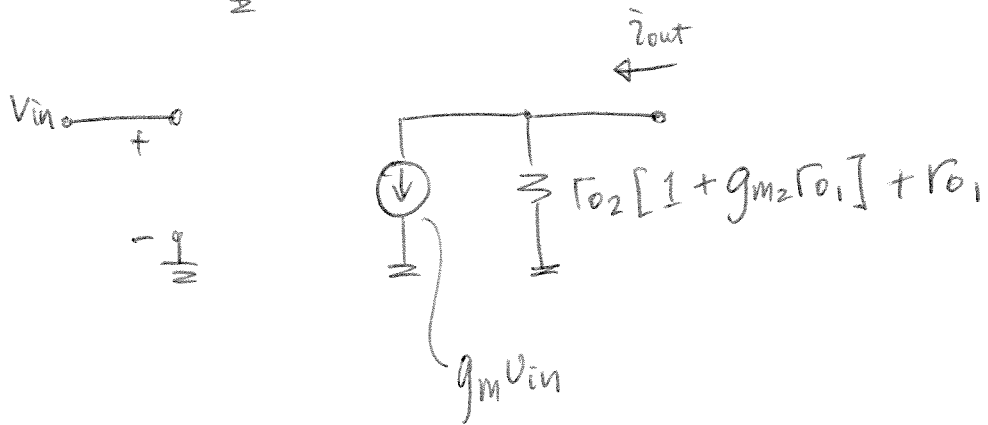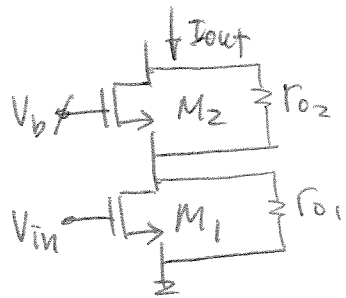



17.

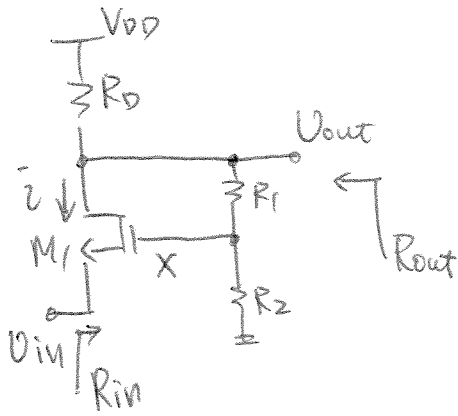


$$-V_{out} = \bar{i} [R_D \parallel (R_1 + R_2)]$$

$$\bar{i} = g_{m1}(V_x - V_{in}) = g_{m1} \left( V_{out} \times \frac{R_2}{R_1 + R_2} - V_{in} \right)$$

Combining the equations above yields:

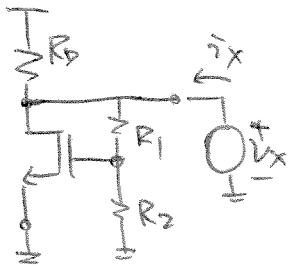
$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} [R_D \parallel (R_1 + R_2)]}{1 + \frac{R_2}{R_1 + R_2} g_{m1} [R_D \parallel (R_1 + R_2)]} \triangleq A_v$$



By KCL,

$$\bar{i}_x = \frac{V_x}{R_1 + R_2} + \frac{V_x}{R_D} + g_{m1} \left( V_x \frac{R_2}{R_1 + R_2} \right)$$
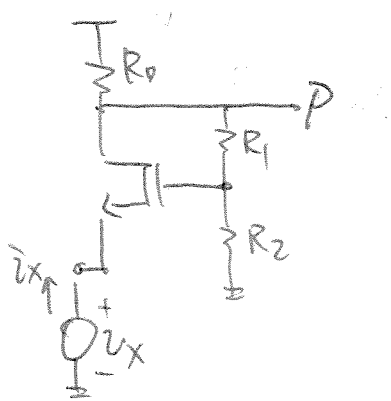
$$\Rightarrow \frac{V_x}{\bar{i}_x} = R_{out} = [(R_1 + R_2) \parallel R_D] \left[ 1 + g_{m1} \frac{R_2}{R_1 + R_2} (R_D \parallel (R_1 + R_2)) \right]$$



By KCL,

$$\bar{i}_x = g_{m1} \left( v_x - v_p \frac{R_2}{R_1 + R_2} \right)$$



$$\Rightarrow v_p = \left( v_x - \frac{\bar{i}_x}{g_{m1}} \right) \left( \frac{R_1 + R_2}{R_2} \right) \quad \text{--- (1)}$$

$$\bar{i}_x = \frac{v_p}{R_D \parallel (R_1 + R_2)} \quad \text{--- (2)}$$

Substitute (1) into (2) & solve for  $\frac{v_x}{\bar{i}_x}$ :


$$\frac{v_x}{\bar{i}_x} = R_{in} = \frac{1}{g_{m1}} \left[ 1 + g_{m1} \left\{ R_D \parallel (R_1 + R_2) \right\} \frac{R_2}{R_1 + R_2} \right]$$

Model:

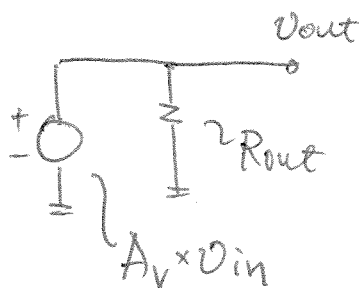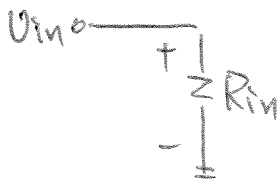

18. (a) Sense Mechanism : Current from  $M_3$   
Return Mechanism : Voltage to Gate of  $M_2$ .
- (b) Sense Mechanism : Voltage output ( $M_3$ )  
Return Mechanism : Voltage to Gate of  $M_2$ .
- (c) Sense Mechanism : Current from  $M_3$   
Return Mechanism : Voltage to Gate of  $M_2$ .
- (d) Sense Mechanism : Current from  $M_3$   
Return Mechanism : Voltage to Gate of  $M_2$ .
- (e) Sense Mechanism : Voltage Divider ( $\frac{R_2}{R_1+R_2}$ )  
Return Mechanism : Voltage to Gate of  $M_2$ .
- (f) Sense Mechanism : From Common Source of  $M_3$   
Return Mechanism : Voltage to Gate of  $M_2$ .

19. (a)

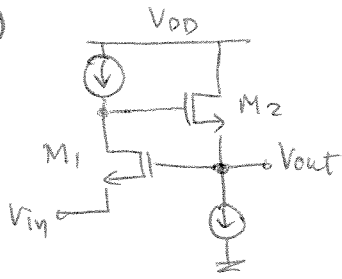


Sense Mechanism:

Voltage sensing at  $V_{out}$ .

Return Mechanism:

Voltage to Gate of  $M_1$ .

(b)

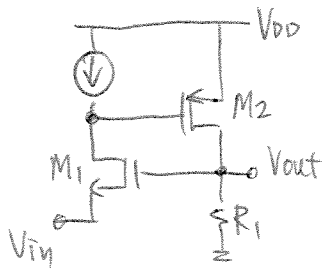


Sense Mechanism:

Voltage output from  $M_2$ .

Return Mechanism:

Voltage to Gate of  $M_1$ .

(c)

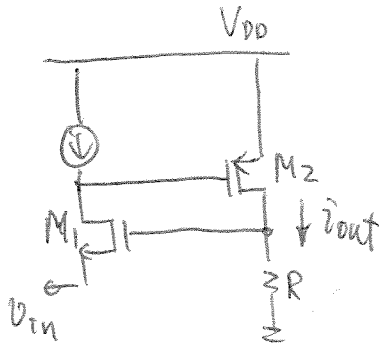


Sense Mechanism:

$R_1$

Return Mechanism:

Voltage to Gate of  $M_1$ .

(d)

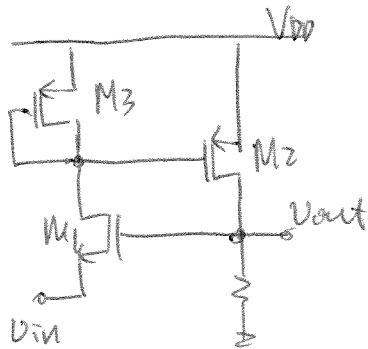

Sense Mechanism:


Voltage output of  $M_2$

Return Mechanism:

Voltage to Gate of  $M_1$

20.

(a)

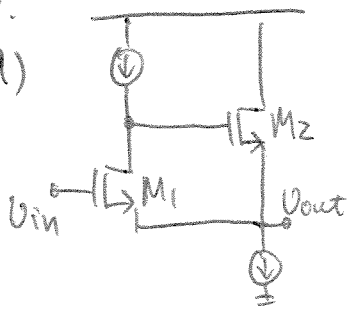


Sense Mechanism:

Voltage output of  $M_2$

Return Mechanism:

Voltage to Source of  $M_1$

(b)

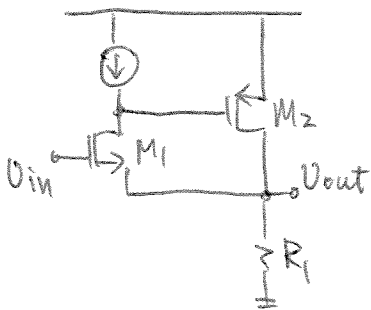


Sense Mechanism:

Voltage output of  $M_2$

Return Mechanism:

Voltage to Source of  $M_1$

(c)

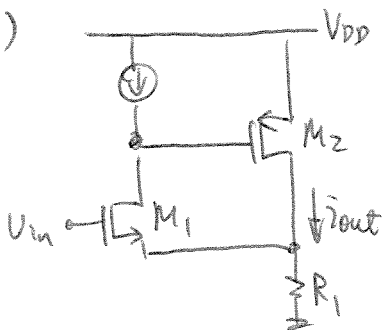


Sense Mechanism:

Current through  $R_1$ .

Return Mechanism:

$i_{out} \times R_1$  to Source of  $M_1$ .

(d)

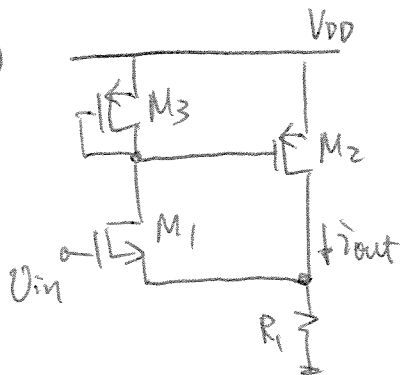

Sense Mechanism:

Current through  $R_1$ .

Return Mechanism:

$i_{out} \times R_1$  to Source of  $M_1$


21. (a)

Sense Mechanism:

Gate of  $M_2$  (Voltage)

Return Mechanism:

Current output of  $M_2$ .

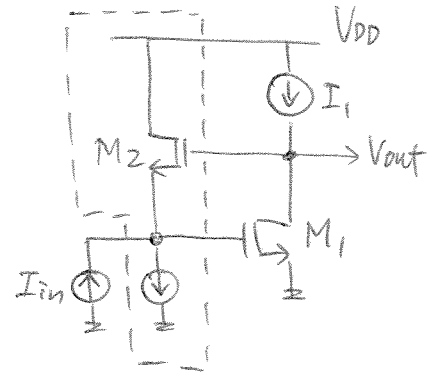


(b)

Sense Mechanism:

Gate of  $M_2$  (Voltage)

Return Mechanism:

Current output of  $M_2$ .

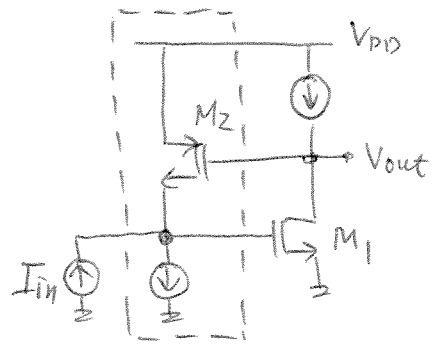


(c)

Sense Mechanism:

Source of  $M_2$  (Voltage)

Return Mechanism:

Current output of  $M_2$

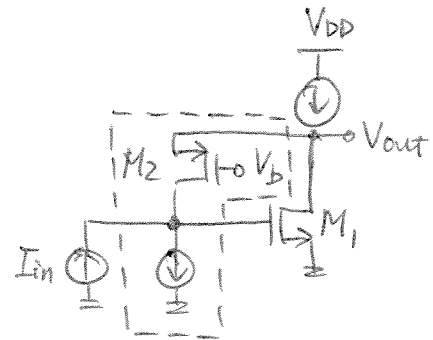


(d) Sense Mechanism:

Gate of  $M_2$  (Voltage)

Return Mechanism:

Current output of  $M_2$

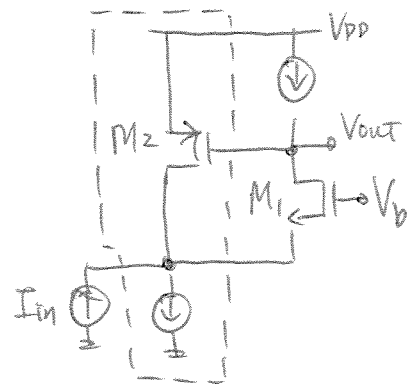


22.

(a) Sense Mechanism:


Resistor ( $R_F$ ) - Voltage

Return Mechanism:

Current through  $R_F$ .

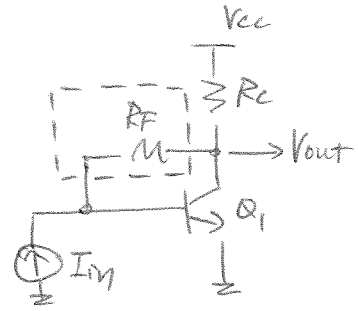

(b)

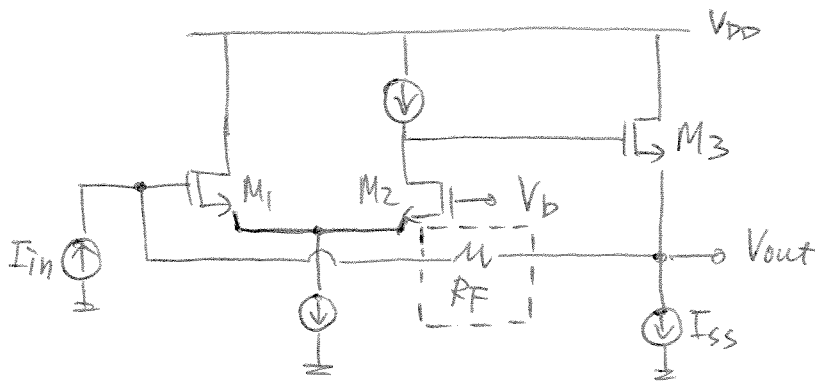


Sense Mechanism:

Resistor ( $R_F$ ) - Voltage

Return Mechanism:

Current through  $R_F$

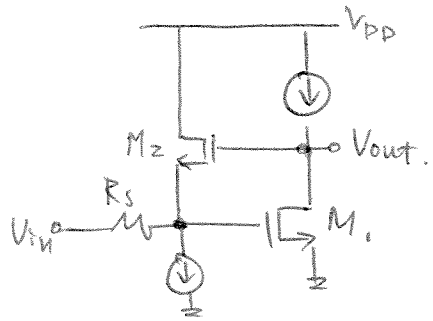23. First, recognize that  
 (a) both input & output are voltages.



\*  $V_{in}$  primarily drives the Gate of  $M_1$ .

Sequence: Suppose  $V_{in}$  increases by  $\Delta V_{in}$

$\Rightarrow V_{out}$  drops by  $+g_{m1} \Delta V_{in} \times r_{o1}$  (Common-Source)

$\Rightarrow$  Source of  $M_2$  decreases by same amount (Source follower)

$\therefore V_{in} \uparrow \Rightarrow V_{M_2, D} \downarrow \Rightarrow V_{M_1, G} \downarrow$   
 $\Rightarrow$  effective  $V_{in}$  driving  $M_{1,G} \downarrow$

$\Rightarrow$  negative feedback

(b)  $V_{in} \uparrow \Rightarrow V_{out} \downarrow \Rightarrow V_{M_2, G} \uparrow$

$\Rightarrow$  effective  $V_{in}$  driving  $M_{1,G} \uparrow$

$\Rightarrow$  positive feedback.



$$(c) \quad v_{in} \uparrow \Rightarrow v_{out} \downarrow \Rightarrow v_{M1, G} \downarrow$$

$\Rightarrow$  effective  $v_{in}$  driving  $M1, G \downarrow$

$\Rightarrow$  negative feedback.


$$(d) \quad v_{in} \uparrow \Rightarrow v_{out} \uparrow \text{ (common-base, } M1, S)$$

$\Rightarrow v_{M1, S} \downarrow$

$\Rightarrow$  effective  $v_{in}$  driving  $M1, S \downarrow$

$\Rightarrow$  negative feedback.

24.

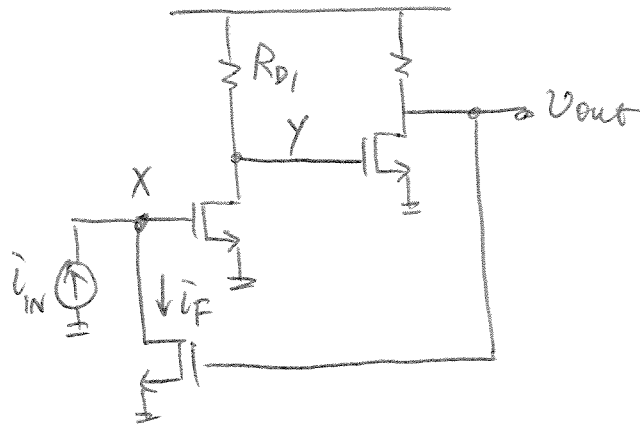

$i_{IN} \uparrow \Rightarrow v_X \uparrow \Rightarrow v_Y \downarrow \Rightarrow v_{out} \uparrow \Rightarrow i_F \uparrow$   
 $\Rightarrow$  effective  $v_X \downarrow$   
 $\Rightarrow$  negative feedback.

25.

Figure 12.79

↑ = increases by  
↓ = decreases by

(a)  $V_{in} \uparrow \Rightarrow V_{G,M3} \uparrow$

$\Rightarrow V_{out} \uparrow$  same amount (Emitter Follower)

$\Rightarrow$  effective  $V_{in} (V_{G,M1} - V_{G,M2}) \downarrow$

$\Rightarrow$  Negative feedback.

(b)  $V_{in} \uparrow \Rightarrow V_{G,M3} \uparrow$

$\Rightarrow V_{out} \uparrow$  by  $\Delta V_{G,M3} \times g_{m3} (\tau_{o3} \parallel R_1)$

$\Rightarrow$  effective  $V_{in} (V_{G,M1} - V_{G,M2}) \downarrow$

$\Rightarrow$  Negative feedback.

(c) Same as (b)

(d) Same as (a)

(e)  $V_{in} \uparrow \Rightarrow V_{out} \uparrow$

$\Rightarrow V_{G,M2} \uparrow$  by  $\Delta V_{out} \times \frac{R_2}{R_1 + R_2}$

$\Rightarrow$  effective  $V_{in} (V_{G,M1} - V_{G,M2}) \downarrow$

$\Rightarrow$  Negative feedback.

- (f)  $V_{in} \uparrow \Rightarrow V_{G,M_3} \uparrow$   
 $\Rightarrow V_{out} \uparrow$  (Common-Source Stage)  
 $\Rightarrow$  effective  $V_{in}$  ( $V_{G,M_1} - V_{G,M_2}$ )  $\downarrow$   
 $\Rightarrow$  Negative feedback.

Figure 12.80

- (a)  $V_{in} \uparrow \Rightarrow V_{G,M_2} \uparrow$  (Common-Gate)  
 $\Rightarrow V_{out} \uparrow$  (Source Follower)  
 $\Rightarrow$  effective  $V_{eff}$  ( $V_{in} - V_{out}$ )  $\downarrow$   
 $\Rightarrow$  Negative feedback.

- (b)  $V_{in} \uparrow \Rightarrow V_{G,M_2} \uparrow$  (Common-Gate)  
 $\Rightarrow V_{out} \uparrow$  (Common Source)  
 $\Rightarrow$  effective  $V_{eff}$  ( $V_{in} - V_{out}$ )  $\downarrow$   
 $\Rightarrow$  Negative feedback.

(c) Same as (b)

- (d)  $V_{in} \uparrow \Rightarrow V_{G,M_2} \uparrow$  (Common-Gate)  
 $\Rightarrow V_{out} \uparrow$  (Common Source)  
 $\Rightarrow$  effective  $V_{eff}$  ( $V_{in} - V_{out}$ )  $\downarrow$   
 $\Rightarrow$  Negative feedback.

Figure 12.81

(a)  $V_{in} \uparrow \Rightarrow V_{G, M_2} \downarrow$  (Common Source)

$\Rightarrow V_{out} \uparrow$  (Source Follower)

$\Rightarrow$  effective  $V_{in}$  ( $V_{in} - V_{out}$ )  $\uparrow$

$\Rightarrow$  Positive feedback.

(b)  $V_{in} \uparrow \Rightarrow V_{G, M_2} \downarrow$  (Common Source)

$\Rightarrow V_{out} \uparrow$  (Common Source)

$\Rightarrow$  effective  $V_{in}$  ( $V_{in} - V_{out}$ )  $\downarrow$

$\Rightarrow$  Negative feedback.

(c) Same as (b) ( $V_{out} = I_{out} \times R_1$ )

(d)  $V_{in} \uparrow \Rightarrow V_{G, M_2}$  (Common Source)

$\Rightarrow V_{out} \uparrow$  (Common Source)

$\Rightarrow$  effective  $V_{in}$  ( $V_{in} - V_{out}$ )  $\downarrow$

$\Rightarrow$  Negative feedback.

## Figure 12.82

- (a)  $\bar{i}_{in} \uparrow \Delta \Rightarrow V_{out} \downarrow$  (Common Source,  
through current gain of  $M_1$ )  
 $\Rightarrow \bar{i}_{D, M_2} \downarrow$  (Source Follower,  $M_2$ )  
 $\Rightarrow$  Counteracts the effect of  $\bar{i}_{in}$   
 $\Rightarrow$  Negative feedback.
- (b)  $\bar{i}_{in} \uparrow \Delta \Rightarrow V_{out} \downarrow$  (Common Source,  
through current gain of  $M_1$ )  
 $\Rightarrow \bar{i}_{D, M_2} \uparrow$  (Common Source,  $M_2$ )  
 $\Rightarrow$  Enhances  $V_{out}$  through  $M_1$   
 $\Rightarrow$  Positive feedback.
- (c)  $\bar{i}_{in} \uparrow \Delta \Rightarrow V_{out} \downarrow$  (Common Source,  
through current gain of  $M_1$ )  
 $\Rightarrow \bar{i}_{D, M_2} \downarrow$  (Common Gate)  
 $\Rightarrow$  Counteracts the effect of  $\bar{i}_{in}$   
 $\Rightarrow$  Negative feedback.
- (d)  $\bar{i}_{in} \uparrow \Delta \Rightarrow V_{out} \uparrow$  (Common Gate)  
 $\Rightarrow \bar{i}_{D, M_2} \downarrow$  (Common Source)  
 $\Rightarrow$  Counteracts the effect of  $\bar{i}_{in}$   
 $\Rightarrow$  Negative feedback.

Figure 12.83

(a)  $\bar{i}_{IN} \uparrow \Delta \Rightarrow V_{out} \downarrow$  (Common Emitter)

$\Rightarrow R_F$  demands more current momentarily

$\Rightarrow$  effective  $\bar{i}_{IN}$  into  $Q_1 \downarrow$

$\Rightarrow V_{out} \uparrow$

$\Rightarrow$  Negative feedback.

(b)  $\bar{i}_{IN} \uparrow \Delta \Rightarrow V_{G_1, M_3} \uparrow$  (Diff Pair Action)

$\Rightarrow V_{out} \uparrow$  (Source Follower)

$\Rightarrow V_{out}$  "tracks" behavior of  $\bar{i}_{IN}$

(Current demanded by  $R_F$  from  $\bar{i}_{IN} \uparrow$ )

$\Rightarrow$  Positive feedback.

2b.

(Without feedback)

$$\frac{V_{out}}{V_{in}} = A_{o.L.} = g_m R_D$$


Feedback factor,  $k$ :

$$k = \frac{R_2}{R_1 + R_2}$$

$$\Rightarrow A_{c.L.} = \left. \frac{V_{out}}{V_{in}} \right|_{c.L.} = \frac{A_{o.L.}}{1 + A_{o.L.} \cdot k} = \frac{g_m R_D}{1 + \frac{R_2}{R_1 + R_2} g_m R_D}$$

$$R_{in, closed} = \frac{1}{g_{m1}} \left( 1 + \frac{R_2}{R_1 + R_2} g_m R_D \right)$$
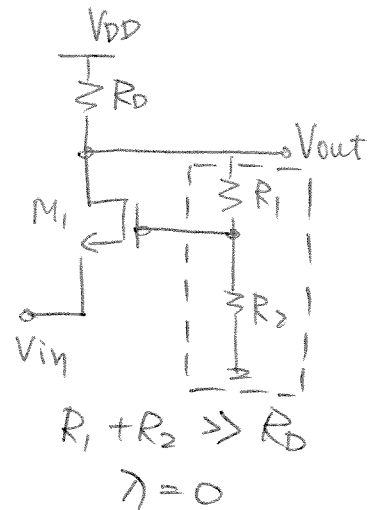
$$R_{out, closed} = \frac{R_D}{1 + \frac{R_2}{R_1 + R_2} g_m R_D}$$






27.

(Without feedback)

$$A_{o.L.} = g_m R_D$$

Feedback factor,  $k$  :

$$k = \frac{C_1}{C_1 + C_2}$$

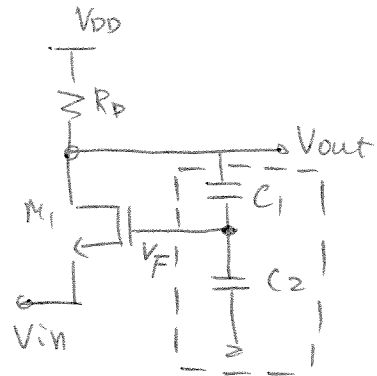


$\lambda = 0$   
 $C_1, C_2$  small.

$$\Rightarrow A_{c.L.} = \left. \frac{V_{out}}{V_{in}} \right|_{c.L.} = \frac{A_{o.L.}}{1 + A_{o.L.} k} = \frac{g_m R_D}{1 + \frac{C_1}{C_1 + C_2} g_m R_D}$$

$$R_{in, closed} = \frac{1}{g_m} \left[ 1 + \frac{C_1}{C_1 + C_2} g_m R_D \right]$$


$$R_{out, closed} = \frac{R_D}{1 + \frac{C_1}{C_1 + C_2} g_m R_D}$$

28.

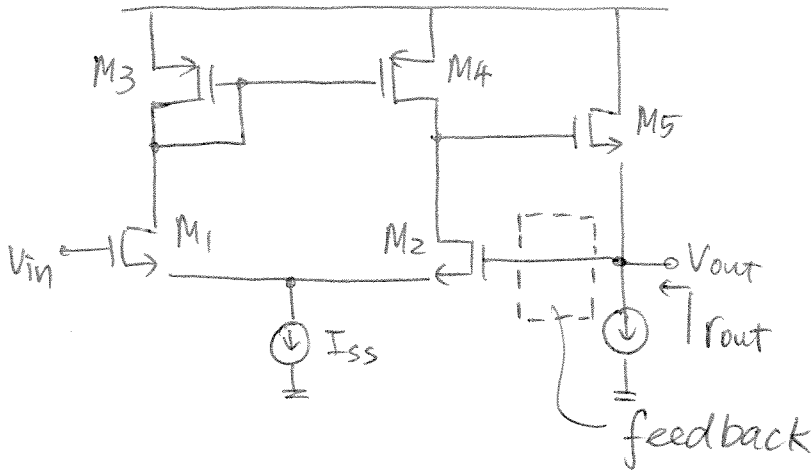

$\lambda > 0$   
 $r_{out}$  low.

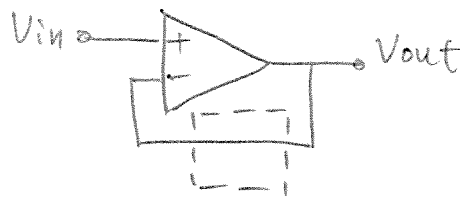Note that  $V_{out}$  is directly fed back to input:



$\therefore$  gain  $\approx 1$   
 (a buffer)  
 $\Rightarrow k = 1.$

$A_{OL}$  (i.e. without feedback)


$$= g_{m1} (r_{o2} \parallel r_{o4}) \times \frac{g_{m5} r_{o5}}{g_{m5} r_{o5} + 1} \left( \approx g_{m1} (r_{o2} \parallel r_{o4}) \right)$$

$$\Rightarrow A_{CL} = \frac{A_{OL}}{1 + A_{OL} \cdot k} = \frac{g_{m1} (r_{o2} \parallel r_{o4}) \left( \frac{g_{m5} r_{o5}}{g_{m5} r_{o5} + 1} \right)}{1 + g_{m1} (r_{o2} \parallel r_{o4}) \left( \frac{g_{m5} r_{o5}}{g_{m5} r_{o5} + 1} \right)}$$

$$r_{out} = \frac{r_{out}(\text{no feedback})}{1 + A_{OL} \cdot k} = \frac{\left( \frac{1}{g_{m5}} \parallel r_{o5} \right)}{1 + g_{m1} (r_{o2} \parallel r_{o4}) \left( \frac{g_{m5} r_{o5}}{g_{m5} r_{o5} + 1} \right)}$$

$$\text{Gain} = A = \frac{g_m r_o}{g_m r_o + 1}$$

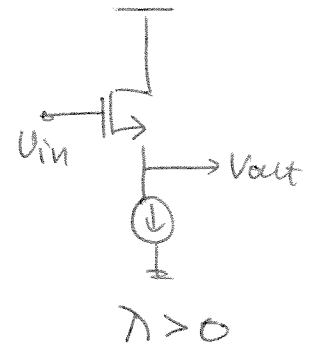
$$r_{out} = \frac{1}{g_m} \parallel r_o$$



In comparison, the amplifier's gain is reduced by  $\frac{g_{m1}(r_{o2} \parallel r_{o4})}{1 + g_{m1}(r_{o2} \parallel r_{o4}) \left( \frac{g_{m5} r_{o5}}{g_{m5} r_{o5} + 1} \right)}$  times.

(=  $\frac{A_{c.L.}}{A}$ ). Output resistance of the amplifier is reduced by  $\left[ 1 + g_{m1}(r_{o2} \parallel r_{o4}) \left( \frac{g_{m5} r_{o5}}{g_{m5} r_{o5} + 1} \right) \right]$  times.

29.

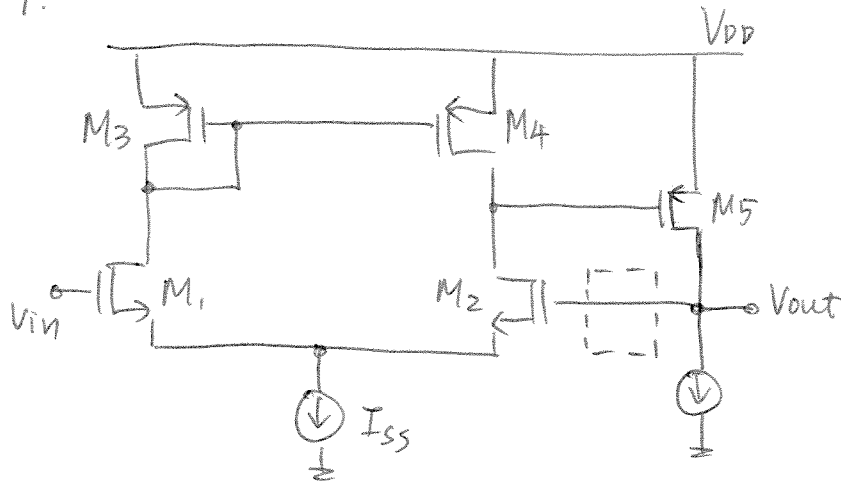

(a) By inspection,

$V_{in} \uparrow \Rightarrow V_{G, M5} \uparrow$

$\Rightarrow \underline{V_{out} \downarrow}$  (Common Source)

$\Rightarrow$  effective  $V_{in}$  ( $V_{in} - V_{out}$ )  $\uparrow \Rightarrow V_{G, M5} \uparrow$

$\Rightarrow$  Positive feedback.

(b)  $A_{o.L.}$  (without feedback)


$$= g_{m1} (r_{o2} \parallel r_{o4}) \times (-g_{m5} r_{o5})$$

$$k \text{ (feedback factor)} = 1$$

$$\Rightarrow \text{loop gain} = A_{o.L.} \times k = -g_{m5} r_{o5} \times g_{m1} (r_{o2} \parallel r_{o4})$$

$\Rightarrow$   $A_{c.L.}$  becomes negative  $\Rightarrow$  Positive feedback.

30.

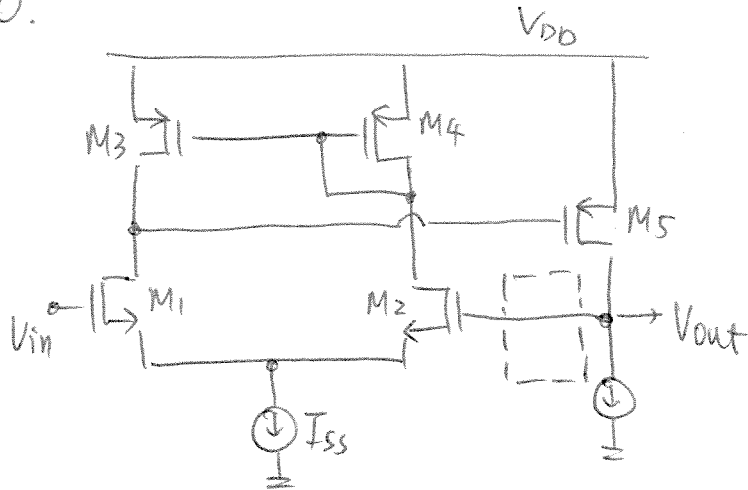

$$k = 1.$$

$$\lambda > 0$$

Ao.L. (without feedback)


$$= -g_{m1}(r_{o1} \parallel r_{o3}) \times (-g_{m5}r_{o5}) = g_{m1}g_{m5}(r_{o1} \parallel r_{o3})r_{o5}$$

$$\Rightarrow A_{c.L.} = \frac{V_{out}}{V_{in}} = \frac{g_{m1}g_{m5}(r_{o1} \parallel r_{o3})r_{o5}}{1 + g_{m1}g_{m5}(r_{o1} \parallel r_{o3})r_{o5}}$$

$$r_{in} \rightarrow \infty$$


$$r_{out} = \frac{r_{out}(\text{no feedback})}{1 + A_{o.L.} \times k} = \frac{r_{o5}}{1 + g_{m1}g_{m5}(r_{o1} \parallel r_{o3})r_{o5}}$$

31.

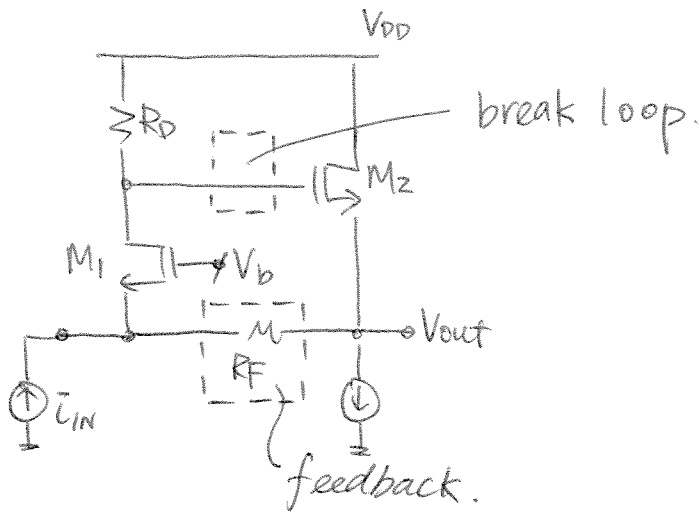

- (a)  $i_{IN} \uparrow \Rightarrow V_{G, M2} \uparrow$  (Common Gate;  $i_{IN}$  mostly flows to  $M_1$   $\because$  resistance  $= \frac{1}{g_{m1}}$ )  
 $\Rightarrow V_{out} \uparrow$  (Source Follower)  
 $\Rightarrow R_F$  momentarily provides more current to source of  $M_1$ )  
 $\Rightarrow V_{G, M2} \uparrow$   
 $\Rightarrow$  Positive feedback.

(b)

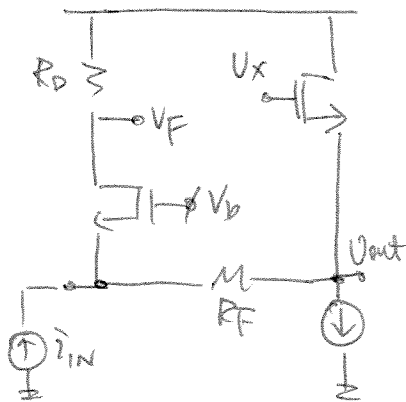

$$V_F = V_x \frac{g_{m1} R_D}{1 + g_{m2} (R_F + \frac{1}{g_{m1}})}$$

$$\Rightarrow -\frac{V_F}{V_x} = \text{Loop Gain} = -\frac{g_{m1} R_D}{1 + g_{m2} (R_F + \frac{1}{g_{m1}})}$$

$\therefore$  feedback is positive.


32.

(a)  $\bar{v}_{in} \uparrow \Delta \Rightarrow \Delta \bar{v}_{in}$  mostly  
flows in  $\frac{1}{g_{m1}} \Rightarrow V_{G,M2} \uparrow$   
(Common Gate)

$\Rightarrow V_{out} \downarrow$  (Common Source)

$\Rightarrow R_F$  momentarily demands  
more current from  $\bar{v}_{in}$

$\Rightarrow$  Negative feedback.

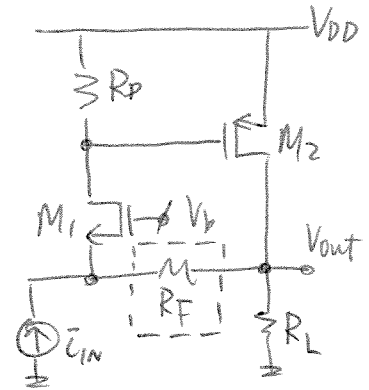

$$\lambda = 0$$

$$R_F \gg 1.$$

$$(b) R_{o.L.} = \left. \frac{V_{out}}{\bar{v}_{in}} \right|_{o.L.} = -R_D \times g_{m2} R_L$$

$$(c) \kappa \text{ (feedback factor)} = \frac{-1}{R_F}$$

$$\Rightarrow R_{c.L.} = \frac{R_{o.L.}}{1 + R_{o.L.} \times \kappa} = \frac{-R_D \times g_{m2} R_L}{1 + \frac{R_D}{R_F} g_{m2} R_L}$$


33.

$$R_{e.l.} = \frac{-g_{m2} R_D R_L}{1 + \frac{g_{m2} R_D R_L}{R_F}}$$

$$\text{loop gain} = \frac{g_{m2} R_D R_L}{R_F}$$

$$r_{in} \approx \frac{1}{g_{m1}}$$

$$\Rightarrow r_{in|c.l.} = \frac{1/g_{m1}}{1 + \frac{g_{m2} R_D R_L}{R_F}}$$

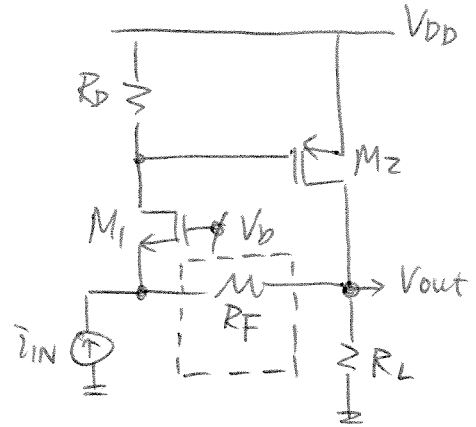

$$r_{out} \approx R_L \quad (R_F \text{ large})$$

$$r_{out|c.l.} = \frac{R_L}{1 + \frac{g_{m2} R_D R_L}{R_F}}$$




34.

$$R_{oL} = \frac{V_{out}}{\bar{v}_{IN}} \text{ (no feedback)}$$

$$= R_D$$

$K$  (feedback factor)
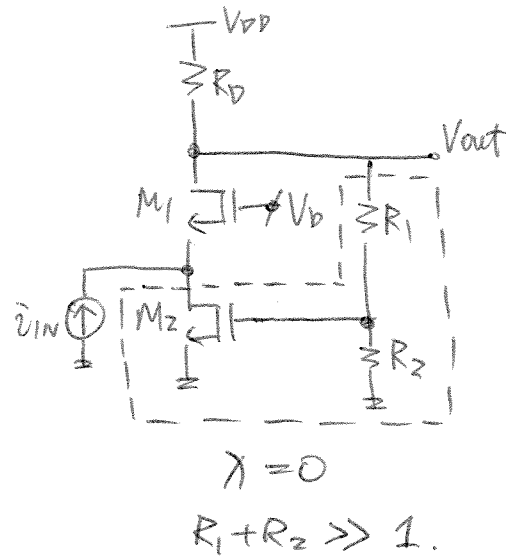
$$= g_{m2} \times \frac{R_2}{R_1 + R_2}$$



$$\Rightarrow R_{c.L.} = \frac{V_{out}}{\bar{v}_{IN}} = \frac{R_D}{1 + R_D \times g_{m2} \frac{R_2}{R_1 + R_2}}$$

$$r_{in|c.L.} = \frac{1/g_{m1}}{1 + R_D \times g_{m2} \frac{R_2}{R_1 + R_2}}$$

$$r_{out|c.L.} = \frac{R_D}{1 + R_D \times g_{m2} \frac{R_2}{R_1 + R_2}}$$

35.

$$R_{o.l.} = \frac{V_{out}}{\bar{v}_{in}} \text{ (no feedback)}$$

$$= R_D$$


$K$  (feedback factor)

$$= g_{m2} \times \frac{C_1}{C_1 + C_2}$$

$$\Rightarrow R_{c.l.} = \frac{V_{out}}{\bar{v}_{in}} = \frac{R_D}{1 + R_D \times g_{m2} \frac{C_1}{C_1 + C_2}}$$

$$\Gamma_{in|c.l.} = \frac{g_{m1}}{1 + R_D \times g_{m2} \frac{C_1}{C_1 + C_2}}$$


$$\Gamma_{out|c.l.} = \frac{R_D}{1 + R_D \times g_{m2} \frac{C_1}{C_1 + C_2}}$$

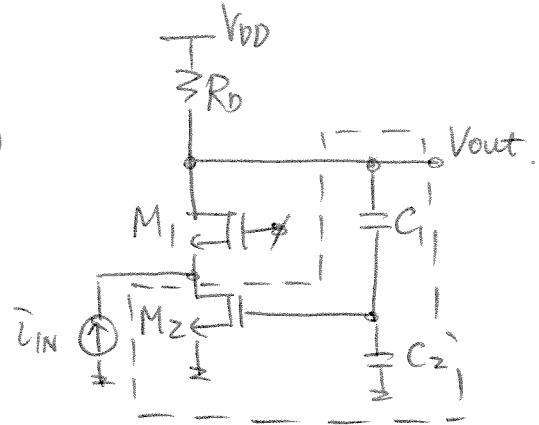

3b.

$$(a) G_{OL} = \frac{i_{out}}{v_{in}} = g_m A_1$$

(common emitter)

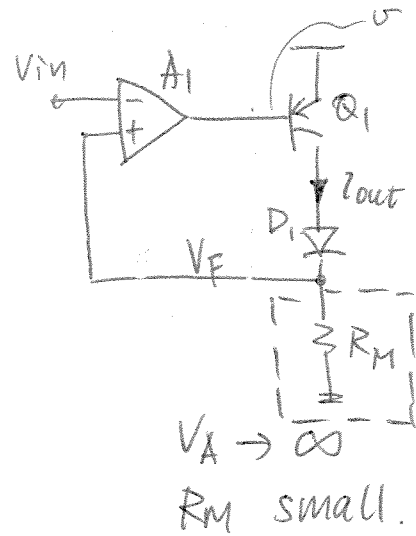

(b)  $K$  (feedback factor)


$$\Rightarrow V_F = i_{out} \times R_M$$

$$\Rightarrow K = \frac{V_F}{i_{out}} = R_M$$


$$\therefore \text{Loop Gain} = G_{OL} K = g_m A_1 R_M$$

$$G_{CL} = \frac{G_{OL}}{1 + G_{OL} K} = \frac{g_m A_1}{1 + g_m A_1 R_M}$$

37.

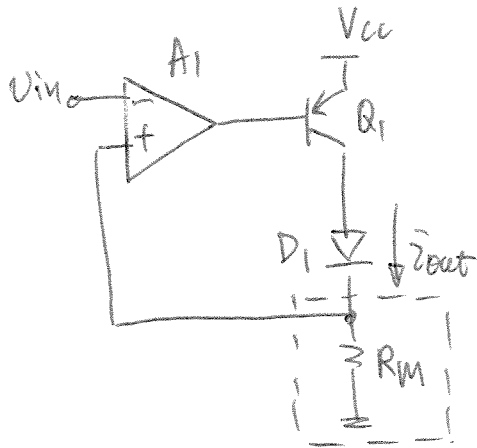

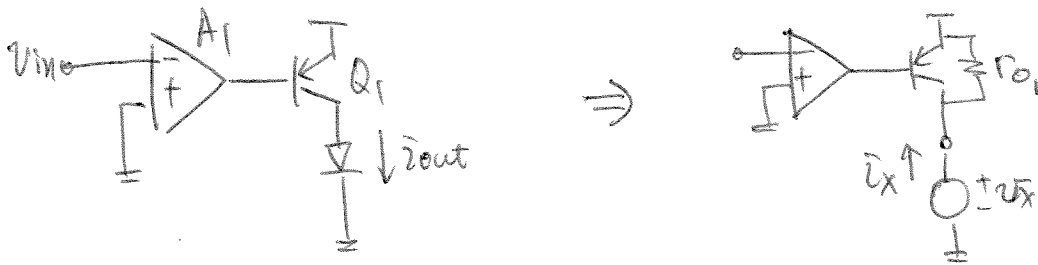Since  $R_M$  is small, the following circuit results:




$$\therefore R_{out, OPEN} = \frac{v_x}{i_x} = r_{O1}$$


$$G_{OL} = \frac{i_{out}}{v_{in}} = A_1 g_{m1} \quad k = R_M$$

$$\begin{aligned} \therefore R_{out, CLOSED} &= R_{out, OPEN} (1 + G_{OL} k) \\ &= r_{O1} (1 + A_1 g_{m1} R_M) \end{aligned}$$

38.

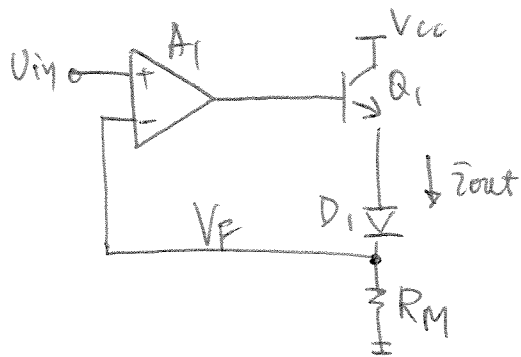

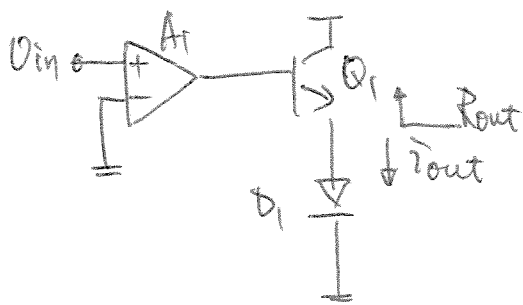Since  $R_M$  is small, the open-loop equivalent becomes the following:



$$G_{OL} = \frac{i_{out}}{i_{in}} \approx A_T g_{m_1}$$

$$R_{out} = \frac{r_T}{\beta + 1} \approx \frac{1}{g_{m_1}}$$

$$K = \frac{V_F}{i_{out}} = R_M$$

$$\Rightarrow G_{CL} = \frac{G_{OL}}{1 + G_{OL}K} = \frac{A_T g_{m_1}}{1 + g_{m_1} A_T R_M}$$

$$\text{Loop Gain} = G_{OL}K = g_{m_1} A_T R_M$$

$$R_{out, \text{closed}} = \frac{1}{g_{m_1}} (1 + g_{m_1} A_T R_M)$$

This circuit provides a much lower output resistance which in general is non-desirable (ideally any current source should have high impedance.)

39.

Using procedure in Ex 12.21


$$G_{o.l.} = \frac{\bar{i}_{out}}{V_{in}} = g_{m2} R_c \times g_{m1}$$

$K$  (feedback factor)

$$= \frac{V_F}{\bar{i}_{out}} = R_M$$

$$\Rightarrow \text{loop gain} = G_{o.l.} \times K = g_{m1} g_{m2} R_c R_M$$
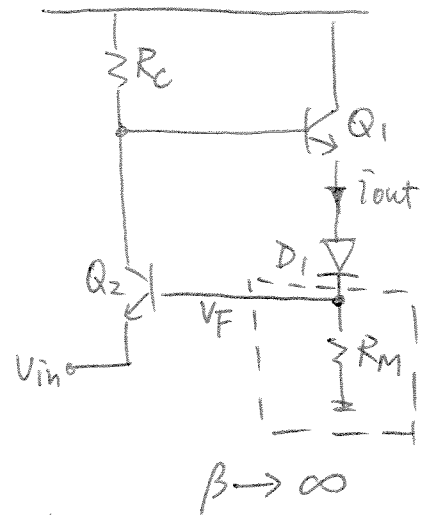
$$\Rightarrow \text{closed-loop gain } G_{c.l.} = \frac{g_{m1} g_{m2} R_c}{1 + g_{m1} g_{m2} R_c R_M}$$



Using procedure in Ex. 12.22

$$G_{o.l.} = g_{m1} g_{m2} R_c$$

$$K = R_M$$

$$r_{in|o.l.} = \frac{1}{g_{m1}}$$

$$r_{out|o.l.} \cong \frac{1}{g_{m2}}$$

$$r_{in|c.l.} = \frac{1}{g_{m1}} (1 + g_{m1} g_{m2} R_c R_M)$$

$$r_{out|c.l.} = \frac{1}{g_{m2}} (1 + g_{m1} g_{m2} R_c R_M)$$

40.


(a)  $\bar{i}_{IN} \uparrow \Delta \Rightarrow$  Most of  $\bar{i}_{IN}$  flows into  $1/g_{m1}$

$\Rightarrow V_{G,M2} \uparrow$  (Common Gate)

$\Rightarrow V_x \uparrow$  (Source Follower)

$\Rightarrow R_F$  momentarily provides more current to Source of  $M_1$

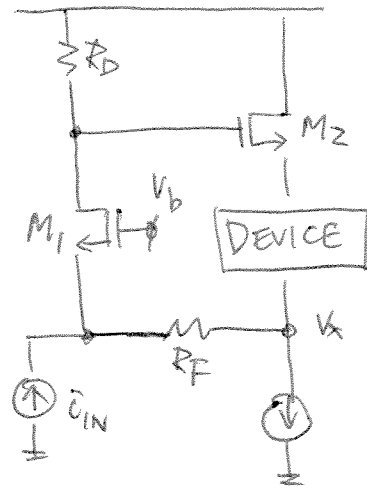$\Rightarrow V_{G,M2} \uparrow \Rightarrow$  Positive feedback.




(b)

$$V_a \times g_{m2} \times R_D = V_b$$



$$\Rightarrow \text{loop gain} = -\frac{V_b}{V_a} = -g_{m2} R_D.$$

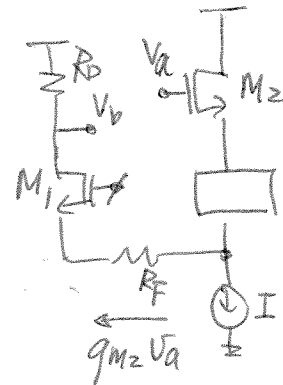Since loop gain is negative, feedback is positive.



41.

(a) The open-loop equivalent becomes:

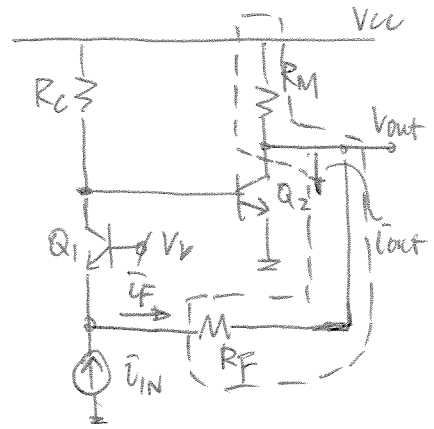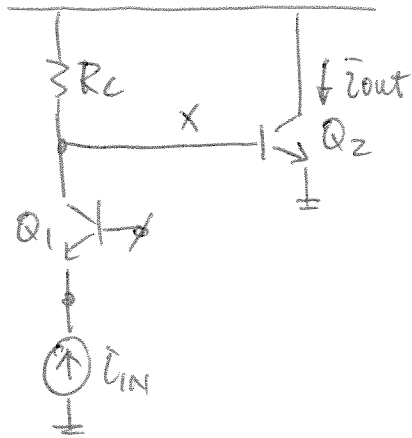


$V_A \rightarrow \infty$   
 $R_M$  small  
 $R_F$  large

$$A_I = \frac{\hat{i}_{out}}{\hat{i}_{IN}} = \frac{\hat{i}_{out}}{v_x} \times \frac{v_x}{\hat{i}_{IN}} \approx g_{m2} \times R_C$$

$$R_{in, OPEN} \approx \frac{1}{g_{m1}}$$

$$R_{out, OPEN} \rightarrow \infty \quad (\because V_{A2} \rightarrow \infty)$$
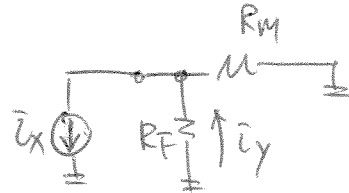
$$K = \frac{\hat{i}_y}{\hat{i}_x} = + \frac{(R_F \parallel R_M)}{R_F}$$





$$A_{CL} = \frac{A_I}{1 + A_I K} = \frac{g_{m2} R_C}{1 + g_{m2} R_C \frac{(R_F \parallel R_M)}{R_F}}$$

$$R_{in, CLOSED} = \frac{\frac{1}{g_{m1}}}{1 + g_{m2} R_C \frac{(R_F \parallel R_M)}{R_F}}$$

$$R_{out, CLOSED} \rightarrow \infty$$



(b) The open-loop equivalent becomes:

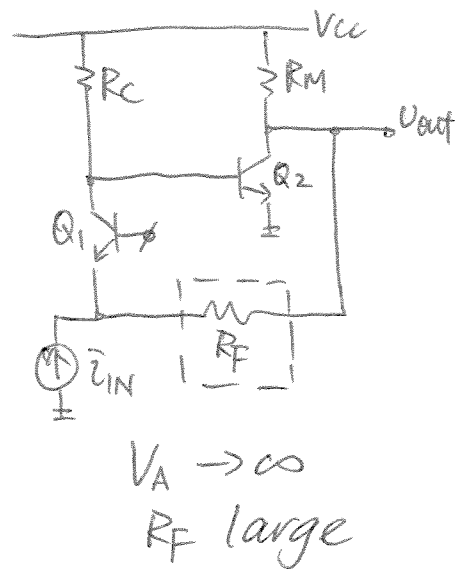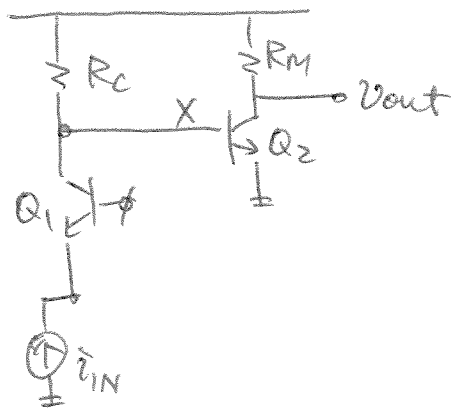

$$R_{OL} = \frac{V_{out}}{\hat{v}_{IN}} = \frac{V_{out}}{V_X} \times \frac{V_X}{\hat{v}_{IN}} \cong -g_{m2} R_M \times R_C$$

$$R_{in, OPEN} = \frac{1}{g_{m1}} \quad R_{out, OPEN} = R_M$$



$$K = -\frac{1}{R_M}$$

$$R_{CL} = \frac{R_{OL}}{1 + R_{OL} K} = \frac{-g_{m2} R_M R_C}{1 + g_{m2} R_C}$$


$$R_{in, CLOSED} = \frac{1/g_{m1}}{1 + g_{m2} R_C}$$

$$R_{out, CLOSED} = \frac{R_M}{1 + g_{m2} R_C}$$

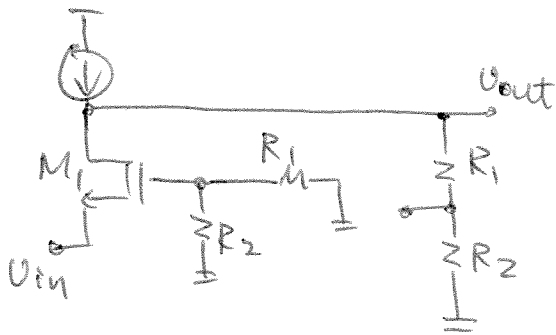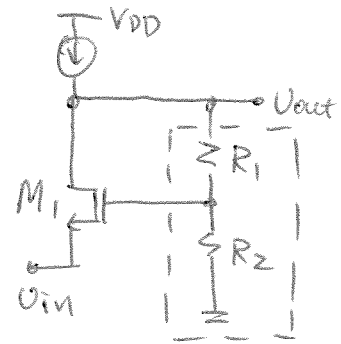42. Breaking the feedback network results in the following circuit:



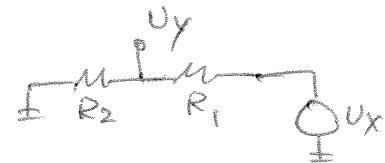Feedback factor  
 $= k = \frac{V_y}{V_x} = \frac{R_2}{R_1 + R_2}$



$$A_{o.L.} = +g_{m1} (R_1 + R_2)$$


$$\text{Loop Gain} = A_{o.L.} k = g_{m1} R_2$$

$$\therefore A_{c.L.} = \frac{A_{o.L.}}{1 + A_{o.L.} k} = \frac{g_{m1} (R_1 + R_2)}{1 + g_{m1} R_2}$$

$$R_{in, \text{closed}} = \frac{1}{g_{m1}} (1 + g_{m1} R_2)$$


$$R_{out, \text{closed}} = \frac{R_1 + R_2}{1 + g_{m1} R_2}$$

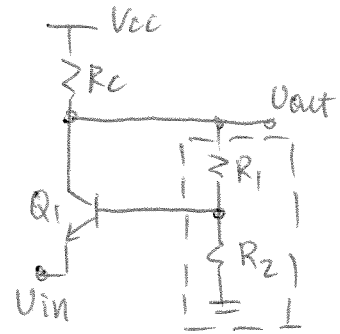43. Breaking the feedback network results in the following circuit:



$$V_A \rightarrow \infty$$


$$1 \ll \beta < \infty$$

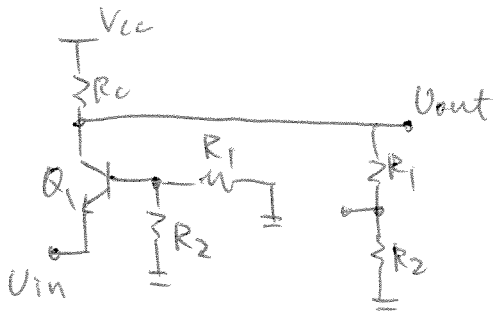

$$A_{OL} \approx g_{m1} [R_c \parallel (R_1 \parallel R_2)] \quad \text{since } \bar{v}_b \rightarrow 0 (\beta \gg 1)$$

Feedback factor
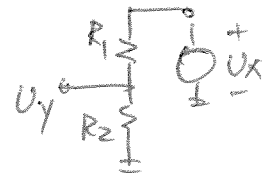
$$= k = \frac{U_Y}{U_X} = \frac{R_2}{R_1 + R_2}$$



$$R_{in, OPEN} = \frac{r_{\pi 1} + (R_1 \parallel R_2)}{\beta_1 + 1} \approx \frac{1}{g_{m1}} + \frac{R_1 \parallel R_2}{\beta_1 + 1}$$


$$R_{out, OPEN} = R_c \parallel (R_1 + R_2)$$

$$\Rightarrow A_{CL} = \frac{A_{OL}}{1 + A_{OL}k} = \frac{g_{m1} [R_c \parallel (R_1 + R_2)]}{1 + g_{m1} [R_c \parallel (R_1 + R_2)] \times \frac{R_2}{R_1 + R_2}}$$

$$R_{in, CLOSED} = \left( \frac{1}{g_{m1}} + \frac{R_1 \parallel R_2}{\beta_1 + 1} \right) (1 + A_{OL}k)$$


$$R_{out, CLOSED} = \frac{R_c \parallel (R_1 + R_2)}{1 + A_{OL}k}$$

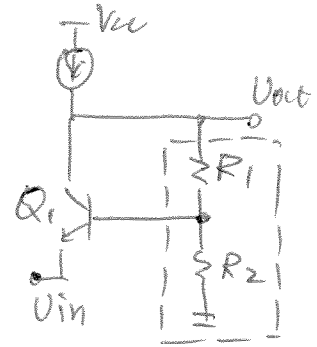44. Breaking the feedback network results in the following circuit:



$$V_A \rightarrow \infty$$


$$1 \ll \beta \ll \infty$$

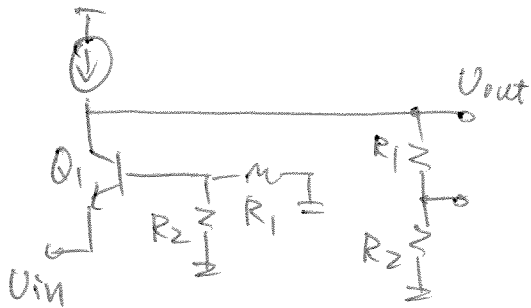

$$A_{OL} \cong g_{m1} (R_1 + R_2) \quad \text{since } i_b \rightarrow 0 (\beta \gg 1)$$

Feedback factor
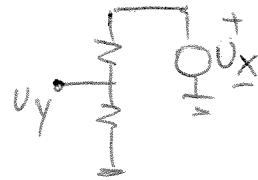
$$= K = \frac{U_Y}{U_X} = \frac{R_2}{R_1 + R_2}$$



$$R_{in, OPEN} \cong \frac{1}{g_{m1}} + \frac{R_1 \parallel R_2}{\beta_1 + 1}$$



$$R_{out, OPEN} = R_1 + R_2$$

$$\Rightarrow A_{CL} = \frac{A_{OL}}{1 + A_{OL}K} = \frac{g_{m1} (R_1 + R_2)}{1 + g_{m1} R_2}$$

$$R_{in, CLOSED} = \left( \frac{1}{g_{m1}} + \frac{R_1 \parallel R_2}{\beta_1 + 1} \right) (1 + g_{m1} R_2)$$

$$R_{out, CLOSED} = \frac{R_1 + R_2}{1 + g_{m1} R_2}$$

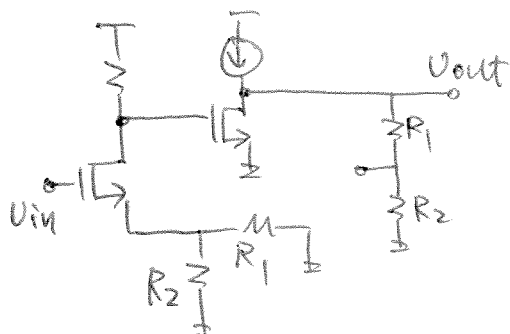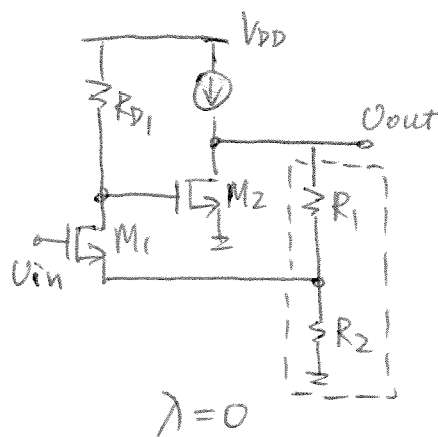45. Breaking the feedback network results in the following circuit:




$$A_{OL} = \frac{-g_{m1} R_{D1}}{1 + g_{m1}(R_1 || R_2)} \times -g_{m2}(R_1 + R_2)$$

$$K = \frac{V_y}{V_x} = \frac{R_2}{R_1 + R_2}$$

$$R_{in, OPEN} \rightarrow \infty$$

$$R_{out, OPEN} = R_1 + R_2$$


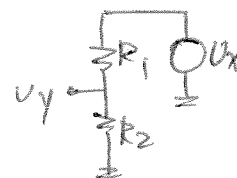


$$\therefore A_{CL} = \frac{A_{OL}}{1 + A_{OL}K} = \frac{\left[ \frac{g_{m1} g_{m2} R_{D1} (R_1 + R_2)}{1 + g_{m1} (R_1 || R_2)} \right]}{1 + \frac{g_{m1} g_{m2} R_{D1}}{1 + g_{m1} (R_1 || R_2)}}$$

$$R_{in, CLOSED} \rightarrow \infty$$

$$R_{out, CLOSED} = \frac{R_1 + R_2}{1 + A_{OL}K}$$

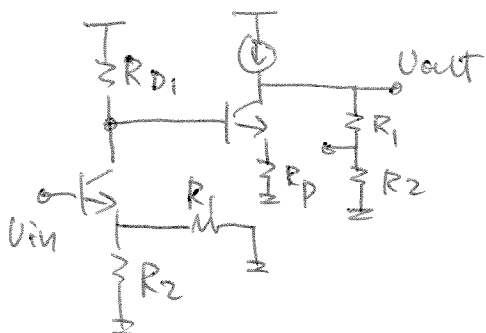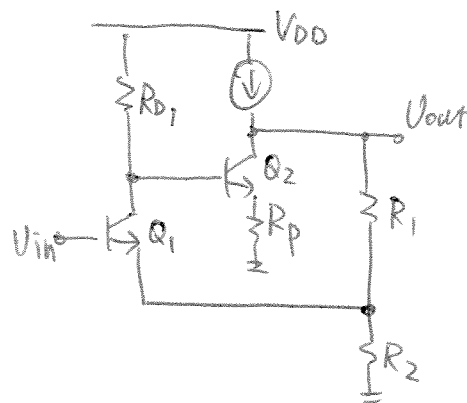4b. Breaking the feedback network results in the following circuit:




$$A_{OL} \cong \frac{-g_{m1} \times \{R_{D1} \parallel [\Gamma_{\pi 2} + (\beta_2 + 1)R_p]\}}{1 + g_{m1}(R_1 \parallel R_2)} \times \frac{-g_{m2}(R_1 + R_2)}{1 + g_{m2}R_p}$$

$$R_{in, OPEN} = \Gamma_{\pi 1} + (R_1 \parallel R_2)$$

$$R_{out, OPEN} = R_1 + R_2$$
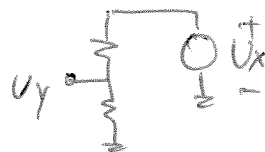
$$K = \frac{V_Y}{V_X} = \frac{R_2}{R_1 + R_2}$$




$$\Rightarrow A_{CL} = \frac{A_{OL}}{1 + A_{OL}K}$$

$$R_{in, CLOSED} = [\Gamma_{\pi 1} + (R_1 \parallel R_2)] (1 + A_{OL}K)$$


$$R_{out, CLOSED} = \frac{R_1 + R_2}{1 + A_{OL}K}$$

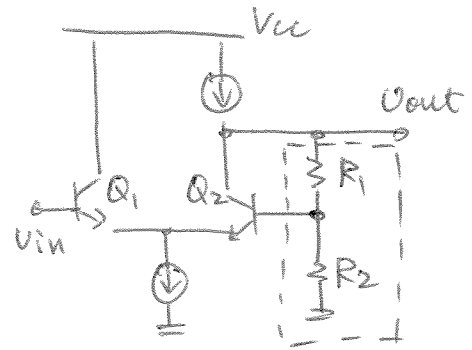47. Breaking the feedback network results in the following circuit:



$(V_A \rightarrow \infty)$

$$K = \frac{R_2}{R_1 + R_2}$$

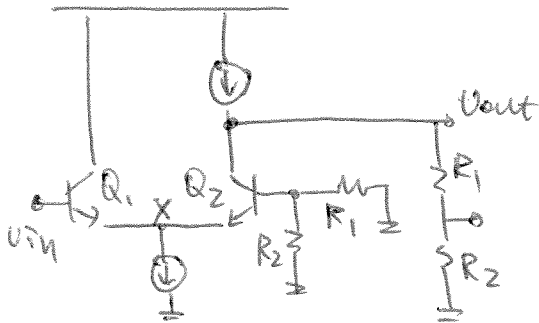

$$A_{OL} \cong \underbrace{\frac{g_{m1} \left( \frac{1}{g_{m2}} + \frac{R_1 || R_2}{\beta_2 + 1} \right)}{1 + g_{m1} \left( \frac{1}{g_{m2}} + \frac{R_1 || R_2}{\beta_2 + 1} \right)}}_{\text{emitter follower (Q}_1\text{)} = \frac{V_x}{V_{in}}} \times \underbrace{g_{m2} (R_1 + R_2)}_{\text{common-base stage (Q}_2\text{)} = \frac{V_{out}}{V_x}}$$

$$R_{in, OPEN} = r_{\pi 1} + (\beta_1 + 1) \left( \frac{1}{g_{m2}} + \frac{R_1 || R_2}{\beta_2 + 1} \right)$$



$$R_{out, OPEN} = R_1 + R_2$$

$$\therefore A_{CL} = \frac{A_{OL}}{1 + A_{OL} K}$$


$$R_{in, CLOSED} = \left[ r_{\pi 1} + (\beta_1 + 1) \left( \frac{1}{g_{m2}} + \frac{R_1 || R_2}{\beta_2 + 1} \right) \right] \times (1 + A_{OL} K)$$

$$R_{out, CLOSED} = \frac{R_1 + R_2}{1 + A_{OL} K}$$

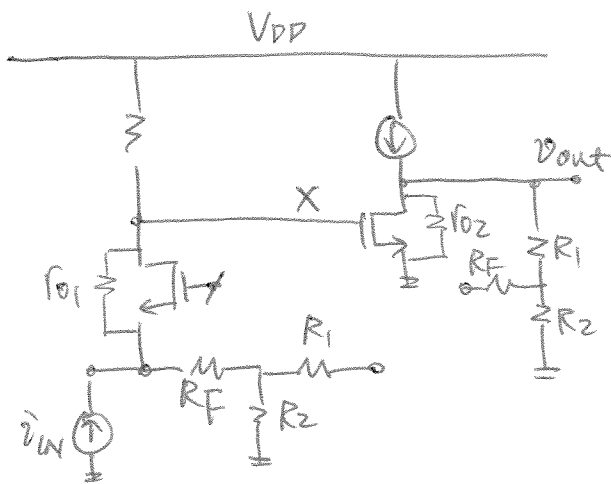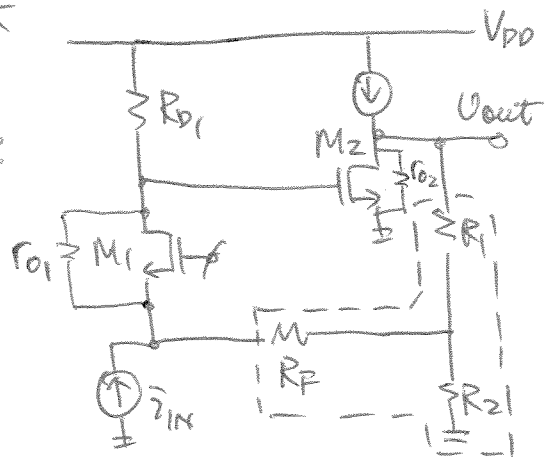48. Breaking the feedback network results in the following circuit:


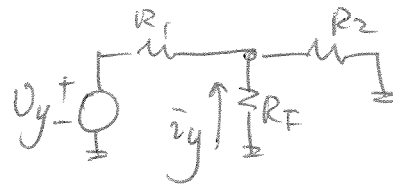
$$K = - \frac{(R_F \parallel R_2) / R_F}{R_F \parallel R_2 + R_1}$$



$$R_{OL} = \frac{v_{out}}{i_{IN}} = \frac{v_{out}}{v_x} \times \frac{v_x}{i_{IN}}$$

$$= -g_{m2} [r_{o2} \parallel (R_1 + R_2)] \times \left\{ \frac{\frac{1}{r_{o1}} + \frac{1}{R_{D1}}}{\frac{1}{r_{o1}} + g_{m1}} \times \left[ \frac{1}{(R_F + R_2) \parallel \frac{1}{g_{m1}}} + \frac{1}{r_{o1}} \right] - \frac{1}{r_{o1}} \right\}$$

$$R_{in, OPEN} \cong \frac{1}{g_{m1}} \parallel (R_F + R_2) \parallel \frac{r_{o1}}{1 - g_{m1} R_{D1}}$$

$$R_{out, OPEN} = r_{o2} \parallel (R_1 + R_2)$$



$$R_{CL} = \frac{R_{OL}}{1 + R_{OL} K}$$

$$R_{in, CLOSED} = \frac{R_{in, OPEN}}{1 + R_{OL} K}$$

$$R_{out, CLOSED} = \frac{R_{out, OPEN}}{1 + R_{OL} K}$$



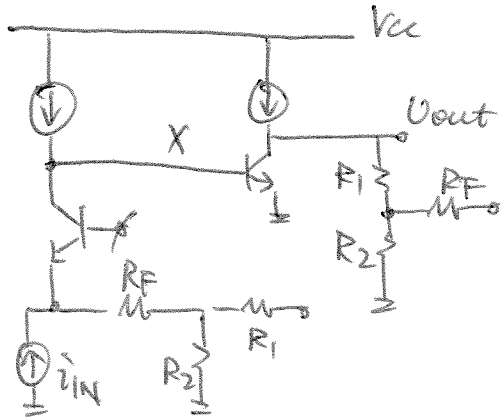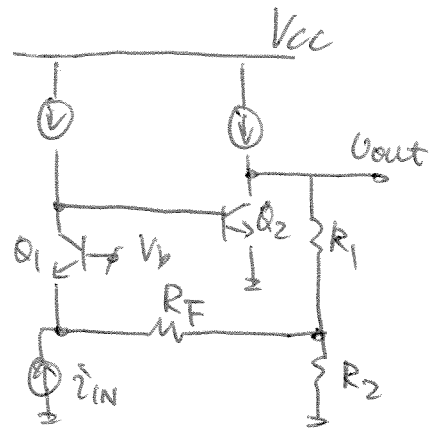49. Breaking the feedback network results in the following circuit:




$$R_{OL} = \frac{U_{out}}{i_{IN}} = \frac{U_{out}}{U_X} \times \frac{U_X}{i_{IN}} = [-g_{m2}(R_1 + R_2)] \times [g_{m1}, r_{\pi 2} \left\{ \frac{1}{g_{m1}} \parallel (R_F + R_2) \right\}]$$

$$R_{in, OPEN} = \frac{1}{g_{m1}} \parallel (R_F + R_2)$$

$$R_{out, OPEN} = R_1 + R_2$$
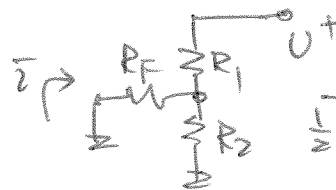
$$K = \frac{\dot{U}}{U} = - \frac{(R_2 \parallel R_F) / R_F}{R_1 + (R_2 \parallel R_F)}$$





$$\therefore R_{CL} = \frac{R_{OL}}{1 + R_{OL}K}$$

$$R_{in, CLOSED} = \frac{\frac{1}{g_{m1}} \parallel (R_F + R_2)}{1 + R_{OL}K}$$

$$R_{out, CLOSED} = \frac{R_1 + R_2}{1 + R_{OL}K}$$

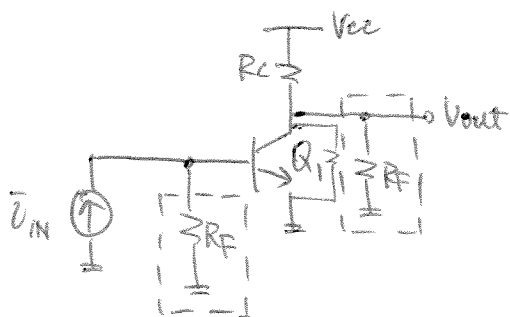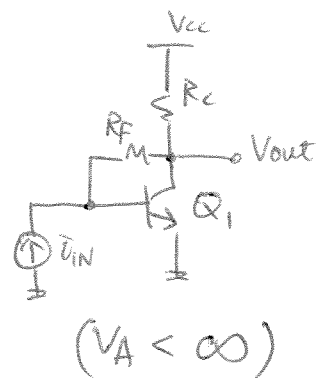50. The feedback network consists of  $R_F$ .

Using the method discussed in lecture, break the circuit as follows:



This is the open-loop circuit with consideration of I/O loading.

- By inspection,

$$v_{out} = i_c \times (R_C \parallel R_F \parallel r_o)$$

$$= -g_m (i_{in} \times (R_F \parallel r_{\pi})) \times (R_C \parallel R_F \parallel r_o)$$

$$\Rightarrow R_{o.l.} = \frac{v_{out}}{i_{in}} = -g_m (R_F \parallel r_{\pi}) (R_C \parallel R_F \parallel r_o) \quad \text{--- (1)}$$

$$R_{in, open} = (R_F \parallel r_{\pi}) \quad R_{out, open} = (R_C \parallel R_F \parallel r_o)$$

- Feedback factor  $k$ :

$$k = \frac{v_x}{i_x} = -\frac{1}{R_F}$$



$$\therefore R_{o.L.} = \frac{R_{o.L.}}{1 + R_{o.L.} \times K} = \frac{-g_m(R_F \parallel r_{\pi})(R_C \parallel R_F \parallel r_o)}{1 + \frac{g_m(R_F \parallel r_{\pi})(R_C \parallel R_F \parallel r_o)}{R_F}}$$



$$R_{in,CLOSED} = \frac{(R_F \parallel r_{\pi})}{1 - \frac{R_{o.L.}}{R_F}}$$

$$R_{out,CLOSED} = \frac{(R_C \parallel R_F \parallel r_o)}{1 - \frac{R_{o.L.}}{R_F}}$$

where  $R_{o.L.}$  is given by (1).

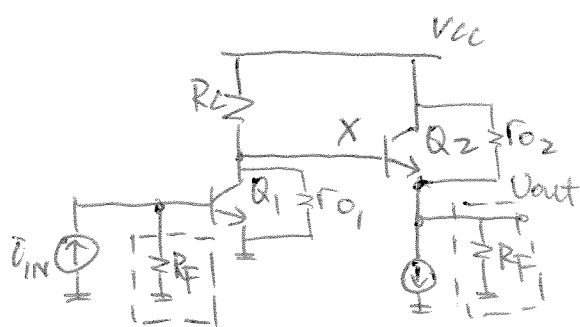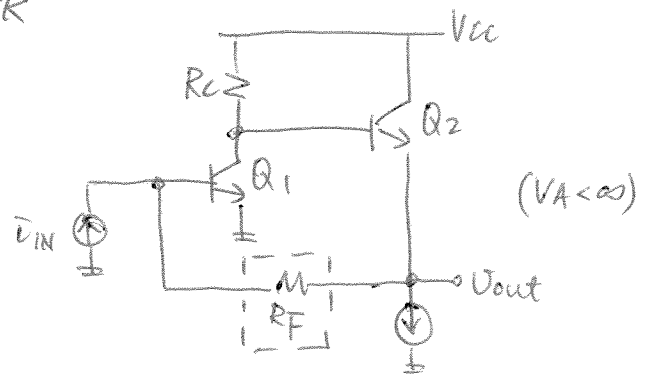51. The feedback network consists of  $R_F$ .

Using the method discussed in lecture, break the circuit as follows:



This is the open-loop circuit with consideration of I/O loading.

- Gain of common-emitter stage:

$$\frac{v_x}{v_{IN}} = -g_{m1}(R_F \parallel r_{\pi 1}) \times \left\{ R_c \parallel r_{O1} \parallel \left[ r_{\pi 2} + (\beta_2 + 1)(R_F \parallel r_{O2}) \right] \right\}$$

- Gain of emitter-follower stage:

$$\frac{v_{out}}{v_x} = \frac{g_{m2}(R_F \parallel r_{O2})}{1 + g_{m2}(R_F \parallel r_{O2})}$$


$$\Rightarrow R_{o.l.} = \frac{v_x}{v_{IN}} \cdot \frac{v_{out}}{v_x} \quad \text{--- (1)}$$

$$R_{in, OPEN} = R_F \parallel r_{\pi 1}$$

$$R_{out, OPEN} \cong R_F \parallel r_{O2} \parallel \frac{1}{g_{m2}}$$

- Feedback factor  $k$ :
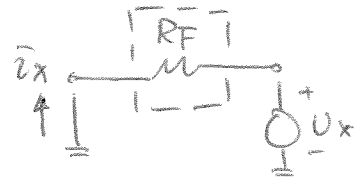
$$k = \frac{v_x}{\bar{v}_x} = -\frac{1}{R_F}$$





$$\therefore R_{o,L} = \frac{R_{o,L}}{1 + R_{o,L} \times k} = \frac{R_{o,L}}{1 - R_{o,L}/R_F}$$

$$R_{in,CLOSED} = \frac{(R_F \parallel \Gamma_{\pi_1})}{1 - \frac{R_{o,L}}{R_F}} \quad R_{out,CLOSED} = \frac{R_F \parallel r_{o2} \parallel \frac{1}{g_{m2}}}{1 - \frac{R_{o,L}}{R_F}}$$

where  $R_{o,L}$  is given by (1).

52.

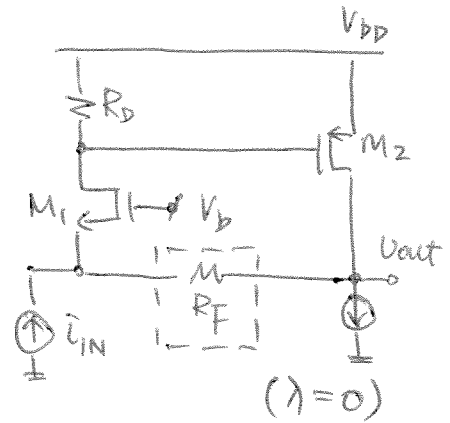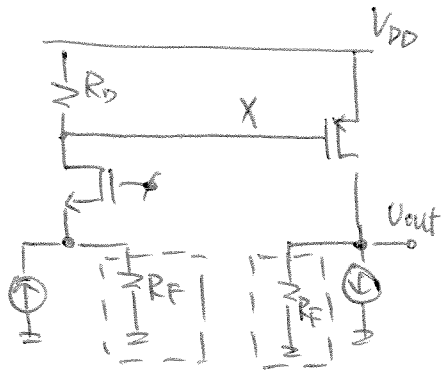(a) Breaking the feedback loop results in the following circuit:



$$R_{o.l.} = \frac{V_X}{i_{IN}} \cdot \frac{V_{out}}{V_X}$$

$$= g_{m1} R_D \left( \frac{1}{g_{m1}} \parallel R_F \right) \times (-g_{m2} R_F)$$

$$R_{in, OPEN} = \frac{1}{g_{m1}} \parallel R_F$$

$$R_{out, OPEN} = R_F$$

- Feedback factor  $k$ :

$$k = \frac{V_X}{V_X} = -\frac{1}{R_F}$$





$$\Rightarrow R_{c.l.} = \frac{R_{o.l.}}{1 + R_{o.l.} \times k} = \frac{-g_{m1} g_{m2} R_D R_F \left( \frac{1}{g_{m1}} \parallel R_F \right)}{1 + g_{m1} g_{m2} R_D \left( \frac{1}{g_{m1}} \parallel R_F \right)}$$

$$R_{in, CLOSED} = \frac{\left( \frac{1}{g_{m1}} \parallel R_F \right)}{1 + g_{m1} g_{m2} R_D \left( \frac{1}{g_{m1}} \parallel R_F \right)}$$

$$R_{out, CLOSED} = \frac{R_F}{1 + g_{m1} g_{m2} R_D \left( \frac{1}{g_{m1}} \parallel R_F \right)}$$

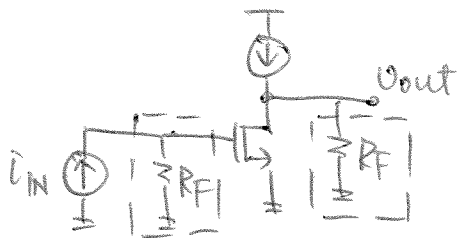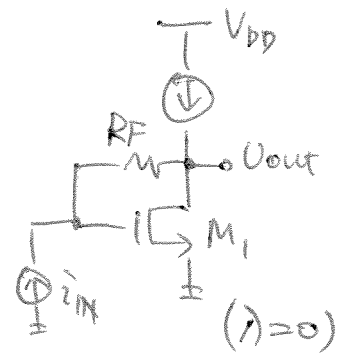(b) Breaking the feedback loop results in the following circuit:




$$R_{o.L.} = \frac{v_{out}}{i_{in}} = -g_m R_F R_F = -g_m R_F^2$$

$$R_{in, OPEN} = R_F \quad R_{out, OPEN} = R_F$$

- Feedback factor  $K$ :

$$K = \frac{v_x}{i_x} = -\frac{1}{R_F}$$

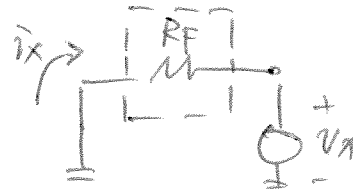


$$\Rightarrow R_{c.L.} = \frac{-g_m R_F^2}{1 + g_m R_F}$$

$$R_{in, CLOSED} = \frac{R_F}{1 + g_m R_F}$$

$$R_{out, CLOSED} = \frac{R_F}{1 + g_m R_F}$$

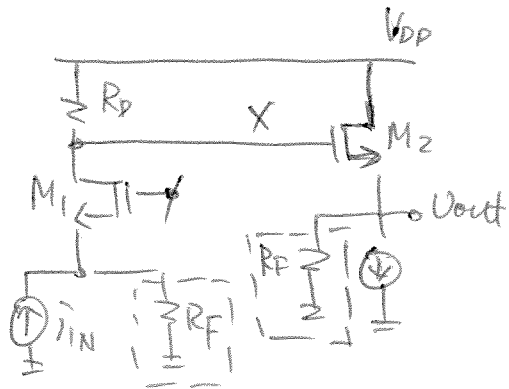(c) Breaking the feedback loop results in the following circuit:



$$R_{in, OPEN} = \left( \frac{1}{g_{m1}} \parallel R_F \right)$$


$$R_{o.L.} = \frac{V_{out}}{i_{IN}} = \frac{V_x}{i_{IN}} \cdot \frac{V_{out}}{V_x}$$

$$= g_{m1} R_D \left( \frac{1}{g_{m1}} \parallel R_F \right) \times g_{m2} \left( R_F \parallel \frac{1}{g_{m2}} \right)$$

$$R_{out, OPEN} = \left( R_F \parallel \frac{1}{g_{m2}} \right)$$

- Feedback factor  $K$ :

$$K = \frac{V_x}{i_x} = -\frac{1}{R_F}$$

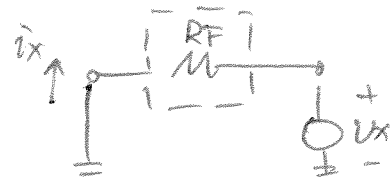

(Note: Feedback is positive.)

$$\Rightarrow R_{c.L.} = \frac{R_{o.L.}}{1 + R_{o.L.} \times K}$$



$$= \frac{g_{m1} g_{m2} R_D \left( \frac{1}{g_{m1}} \parallel R_F \right) \left( \frac{1}{g_{m2}} \parallel R_F \right)}{1 - g_{m1} g_{m2} \left( \frac{R_D}{R_F} \right) \left( \frac{1}{g_{m1}} \parallel R_F \right) \left( \frac{1}{g_{m2}} \parallel R_F \right)}$$

$$R_{in, CLOSED} = \frac{\left( \frac{1}{g_{m1}} \parallel R_F \right)}{1 - \frac{R_{o.L.}}{R_F}}$$

$$R_{out, CLOSED} = \frac{\left( \frac{1}{g_{m2}} \parallel R_F \right)}{1 - \frac{R_{o.L.}}{R_F}}$$



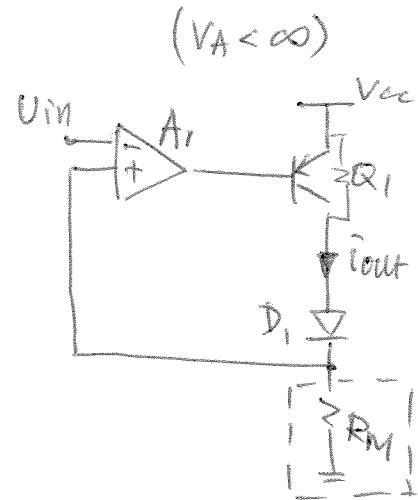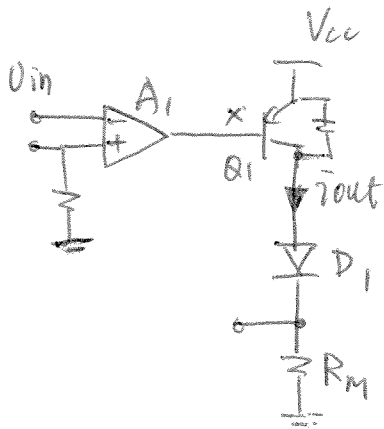
53. Breaking the feedback network (i.e.  $R_M$ ) results in the following circuit:



$$G_{OL} = \frac{\bar{i}_{out}}{U_{in}} = \frac{\bar{i}_{out}}{U_x} \times \frac{U_x}{U_{in}} \quad (1)$$

$$= \underbrace{g_{m1} \times \frac{[R_L + R_M] \parallel r_{o1}}{(R_L + R_M)}}_{\text{(current division)}} \times (-A_1)$$

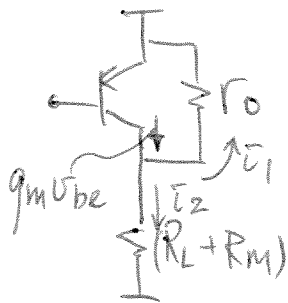Note: current ( $g_m V_{be}$ ) splits between  $r_o$  &  $[R_L$  (impedance of  $D_1$ ) +  $R_M$ ]




$$g_m V_{be} = \bar{i}_1 + \bar{i}_2$$

$$R_{in, OPEN} \rightarrow \infty$$

$$R_{out, OPEN} = r_{o1} + R_M$$

- Feedback factor  $K$ :

$$K = \frac{U_x}{\bar{i}_x} = R_M$$

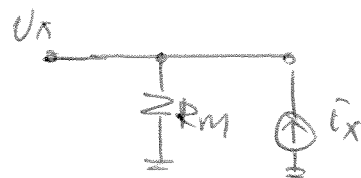

$$\therefore G_{o.l.} = \frac{G_{o.l.}}{1 + G_{o.l.} \times K} = \frac{G_{o.l.}}{1 + G_{o.l.} \times R_M}$$



$$R_{in, CLOSED} \rightarrow \infty$$

$$R_{out, CLOSED} = (T_{o1} + R_M)(1 + G_{o.l.} \times R_M)$$

where  $G_{o.l.}$  is given by (1)

54.

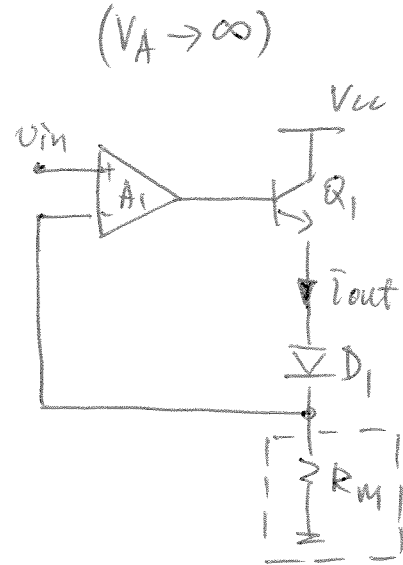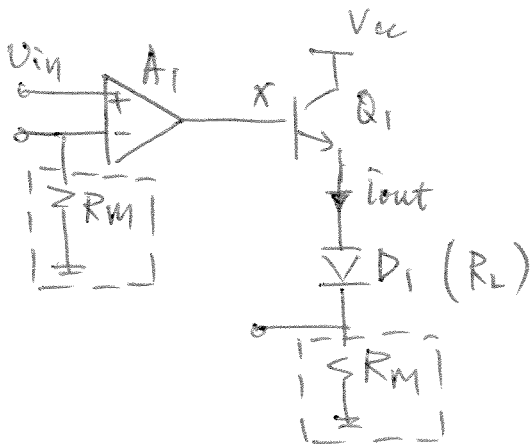(a) Breaking the feedback loop results in the following circuit:



$$G_{o.l.} = \frac{i_{out}}{v_{in}} = \frac{i_{out}}{v_x} \cdot \frac{v_x}{v_{in}} = \frac{g_{m1}(R_L + R_M)}{1 + g_{m1}(R_L + R_M)} \times A_1$$

$$R_{in, OPEN} \rightarrow \infty$$

$$R_{out, OPEN} \approx R_M + \frac{1}{g_{m1}}$$

- Feedback factor  $k$ :

$$k = \frac{v_x}{v_x} = R_M$$





$$G_{c.l.} = \frac{G_{o.l.}}{1 + G_{o.l.} k} = \frac{G_{o.l.}}{1 + G_{o.l.} R_M}$$

$$R_{in, CLOSED} \rightarrow \infty$$

$$R_{out, CLOSED} = \left(R_M + \frac{1}{g_{m1}}\right) \times (1 + G_{o.l.} R_M)$$

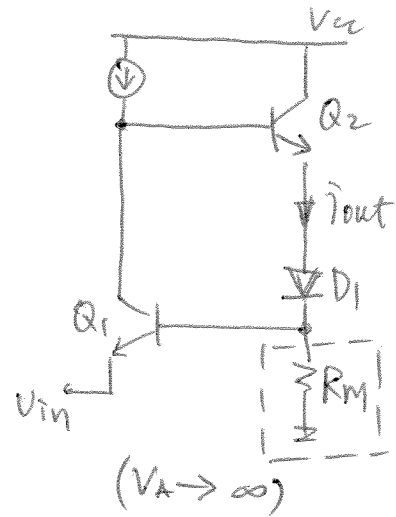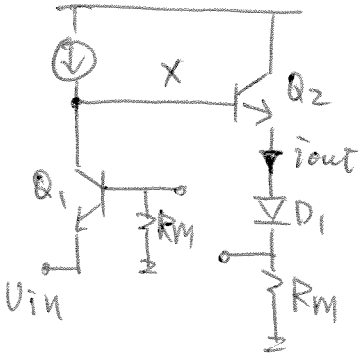(b) Breaking the feedback loop results in the following circuit:




$$G_{o.L.} = \frac{i_{out}}{v_{in}} = \frac{i_{out}}{v_x} \times \frac{v_x}{v_{in}} \approx \frac{g_{m2}(R_L + R_M)}{1 + g_{m2}(R_L + R_M)} \times g_{m1} [\tau_{\pi 2} + (\beta_2 + 1)(R_L + R_M)]$$

$$R_{in, OPEN} = \frac{\tau_{\pi 1} + R_M}{\beta_1 + 1} \approx \frac{1}{g_{m1}} + \frac{R_M}{\beta_1 + 1}$$

$$R_{out, OPEN} = \frac{1}{g_{m2}} + R_M$$

- Feedback Factor  $k$ :

$$k = \frac{v_x}{i_x} = R_M$$

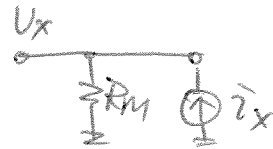

$$\Rightarrow G_{c.L.} = \frac{G_{o.L.}}{1 + G_{o.L.} \times k} = \frac{G_{o.L.}}{1 + G_{o.L.} R_M}$$

$$R_{in, CLOSED} = \left( \frac{1}{g_{m1}} + \frac{R_M}{\beta_1 + 1} \right) (1 + G_{o.L.} R_M)$$

$$R_{out, CLOSED} = \left( \frac{1}{g_{m2}} + R_M \right) (1 + G_{o.L.} R_M)$$

55.

$$V_{out} = [-g_{m1}(V_{in} - V_x)R_D] \cdot [-g_{m2} \{r_{o2} \parallel (\frac{1}{g_{m1}} + R_L)\}]$$

(ignore  $r_{o1}$  for now) — ①

$$\frac{V_{out} - V_x}{R_L} = \bar{i}_{out}$$

$$\Rightarrow V_{out} = \bar{i}_{out} R_L + V_x \quad \text{--- ②}$$

$$\bar{i}_{out} = -g_{m1}(V_{in} - V_x) \Rightarrow V_{in} + \frac{\bar{i}_{out}}{g_{m1}} = V_x \quad \text{--- ③}$$

- Substitute ② & ③ into ① and solve for



$$\frac{\bar{i}_{out}}{V_{in}} :$$

$$\frac{\bar{i}_{out}}{V_{in}} \cong - \frac{1}{R_L + \frac{1}{g_{m1}} + g_{m2}R_D \{r_{o2} \parallel (\frac{1}{g_{m1}} + R_L)\}} = G_{c.l.}$$



$$R_{in, closed} \rightarrow \infty$$

$$R_{out, closed}$$
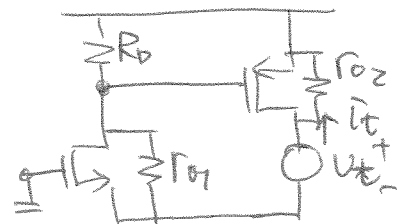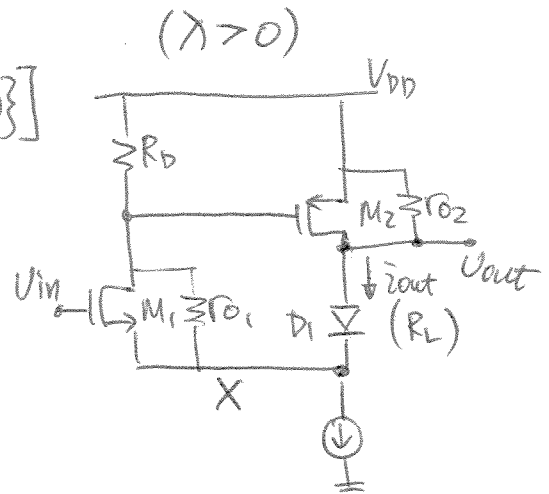
$$= r_{o2} + \left( \frac{r_{o1} + R_D}{1 + g_{m1}r_{o1}} \right)$$



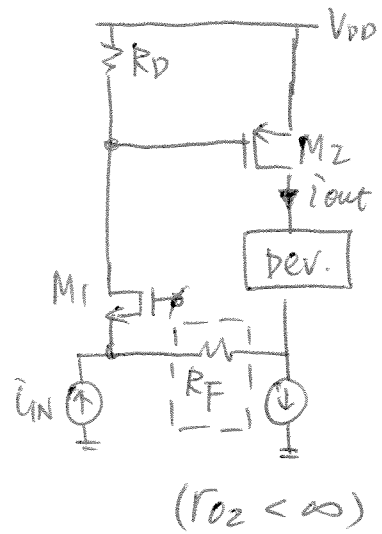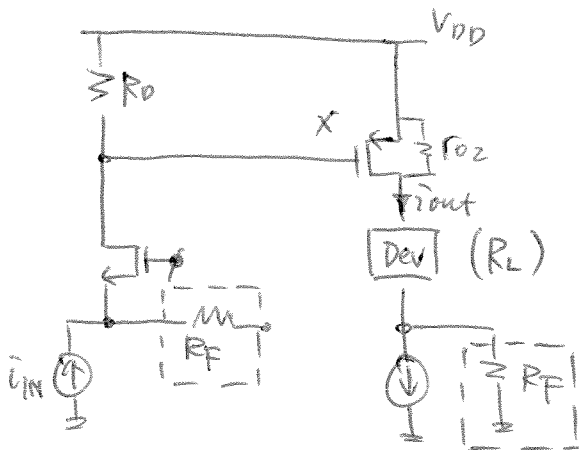5b. Breaking the feedback loop results in the following circuit :



$$A_{I, o.l.} = \frac{\hat{i}_{out}}{\hat{i}_{IN}} = \frac{\hat{i}_{out}}{V_x} \times \frac{V_x}{\hat{i}_{IN}}$$

$$= -g_{m2} \times \frac{(R_L + R_F) \parallel r_{o2}}{(R_L + R_F)} \times R_D$$

$$R_{in, open} = \frac{1}{g_{m1}}$$

$$R_{out, open} = r_{o2} + R_F$$

- Feedback factor  $K$  :

$$K = \frac{\hat{i}_Y}{\hat{i}_X} = -1$$





$$\Rightarrow A_{I, c.l.} = \frac{A_{I, o.l.}}{1 + A_{I, o.l.} \times K} = \frac{A_{I, o.l.}}{1 - A_{I, o.l.}}$$

$$R_{in, closed} = \frac{1/g_{m1}}{1 - A_{I, c.l.}}$$

$$R_{out, closed} = (r_{o2} + R_F)(1 - A_{I, c.l.})$$

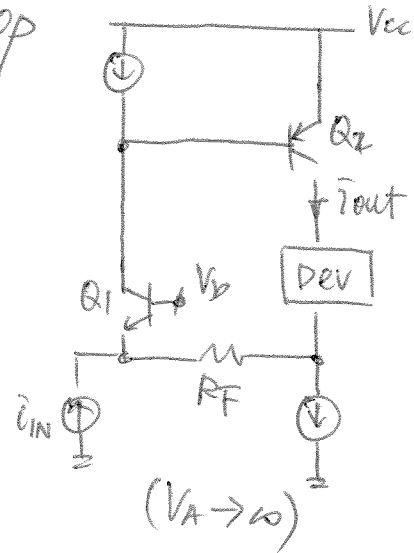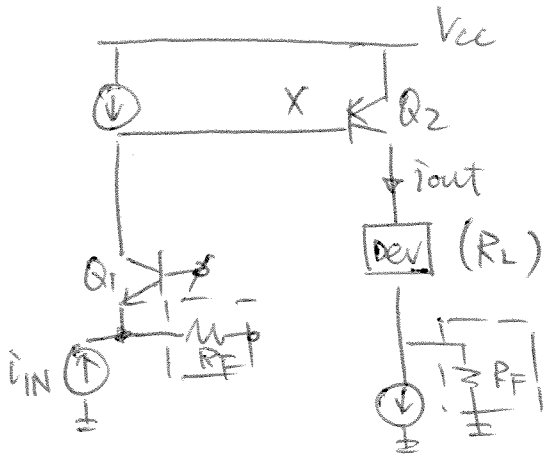57. Breaking the feedback loop results in the following circuit:





$$A_{I, o.l.} = \frac{i_{out}}{i_{in}} = \frac{i_{out}}{v_x} \times \frac{v_x}{i_{in}}$$

$$\cong -g_{m2} \times r_{\pi2} = \beta_2$$

$$R_{in, OPEN} = \frac{r_{\pi1}}{\beta_1 + 1} \approx \frac{1}{g_{m1}} \quad R_{out, OPEN} \rightarrow \infty$$

(Note:  $R_{out} \rightarrow \infty$  because there is no current path:)

- Feedback factor  $k$ :

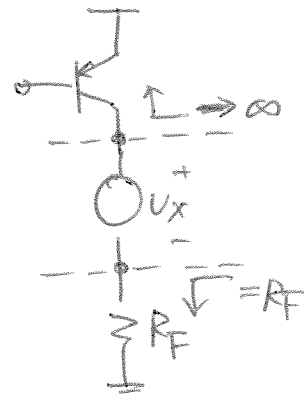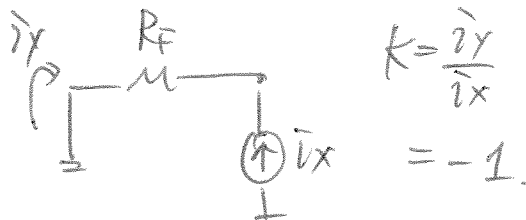



$$\Rightarrow A_{I, C.L.} = \frac{A_{I, O.L.}}{1 + A_{I, O.L.} \times K} = \frac{\beta_2}{1 - \beta_2}$$

$$R_{in, CLOSED} = \frac{1/g_{m_1}}{1 - \beta_2}$$

$$R_{out, CLOSED} \rightarrow \infty$$



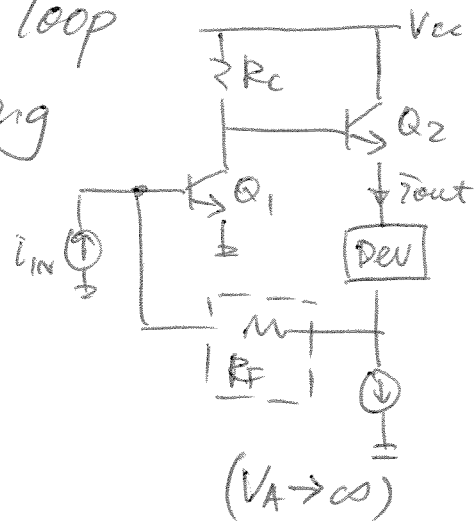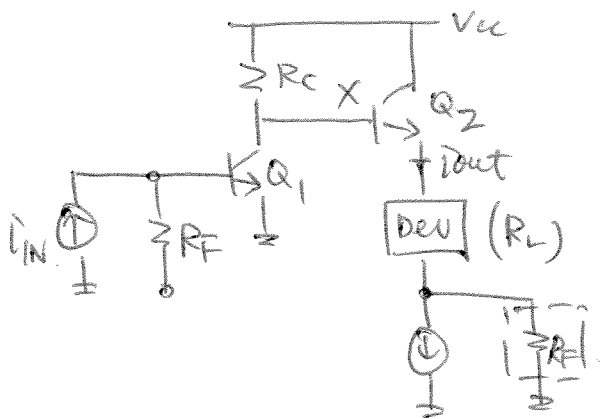58. Breaking the feedback loop results in the following circuit:



$$A_{I,OL} = \frac{i_{out}}{i_{in}} = \frac{i_{out}}{u_x} \times \frac{u_x}{i_{in}}$$


$$= \frac{g_{m2}(R_L + R_F)}{1 + g_{m2}(R_L + R_F)} \times \left[ \beta_1 \times \left[ R_C \parallel \left\{ r_{\pi 2} + (\beta_2 + 1)(R_L + R_F) \right\} \right] \right]$$

$$R_{in,OPEN} = r_{\pi 1}$$

$$R_{out,OPEN} \approx \frac{1}{g_{m2}} + R_F$$

- Feedback factor  $K$ :

$$K = \frac{i_Y}{i_X} = -1$$

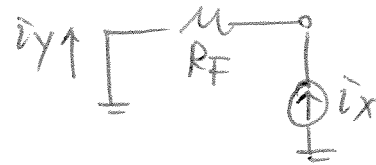


$$\Rightarrow A_{I,C.L.} = \frac{A_{I,OL}}{1 + A_{I,OL} \times K} = \frac{A_{I,OL}}{1 - A_{I,OL}}$$

$$R_{in,CLOSED} = \frac{r_{\pi 1}}{1 - A_{I,OL}}$$


$$R_{out,CLOSED} = \left( \frac{1}{g_{m2}} + R_F \right) (1 - A_{I,OL})$$

59.

(a)

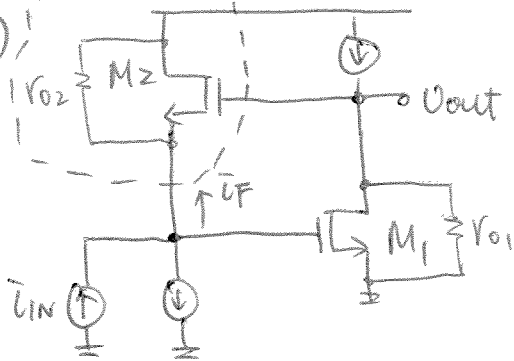

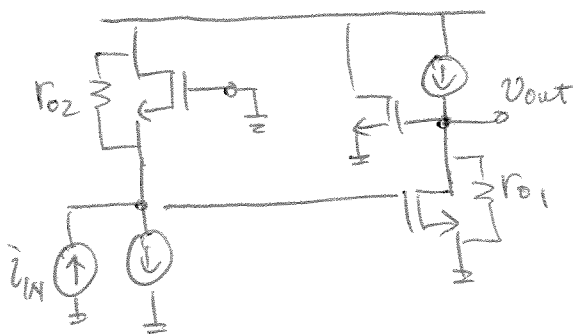
Breaking the feedback network results in the following:



$$R_{OL} = \frac{v_{out}}{i_{IN}} = -(r_{O2} \parallel \frac{1}{g_{m2}}) g_{m1} r_{O1}$$

$$R_{in, OPEN} = r_{O2} \parallel \frac{1}{g_{m2}}$$

$$R_{out, OPEN} = r_{O1}$$

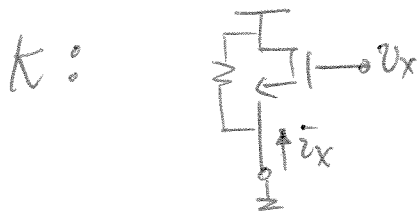



$$k = \frac{i_x}{v_x} = g_{m2}$$

$$\therefore R_{CL} = \frac{R_{OL}}{1 + R_{OL}k} = \frac{(r_{O2} \parallel \frac{1}{g_{m2}}) g_{m1} r_{O1}}{1 + g_{m1} g_{m2} r_{O1} (r_{O2} \parallel \frac{1}{g_{m2}})}$$

$$R_{IN, CLOSED} = \frac{(r_{O2} \parallel \frac{1}{g_{m2}})}{1 + g_{m1} g_{m2} r_{O1} (r_{O2} \parallel \frac{1}{g_{m2}})}$$

$$R_{out, CLOSED} = \frac{r_{O1}}{1 + g_{m1} g_{m2} r_{O1} (r_{O2} \parallel \frac{1}{g_{m2}})}$$

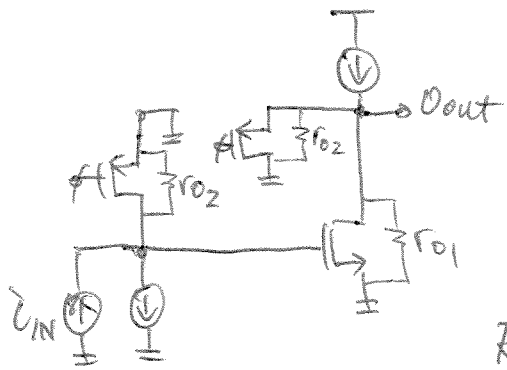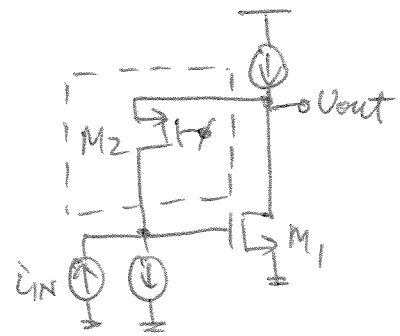(b) Breaking the feedback network results in the following:



$$R_{OL} = \frac{u_{out}}{i_{IN}}$$

$$= -r_{o2} \times g_{m1} [r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}}]$$

$$R_{in, OPEN} = r_{o2}$$

$$R_{out, OPEN} = r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}}$$





$$K = \frac{i_x}{u_x} = -g_{m2}$$

$$\therefore R_{CL} = \frac{R_{OL}}{1 + R_{OL}K} = \frac{-g_{m1}r_{o2} [r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}}]}{1 + g_{m1}g_{m2}r_{o2} [r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}}]}$$

$$R_{in, CLOSED} = \frac{r_{o2}}{1 + R_{OL}K}$$

$$R_{out, CLOSED} = \frac{r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}}}{1 + R_{OL}K}$$

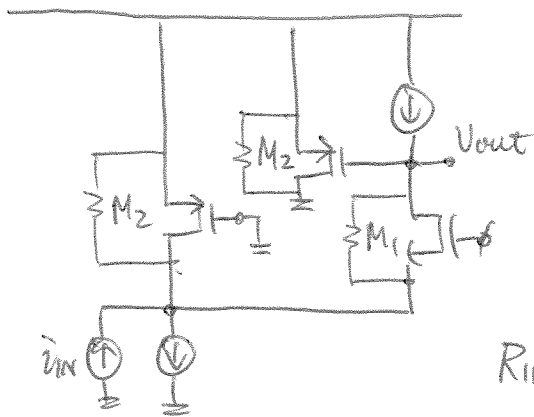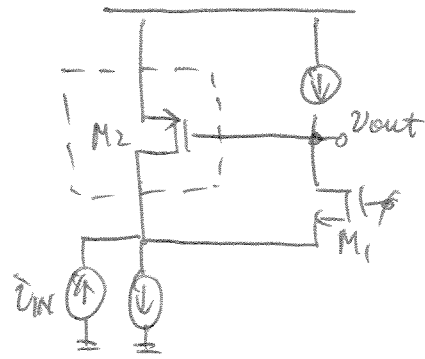(c) Breaking the feedback network results in the following:




$$R_{OL} = \frac{v_{out}}{i_{IN}}$$

$$\approx \left( \frac{1}{g_{m1}} \parallel r_{o2} \right) (1 + g_{m1} r_{o1})$$

$$R_{in, OPEN} \approx \frac{1}{g_{m1}} \parallel r_{o2}$$

$$R_{out, OPEN} = r_{o2} + r_{o1} (1 + g_{m1} r_{o2})$$

K:

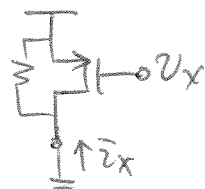

$$K = \frac{i_x}{v_x} = g_{m2}$$


$$\therefore R_{CL} = \frac{R_{OL}}{1 + R_{OL} K} = \frac{\left( \frac{1}{g_{m2}} \parallel r_{o2} \right) (1 + g_{m1} r_{o1})}{1 + g_{m2} \left( \frac{1}{g_{m1}} \parallel r_{o2} \right) (1 + g_{m1} r_{o1})}$$

$$R_{IN, CLOSED} = \frac{\frac{1}{g_{m1}} \parallel r_{o2}}{1 + R_{OL} \cdot K}$$


$$R_{out, CLOSED} = \frac{r_{o2} + r_{o1} (1 + g_{m1} r_{o2})}{1 + R_{OL} \cdot K}$$

60.


(a)

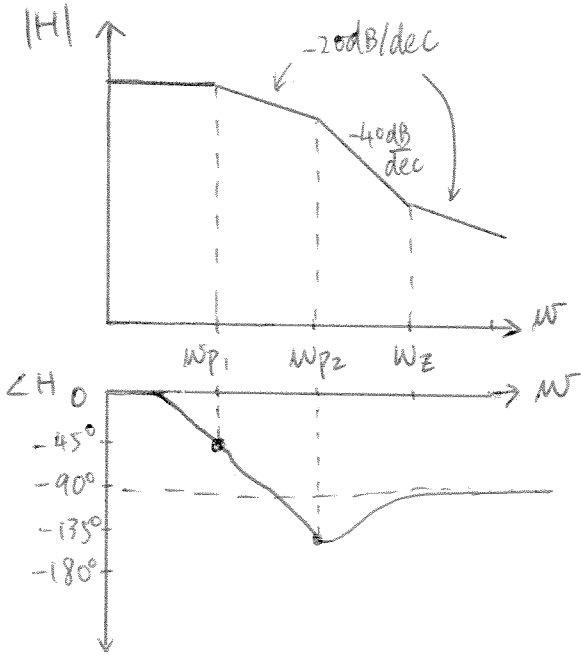


(b)

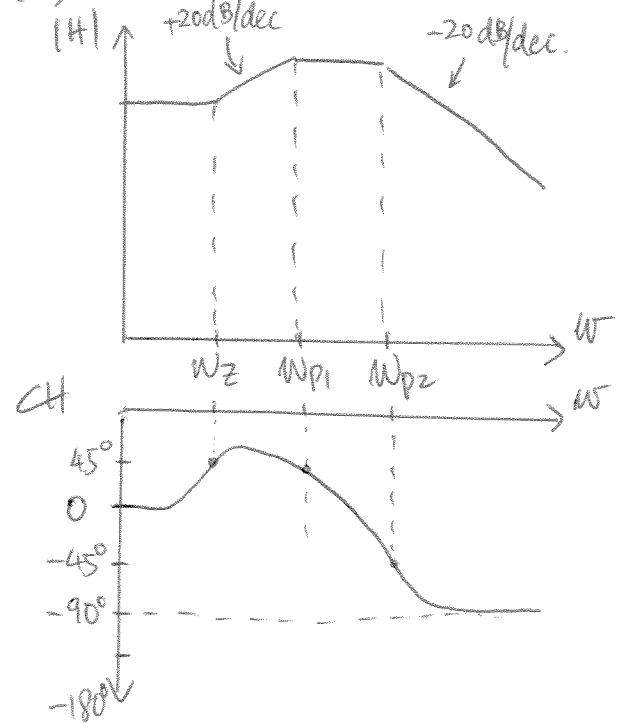

(c)

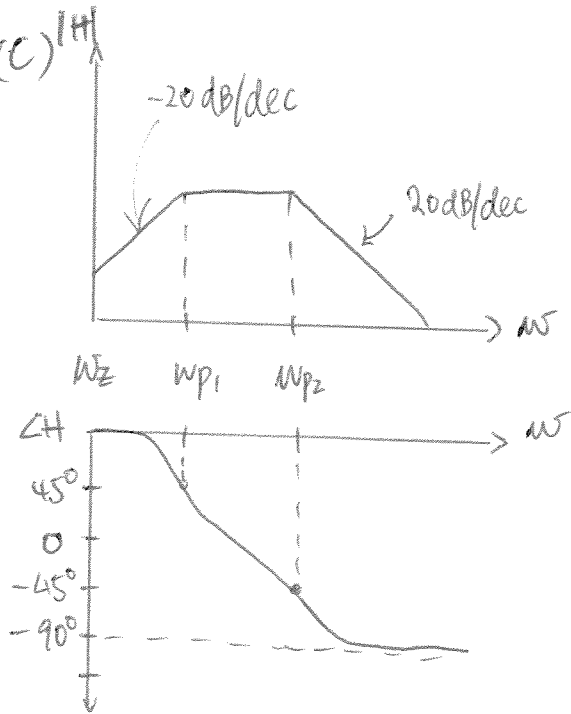



(d)

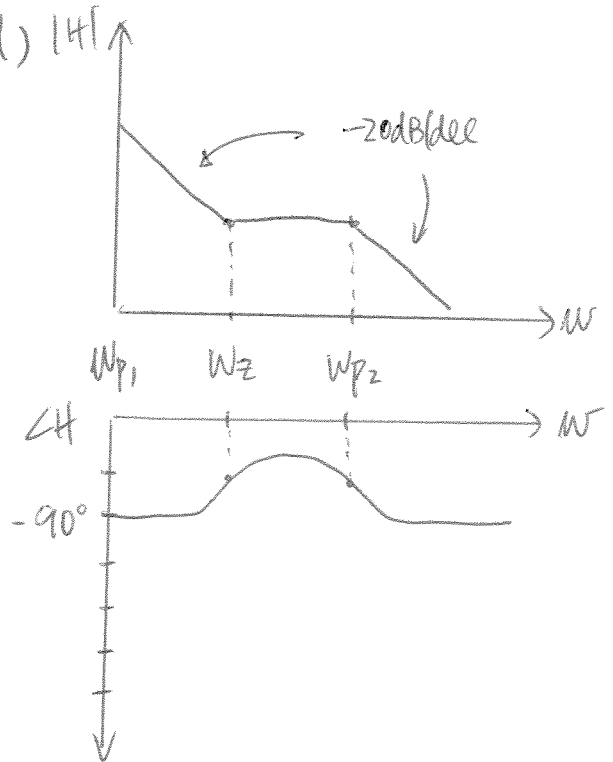

61. As  $\omega_z$  comes closer to  $\omega_{p1}$  or  $\omega_{p2}$ , it cancels out the effect (i.e.  $-20\text{dB/dec}$  decrease) — pole-zero cancellation. It would appear as if nothing occurred at that overlapping frequency.


62.

Calculate  $G_m(s)$  of circuit:

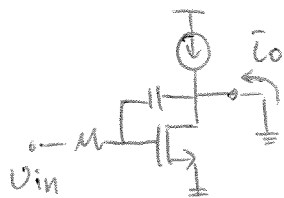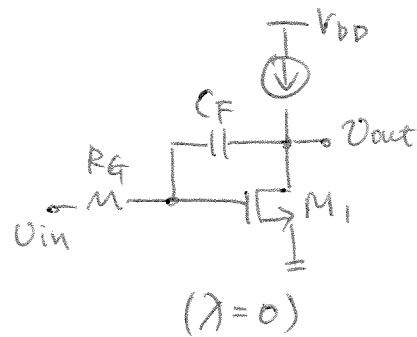



$$G_m = \frac{\bar{i}_o}{v_{in}}$$
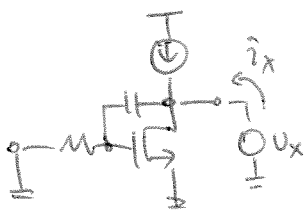
$$= g_{m1} \times \frac{1}{1 + sC_F R_G}$$



$$Z_{out} = \frac{v_x}{i_x} = \frac{1 + sC_F R_G}{sC_F (1 + g_{m1} R_G)}$$

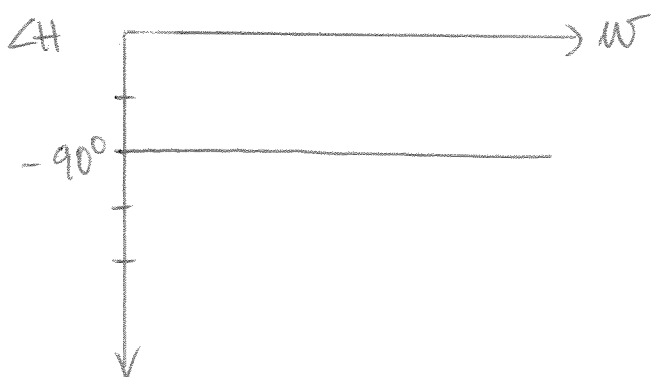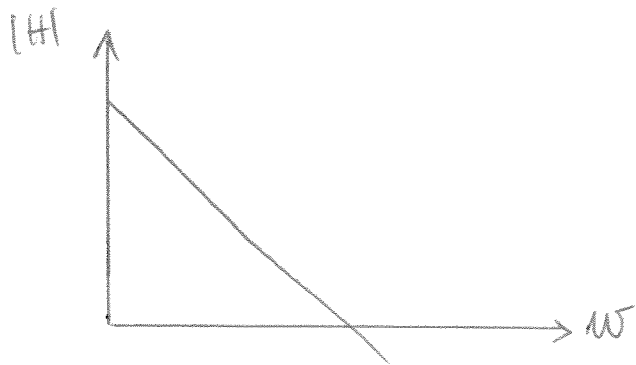
$$\Rightarrow H(s) = G_m \times Z_{out} = \frac{g_{m1}}{g_{m1} R_G + 1} \times \frac{1}{sC_F} = \frac{1}{(g_{m1} R_G + 1) s \left( \frac{C_F}{g_{m1}} \right)}$$



63. By Nyquist Criterion, decreasing  $K$  ( $K \rightarrow 0$ ) eventually leads to  $|KH| < 1$  at  $\angle H = -180^\circ$ , which implies stability.



6A.

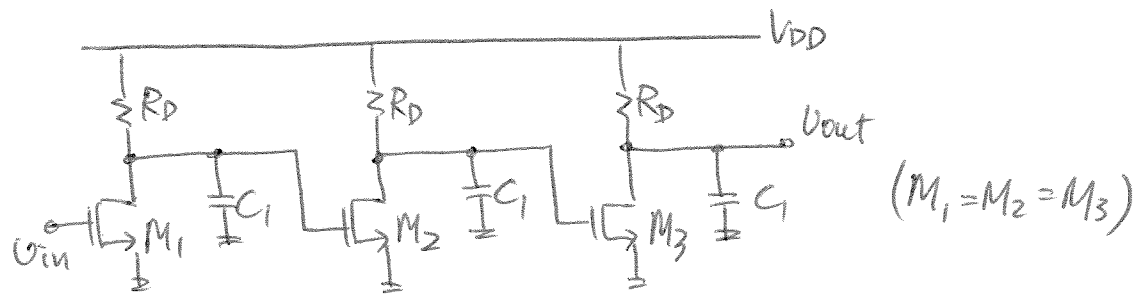

$$H(s) = \frac{V_{out}}{V_{in}}(s) = \frac{(-g_m R_D)^3}{\left(1 + \frac{s}{\omega_p}\right)^3} \quad \text{where } \omega_p = \frac{1}{R_D C_1}$$

$$\begin{aligned} \Rightarrow \angle H(j\omega) &= \angle (-g_m R_D)^3 - \angle \left(1 + j\frac{\omega}{\omega_p}\right)^3 \\ &= 0 - 3 \text{TAN}^{-1}\left(\frac{\omega}{\omega_p}\right) \end{aligned}$$

$$\therefore \angle H \Big|_{\omega=0.1\omega_p} = -3 \text{TAN}^{-1}\left(\frac{0.1\omega_p}{\omega_p}\right) \cong -17.1^\circ$$


$$65. \quad H(s) = \frac{(-g_m R_D)^3}{\left(1 + \frac{s}{\omega_p}\right)^3} \quad (M_1 = M_2 = M_3)$$

$$\Rightarrow |H| \Big|_{\omega=\omega_p} = \frac{|g_m R_D|^3}{\left|(1 + j \frac{\omega_p}{\omega_p})^3\right|} = \frac{(g_m R_D)^3}{(\sqrt{1+1})^3} = \frac{(g_m R_D)^3}{\sqrt{8}}$$

$$\begin{aligned} \Rightarrow 20 \log |H| \Big|_{\omega=\omega_p} &= 20 \log (g_m R_D)^3 - 20 \log \sqrt{8} \\ &\cong 20 \log (g_m R_D)^3 - (9 \text{ dB}) \end{aligned}$$

$\therefore |H|$  falls by 9 dB due to the three coincident poles.

6b.

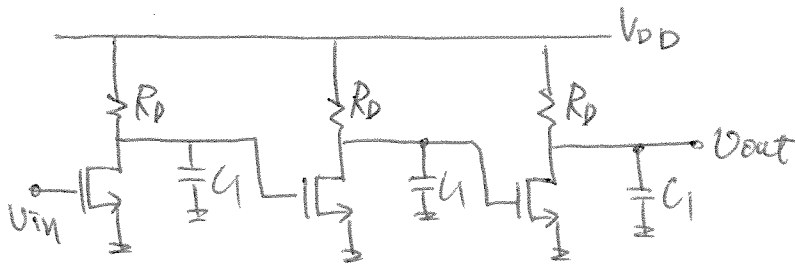


$$\omega_p = \frac{1}{R_D C_1}$$

$$k = 0.1$$

$$H(j\omega) = \frac{(-g_m R_D)^3}{(1 + j\frac{\omega}{\omega_p})^3}$$
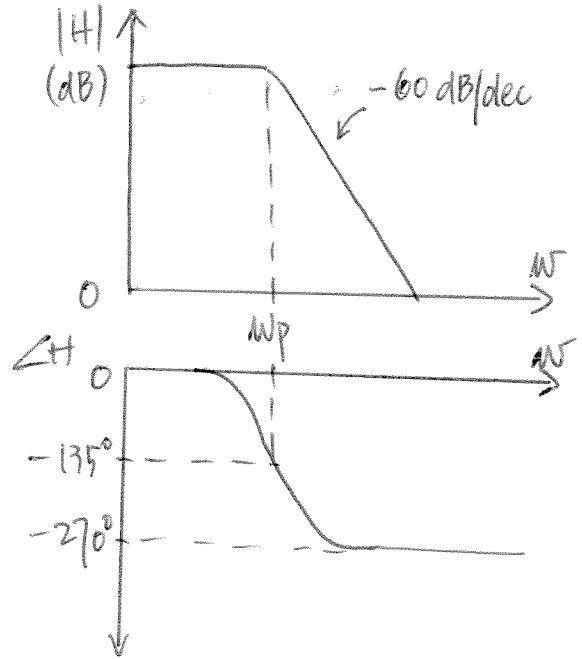
$$\angle H = -3 \tan^{-1}\left(\frac{\omega}{\omega_p}\right)$$




- Need to guarantee that  $|KH| < 1$  when  $\angle H = -180^\circ$ :

$$\angle H = -180^\circ = -3 \tan^{-1}\left(\frac{\omega}{\omega_p}\right) \Rightarrow \omega = \sqrt{3} \omega_p$$

$$|KH(j\omega)|_{\omega=\omega_p\sqrt{3}} = \frac{(g_m R_D)^3}{(\sqrt{1+3})^3} \times 0.1 < 1$$



$$\Rightarrow g_m R_D < \sqrt[3]{80} \approx 8.94$$

67.

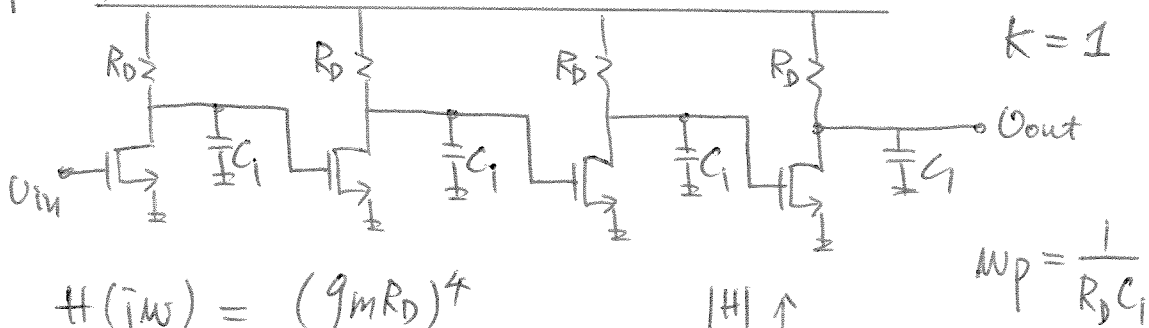

$$H(j\omega) = \frac{(g_m R_D)^4}{(1 + j\frac{\omega}{\omega_p})^4}$$
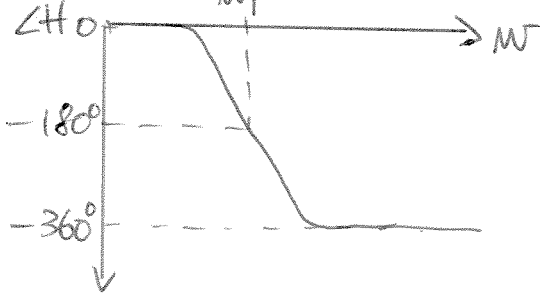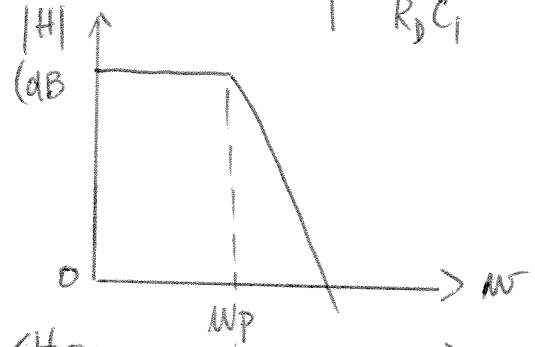
$$\angle H = -4 \tan^{-1}\left(\frac{\omega}{\omega_p}\right)$$



- To guarantee stability,

$$|KH| < 1 \text{ when } \angle H = -180^\circ$$

$$\angle H = -180^\circ = -4 \tan^{-1}\left(\frac{\omega}{\omega_p}\right) \Rightarrow \omega = \omega_p$$

$$|KH| \Big|_{\omega=\omega_p} = \frac{(g_m R_D)^4}{(\sqrt{1+1})^4} < 1$$


$$\Rightarrow g_m R_D < \sqrt{2}$$

This four-pole system implies a lower upper-limit ( $=\sqrt{2}$ ) on  $g_m R_D$ , which makes sense since  $|H|$  drops faster here.

68.

$$H(s) = \frac{A_0}{1 + \frac{s}{\omega_p}}$$

$$k = 1.$$

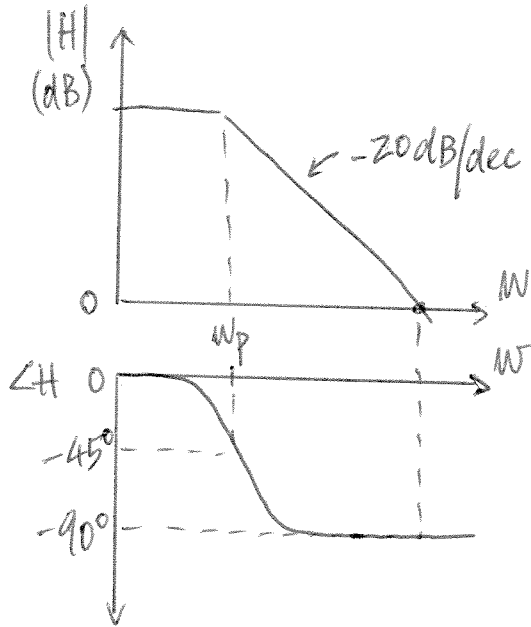


$$\therefore \text{Phase margin} = 180^\circ - 90^\circ = 90^\circ$$

(i.e. system is stable.)

69.  $H(s) = \frac{A_0}{1 + \frac{s}{\omega_p}}$

$K = 0.5$

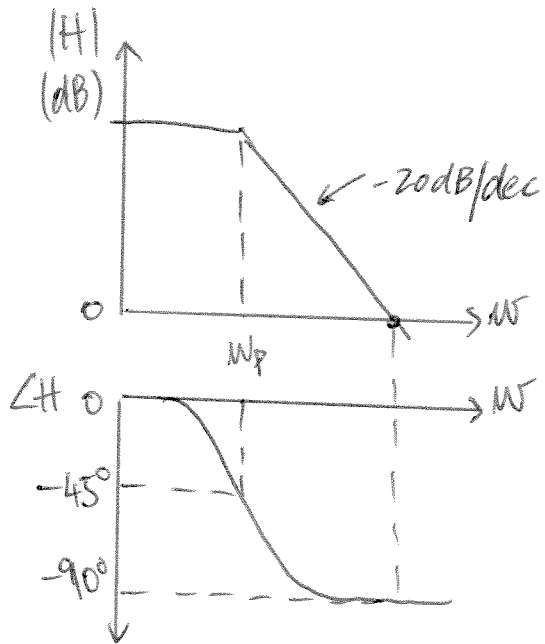

Phase margin =  $90^\circ$   
 (independent of  $K$  for one-pole systems.)

70. All three scenarios will become stable eventually (depending on how far  $w_{ax}$  is from  $w_{px}$ , &  $w_{ax} < w_{px}$ .)

71. In the  $20 \cdot \log |kH|$  vs.  $\log |w|$  plot, the magnitude plot decreases at a rate of 20 dB/dec. between  $w_{p1}$  &  $w_{p2}$ .

$$k=1 \Rightarrow 20 \log |H|$$


$$k=0.5 \Rightarrow 20 \log \left| \frac{H}{2} \right| = 20 \log |H| - 6 \text{ dB}$$

$\therefore k=0.5$  induces a 6dB decrease on the magnitude plot at all frequencies.

$$\Rightarrow \Delta W_{ax} [\log] = \frac{6 \text{ dB}}{20 \text{ dB}} \approx -0.3$$

$$\frac{W_{ax}}{W_{ax}'} = 10^{\frac{6 \text{ dB}}{20 \text{ dB}}} \approx 0.5$$
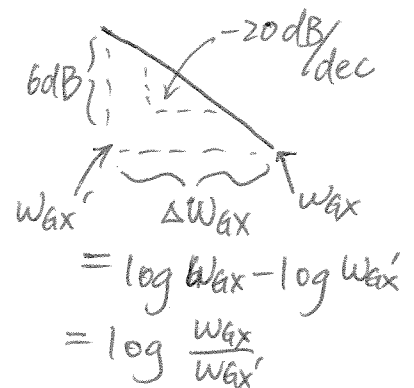
$$\Rightarrow W_{ax}' = \frac{W_{ax}}{0.5} = 2W_{ax}$$



$$\angle H = -\text{TAN}^{-1} \left[ w \left( \frac{1}{w_{p1}} + \frac{1}{w_{p2}} \right) \right] \approx -\text{TAN}^{-1} \left( \frac{w}{w_{p1}} \right) \quad (w_{p2} \gg w_{p1})$$

$\Rightarrow$  Phase plot stays the same with  $k=0.5$ .

$$\text{In original example } \angle H(w_{p2}) \approx -\text{TAN}^{-1} \left( \frac{w_{ax}}{w_{p1}} \right) = -135^\circ$$


$$\angle H(w_{ax}') = \angle H(2w_{ax}) \approx -\text{TAN}^{-1} \left( \frac{2w_{ax}}{w_{p1}} \right)$$

$$\Rightarrow \angle H(w_{ax}') = -\text{TAN}^{-1} [2 \text{TAN } 135^\circ] \approx -116^\circ$$


$$\Rightarrow \text{Phase Margin} = 180^\circ + \angle H(w_{ax}') \approx 63^\circ$$



(72) When  $k$  drops by a factor of 2, the phase margin improves. This is because a lower  $k$  corresponds to shifting the amplitude part of  $kH$  down by 6 dB. (The phase  $\angle kH$  remains unchanged, since phase is only dependent on pole location and is independent of amplitude of  $kH$ .)  
 Thus, the gain  $|kH|$  drops to 0 dB at a lower frequency. This results in a larger phase margin.

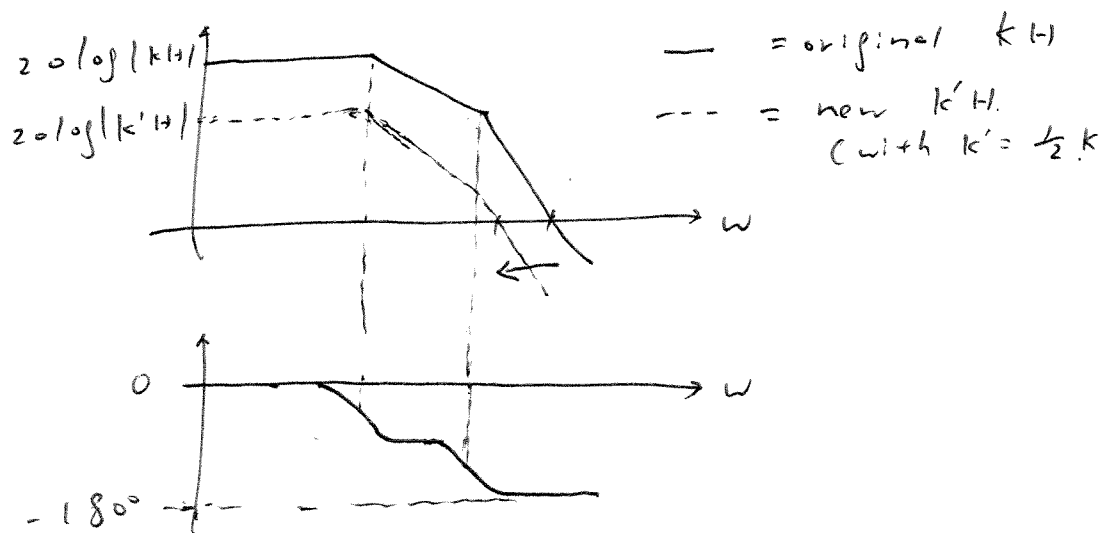

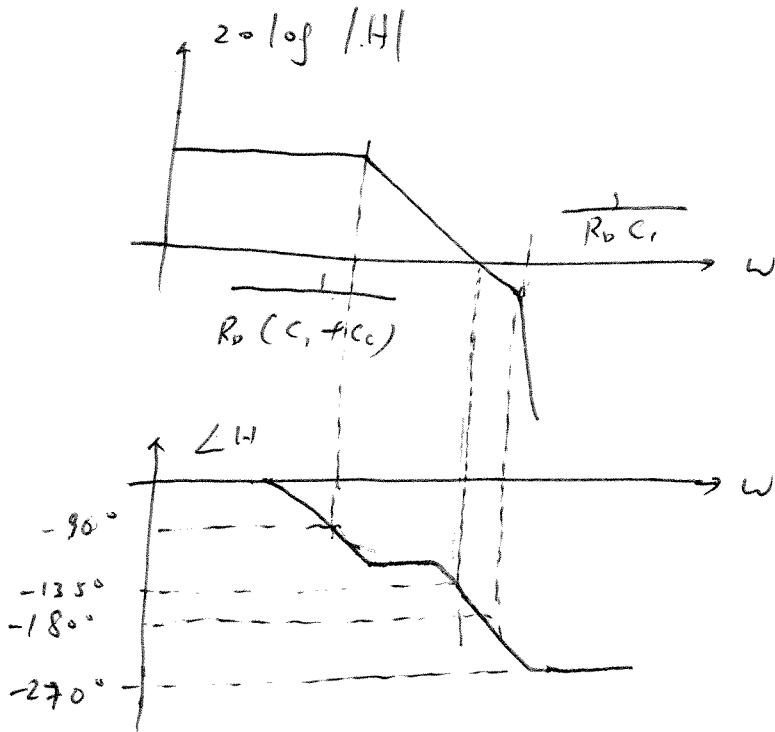73) With the compensation capacitor  $C_c$  in place, the pole associated with  $C_c$  becomes dominant (i.e. at a lower frequency than the other 2 poles at  $\frac{1}{R_D C_1}$ ).



74

Open-loop gain,  $A_o = f_{mN} (r_{oN} // r_{op})$

$$= 50$$

Closed-loop gain,  $\frac{V_{out}}{V_{in}} = \frac{f_{mN} (r_{oN} // r_{op})}{1 + \frac{R_2}{R_1 + R_2} f_{mN} (r_{oN} // r_{op})}$

$$= \frac{50}{1 + \frac{R_2}{R_1 + R_2} \times 50}$$

$$= 4$$

$$\therefore 4 = \frac{50}{1 + \frac{R_2}{R_1 + R_2} \times 50}$$

$$1 + \frac{50 R_2}{R_1 + R_2} = 12.5$$

$$\frac{R_2}{R_1 + R_2} = 0.23$$

Choosing  $r_{o2} // r_{o4} = 5 \text{ k}\Omega$ ,

i.e.  $f_{mN} = 10 \text{ mS} //$

and  $R_1 + R_2 \approx 50 \text{ k}\Omega$ ,

$$\therefore R_2 = 0.23 \times 50 \text{ k}\Omega$$

$$= 11.5 \text{ k}\Omega //$$

$$\text{and } R_1 = 38.5 \text{ k}\Omega //$$

75

Open loop gain,  $A_0 = \beta_m R_D$

(assuming  $R_1 + R_2$  is very large.)

$$\text{i.e. } \beta_m R_D = 10$$

$$\begin{aligned} \text{Closed-loop gain} &= \frac{\beta_m R_D}{1 + \left(\frac{R_2}{R_1 + R_2}\right) \beta_m R_D} \\ &= 2 \end{aligned}$$

$$\therefore \frac{10}{1 + \left(\frac{R_2}{R_1 + R_2}\right) \times 10} = 2$$

$$\frac{R_2}{R_1 + R_2} = 0.4$$

$$\begin{aligned} \text{Closed-loop input impedance} &= \frac{1}{\beta_m} \left[ 1 + \frac{R_2}{R_1 + R_2} \times 10 \right] \\ &= 50 \Omega. \end{aligned}$$

$$\therefore \frac{1}{\beta_m} \times 5 = 50$$

$$\beta_m = 0.15 //$$

$$\therefore R_D = 100 \Omega //$$

$$\begin{aligned} \therefore R_1 + R_2 &= 10 \times 100 \Omega \\ &= 1 \text{ k}\Omega. \end{aligned}$$

$$\therefore R_2 = 400 \Omega //$$

$$R_1 = 600 \Omega //$$

$$\textcircled{76} \quad \text{Open-loop gain} = R_{D1} (g_{m2} R_{D2})$$

$$= 10 \text{ k}\Omega$$

$$\text{Closed-loop gain} = \frac{10 \text{ k}\Omega}{1 + \frac{10 \text{ k}\Omega}{R_F}}$$

$$= 1 \text{ k}\Omega.$$

$$\frac{10}{1 + \frac{10 \text{ k}\Omega}{R_F}} = 1 \text{ k}\Omega$$

$$\therefore R_F = 1.11 \text{ k}\Omega //$$

$$\text{Closed-loop input impedance} = \frac{1}{g_{m1}} (1 + g) ^{-1}$$

$$= 50 \Omega.$$

$$\therefore g_{m1} = 2 \text{ mS} //$$

$$\text{Closed-loop output impedance} = \frac{R_{D2}}{10}$$

$$= 200 \Omega.$$

$$\therefore R_{D2} = 2000 \Omega //$$

$$\therefore R_{D1} = 1 \text{ k}\Omega.$$

$$\therefore g_{m2} = 5 \text{ mS} //$$

(77) Assuming  $R_F$  is very large,

$$\text{open-loop gain} = R_D (\beta m_2 R_C)$$

$$= 10 \text{ k}\Omega$$

$$\text{closed-loop gain} = \frac{10 \text{ k}\Omega}{1 + \frac{10 \text{ k}\Omega}{R_F}}$$

$$= 1 \text{ k}\Omega.$$

$$\therefore R_F = 1.11 \text{ k}\Omega //$$

$$\text{closed-loop input impedance} = \frac{1}{\beta m_1} (1 + \beta)^{-1} = 50 \Omega.$$

$$\beta m_1 = 2 \text{ mS} //$$

$$\text{closed-loop output impedance} = \frac{R_C}{10}$$

$$\therefore R_C = 2000 \Omega //$$

$$R_D = 1 \text{ k}\Omega.$$

$$\therefore \beta m_2 = 5 \text{ mS} //$$

$$\textcircled{78} \text{ a) open-loop gain} = R_c (f_m R_m)$$

$$\approx 20 \text{ k}\Omega$$

$$f_m = \frac{I}{V_T}$$

$$\therefore f_m = \frac{1 \text{ mA}}{26 \text{ mV}} = 38.5 \text{ ms}$$

$$\therefore R_c R_m = \frac{20 \text{ k}\Omega}{38.5 \text{ ms}}$$

$$\text{open-loop output impedance} = R_m \quad (-: V_o = \infty)$$

$$\therefore R_m = 500 \Omega //$$

$$R_c = 1040 \Omega //$$

---

$$\text{b) closed-loop gain} = \frac{20 \text{ k}\Omega}{1 + \frac{20 \text{ k}\Omega}{R_F}}$$

$$= 1 \text{ k}\Omega$$

$$\therefore R_F = 1053 \Omega //$$

$$\text{c) closed-loop input impedance} = \frac{\frac{1}{38.5 \text{ ms}}}{1 + \frac{20 \text{ k}}{1053}}$$

$$= 1.30 \Omega //$$

$$\text{closed-loop output impedance} \approx (500) \left( \frac{1}{20} \right)$$

$$= 25 \Omega //$$

79

Open-loop voltage gain

$$= \frac{R_{D1}}{\frac{1}{g_{m1}} + R_1 // R_2} \cdot [g_{m2} (R_1 // R_2)]$$

$$= 20 \quad \text{--- (1)}$$

$$\text{closed-loop gain} = \frac{20}{1 + 20 \left( \frac{R_2}{R_1 + R_2} \right)} = 4$$

$$\therefore \frac{R_2}{R_1 + R_2} = 0.2 \quad \text{--- (2)}$$

Open-loop output impedance =  $R_1 + R_2$

$$= 2 \text{ k}\Omega$$

$$\therefore R_2 = 0.4 \text{ k}\Omega //$$

$$R_1 = 1.6 \text{ k}\Omega //$$

From (1),

$$\frac{R_{D1}}{\frac{1}{g_{m1}} + 2 \text{ k}\Omega} [g_{m2} \times 320 \Omega] = 20$$

$$\frac{g_{m1} R_{D1}}{1 + 2 \text{ k} g_{m1}} \times g_{m2} = 0.0625$$

$$\text{Setting } g_{m1} = g_{m2} = 20 \text{ mS} //$$

$$R_{D1} = 6400 \Omega //$$

To minimize power consumption,  $g_{m1}$  and  $g_{m2}$  should be minimized. (and  $R_D$  maximized)



80

$$\text{Since } A_{OL} = \frac{f_{m1} \left( \frac{1}{f_{m2}} + \frac{R_1 // R_2}{\beta_2 + 1} \right)}{1 + f_{m1} \left( \frac{1}{f_{m2}} + \frac{R_1 // R_2}{\beta_2 + 1} \right)} \times f_{m2} (R_1 + R_2)$$

$$R_{out, closed} = \frac{R_1 + R_2}{1 + A_{OL} k}$$

$$\therefore A_{OL} = 2$$

$$\therefore 2 = \frac{A_{OL}}{1 + A_{OL} k}$$

$$\text{set } f_{m1} = f_{m2} = 50 \text{ mV}, \quad (R_1 + R_2) = 1 \text{ k}$$

$$A_{OL} = \frac{50 \text{ mV} \left( \frac{1}{50 \text{ mV}} + \frac{R_1 // R_2}{101} \right)}{1 + 50 \text{ mV} \left( \frac{1}{50 \text{ mV}} + \frac{R_1 // R_2}{101} \right)} \times 50 \text{ mV} (1 \text{ k})$$

$$\approx \frac{1 + 10^{-5} (R_1 // R_2)}{2 + 10^{-5} (R_1 // R_2)} \times 50$$

$$\approx 25$$

$$\therefore 2 = \frac{25}{1 + .25 \text{ k}}$$

$$\therefore k = 0.46 \quad \left[ \therefore R_1 = 460 \Omega, \quad R_2 = 540 \Omega \right]$$

$$R_{out, closed} = \frac{1 \text{ k}}{1 + 25 \times 0.46}$$

$$= 80 \Omega //$$

$$\textcircled{81} \text{ open-loop gain } (A_{OL}) = -\beta m_1 (R_F // r_{\pi 1}) / x \\ \left[ R_C // [r_{\pi 2} + (\beta_2 + 1) R_F] \right]$$

$$A_{CL} = \frac{A_{OL}}{1 + A_{OL} \frac{1}{R_F}}$$

$$\therefore A_{CL} = 1000 \Omega$$

$$1000 = \frac{A_{OL}}{1 + \frac{A_{OL}}{R_F}}$$

$$R_{in, \text{closed}} = \frac{R_F // r_{\pi 1}}{1 + \frac{A_{OL}}{R_F}} = 50 \Omega$$

$$R_{out, \text{closed}} = \frac{R_C}{1 + \frac{A_{OL}}{R_F}} = 50 \Omega$$

setting  $R_F = 1200 \Omega$ .

$$\therefore A_{OL} = 6000 \Omega //$$

$$\therefore r_{\pi 1} = 400 //$$

$$\beta m_2 = 2.5 \text{ mV} //$$

Assume  $\beta_2 = 100$ , and  $\beta m_1 = \beta m_2$ ,


$$R_C = 8570 \Omega //$$

$$1. \quad A_v = \frac{g_{m1} R_L}{1 + g_{m1} R_L}$$

$$(a) \quad 0.8 = \frac{g_{m1} (85\Omega)}{1 + g_{m1} (85\Omega)}$$

$$\Rightarrow g_{m1} = 0.5 = \frac{I_c}{V_T} = \frac{I_1}{V_T}$$

$$\therefore I_1 = 13 \text{ mA}$$

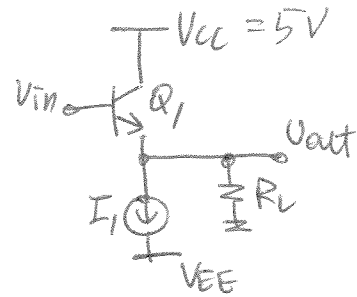

$$P_{\text{LOAD}} = 0.5 \text{ W}$$

$$R_L = 85\Omega$$

(Assume  $V_{\text{out}}$  biased at

$$V_{\text{BE(ON)}_1} \approx 800 \text{ mV}$$

(b) When  $V_{\text{in}} = V_p = V_{\text{cc}}$ ,  $V_{\text{out}} \approx V_{\text{cc}} - V_{\text{BE(ON)}_1}$

$$I_{c1} = I_1 + \frac{V_{\text{out}}}{R_L} \Rightarrow I_{c1} = I_1 + \frac{5 - 0.8}{8} \approx 0.54 \text{ A}$$

$$\Rightarrow g_{m1} = \frac{I_{c1}}{V_T} = \frac{0.54 \text{ A}}{0.026 \text{ V}} = 20.8 \text{ S}$$


$$\Rightarrow A_v \Big|_{V_{\text{in}}=V_p} = \frac{g_{m1} R_L}{1 + g_{m1} R_L} = \frac{(20.8 \text{ S})(85\Omega)}{1 + (20.8 \text{ S})(85\Omega)} \approx 0.99$$

2.

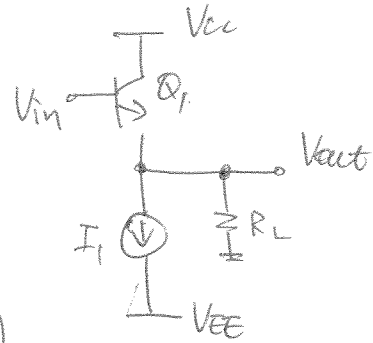(a)  $I_1 = V_p / R_L$        $V_p \gg V_T$

$$A_v = \frac{I_c R_L}{I_c R_L + V_T}$$

$$= \frac{\frac{I_c}{I_1} V_p}{\frac{I_c}{I_1} V_p + V_T} = \frac{V_p}{V_p + V_T} \quad (\approx 1)$$



(b) When  $V_{out} = V_p$ ,  $I_{c1} = I_1 + \frac{V_{out}}{R_L} = \frac{V_p}{R_L} + \frac{V_p}{R_L}$   
 $= \frac{2V_p}{R_L}$


$$\therefore A_v = \frac{\left(\frac{2V_p}{R_L}\right) R_L}{\left(\frac{2V_p}{R_L}\right) R_L + V_T} = \frac{2V_p}{2V_p + V_T} \quad \left(\approx \frac{2V_p}{2V_p} = 1\right)$$

$$\Delta A_v = \frac{\frac{2V_p}{2V_p + V_T} - \frac{V_p}{V_p + V_T}}{\frac{V_p}{V_p + V_T}} = \frac{V_T}{2V_p + V_T} \quad \left(\approx \frac{V_T}{V_p}\right)$$

3.  $A_v = 0.7$        $R_L = 4\Omega$

$Q_1$  shuts off when:

$$I_1 = \frac{V_P}{R_L}$$

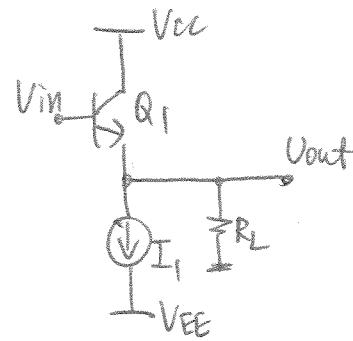

• Suppose  $V_{out} = V_P \sin \omega t$ .       $(\omega = \frac{2\pi}{T})$

$$P_{R_L, AVG} = \frac{1}{T} \int_0^T \frac{(V_{out})^2}{R_L} dt = \frac{1}{T} \int_0^T \frac{V_P^2 \sin^2 \omega t}{R_L} dt$$


$$\therefore \text{Largest power (average)} = \frac{1}{2} \frac{(I_1 R_L)^2}{R_L} = \frac{1}{2} V_P^2 / R_L$$

$$A_v = 0.7 = \frac{g_{m1} R_L}{1 + g_{m1} R_L} \Rightarrow g_{m1} = \frac{A_v}{(1 - A_v) R_L} = \frac{0.7}{(1 - 0.7)(4)} = 0.58 \text{ S}$$

$$\Rightarrow I_{C1} (= I_1) = g_{m1} V_T = 0.015 \text{ A}$$

$$\therefore P_{AV, MAX} = \frac{1}{2} I_1^2 R_L = \frac{1}{2} (0.015 \text{ A})^2 (4\Omega) = 0.45 \text{ W}$$
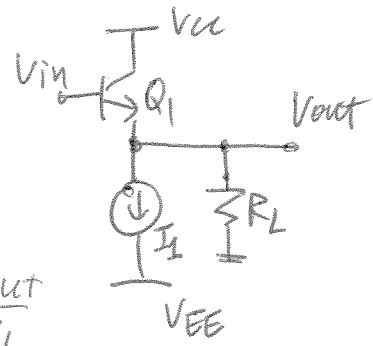
$$4. A_v = \frac{g_{m1} R_L}{1 + g_{m1} R_L} \quad (g_m = \frac{I_{C1}}{V_T})$$



- $Q_1$  shuts off when  $I_1 = -\frac{V_{out}}{R_L}$   
 $\Rightarrow V_p = I_1 \times R_L$

$$g_{m1} = \frac{A_v}{(1 - A_v) R_L} = \frac{I_{C1}}{V_T} \Rightarrow I_{C1} = \frac{V_T A_v}{R_L (1 - A_v)} (= I_1)$$

- Power delivered to  $R_L$ :

$$P_{R_L} = \frac{1}{T} \int_0^T \frac{V_{out}^2}{R_L} dt = \frac{1}{T} \int_0^T \frac{V_p^2 \sin^2 \omega t}{R_L} dt$$

$$= \frac{1}{2} \frac{V_p^2}{R_L}$$

$$\therefore \text{Maximum power} = \frac{1}{2} \frac{(I_1 R_L)^2}{R_L}$$

$$= \frac{1}{2} \left[ \frac{V_T A_v}{(1 - A_v)} \right]^2 \cdot \frac{1}{R_L}$$

5.

(a) By KCL,

$$I_1 = I_{S1} \cdot \exp\left(\frac{V_{in} - V_{out}}{V_T}\right) + \frac{V_{cc} - V_{out}}{R_L}$$


$$\Rightarrow V_{in} = V_{out} + V_T \ln\left(\frac{I_1}{I_{S1}} - \frac{V_{cc} - V_{out}}{I_{S1} R_L}\right)$$

$$= 0 \quad (X) \text{—no solution}$$

$$\therefore V_{out} = 5 - I_1 R_L = 4.84 \text{ V}$$

(i.e.  $Q_1$  is off.)

Assume  $V_{cc} = 5 \text{ V}$

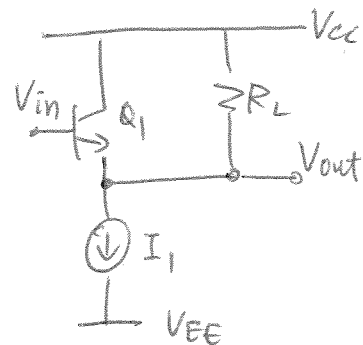

$$I_{S1} = 5 \cdot 10^{-17} \text{ A}$$

$$R_L = 8 \Omega$$

$$I_1 = 20 \text{ mA}$$

$$(b) (0.01)I_1 = I_1 - \frac{V_{cc} - V_{out}}{R_L}$$

$$\Rightarrow V_{out} = 4.84 \text{ V}$$

$$I_{C1} = (0.01)I_1 = I_{S1} \exp\left(\frac{V_{in} - V_{out}}{V_T}\right)$$

$$\Rightarrow V_{in} = V_{out} + V_T \ln\left(0.01 \frac{I_1}{I_{S1}}\right)$$

$$= 4.84 + (0.026) \ln\left(0.01 \frac{20 \text{ mA}}{5 \cdot 10^{-17} \text{ A}}\right)$$

$$\approx 5.59 \text{ V}$$

(exceeds  $V_{cc}$ )

b.

(a) Calculate  $V_{BE}$  for

$$\underline{V_{in} = 1 \text{ V} :}$$

$$I_{C1} = I_1 + \frac{V_{out}}{R_L}$$

$$\Rightarrow I_{S1} \cdot \exp\left(\frac{V_{in} - V_{out}}{V_T}\right) = I_1 + \frac{V_{out}}{R_L}$$

Solving for  $V_{out}$  gives:

$$V_{out} \approx 0.113 \text{ V}$$


$$\therefore V_{BE} \Big|_{V_{in}=1\text{V}} = V_{in} - V_{out} = 1 - 0.113 = 0.887 \text{ V}$$

$$\underline{V_{in} = -1 \text{ V} :}$$

$$I_{C1} = I_1 + \frac{-V_{out}}{R_L} \Rightarrow I_{S1} \exp\left(\frac{V_{in} - V_{out}}{V_T}\right) = I_1 - \frac{V_{out}}{R_L}$$

Solving for  $V_{out}$  gives:  $V_{out} \approx -1.95 \text{ V}$

$$\therefore V_{BE} \Big|_{V_{in}=-1\text{V}} = V_{in} - V_{out} = -1 - (-1.95\text{V}) = 0.95 \text{ V}$$

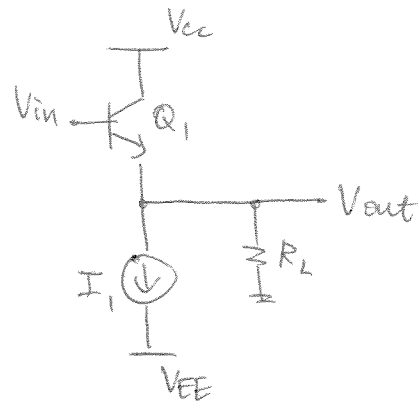


$$I_{S1} = 6 \cdot 10^{-17} \text{ A}$$

$$R_L = 85 \Omega$$

$$I_1 = 25 \text{ mA}$$

$$V_P = 1 \text{ V}$$

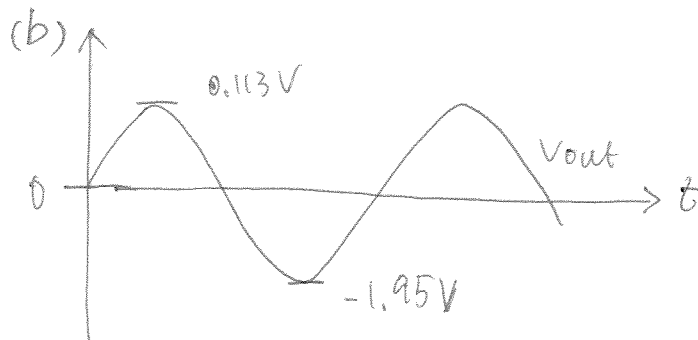



7. Determine  $V_p$  such that

$$V_{BE} \Big|_{V_{in}=+V_p} - V_{BE} \Big|_{V_{in}=-V_p} = 10 \text{ mV}$$

$$\Rightarrow (V_p^+ - V_{out,+}) - (V_p^- - V_{out,-}) = 10 \text{ mV}$$

$$I_S \exp\left(\frac{V_p^+ - V_{out,+}}{V_T}\right) = I_1 + \frac{V_{out,+}}{R_L} \quad \text{--- (1)}$$


$$I_S \exp\left(\frac{V_p^- - V_{out,-}}{V_T}\right) = I_1 - \frac{V_{out,-}}{R_L} \quad \text{--- (2)}$$

Iterate (1) & (2). This gives:

$$V_p \approx 0.7 \text{ V}$$

$$\Rightarrow \text{Nonlinearity} = \frac{10 \text{ mV}}{0.7 \times 2} \approx 0.007.$$

8.

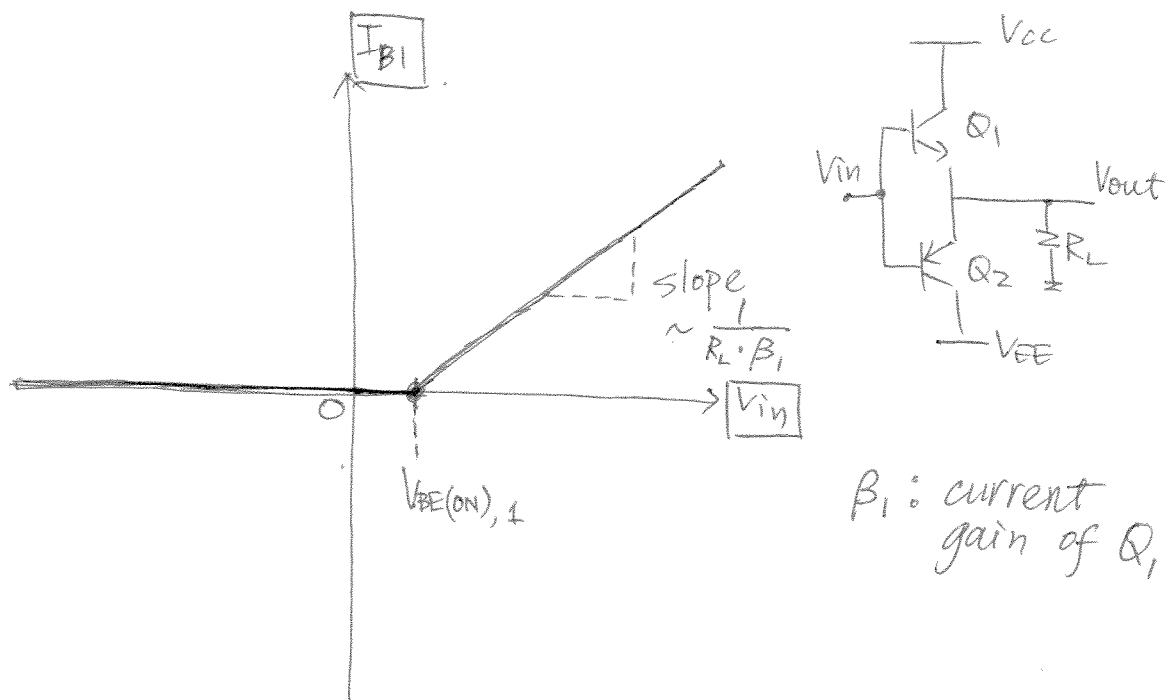

- $Q_1$  is on whenever  $V_{in} \geq V_{BE(ON),1}$ . In this region,

$$V_{out} = V_{in} - V_{BE(ON),1}$$

$$I_{C1} = \frac{V_{out}}{R_L}$$

$$\therefore I_{B1} = \frac{I_{C1}}{\beta} = \frac{V_{out}}{\beta R_L} = \frac{V_{in} - V_{BE(ON),1}}{\beta R_L}$$

9.

(a) To guarantee  $Q_1$  on,

$$\bullet V_{out} \approx V_{in} - V_{BE(ON)1} = -800 \text{ mV}$$


$$\Rightarrow I_{C1} = I_1 + \frac{V_{out}}{R_L} \quad (Q_2 \text{ is off})$$

$$\bullet I_{C1} \geq 0 \Rightarrow I_1 + \frac{V_{out}}{R_L} \geq 0$$

$$\Rightarrow I_1 + \frac{-800 \text{ mV}}{R_L} \geq 0$$

$$\therefore I_1 R_L \geq 800 \text{ mV}$$

————— ①

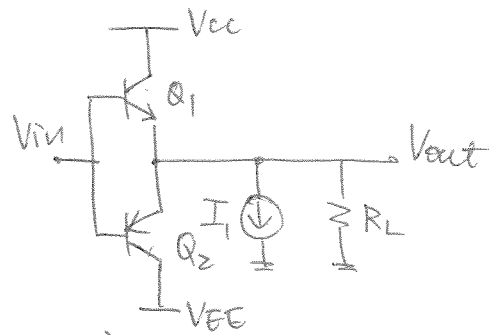

$$I_{S2} = 6 \cdot 10^{-17} \text{ A}$$

$$R_L = 8 \Omega$$

(b) When  $Q_2$  turns on,

$$-\frac{V_{out}}{R_L} - I_1 = I_{C2}$$

$$\Rightarrow -\frac{V_{out}}{R_L} - \left(\frac{800 \text{ mV}}{R_L}\right) = I_{S2} \exp\left(\frac{V_{BE2}}{V_T}\right)$$


$$\begin{aligned} \Rightarrow V_{out} &= -R_L I_{S2} \cdot \exp\left(\frac{V_{BE2}}{V_T}\right) - 0.8 \\ &= -(8 \Omega)(6 \cdot 10^{-17} \text{ A}) \exp\left(\frac{0.8}{0.026}\right) - 0.8 \\ &\approx -0.81 \text{ V} \end{aligned}$$

$$\therefore V_{in} = V_{out} - |V_{BE(ON)2}| = -0.81 - 0.8 = -1.61 \text{ V}$$

10. Consider two scenarios:

- In gain regions ( $|V_{in}| \geq |V_{BE(on)}|$ ),  $V_{out}$  tracks  $V_{in}$ .
- In dead zone, both transistors shut off.

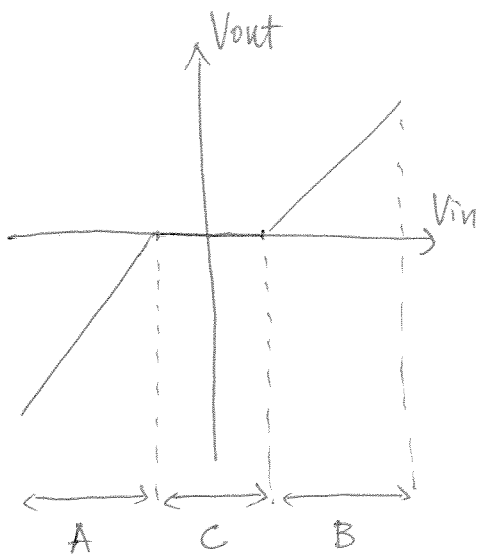In both cases,  $V_{out}$  has an important role. Current source  $I_1$  affects the input/output characteristic by modulating  $V_{out}$ :



I/O characteristic of push-pull stage.

Consider region A:

$$I_{C2} + I_1 = \frac{-V_{out}}{R_L}$$

$\therefore I_1 \uparrow \downarrow \Rightarrow |V_{BE2}| = |V_{out} - V_{in}|$  stays relatively constant.

( $Q_2$  absorbs/sinks all the currents from  $I_1$  in order to have the same  $|V_{BE2}|$ )

Consider region B:

$$I_{C1} = I_1 + \frac{V_{out}}{R_L}$$

$\therefore I_1 \uparrow \downarrow \Rightarrow |V_{BE1}| = |V_{in} - V_{out}|$  stays relatively constant.

( $Q_1$  provides/sources current to  $I_1$  in order to have  $|V_{BE1}|$  constant.)

Consider region C: (Dead zone).

$$I_1 = -\frac{V_{out}}{R_L} \quad (\text{Both transistors off})$$



$$\therefore I_1 \uparrow \Rightarrow V_{out} \downarrow$$

$$I_1 \downarrow \Rightarrow V_{out} \uparrow$$

i.e. In the dead zone,  $V_{out}$  is predominantly controlled by  $I_1$ . One can use this to control  $V_{out}$  and effectively shift the region of dead zone.

( $\because V_{out}|_{v_{in}=0} \neq 0$  anymore)

11.

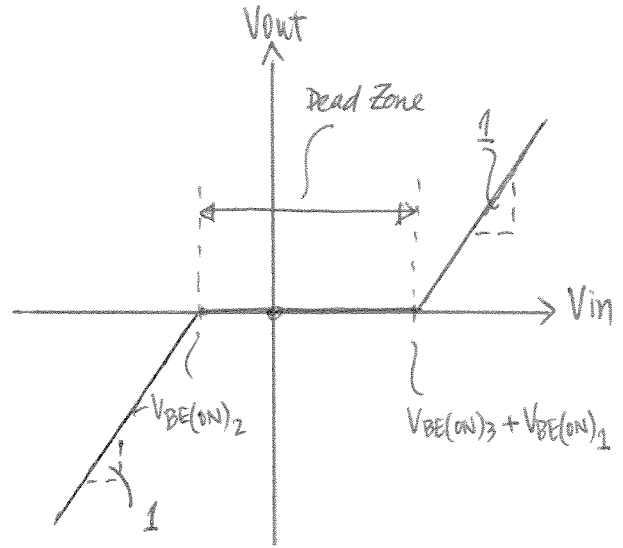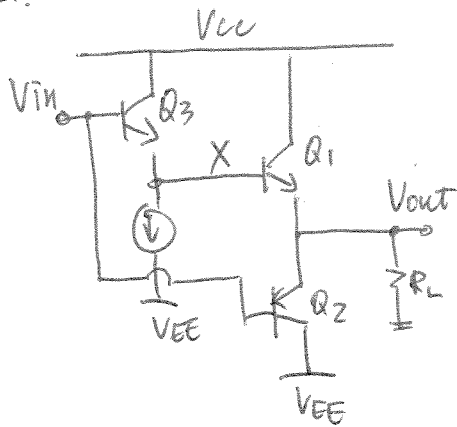



## Analysis

Dead Zone

$$= |V_{BE(ON)2}| + V_{BE(ON)3} + V_{BE(ON)1}$$

- $(0 < V_{in} < V_{BE(ON)3} + V_{BE(ON)1})$ :
  - $Q_1$  is OFF ( $V_{in} < V_{BE(ON)1}$ )
  - $Q_2$  is OFF ( $V_{BE2}$  reverse-biased) $\Rightarrow V_{out} = 0$
- $(-|V_{BE(ON)2}| < V_{in} < 0)$ :
  - $Q_1, Q_2$  OFF. $\Rightarrow V_{out} = 0$
- $(V_{BE(ON)3} + V_{BE(ON)1} < V_{in} < V_{cc})$ 
  - $Q_1$  ON
  - $Q_2$  OFF $\Rightarrow V_{out} = V_{in} - V_{BE(ON)3} - V_{BE(ON)1}$
- $(-|V_{EE}| < V_{in} < -|V_{BE(ON)2}|)$ 
  - $Q_2$  ON
  - $Q_1$  OFF $\Rightarrow V_{out} = V_{in} + |V_{BE(ON)2}|$

12.

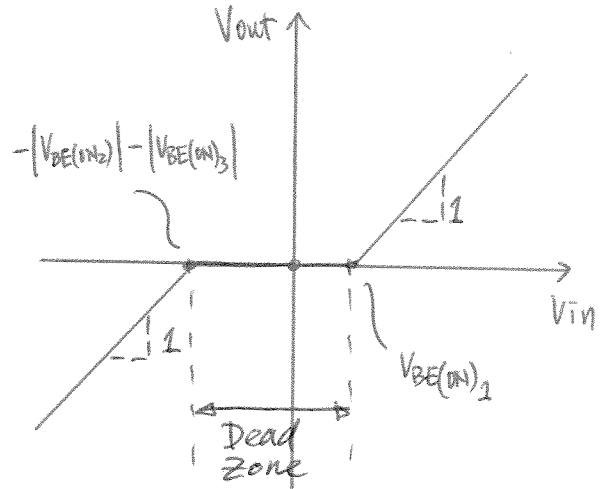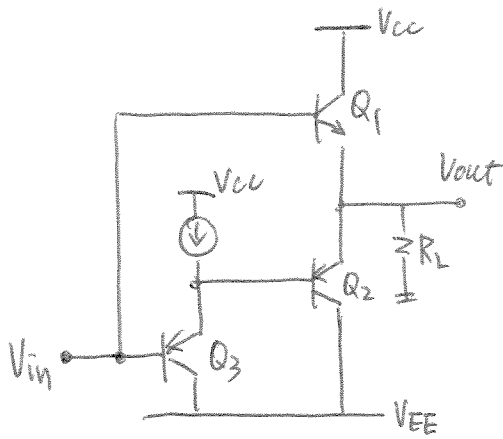

$$\underline{-V_{EE} < V_{in} < -(|V_{BE(on)2}| + |V_{BE(on)3}|) :}$$

$$\Rightarrow \left. \begin{array}{l} Q_2, Q_3 \text{ ON} \\ Q_1 \text{ OFF} \end{array} \right\} V_{out} = V_{in} + |V_{BE(on)3}| + |V_{BE(on)2}|$$

$$\underline{-(|V_{BE(on)2}| + |V_{BE(on)3}|) < V_{in} < V_{BE(on)1} :}$$

$$\Rightarrow Q_1, Q_2 \text{ OFF} \Rightarrow V_{out} \cong 0$$

$$\underline{V_{BE(on)1} < V_{in} < V_{CC} :}$$

$$\Rightarrow \left. \begin{array}{l} Q_1 \text{ ON} \\ Q_2, Q_3 \text{ OFF} \end{array} \right\} V_{out} = V_{in} - V_{BE(on)1}$$

$$\text{Dead Zone} = V_{BE(on)1} + |V_{BE(on)2}| + |V_{BE(on)3}|$$

13.

(a)

$$\underline{-|V_{EE}| < V_{in} < -|V_{t,p}| :}$$


$$\Rightarrow \left. \begin{array}{l} M_1 \text{ OFF} \\ M_2 \text{ ON} \\ \text{(saturation)} \end{array} \right\} V_{out} = V_{in} + V_{sg,2}$$

$$\underline{V_{cc} > V_{in} > V_{t,n} :}$$

$$\Rightarrow \left. \begin{array}{l} M_1 \text{ ON} \\ M_2 \text{ OFF} \end{array} \right\} V_{out} = V_{in} - V_{gs,1}$$

$$\underline{-|V_{t,p}| < V_{in} < V_{t,n} :}$$
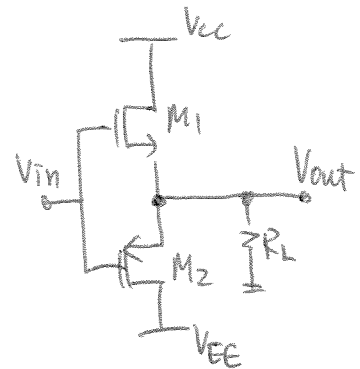
$$M_1, M_2 \text{ OFF} \Rightarrow V_{out} = 0$$




Ignore body effect.

$\Rightarrow M_1$  &  $M_2$  can never on at the same time.

For MOS,  $I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{gs} - |V_t|)^2$  - saturation region.

$$\Rightarrow M_1 \text{ ON: } \frac{V_{out}}{R_L} = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{t,n})^2, V_{out} > 0$$
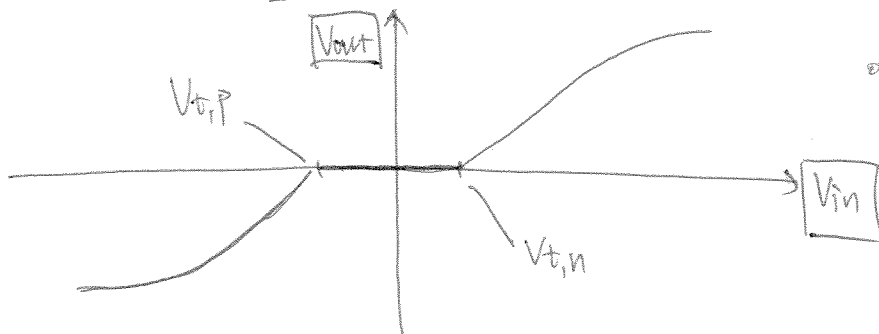
$$M_2 \text{ ON: } -\frac{V_{out}}{R_L} = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{out} - V_{in} - V_{t,p})^2, V_{out} < 0$$




• Solve for  $V_{out}$  in both cases.



(b) Outside dead zone

⇒ either  $M_1$  or  $M_2$  is on.


• For positive inputs:

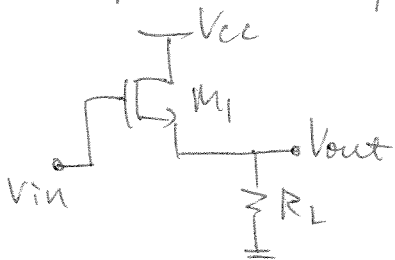

Source follower:

$$\therefore \frac{V_{out}}{V_{in}} = \frac{g_{m1}}{1 + g_{m1}R_L}$$

• For negative inputs:


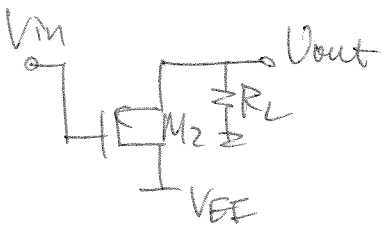


Source follower:

$$\therefore \frac{V_{out}}{V_{in}} = \frac{g_{m2}}{1 + g_{m2}R_L}$$

14. Dead zone :



$$V_{out} \in [-|V_{BE(on)2}|, V_{BE(on)3} + V_{BE(on)1}]$$

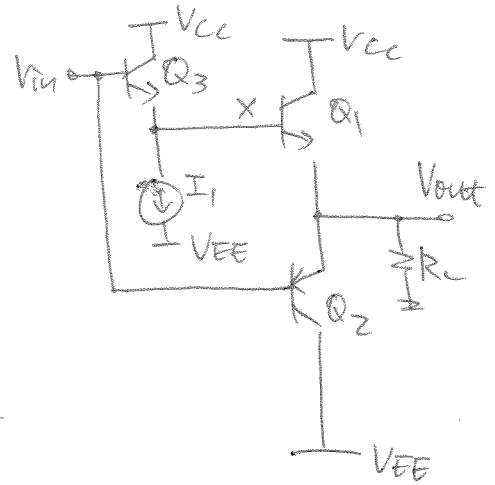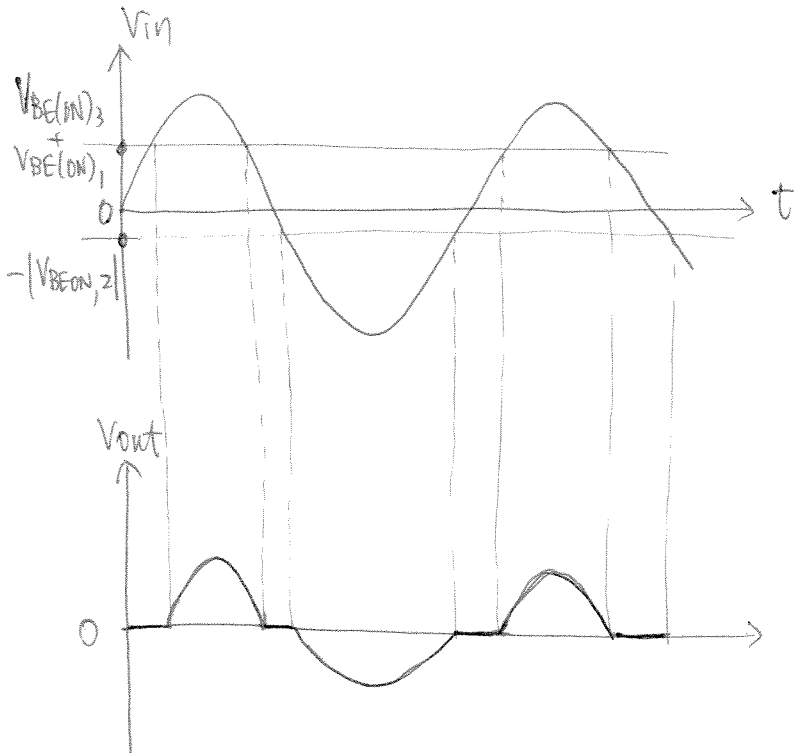




15.

Dead zone:

$$V_{out} \in [-(|V_{BE,ON,2}| + |V_{BE,ON,3}|), V_{BE,ON,1}]$$

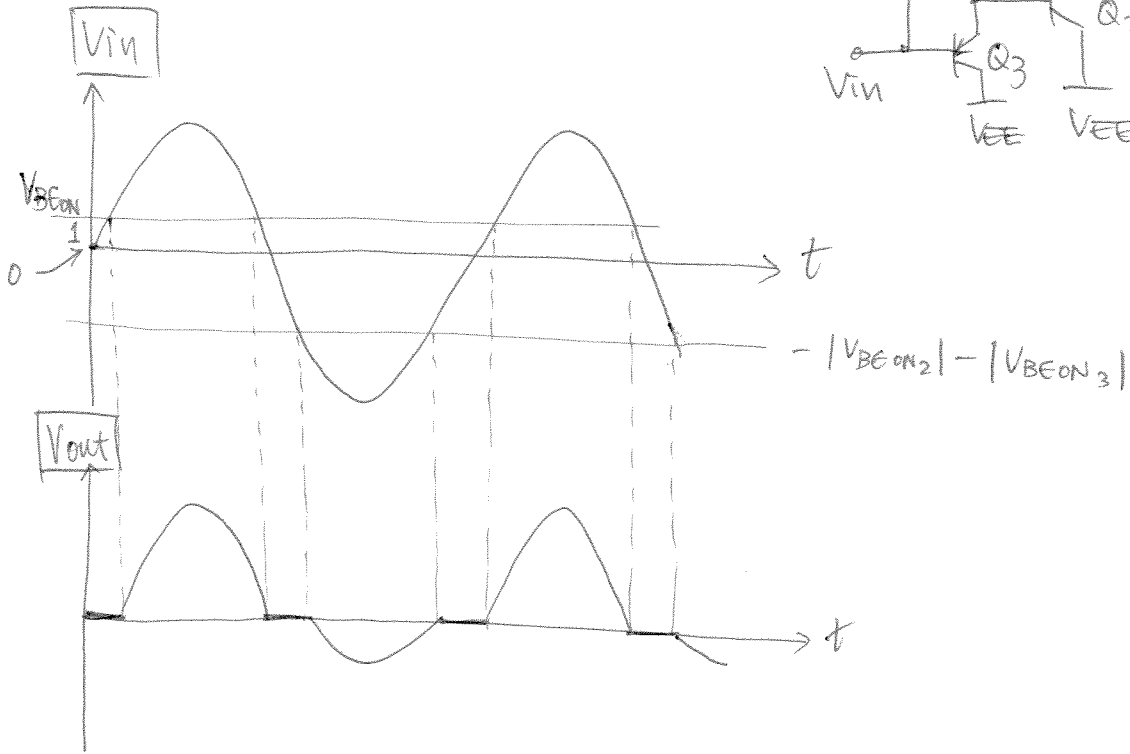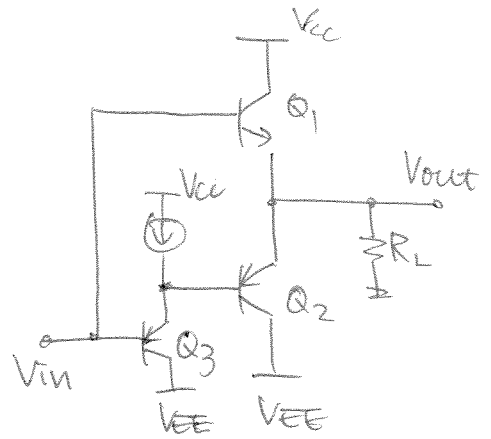

(b.)  
(a)

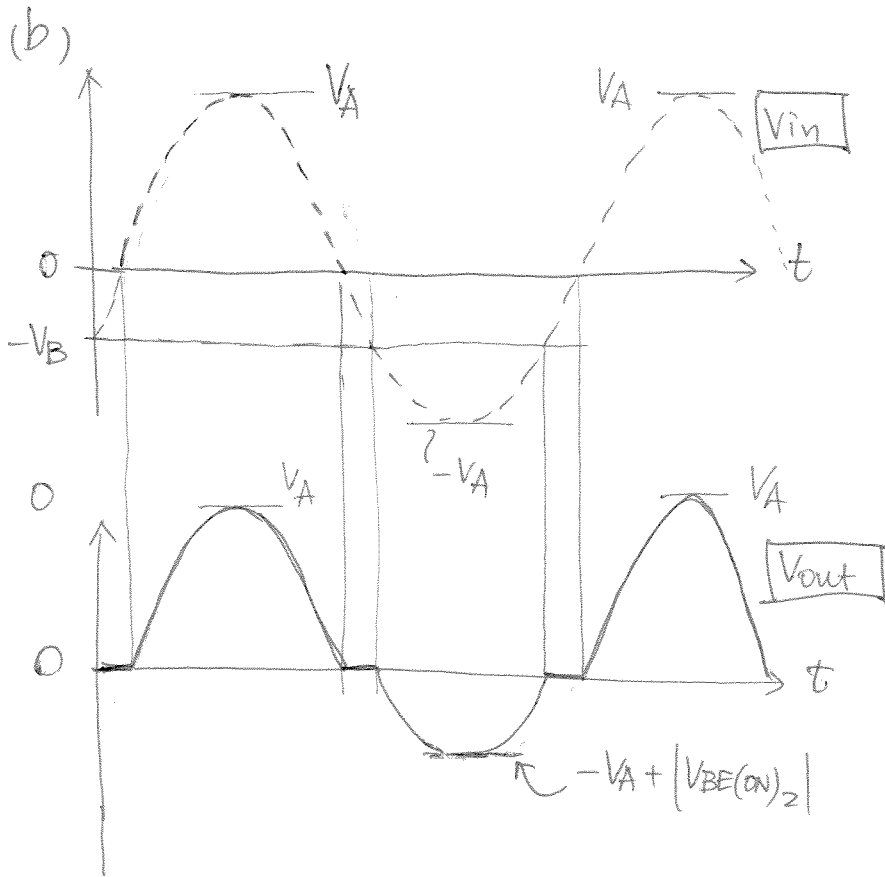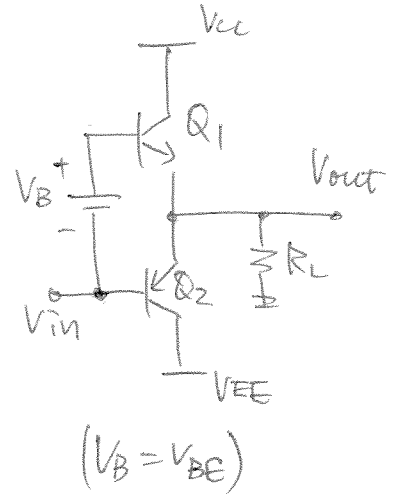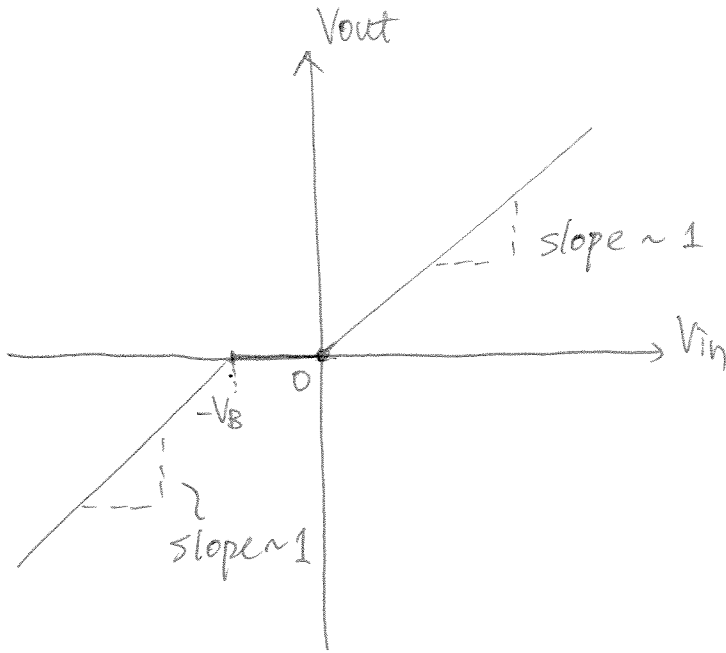

17.

•  $V_{out} = 0$ :

$$\Rightarrow I_{C1} = I_{C2} = I_{BIAS}$$

$$\Rightarrow I_{S1} \exp\left(\frac{V_{in} + V_B - V_{out}}{V_T}\right) = I_{S2} \exp\left(\frac{V_{out} - V_{in}}{V_T}\right)$$

$$\ln\left(\frac{I_{S1}}{I_{S2}}\right) + \frac{V_{in} + V_B - V_{out}}{V_T} = \frac{V_{out} - V_{in}}{V_T}$$

• For  $V_{out} = 0$ ,  $V_T = 0.026$  V:

$$\Rightarrow \ln\left(\frac{5}{8}\right) + \frac{V_{in} + V_B}{0.026} = +\frac{V_{in}}{0.026}$$


• Given  $I_{C2} = 5$  mA

$$\Rightarrow I_{S2} \exp\left(\frac{-V_{in}}{0.026}\right) = 5 \text{ mA} \Rightarrow V_{in} = -0.83 \text{ V}$$

$$I_{C1} = I_{S1} \exp\left(\frac{V_{in} + V_B - V_{out}}{V_T}\right) = (5 \cdot 10^{-7} \text{ A}) \exp\left(\frac{-0.83 + V_B}{V_T}\right)$$

$$\Rightarrow V_B = 0.83 + 0.026 \ln\left(\frac{5 \text{ mA}}{5 \cdot 10^{-7} \text{ A}}\right)$$

$$\approx 1.67 \text{ V}$$

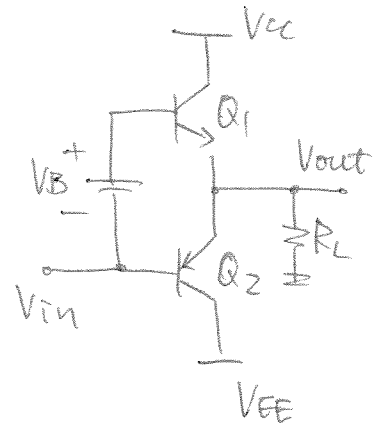

$$I_{S1} = 5 \cdot 10^{-17} \text{ A}$$



$$I_{S2} = 8 \cdot 10^{-17} \text{ A}$$

$$I_{BIAS} = 5 \text{ mA}$$

$$(V_{out} = 0)$$

18.

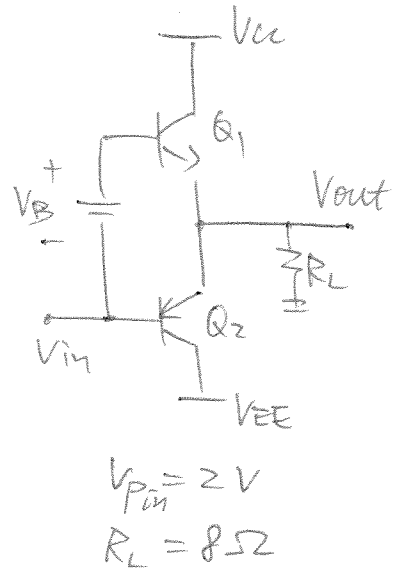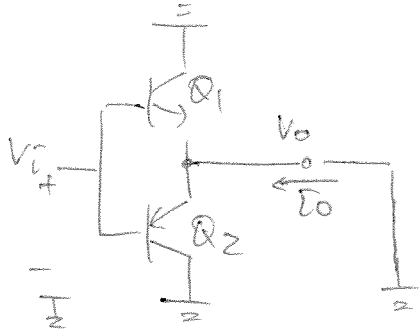(a) Equivalent circuit (small-signal) around  $V_{out} = 0$  :



$$\begin{aligned}\hat{i}_o &= -g_{m1} v_i + (-v_i) g_{m2} \\ &= -(g_{m1} + g_{m2}) v_i\end{aligned}$$

$$\therefore G_m = \frac{\hat{i}_o}{v_i} = -(g_{m1} + g_{m2})$$

$$\therefore A_v = \frac{v_o}{v_i} = \frac{\hat{i}_o \times R_L}{v_i} = -(g_{m1} + g_{m2}) R_L$$

$$\begin{aligned}(b) A_v &= -(g_{m1} + g_{m2}) R_L = -\left(\frac{I_{C1}}{V_T} + \frac{I_{C2}}{V_T}\right) R_L \\ &= -\left(\frac{5mA}{0.026V} + \frac{5mA}{0.026V}\right) (85\Omega) = -3.08\end{aligned}$$



$$\Rightarrow |V_o|_P = |v_i A_v|_P = |(2V)(-3.08)| = 6.16V$$

(Assume  $V_{CC}$  is large enough)

$$(c) \quad I_{c1} = I_{c2} + \frac{V_{out}}{R_L}$$


$$\begin{aligned} I_{c1, peak} &= I_{c2} + \frac{V_P}{R_L} \\ &= 5 \text{ mA} + \frac{6.16 \text{ V}}{8.52} \\ &= 775 \text{ mA} \end{aligned}$$

19.

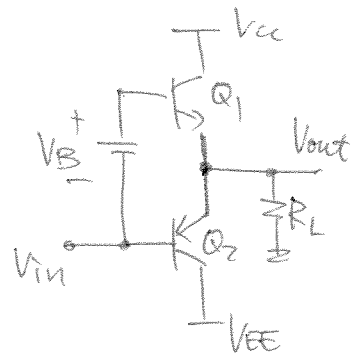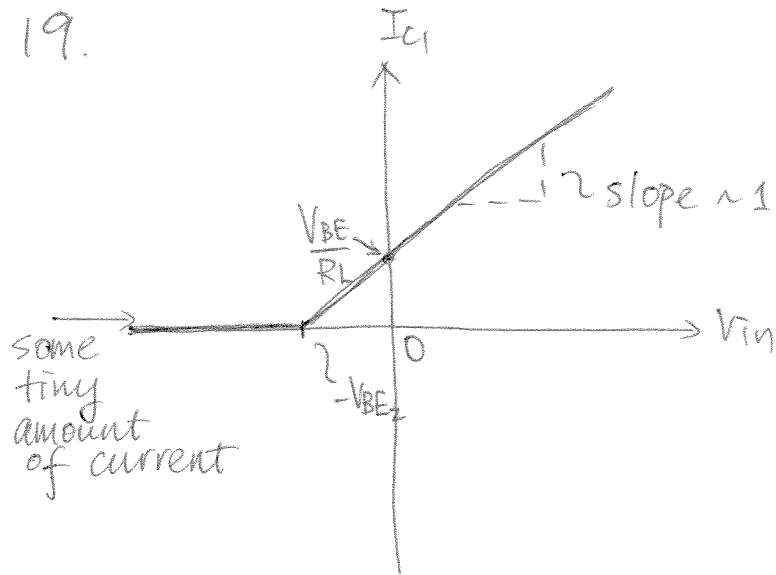



$$V_{out} = V_{in} + |V_{BE2}|$$
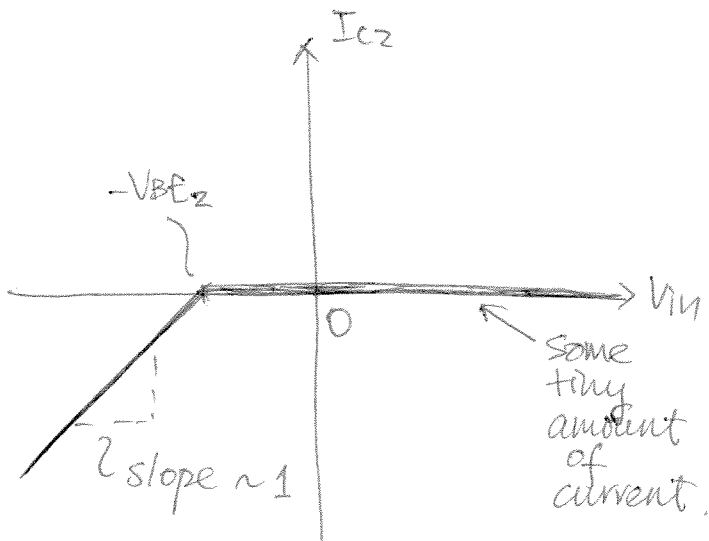
$$\Rightarrow I_{c1} = I_{c2} + \frac{V_{out}}{R_L}$$





20.

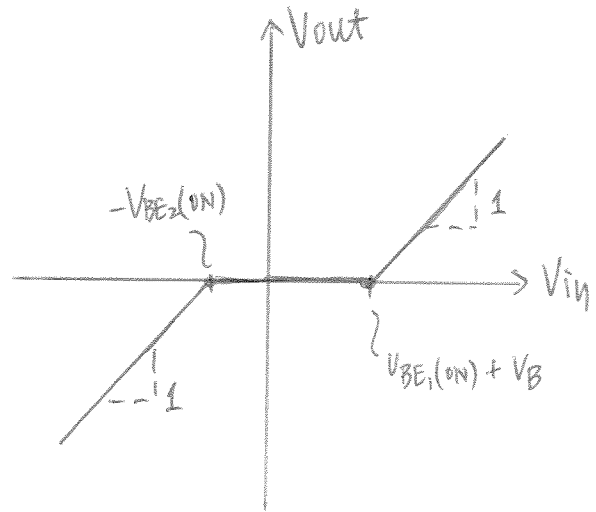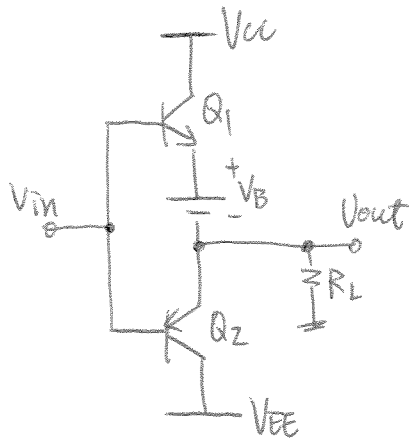

• To analyze such circuit, assume  $V_{out} = 0$ :

$$\Rightarrow -V_{BE2(ON)} < V_{in} < V_{BE1(ON)} + V_B$$

$$(V_{BE1(ON)} + V_B) < V_{in} \quad \therefore \quad V_{out} = V_{in} - V_{BE1(ON)} - V_B$$

$$V_{in} < -V_{BE2(ON)} \quad \therefore \quad V_{out} = V_{in} + |V_{BE2(ON)}|$$

$$21. \quad V_{BE1} + |V_{BE2}| = V_{D1} + V_{D2}$$

$$\Rightarrow V_T \left[ \ln \frac{I_{C1}}{I_{S_{Q1}}} + \ln \frac{I_{C2}}{I_{S_{Q2}}} \right] = V_T \left[ \ln \frac{I_{D1}}{I_{S_{D1}}} + \ln \frac{I_{D2}}{I_{S_{D2}}} \right]$$

$$\Rightarrow \frac{I_{C1} I_{C2}}{I_{S_{Q1}} I_{S_{Q2}}} = \frac{I_{D1} I_{D2}}{I_{S_{D1}} I_{S_{D2}}}$$

$\therefore$  If  $I_{S_{Q1}} I_{S_{Q2}} = I_{S_{D1}} I_{S_{D2}}$ ,

then  $I_{C1} I_{C2} = I_{D1} I_{D2}$

$$22. \quad V_{BE1} + |V_{BE2}| = V_{D1} + V_{D2}$$

$$\Rightarrow V_T \ln\left(\frac{I_{C1} I_{C2}}{I_{S,R1} I_{S,R2}}\right) = V_T \ln\left(\frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}}\right)$$

$$\Rightarrow \frac{I_{C1} I_{C2}}{I_{S,R1} I_{S,R2}} = \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \quad \text{————— (1)}$$

$$I_1 = I_{D1} = I_{D2} = 1 \text{ mA}; \quad I_{S,R} = 16 I_{S,D}$$

$$V_{out} = 0 \Rightarrow I_{C1} = I_{C2} \quad \text{————— (2)}$$

Substitute all into (1):

$$\frac{I_{C1} I_{C1}}{(16 I_{S,D})^2} = \frac{(1 \text{ mA})^2}{(I_{S,D})^2} \Rightarrow I_{C1} = I_{C2} = 16 \text{ mA}$$

$$23. \quad V_{BE1} + |V_{BE2}| = V_{D1} + V_{D2}$$

$$\Rightarrow \frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}} = \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \quad \text{_____} \quad \textcircled{1}$$

$$I_{C1} = I_{C2} = 5 \text{ mA} \quad \text{_____} \quad \textcircled{2}$$

$$I_{S,Q} = 8 I_{S,D} \quad \text{_____} \quad \textcircled{3}$$

Substitute all into  $\textcircled{1}$ :

$$\frac{(5 \text{ mA})^2}{(8 I_{S,D})^2} = \frac{I_{D1} I_{D2}}{(I_{S,D})^2} \Rightarrow I_1 = I_D = 0.625 \text{ mA}$$

$$24. \quad V_{BE1} + |V_{BE2}| = V_{D1} + V_{D2}$$

$$\Rightarrow \frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}} = \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \quad \text{--- ①}$$

$$I_1 = I_D = 2 \text{ mA}$$

$$I_{S,Q1} = 8 I_{S,D1} \quad ; \quad I_{S,Q2} = 16 I_{S,D2}$$

Substitute all into ①:

$$\frac{I_{C1} I_{C2}}{(8 I_{S,D1})(16 I_{S,D2})} = \frac{(2 \text{ mA})^2}{I_{S,D1} I_{S,D2}}$$

$$\Rightarrow I_{C1} = I_{C2} \cong 22.6 \text{ mA}$$

$$25. V_{BE1} + |V_{BE2}| = V_{D1} + V_{D2}$$

$$\Rightarrow \frac{kT_Q}{q} \left[ \ln \left( \frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}} \right) \right] = \frac{kT_D}{q} \left[ \ln \left( \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \right) \right]$$

Suppose  $T_D = (T_Q + \Delta T)$ :

$$\Rightarrow T_Q \left[ \ln \frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}} - \ln \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \right] = \Delta T \cdot \ln \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}}$$


$$\Rightarrow I_{C1} \cdot I_{C2} = I_{S,Q1} \cdot I_{S,Q2} \cdot \left( \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \right)^{1 + \frac{\Delta T}{T_Q}}$$

Typically,  $\frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} > 1$

$\Rightarrow$  A  $\Delta T$  introduces a factor  $\left( \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \right)^{\frac{\Delta T}{T_Q}} < 1$ ,

implying that the  $I_{C1} I_{C2}$  product drops corresponding to a change (positive) in temperature.


26. Small Signal:

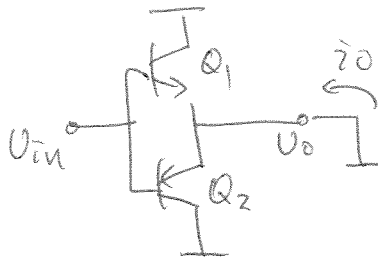

$$G_m = \frac{i_o}{v_{in}} = -(g_{m1} + g_{m2})$$

$$\Rightarrow \frac{v_o}{v_{in}} = \frac{i_o R_L}{v_{in}} = +(g_{m1} + g_{m2}) R_L$$

27. Small-signal:

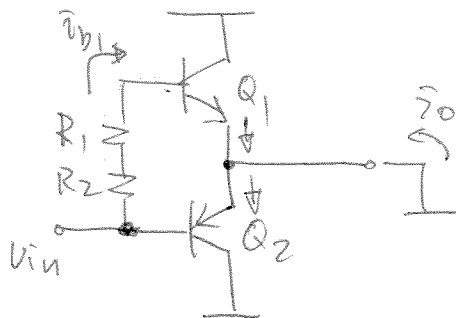

$$\bar{i}_o = -g_{m1} U_{be1} + g_{m2} |U_{be2}| \quad (\bar{i}_o = \bar{i}_{c2} - \bar{i}_{c1})$$

$$|U_{be2}| = U_{in}$$

$$U_{be1} = U_{in} - \bar{i}_{b1} (R_1 + R_2) = U_{in} - \frac{\bar{i}_{c1}}{\beta_1} (R_1 + R_2)$$

$$= U_{in} - \frac{\bar{i}_{c2} - \bar{i}_o}{\beta_1} (R_1 + R_2)$$

$$= U_{in} + \frac{g_{m2} U_{in} + \bar{i}_o}{\beta_1} (R_1 + R_2)$$

$$\therefore g_{m1} \left[ U_{in} + \frac{g_{m2} U_{in} + \bar{i}_o}{\beta_1} (R_1 + R_2) \right] + \bar{i}_o = -g_{m2} U_{in}$$


Solving for  $\frac{\bar{i}_o}{U_{in}}$  gives:

$$G_m = \frac{\bar{i}_o}{U_{in}} = - \frac{\left[ g_{m1} + \frac{g_{m1} g_{m2}}{\beta_1} (R_1 + R_2) + g_{m2} \right]}{1 + \frac{g_{m1} (R_1 + R_2)}{\beta_1}}$$



$R_{out}$ :
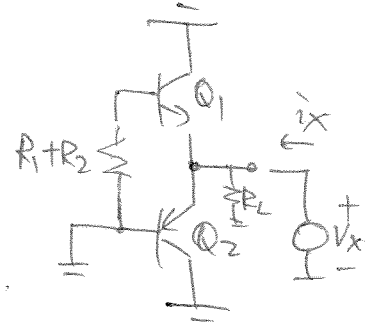
$$\frac{V_x}{i_x} = R_{out} = \left( r_{\pi 2} \parallel \frac{1}{g_{m2}} \right) \parallel \left[ \left( r_{\pi 1} + R_1 + R_2 \right) \parallel \frac{1}{g_{m1}} \right] \parallel R_L$$



$\therefore A_v = G_m R_{out}$

$$= - \left[ \frac{g_{m1} + \frac{g_{m1}g_{m2}(R_1+R_2)}{\beta_1} + g_{m2}}{1 + \frac{g_{m1}(R_1+R_2)}{\beta_1}} \right] \cdot \left\{ \left[ r_{\pi 2} \parallel \frac{1}{g_{m2}} \right] \parallel \left[ \left( r_{\pi 1} + R_1 + R_2 \right) \parallel \frac{1}{g_{m1}} \right] \parallel R_L \right\}$$


28. Small signal gain  
around  $V_{out} = 0$ :

$$A_v = +(g_{m1} + g_{m2}) R_L$$

$$0.8 = (I_{c1} + I_{c2}) \frac{R_L}{V_T}$$



If  $I_{c1} = I_{c2} = I_{BIAS}$ , then
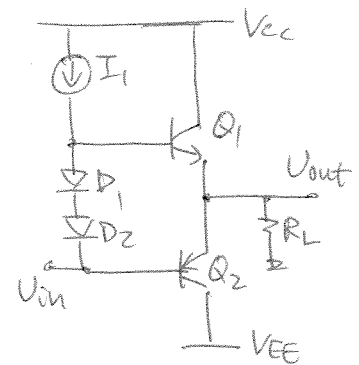
$$I_c = \frac{0.8}{2} \times \frac{V_T}{R_L} = 0.4 \frac{V_T}{R_L} = 0.01 \cdot R_L = 0.08 \text{ A}$$



$$R_L = 8 \Omega$$

29. Small-signal equivalent:

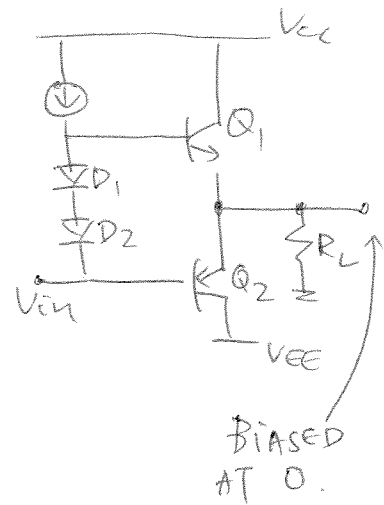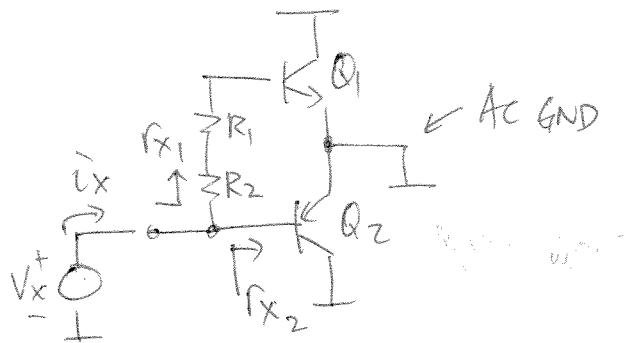

$$R_{in} = \frac{V_x}{I_x} = r_{x1} \parallel r_{x2}$$

$$= (R_1 + R_2 + r_{\pi 1}) \parallel r_{\pi 2}$$

•  $R_1$  &  $R_2$  can be neglected when  $r_{\pi 1} \gg (R_1 + R_2)$


30.  $I_{C1} = I_{C2} = 10 \text{ mA}$

$I_{C3} = I_{C4} = 1 \text{ mA}$


$\beta_1 = 40 \quad \beta_2 = 20$

$R_L = 8 \Omega$

$R_{D1} = R_{D2} = 0$

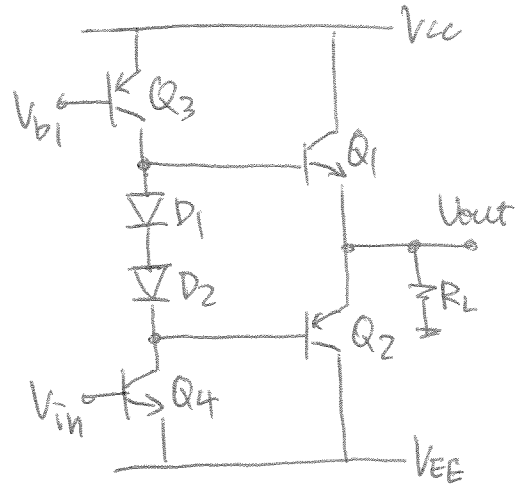

Small-signal

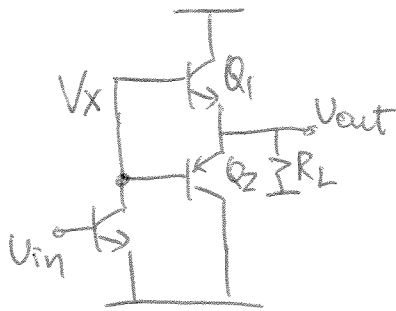

$$A_V = \frac{V_{out}}{V_x} \cdot \frac{V_x}{V_{in}}$$

$$= -g_{m4} \left[ (g_{m1} + g_{m2}) (r_{\pi 1} \parallel r_{\pi 2}) R_L + (r_{\pi 1} \parallel r_{\pi 2}) \right] \times \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}}$$

$$= -g_{m4} (r_{\pi 1} \parallel r_{\pi 2}) (g_{m1} + g_{m2}) R_L$$

$$\therefore A_V = - \frac{I_{C4}}{V_T} \left( \frac{\beta_1 V_T}{I_{C1}} \parallel \frac{\beta_2 V_T}{I_{C2}} \right) \left( \frac{I_{C1}}{V_T} + \frac{I_{C2}}{V_T} \right) R_L$$

$$= - \frac{1 \text{ mA}}{0.026} [35] \cdot \left( 2 \times \frac{10 \text{ mA}}{V_T} \right) (8)$$

$$\approx -8.3$$

31.

$$\frac{V_{out}}{V_{in}} = -g_{m4} (\Gamma_{\pi_1} \parallel \Gamma_{\pi_2}) (g_{m_1} + g_{m_2}) R_L \quad (\Gamma_{\pi} = \frac{\beta}{g_m})$$

When  $g_{m_1} \approx g_{m_2}$  : ( $\Rightarrow \Gamma_{\pi}$ )

$$\begin{aligned} \frac{V_{out}}{V_{in}} &\hat{=} -g_{m4} R_L (2g_{m_1}) \left( \frac{\beta_1}{g_{m_1}} \parallel \frac{\beta_2}{g_{m_1}} \right) \\ &= -g_{m4} R_L (2g_{m_1}) \left[ \frac{1}{g_{m_1}} \cdot \frac{\beta_1 \beta_2}{\beta_1 + \beta_2} \right] \\ &= - \frac{2\beta_1 \beta_2}{\beta_1 + \beta_2} g_{m4} R_L \end{aligned}$$


32. From lecture, small-signal gain of the output stage is:

$$\left| \frac{V_{out}}{V_{in}} \right| = +g_{m4} (r_{\pi 1} \parallel r_{\pi 2}) (g_{m1} + g_{m2}) R_L$$

$$\approx +g_{m4} R_L \times \frac{2\beta_1\beta_2}{\beta_1 + \beta_2}$$

$$\Rightarrow 4 = + \frac{I_{c4}}{V_T} (85\Omega) \times \frac{2(40)(20)}{40 + 20}$$
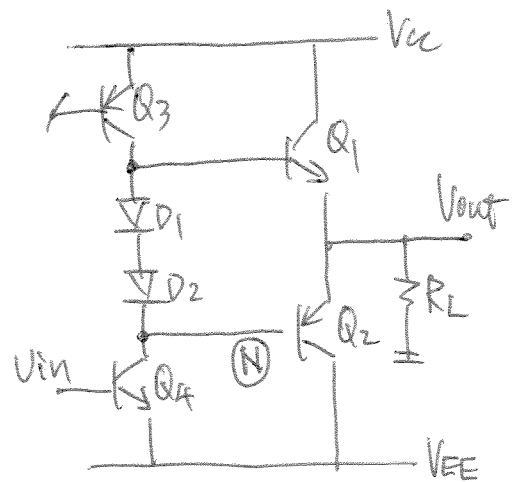
$$\begin{aligned} \Rightarrow I_{c4} &\approx I_{c3} \\ &= \frac{4V_T}{(85\Omega)} \cdot \frac{40 + 20}{2(40)(20)} \\ &= 0.49 \text{ mA} \end{aligned}$$



$$A_V = \frac{V_{out}}{V_{in}} = 4$$

$$\beta_1 = 40$$

$$\beta_2 = 20$$

$$R_L = 85\Omega$$


33. From lecture,

$$\frac{v_x}{i_x} = \frac{1}{g_{m1} + g_{m2}} + \frac{r_{o3} \parallel r_{o4}}{(g_{m1} + g_{m2})(r_{\pi1} - r_{\pi2})}$$

If  $g_{m1} \approx g_{m2} = g_m$ :

$$\begin{aligned} \frac{v_x}{i_x} &\approx \frac{1}{2g_m} + \frac{r_{o3} \parallel r_{o4}}{2g_m \left( \frac{\beta_1}{g_m} \parallel \frac{\beta_2}{g_m} \right)} \\ &= \frac{1}{2g_m} + \frac{r_{o3} \parallel r_{o4}}{2g_m \left( \frac{1}{g_m} \frac{\beta_1 \beta_2}{\beta_1 + \beta_2} \right)} \\ &= \frac{1}{2g_m} + \frac{r_{o3} \parallel r_{o4}}{2\beta_1 \beta_2} (\beta_1 + \beta_2) \end{aligned}$$

34.

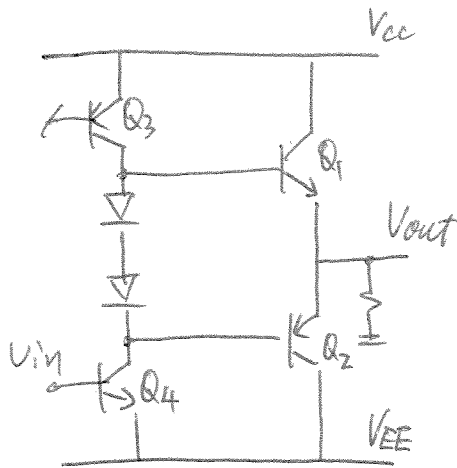


$$I_3 = I_4 = 1 \text{ mA}$$

$$I_1 = I_2 = 8 \text{ mA}$$


$$V_{A3} = 10 \text{ V}$$

$$V_{A4} = 15 \text{ V}$$

(a) Small-signal equivalent:

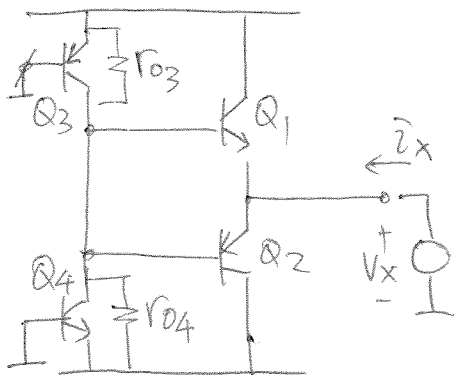

$\Rightarrow$

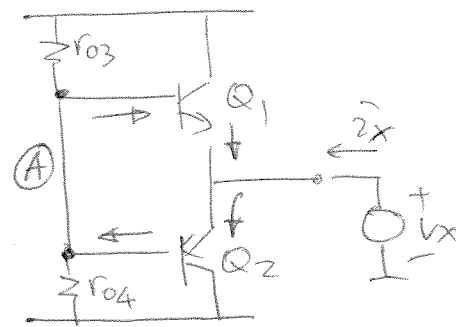

$$V_{eb} = v_x \frac{(r_{\pi 1} \parallel r_{\pi 2})}{(r_{\pi 1} \parallel r_{\pi 2}) + (r_{o3} \parallel r_{o4})}$$

$$v_{be} = v_A - v_x$$

$$\bar{i}_x + \bar{i}_{c1} = \bar{i}_{c2} \Rightarrow \bar{i}_x = \bar{i}_{c2} - \bar{i}_{c1} = g_{m2} v_{eb} - g_{m1} v_{be}$$

$$\therefore \bar{i}_x = [g_{m2} + g_{m1}] v_x \frac{(r_{\pi 1} \parallel r_{\pi 2})}{(r_{\pi 1} \parallel r_{\pi 2}) + (r_{o3} \parallel r_{o4})}$$

$$\Rightarrow \frac{v_x}{\bar{i}_x} = R_{out} = \frac{(r_{\pi 1} \parallel r_{\pi 2}) + (r_{o3} \parallel r_{o4})}{[g_{m1} + g_{m2}] (r_{\pi 1} \parallel r_{\pi 2})}$$



$$\Gamma_{\pi_1} = \frac{\beta_1 V_T}{I_{c1}} = 130 \Omega$$

$$\Gamma_{\pi_2} = \frac{\beta_2 V_T}{I_{c2}} = 65 \Omega$$

$$r_{o3} = \frac{V_{A3}}{I_{c3}} = 10 \text{ k}\Omega$$

$$r_{o4} = \frac{V_{A4}}{I_{c4}} = 15 \text{ k}\Omega$$


$$g_{m1} = 0.31 \text{ S}$$

$$g_{m2} = 0.31 \text{ S}$$

$$\Rightarrow R_{out} = \frac{43.3 + 6000}{(0.62)(43.3)} \approx 6001 \Omega$$

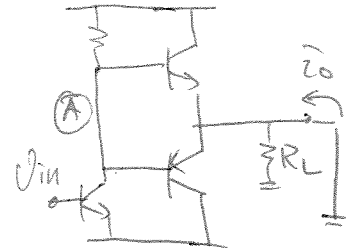(b) Effective  $R_{out} = R_{out,a} \parallel 8 \Omega \approx 8 \Omega$ .

$$\begin{aligned} G_m &= \frac{i_o}{v_A} \cdot \frac{v_A}{v_{in}} \\ &= -g_{m4} (\Gamma_{\pi_1} \parallel \Gamma_{\pi_2} \parallel r_{o3}) \cdot (g_{m1} + g_{m2}) \end{aligned}$$



$$\begin{aligned} g_{m4} &= \frac{I_{c4}}{V_T} \\ &= 0.038 \text{ S} \end{aligned}$$

$$\therefore A_v = G_m R_{out}$$


$$= -g_{m4} (\Gamma_{\pi_1} \parallel \Gamma_{\pi_2} \parallel r_{o3}) (g_{m1} + g_{m2}) R_{out}$$

$$= -0.038 [130 \parallel 65 \parallel 10 \text{ k}] [0.62] (8)$$

$$\approx -8.1$$

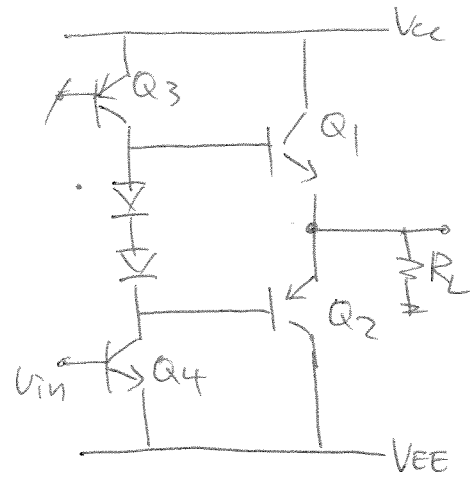35. Max current delivered  
 by  $Q_1 = I_{C3} \beta_1 = 1 \text{ mA} \cdot 40$   
 $= 40 \text{ mA. (} Q_4 \text{ off)}$

Max current delivered  
 by  $Q_2 = I_{C4} \cdot \beta_2$   
 $= 1 \text{ mA} \cdot 20$   
 $= 20 \text{ mA. (} Q_3 \text{ off)}$




$I_{C3} = I_{C4} = 1 \text{ mA}$   
 $\beta_1 = 40 \quad \beta_2 = 20$

36.  $P = 0.5 \text{ W}$      $R_L = 8 \Omega$   
 $\beta_1 = 40$      $\beta_2 = 20$ .

$$P_{\text{AVG}} = \frac{1}{2} \frac{V_p^2}{R_L} = 0.5$$

$$\Rightarrow V_p^2 = 2(0.5)R_L$$
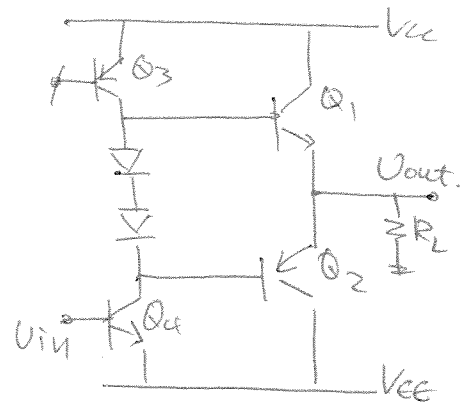
$$\Rightarrow V_p = \sqrt{R_L} = 2\sqrt{2}$$



At positive  $V_p$ ,  $I_{C1} = \frac{V_p}{R_L} = \frac{2\sqrt{2}}{8} = 0.35 \text{ A}$ .

At negative  $V_p$ ,  $I_{C2} = \frac{V_p}{R_L} \Rightarrow I_{C2} = 0.35 \text{ A}$ .

- At  $+V_p$ , all of  $I_{C3}$  supports the base current of  $Q_1$

$$\Rightarrow I_{C3} = I_{B1} = \frac{I_{C1}}{\beta_1} = \frac{0.35 \text{ A}}{40} = 8.75 \text{ mA}$$

- At  $-V_p$ , all of  $I_{C4}$  supports the base current of  $Q_2$


$$\Rightarrow I_{C4} = I_{B2} = \frac{I_{C2}}{\beta_2} = \frac{0.35 \text{ A}}{20} = 17.5 \text{ mA}$$

37.  $P_{AVG} = 0.5 \text{ W}$      $R_L = 8 \Omega$

$V_{CC} = 5 \text{ V}$

$\Rightarrow 0.5 \text{ W} = \frac{1}{2} \frac{V_p^2}{R_L}$

$\Rightarrow V_p = 2\sqrt{2} \text{ V}$

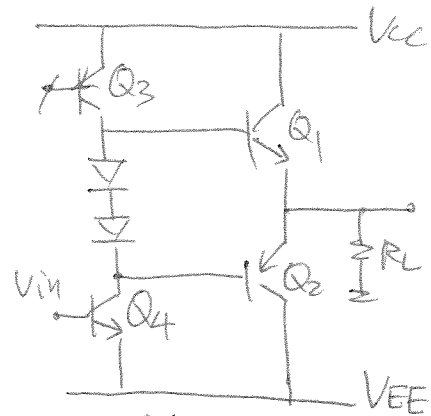

(Assume negligible currents at  $V_{out} = 0$ )

$P_{Q1} = \frac{1}{T} \int_0^{T/2} I_{C1} V_{CE1} dt$

$= \frac{1}{T} \int_0^{T/2} \left( \frac{V_p \sin \omega t}{R_L} \right) \cdot (V_{CC} - V_p \sin \omega t) dt$

$= \frac{1}{T} \int_0^{T/2} \left[ \frac{V_{CC} V_p}{R_L} \sin \omega t - \frac{V_p^2}{2R_L} \right] dt$

$= \frac{V_p}{R_L} \left( \frac{V_{CC}}{\pi} - \frac{V_p}{4} \right) = \frac{2\sqrt{2}}{8} \left( \frac{5}{\pi} - \frac{2\sqrt{2}}{4} \right)$


$\approx 0.31 \text{ W}$

38.  $P_{Q,MAX} = 0.75W$ .

$R_L = 8\Omega$

$V_{CC} = 5V$

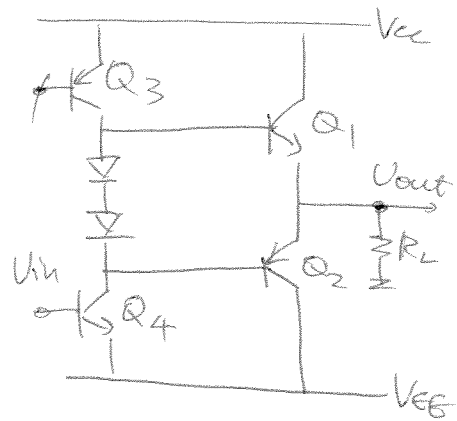• Out of all 4 transistors,  $Q_1$  &  $Q_2$  must sustain the most currents.



$$P_{Q_1,MAX} = V_{CE} \times I_{C_1,MAX} = (V_{CC} - V_{out}) I_{C_1,MAX}$$

(INST)

$$\Rightarrow P_{Q_1,MAX} = \frac{1}{T} \int_0^{T/2} \frac{V_p \sin \omega t}{R_L} \cdot (V_{CC} - V_p \sin \omega t) dt$$

(AVG)

$$= \frac{1}{T} \int_0^{T/2} \left( \frac{V_{CC} V_p}{R_L} \sin \omega t - \frac{V_p^2}{2R_L} \right) dt$$

$$= \frac{V_p}{R_L} \left( \frac{V_{CC}}{\pi} - \frac{V_p}{4} \right)$$

$$\Rightarrow \frac{dP_Q}{dV_p} = \frac{V_{CC}}{\pi R_L} - \frac{V_p}{2R_L}$$

$$= 0 \quad \text{when} \quad V_p = \frac{2V_{CC}}{\pi} = 3.18V$$

$$P_Q|_{V_p} = \frac{2V_{CC}}{\pi} = 0.32W$$

$$\therefore P_{R_L,MAX} = \frac{1}{2} \frac{V_p^2}{R_L} = 0.63W$$

$$39. P_{Q1, \text{MAX}} = \left( \frac{V_{CC}}{\pi} - \frac{2V_{CC}}{4\pi} \right) \cdot \frac{2V_{CC}}{\pi R_L} \leq 0.75 \text{ W}$$

$$\Rightarrow V_{CC, \text{MAX}} = 7.7 \text{ V}$$


$$\Rightarrow V_{P, \text{MAX}} = \frac{2V_{CC, \text{MAX}}}{\pi} = 4.9 \text{ V}$$

$$\Rightarrow P_{R_L, \text{MAX}} = \frac{1}{2} \frac{V_{P, \text{MAX}}^2}{R_L} = 1.5 \text{ W}$$

$$\begin{aligned}
 40. \quad I_1 &= I_{C1} + I_{E2} \\
 &= I_{C1} + \frac{\beta_1 + 1}{\beta_1} I_{C2} \\
 &= I_{C1} + \frac{\beta_1 + 1}{\beta_1} I_{B1} \\
 &= \beta_1 I_{B1} + \frac{\beta_1 + 1}{\beta_1} I_{B1}
 \end{aligned}$$

$$\begin{aligned}
 \Rightarrow I_{B1} &= \frac{I_1}{\beta_1 + \frac{\beta_1 + 1}{\beta_1}} = \frac{0.005}{40 + \frac{41}{40}} \\
 &= 0.12 \text{ mA}
 \end{aligned}$$
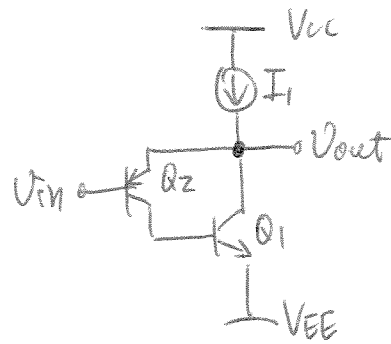
$$\Rightarrow I_{B2} = \frac{I_{C2}}{\beta_2} = \frac{I_{B1}}{\beta_2} = 0.0024 \text{ mA}$$




$$\begin{aligned}
 I_1 &= 5 \text{ mA} \\
 \beta_1 &= 40 \\
 \beta_2 &= 50.
 \end{aligned}$$

41.  $V_{in} = 0.5 \text{ V}$   
 $I_{S2} = 6 \cdot 10^{-17} \text{ A}$

$$I_{B1} = I_{C2} = 0.12 \text{ mA}$$


$$\Rightarrow I_{C2} = I_{S2} \cdot \exp\left(\frac{V_{out} - V_{in}}{V_T}\right)$$
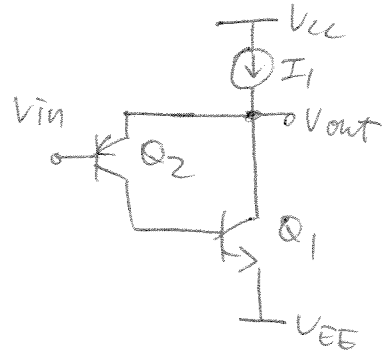
$$\begin{aligned} \therefore V_{out} &= V_T \ln\left(\frac{I_{C2}}{I_{S2}}\right) + V_{in} \\ &= 0.026 \ln\left(\frac{0.12 \text{ mA}}{6 \cdot 10^{-17} \text{ A}}\right) + 0.5 \\ &\hat{=} 1.24 \text{ V} \end{aligned}$$





42.

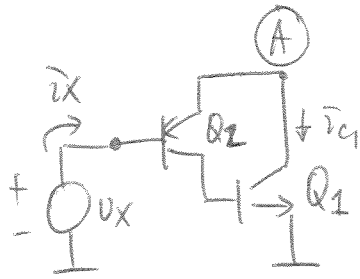

$$\bar{v}_{c2} = \bar{v}_x \beta_2$$

$$\bar{v}_{c1} = -g_{m2} v_{eb2} = \bar{v}_{e2} = \bar{v}_{c2} + \bar{v}_{b2} = \bar{v}_x (\beta_2 + 1)$$


$$v_{eb2} = v_A - v_x$$

$$\text{where } v_A = v_x - \bar{v}_x r_{\pi 2}$$

$$\therefore \bar{v}_{b1} = -g_{m2} (\bar{v}_x r_{\pi 2})$$

$$\bar{v}_{c1} = \bar{v}_{b1} + \bar{v}_{b1} \beta_1 = -g_{m2} \bar{v}_x r_{\pi 2} (1 + \beta_1)$$
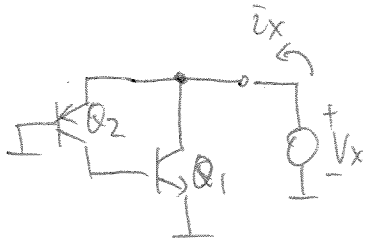
$$\Rightarrow \frac{v_x}{\bar{v}_x} \rightarrow \infty \quad (R_{in})$$



$$\bar{v}_x = \bar{v}_{e2} + \bar{v}_{c1}$$

$$= \bar{v}_{e2} + \bar{v}_{b1} \beta_1$$

$$= \bar{v}_{e2} + \bar{v}_{c2} \beta_1$$

$$= \bar{v}_{c2} + \bar{v}_{b2} + \bar{v}_{c2} \beta_1$$

$$= \bar{v}_{c2} (1 + \beta_1 + \frac{1}{\beta_1})$$

$$= v_x g_{m2} (1 + \beta_1 + \frac{1}{\beta_1})$$

$$\Rightarrow R_{out} = \frac{v_x}{\bar{v}_x} = \frac{1}{g_{m2} (1 + \beta_1 + \frac{1}{\beta_1})}$$

$$= 0.005 \Omega$$

$$g_{m2} = \frac{I_{B2} \beta_2}{V_T}$$

$$= 4.6 \text{ S}$$

$$43. R_{out} = 1 \Omega.$$

$$\beta_1 = 40 \quad \beta_2 = 50.$$

$$R_{out} = 1 = \frac{1}{g_{m2} \left(1 + \beta_1 + \frac{1}{\beta_1}\right)}$$

$$\Rightarrow g_{m2} = 0.024 \text{ S} = \frac{I_{B2} \beta_2}{V_T}$$

$$\Rightarrow I_{B2} = 0.012 \text{ mA}.$$


$$I_1 = I_{C1} + I_{E2} = I_{B1} \beta_1 + (I_{C2} + I_{B2})$$

$$= I_{C2} \beta_1 + I_{B2} (\beta_2 + 1)$$

$$= I_{B2} \beta_2 \beta_1 + I_{B2} (\beta_2 + 1)$$

$$= 0.012 [50 \times 40 + 50 + 1]$$

$$= 25.6 \text{ mA}$$

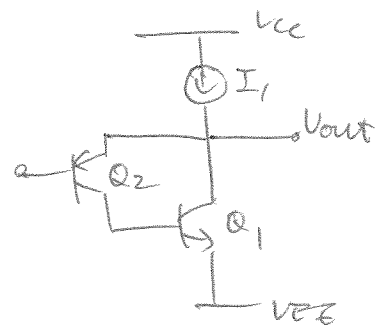


44.  $V_p = 0.5V$   
 $R_L = 8\Omega$

$$P_{R_L} = \frac{V_p^2}{2R_L} = \frac{0.25}{16} = 0.0156 \text{ W}$$

$$P_I = -I \times V_{EE} = 0.14 \text{ W}$$

$$P_{Q_1} = I_1 \left( V_{CC} - \frac{V_p}{2} \right) = 0.1225 \text{ W}$$
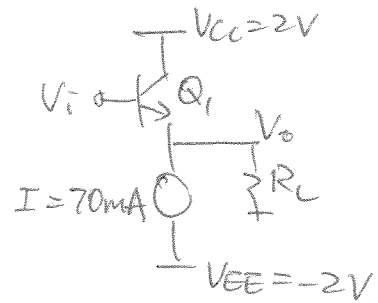
$$\therefore \eta = \frac{P_{R_L}}{P_{R_L} + P_I + P_{Q_1}} = \frac{0.0156}{0.2781} = 5.6\%$$



$$45. P_{R_L} = \frac{V_P^2}{2R_L} = \frac{(V_{CC} - V_{BE})^2}{2R_L}$$

$$P_{Q_1} = I_1 \left( V_{CC} - \frac{V_{CC} - V_{BE}}{2} \right)$$

$$P_I = +I_1 |V_{EE}|$$

• Assume

$$|V_{CC}| = |V_{EE}|,$$

$$I_1 = \frac{V_P}{R_L} = \frac{V_{CC} - V_{BE}}{R_L}$$

$$\begin{aligned} \therefore \eta &= \frac{P_{R_L}}{P_{R_L} + P_{Q_1} + P_I} = \frac{\frac{(V_{CC} - V_{BE})^2}{2R_L}}{\frac{(V_{CC} - V_{BE})^2}{2R_L} + I_1 \left[ V_{CC} - \frac{V_{CC} - V_{BE}}{2} + |V_{EE}| \right]} \\ &= \frac{\frac{1}{2R_L}}{\frac{1}{2R_L} + \frac{3V_{CC} - V_{BE}}{2R_L(V_{CC} - V_{BE})}} \\ &= \frac{1}{1 + \frac{3V_{CC} - V_{BE}}{V_{CC} - V_{BE}}} \approx \frac{V_{CC} - V_{BE}}{3V_{CC} - V_{BE}} \end{aligned}$$

$$46. \eta = \frac{\frac{V_p^2}{2R_L}}{\frac{V_p^2}{2R_L} + \frac{2V_p}{R_L} \left( \frac{V_{CC}}{\pi} - \frac{V_p}{4} \right)}$$
$$= \frac{\pi}{4} \frac{V_p}{V_{CC}}$$

$$\Rightarrow \eta \Big|_{V_p = V_{CC} - V_{BE}} = \frac{\pi}{4} - \frac{\pi}{4} \cdot \frac{V_{BE}}{V_{CC}}$$

$$\begin{aligned}
 47. \quad \eta &= \frac{\frac{(V_p/2)^2}{2R_L}}{\frac{(V_p/2)^2}{2R_L} + \frac{2(V_p/2)(V_{CC} - V_p/2)}{R_L}} \\
 &= \frac{V_p^2/8R_L}{\frac{V_p^2}{8R_L} + \frac{V_p}{R_L} \left( \frac{V_{CC}}{\pi} - \frac{V_p}{8} \right)} = \frac{1/8R_L}{1/8R_L + \frac{1}{R_L} \left( \frac{V_{CC}}{\pi} - \frac{1}{8} \right)} \\
 &= \frac{1}{1 + \left( \frac{8V_{CC}}{V_p\pi} - 1 \right)} = \frac{\pi}{8} \frac{V_p}{V_{CC}} \approx 39\%.
 \end{aligned}$$

$$48. \quad V_{CC} = 3V \quad P_{RL} = 0.2W \quad R_L = 8\Omega.$$

$$P_{RL} = \frac{1}{2} \frac{V_p^2}{R_L} \Rightarrow V_p = \sqrt{2P_{RL} \times R_L} = 1.8V$$

$$\therefore \eta = \frac{P_{RL}}{P_{RL} + \frac{2V_p}{R_L} \left( \frac{V_{CC}}{\pi} - \frac{V_p}{4} \right)} = \frac{0.2}{0.2 + \frac{3.6}{8} \left( \frac{3}{\pi} - \frac{1.8}{4} \right)}$$

$$\approx 18\%$$


49. Power = 1 W  
 $R_L = 8\Omega$

$$P_{LOAD} = \frac{1}{2} \frac{V_p^2}{R_L} = 1 \text{ W}$$

$$\Rightarrow V_p = 4 \text{ V} \Rightarrow I_1 = \frac{V_p}{R_L} = 0.5 \text{ mA}$$

(Note: the problem does not specify small-signal voltage gain, so choose  $V_p = I_1 R_L$ )
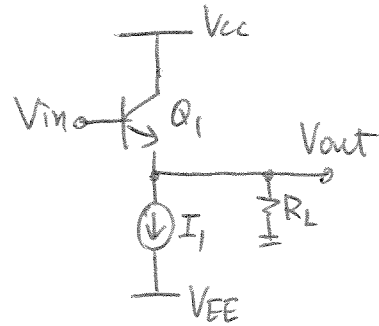
$$\begin{aligned} P_{Q_1} (\text{power rating}) &= I_1 (V_{CC}) \\ &= (0.5 \text{ mA})(5 \text{ V}) \\ &= 2.5 \text{ mW} \end{aligned}$$





50.  $A_V = 0.8$   
 $R_L = 4 \Omega$


$$A_V = \frac{R_L}{R_L + \frac{1}{g_{m_1}}} = \frac{4}{4 + \frac{0.026}{I_{C_1}}} = 0.8$$

$$\Rightarrow I_{C_1} = 26 \text{ mA}$$

$$\therefore I_1 = I_{C_1} = 26 \text{ mA} \quad (V_{out} \text{ biased at } 0 \text{ V.})$$

$$\begin{aligned} \text{Max Output Swing} &= I_1 R_L \\ &\approx (26 \text{ mA})(8 \Omega) \\ &= 0.208 \text{ V} \end{aligned}$$
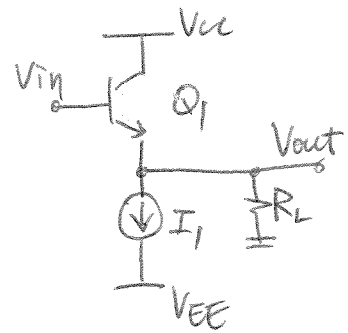
$$\begin{aligned} P_{Q_1} (\text{power rating}) &= I_1 V_{CC} (V_p = 0) \\ &= (26 \text{ mA})(5 \text{ V}) = 130 \text{ mW} \end{aligned}$$




51.  $A_v = 0.6$   
 $R_L = 8 \Omega$   
 $r_{D_1} = r_{D_2} = 0$

$$A_v = \frac{R_L}{R_L + \frac{1}{g_{m_1}}} = \frac{(8 \Omega)}{(8 \Omega) + \frac{0.026 V}{I_{Q_1}}}$$

$$= 0.6$$
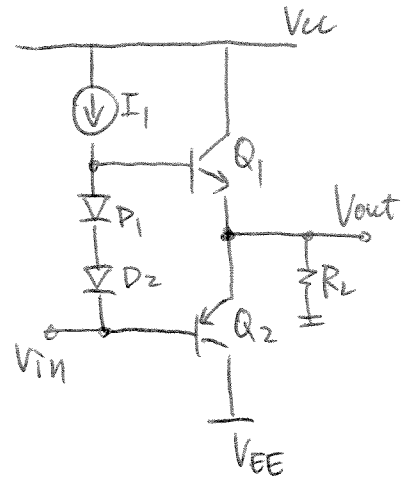
$$\Rightarrow I_{Q_1} = I_{Q_2} = 4.8 \text{ mA}$$



( $V_{out}$  biased at 0V.)

52. Power = 1 W (to load)

$$R_L = 8 \Omega$$

$$|V_{BE}| \approx 0.8 \text{ V}$$

$$\beta_1 = 40$$

$$P_L = \frac{1}{2} \frac{V_p^2}{R_L} = 1 \text{ W}$$


$$\Rightarrow V_p = 4 \text{ V}$$

$\therefore$  Min allowable supply =  $V_p + |V_{BE}| = 4.8 \text{ V}$   
voltage

• At  $+V_p$ , all of  $I_1$  goes to base of  $Q_1$

$$\Rightarrow I_1 = I_{B_1} = \frac{I_{C_1}}{\beta_1} = \frac{V_p}{R_L} \cdot \frac{1}{\beta_1} \quad (Q_2 \text{ off})$$
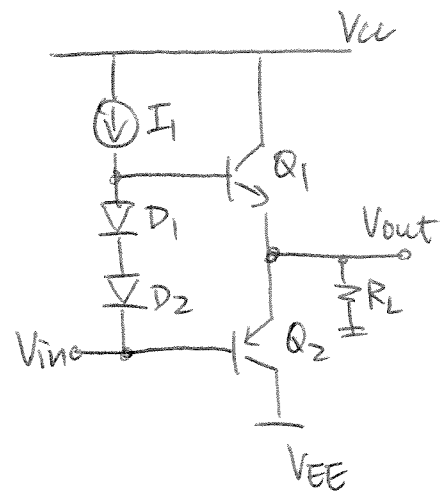
$$= \frac{4}{8} \cdot \frac{1}{40} = \frac{1}{80} = 12.5 \text{ mA}$$




53.  $P_{Q, \text{MAX}} = 2 \text{ W}$   
 $R_L = 8 \Omega.$

For this circuit,

$$P_{\text{AVG}, \text{MAX}} = \frac{V_{cc}^2}{\pi^2 R_L} \quad \left( V_p = \frac{2V_{cc}}{\pi} \right)$$

$$= 2 \text{ W}$$

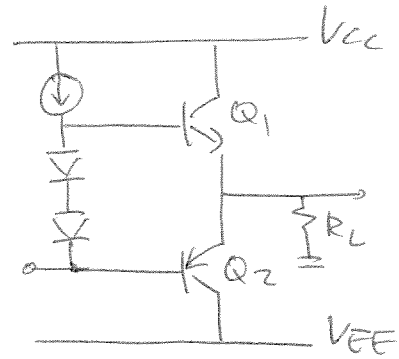

$$\Rightarrow V_{cc} \Big|_{\text{MAX}} = 12.6 \text{ V} \quad \Rightarrow V_p \Big|_{\text{MAX}} = \frac{2 \cdot 12.6}{\pi} = 8.02 \text{ V}$$

$$\therefore P_{R_L \text{ MAX}} = \frac{V_{p \text{ MAX}}^2}{2R_L} = \frac{(8.02)^2}{2 \cdot 8} = 4.02 \text{ W}$$

54. For this circuit,

$$P_{Q,MAX} = 2W$$

$$R_L = 4\Omega$$

$$P_{AVG,MAX} = \frac{V_{CC}^2}{2R_L} \quad \left( V_p = \frac{2V_{CC}}{\pi} \right)$$

$$\Rightarrow V_{CC,MAX} = \sqrt{\frac{\pi^2 R_L P_{Q,MAX}}{1}} = 8.9 V$$

$$\Rightarrow V_{p,MAX} = \frac{2V_{CC,MAX}}{\pi} = 5.6 V$$

$$\therefore P_{R_L,MAX} = \frac{V_{p,MAX}^2}{2R_L} = \frac{32}{2(4)} = 4W$$

$$55. \quad A_v = 4 \quad R_L = 8 \Omega \quad I_{C1} \approx I_{C2}$$

$$\beta_1 = 40 \quad \beta_2 = 20$$

Suppose we want 1st-stage (CE amplifier)  
to have gain = 5  $\Rightarrow$  2nd stage gain = 0.8.

$$\Rightarrow 0.8 = \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}}$$

$$0.8 = \frac{8}{8 + \frac{1}{2g_m}} \Rightarrow g_{m1} = g_m \Rightarrow I_{C1} = I_{C2} = 6.5 \text{ mA}$$

$$r_{\pi 1} \parallel r_{\pi 2} = \frac{\beta_1 V_T}{I_{C1}} \parallel \frac{\beta_2 V_T}{I_{C2}} = \frac{40(0.026)}{6.5 \text{ mA}} \parallel \frac{20(0.026)}{6.5 \text{ mA}} \approx 133 \Omega$$

$$\bullet \quad A_v = 4 = g_{m4} (r_{\pi 1} \parallel r_{\pi 2}) (g_{m1} + g_{m2}) R_L$$

$$= \frac{I_{C4}}{V_T} (133) (0.5) 8$$

$$\Rightarrow I_{C4} = I_{C3} = \frac{4 V_T}{8 (133) (0.5)} = 0.195 \text{ mA}$$

Max  $I_{Q1}$  when all of  $I_{C3}/I_{C4}$  supports  
base current of  $Q_1$

$$\Rightarrow I_{Q1, \text{MAX}} = I_{C4} = 0.195 \text{ mA}$$

$$56. \quad A_v = 4 \quad R_L = 4 \Omega \quad I_{C1} \approx I_{C2}$$

$$\beta_1 = 40 \quad \beta_2 = 20$$

1st stage gain = 5 (CE amplifier)

$$\text{2nd } v \quad v = 0.8$$

$$\bullet \quad 0.8 = \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}} = \frac{4}{4 + \frac{1}{2g_{m1}}}$$

$$\Rightarrow g_{m1} = 0.5 \text{ S} \Rightarrow I_{C1} = I_{C2} = 13 \text{ mA}$$

$$r_{\pi 1} \parallel r_{\pi 2} = \frac{\beta_1 V_T}{I_{C1}} \parallel \frac{\beta_2 V_T}{I_{C2}} = 80 \parallel 40 = 26.7 \Omega$$

$$\bullet \quad A_v = 4 = g_{m4} (r_{\pi 1} \parallel r_{\pi 2}) (g_{m1} + g_{m2}) R_L$$


$$= \frac{I_{C4}}{V_T} (26.7) (1) (4)$$

$$\Rightarrow I_{C4} = I_{B3} = \frac{4 V_T}{(26.7)(1)(4)} = 0.974 \text{ mA}$$

• Max  $I_{Q1}$  ( $I_{Q1, \text{MAX}}$ ) when  $I_{C4} = I_{Q, \text{MAX}} = 0.974 \text{ mA}$ .

• For a reduction of 2x the  $R_L$ , we have to provide  $\sim 5x$  current to base of  $Q_1$ . ( $\frac{0.974}{0.195} \approx 5$ )

57.  $P_{RL} = 2W$        $\beta_1 = 40$   
 $R_L = 8\Omega$        $\beta_2 = 20$   
 $|V_{BE}| = 0.8V$

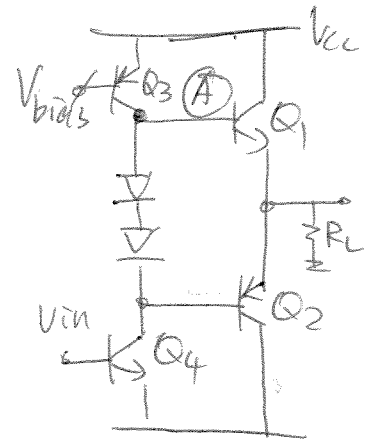

(a)  $P_{RL} = \frac{1}{2} \frac{V_p^2}{R_L} \Rightarrow V_p \approx 5.6V$

• At  $+V_p$ ,  $V_A = V_p + |V_{BE}|$ .

• For  $Q_3$  in active region,  $V_A \leq V_{bias}$

$$\Rightarrow V_{CC} \geq V_{bias} + |V_{BE}| = V_p + 2|V_{BE}|$$

$$\geq 5.6 + 1.6 = 7.2V.$$

(b)  $I_p = \frac{V_p}{R_L} = 0.7A$ . ( $= I_{E1}$ ), ( $= I_{E2}$ )

$$\Rightarrow I_{B1} = \frac{I_{E1}}{1 + \beta_1} = 17mA.$$

$\therefore$  We bias  $Q_3$  &  $Q_4$  with  $I_C = 17mA$ .



$$(c) P_{AV} = \frac{V_P}{R_L} \left( \frac{V_{CC}}{\pi} - \frac{V_P}{4} \right)$$
$$= \frac{5.6}{8} \left( \frac{5}{\pi} - \frac{5.6}{4} \right) = 3.66 \text{ W}$$

$$(d) P_{I_{Q3}} = 2V_{CC} \times I_{Q3} = 10 \times 17 \text{ mA} = 170 \text{ mW}$$

$$P_{AV, Q_1} = \frac{V_P}{R_L} \left( \frac{V_{CC}}{\pi} - \frac{V_P}{4} \right) = 3.66 \text{ W}$$

$$P_{R_L} = 2 \text{ W}$$

$$\Rightarrow \eta = \frac{P_{R_L}}{P_{I_{Q3}} + 2 \cdot P_{AV, Q_1} + P_{R_L}}$$
$$= \frac{2}{170 \text{ m} + 3.66 \times 2 + 2} = 0.21 = 21\%$$


58.

(a)  $A_V = 5$     $R_L = 4\Omega$     $\beta_1 = 40$     $\beta_2 = 20$ .

Assume  $I_{C1} \approx I_{C2}$ .

$$\frac{V_{out}}{V_{in}} = \frac{R_L}{(g_{m1} + g_{m2})^{-1} + R_L} = 0.8$$
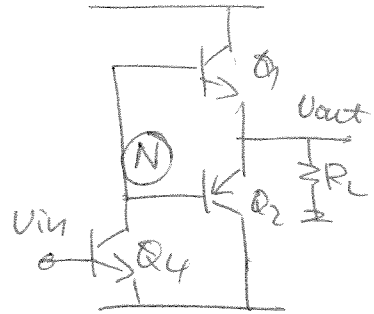
$$\Rightarrow 2g_{m1}^{-1} = 1 \Rightarrow I_{C1} = 2V_T = 0.052 \text{ A.}$$



$$\Rightarrow \frac{V_{out}}{V_{in}} = +g_{m4} (r_{\pi1} \parallel r_{\pi2}) (g_{m1} + g_{m2}) R_L = 5$$

Assume  $g_{m1} \approx g_{m2}$ :

$$\Rightarrow I_{C4} = V_T \frac{5}{(r_{\pi1} \parallel r_{\pi2}) (g_{m1} + g_{m2}) R_L}$$

$$= V_T \times \frac{5}{(r_{\pi1} \parallel r_{\pi2}) (g_{m1} \times 2) R_L}$$

$$= 0.026 \frac{5}{(6.7\Omega) (2 \times 2) (4)}$$

$$\approx 1.2 \text{ mA.}$$

$$\Rightarrow \text{Max } I \text{ by } Q_1 = \beta_1 \times I_{C4} = 48 \text{ mA}$$

$$\Rightarrow P_{R_L} = \frac{1}{2} I^2 R_L = 24 \times 4 \text{ mW} = 96 \text{ mW, BELOW requirement!}$$

$$(b) P = 5 \text{ W} = \frac{1}{2} \frac{V_p^2}{R_L} \Rightarrow V_p = 6.3 \text{ V}$$

$$\Rightarrow I_p = \frac{V_p}{R_L} = 1.6 \text{ A}$$

$$\Rightarrow I_{B2, \text{MAX}} = \frac{I_p}{\beta_2} = \frac{1.6}{20} = 79 \text{ mA}$$

$\Rightarrow I_{C2}$  must equal 79 mA to allow max output swing  $V_p$

$$\Rightarrow g_{m4} = \frac{I_{C4}}{V_T} = 3.04 \text{ S}$$

Suppose 2nd stage gain = 0.8 ( $I_{C1} = I_{C2}$ )

$$\Rightarrow \frac{v_{out}}{v_{in}} = \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}} \Rightarrow g_{m1} = 0.5 \text{ S}$$



$$= 0.8 \Rightarrow I_{C1} = I_{C2} = 13 \text{ mA}$$

$$r_{\pi 1} \parallel r_{\pi 2} = \frac{\beta_1 V_T}{I_{C1}} \parallel \frac{\beta_2 V_T}{I_{C2}} = 26.7 \Omega$$



$$\therefore \frac{v_{out}}{v_{in}} = -(3.04)(26.7 \Omega)(0.5 + 0.5)4$$

$$= -324 \text{ !! (Huge! Impractical)}$$

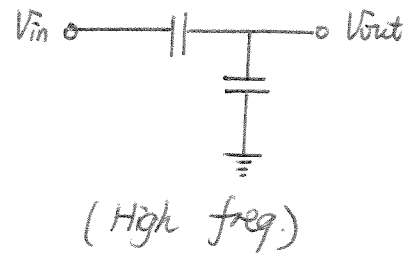
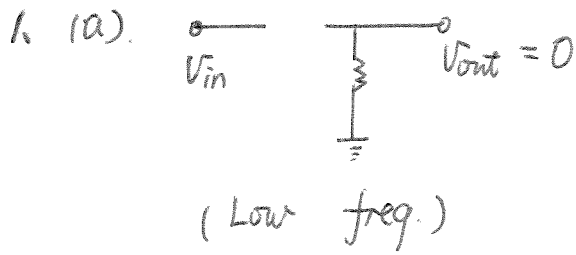
• Even when the 2nd stage gets close to 1, we still need huge gain from first stage.





This is a high pass filter.

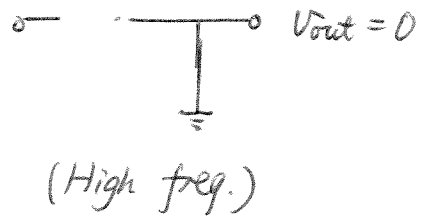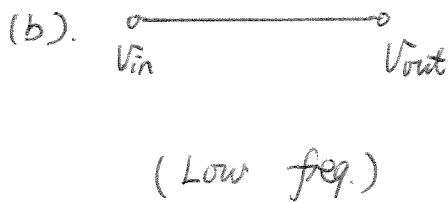



This is a low pass filter.

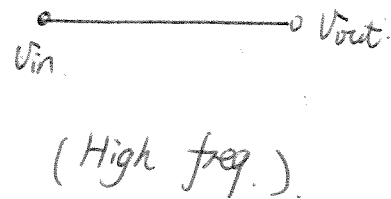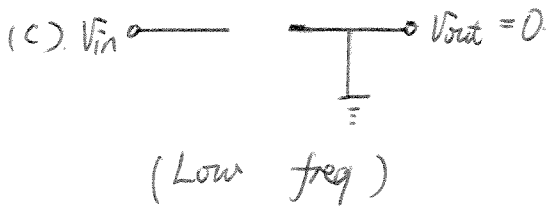


This is a high pass filter.

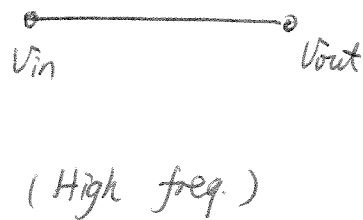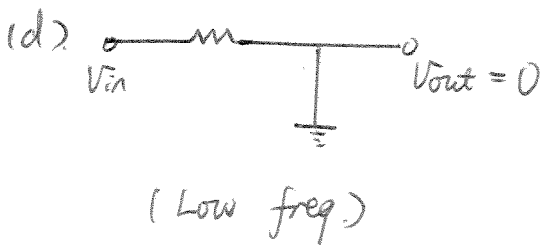

This is a high pass filter.

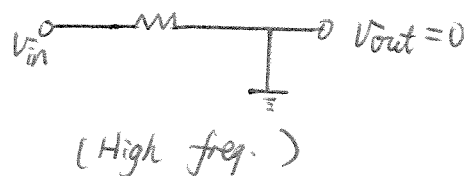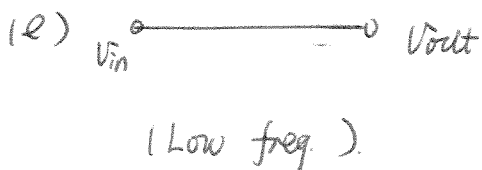


This is a low pass filter.

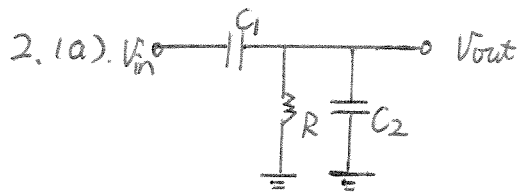

$$V_{out} = \frac{R // \frac{1}{sC_2}}{\frac{1}{sC_1} + R // \frac{1}{sC_2}} V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{C_1}{C_1 + C_2} s}{s + \frac{1}{R(C_1 + C_2)}}$$

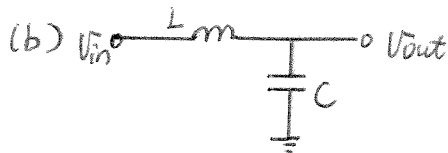
zero = 0; pole =  $-\frac{1}{R(C_1 + C_2)}$



$$V_{out} = \frac{\frac{1}{sC}}{sL + \frac{1}{sC}} V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{1/\sqrt{LC}}{s^2 + \frac{1}{LC}}$$

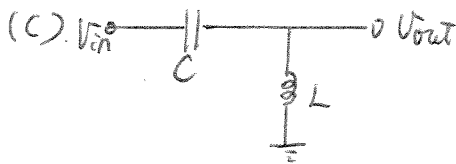
zero: No finite zero; poles =  $\pm i\sqrt{\frac{1}{LC}}$



$$V_{out} = \frac{sL}{sL + \frac{1}{sC}} V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{s^2 \frac{L}{C}}{s^2 + \frac{1}{LC}}$$

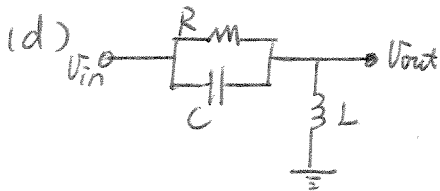zeros: Two zeros at 0; poles =  $\pm i\sqrt{\frac{1}{LC}}$




$$V_{out} = \frac{sL}{sL + R // \frac{1}{sC}} V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{s(s + \frac{1}{RC}) (RC)^2}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$

zeros: 0,  $-\frac{1}{RC}$
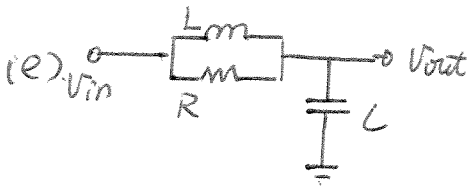
$$\text{poles} = \frac{-\frac{1}{RC} \pm \sqrt{(\frac{1}{RC})^2 - \frac{4}{LC}}}{2}$$



$$V_{out} = \frac{\frac{1}{sC}}{\frac{1}{sC} + sL // R} V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{RC} (s + \frac{R}{L})}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$


zero =  $-\frac{R}{L}$ ; poles =  $\frac{-\frac{1}{RC} \pm \sqrt{(\frac{1}{RC})^2 - \frac{4}{LC}}}{2}$

B.

Since  $\frac{V_{out}}{V_{in}} = \frac{1}{(s+a)(s+b)}$ , where  $a$  and  $b$


are real and positive, the transfer function contains no finite zero and two real poles on the left hand plane. But, after reviewing Problem #2 we discover that **NONE** of the networks yield this case.

4.

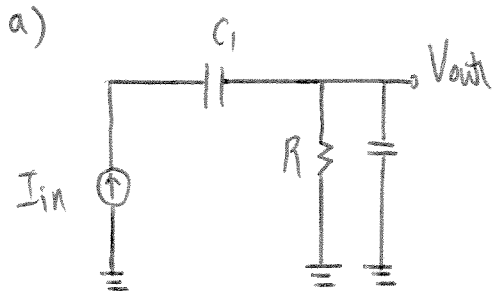


$$\frac{V_{out}}{I_{in}} = \frac{1/C_2}{s + 1/(RC_2)}$$

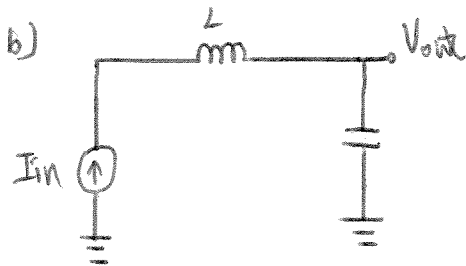Zero: No finite zero  
Pole:  $-1/(RC_2)$




$$\frac{V_{out}}{I_{in}} = \frac{1}{sC}$$

Zero: No finite zero  
Pole: 0

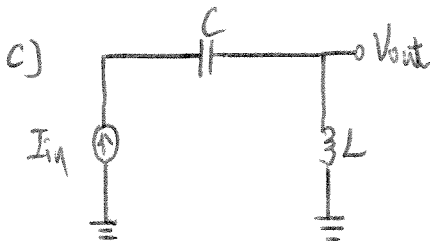


$$\frac{V_{out}}{I_{in}} = sL$$

Zero: 0  
Pole: No finite pole

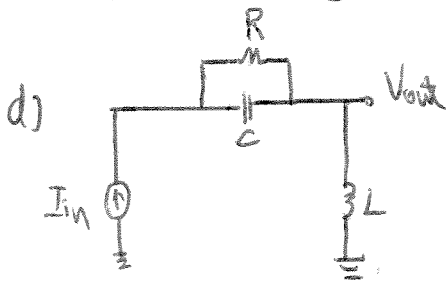


$$\frac{V_{out}}{I_{in}} = sL$$

Zero: 0  
Pole: No finite pole

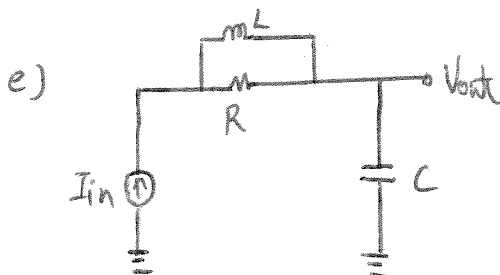

$$\frac{V_{out}}{I_{in}} = \frac{1}{sC}$$

Zero: No finite zero  
Pole: 0

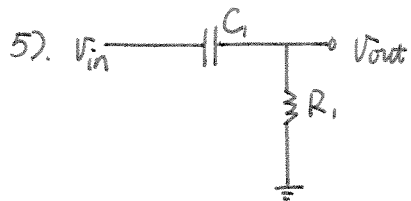

$$\frac{V_{out}}{V_{in}} = \frac{R_1}{R_1 + \frac{1}{sC_1}} = \frac{s}{s + \frac{1}{R_1 C_1}}$$

$$\text{zero} = 0; \quad \text{pole} = -\frac{1}{R_1 C_1}$$

$$\frac{dP}{dC_1} = \frac{1}{(R_1 C_1)^2} \cdot \frac{1}{R_1} = \frac{1}{R_1 C_1^2}$$

$$S_{C_1}^P = \frac{\frac{dP}{P}}{\frac{dC_1}{C_1}} = \frac{dP}{dC_1} \cdot \frac{C_1}{P} = -\frac{1}{R_1 C_1^2} \cdot C_1 \cdot (R_1 C_1) = -1$$


Similarly

$$S_{R_1}^P = -1$$

As for the sensitivity of zero, since the zero is at 0, which

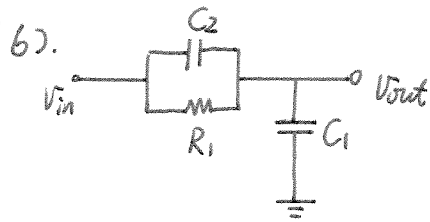is independent of  $R_1$  and  $C_1$ ,  $S_{R_1}^z = S_{C_1}^z = 0$ .





$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{sC_1}}{\frac{1}{sC_1} + R_1 \parallel \frac{1}{sC_2}}$$

$$= \frac{1}{R_1 C_2} \cdot \frac{s + \frac{1}{R_1 C_2}}{R_1 (C_1 + C_2) \left[ s + \frac{1}{R_1 (C_1 + C_2)} \right]}$$

$$\text{zero} = -\frac{1}{R_1 C_2}, \quad \text{pole} = -\frac{1}{R_1 (C_1 + C_2)}$$

$$\frac{dP}{dR_1} = [R_1 (C_1 + C_2)]^{-2} \cdot (C_1 + C_2) = -\frac{C_1 + C_2}{R_1 (C_1 + C_2)} \cdot P = -\frac{P}{R_1}$$

$$S_{R_1}^P = \frac{\frac{dP}{P}}{\frac{dR_1}{R_1}} = \frac{dP}{dR_1} \cdot \frac{R_1}{P} = -1.$$

$$\frac{dP}{dC_1} = [R_1 (C_1 + C_2)]^{-2} \cdot R_1 = -\frac{P}{C_1 + C_2}$$


$$S_{C_1}^P = \frac{\frac{dP}{P}}{\frac{dC_1}{C_1}} = \frac{dP}{dC_1} \cdot \frac{C_1}{P} = -\frac{C_1}{C_1 + C_2}$$

Conversely,

$$S_{C_2}^P = -\frac{C_2}{C_1 + C_2}.$$

From Problem 5).

$$S_{R_1}^Z = S_{C_2}^Z = -1.$$

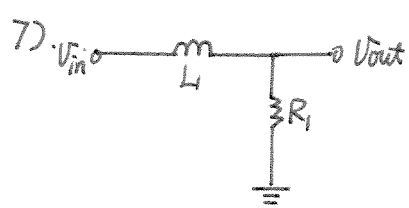

$$\frac{V_{out}}{V_{in}} = \frac{R_1}{R_1 + Ls} = \frac{R_1/L}{s + R_1/L}$$


$$\text{pole} = -\frac{R_1}{L}$$

$$dP = \frac{\partial P}{\partial R_1} \cdot dR_1 + \frac{\partial P}{\partial L} dL = -\frac{1}{L} dR_1 + \frac{R}{L^2} dL$$

$$\Rightarrow \frac{dP}{P} = \frac{dR_1}{R_1} - \frac{dL}{L}$$

$$\left| \frac{dP}{P} \right| \leq 5\%, \text{ and } \left| \frac{dR_1}{R_1} \right| \leq 3\%$$

$$\Rightarrow \left| \frac{dL}{L} \right| \leq 2\%$$

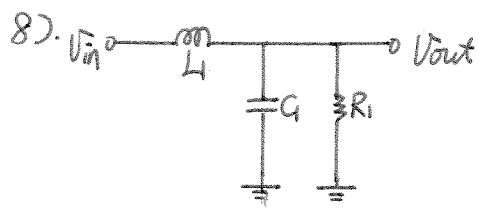

$$\begin{aligned}
 \text{a). } V_{out} &= V_{in} \cdot \frac{R_1 // \frac{1}{Cs}}{R_1 // \frac{1}{Cs} + sL} \\
 &= V_{in} \cdot \frac{\frac{R_1}{R_1Cs + 1}}{\frac{R_1}{R_1Cs + 1} + sL}
 \end{aligned}$$



$$\frac{V_{out}}{V_{in}} = \frac{R_1}{R_1Cs + 1} \cdot \frac{1}{sL + \frac{R_1}{R_1Cs + 1}} = \frac{1}{4C} \cdot \frac{1}{s^2 + \frac{1}{RC}s + \frac{1}{4C}}$$

$$\text{b). poles} = \frac{-\frac{1}{RC} \pm \sqrt{\left(\frac{1}{RC}\right)^2 - \frac{4}{4C}}}{2}$$

$$\text{For them to be real} \Rightarrow \left(\frac{1}{RC}\right)^2 - \frac{4}{4C} \geq 0$$

$$\Rightarrow \frac{1}{RC} \geq \frac{2}{\sqrt{4C}}$$

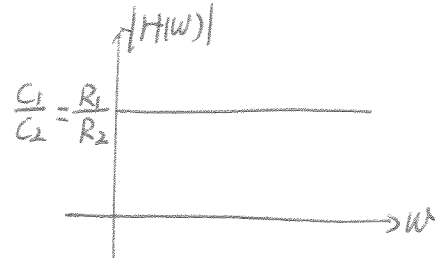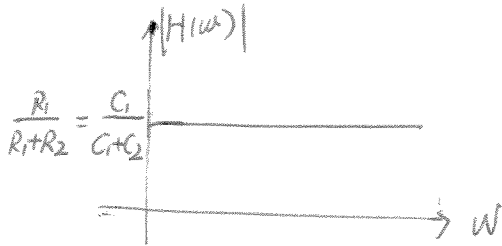9). If the zero and pole coincide, they will neutralize each other, and also render the transfer function flat.



$$10). \quad H(s) = \frac{\alpha s^2 + \beta s + \gamma}{s^2 + \frac{W_n}{Q} s + W_n^2}$$

$$P_{1,2} = -\frac{W_n}{2Q} \pm jW_n \sqrt{1 - \frac{1}{4Q^2}}$$

$$\text{If } Q = \frac{1}{2}, \text{ then } P_{1,2} = -\frac{W_n}{2Q}.$$

11.

$$|H(j\omega)|^2 = \frac{Y^2}{(\omega_n^2 - \omega^2)^2 + \left(\frac{\omega_n}{Q}\omega\right)^2}$$

No peaking means no local minimum for  $(\omega_n^2 - \omega^2)^2 + \left(\frac{\omega_n}{Q}\omega\right)^2$ , which is also known as  $D(\omega)$ .

A local min exists if  $\frac{\partial D(\omega)}{\partial \omega} = 0$ .

$$\frac{\partial D(\omega)}{\partial \omega} = \left(\frac{\partial D(\omega)}{\partial \omega^2}\right) \left(\frac{\partial \omega^2}{\partial \omega}\right), \quad \frac{\partial D(\omega)}{\partial \omega^2} = -2(\omega_n^2 - \omega^2) + \left(\frac{\omega_n}{Q}\right)^2$$

$$\frac{\partial \omega^2}{\partial \omega} = 2\omega, \text{ so } \frac{\partial D(\omega)}{\partial \omega} = 2\omega \left[ -2(\omega_n^2 - \omega^2) + \left(\frac{\omega_n}{Q}\right)^2 \right] = 0$$

$$\text{Solving for } \omega, \text{ we have } \omega = 0, \pm \sqrt{\omega_n^2 - \frac{1}{2} \left(\frac{\omega_n}{Q}\right)^2}$$

Will bring  $D(\omega)$  to its min value.

At  $\omega=0$ , we have the DC value of the transfer function.

However if  $Q^2 < \frac{1}{2}$  or  $Q < \frac{1}{\sqrt{2}}$ ,  $\omega_n^2 - \frac{1}{2} \left(\frac{\omega_n}{Q}\right)^2$  becomes negative, which is not physical. Therefore, there is no peaking for  $Q < \frac{1}{\sqrt{2}}$ . And at  $Q = \frac{1}{\sqrt{2}}$ , we have  $\omega = \pm 0$ , which corresponding to the DC value of the transfer function, not peaking. Therefore, the only option left is for  $Q > \frac{1}{\sqrt{2}}$ , and that is the condition for peaking.

$$12). |H(j\omega)|^2 = \frac{\gamma^2}{(\omega_n^2 - \omega^2)^2 + \left(\frac{\omega_n}{Q}\omega\right)^2}$$

If  $Q > \sqrt{2}$ , it will peak at  $\omega_0 = \omega_n \sqrt{1 - 1/(2Q)^2}$

$$H(j\omega) = \frac{\gamma}{\sqrt{(\omega_n^2 - \omega^2)^2 + \left(\frac{\omega_n}{Q}\omega\right)^2}}$$

$$\Rightarrow H(j\omega_0) = \frac{\gamma}{\sqrt{\left[\omega_n^2 - \left(\omega_n \sqrt{1 - \frac{1}{2Q^2}}\right)^2\right]^2 + \left(\frac{\omega_n}{Q} \omega_n \sqrt{1 - \frac{1}{2Q^2}}\right)^2}}$$


$$= \frac{\gamma}{\sqrt{\left(\omega_n^2 \cdot \frac{1}{2Q^2}\right)^2 + \frac{\omega_n^4}{Q^2} \left(1 - \frac{1}{2Q^2}\right)}}$$

$$= \frac{\gamma}{\sqrt{\frac{\omega_n^4}{4Q^4} + \frac{\omega_n^4}{Q^2} - \frac{\omega_n^4}{2Q^4}}}$$

$$= \frac{Q\gamma}{\omega^2 \sqrt{1 - \frac{1}{4Q^2}}}$$

Normalize to passband  $\Rightarrow \frac{Q}{\sqrt{1 - \frac{1}{4Q^2}}}$

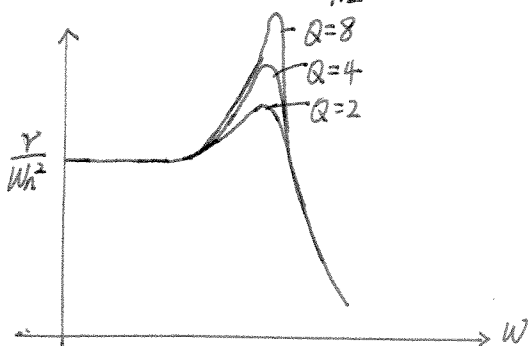$Q=2$ , peak =  $\frac{2}{\sqrt{1 - \frac{1}{4 \cdot 2^2}}} = 2.07$ ;  $Q=4$ , peak = 4.03;  $Q=8$ , peak = 8.02




$$13). \quad H(s) = \frac{\beta s}{s^2 + \frac{\omega_n}{Q}s + \omega_n^2}, \quad H(j\omega) = \frac{j\beta\omega}{\omega_n^2 + j\frac{\omega_n}{Q}\omega - \omega^2}$$

$$|H(j\omega)| = \frac{\beta\omega}{\sqrt{(\omega_n^2 - \omega^2)^2 + \left(\frac{\omega_n}{Q}\omega\right)^2}}$$

At  $\omega = \omega_n$ ,


$$|H(j\omega_n)| = \frac{\beta\omega_n}{\frac{\omega_n}{Q}\omega_n} = \frac{Q}{\omega_n} \beta.$$

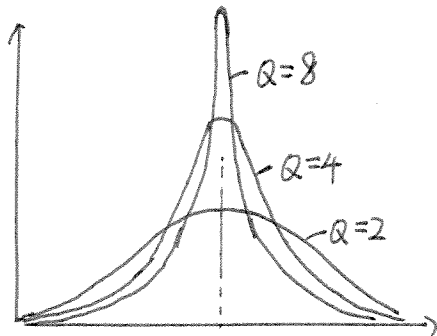So if we normalize to  $\beta$ , we get  $\frac{Q}{\omega_n}$ .








14).

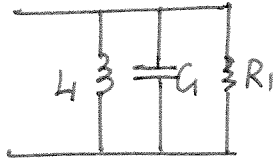

Assume  $R$  is never negative

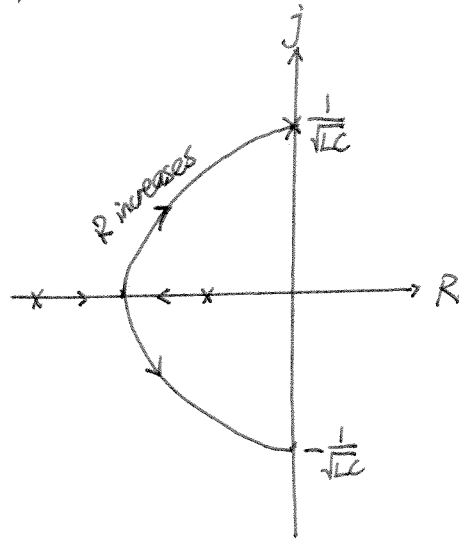

15).

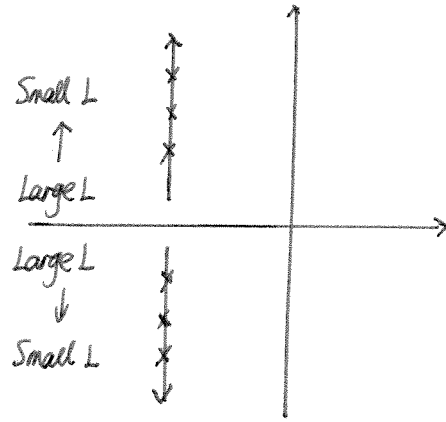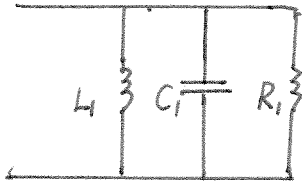

16.

$$1 \text{ dB peaking} \Rightarrow \frac{Q^2}{\left(1 - \frac{1}{4Q^2}\right)} = (1.1)^2 = 1.21$$

$$Q^2 = 1.21 \left(1 - \frac{1}{4Q^2}\right) \Rightarrow 4Q^4 - 4(1.1)^2 Q^2 + (1.1)^2 = 0$$


$$Q^2 = 0.85704, 0.35296, Q = 0.925765, 0.59410$$

$Q = 0.925765$ , since  $Q > \frac{1}{\sqrt{2}}$  for peaking

$$Q = \frac{\omega_n}{\beta} = \frac{RC}{\sqrt{LC}} = R\sqrt{\frac{C}{L}} = 0.925765$$

17.

Sallen and Key filter

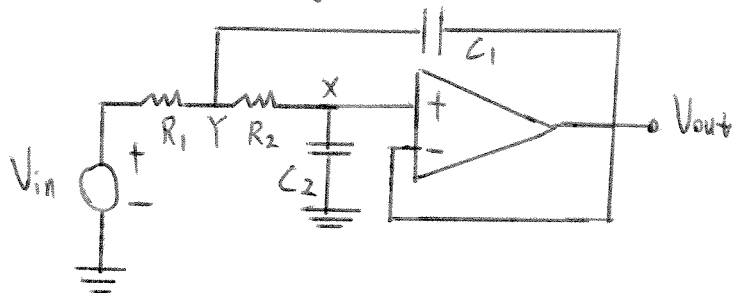

$$H(s) = \frac{1}{R_1 R_2 C_1 C_2 s^2 + (R_1 + R_2) C_2 s + 1}, \quad Q = \frac{1}{R_1 + R_2} \sqrt{\frac{R_1 R_2 C_1}{C_2}}$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$H(s) = \left( s^2 + \frac{(R_1 + R_2) C_2}{R_1 R_2 C_1 C_2} s + \frac{1}{R_1 R_2 C_1 C_2} \right)^{-1}$$

$$P_{1,2} = -\frac{(R_1 + R_2)}{R_1 R_2 C_1} \pm \sqrt{\left( \frac{R_1 + R_2}{R_1 R_2 C_1} \right)^2 - \frac{4}{R_1 R_2 C_1 C_2}}$$

$$P_{1,2} = -\frac{1}{2(R_1 // R_2) C_1} \pm \sqrt{\left( \frac{1}{(R_1 // R_2) C_1} \right)^2 - \frac{4}{R_1 C_1 R_2 C_2}}$$

Assuming  $\frac{4}{R_1 C_1 R_2 C_2} > \frac{1}{[(R_1 // R_2) C_1]^2}$

$$P_{1,2} = -\frac{1}{2(R_1 // R_2) C_1} \pm j 2 \sqrt{\frac{1}{R_1 C_1 R_2 C_2} - \frac{1}{4[(R_1 // R_2) C_1]^2}}$$

17.

a)  $R_1: 0 \rightarrow \infty$


When  $R_1 = 0$ , Poles are at  $\pm\infty$ , so no finite poles. As  $R_1 \uparrow$ ,  $\frac{1}{R_1 C_1 R_2 C_2}$  approaches 0, and

$\frac{1}{4[(R_1/R_2)C_1]^2}$  approaches  $\frac{1}{4[R_2 C_1]^2}$ . There exists

a  $R_1$  such that  $\frac{1}{R_1 C_1 R_2 C_2} = \frac{1}{4[(R_1/R_2)C_1]^2} \Rightarrow$

$$P_{1,2} = -\frac{1}{2(R_1/R_2)C_1}$$

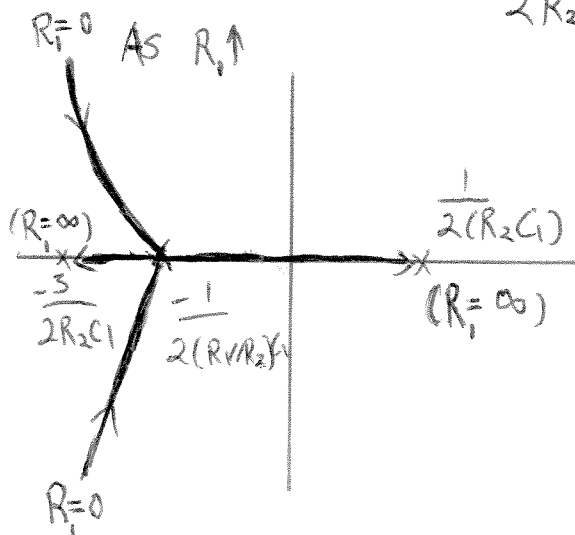As  $R_1 \rightarrow \infty$ ,  $P_{1,2} = -\frac{1}{2R_2 C_1} \pm \frac{1}{R_2 C_1} = -\frac{3}{2R_2 C_1}, \frac{1}{2R_2 C_1}$



17. b)

$R_2$  from  $0 \rightarrow \infty$

When  $R_2 = 0$ ,  $P_{1,2}$  are at  $\pm \infty$

$$\text{As } R_2 \uparrow, \frac{-1}{2(R_1 \parallel R_2)C_1} \rightarrow -\frac{1}{2R_1C_1}$$

$$\frac{1}{R_1C_1R_2C_2} \rightarrow 0, \text{ and } \frac{1}{4[(R_1 \parallel R_2)C_1]^2} \rightarrow \frac{1}{4[R_1C_1]^2}$$


$$\text{For a certain } R_2, \frac{1}{R_1C_1R_2C_2} = \frac{1}{4[(R_1 \parallel R_2)C_1]^2}$$

$$\text{and } P_{1,2} = \frac{-1}{2(R_1 \parallel R_2)C_1}$$

Finally, when  $R_2 = \infty$ ,

$$P_{1,2} = -\frac{1}{2R_1C_1} \pm 2\sqrt{\frac{1}{4[R_1C_1]^2}} = -\frac{1}{2R_1C_1} \pm \frac{1}{R_1C_1}$$
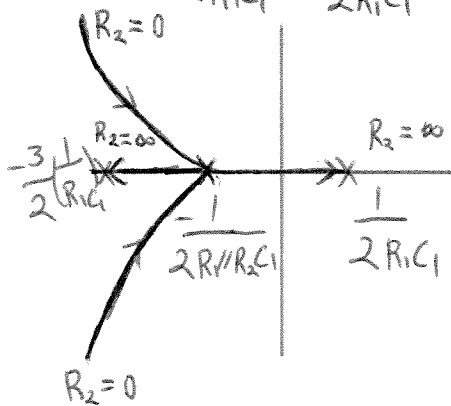
$$P_{1,2} = -\frac{3}{2} \frac{1}{R_1C_1}, \frac{1}{2R_1C_1}$$




17. c)

As  $C_1: 0 \rightarrow \infty$

When  $C_1 = 0$ , poles are at  $\pm \infty$

As  $C_1 \uparrow$ , poles approach 0.

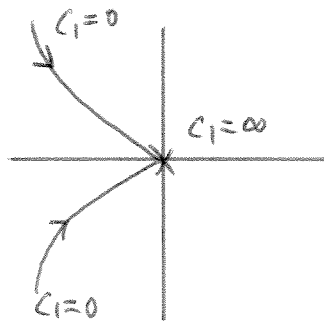



d) As  $C_2: 0 \rightarrow \infty$

When  $C_2 = 0$ , poles are at  $\pm \infty$

When  $C_2 = \infty$ , poles:  $-\frac{1}{2(R_1//R_2)C_1} \pm \frac{1}{R_1//R_2 C_1} = -\frac{3}{2} \left( \frac{1}{R_1//R_2 C_1} \right)$

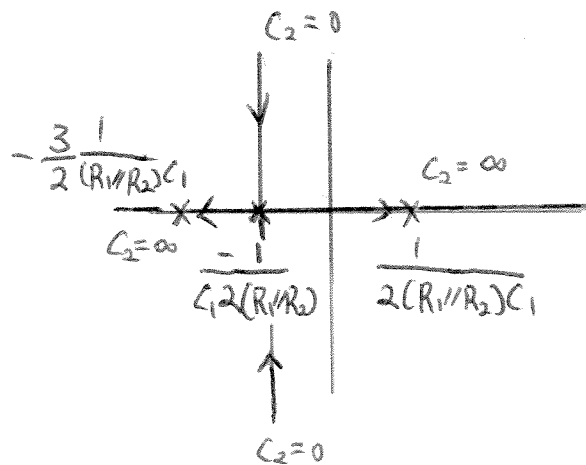$\pm \frac{1}{2 R_1//R_2 C_1}$  (note, real part doesn't depend on  $C_2$ ).



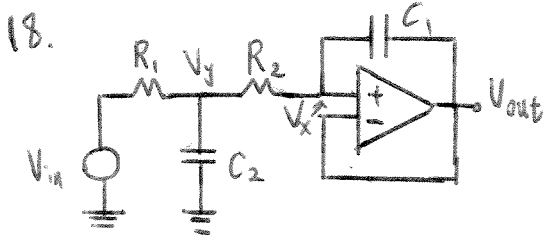


Assuming an ideal op-amp,  $V_x = V_{out}$ . Therefore, no current will flow thru  $C_1$ . Moreover, since the input impedance of an op-amp (ideal) is infinite, no current will flow thru  $R_2$  as well, which means  $V_y = V_x = V_{out}$ .

$$\Rightarrow V_y = V_{out} = \frac{1/C_2 s}{R_1 + 1/C_2 s}$$

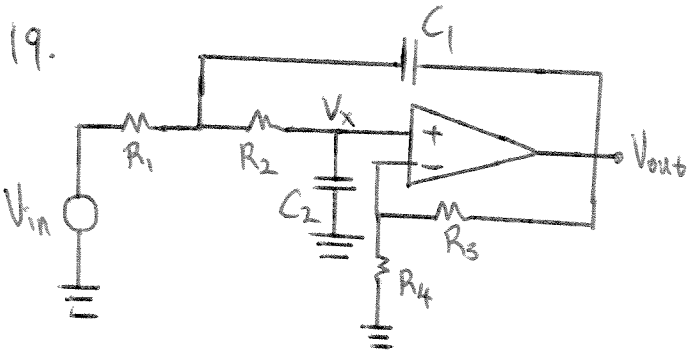Not very useful since it's only a simple single pole lowpass filter. We can implement it with passive components, instead of op-amp.





$$K=4, \quad C_1=C_2$$

$$Q=4$$

$$K = 1 + \frac{R_3}{R_4} = 4 \Rightarrow \frac{R_3}{R_4} = 3, \quad \frac{C_1}{C_2} = 1$$

$$\frac{1}{Q} = \sqrt{\frac{R_1 C_2}{R_2 C_1}} + \sqrt{\frac{R_2 C_2}{R_1 C_1}} - \sqrt{\frac{R_1 C_1}{R_2 C_2}} \frac{R_3}{R_4}$$

$$\frac{1}{Q} = \sqrt{\frac{R_1}{R_2}} + \sqrt{\frac{R_2}{R_1}} - 3\sqrt{\frac{R_1}{R_2}} \Rightarrow \sqrt{\frac{R_2}{R_1}} - 2\sqrt{\frac{R_1}{R_2}} = \frac{1}{Q}$$

$$\frac{1}{Q} = \left(\frac{R_1}{R_2}\right)^{\frac{1}{2}} - 2\left(\frac{R_1}{R_2}\right)^{\frac{1}{2}} \Rightarrow \text{squaring both sides} \Rightarrow$$

$$\frac{1}{Q^2} = 4\left(\frac{R_1}{R_2}\right) - 4 + \left(\frac{R_1}{R_2}\right)^{-1} \Rightarrow \frac{1}{16} = 4\left(\frac{R_1}{R_2}\right) - 4 + \left(\frac{R_2}{R_1}\right)$$

$$\left(\frac{1}{16} + 4\right) \frac{R_1}{R_2} = \frac{R_1}{R_2} \left(4\frac{R_1}{R_2} + \frac{R_2}{R_1}\right) \Rightarrow 4.0625 \frac{R_1}{R_2} = 4\left(\frac{R_1}{R_2}\right)^2 + 1$$

$$4\left(\frac{R_1}{R_2}\right)^2 - 4.0625\left(\frac{R_1}{R_2}\right) + 1 = 0, \quad \frac{R_1}{R_2} = 0.41908, \quad 0.59655$$

This leads to a negative Q.

19.

$$S_{R_1}^{\theta} = -\frac{1}{2} \left[ \sqrt{\frac{R_1 C_2}{R_2 C_1}} - \sqrt{\frac{R_2 C_2}{R_1 C_1}} - (K-1) \sqrt{\frac{R_1 C_1}{R_2 C_2}} \right] \theta$$

$$S_{R_1}^{\theta} = -\frac{1}{2} \left[ \sqrt{0.41908} - \sqrt{1/0.41908} - 3\sqrt{0.41908} \right] \theta$$

$$S_{R_1}^{\theta} = 5.68$$

20.

$$H(s) = \frac{1}{R_1 R_2 C_1 C_2 s^2 + (R_1 + R_2) C_2 s + 1}$$

$$Q = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}}, \quad \omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$\frac{Q}{\sqrt{1 - \frac{1}{4Q^2}}} = 1 \Rightarrow Q^2 = (1.1)^2 \left(1 - \frac{1}{4Q^2}\right)$$

$$\Rightarrow 3.3058 Q^4 - 4Q^2 + 1 = 0$$

$$Q^2 = 0.85704, 0.35296,$$

$$Q = \pm 0.925765, \pm 0.5941$$

$$\text{In order to peak, } Q > \frac{1}{\sqrt{2}} \Rightarrow Q = 0.925765$$

$$\Rightarrow \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}} = 0.925765$$

$$\text{let } \frac{C_1}{C_2} = 1 \Rightarrow \frac{1}{R_1 + R_2} \sqrt{R_1 R_2} = 0.925765$$

$$\Rightarrow R_1 R_2 = (0.925765)^2 (R_1 + R_2)^2$$

$$\frac{R_1 R_2}{R_1 + R_2} = R_1 // R_2 = 0.85704 (R_1 + R_2)$$

$$R_1 // R_2 = 0.85704 (R_1 + R_2)$$

$$\text{only if } \frac{C_1}{C_2} = 1$$

21.


$$S_{R_1}^Q = 2, \quad C_2 = C_1, \quad Q = f\left(\sqrt{\frac{R_2}{R_1}}\right)$$

Range of  $Q$  and  $\sqrt{R_2/R_1}$

$$S_{R_1}^Q = -\frac{1}{2} \left[ \sqrt{\frac{R_1 C_2}{R_2 C_1}} - \sqrt{\frac{R_2 C_2}{R_1 C_1}} - (K-1) \sqrt{\frac{R_1 C_1}{R_2 C_2}} \right] Q$$

$$S_{R_1}^Q = -\frac{1}{2} + Q \sqrt{\frac{R_2 C_2}{R_1 C_1}} \Rightarrow 2 = -\frac{1}{2} + Q \sqrt{\frac{R_2}{R_1}}$$
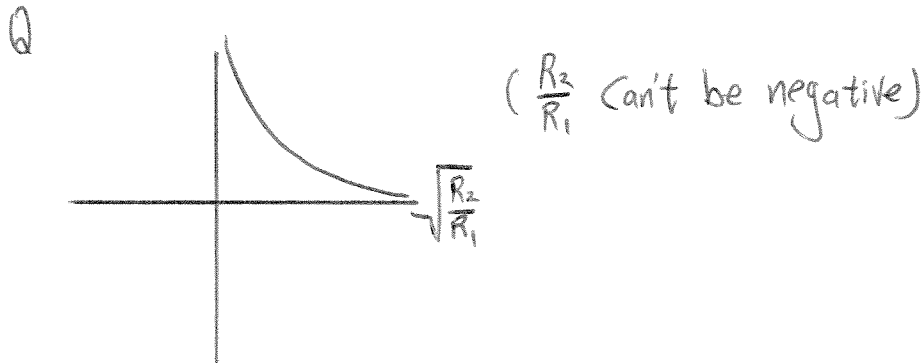
$$\Rightarrow 2.5 = Q \sqrt{\frac{R_2}{R_1}}, \quad Q = \frac{2.5}{\sqrt{R_2/R_1}}$$




Range:

$$0 < Q < \infty$$

$$0 < \sqrt{\frac{R_2}{R_1}} < \infty$$

If the transfer function does not want to experience peaking, then  $0 < Q \leq \frac{1}{\sqrt{2}} \Rightarrow 3.5356 \leq \sqrt{\frac{R_2}{R_1}} < \infty$

22.

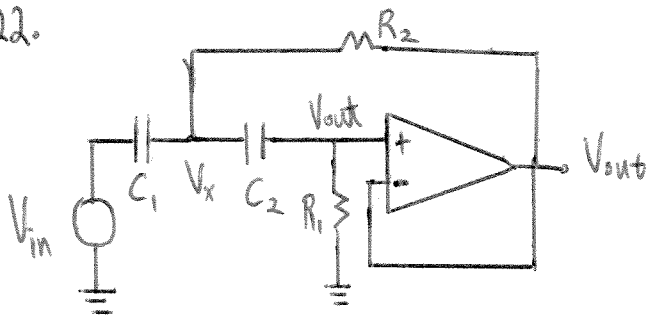

Assuming an ideal  
op amp.

$$1) (V_x - V_{in})C_1 s + (V_x - V_{out})\left(C_2 s + \frac{1}{R_2}\right) = 0, \text{ nodal equation at } V_x.$$

$$2) (V_x - V_{out})C_2 s - \frac{V_{out}}{R_1} = 0, \text{ nodal equation at } V_{out}.$$

$$2) \Rightarrow V_x = V_{out} \left[ \frac{C_2 s + 1/R_1}{C_2 s} \right] \quad (A) \quad \text{The stuff in the bracket becomes "A"}$$

$$1) \Rightarrow (AV_{out} - V_{in})C_1 s + (AV_{out} - V_{out})\left[C_2 s + \frac{1}{R_2}\right] = 0$$

$$\Rightarrow AV_{out}C_1 s + V_{out}(A-1)\left(C_2 s + \frac{1}{R_2}\right) = V_{in}C_1 s$$

$$A-1 = \frac{1}{R_1 C_2 s}, \quad A = \frac{C_2 s + 1/R_1}{C_2 s}$$

substitute  $(A-1)$  and  $A$  into 1)  $\Rightarrow$

$$\left(\frac{C_2 s + 1/R_1}{C_2 s}\right) C_1 s V_{out} + \left(C_2 s + \frac{1}{R_2}\right) \frac{1}{R_1 C_2 s} V_{out} = V_{in} C_1 s$$

22.

$$\frac{V_{out}}{V_{in}} = \frac{C_1 S}{\frac{C_1}{C_2} \left( C_2 S + \frac{1}{R_1} \right) + \frac{1}{R_1 C_2 S} \left( C_2 S + \frac{1}{R_2} \right)}$$

Rearranging

$$H(s) = \frac{V_{out}}{V_{in}} = \frac{S^2}{S^2 + \left( \frac{C_1 + C_2}{C_2 R_1 C_1} \right) S + \frac{1}{R_2 C_2 R_1 C_1}}$$

$$\omega_n^2 = \frac{1}{R_2 C_2 R_1 C_1}, \quad \frac{\omega_n}{Q} = \frac{C_1 + C_2}{C_2 R_1 C_1}$$

$$\omega_n = \frac{1}{\sqrt{R_2 C_2 R_1 C_1}}, \quad Q = \sqrt{\frac{C_2 C_1 R_1}{R_2}} \left( \frac{1}{C_1 + C_2} \right)$$

23.

$$Q = \frac{1}{C_1 + C_2} \sqrt{\frac{C_2 C_1 R_1}{R_2}} \Rightarrow \frac{1}{Q} = (C_1 + C_2) \sqrt{\frac{R_2}{C_2 C_1 R_1}}$$

$$1) \frac{d}{dQ} \left[ \frac{1}{Q} \right] = -\frac{1}{Q^2} \Rightarrow d \left[ \frac{1}{Q} \right] = -\frac{1}{Q^2} dQ$$

$$2) \frac{d \left[ \frac{1}{Q} \right]}{dR_2} = \frac{1}{2} \frac{C_1 + C_2}{\sqrt{C_2 C_1 R_1 R_2}} \Rightarrow d \left[ \frac{1}{Q} \right] = \frac{1}{2} \frac{C_1 + C_2}{\sqrt{C_2 C_1 R_1 R_2}} dR_2$$

Equating 1) and 2) and multiple 2) by  $\frac{R_2}{R_2}$

$$-\frac{dQ}{Q^2} = \frac{1}{2} \frac{(C_1 + C_2) R_2}{\sqrt{C_2 C_1 R_1 R_2}} \frac{dR_2}{R_2}$$

$$\frac{dQ}{Q} / \frac{dR_2}{R_2} = -\frac{Q}{2} \frac{(C_1 + C_2)}{\sqrt{C_1 C_2 R_1}} \sqrt{\frac{R_2}{R_2}}$$

$$S_{R_2}^Q = -\frac{Q}{2} \frac{(C_1 + C_2)}{\sqrt{C_1 C_2 R_1}} = -\frac{1}{2}$$

$$\frac{1}{Q} = (C_1 + C_2) \sqrt{\frac{R_2}{C_2 C_1 R_1}} = C_1 \sqrt{\frac{R_2}{C_2 C_1 R_1}} + C_2 \sqrt{\frac{R_2}{C_2 C_1 R_1}}$$

$$\frac{\partial \left( \frac{1}{Q} \right)}{\partial C_1} = \frac{1}{2} \sqrt{\frac{R_2}{C_2 R_1 C_1}} - \frac{C_2}{2 C_1} \sqrt{\frac{R_2}{C_2 R_1 C_1}}, \quad \frac{d \left( \frac{1}{Q} \right)}{dQ} = -\frac{1}{Q^2}$$

$$\text{Rearranging} \Rightarrow -\frac{\partial Q}{Q^2} = \frac{\partial C_1}{C_1} \left( \frac{C_1 - C_2}{2} \sqrt{\frac{R_2}{C_2 R_1 C_1}} \right)$$

$$\frac{\partial Q}{Q} / \frac{\partial C_1}{C_1} = S_{C_1}^Q = -Q \left( \frac{C_1 - C_2}{2} \sqrt{\frac{R_2}{C_2 R_1 C_1}} \right)$$

23.

Similarly:

$$S_{C_2}^R = -R \left( \frac{C_2 - C_1}{2} \sqrt{\frac{R_2}{C_2 R_1 C_1}} \right)$$

$$S_{R_1}^R = R \left( \frac{C_1 + C_2}{2} \sqrt{\frac{R_2}{C_2 C_1 R_1}} \right) = \frac{1}{2}$$



24.

$$\frac{V_{out}(s)}{V_{in}} = \frac{\alpha s^2}{s^2 + \frac{\omega_n s}{Q} + \omega_n^2}$$


Cross-multiply.

$$V_{out} s^2 + V_{out} \frac{\omega_n s}{Q} + V_{out} \omega_n^2 = V_{in} \alpha s^2$$

Rearranging

$$V_{out} = V_{in} \frac{\alpha}{\omega_n^2} s^2 - V_{out} \frac{s^2}{\omega_n^2} - V_{out} \frac{s}{Q \omega_n}$$

Block diagram:

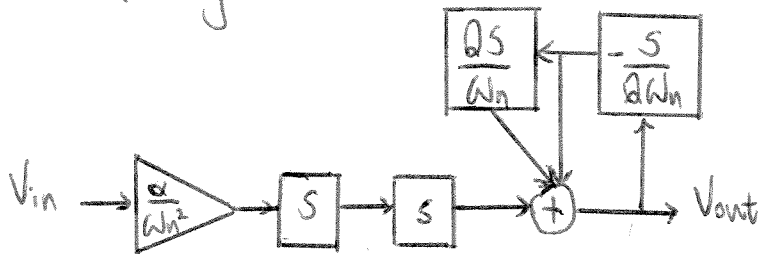

25.

$$Q = 2, \omega_n = (2\pi)(2 \times 10^6)$$

$$R_6 = R_3, R_1 = R_2, C_1 = C_2$$

$$100 \text{ pF} < \text{Total } C < 1 \text{ nF}, \quad 1 \text{ k}\Omega < \text{Total } R < 50 \text{ k}\Omega$$

$$\frac{\omega_n}{Q} = \frac{R_4}{R_4 + R_5} \left( \frac{1}{R_1 C_1} \right), \quad \omega_n^2 = \frac{R_6}{R_3} \left( \frac{1}{R_1 R_2 C_1 C_2} \right)$$

$$\text{Since } R_6 = R_3 \Rightarrow \omega_n^2 = \left( \frac{1}{R_1 C_1} \right)^2 = (2\pi \times 2 \times 10^6)^2$$

$$\frac{1}{R_1 C_1} = 2\pi \times 2 \times 10^6 = \omega_n$$

$$Q = \frac{R_4 + R_5}{R_4} = 2 \Rightarrow R_5 = R_4$$

$$\text{Let } C_1 = C_2 = 100 \text{ pF}, \quad R_1 = \frac{1}{(2\pi)(2 \times 10^6)(100 \text{ pF})} = 795.77 \Omega$$

$$\text{So } R_1 = R_2 = 795.77 \Omega, \quad C_1 = C_2 = 100 \text{ pF.}$$

Since  $R_3, R_4, R_5, R_6$  don't affect  $Q$  and  $\omega_n$ ,  
let them be  $500 \Omega$  each.

$$\text{Total } R: (4)(500) + (2)(795.77) = 3.6 \text{ k}\Omega$$

$$\text{Total } C: 100 \text{ pF} + 100 \text{ pF} = 200 \text{ pF.}$$

26.


$$\frac{\omega_n}{Q} = \frac{R_4}{R_4 + R_5} \frac{1}{R_1 C_1}, \quad \omega_n^2 = \frac{R_6}{R_3} \cdot \frac{1}{R_1 R_2 C_1 C_2}$$

$$Q = \omega_n \left( \frac{R_4 + R_5}{R_4} \right) R_1 C_1, \quad \omega_n = \sqrt{\frac{R_6}{R_3} \left( \frac{1}{R_1 R_2 C_1 C_2} \right)}$$

$$Q = \sqrt{\frac{R_6}{R_3} \left( \frac{1}{R_1 R_2 C_1 C_2} \right)} \left( \frac{R_4 + R_5}{R_4} \right) R_1 C_1$$

$$Q = \sqrt{\frac{R_6}{R_3}} \sqrt{\frac{R_1 C_1}{R_2 C_2}} \left( \frac{R_4 + R_5}{R_4} \right)$$

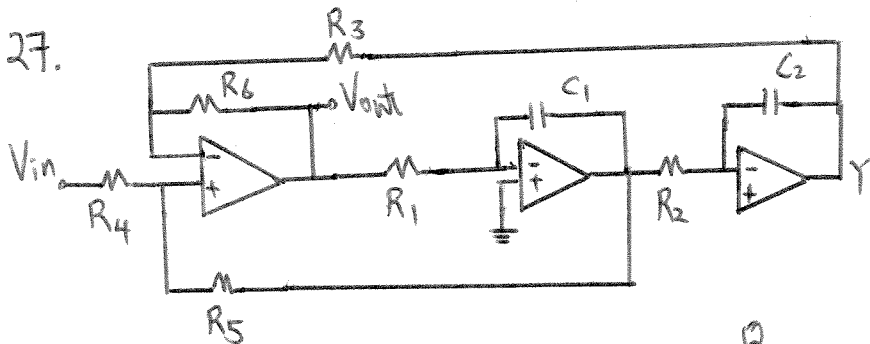If  $R_6 = R_3$ ,  $Q$  doesn't depend on  $R_6$  and  $R_3$ ,  
hence zero sensitivity.



Low pass, low freq gain of 2.  $S_{R_3, R_6}^Q = 0$

$$\frac{V_Y}{V_{in}} = \left( \frac{\alpha S^2}{S^2 + \frac{\omega_n}{Q} S + \omega_n^2} \right) \left( \frac{1}{R_1 R_2 C_1 C_2 S^2} \right) \quad \text{Low pass transfer function}$$

Low freq gain:  $\frac{\alpha}{\omega_n^2 R_1 R_2 C_1 C_2}$ , where  $\alpha = \frac{R_5}{R_4 + R_5} \left( 1 + \frac{R_6}{R_3} \right)$

and  $\omega_n^2 = \frac{R_6}{R_3} \left( \frac{1}{R_1 R_2 C_1 C_2} \right)$

Therefore, low freq gain:  $\frac{\alpha}{\frac{R_6}{R_3}} = \frac{R_5}{R_4 + R_5} \left( 1 + \frac{R_6}{R_3} \right) \left( \frac{R_3}{R_6} \right)$

$$S_{R_3, R_6}^Q = \frac{Q}{2} \frac{|R_3 - R_6|}{1 + R_5/R_4} \sqrt{\frac{R_2 C_2}{R_3 R_6 R_1 C_1}}$$

To obtain  $S_{R_3, R_6}^Q = 0$ ,  $R_3 = R_6$ , however this makes the low freq gain:  $2 \left( \frac{R_5}{R_4 + R_5} \right) \neq 2$ .

Therefore, it's impossible a low freq gain of 2 if  $S_{R_3, R_6}^Q = 0$ .

28.

Peaking: 1 dB,  $R_3 = R_6$

Normalized Peak Value:  $\frac{Q}{\sqrt{1 - (4Q^2)^{-1}}} = 1.01$

solving for  $Q^2$ :  $0.8570, 0.3830$  (not possible for peaking)

$$\frac{\omega_n}{Q} = \frac{R_4}{R_4 + R_5} \left( \frac{1}{R_1 C_1} \right), \quad \left( \frac{\omega_n}{Q} \right)^2 = \left( \frac{R_4}{R_4 + R_5} \right)^2 \left( \frac{1}{R_1 C_1} \right)^2$$

$$\omega_n^2 = \frac{R_6}{R_3} \left( \frac{1}{R_1 R_2 C_1 C_2} \right) = \frac{1}{R_1 R_2 C_1 C_2} \quad (\text{since } R_6 = R_3)$$

$$\text{Therefore, } Q^2 = \left( \frac{R_1 C_1}{R_2 C_2} \right) \left( \frac{R_4 + R_5}{R_4} \right)^2 = 0.8570$$

$$\text{Low pass gain: } 2 \frac{R_5}{R_4 + R_5} = \alpha \quad (\text{since } R_6 = R_3)$$


$$\text{so } \frac{\alpha}{2} = \frac{R_5}{R_4 + R_5}, \quad \frac{R_4}{R_4 + R_5} = 1 - \frac{\alpha}{2} \Rightarrow \frac{R_4 + R_5}{R_4} = \left( 1 - \frac{\alpha}{2} \right)^{-1}$$

$$\text{so } \left( \frac{R_1 C_1}{R_2 C_2} \right) \left( 1 - \frac{\alpha}{2} \right)^{-2} = 0.8570, \quad \text{if } \alpha = 1 \Rightarrow \frac{R_1 C_1}{R_2 C_2} = 0.214.$$

However, can't go down any further without knowing

more information.

29.

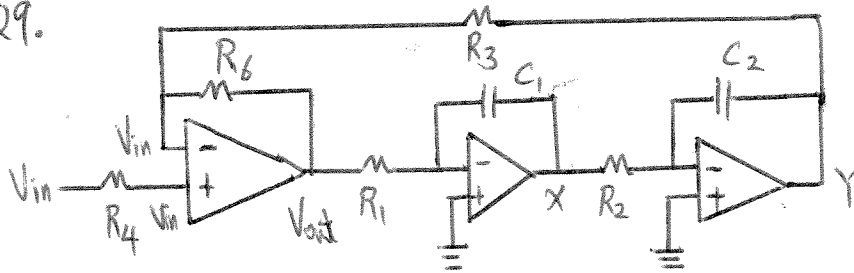

$$V_x = -\frac{V_{out}}{R_1} \left( \frac{1}{C_1 s} \right), \quad V_Y = -\frac{V_x}{R_2} \left( \frac{1}{C_2 s} \right), \quad V_{out} = V_{in} - \frac{(V_Y - V_{in}) R_6}{R_3}$$

$$\text{Substituting } V_x \text{ into } V_Y \Rightarrow V_Y = \frac{V_{out}}{R_1} \left( \frac{1}{C_1 s} \right) \left( \frac{1}{R_2 C_2 s} \right)$$

Substituting  $V_Y$  into  $V_{out}$  and rearranging:

$$\frac{V_{out}}{V_{in}} = \frac{(R_1 C_1)(R_2 C_2) s^2 \left( 1 + \frac{R_6}{R_3} \right)}{(R_1 C_1)(R_2 C_2) s^2 + \frac{R_6}{R_3}}$$

$$\frac{V_{out}}{V_{in}} = \frac{s^2 \left( 1 + \frac{R_6}{R_3} \right)}{s^2 + \frac{R_6}{R_3} \left( \frac{1}{R_1 C_1 R_2 C_2} \right)}$$


Simplifying

$$\omega_n^2 = \frac{R_6}{R_3} \left( \frac{1}{R_1 C_1 R_2 C_2} \right), \quad Q = \infty$$

$$\alpha = \left( 1 + \frac{R_6}{R_3} \right)$$

30.

TOW-Thomas Biquad:

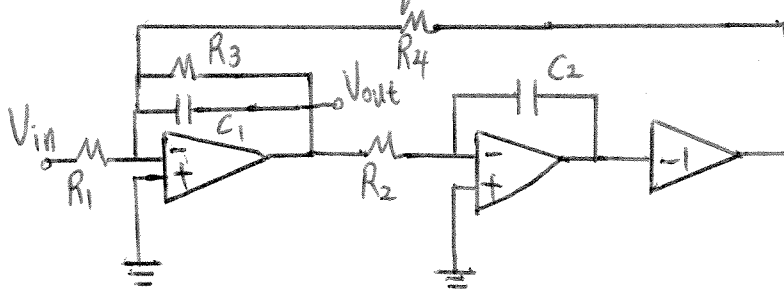

$$\omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}, \quad Q^{-1} = \frac{1}{R_3} \sqrt{\frac{R_2 R_4 C_2}{C_1}}$$

$$\frac{\partial \omega_n}{\partial R_2} = -\frac{1}{2} \frac{1}{R_2 \sqrt{R_2 R_4 C_1 C_2}} = -\frac{1}{2} \frac{\omega_n}{R_2}$$

$$\frac{\partial \omega_n}{\omega_n} / \frac{\partial R_2}{R_2} = S_{R_2}^{\omega_n} = -\frac{1}{2}$$

Since  $R_2, R_4, C_1, C_2$  are equivalent in  $\omega_n$ 's definition, all of their sensitivities =  $-\frac{1}{2}$

Sensitivities of  $Q$ :

$$\frac{\partial Q}{\partial R_3} = \frac{1}{\sqrt{R_2 R_4 C_2}} \left( \frac{R_3}{R_3} \right) \Rightarrow \frac{\partial Q}{Q} = \frac{\partial R_3}{R_3} \Rightarrow S_{R_3}^Q = 1$$

$$\frac{\partial Q}{\partial C_1} = \frac{1}{2} R_3 \left( \frac{C_1}{R_2 R_4 C_2} \right)^{-\frac{1}{2}} \left( \frac{1}{R_2 R_4 C_2} \right) \frac{C_1}{C_1} \Rightarrow \frac{\partial Q}{Q} = \frac{1}{2} \frac{\partial C_1}{C_1} \Rightarrow S_{C_1}^Q = \frac{1}{2}$$

$$\frac{\partial Q}{\partial R_2} = -\frac{1}{2} R_3 \left( \frac{C_1}{R_2 R_4 C_2} \right)^{-\frac{1}{2}} \frac{C_1}{R_4 C_2} \left( \frac{1}{R_2^2} \right) \Rightarrow \frac{\partial Q}{Q} = -\frac{1}{2} \frac{\partial R_2}{R_2} \Rightarrow S_{R_2}^Q = -\frac{1}{2}$$

30.

Since  $R_2, R_4$  and  $C_2$  are equivalent in the expression

$$S_{R_2, R_4, C_2}^Q = -\frac{1}{2}$$


$$\text{So, } S_{R_2, R_4, C_1, C_2}^{\omega_1} = -\frac{1}{2}, \quad S_{R_1, R_3}^{\omega_1} = 0$$

$$S_{R_2, R_4, C_2}^Q = -\frac{1}{2}, \quad S_{C_1}^Q = \frac{1}{2}, \quad S_{R_3}^Q = 1$$

$$S_{R_1}^Q = 0$$



31.

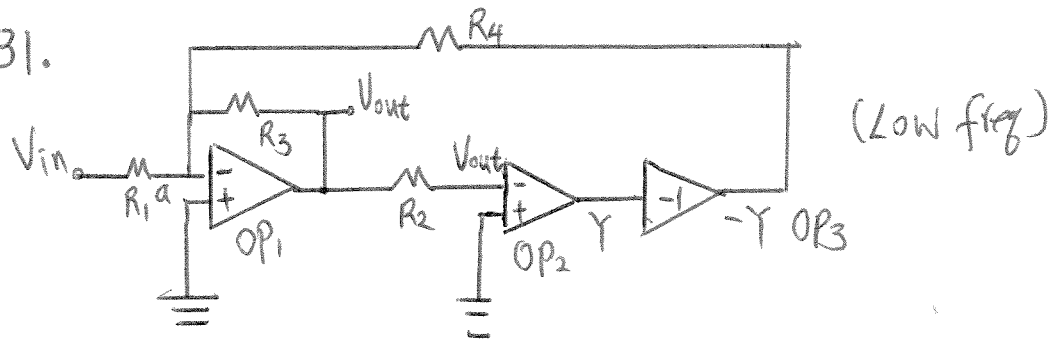

$V_{out}$  equals zero because of OP2's negative feedback.

Likewise,  $V_a$  equals to zero as well.

So, summing all the currents thru  $R_3$ , we have

$$-\left(\frac{0 - V_Y}{R_4} + \frac{V_{in}}{R_1}\right) R_3 = V_{out} = 0$$

$$\Rightarrow \frac{V_{in}}{R_1} = \frac{V_Y}{R_4} \Rightarrow \frac{V_Y}{V_{in}} = \frac{R_4}{R_1}$$

32.

$$\frac{V_Y}{V_{in}} = \frac{R_3 R_4}{R_1} \left( \frac{1}{R_2 R_3 R_4 C_1 C_2 S^2 + R_2 R_4 C_2 S + R_3} \right)$$

$$\omega_n = (2\pi)(10 \text{ MHz}), \quad R_3 = 1\text{K}, \quad R_2 = R_4, \quad C_1 = C_2$$

$$\omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}, \quad Q = \frac{1}{R_3} \sqrt{\frac{R_2 R_4 C_2}{C_1}}$$

Peaking: 1dB

$$\frac{Q}{\sqrt{1 - (4Q^2)^{-1}}} = 1.1, \quad Q^2 = 0.8570$$


$$\omega_n = \frac{1}{\sqrt{(R_2 C_1)^2}} = (2\pi)(10 \times 10^6) \Rightarrow \frac{1}{R_2 C_1} = (2\pi)(10 \times 10^6)$$

$$\frac{1}{Q} = \frac{1}{1000} \sqrt{R_2^2} = \frac{1}{Q} = \frac{R_2}{1000} \Rightarrow \begin{array}{l} R_2 = 1166.860 \text{ ohm} \\ R_2 = 1.2 \text{ K}\Omega \end{array}$$

Solving for  $C_1$  we have:  $C_1 = 13.64 \text{ pf}$ .

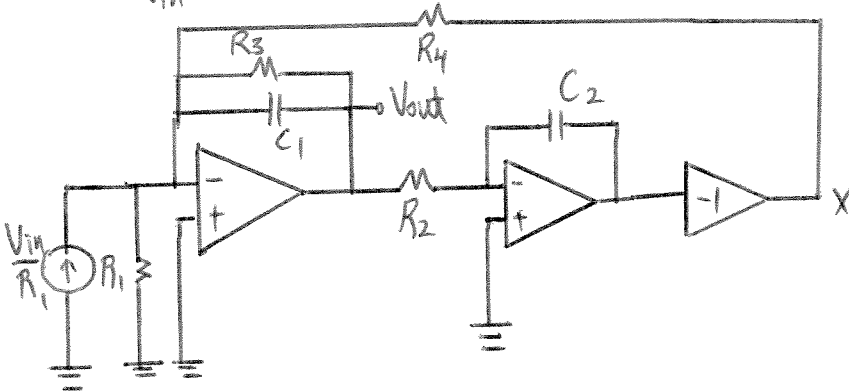33.

$$\frac{V_Y}{V_{in}} = \frac{R_3 R_4}{R_1} \left( \frac{1}{R_2 R_3 R_4 C_1 C_2 S^2 + R_2 R_4 C_2 S + R_3} \right)$$



When  $R_1$  and  $V_{in}$  are replaced with its Norton equivalent, we see that the "upper" terminal of  $R_1$  is at virtual ground. Since  $R_1$ 's two terminals are at the same potential, no current will flow through it, therefore it can be seen as an open. So  $R_1$  is not in the signal path, and therefore will not affect the frequency response. However, since its magnitude is embedded in the Norton current source, it will affect the DC gain.

34.


$$Z_{in} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4} \quad (\text{for circuit diagram, please refer to Problem \# 35})$$

For  $Z_{in}$  to be inductive, the following combinations will work.

| <u>1</u>  | <u>2</u>  | <u>3</u>  |
|-----------|-----------|-----------|
| $Z_5 = R$ | $Z_5 = R$ | $Z_5 = R$ |
| $Z_4 = R$ | $Z_4 = C$ | $Z_4 = C$ |
| $Z_3 = R$ | $Z_3 = R$ | $Z_3 = R$ |
| $Z_2 = C$ | $Z_2 = C$ | $Z_2 = R$ |
| $Z_1 = R$ | $Z_1 = C$ | $Z_1 = R$ |

Any other combination will result in DC path blockage at a node. Moreover, in #2 it's assumed that the input can provide a DC bias.

35.

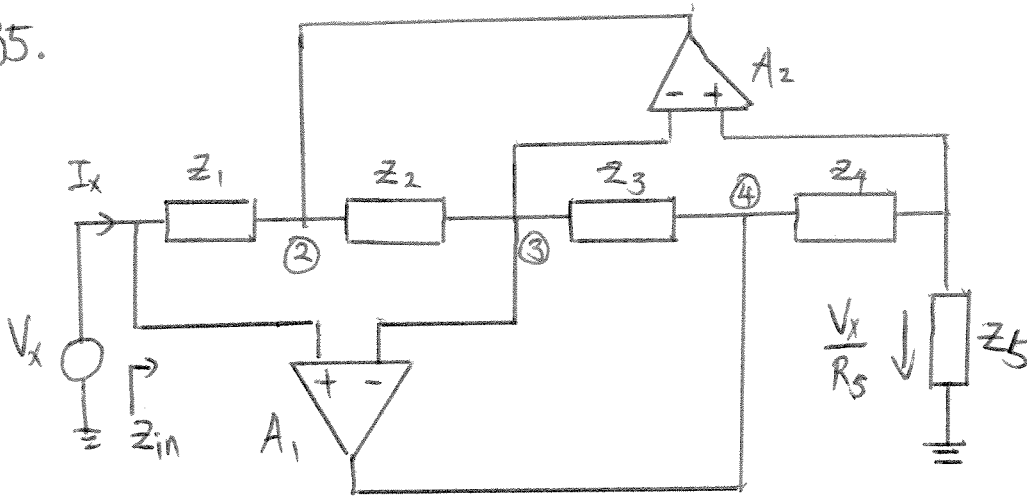

$$z_{in} = \frac{z_1 z_3 z_5}{z_2 z_4}$$

For  $z_{in}$  to be Capacitive, the following combinations can be used.

| <u>1</u>  | <u>2</u>  | <u>3</u>  | <u>4</u>  | <u>5</u>  |
|-----------|-----------|-----------|-----------|-----------|
| $z_5 = C$ | $z_5 = C$ | $z_5 = R$ | $z_5 = R$ | $z_5 = R$ |
| $z_4 = R$ | $z_4 = R$ | $z_4 = R$ | $z_4 = R$ | $z_4 = C$ |
| $z_3 = R$ | $z_3 = R$ | $z_3 = R$ | $z_3 = C$ | $z_3 = C$ |
| $z_2 = R$ | $z_2 = C$ | $z_2 = R$ | $z_2 = R$ | $z_2 = R$ |
| $z_1 = R$ | $z_1 = C$ | $z_1 = C$ | $z_1 = R$ | $z_1 = C$ |

Any other combination results in a DC path blockage at a node. Moreover, in # 2, 3, 5, it is assumed that the input node will produce a DC bias.

36.

$$z_{in} = \frac{z_1 z_3 z_5}{z_2 z_4}$$

$$z_5 = R_x + \frac{1}{Cs}, \quad z_4 = R_x, \quad z_3 = R_x, \quad z_2 = R_x,$$

$$z_1 = \frac{1}{Cs}$$

$$z_{in} = \frac{\frac{R_x}{Cs} (R_x + \frac{1}{Cs})}{R_x^2} = \frac{1}{Cs R_x} (R_x + \frac{1}{Cs})$$

$$z_{in} = \frac{1}{Cs} + \frac{1}{Cs^2 R_x}$$

$$V_{out} = \frac{V_{in} [s^2 [C^2 R_x] + Cs]}{[s^2 [C^2 R_x] + sC + R_1 [s^3 C^3 R_x]}$$

$$\frac{V_{out}}{V_{in}} = \frac{sCR_x + 1}{s^2 R_1 R_x C^2 + sCR_x + 1}$$

37. 
$$Z_{in} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4}$$
 (for circuit diagram, please refer to problem # 35)

Let  $Z_5$  be a capacitor,  $Z_2$  and  $Z_4$  be large resistors and  $Z_1$  and  $Z_3$  be small resistors compared to  $Z_2$  and  $Z_4$ .

For example, let  $Z_1$  and  $Z_3$  equal  $50\Omega$  and  $Z_2$  and  $Z_4$  equal  $5k\Omega$ . Then there's a  $(100)^2 = 10000$  multiplication factor onto  $C_5$ .

38.

Butterworth filter: roll-off of 1dB @  $\omega = 0.9\omega_0$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (0.9)^{2n}}} = 0.9 \Rightarrow 2n = \frac{\log(0.2345679)}{\log(0.9)}$$

$$n = 6.88$$


So we need a 7th order.



39.

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (0.9)^{2n}}}$$

|                    |                     |
|--------------------|---------------------|
| $n=0 \Rightarrow$  | $-3 \text{ dB}$     |
| $n=1 \Rightarrow$  | $-2.577 \text{ dB}$ |
| $n=3 \Rightarrow$  | $-1.851 \text{ dB}$ |
| $n=5 \Rightarrow$  | $-1.299 \text{ dB}$ |
| $n=7 \Rightarrow$  | $-0.895 \text{ dB}$ |
| $n=9 \Rightarrow$  | $-0.607 \text{ dB}$ |
| $n=11 \Rightarrow$ | $-0.408 \text{ dB}$ |
| $n=13 \Rightarrow$ | $-0.272 \text{ dB}$ |
| $n=15 \Rightarrow$ | $-0.180 \text{ dB}$ |

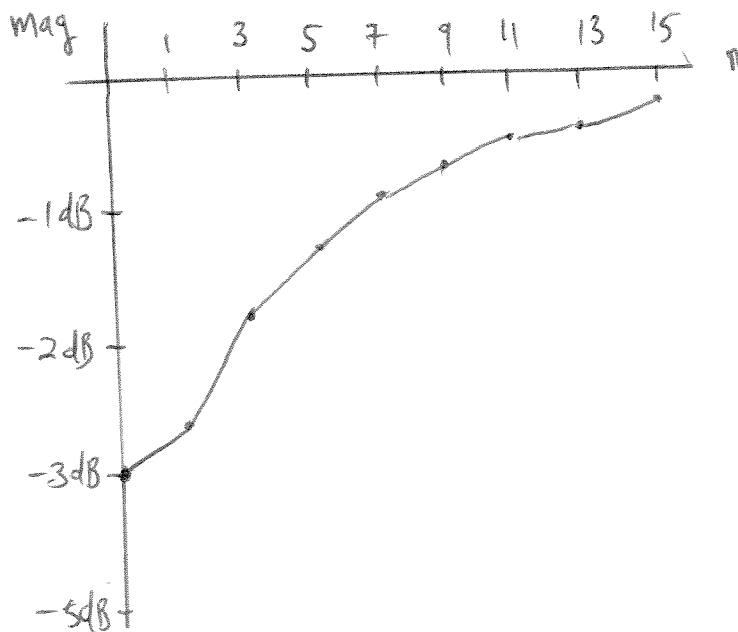


40.


$1.1W_0$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (1.1)^{2n}}} = 0.1 \Rightarrow 2n = \frac{\log(99)}{\log(1.1)}$$

$n = 24.106$  so needs  $n = 25$ .

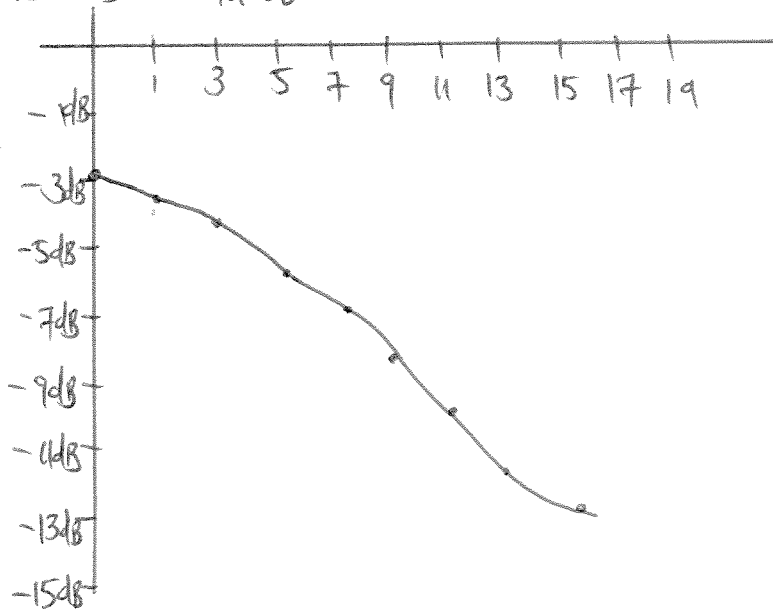- $n=0 \Rightarrow -3 \text{ dB}$
- $n=1 \Rightarrow -3.4439 \text{ dB}$
- $n=3 \Rightarrow -4.427 \text{ dB}$
- $n=5 \Rightarrow -5.555 \text{ dB}$
- $n=7 \Rightarrow -6.810 \text{ dB}$
- $n=9 \Rightarrow -8.169 \text{ dB}$
- $n=11 \Rightarrow -9.61 \text{ dB}$
- $n=13 \Rightarrow -11.112 \text{ dB}$
- $n=15 \Rightarrow -12.66 \text{ dB}$



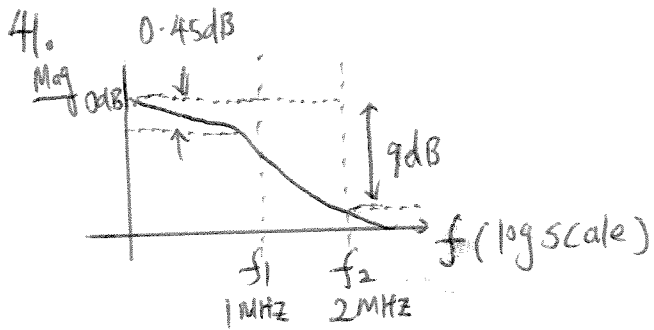

$$|H(f)| = \frac{1}{\left(1 + \left(\frac{2\pi f}{\omega_0}\right)^6\right)^{\frac{1}{2}}}$$

$$|H(5\text{MHz})| = 0.02438$$

$$\text{Suppression: } 20 \log(0.02438) = -32.26 \text{ dB}$$

42.

Low-pass Butterworth: Passband flatness of 0.5 dB  
 $f_1 = 1 \text{ MHz}$ ,  $f_2 = 2 \text{ MHz}$ , order  $< 5$

$$-0.5 \text{ dB} = 20 \log(x) \Rightarrow x = 0.944$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^{2n}}} = 0.944 \Rightarrow \frac{1}{\left(1 + \left(\frac{1}{f_0}\right)^{2n}\right)} = (0.944)^2$$

@  $f = 1 \text{ MHz}$

$$\Rightarrow 1 + \frac{1}{(f_0)^{2n}} = \frac{1}{(0.944)^2} \Rightarrow f_0 = 10^{\frac{0.91306}{2n}}$$

for  $n=1$ ,  $f_0 \approx 2.86 \text{ MHz}$

for  $n=5$ ,  $f_0 \approx 1.234 \text{ MHz}$

Therefore, for greatest attenuation  $n=5$

$$\text{So } H(2 \text{ MHz}) = \frac{1}{\sqrt{1 + \left(\frac{2}{1.234}\right)^{10}}} = 0.089$$


$$20 \log(0.089) = -21.0 \text{ dB at } n=5$$

43.

$$P_k = \omega_0 \exp\left(\frac{j\pi}{2}\right) \exp\left(j \frac{2k-1}{2n} \pi\right), \quad k=1, 2, \dots, n$$

The poles lie on a circle because all of their magnitude, which is the distance from the origin to the poles, are the same ( $\omega_0$ ) with each  $k$ ; only the phase, which is the angle the poles make with the positive real axis, differ. Therefore, a circle is formed.

44.

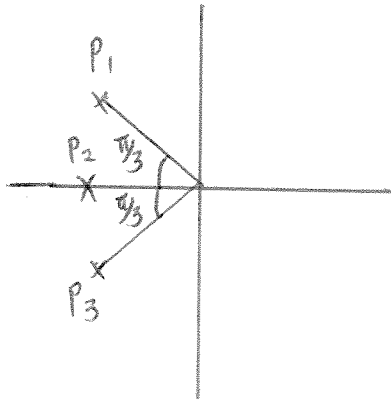

$$P_1 = 2\pi(1.45 \text{ MHz}) \left[ \cos\left(\frac{2\pi}{3}\right) + j \sin\left(\frac{2\pi}{3}\right) \right]$$

$$P_2 = (2\pi)(1.45 \text{ MHz})$$

$$P_3 = (2\pi)(1.45 \text{ MHz}) \left[ \cos\left(\frac{2\pi}{3}\right) - j \sin\left(\frac{2\pi}{3}\right) \right]$$

$$H(s) = \frac{(-P_1)(-P_3)}{(s-P_1)(s-P_3)} = \frac{[2\pi(1.45 \text{ MHz})]^2}{s^2 - [4\pi(1.45 \text{ MHz}) \cos\left(\frac{2\pi}{3}\right)]s + [2\pi(1.45 \text{ MHz})]^2}$$

KHN Low pass Transfer function:

$$\frac{\alpha s^2}{s^2 + \frac{\omega_n}{Q}s + \omega_n^2} \cdot \frac{1}{R_1 R_2 C_1 C_2 s^2} = \frac{\alpha / (R_1 R_2 C_1 C_2)}{s^2 + \frac{\omega_n}{Q}s + \omega_n^2}$$

$$\frac{\alpha}{R_1 R_2 C_1 C_2} = (2\pi \times 1.45 \times 10^6)^2, \quad \omega_n^2 = \frac{R_6}{R_3} \left( \frac{1}{R_1 R_2 C_1 C_2} \right) = [2\pi \times 1.45 \times 10^6]^2$$

$$\frac{\omega_n}{Q} = \frac{R_4}{R_4 + R_5} \left( \frac{1}{R_1 C_1} \right) = -(4\pi \times 1.45 \times 10^6 \times \cos\left(\frac{2\pi}{3}\right))$$

$$\frac{\alpha}{R_1 R_2 C_1 C_2} = \frac{R_5}{R_4 + R_5} \left( 1 + \frac{R_6}{R_3} \right) \left( \frac{1}{R_1 R_2 C_1 C_2} \right)$$

Let  $R_6 = R_3$ ,  $R_2 = 4R_1$ ,  $C_1 = C_2$

$$\omega_n^2 = \left( \frac{1}{4R_1 C_1} \right)^2 = (2\pi \times 1.45 \times 10^6)^2 \Rightarrow \frac{1}{2R_1 C_1} = 2\pi \times 1.45 \times 10^6$$

44.

Let  $R_1 = 5K \Rightarrow C_1 = 10.98pf$ ,  $R_2 = 20K$ ,  $C_2 = 10.98pf$

$$\frac{\omega_H}{Q} = \frac{R_4}{R_4 + R_5} \left( \frac{1}{R_1 C_1} \right) = 9110618.7$$

$$\Rightarrow \frac{R_4}{R_4 + R_5} = \frac{1}{2}$$


$$\frac{R_5}{R_4 + R_5} \left( 1 + \frac{R_6}{R_3} \right) \left( \frac{1}{R_1 R_2 C_1 C_2} \right) = \left( \frac{1}{2} \right) (2) (2\pi \times 1.45 \times 10^6)^2 = (2\pi \times 1.45 \times 10^6)^2$$

let  $R_5$  and  $R_4$  be  $1K$  apiece.

So  $R_5 = R_4 = R_6 = R_3 = 1K$

$R_1 = 5K$ ,  $R_2 = 20K$

$C_1 = C_2 = 10.98pf$

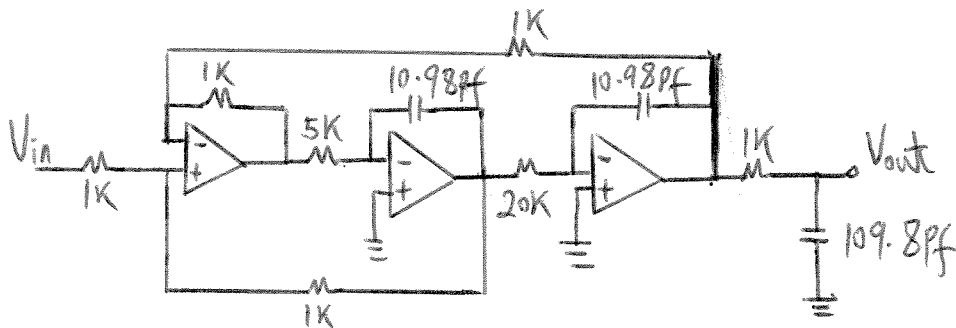

45.

ToW-Thomas Biquad

$$\frac{V_Y}{V_{in}} = \frac{R_3 R_4}{R_1} \left( \frac{1}{R_2 R_3 R_4 C_1 C_2 s^2 + R_2 R_4 C_2 s + R_3} \right)$$

$$\frac{V_Y}{V_{in}} = \frac{1 / (R_1 R_2 C_1 C_2)}{s^2 + 1 / (R_3 C_1) s + 1 / (R_2 R_4 C_1 C_2)}$$

$$\frac{V_Y}{V_{in}} = \frac{(2\pi \times 1.45 \times 10^6)^2}{s^2 - (4\pi \times 1.45 \times 10^6 \times \cos(29/3))s + (2\pi \times 1.45 \times 10^6)^2}$$


$$\frac{1}{R_1 R_2 C_1 C_2} = (2\pi \times 1.45 \times 10^6)^2, \quad \frac{1}{R_2 R_4 C_1 C_2} = (2\pi \times 1.45 \times 10^6)^2$$

$$\frac{1}{R_3 C_1} = 2\pi \times 1.45 \times 10^6$$

Let  $R_1 = R_2 = R_3 = R_4$ ,  $C_1 = C_2$

Let  $R_3 = 5K \Rightarrow C_1 = 21.95 \text{ pF}$

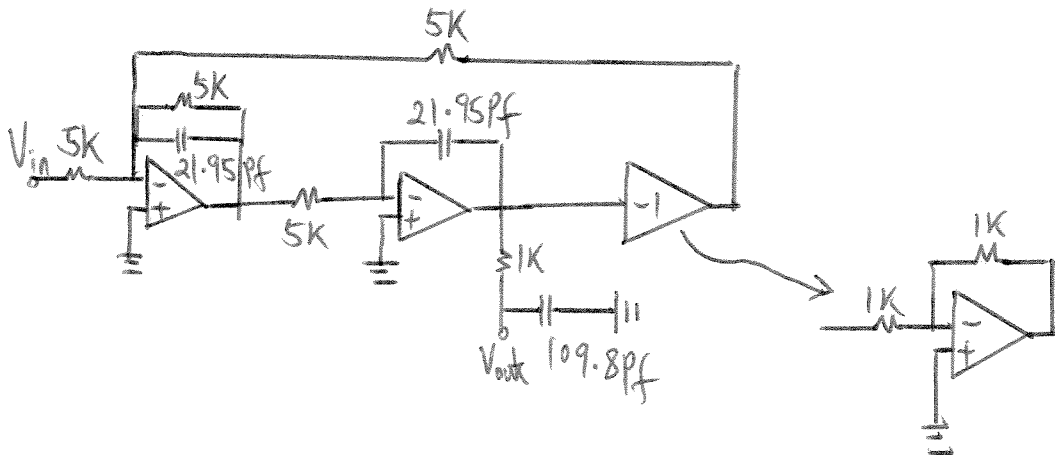So  $R_1 = R_2 = R_3 = R_4 = 5K$ , and  $C_1 = C_2 = 21.95 \text{ pF}$





46.

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 C_n^2\left(\frac{\omega}{\omega_0}\right)}} \quad n=4$$

$$\epsilon = 0.2$$

$$C_n\left(\frac{\omega}{\omega_0}\right) = \cos\left(n \cos^{-1}\frac{\omega}{\omega_0}\right) = \cos\left(4 \cos^{-1}\frac{\omega}{\omega_0}\right)$$

$$C_n^2\left(\frac{\omega}{\omega_0}\right) = \cos^2\left(n \cos^{-1}\frac{\omega}{\omega_0}\right) = \frac{1}{2} \left(1 + \cos\left(2n \cos^{-1}\frac{\omega}{\omega_0}\right)\right)$$


$$2n \cos^{-1}\frac{\omega}{\omega_0} = \pi, \quad n=4 \Rightarrow \frac{\omega}{\omega_0} = 0.924$$

$$2n \cos^{-1}\frac{\omega}{\omega_0} = 3\pi, \quad n=4 \Rightarrow \frac{\omega}{\omega_0} = 0.383$$


$$2n \cos^{-1}\frac{\omega}{\omega_0} = 0, \quad n=4 \Rightarrow \frac{\omega}{\omega_0} = 1$$

$$2n \cos^{-1}\frac{\omega}{\omega_0} = 2\pi, \quad n=4 \Rightarrow \frac{\omega}{\omega_0} = 0.707$$

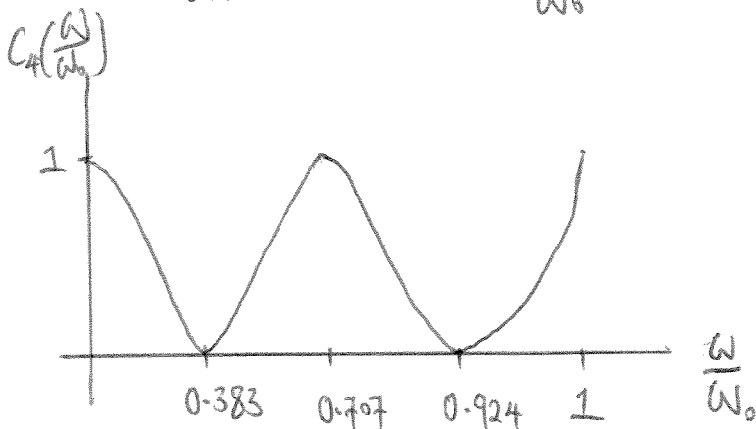
$$2n \cos^{-1}\frac{\omega}{\omega_0} = 4\pi, \quad n=4 \Rightarrow \frac{\omega}{\omega_0} = 0$$



46.

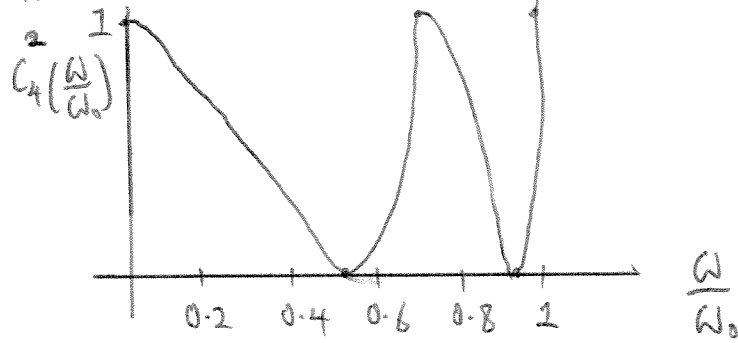
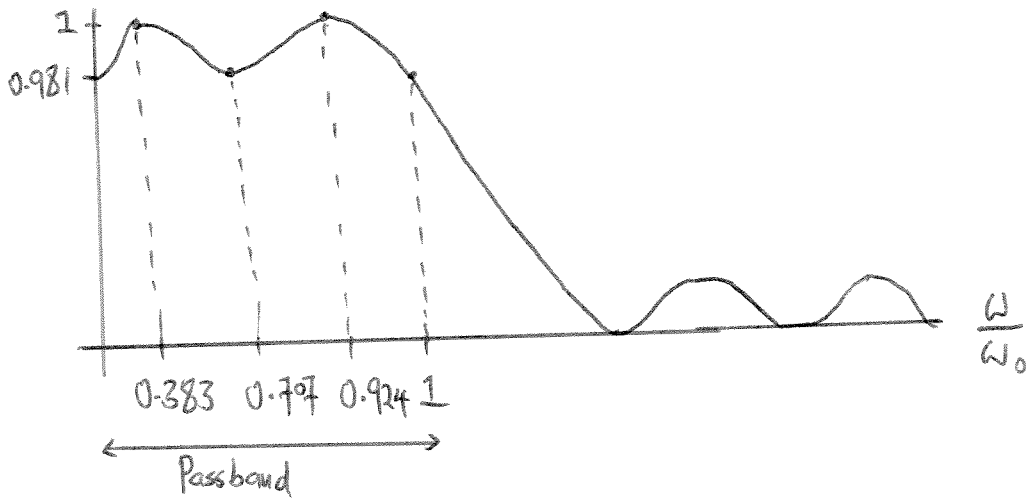
$$H(j\omega) = \frac{1}{\sqrt{1 + (0.2)^2 [C_4^2(\frac{\omega}{\omega_0})]}}$$



47. Chebyshev: 25 dB at 5 MHz.

$$n=5, \quad \omega_0 = 2 \text{ MHz}, \quad \frac{\omega}{\omega_0} = \frac{5}{2}$$

$$\frac{1}{\sqrt{1 + \epsilon^2 \cosh^2(n \cosh^{-1} \frac{5}{2})}} = -25 \text{ dB} = 0.056234$$

$$\Rightarrow \frac{1}{1 + \epsilon^2 (115939 \times 10^6)} = 0.0031622771$$

$$\Rightarrow \epsilon^2 = 1.9777 \times 10^{-4}$$

$\Rightarrow$  Minimum Ripple

$$\frac{1}{\sqrt{1 + (1.9777 \times 10^{-4})}} = 0.99990 = -8.6 \times 10^{-4} \text{ dB.}$$

$$48. \quad n=6$$

$$\cosh^2\left(6 \cos^{-1}\left(\frac{5}{2}\right)\right) = 36590401$$

$$\frac{1}{\sqrt{1 + \epsilon^2(36590401)}} = 0.056234$$

$$\epsilon^2 = 8.615 \times 10^{-6}$$

$$\text{Minimum Ripple} = \frac{1}{\sqrt{1 + 8.615 \times 10^{-6}}} = -374 \times 10^{-5} \text{ dB}$$

Smaller than when  $n=5$ .

$$49. \quad \epsilon = 0.509, \quad n = 4$$

$$P_{1,4} = -0.140\omega_0 \pm 0.983j\omega_0$$

$$P_{2,3} = -0.337\omega_0 \pm 0.407j\omega_0$$

$$H_{1,4}(s) = \frac{0.986\omega_0^2}{s^2 + 0.28\omega_0 s + 0.986\omega_0^2} = \frac{\alpha / (R_1 R_2 C_1 C_2)}{s^2 + \frac{\omega_n}{Q} s + \omega_n^2}$$

$$Q = 3.55$$

$$\omega_n = (2\pi)(4.965 \text{ MHz})$$

$$\omega_n^2 = [(2\pi)(4.965 \times 10^6)]^2 = \frac{R_6}{R_3} \left( \frac{1}{R_1 R_2 C_1 C_2} \right)$$

$$\frac{\omega_n}{Q} = (0.28)(5 \text{ MHz})(2\pi) = (1.4 \text{ MHz})(2\pi) = \frac{R_4}{R_4 + R_5} \left( \frac{1}{R_1 C_1} \right)$$

$$\frac{R_5}{R_4 + R_5} \left( 1 + \frac{R_6}{R_3} \right) \left( \frac{1}{R_1 R_2 C_1 C_2} \right) = \frac{R_6}{R_3} \left( \frac{1}{R_1 R_2 C_1 C_2} \right)$$

$$\Rightarrow \frac{R_5}{R_4 + R_5} \left( 1 + \frac{R_6}{R_3} \right) = \frac{R_6}{R_3}$$

$$\Rightarrow \frac{R_5}{R_4 + R_5} = \frac{\frac{R_6}{R_3}}{1 + \frac{R_6}{R_3}}$$

$$\Rightarrow 1 - \alpha = \frac{\frac{R_6}{R_3}}{1 + \frac{R_6}{R_3}}, \quad \alpha = \frac{R_4}{R_4 + R_5}$$

$$\Rightarrow \frac{R_6}{R_3} = \frac{1 - \alpha}{\alpha}$$

$$\text{Let } \alpha = 0.5 \Rightarrow \frac{R_6}{R_3} = 1$$

49.

$$\Rightarrow \omega_n^2 = \frac{R_6}{R_3} \left( \frac{1}{R_1 C_1 R_2 C_2} \right) = \frac{1}{R_1 C_1 R_2 C_2} \quad (*)$$

$$\text{Since } \frac{\omega_n}{\omega} = \alpha \left( \frac{1}{R_1 C_1} \right) = 14 \times 10^6 \times 2\pi, \quad \alpha = 0.5$$

$$\Rightarrow \frac{1}{R_1 C_1} = 1.76 \times 10^7 \quad (1)$$

Consider (\*)

$$\Rightarrow \frac{1}{R_2 C_2} = \omega_n^2 \cdot R_1 C_2 = 5.53 \times 10^7 \quad (2)$$

$R_6 = R_3 = R_5 = R_4 = 1k$ . According to (1), (2), choose

$$R_1 = 5k, \quad C_1 = 11.368p$$

$$R_2 = 5k, \quad C_2 = 3.62p$$

$$\text{For } H_{2,3}(s) = \frac{0.279\omega_0^2}{s^2 + 0.674\omega_0 s + 0.279\omega_0^2}$$

$$\omega_n = (2\pi) (2.64 \times 10^6)$$

$$\frac{\omega_n}{\omega} = (2\pi) (0.674 \times 5 \times 10^6) = (2\pi) (3.37 \times 10^6)$$

$$\text{Let } \alpha = 0.5$$

$$49. \frac{W_n}{Q} = (\alpha) \left( \frac{1}{R_1 C_1} \right)$$

$$\Rightarrow \frac{1}{R_1 C_1} = \frac{W_n}{Q} \cdot \frac{1}{\alpha} = 4.23 \times 10^7 \quad (3)$$


$$\frac{R_6}{R_3} = 1, \quad W_n^2 = \frac{R_6}{R_3} \left( \frac{1}{R_1 C_1 R_2 C_2} \right) = \frac{1}{R_1 C_1 R_2 C_2}$$

$$\Rightarrow \frac{1}{R_2 C_2} = W_n^2 \cdot R_1 C_1 = 6.50 \times 10^6 \quad (4)$$

Consider (3) (4), choose

$$R_1 = 5K, \quad C_1 = 4.72p; \quad R_2 = 5K, \quad C_2 = 30.78p$$

$$R_6 = R_3 = R_5 = R_4 = 1K.$$

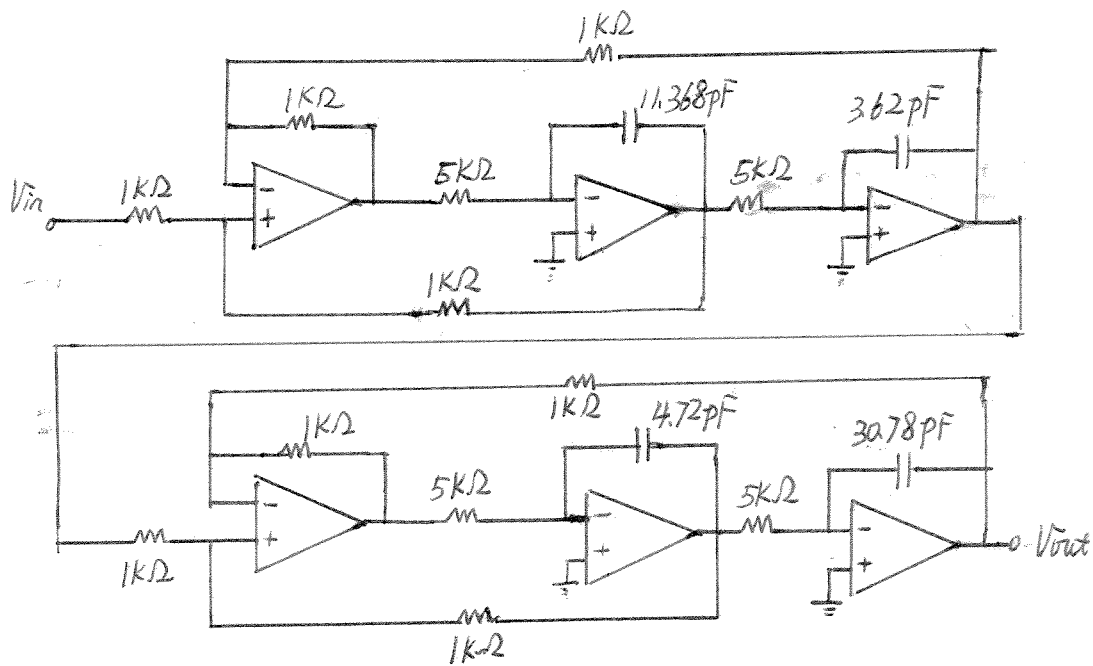

50. Tow Thomas

Low Pass Transfer Function

$$P_{1,4} = \frac{V_4}{V_{in}} = \frac{\frac{1}{R_1 R_2 C_1 C_2}}{s^2 + \frac{1}{R_3 C_1} s + \frac{1}{R_2 R_4 C_1 C_2}} = \frac{0.986 \omega_0^2}{s^2 + 0.28 \omega_0 s + 0.986 \omega_0^2}$$

$$\frac{1}{R_1 R_2 C_1 C_2} = \frac{1}{R_2 R_4 C_1 C_2} = [(12\pi)(4.965 \times 10^6)]^2 \quad (*)$$

$$\frac{1}{R_3 C_1} = 2\pi \times 1.4 \times 10^6$$

Let  $R_3 = 5K$ ,  $C_1 = 22.736P$

Let  $C_1 = C_2$ ,  $C_2 = 22.736P$

$$\left. \begin{aligned} R_1 = R_2 &\stackrel{+}{\Rightarrow} R_1 = R_2 = R_4 = 1.4K \\ R_3 = 5K, C_1 = C_2 = 22.736P \end{aligned} \right\} \text{for } P_{1,4}$$

$$P_{2,3} = \frac{0.279 \omega_0^2}{s^2 + 0.674 \omega_0 s + 0.279 \omega_0^2} = \frac{\frac{1}{R_1 R_2 C_1 C_2}}{s^2 + \frac{1}{R_3 C_1} s + \frac{1}{R_2 R_4 C_1 C_2}}$$

$$\frac{1}{R_1 R_2 C_1 C_2} = \frac{1}{R_2 R_4 C_1 C_2} = [(2\pi)(2.64 \times 10^6)]^2 \quad (*)$$


$$\frac{1}{R_3 C_1} = (2\pi)(3.37 \times 10^6)$$



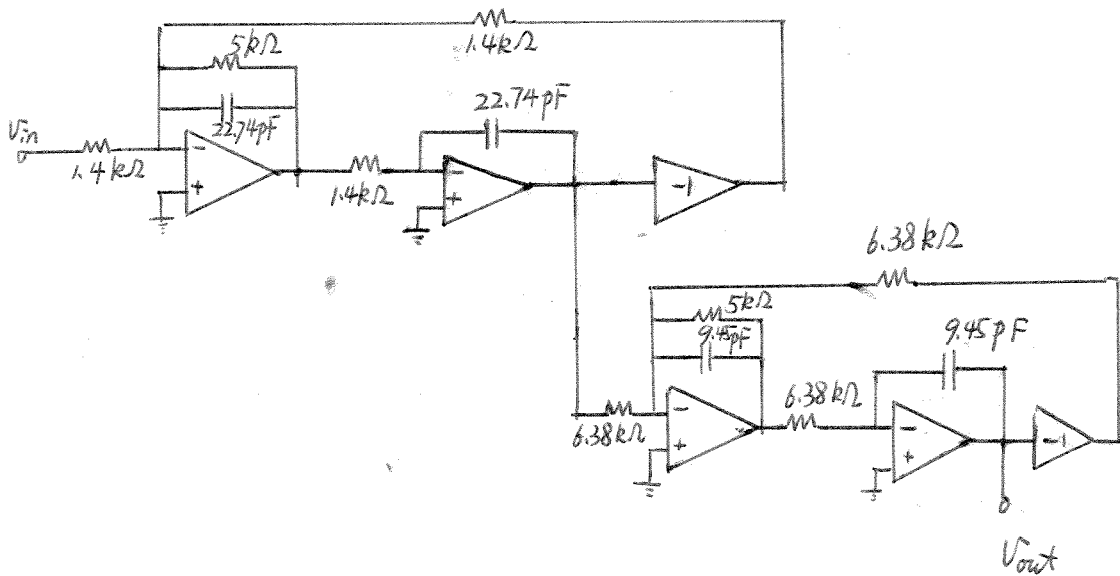
50. Let  $R_3 = 5K$ ,  $C_1 = 9.45 p$

Let  $C_1 = C_2 = 9.45 p$ ,  $R_1 = R_2 \xrightarrow{(*)} R_1 = R_2 = R_4 = 6.38K$ .

For  $P_{14}$  :  $\left\{ \begin{array}{l} R_1 = R_2 = R_4 = 6.38K, R_3 = 5K \\ C_1 = C_2 = 9.45 p. \end{array} \right.$




51.

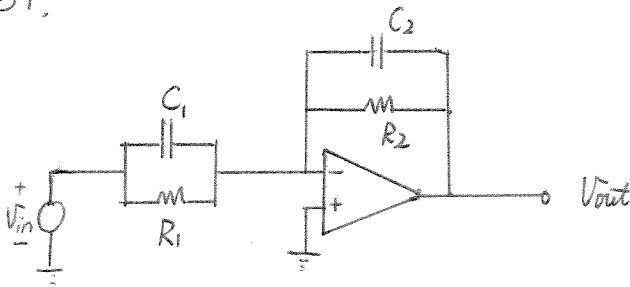

High pass,  $1\text{MHz} \Rightarrow 10\text{dB atten}$

$f > 5\text{MHz}$ , gain = 1

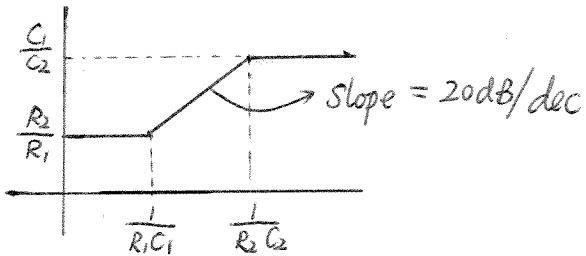

$$\frac{1}{R_2 C_2} = (5\text{MHz})(2\pi)$$

$$\text{Let } \frac{C_2}{C_1} = 1, \quad \frac{R_2}{R_1} = -10\text{dB} = 0.316$$


$$\text{So } \frac{1}{0.316} = 3.1623, \quad \frac{5\text{MHz}}{3.1623} = 1.58\text{MHz}$$

$$\Rightarrow \frac{1}{R_1 C_1} = (1.58\text{MHz})(2\pi)$$

$$\text{Choose } C_2 = 31.83\text{pF} \Rightarrow R_2 = 1\text{k}\Omega$$

$$C_1 = 31.83\text{pF} \Rightarrow R_1 = 3.16\text{k}\Omega$$

52.

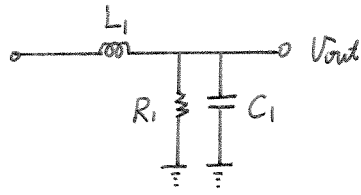

Peaking : 1dB

bandwidth: 100MHz

 $L_1 < 100\text{nH}$ 

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{L_1 C_1}}{s^2 + \frac{1}{R_1 C_1} s + \frac{1}{L_1 C_1}} = \frac{\gamma}{s^2 + \frac{\omega_n}{Q} s + \omega_n^2} \Big|_{s=j\omega} = \frac{\gamma}{(j\omega)^2 + \frac{\omega_n}{Q} (j\omega) + \omega_n^2}$$

$$H(j\omega) = \frac{\gamma}{(\omega_n^2 - \omega^2) + \frac{\omega_n}{Q} \omega j}$$

$$|H(j\omega)| = \frac{\gamma}{\sqrt{(\omega_n^2 - \omega^2)^2 + \left(\frac{\omega_n}{Q} \omega\right)^2}}$$

$$\text{At } \omega_1, |H(j\omega_1)| = \frac{\gamma}{\sqrt{(\omega_n^2 - \omega_1^2)^2 + \left(\frac{\omega_n}{Q} \omega_1\right)^2}} = \frac{\gamma}{\omega_n^2 \sqrt{2}}$$

$$\Rightarrow \sqrt{\frac{(\omega_n^2 - \omega_1^2)^2 + \left(\frac{\omega_n}{Q} \omega_1\right)^2}{\omega_n^4}} = \sqrt{2}$$

$$\Rightarrow (\omega_n^2 - \omega_1^2)^2 + \left(\frac{\omega_n}{Q} \omega_1\right)^2 = 2\omega_n^4 \quad (*)$$

$$\frac{Q}{\sqrt{1 - (4Q^2)^{-1}}} = 1.1 \Rightarrow Q = 0.9258, 0.5941 (< \frac{1}{\sqrt{2}}, \text{ can't produce peaking})$$

So  $Q = 0.9258$ .Solve (\*) gives  $\omega = \sqrt{1.5} \omega_n$ .

$$\omega = \sqrt{1.5} \frac{1}{\sqrt{L_1 C_1}} = (127) (100 \times 10^6) \quad (1)$$


52.

$$\frac{W_n}{Q} = \frac{1}{R_1 C_1} \Rightarrow Q = R_1 C_1 \frac{1}{\sqrt{4C_1}} = R_1 \sqrt{\frac{C_1}{4}} = 0.9258 \quad (2)$$

$$\text{Let } L_1 = 90 \text{ nH} \stackrel{(1)}{\Rightarrow} C_1 = 42.22 \text{ pF} \stackrel{(2)}{\Rightarrow} R_1 = 42.74 \Omega.$$

53.  $\omega_n = (2\pi)(50\text{MHz})$ ,  $Q = 1.5$ , Low frequency gain = 2.

$C = 10\text{pF}$  to  $100\text{pF}$ .

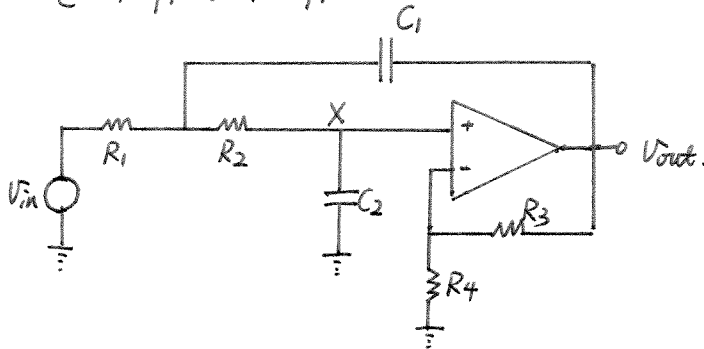

$$\frac{V_{out}}{V_{in}} = \frac{1 + \frac{R_3}{R_4}}{R_1 R_2 C_1 C_2 S^2 + (R_1 C_2 + R_2 C_2 - R_1 \frac{R_3}{R_4} C_1) S + 1}$$

$$= \frac{(1 + \frac{R_3}{R_4}) / (R_1 R_2 C_1 C_2)}{S^2 + \frac{(R_1 C_2 + R_2 C_2 - \frac{R_1 R_3}{R_4} C_1) S + \frac{1}{R_1 R_2 C_1 C_2}}{R_1 R_2 C_1 C_2}}$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad \frac{\omega_n}{Q} = \frac{R_1 C_2 + R_2 C_2 - R_1 \frac{R_3}{R_4} C_1}{R_1 R_2 C_1 C_2}$$

Low frequency gain  $(1 + \frac{R_3}{R_4}) = 2$ , Let  $\frac{R_3}{R_4} = 1$ .

$$\frac{1}{\sqrt{R_1 R_2 C_1 C_2}} = \omega_n = (2\pi)(50 \times 10^6) \quad \textcircled{1}$$

$$R_1 C_2 + R_2 C_2 - R_1 C_1 = \frac{\omega_n}{Q} (R_1 R_2 C_1 C_2) = \frac{1}{(1.5)(2\pi)(50 \times 10^6)} \quad \textcircled{2}$$

Let  $C_1 = C_2 = 10\text{pF}$

$$\textcircled{2} \Rightarrow R_2 = \frac{1}{(1.5)(2\pi)(50 \times 10^6)} \cdot \frac{1}{C_2} = 212.2 (\Omega)$$

$$\textcircled{1} \Rightarrow R_1 = \sqrt{[(2\pi)^2 (50 \times 10^6)^2 \cdot R_2 C_1 C_2]} = 477.5 (\Omega)$$

Let  $R_3 = R_4 = 1\text{k}\Omega$ .

54.  $W_{3dB} = (30 \times 10^6) (2Z)$ , gain = 2, sensitivities no greater than 1.

$$H(s) = \frac{K W_n^2}{s^2 + \frac{W_n}{Q} s + W_n^2}, \quad s = j\omega \Rightarrow$$

$$H(j\omega) = \frac{K W_n^2}{W_n^2 - \omega^2 + \frac{W_n}{Q} \omega j}$$

$$|H(j\omega)| = \frac{K W_n^2}{\sqrt{(W_n^2 - \omega^2)^2 + \left(\frac{W_n}{Q} \omega\right)^2}}$$

$$|H(j\omega)| = \frac{K}{\sqrt{2}} \Rightarrow \frac{W_n^2}{\sqrt{(W_n^2 - \omega^2)^2 + \left(\frac{W_n}{Q} \omega\right)^2}} = \frac{1}{\sqrt{2}}$$

$$\Rightarrow (W_n^2 - \omega^2)^2 + \left(\frac{W_n}{Q} \omega\right)^2 = 2W_n^4$$

$$\Rightarrow W_n^4 \left(1 - \frac{\omega^2}{W_n^2}\right)^2 + W_n^4 \left[\left(\frac{1}{Q}\right)^2 \cdot \left(\frac{\omega}{W_n}\right)^2\right] = 2W_n^4$$

$$\Rightarrow \left[1 - \left(\frac{\omega}{W_n}\right)^2\right]^2 + \left(\frac{1}{Q}\right)^2 \left(\frac{\omega}{W_n}\right)^2 = 2$$

$$\Rightarrow \left(\frac{\omega}{W_n}\right)^4 + \left[\left(\frac{1}{Q}\right)^2 - 2\right] \left(\frac{\omega}{W_n}\right)^2 - 1 = 0$$

$$S_{R_2, C_1, C_2, R_1}^{W_n} = -\frac{1}{2} \quad (\text{sensitivities of } W_n \text{ all } < 1)$$

$$S_{R_1}^Q = -S_{R_2}^Q = -\frac{1}{2} + Q \sqrt{\frac{R_2 C_2}{R_1 C_1}}$$

$$S_{C_1}^Q = -S_{C_2}^Q = -\frac{1}{2} + Q \left( \sqrt{\frac{R_1 C_2}{R_2 C_1}} + \sqrt{\frac{R_2 C_2}{R_1 C_1}} \right) = \frac{1}{2} + Q \sqrt{\frac{R_1 C_1}{R_2 C_2}}$$

$$S_K^Q = QK \sqrt{\frac{R_1 C_1}{R_2 C_2}} = 2Q \sqrt{\frac{R_1 C_1}{R_2 C_2}}$$

Let  $\sqrt{\frac{R_1 C_2}{R_2 C_1}} = 1$ , and  $Q = \frac{1}{2}$ ,

$$S_K^Q = 2 \cdot \left(\frac{1}{2}\right) = 1, \quad S_{C_1}^Q = \frac{1}{2} + \frac{1}{2} = 1$$

$$S_{C_2}^Q = -1, \quad S_{R_1}^Q = -\frac{1}{2} + \frac{1}{2} = 0, \quad S_{R_2}^Q = 0$$

Since  $Q = \frac{1}{2}$ ,

$$\left(\frac{\omega}{\omega_n}\right)^4 + 2 \left(\frac{\omega}{\omega_n}\right)^2 - 1 = 0$$

$$\Rightarrow \left(\frac{\omega}{\omega_n}\right)^2 = 0.4142$$

$$\Rightarrow \omega = \sqrt{0.4142} \omega_n$$

Since  $R_1 C_1 = R_2 C_2$ ,

$$\omega_n = \frac{1}{\sqrt{(RC)^2}} = \frac{1}{R_1 C_1}$$

$$\Rightarrow \sqrt{0.4142} \omega_n = \frac{\sqrt{0.4142}}{R_1 C_1} = (2\pi)(30 \times 10^6) \quad \textcircled{1}$$

$$\text{Also } \frac{1}{Q\omega_n} = R_1 C_2 + R_2 C_2 - R_1 C_1 = R_1 C_2 \quad \textcircled{2}$$

$$\Rightarrow \frac{R_1 C_1}{R_1 C_2} = \frac{\frac{1}{\omega_n}}{\frac{1}{Q\omega_n}} = Q = \frac{1}{2}$$


$$\Rightarrow \frac{C_1}{C_2} = \frac{1}{2}$$

$$\text{Let } R_1 = 1K\Omega \xrightarrow{\textcircled{1}} C_1 = \frac{\sqrt{0.4142}}{(2\pi)(30 \times 10^6) \cdot R_1} = 3.4 \text{ pF}$$

$$\Rightarrow C_2 = 2C_1 = 6.8 \text{ pF}$$


$$\Rightarrow R_2 = R_1 \frac{C_1}{C_2} = 500\Omega$$

And as before,  $R_3 = R_4 = 1K\Omega$ .

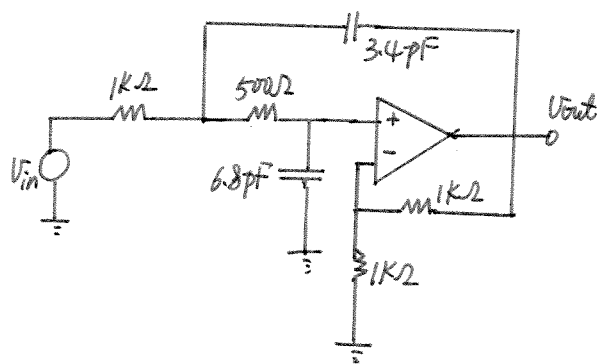

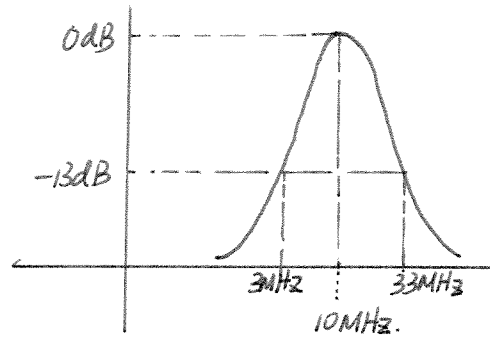55. 10MHz, Gain=1 (peak),  $R_6=R_3$ , -13dB @ 3MHz, 33MHz.

$$\frac{V_x}{V_{in}} = \frac{\alpha S^2}{S^2 + \frac{W_n}{Q} S + W_n^2} \cdot \frac{-1}{R_1 C_1}$$



$$1 = \left(\frac{\alpha}{R_1 C_1}\right) \cdot \frac{Q}{W_n}, \quad \alpha = \frac{R_5}{R_4 + R_5} \left(1 + \frac{R_6}{R_3}\right), \quad \frac{W_n}{Q} = \frac{R_4}{R_4 + R_5} \cdot \frac{1}{R_1 C_1}$$

$$\text{since } R_6 = R_3, \quad \alpha = 2 \frac{R_5}{R_4 + R_5} \Rightarrow \frac{\alpha}{2} = \frac{R_5}{R_4 + R_5}$$

$$\Rightarrow \frac{R_4}{R_4 + R_5} = 1 - \frac{\alpha}{2} \Rightarrow \frac{Q}{W_n} = \frac{R_1 C_1}{1 - \frac{\alpha}{2}}$$

$$\Rightarrow \left(\frac{\alpha}{R_1 C_1}\right) \cdot \left(\frac{R_1 C_1}{1 - \frac{\alpha}{2}}\right) = 1 \Rightarrow \alpha = 1 - \frac{\alpha}{2}$$

$$\Rightarrow \alpha = \frac{2}{3}, \quad \frac{R_5}{R_4 + R_5} = \frac{1}{3}$$

$$\Rightarrow R_5 = \frac{1}{2} R_4$$

$$\left. \begin{array}{l} \frac{W_n}{Q} = \left(\frac{2}{3}\right) \left(\frac{1}{R_1 C_1}\right) \\ W_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \end{array} \right\} \Rightarrow \frac{3}{2} \frac{R_1 C_1}{\sqrt{R_1 R_2 C_1 C_2}} = Q$$

$$\Rightarrow \frac{3}{2} \sqrt{\frac{R_1 C_1}{R_2 C_2}} = Q$$

$$\text{Let } R_1 C_1 = R_2 C_2 \Rightarrow Q = \frac{3}{2}, \quad W_n = \frac{1}{R_1 C_1}$$



$$H(j\omega) = \frac{\frac{2}{3}\omega^2}{\frac{\omega}{\omega_n} \sqrt{(1 - \frac{\omega^2}{\omega_n^2})^2 + (\frac{2}{3}\frac{\omega}{\omega_n})^2}} = \frac{\frac{2}{3}\omega^2}{\frac{\omega}{\omega_n} \sqrt{\omega_n^4 - \frac{14}{9}(\omega_n\omega)^2 + \omega^4}}$$

$$H(j\omega) = 1$$

$$\Rightarrow \frac{4}{9}\omega^2 = \omega_n^2 - \frac{14}{9}\omega^2 + \frac{\omega^4}{\omega_n^2}$$

$$\Rightarrow \omega_n^4 - 2\omega^2\omega_n^2 + \omega^4 = 0$$

$$\Rightarrow \omega_n^2 = \omega^2 = [(2\pi)(10\text{MHz})]^2$$


$$\text{As derived, } \omega_n = \frac{1}{R_1 C_1}$$

$$\text{Let } R_1 = 5\text{k}\Omega \Rightarrow C_1 = 3.183\text{pF.}$$


$$\text{Let } R_2 = R_1 = 5\text{k}\Omega \Rightarrow C_2 = C_1 = 3.183\text{pF}$$

$$\text{Let } R_4 = 5\text{k}\Omega \Rightarrow R_5 = \frac{1}{2}R_4 = 2.5\text{k}\Omega.$$
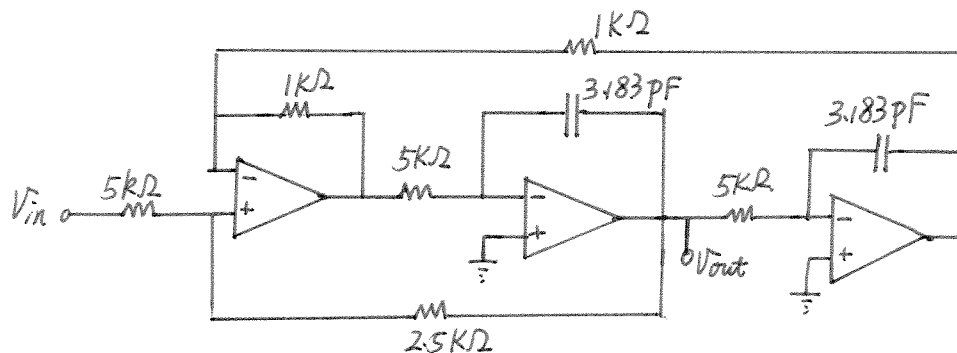
$$\text{Let } R_3 = R_6 = 1\text{k}\Omega.$$



56.

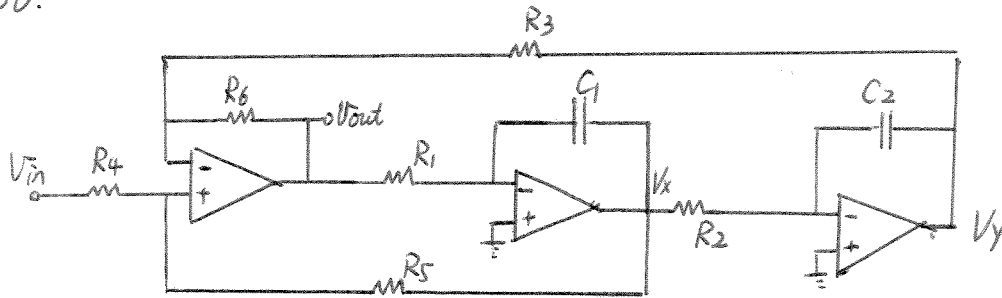

Low pass, 
$$\frac{V_y}{V_{in}} = \frac{\alpha S^2}{S^2 + \frac{W_n}{Q} S + W_n^2} \cdot \frac{1}{R_1 R_2 C_1 C_2 S^2}$$

$$= \frac{\alpha}{(S^2 + \frac{W_n}{Q} S + W_n^2) (R_1 R_2 C_1 C_2)}$$

$$H(S) = \frac{\alpha / (R_1 R_2 C_1 C_2)}{S^2 + \frac{W_n}{Q} S + W_n^2}$$

$$H(jW) = \frac{\alpha / (R_1 R_2 C_1 C_2)}{(W_n^2 - W^2) + j \frac{W_n}{Q} W}$$

$$|H(jW)| = \frac{\alpha / (R_1 R_2 C_1 C_2)}{\sqrt{(W_n^2 - W^2)^2 + (\frac{W_n W}{Q})^2}}$$

$$|H(W_{3dB})| = \frac{\alpha / (R_1 R_2 C_1 C_2)}{\sqrt{(W_n^2 - W_{3dB}^2)^2 + (\frac{W_n W_{3dB}}{Q})^2}} = \frac{\alpha}{W_n^2 (R_1 R_2 C_1 C_2) \sqrt{2}}$$

$$\Rightarrow \frac{\sqrt{(W_n^2 - W_{3dB}^2)^2 + (\frac{W_n W_{3dB}}{Q})^2}}{W_n^2} = \sqrt{2}$$

$$\Rightarrow 1 - 2 \left( \frac{W_{3dB}}{W_n} \right)^2 + \left( \frac{W_{3dB}}{W_n} \right)^4 + \frac{1}{Q^2} \left( \frac{W_{3dB}}{W_n} \right)^2 = 2$$

$$\Rightarrow \left(\frac{\omega_{3dB}}{\omega_n}\right)^4 + \left(\frac{1}{Q^2} - 2\right) \left(\frac{\omega_{3dB}}{\omega_n}\right)^2 - 1 = 0$$

$$Q = 1.5 \Rightarrow \left(\frac{\omega_{3dB}}{\omega_n}\right)^4 - 1.556 \left(\frac{\omega_{3dB}}{\omega_n}\right)^2 - 1 = 0$$

$$\Rightarrow \left(\frac{\omega_{3dB}}{\omega_n}\right)^2 = 2.0446, -0.4891 \text{ (impossible)}$$

$$\Rightarrow \omega_{3dB} = 1.43 \omega_n$$

$\Rightarrow$  Low pass corner = 14.3 MHz.

High pass:

$$\frac{V_{out}}{V_{in}}(s) = \frac{\alpha s^2}{s^2 + \frac{\omega_n}{Q}s + \omega_n^2}$$

$$|H(j\omega)| = \frac{\alpha \omega^2}{\sqrt{(\omega_n^2 - \omega^2)^2 + \left(\frac{\omega \omega_n}{Q}\right)^2}}$$

$$|H(j\omega_{3dB})| = \frac{\alpha \omega_{3dB}^2}{\sqrt{(\omega_n^2 - \omega_{3dB}^2)^2 + \left(\frac{\omega_{3dB} \omega_n}{Q}\right)^2}} = \frac{\alpha}{\sqrt{2}}$$


$$\Rightarrow \left(\frac{\omega_n}{\omega_{3dB}}\right)^4 + \left(\frac{1}{Q^2} - 2\right) \left(\frac{\omega_n}{\omega_{3dB}}\right)^2 - 1 = 0$$

Since  $Q = 1.5$

$$\Rightarrow \left(\frac{\omega_n}{\omega_{3dB}}\right)^2 = 2.0446 \Rightarrow \omega_{3dB} = \frac{\omega_n}{1.43}$$

$\Rightarrow \omega_{3dB} = 7 \text{ MHz. (high pass corner)}$

57.

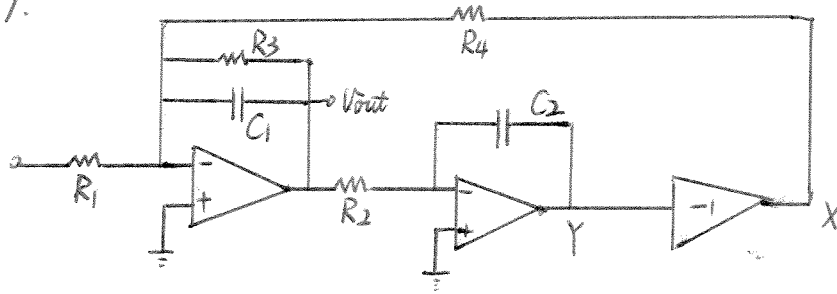

$$\omega_n = 10 \text{ MHz},$$

$$-13 \text{ dB} = 3 \text{ MHz},$$

$$33 \text{ MHz}.$$

$$\frac{V_{out}}{V_{in}} = - \frac{R_2 R_3 R_4}{R_1} \left( \frac{C_2 S}{R_2 R_3 R_4 C_1 C_2 S^2 + R_2 R_4 C_2 S + R_3} \right)$$

Same as in #55,  $Q = \frac{10}{6.684} = 1.5.$

$$\frac{V_{out}}{V_{in}} = - \frac{\frac{1}{R C_1} S}{S^2 + \frac{1}{R_3 C_1} S + \frac{1}{R_2 R_4 C_1 C_2}}$$

$$\frac{\omega_n}{Q} = \frac{1}{R_3 C_1}, \quad \omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}$$

$$Q = \frac{R_3 C_1}{\sqrt{R_2 R_4 C_1 C_2}} = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}$$

$$\frac{V_{out}}{V_{in}} = \frac{-\beta S}{S^2 + \frac{\omega_n}{Q} S + \omega_n^2},$$

At  $\omega = \omega_n \Rightarrow |H(j\omega_n)| = 1 = \frac{\beta Q}{\omega_n}.$

$$\frac{\beta Q}{\omega_n} = \left( \frac{1}{R C_1} \right) (R_3 C_1) = \frac{R_3}{R_1} = 1$$

$$Q = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}} = 15, \quad W_n = \frac{1}{\sqrt{R_2 R_4 C_2 C_1}} = (10 \times 10^6)(2\pi)$$

$$\text{Let } R_2 = R_4 = 1 \text{ k}\Omega.$$

$$\frac{1}{\sqrt{10^6 \times C_1 C_2}} = (10 \times 10^6)(2\pi) \Rightarrow C_1 C_2 = 2.533 \times 10^{-22}$$

$$\text{Let } C_1 = C_2 = 15.9 \text{ pF}$$

$$R_3 \sqrt{\frac{1}{10000 \times 10000}} = 15.$$

$$\Rightarrow R_3 = 1.5 \text{ k}\Omega = R_1$$


$$\text{So : } R_1 = 1.5 \text{ k}\Omega, R_2 = 1 \text{ k}\Omega, R_3 = 1.5 \text{ k}\Omega, R_4 = 1 \text{ k}\Omega.$$

$$C_1 = C_2 = 15.9 \text{ pF}.$$

58. Peaking : 1dB @ 7MHz.

Corner : 3.69MHz

-13.6dB @ 2MHz.

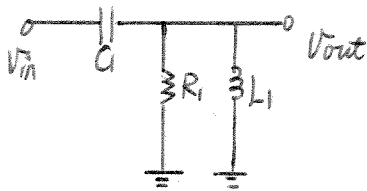

$$\frac{V_{out}}{V_{in}} = \frac{S^2}{S^2 + \frac{1}{R_1 C_1} S + \frac{1}{L_1 C_1}}$$

Peaking 1dB  $\Rightarrow Q = 0.926$ .

$$\frac{\omega_n}{\sqrt{1 - 1/(2Q^2)}} = (2\pi)(7\text{MHz}) \Rightarrow \omega_n = (2\pi)(4.52\text{MHz})$$

$$\frac{\omega_n}{Q} = \frac{(2\pi)(4.52\text{MHz})}{0.926} = (2\pi)(4.88\text{MHz}) = \frac{1}{R_1 C_1}$$

$$\omega_n^2 = [(2\pi)(4.52\text{MHz})]^2 = \frac{1}{L_1 C_1}$$

Let  $C_1 = 100\text{pF}$ ,  $L_1 = 12.4\mu\text{H}$ ,  $R_1 = 326.1\Omega$ .

With simulated inductor


$$Z_{in} = \left( \frac{Z_1 Z_3}{Z_2 Z_4} \right) Z_5 = R_Y R_X C_S$$

Let  $Z_1 = Z_3 = Z_4 = R_Y$ ,  $Z_5 = R_X$ ,  $Z_2 = C_S^{-1}$

Let  $R_Y = 1\text{k}\Omega$ ,  $R_X = 5\text{k}\Omega$ .

$$12.4 \times 10^{-6} = (1000)(5000) C$$

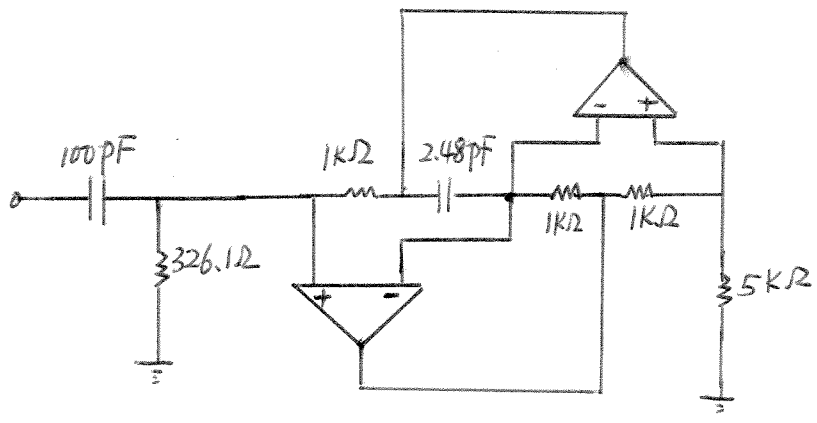$\Rightarrow C = 2.48\text{pF}$  to simulate an  $L$  of  $12.4\mu\text{H}$ .



59. Corner @ 16.38 MHz, Peaking 0.5 dB @ 8 MHz.

5.9 dB  $\approx$  6 dB attenuation @ 20 MHz.

$$\frac{V_{out}}{V_{in}} = \frac{1}{R_1 R_x C^2 S^2 + R_1 C S + 1} = \frac{1 / (R_1 R_x C^2)}{S^2 + \frac{S}{R_x C} + \frac{1}{R_1 R_x C^2}}$$

$$0.5 \text{ dB} \Leftrightarrow 1.05292$$

$$\frac{Q}{\sqrt{1 - \frac{1}{4Q^2}}} = 1.05292 \Rightarrow Q = 0.8636$$


$$\omega_n \sqrt{1 - \frac{1}{2Q^2}} = (2\pi)(8 \times 10^6)$$

$$\Rightarrow \omega_n = (2\pi)(13.934 \times 10^6)$$

$$\frac{1}{R_1 R_x C^2} = \omega_n^2, \quad \frac{1}{R_x C} = \frac{\omega_n}{Q} = (2\pi)(16.134 \times 10^6)$$

$$\Rightarrow \frac{1}{R_x C} = 7.56 \times 10^7$$

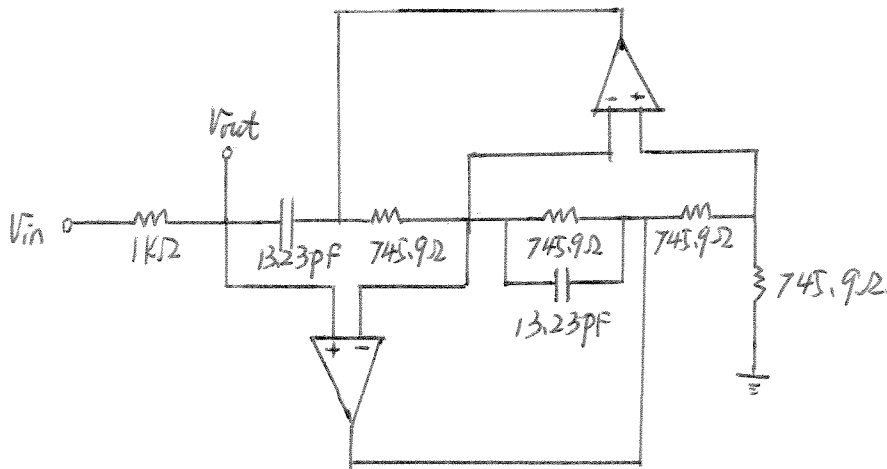Let  $R_1 = 1 \text{ k}\Omega$ ,  $C = 13.23 \text{ pF}$ ,  $R_x = 745.9 \Omega$ .





60. Butterworth

a) Passband 0.5 dB @ 1 MHz,  $-0.5 \text{ dB} \Leftrightarrow 0.944$

Attenuation 12 dB @ 2.5 MHz,  $-12 \text{ dB} \Leftrightarrow 0.2512$

$$|H(j\omega)|_{1\text{MHz}}^2 = \frac{1}{1 + \left[\frac{(2\pi)(10^6)}{W_0}\right]^{2n}} = 0.944^2 \quad (1)$$

$$|H(j\omega)|_{2.5\text{MHz}}^2 = \frac{1}{1 + \left[\frac{2\pi \times 2.5 \times 10^6}{W_0}\right]^{2n}} = 0.2512^2 \quad (2)$$

$$(1) \Rightarrow 1 = (0.944)^2 \left[ \left( \frac{2\pi \times 10^6}{W_0} \right)^{2n} + 1 \right]$$

$$\Rightarrow W_0^{2n} = 8.186 \times (2\pi \times 10^6)^{2n} \quad (3)$$

$$(2) \Rightarrow 1 = (0.2512)^2 \left[ \frac{(2\pi \times 2.5 \times 10^6)^{2n}}{8.186 \times (2\pi \times 10^6)^{2n}} + 1 \right]$$

$$\Rightarrow n = 2.62$$

So choose  $n = 3$ .  $(3) \Rightarrow W_0 = 2\pi \times 1.42 \text{ MHz}$ .

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left( \frac{\omega}{2\pi \times 1.42 \times 10^6} \right)^6}}$$

b). Passband: 0.1 dB @ 1 MHz

$$\frac{1}{1 + \left(\frac{2\pi \times 10^6}{\omega_0}\right)^{2n}} = (0.98855)^2 \quad (1)$$

Stopband attenuation: 12 dB @ 2.5 MHz

$$\frac{1}{1 + \left(\frac{2\pi \times 2.5 \times 10^6}{\omega_0}\right)^{2n}} = (0.2512)^2 \quad (2)$$

$$(1) \Rightarrow \omega_0^{2n} = 42.931 \times (2\pi \times 10^6)^{2n}$$

$$(2) \Rightarrow n = 3.52$$

$$\text{Choose } n = 4 \quad (3) \Rightarrow \omega_0 = 2\pi \times 1.6 \text{ MHz.}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{2\pi \times 1.6 \times 10^6}\right)^8}}$$

$$c). \text{ Passband } 1 \text{ dB @ } 1 \text{ MHz} \Rightarrow \frac{1}{1 + \left(\frac{2\pi \times 10^6}{\omega_0}\right)^{2n}} = (0.90)^2 \quad (4)$$

$$\text{Attenuation } 18 \text{ dB @ } 2.5 \text{ MHz} \Rightarrow \frac{1}{1 + \left(\frac{2\pi \times 2.5 \times 10^6}{\omega_0}\right)^{2n}} = (0.259)^2 \quad (5)$$

$$(4) \Rightarrow \omega_0^{2n} = 4.263 \times (2\pi \times 10^6)^{2n} \quad (6)$$

$$(5) \Rightarrow n = 3.0$$

$$\text{Choose } n = 3 \quad (6) \Rightarrow \omega_0 = 2\pi \times 1.27 \text{ MHz}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{2\pi \times 1.27 \times 10^6}\right)^6}}$$

$$d) \text{ Passband: } 0.5\text{dB @ } 1\text{MHz} \Rightarrow \frac{1}{1 + \left(\frac{2\pi \times 10^6}{W_0}\right)^{2n}} = 0.944^2 \quad (1)$$

$$\text{Attenuation: } 18\text{dB @ } 2.5\text{MHz} \Rightarrow \frac{1}{1 + \left(\frac{2\pi \times 2.5 \times 10^6}{W_0}\right)^{2n}} = 0.1259^2 \quad (2)$$

$$(1) \Rightarrow W_0^{2n} = 8.186 \times (2\pi \times 10^6)^{2n} \quad (3)$$

$$(2) \Rightarrow n = 3.4$$

$$\text{Choose } n = 4 \Rightarrow W_0 = 2\pi \times 1.3\text{MHz}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{2\pi \times 1.3 \times 10^6}\right)^8}}$$

Chebyshev

$$a) \text{ Passband } 0.5\text{dB @ } 1\text{MHz} \Rightarrow 0.5 = 20 \log(\sqrt{1 + \epsilon^2})$$

$$\Rightarrow \epsilon = 0.3493, W_0 = 1\text{MHz}$$

$$\text{Attenuation } 12\text{dB @ } 2.5\text{MHz}$$

$$\Rightarrow \frac{1}{\sqrt{1 + \epsilon^2 \cosh^2 \left[ n \cosh^{-1} \left( \frac{\omega}{W_0} \right) \right]}} = 0.2512, \text{ when } \omega = 2.5 \times 10^6 \times 2\pi$$

Since  $\omega, W_0, \epsilon$ , known

$$\Rightarrow n = 1.9733$$

$$\text{Choose } n = 2, |H(j\omega)| = \frac{1}{\sqrt{1 + 0.3493^2 \left( 2 \frac{\omega}{W_0} \right)^2}}, W_0 = 2\pi \times 1\text{MHz}$$

b). Passband 0.1 dB @ 1 MHz,  $\omega_0 = 1 \text{ MHz}$

$$\Rightarrow 0.1 = 20 \log(\sqrt{1+\epsilon^2}) \Rightarrow \epsilon = 0.1526.$$

Attenuation 12 dB @ 25 MHz

$$\Rightarrow \frac{1}{1 + 0.1526^2 \cosh^2[n \cosh^{-1}(25)]} = 0.2512^2$$

$$\Rightarrow n = 2.5$$

$$\text{Choose } n=3, |H(j\omega)| = \frac{1}{\sqrt{1 + 0.1526^2 \left(3^2 \left(\frac{\omega}{\omega_0}\right)^2\right)}}, \omega_0 = (2\pi)(1 \text{ MHz})$$

c). Passband 1 dB @ 1 MHz,  $\omega_0 = 1 \text{ MHz}$

$$\Rightarrow 1 = 20 \log \sqrt{1+\epsilon^2} \Rightarrow \epsilon = 0.5089.$$

Attenuation 18 dB @ 25 MHz

$$\Rightarrow \frac{1}{1 + 0.5089^2 \cosh^2[n \cosh^{-1}(25)]} = 0.1259^2 \Rightarrow n = 2.19$$

$$\text{Choose } n=3, |H(j\omega)| = \frac{1}{\sqrt{1 + 0.5089^2 \left(3^2 \left(\frac{\omega}{\omega_0}\right)^2\right)}}, \omega_0 = (2\pi)(1 \text{ MHz})$$

d). Passband 0.5 dB @ 1 MHz  $\Rightarrow \epsilon = 0.3493$

Attenuation 18 dB @ 25 MHz

$$\Rightarrow \frac{1}{1 + 0.3493^2 \cosh^2[n \cosh^{-1}(25)]} = 0.1259^2 \Rightarrow n = 2.43$$

$$\text{Choose } n=3, |H(j\omega)| = \frac{1}{\sqrt{1 + 0.3493^2 \left(3^2 \left(\frac{\omega}{\omega_0}\right)^2\right)}}, \omega_0 = (2\pi)(1 \text{ MHz})$$

61. a) Butterworth in Sallen and Key

$$\pi = 3, \omega_0 = (2\pi)(1.42\text{MHz})$$

$$P_k = \omega_0 \cdot \exp\left(\frac{j\pi}{2}\right) \exp\left(j\frac{2k-1}{2n}\pi\right), \quad k=1,2,3.$$

$$P_1 = \omega_0 \exp\left(j\frac{2\pi}{3}\right) = (2\pi)(1.42\text{MHz}) \times \left(\cos\frac{2\pi}{3} + j\sin\frac{2\pi}{3}\right).$$

$$P_2 = \omega_0 \exp(j\pi) = -(2\pi)(1.42\text{MHz})$$

$$P_3 = \omega_0 \exp\left(j\frac{4\pi}{3}\right) = (2\pi)(1.42\text{MHz}) \times \left(\cos\frac{2\pi}{3} - j\sin\frac{2\pi}{3}\right)$$

$$H_{p,1/3}(s) = \frac{(-P_1)(-P_3)}{(s-P_1)(s-P_3)}$$

$$= \frac{[2\pi \times (1.42\text{MHz})]^2}{s^2 - [4\pi \times (1.42\text{MHz}) \cos\frac{2\pi}{3}]s + [2\pi \times (1.42\text{MHz})]^2}$$

$$\omega_n = 2\pi \times 1.42\text{MHz} \left( = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \right)$$

$$\frac{\omega_n}{Q} = 2\pi \times 1.42\text{MHz} \cdot \cos\left(\frac{2\pi}{3}\right) \Rightarrow Q = \frac{-1}{2 \cos\left(\frac{2\pi}{3}\right)} = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}}$$


$$\text{Let } C_1 = 4C_2, R_1 = R_2, \text{ so that it satisfies } Q = \frac{-1}{2 \cos\left(\frac{2\pi}{3}\right)} = 1$$

$$\text{Also } \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} = 2\pi \times 1.42\text{MHz}$$

$$\text{Let } R_1 = R_2 = 1\text{k}\Omega \Rightarrow C_1 = 224\text{pF}, C_2 = 56\text{pF}$$

$$P_2 = -W_0, \quad \frac{1}{R_3 C_3} = (2\pi)(1.42 \text{ MHz})$$
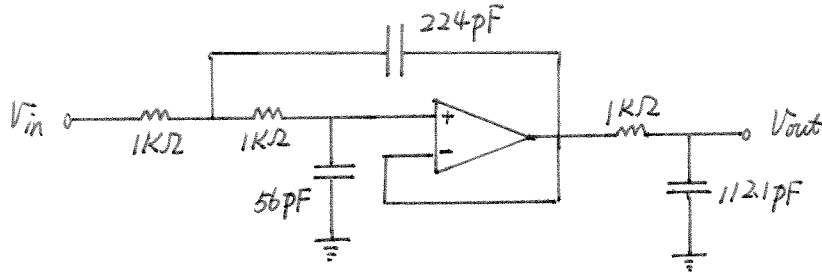
$$\text{Let } R_3 = 1 \text{ k}\Omega \Rightarrow C_3 = 112.1 \text{ pF}$$



Chebyshev in Sallen and Key

$$P_k = -W_0 \sin \frac{(2k-1)\pi}{2n} \sinh \left( \frac{1}{n} \sinh^{-1} \frac{1}{\epsilon} \right) + j W_0 \cos \frac{(2k-1)\pi}{2n} \cosh \left( \frac{1}{n} \sinh^{-1} \frac{1}{\epsilon} \right)$$

$$n=2, \quad W_0 = (2\pi)(1 \text{ MHz}), \quad \epsilon = 0.3493, \quad K=1, 2.$$

$$P_{1,2} = -0.7128 W_0 \pm j 1.0041 W_0$$

$$H_{SK}(s) = \frac{(s-P_1)(s-P_2)}{(s-P_1)(s-P_2)} = \frac{(1.2314)^2 W_0^2}{s^2 + 1.4256 W_0 s + (1.2314)^2 W_0^2}$$

$$W_n = 1.2314 W_0 = (2\pi)(1.2314 \text{ MHz})$$


$$\frac{W_n}{Q} = 1.4256 W_0 \Rightarrow Q = \frac{1.2314}{1.4256} = 0.8638$$

$$W_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad Q = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}}$$

$$\text{Let } R_1 = R_2 \quad Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}} \Rightarrow \frac{C_1}{C_2} = 4Q^2 = 2984.4$$

$$\frac{1}{\sqrt{R_1 R_2 C_1 C_2}} = W_n = 2\pi(1.2314 \text{ MHz}), \Rightarrow \frac{1}{R_1 C_2 \sqrt{2984.4}} = 2\pi(1.2314 \text{ MHz})$$
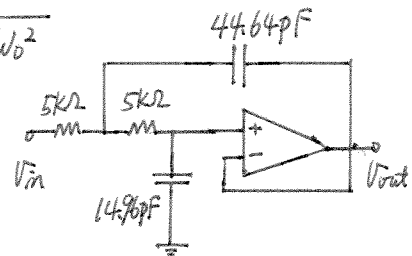
$$\text{Let } R_1 = R_2 = 5 \text{ k}\Omega \Rightarrow C_2 = 14.96 \text{ pF}, \quad C_1 = 44.64 \text{ pF}$$



b). Butterworth with SK

$$n=4, \omega_0 = (2\pi)(1.6\text{MHz})$$

$$P_k = \omega_0 \exp(j\frac{\pi}{2}) \exp(j\frac{2k-1}{2n}\pi), \quad k=1, 2, 3, 4.$$

$$P_1 = \omega_0 \exp(j\frac{5\pi}{8}), \quad P_2 = \omega_0 \exp(j\frac{7\pi}{8}), \quad P_3 = \omega_0 \exp(-j\frac{5\pi}{8}), \quad P_4 = \omega_0 \exp(-j\frac{7\pi}{8})$$

$$H_{SK1,4}(s) = \frac{(-P_1)(-P_4)}{(s-P_1)(s-P_4)} = \frac{[(2\pi)(1.6 \times 10^6)]^2}{s^2 - [4\pi(1.6 \times 10^6) \cos(\frac{5\pi}{8})]s + [2\pi(1.6 \times 10^6)]^2}$$

$$\omega_n = 2\pi \times 1.6 \times 10^6$$

$$\frac{\omega_n}{Q} = (4\pi)(1.6 \times 10^6) \cos(\frac{5\pi}{8}) \Rightarrow Q = 1.31.$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad Q = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}}.$$


$$\text{Let } R_1 = R_2, \quad Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}} \Rightarrow \frac{C_1}{C_2} = 4Q^2 = 6.83.$$

$$\omega_n = \frac{1}{\sqrt{6.83} R_1 C_2} = 2\pi \times 1.6 \times 10^6$$

$$\text{Let } R_1 = R_2 = 5\text{K}\Omega \Rightarrow C_2 = 7.61\text{pF}, \quad C_1 = 52\text{pF}.$$

Similarly,  $H_{SK2,3}(s) = \frac{(-P_2)(-P_3)}{(s-P_2)(s-P_3)}$ , it can be derived for  $H_{SK2,3}$ .
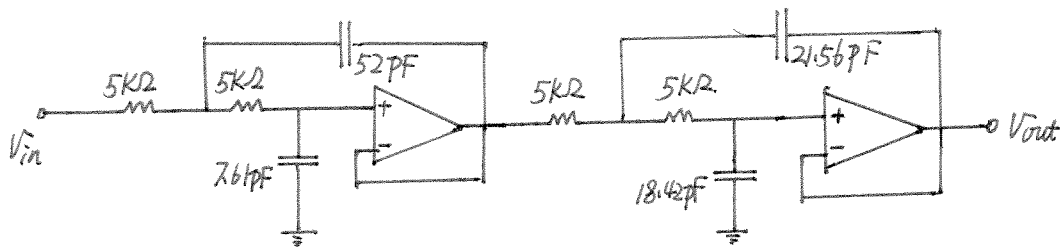
$$R_1 = R_2 = 5\text{K}\Omega, \quad C_2 = 18.42\text{pF}, \quad C_1 = 21.55\text{pF}.$$



b) Chebyshev in SK.

$$n=3, \omega_0 = (2\pi)(1 \times 10^6), \epsilon = 0.1536$$

$$P_1 = -\omega_0(0.9694) \sin\left(\frac{1}{6}\pi\right) + j\omega_0(1.3927) \cos\left(\frac{\pi}{6}\right) = -0.4847\omega_0 + j1.2061\omega_0$$

$$P_2 = -\omega_0(0.9694) \sin\left(\frac{3}{6}\pi\right) + j\omega_0(1.3927) \cos\left(\frac{3\pi}{6}\right) = -0.9496\omega_0$$

$$P_3 = -\omega_0(0.9694) \sin\left(\frac{5}{6}\pi\right) + j\omega_0(1.3927) \cos\left(\frac{5\pi}{6}\right) = -0.4847\omega_0 - j1.2061\omega_0$$

$$H_{SK}(s) = \frac{(-P_1)(-P_3)}{(s-P_1)(s-P_3)} = \frac{1.3^2 \omega_0^2}{s^2 + 0.9694\omega_0 s + (1.3)^2 \omega_0^2}$$

$$\omega_n = 1.3 \omega_0$$

$$\frac{\omega_n}{\alpha} = 0.9694 \omega_0 \Rightarrow \alpha = 13410.$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad \alpha = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}}$$

$$\text{Let } R_1 = R_2 \Rightarrow \alpha = \frac{1}{2} \sqrt{\frac{C_1}{C_2}} \Rightarrow \frac{C_1}{C_2} = (2\alpha)^2 = 71931.$$


$$\omega_n = \frac{1}{\sqrt{71931} R_1 C_2} = (1.3)(2\pi)(1 \times 10^6)$$

$$\text{Let } R_1 = R_2 = 5k\Omega \Rightarrow C_1 = 9.13 \text{ pF} \Rightarrow C_1 = 65.67 \text{ pF}$$

$$P_2 = (2\pi)(0.9694 \times 10^6), \text{ and}$$

$$\frac{1}{R_3 C_3} = P_2$$
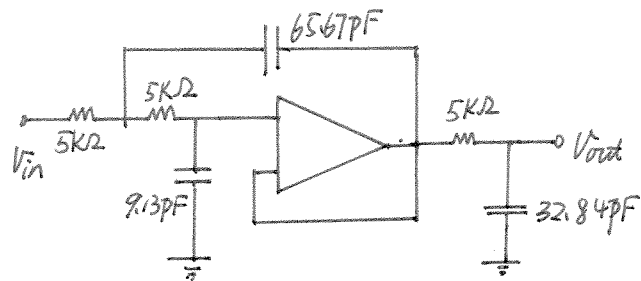
$$\text{Let } R_3 = 5k\Omega \Rightarrow C_3 = 32.84 \text{ pF}$$





c). Butterworth in SK.

$$n=3, \omega_0 = (2\pi)(1.27 \times 10^6)$$

$$P_k = \omega_0 \exp(j\frac{\pi}{2}) \exp(j\frac{2k-1}{2n}\pi), \quad k=1, 2, 3.$$

$$H_{p,3}(s) = \frac{(s-P_1)(s-P_3)}{(s-P_1)(s-P_3)} = \frac{[(2\pi)(1.27 \times 10^6)]^2}{s^2 - [4\pi \times (1.27 \times 10^6) \cos(\frac{2\pi}{3})]s + [2\pi(1.27 \times 10^6)]^2}$$

$$\omega_n = (2\pi)(1.27 \times 10^6)$$

$$\frac{\omega_n}{\Omega} = (4\pi)(1.27 \times 10^6) \cos(\frac{2\pi}{3}) \Rightarrow \Omega = 1.$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad \Omega = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2} \frac{C_1}{C_2}$$


Let  $C_1 = 4C_2, R_1 = R_2$

$$\omega_n = \frac{1}{2R_1 C_2} = (2\pi)(1.27 \times 10^6)$$

Let  $R_1 = R_2 = 5k\Omega \Rightarrow C_2 = 12.53 \text{ pF}, C_1 = 50.13 \text{ pF}.$

$$P_2 = -\omega_0 = (2\pi)(1.27 \times 10^6) = \frac{1}{R_3 C_3}$$

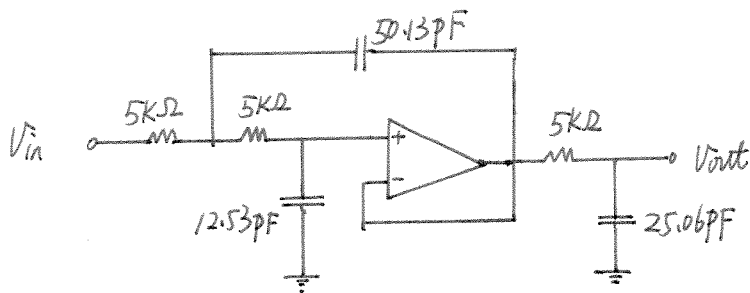Let  $R_3 = 5k\Omega \Rightarrow C_3 = 25.06 \text{ pF}$



c). Chebyshev in SK.

$$n=3, \epsilon \approx 0.5089, \omega_0 = (2\pi)(10^6)$$

$$p_1 = -0.2470\omega_0 + j0.9660\omega_0$$

$$p_2 = -0.4941\omega_0$$

$$p_3 = -0.2470\omega_0 - j0.9660\omega_0$$

$$H_{p,3}(s) = \frac{(-p_1)(-p_3)}{(s-p_1)(s-p_3)} = \frac{[(2\pi)(0.9971 \times 10^6)]^2}{s^2 + (0.4940)(2\pi)(10^6)s + (2\pi \times 0.9971 \times 10^6)^2}$$

$$\omega_n = (2\pi)(0.9971 \times 10^6)$$

$$\frac{\omega_n}{Q} = (0.4940)(2\pi \times 10^6) \Rightarrow Q = 2.02.$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad Q = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}}$$

$$\text{Let } R_1 = R_2 \Rightarrow Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}} \Rightarrow \frac{C_1}{C_2} = 4Q^2 = 16.296$$


$$\omega_n = \frac{1}{\sqrt{16.296} R_1 C_2} = (2\pi)(0.9971 \times 10^6)$$

$$\text{Let } R_1 = R_2 = 5 \text{ k}\Omega \Rightarrow C_2 = 7.91 \text{ pF} \Rightarrow C_1 = 128.87 \text{ pF}$$

$$R_2 = 2\pi \times 0.4941 \times 10^6 = \frac{1}{R_3 C_3}$$

$$\text{Let } R_3 = 5 \text{ k}\Omega$$

$$\Rightarrow C_3 = 64.42 \text{ pF}$$

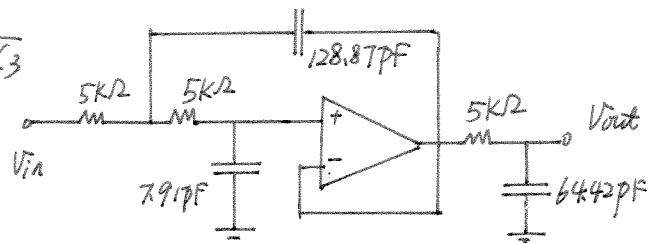

d). Butterworth in SK.

$$n=4, \omega_0 = (2\pi)(1.3 \times 10^6)$$

$$P_k = \omega_0 \exp(j\frac{\pi}{2}) \exp(j\frac{2k-1}{2n}\pi), \quad k=1,2,3,4.$$

$$H_{SK,4}(s) = \frac{(-P_1)(-P_4)}{(s-P_1)(s-P_4)} = \frac{\omega_0^2}{s^2 - [2\omega_0 \cos(\frac{5\pi}{8})]s + \omega_0^2}$$

$$\omega_n = \omega_0 = (2\pi)(1.3 \times 10^6)$$

$$\frac{\omega_n}{\alpha} = 4\pi(1.3 \times 10^6) \cos(\frac{5\pi}{8}) \Rightarrow Q = 1.31$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad Q = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}}$$


$$\text{Let } R_1 = R_2 \Rightarrow Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}} \Rightarrow \frac{C_1}{C_2} = 4Q^2 = 6.828$$

$$\omega_n = \frac{1}{\sqrt{6.828} R_1 C_2} = (2\pi)(1.3 \times 10^6)$$

$$\text{Let } R_1 = R_2 = 5k\Omega \Rightarrow C_2 = 9.37pF \Rightarrow C_1 = 63.98pF$$

Similarly,  $H_{SK,3}(s) = \frac{(-P_2)(-P_3)}{(s-P_2)(s-P_3)}$ . It can be derived that
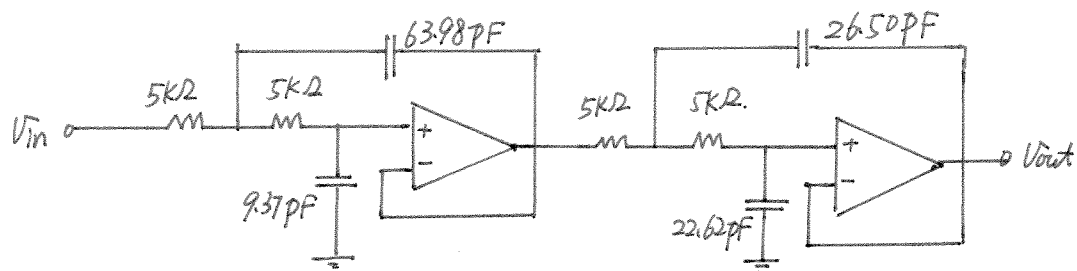
$$R_1 = R_2 = 5k\Omega, \quad C_2 = 22.62pF, \quad C_1 = 26.50pF.$$



d). Chebyshev in SK.

$$n=3, \epsilon=0.3493, \omega_0=(2\pi)(1 \times 10^6)$$

$$P_1 = -\omega_0 0.6265 \sin\left(\frac{1}{8}\pi\right) + j\omega_0(1.1800) \cos\left(\frac{1}{8}\pi\right)$$

$$P_2 = -\omega_0 0.6265$$

$$P_3 = -\omega_0 0.6265 \sin\left(\frac{5}{8}\pi\right) + j\omega_0(1.1800) \cos\left(\frac{5}{8}\pi\right)$$

$$H_{P13} = \frac{(-P_1)(-P_3)}{(s-P_1)(s-P_3)} = \frac{[2\pi \times 1.069 \times 10^6]^2}{s^2 + (0.6265)(2\pi \times 10^6)s + (2\pi \times 1.069 \times 10^6)^2}$$

$$\omega_n = (2\pi)(1.069 \times 10^6)$$

$$\frac{\omega_n}{Q} = (0.6265)(2\pi \times 10^6) \Rightarrow Q = 1.7063$$


$$\text{Let } R_1 = R_2 \Rightarrow Q = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}} = \frac{1}{2} \sqrt{\frac{Q}{C_2}} \Rightarrow \frac{Q}{C_2} = 4Q^2 = 11.6459$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} = \frac{1}{\sqrt{11.6459} R_1 C_2} = (2\pi)(1.069 \times 10^6)$$

$$\text{Let } R_1 = R_2 = 5k\Omega \Rightarrow C_2 = 8.73 \text{ pF} \Rightarrow C_1 = 101.62 \text{ pF}$$

$$-P_2 = (0.6265)(2\pi \times 10^6) = \frac{1}{R_3 C_3}$$
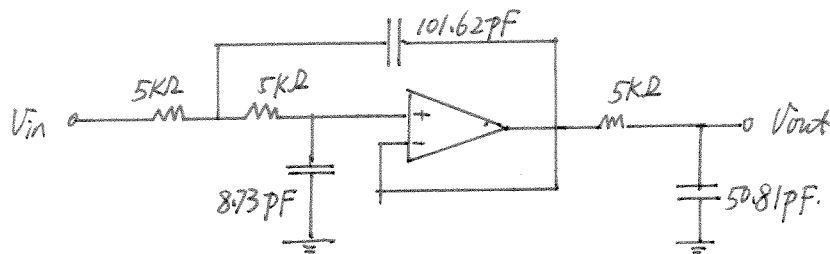
$$\text{Let } R_3 = 5k\Omega \Rightarrow C_3 = 50.81 \text{ pF}$$



62) a). Butterworth TT

$$n=3, \omega_0 = (2\pi)(1.42 \times 10^6)$$

$$P_1 = \omega_0 \exp(j\frac{2\pi}{3}), P_2 = -\omega_0, P_3 = \omega_0 \exp(-j\frac{2\pi}{3})$$

$$H_{P,3} = \frac{[2\pi \times (1.42 \times 10^6)]^2}{s^2 - [4\pi \times (1.42 \times 10^6) \cos(\frac{2\pi}{3})]s + [2\pi \times 1.42 \times 10^6]^2}$$

$$\omega_n = (2\pi)(1.42 \times 10^6)$$


$$Q = \frac{-1}{2 \cos(\frac{2\pi}{3})} = 1$$

$$\omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}, \quad Q = R_3 \sqrt{\frac{C_1}{C_2 R_2 R_4}}$$

$$\text{Let } R_2 = R_4 = R_3 = 5K\Omega, \quad C_1 = C_2 = 22.42 \text{ pF}$$

$$-P_2 = + (2\pi)(1.42 \times 10^6) = \frac{1}{R_3 C_3}$$
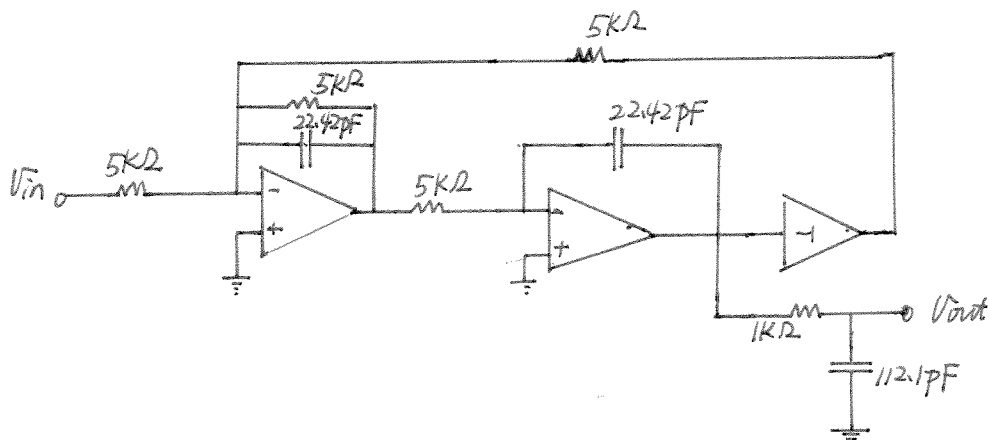
$$\text{Let } R_3 = 1K\Omega \Rightarrow C_3 = 112.1 \text{ pF}$$



$R_1 = R_2 = R_4$ , to match low frequency gain requirement.

a) Chebyshev TT

$$n=2, \omega_0 = (2\pi)(1\text{MHz}), \epsilon = 0.3493$$

$$H_{P_{0.2}} = \frac{(1.2314)^2 \omega_0^2}{s^2 + 1.4256 \omega_0 s + (1.2314)^2 \omega_0^2}$$

$$\omega_n = (2\pi)(1.2314 \times 10^6)$$

$$Q = \frac{1.2314}{1.4256} = 0.8638$$

$$Q = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}, \quad \omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}$$


$$\text{Let } C_1 = C_2, R_2 = R_4$$

$$\omega_n = \frac{1}{R_2 C_1} = (2\pi)(1.2314 \times 10^6)$$

$$\text{Let } R_2 = R_4 = 5\text{k}\Omega, C_1 = C_2 = 25.85\text{pF}$$

$R_1 = R_2 = R_4 = 5\text{k}\Omega$ , to match low frequency gain of unity.
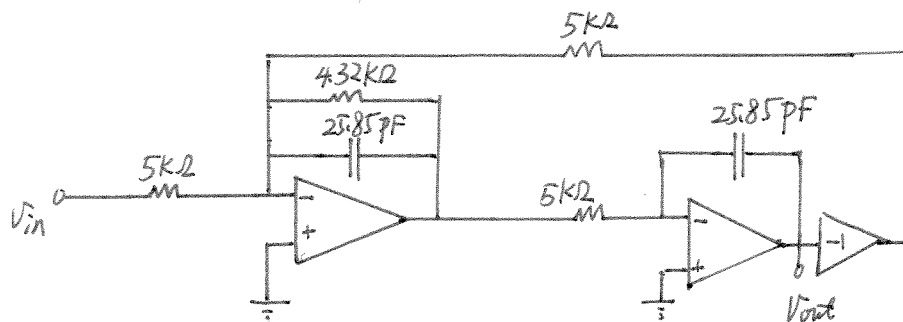
$$Q = \frac{R_3}{R_2} \Rightarrow R_3 = 4.32\text{k}\Omega.$$



b). Butterworth with TT

$$n=4, \omega_0 = (2\pi)(1.6 \times 10^6)$$

$$P_1 = \omega_0 \exp(j\frac{5\pi}{8}), \quad P_4 = \omega_0 \exp(-j\frac{5\pi}{8})$$

$$P_2 = \omega_0 \exp(j\frac{7\pi}{8}), \quad P_3 = \omega_0 \exp(-j\frac{7\pi}{8})$$

$$H_{P_{1,4}} = \frac{\omega_0^2}{s^2 - [2\omega_0 \cos(\frac{5\pi}{8})]s + \omega_0^2}$$

$$\omega_n = \omega_0 = (2\pi)(1.6 \times 10^6)$$

$$\frac{\omega_n}{\alpha} = (4\pi)(1.6 \times 10^6) \cos(\frac{5\pi}{8}) \Rightarrow \alpha = 1.31$$

$$\omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}, \quad \alpha = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}$$

$$\text{Let } R_2 = R_4, C_1 = C_2 \Rightarrow \omega_n = \frac{1}{R_2 C_1} = (2\pi)(1.6 \times 10^6)$$


$$\text{Let } R_2 = R_4 = 5\text{K}\Omega \Rightarrow C_1 = C_2 = 19.89\text{pF}$$

$R_1 = R_2 = R_4 = 5\text{K}\Omega$ , to obtain a low-frequency gain of unity.

$$\alpha = \frac{R_3}{R_2} = 1.31 \Rightarrow R_3 = 1.31 R_2 = 6.55\text{K}\Omega$$

Similarly for  $H_{P_{2,3}}$ , it can be derived that  $R_1 = R_2 = R_4 = 5\text{K}\Omega, R_3 = 2.7\text{K}\Omega$

$$C_1 = C_2 = 19.89\text{pF}$$

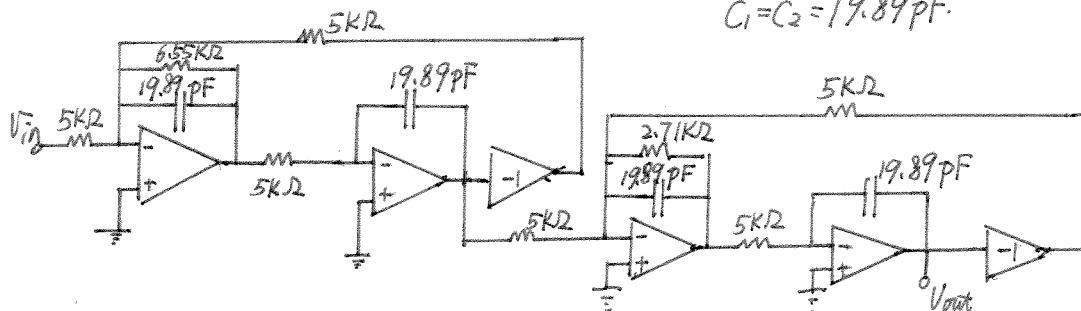

b). Chebyshev with TT

$$n=3, \epsilon = 0.1526, \omega_0 = (2\pi)(1 \times 10^6)$$

$$P_{1,3} = 0.4847\omega_0 \pm j 1.2061\omega_0$$

$$P_2 = -0.9694\omega_0$$

$$H_{p,3}(s) = \frac{(1.3)^2 \omega_0^2}{s^2 + 0.9694\omega_0 s + (1.3)^2 \omega_0^2}$$

$$\omega_n = 1.3\omega_0, \quad \frac{\omega_n}{Q} = 0.9694\omega_0$$

$$Q = \frac{1.3}{0.9694} = 1.3410$$

$$Q = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}, \quad \omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}$$


$$\text{Let } R_2 = R_4, C_1 = C_2, \quad \frac{1}{R_2 C_1} = (1.3)(2\pi)(10^6)$$

$$\text{Let } R_2 = R_4 = 5\text{K}\Omega, \Rightarrow C_1 = C_2 = 24.49\text{pF}$$

$R_1 = R_2 = R_4 = 5\text{K}\Omega$ , to obtain low-frequency gain of unity.

$$R_3 = Q R_2 = 6.705\text{K}\Omega$$
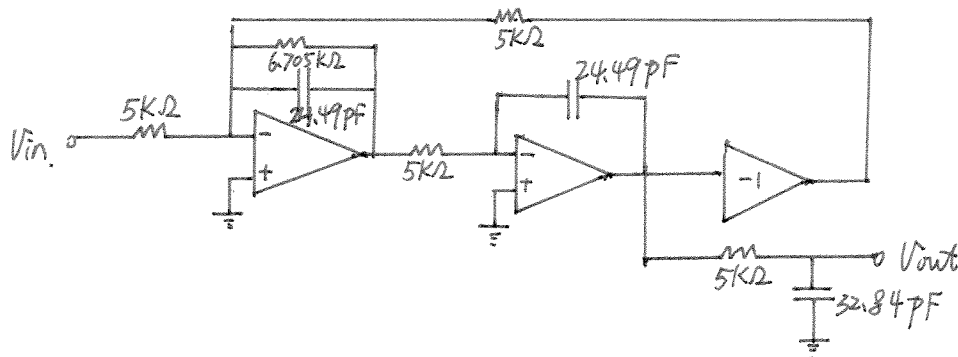
$$-P_2 = (2\pi)(0.9694 \times 10^6) = \frac{1}{R_5 C_5}, \quad \text{Let } R_5 = 5\text{K}\Omega \Rightarrow C_5 = 32.84\text{pF}$$





c) Butterworth with TT

$$n=3, \omega_0 = (2\pi)(1.27 \times 10^6)$$

$$P_1 = \omega_0 \exp(j\frac{2\pi}{3}), P_2 = \omega_0 \exp(-j\frac{2\pi}{3}), P_3 = -\omega_0$$

$$H_{P_{1,2}}(s) = \frac{[(2\pi)(1.27 \times 10^6)]^2}{s^2 - [(4\pi)(1.27 \times 10^6) \cos(\frac{2\pi}{3})]s + [(2\pi)(1.27 \times 10^6)]^2}$$

$$\omega_n = (2\pi)(1.27 \times 10^6), \quad \frac{\omega_n}{Q} = (4\pi)(1.27 \times 10^6) \cos(\frac{2\pi}{3})$$

$$Q = -\frac{1}{2 \cos(\frac{2\pi}{3})} = 1$$

$$Q = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}, \quad \omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}$$

$$\text{Let } R_2 = R_4, C_1 = C_2, \quad \frac{1}{R_2 C_1} = (2\pi)(1.27 \times 10^6)$$


$$\text{Let } R_2 = R_4 = 5k\Omega \Rightarrow C_1 = C_2 = 25.06 \text{ pF}$$

$$R_1 = R_2 = R_4 = 5k\Omega, \text{ to obtain Low-frequency gain of unity.}$$

$$R_3 = Q R_2 = 5k\Omega$$

$$-P_3 = \omega_0 \Rightarrow \frac{1}{R_5 C_5} = (2\pi)(1.27 \times 10^6)$$
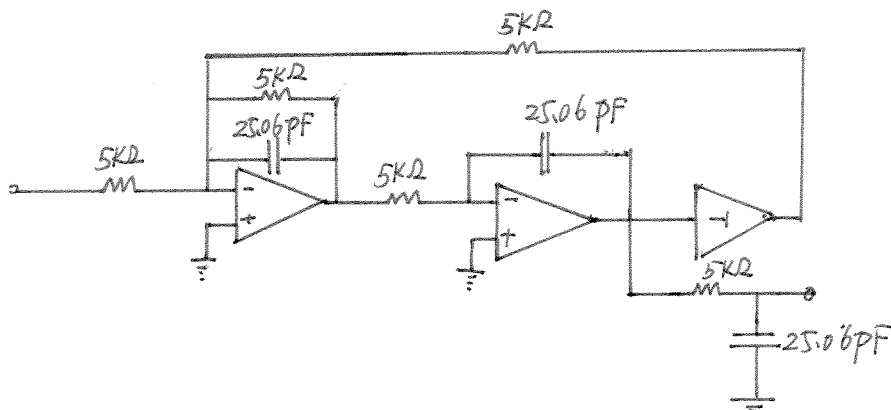
$$\text{Let } R_5 = 5k\Omega \Rightarrow C_5 = 25.06 \text{ pF}$$



c) Chebyshev TT

$$n=3, \epsilon=0.5089, \omega_0 = (2\pi)(1 \times 10^6)$$

$$P_{1,3} = -0.2470 \omega_0 \pm j 0.9660 \omega_0, P_2 = -0.4941 \omega_0$$

$$H_{P_{1,3}}(s) = \frac{[(2\pi)(10.9971 \times 10^6)]^2}{s^2 + (0.4940)(2\pi \times 10^6)s + [2\pi \times 0.9771 \times 10^6]^2}$$

$$\omega_n = (2\pi)(10.9971 \times 10^6)$$

$$\frac{\omega_n}{Q} = (0.4940)(2\pi \times 10^6) \Rightarrow Q = 2.02$$

$$Q = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}, \quad \omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}$$


$$\text{Let } R_2 = R_4, C_1 = C_2 \Rightarrow \frac{1}{R_2 C_1} = (2\pi)(10.9971 \times 10^6)$$

$$\text{Let } R_2 = R_4 = 5 \text{ k}\Omega \Rightarrow C_1 = C_2 = 31.92 \text{ pF}$$

$R_1 = R_2 = R_4 = 5 \text{ k}\Omega$ , to obtain Low-frequency gain of unity.

$$R_3 = QR_2 = 10.1 \text{ k}\Omega.$$
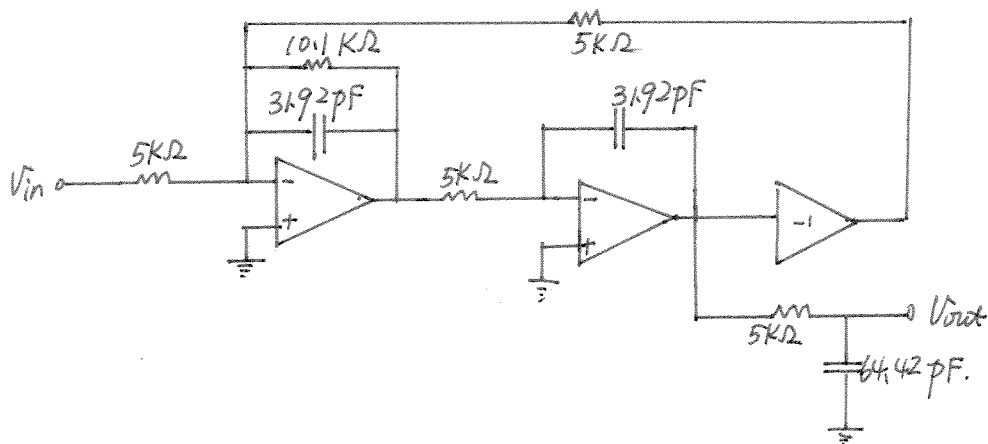
$$-P_2 = (2\pi)(0.4941 \times 10^6) = \frac{1}{R_5 C_5}. \quad \text{Let } R_5 = 5 \text{ k}\Omega \Rightarrow C_5 = 64.42 \text{ pF}.$$



d). Butterworth in TT

$$n=4, \omega_0 = (2\pi)(1.3 \times 10^6)$$

$$P_{1,4} = \omega_0 \exp(\pm j \frac{5\pi}{8}), \quad P_{2,3} = \omega_0 \exp(\pm j \frac{7\pi}{8})$$

$$H_{P_{1,4}}(s) = \frac{\omega_0^2}{s^2 - [2\omega_0 \cos(\frac{5\pi}{8})]s + \omega_0^2}$$

$$\omega_n = (2\pi)(1.3 \times 10^6)$$

$$\frac{\omega_n}{Q} = (4\pi)(1.3 \times 10^6) \cos(\frac{5\pi}{8}) \Rightarrow Q = -\frac{1}{2\cos(\frac{5\pi}{8})} = 1.31$$

$$\omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}, \quad Q = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}$$

$$\text{Let } R_2 = R_4, C_1 = C_2, \omega_n = \frac{1}{\sqrt{R_2^2 C_1^2}} = \frac{1}{R_2 C_1} = (2\pi)(1.3 \times 10^6)$$


$$\text{Let } R_2 = R_4 = 5k\Omega \Rightarrow C_1 = C_2 = 24.49 \text{ pF}$$

$$R_1 = R_2 = R_4 = 5k\Omega, \text{ to obtain a low-frequency gain of unity.}$$

$$R_3 = Q R_2 = 6.55k\Omega$$

$$\text{Similarly, } H_{P_{2,3}}(s) = \frac{\omega_0^2}{s^2 - [2\omega_0 \cos(\frac{7\pi}{8})]s + \omega_0^2}$$

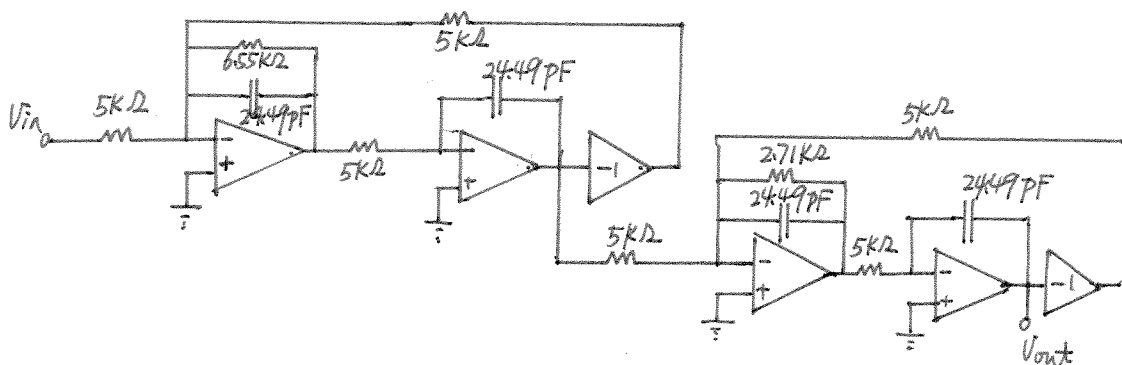It can be obtained that  $R_1 = R_2 = R_4 = 5k\Omega, R_3 = 2.71k\Omega, C_1 = C_2 = 24.49 \text{ pF}$ .



d). Chebyshev TT

$$n=3, \epsilon = 0.3493, \omega_0 = (2\pi)(1 \times 10^6)$$

$$P_{1,3} = -0.3133 \omega_0 \pm j1.022 \omega_0, \quad P_2 = -0.6265 \omega_0$$

$$H_{P_{1,3}} = \frac{[2\pi \times 1.069 \times 10^6]^2}{s^2 + (0.6265)(2\pi \times 10^6)s + (2\pi \times 1.069 \times 10^6)^2}$$

$$\omega_n = (2\pi)(1.069 \times 10^6)$$

$$\frac{\omega_n}{Q} = (0.6265)(2\pi \times 10^6) \Rightarrow Q = \frac{1.069}{0.6265} = 1.7063$$

$$\omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}, \quad Q = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}$$


$$\text{Let } R_2 = R_4, \quad C_1 = C_2, \quad \frac{1}{R_2 C_1} = (2\pi)(1.069 \times 10^6)$$

$$\text{Let } R_2 = R_4 = 5 \text{ k}\Omega \Rightarrow C_1 = C_2 = 29.78 \text{ pF}$$


$R_1 = R_2 = R_4 = 5 \text{ k}\Omega$ , to obtain a low-frequency gain of unity.

$$R_3 = Q R_2 = 8.53 \text{ k}\Omega$$
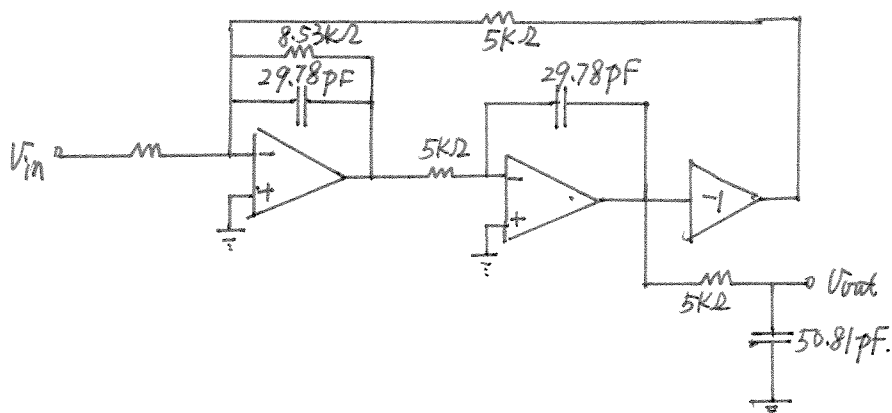
$$-P_2 = 0.6265 \times (2\pi \times 10^6) = \frac{1}{R_5 C_5}, \quad \text{Let } R_5 = 5 \text{ k}\Omega \Rightarrow C_5 = 50.81 \text{ pF}$$



1.

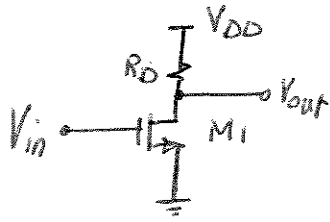

$M_1$  operates in the triode region

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - V_{TH}) V_{out, min} - V_{out, min}^2 \right]$$

$$R_D = 10K$$

$$V_{out} = V_{DD} - R_D I_D$$

$$\left(\frac{W}{L}\right)_1 = \frac{3}{0.18}$$

$$V_{out, min} = ? \text{ when } V_{in} = V_{DD}$$

$$V_{out, min} = V_{DD} - R_D I_{D, max}$$

$$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - V_{TH}) V_{out, min} - V_{out, min}^2 \right] \times R_D$$


If the second term in the square brackets is neglected, then

$$V_{out, min} \approx \frac{V_{DD}}{1 + \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH}) \times R_D}$$

$$= \frac{1.8}{1 + 100 \times 10^{-6} \times \frac{3}{0.18} \times (1.8 - 0.4) \times 10^5}$$

$$V_{out, min} \approx 74 \text{ mV}$$

2.

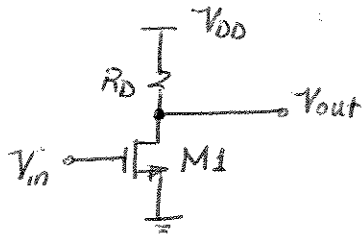

$$V_{out, min} \leq 100 \text{ mV}$$

$$R_D = 5 \text{ k}\Omega$$

$$\left(\frac{W}{L}\right)_{1, min} = ?$$

Output low level establishes for  $V_{in} = V_{DD}$ , driving  $M_1$  into the triode region.

$$I_{D, max} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - V_{TH}) V_{out, min} - V_{out, min}^2 \right]$$

$$V_{out, min} = V_{DD} - R_D \times I_{D, max}$$


$$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - V_{TH}) V_{out, min} - V_{out, min}^2 \right] \times R_D$$

$$\left(\frac{W}{L}\right)_1 = \frac{V_{DD} - V_{out, min}}{\frac{1}{2} \mu_n C_{ox} \left[ 2(V_{DD} - V_{TH}) V_{out, min} - V_{out, min}^2 \right] \times R_D}$$

$$\left(\frac{W}{L}\right)_{1, min} = \frac{1.8 - 100 \times 10^{-3}}{\frac{1}{2} \times 100 \times 10^{-6} \left[ 2(1.8 - 0.4) 100 \times 10^{-3} - (100 \times 10^{-3})^2 \right] \times 5 \times 10^3}$$

$$\boxed{\left(\frac{W}{L}\right)_{1, min} = 25}$$

3.

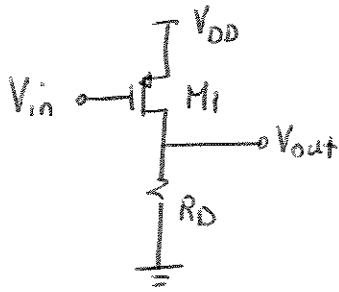

$$\left(\frac{W}{L}\right)_1 = 20/0.18, \quad R_D = 5K$$

$$V_{OL}, V_{OH} = ?$$

$$(1) \quad V_{in} = V_{DD} \rightarrow M_1 \text{ off} \rightarrow I_D = 0 \rightarrow \boxed{V_{out} = V_{OL} = 0}$$

(2)  $V_{in} = 0 \rightarrow M_1$  operates in the triode region

$$I_D = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{SG} - |V_{THP}|) V_{SD} - V_{SD}^2 \right]$$

$$I_{D, \max} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - |V_{THP}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right] \quad (1)$$

$$I_{D, \max} = \frac{V_{out}}{R_D} \quad (2)$$

Equating (1) and (2) and neglecting the second order term in the brackets

$$\frac{V_{out}}{R_D} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_1 \times 2(V_{DD} - |V_{THP}|)(-V_{out} + V_{DD})$$

$$V_{out} \left[ \frac{1}{R_D} + \mu_p C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - |V_{THP}|) \right] = \mu_p C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - |V_{THP}|) V_{DD}$$


$$V_{out} = \frac{R_D}{R_D + \frac{1}{\mu_p C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - |V_{THP}|)}} V_{DD}$$

$$V_{out} = \frac{5000}{5000 + \frac{1}{50 \times 10^{-6} \times \left(\frac{20}{0.18}\right) \times (1.8 - 0.5)}} \times 1.8$$

$$V_{out} = V_{OH} = 1.75 \text{ V}$$



4.

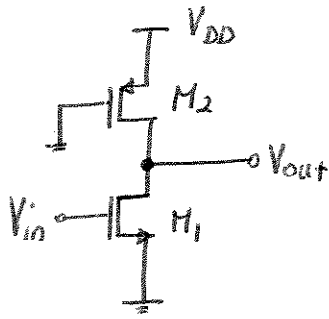

$$\left(\frac{W}{L}\right)_1 = 3/0.18 \quad \left(\frac{W}{L}\right)_2 = 2/0.18$$

(a) if  $V_{in} = V_{DD}$ ,  $M_2$  saturated  $\rightarrow V_{OL} = ?$

(b) if  $V_{in} = V_{out} \rightarrow V_{in} = ?$

$$(a) I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{SG} - |V_{THP}|)^2$$

$$I_{D2} = \frac{1}{2} \times 50 \times 10^{-6} \times \left(\frac{2}{0.18}\right) (1.8 - 0.5)^2, \text{ Note that } V_{SG} = V_{DD}$$

$$I_{D2} = 4.7 \times 10^{-4} \text{ A}$$

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{GS} - V_{THN}) V_{DS} - V_{DS}^2 \right]$$

$$= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - V_{THN}) V_{OL} - V_{OL}^2 \right]$$

However  $I_{D1} = I_{D2}$

$$4.7 \times 10^{-4} = \frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{3}{0.18}\right) \left[ 2(1.8 - 0.4) V_{OL} - V_{OL}^2 \right]$$

Neglecting the second-order term yields:

$$\boxed{V_{OL} = 0.2 \text{ V}}$$

As  $(V_{in} - V_{THN}) = (V_{DD} - V_{THN}) = (1.8 - 0.4) = 1.4 > V_{DS1} = V_{OL} = 0.2 \text{ V}$

The assumption of  $M_1$  being in Triode region is correct

We define,  $V_x = V_{in} - V_{TH,N} \rightarrow V_{in} = V_x + V_{TH,N}$

$$\frac{\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1}{\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2} V_x^2 = 2(V_{DD} - |V_{TH,P}|)(V_{DD} - V_{TH,N} - V_x) - (V_{DD} - V_{TH,N} - V_x)^2$$

$$\frac{100}{50} \times \frac{3/0.18}{2/0.18} V_x^2 = 2(1.8 - 0.5)(1.8 - 0.4 - V_x) - (1.8 - 0.4 - V_x)^2$$

$$3V_x^2 = 2.6(1.4 - V_x) - (1.4 - V_x)^2$$

$$3V_x^2 = 3.64 - 2.6V_x - 1.96 + 2.8V_x - V_x^2$$

$$4V_x^2 - 0.2V_x - 1.68 = 0$$

$$V_x = \frac{0.2 \pm \sqrt{0.2^2 + 4 \times 4 \times 1.68}}{8} \rightarrow \boxed{V_x = 0.67 \text{ V}}$$

$$V_{in} = V_x + V_{TH,N} = 0.67 + 0.4 \rightarrow \boxed{V_{in} = V_{out} = 1 \text{ V}}$$

This value of  $V_{out}$  guarantees that  $M_2$  operates in the triode region.

Now, let's investigate the region of operation of  $M_2$

$$V_{SD2} = V_{DD} - V_{out}$$

$$= 1.8 - 0.2$$

$$V_{SD2} = 1.6 \text{ V}$$

$$V_{SG2} - |V_{THP}| = V_{DD} - |V_{THP}|$$

$$= 1.8 - 0.5$$

$$V_{SG2} - |V_{THP}| = 1.3$$

As  $V_{SD2} > V_{SG2} - |V_{THP}|$ ,  $M_2$  operates in the saturation region and the initial assumption is valid.

(b) As  $V_{in} = V_{out} \rightarrow M_1$  is saturated.


We assume that  $M_2$  is in the triode region and check the

validity of this assumption

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{THN})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - |V_{THP}|) \times (V_{DD} - V_{in}) - (V_{DD} - V_{in})^2 \right]$$

5.

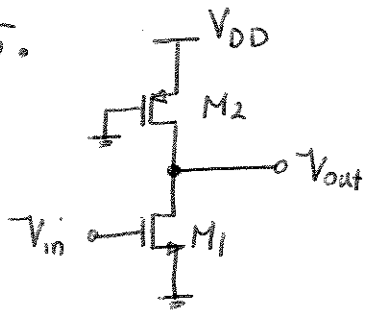

$$V_{OL} \leq 100 \text{ mV}$$

$$\left(\frac{W}{L}\right)_2 = 3/0.18$$

$$\left(\frac{W}{L}\right)_{1, \min} = ?$$

$V_{in} = V_{DD} \rightarrow M_1$  operates in the triode region and  $M_2$  in the saturation.

$$I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{SG} - |V_{TH,P}|)^2$$

$$= \frac{1}{2} \times 50 \times 10^{-6} \times \left(\frac{3}{0.18}\right) \times (1.8 - 0.5)^2$$


$$I_{D2} = 7.041 \times 10^{-4} \text{ A}$$

$$I_{D1} = I_{D2} = 7.041 \times 10^{-4} \text{ A}$$

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{GS} - V_{TH,N}) V_{DS} - V_{DS}^2 \right]$$

$$7.041 \times 10^{-4} = \frac{1}{2} \times 100 \times 10^{-6} \left(\frac{W}{L}\right)_1 \left[ 2(1.8 - 0.4) 0.1 - (0.1)^2 \right]$$
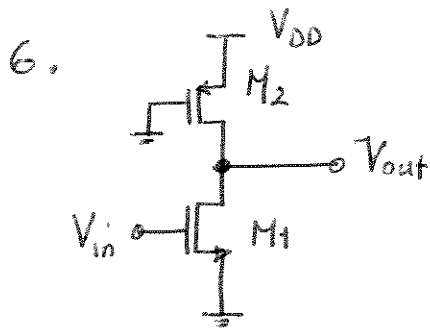
$$\boxed{\left(\frac{W}{L}\right)_{1, \min} = 52.16}$$



$$V_{OL} \leq 80 \text{ mV}$$

$$\left(\frac{W}{L}\right)_1 = 2/0.18$$

$$\left(\frac{W}{L}\right)_{2, \max}$$

$V_{in} = V_{DD} \rightarrow M_1$  operates in the triode region and  $M_2$  in the saturation

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{GS} - V_{TH,N})V_{DS} - V_{DS}^2 \right]$$

$$I_{D1} = \frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{2}{0.18}\right) \times \left[ 2(1.8 - 0.4)0.08 - 0.08^2 \right]$$

$$I_{D1} = 1.2 \times 10^{-4} \text{ A}$$


$$I_{D2} = I_{D1} = 1.2 \times 10^{-4} \text{ A}$$

$$I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{SG} - |V_{TH,P}|)^2$$

$$1.2 \times 10^{-4} = \frac{1}{2} \times 50 \times 10^{-6} \left(\frac{W}{L}\right)_2 (1.8 - 0.5)^2$$

$$\left(\frac{W}{L}\right)_{2, \max} = 2.86$$

7.

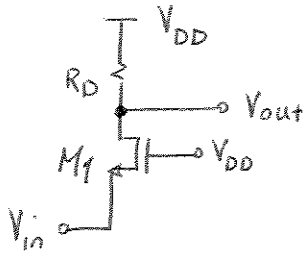

(a) If  $V_{in} = 0$ ,  $V_{DD}$ ,  $V_{out} = ?$

If  $V_{in} = 0 \rightarrow M_1$  operates in the triode region.


$$R_{on1} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH,N})}$$


$$V_{out} \cong \frac{R_{on1}}{R_{on1} + R_D} \times V_{DD} \rightarrow V_{out} \cong \frac{1}{1 + \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH,N}) R_D} \times V_{DD}$$

If  $V_{in} = V_{DD} \rightarrow V_{out} = V_{DD}$

No, this circuit does not invert.

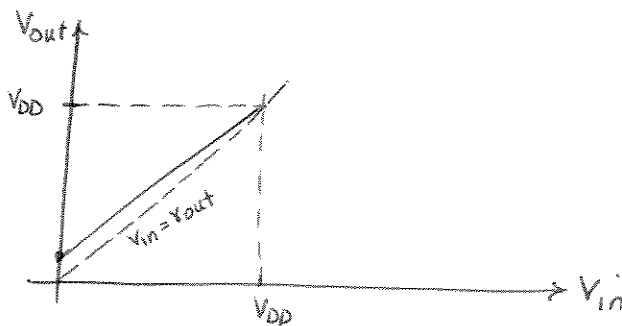(b) A trip point cannot be found for this circuit because  $V_{out} = V_{in}$  line does not intersect the transfer characteristic of this buffer.



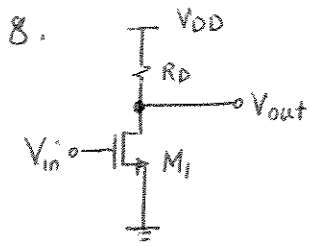

$$\left(\frac{W}{L}\right)_1 = 5/0.18$$

$$R_D = 2\text{K}\Omega$$

$$NM_L, NM_H = ?$$

Small signal gain of the circuit is equal to  $-g_m R_D$

$$\text{and } g_m = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH,N})$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH,N}) R_D = 1, \quad V_{GS} = V_{IL}$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{IL} - V_{TH,N}) R_D = 1$$

$$V_{IL} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} + V_{TH} = \frac{1}{100 \times 10 \times \frac{5}{0.18} \times 2000} + 0.4$$

$$\boxed{V_{IL} = 0.58\text{V}}$$

To determine  $NM_H$ , we note that  $V_{in}$  drives  $M_1$  into the triode region

$$V_{out} = V_{DD} - R_D I_D$$

$$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{TH,N}) V_{out} - V_{out}^2 \right] R_D \quad (1)$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{TH,N}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] R_D + 2V_{out}$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -1 \quad \text{at } V_{IH}$$

$$-1 = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ -2(V_{in} - V_{TH,N}) + 2V_{out} \right] R_D$$

$$I = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ -V_{in}^2 + V_{TH,N} + 2V_{out} \right] R_D$$

$$\frac{I}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} = -(V_{in} - V_{TH,N}) + 2V_{out}$$

$$V_{out} = \frac{I}{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} + \frac{V_{in} - V_{TH,N}}{2} \rightarrow V_{out} = 0.5V_{in} - 0.11$$

Substituting this in (1) yields:


$$0.5V_{in} - 0.11 = 1.8 - \frac{1}{2} \times 100 \times 10^{-6} \times \frac{5}{0.18} \times 2000 \left[ 2(V_{in} - 0.4)(0.5V_{in} - 0.11) - (0.5V_{in} - 0.11)^2 \right]$$

$$0.75V_{in}^2 - 0.33V_{in} - 0.6117 = 0$$

$$V_{in} = V_{IH} = 1.15$$
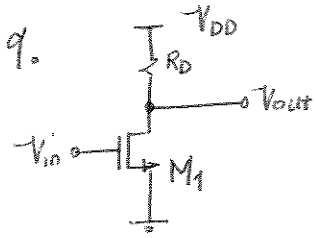
$$NM_H = V_{DD} - V_{IH} = 1.8 - 1.15 \rightarrow \boxed{NM_H = 0.65V}$$





Small signal gain of the inverter is equal to  $-g_m R_D$

and  $g_m = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH,N})$

$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH,N}) R_D = 1$ ,  $V_{GS} = V_{IL}$

$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{IL} - V_{TH,N}) R_D = 1 \rightarrow V_{IL} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} + V_{TH,N}$

If we double the value of  $\left(\frac{W}{L}\right)_1$  or  $R_D$

$V_{IL} = \frac{1}{100 \times 10^8 \times \frac{5}{0.18} \times 20000 \times 2} + 0.4 \rightarrow \boxed{V_{IL} = 0.49}$

To determine  $NM_H$ , we note that  $V_{in}$  drives  $M_1$  into the triode region

$V_{out} = V_{DD} - R_D I_D$

$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{TH}) V_{out} - V_{out}^2 \right] R_D$  (1)

$\frac{\partial V_{out}}{\partial V_{in}} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2 V_{out} + 2(V_{in} - V_{TH}) \frac{\partial V_{out}}{\partial V_{in}} - 2 V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right]$

$\frac{\partial V_{out}}{\partial V_{in}} = -1$  (a)  $V_{IH}$

$V_{out} = \frac{1}{2 \mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} + \frac{V_{in} - V_{TH,N}}{2}$

Doubling  $\left(\frac{W}{L}\right)_1$  or  $R_D$  leads to

$$V_{out} = 0.5V_{in} - 0.155$$


Substituting in (1) yields:

$$0.5V_{in} - 0.155 = 1.8 - \frac{1}{2} \times 100 \times 10^{-6} \times \frac{5}{0.18} \times 2000 \times 2 \left[ 2(V_{in} - 0.4)(0.5V_{in} - 0.155) - (0.5V_{in} - 0.155)^2 \right]$$

$$0.75V_{in}^2 - 0.465V_{in} - 0.251925 = 0$$

$$V_{in} = 0.967 \text{ V} \rightarrow NM_H = 1.8 - 0.967$$

$$NM_H = 0.833 \text{ V}$$

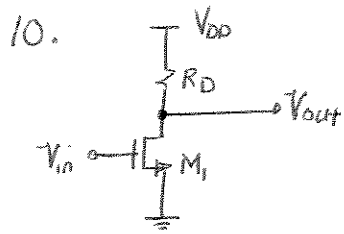

$$\left(\frac{W}{L}\right)_1 = \frac{5}{0.18}$$

$$R_D = 2K$$

$$NM_L \text{ and } NM_H = ? \text{ if } \frac{\partial V_{out}}{\partial V_{in}} = -0.5 \text{ instead of } -1$$

Small signal gain of the inverter is equal to " $-g_m R_D$ "

$$\text{and } g_m = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH,N})$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{IL} - V_{TH,N}) R_D = 0.5$$

$$V_{IL} = \frac{1}{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} + V_{TH,N} = \frac{1}{2 \times 100 \times 10^{-6} \times \frac{5}{0.18} \times 2000} + 0.4$$

$$\boxed{V_{IL} = 0.49} \text{ which is less than } 0.58 \text{ obtained in problem 8.}$$

To determine  $NM_H$ , note that  $M_1$  operates in the triode region

$$V_{out} = V_{DD} - R_D I_D$$

$$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{TH}) V_{out} - V_{out}^2 \right] R_D \quad (1)$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2V_{out} + 2(V_{in} - V_{TH}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] R_D$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -0.5 \quad \text{at } V_{IH}$$

$$-0.5 = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ -(V_{in} - V_{TH,N}) + 3V_{out} \right] R_D$$

$$V_{out} = \frac{1}{3\mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} + \frac{V_{in} - V_{TH,N}}{3} \rightarrow V_{out} = -73.33 \times 10^{-3} + 0.33 V_{in}^0$$

$$\text{or } V_{out} = -\frac{0.22}{3} + \frac{V_{in}}{3}$$

Substituting in (1) yields:

$$-\frac{0.22}{3} + \frac{V_{in}}{3} = 1.8 - \frac{1}{2} \times 100 \times 10^{-6} \times \frac{5}{0.18} \times 2000 \left[ 2(V_{in} - 0.4) \left( -\frac{0.22}{3} + \frac{V_{in}}{3} \right) - \left( -\frac{0.22}{3} + \frac{V_{in}}{3} \right)^2 \right]$$

$$5V_{in}^2 - 2.2V_{in} - 5.59 = 0$$


$$V_{in} = V_{IH} = 1.3$$

$$NM_H = 1.8 - 1.3$$

$$\boxed{NM_H = 0.5 \text{ V}}$$

less than 0.65 V obtained in problem 8 because

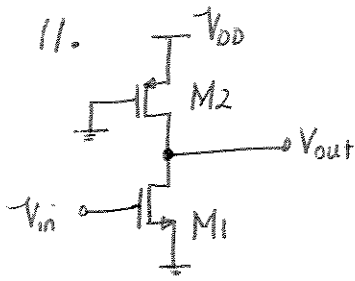$V_{IH}$  is now further pushed up toward  $V_{DD}$ .



$$\left(\frac{W}{L}\right)_1 = \frac{4}{0.18}$$

$$\left(\frac{W}{L}\right)_2 = \frac{9}{0.18}$$

To calculate  $V_{IL}$ , we assume that  $M_1$  and  $M_2$  operate in saturation and triode region respectively.

$$I_{D1} = I_{D2} \quad (1)$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH,N})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - |V_{TH,P}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right]$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH,N}) = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - |V_{TH,P}|) \left(-\frac{\partial V_{out}}{\partial V_{in}}\right) - 2(V_{DD} - V_{out}) \left(-\frac{\partial V_{out}}{\partial V_{in}}\right) \right]$$

By substituting  $\frac{\partial V_{out}}{\partial V_{in}}$  with "-1" in the above relationship:

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH,N}) = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - |V_{TH,P}|) - 2(V_{DD} - V_{out}) \right]$$

$$V_{out} = \frac{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH,N}) + |V_{TH,P}|}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2} = \frac{100 \times 10^{-6} \times 4 / 0.18}{50 \times 10^{-6} \times 9 / 0.18} (V_{in} - 0.4) + 0.5$$

$$V_{out} = 0.144 + 0.88 V_{in}^o \quad \text{or} \quad \boxed{V_{out} = \frac{8}{9} V_{in}^o + \frac{1.3}{9}}$$

Substituting  $V_{out}$  in (1) by the derivation versus  $V_{in}$  gives:

$$136 V_{in}^2 - 108.8 V_{in}^o - 115.13 = 0$$

$$\boxed{V_{in}^o = V_{IL} = NM_L = 1.4 V}$$

To calculate  $V_{IH}$ , we assume that  $M_1$  and  $M_2$  operate in the triode and saturation region respectively.

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{THN})V_{out} - V_{out}^2 \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{THP}|)^2 \quad (2)$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2V_{out} + 2(V_{in} - V_{THN}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] = 0$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -1$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2V_{out} - 2(V_{in} - V_{THN}) + 2V_{out} \right] = 0$$

$$V_{out} = \frac{V_{in} - V_{THN}}{2} \quad \text{Substituted in (2) yields:}$$

$$V_{in} = \sqrt{\frac{3}{2}} (V_{DD} - |V_{THP}|) + V_{THN}$$

$V_{in} = 2 \rightarrow V_{out} = 0.8$  This value of  $V_{out}$  puts  $M_2$  into the triode region so our initial assumption is not correct

Now we assume that both  $M_1$  and  $M_2$  operate in the triode region.

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{THN})V_{out} - V_{out}^2 \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - |V_{THP}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right] \quad (3)$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2V_{out} + 2(V_{in} - V_{THN}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] = \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \times$$

$$\left[ 2(V_{DD} - |V_{THP}|) \left(-\frac{\partial V_{out}}{\partial V_{in}}\right) - 2(V_{DD} - V_{out}) \left(-\frac{\partial V_{out}}{\partial V_{in}}\right) \right]$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2V_{out} - 2(V_{in} - V_{THN}) + 2V_{out} \right] = \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \times$$

$$\left[ 2(V_{DD} - |V_{THP}|) - 2(V_{DD} - V_{out}) \right]$$

$$V_{out} = \frac{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{THN}) - |V_{THP}|}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2}$$

$$2 \frac{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 - 1}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2}$$

$$V_{out} = \frac{8}{7} V_{in} - 1.1$$

After substituting in (3) it leads to:


$$2.1769 V_{in}^2 - 4.19 V_{in} + 0.576 = 0$$

$$\boxed{V_{in} = 1.77 \text{ V}}$$

$V_{out} = 0.93 \text{ V} \rightarrow$  The assumption is correct

$$V_{IH} = 1.77 \text{ V} \rightarrow NM_H = 1.8 - 1.77$$

$$\boxed{NM_H = 0.03 \text{ V}}$$

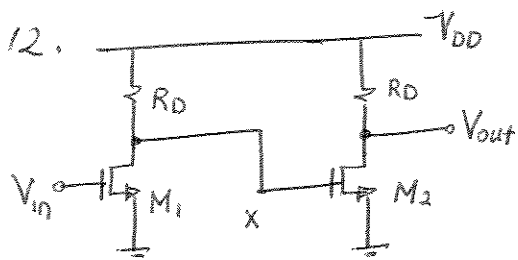

The small signal gain of the circuit is equal to  $-g_m R_D$  and since

$$g_m = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{THN})$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{IL} - V_{THN}) R_D = 1$$

$$V_{IL} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} + V_{THN} = \frac{2}{5} + 0.4 ; \left(\frac{W}{L}\right)_{1,2} = 5$$

Now we calculate the output of  $M_1$  for  $V_{in} = V_{DD}$ :

$$V_{DD} - R_D I_D = V_{out}$$

$$V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - V_{THN}) V_{out} - V_{out}^2 \right] R_D = V_{out} ; \left(\frac{W}{L}\right)_{1,2} = 5$$

$$1.8 - \frac{1}{2} \times 100 \times 10^{-6} \times 5 \left[ 2(1.8 - 0.4) \left(\frac{2}{5} + 0.4\right) - \left(\frac{2}{5} + 0.4\right)^2 \right] \times 5000 = \left(\frac{2}{5} + 0.4\right)$$

$$1.8 - 0.25 \times \left[ 2.8(2 + 0.45) - 5 \left(\frac{2}{5} + 0.4\right)^2 \right] = \frac{2}{5} + 0.4$$

$$1.85 - 0.25 \times \left[ 2.8(2.5 + 0.45^2) - 5 \left(\frac{2}{5} + 0.4\right)^2 \right] = 2 + 0.45$$





$$1.85 - 0.25 \times \left[ 5.65 + 1.125^2 - 4 - 1.65 - 0.165^2 \right] = 2 + 0.45$$

$$0.245^2 - 0.45 + 1 = 0$$


$$\Delta < 0!$$



13.

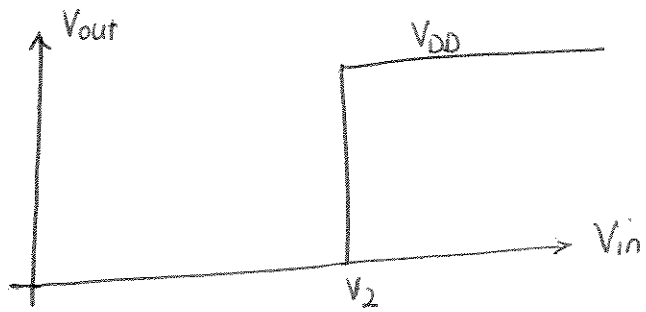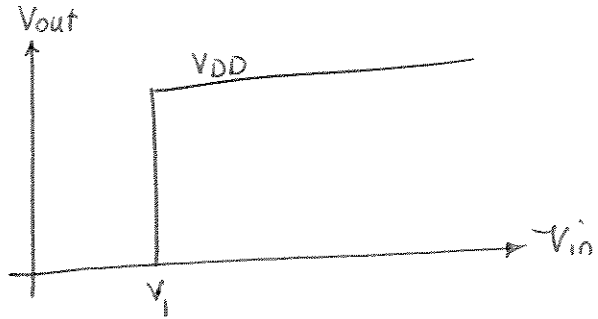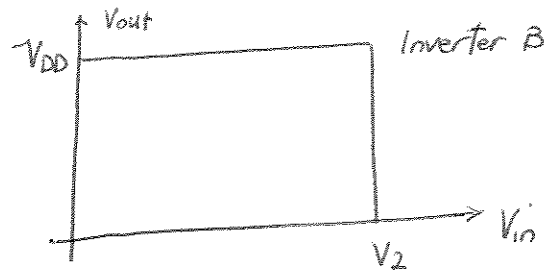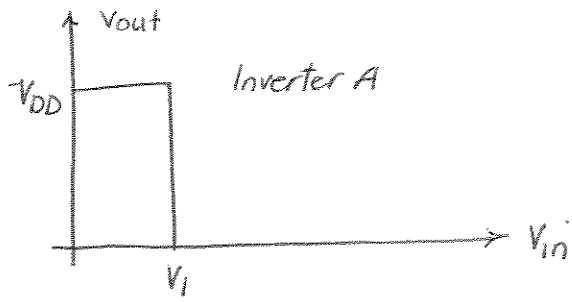

14.

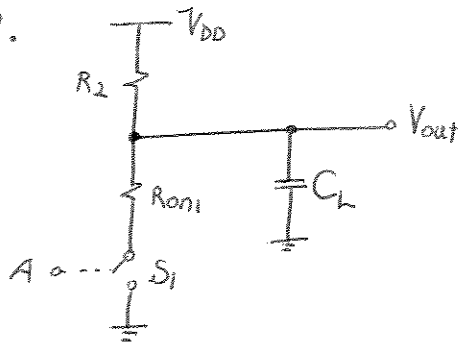

$$R_{on1} \ll R_2 \rightarrow V_{out, min} \approx 0$$

$$(a) \quad V_{out}(t) = V_{out}(\bar{0}) + [V_{DD} - V_{out}(\bar{0})] \left(1 - \exp\left(-\frac{t}{R_2 C_L}\right)\right) \quad t > 0$$

$$\text{Note that } V_{out}(\bar{0}) = 0, \quad V_{out}(\infty) = V_{DD}$$

$$V_{out}(t) = V_{DD} \times \left(1 - \exp\left(-\frac{t}{R_2 C_L}\right)\right) \quad t > 0$$

$$0.95 V_{DD} = V_{DD} \times \left(1 - \exp\left(-\frac{T_{95\%}}{R_2 C_L}\right)\right)$$

$$\boxed{T_{95\%} = 3 R_2 C_L}$$

$$(b) \quad V_{out}(t) = V_{out}(\bar{0}) + [V_{out}(\infty) - V_{out}(\bar{0})] \times \left(1 - \exp\left(-\frac{t}{R_2 C_L}\right)\right)$$

$$V_{out}(t) = V_{DD} + [0 - V_{DD}] \times \left(1 - \exp\left(-\frac{t}{R_2 C_L}\right)\right)$$


$$V_{out}(t) = V_{DD} \exp\left(-\frac{t}{R_2 C_L}\right)$$

$$0.05 V_{DD} = V_{DD} \exp\left(-\frac{T_{0.05}}{R_2 C_L}\right)$$

$$\boxed{T_{5\%} = 3 R_2 C_L}$$

If  $R_{on1} \ll R_2$ , inverter exhibits equal rise and fall time (or low-to-high and high-to-low delay) at the output.

15.

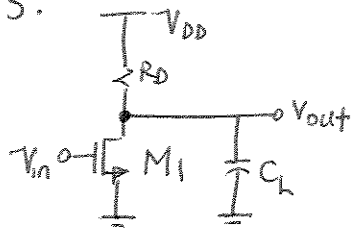

$$C_L = 50 \text{ fF}$$

$$T_R = 100 \text{ pS}$$


$$T_R = 3 Z_{out}$$

$$R_{D,max} = ?$$

$$T_R = 3 R_D C_L = 100 \text{ pS}$$

$$R_D \leq \frac{100 \text{ pS}}{3 \times 50 \text{ fF}}$$

$$R_D \leq 666.67 \Omega$$

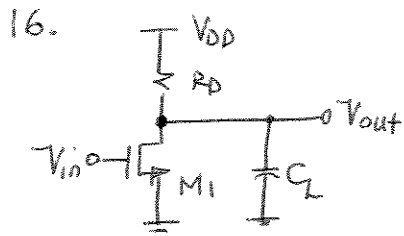

$$C_L = 100 \text{ fF}$$

$$V_{out, \min} = 50 \text{ mV}$$

$$T_R = 200 \text{ pS}$$

$$R_D, \left(\frac{W}{L}\right)_1 = ?$$

$$T_R = 3\tau_{out}$$

$$T_R = 3R_D C_L$$

$$200 \times 10^{-12} = 3 \times R_D \times 100 \times 10^{-15}$$

$$R_D = 666.667 \Omega$$

$V_{in} = V_{DD}$  places  $M_1$  in the triode region

$$V_{out, \min} = V_{DD} - R_D I_{D, \max}$$

$$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D \left[ 2(V_{DD} - V_{THN}) V_{out, \min} - V_{out, \min}^2 \right]$$


Neglecting the 2<sup>nd</sup> order term in the square brackets yields:

$$V_{out, \min} = \frac{V_{DD}}{1 + \mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D (V_{DD} - V_{THN})}$$

$$50 \times 10^{-3} = \frac{1.8}{1 + 100 \times 10^{-6} \times \left(\frac{W}{L}\right)_1 \times 666.7 \times (1.8 - 0.4)}$$

$$\left(\frac{W}{L}\right)_1 = 375$$

17.

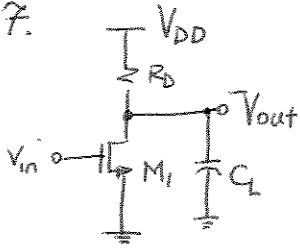

$$C_L = 100 \text{ fF}$$

$$V_{out, \min} \approx 0$$

$$I_{D, \max} \leq 1 \text{ mA}$$

$$T_{R, \min} = 0$$

$$I_{D, \max} = \frac{V_{DD} - V_{out, \min}}{R_D}$$

$$10^{-3} = \frac{1.8 - 0}{R_D}$$

$$R_D = 1.8 \text{ k}\Omega$$

$$V_{out}(t) = V_{out}(\bar{0}) + [V_{out}(\infty) - V_{out}(\bar{0})] \left(1 - \exp\left(-\frac{t}{R_D C_L}\right)\right) \quad t > 0$$

$$V_{out}(t) = V_{out, \min} + [V_{DD} - V_{out, \min}] \times \left(1 - \exp\left(-\frac{t}{R_D C_L}\right)\right) \quad t > 0$$


$$V_{out}(t) = V_{DD} \left(1 - \exp\left(-\frac{t}{R_D C_L}\right)\right) \quad t > 0$$

$$0.1 V_{DD} = V_{DD} \left(1 - \exp\left(-\frac{T_{10\%}}{R_D C_L}\right)\right) \rightarrow T_{10\%} = 0.105 R_D C_L$$

$$0.9 V_{DD} = V_{DD} \left(1 - \exp\left(-\frac{T_{90\%}}{R_D C_L}\right)\right) \rightarrow T_{90\%} = 2.3 R_D C_L$$

$$T_R = T_{90\%} - T_{10\%} = 2.197 R_D C_L = 2.197 \times 1.8 \times 10^3 \times 100 \times 10^{-15}$$

$$T_R = 395.5 \text{ pS}$$

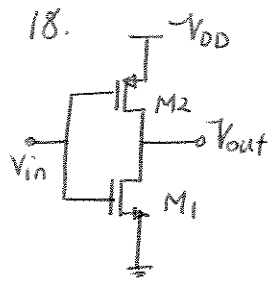

$$\left(\frac{W}{L}\right)_1 = \frac{2}{0.18}$$

$$\left(\frac{W}{L}\right)_2 = \frac{3}{0.18}$$

$$I_{D1} = I_{D2}$$

At the trip point  $V_{in} = V_{out}$ ; therefore, both  $M_1$  and  $M_2$  operate in the Saturation region.

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in}^o - V_{THN})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in}^o - |V_{THP}|)^2$$


$$V_{in}^o = \frac{V_{DD} - |V_{THP}| + \sqrt{\frac{\mu_n C_{ox} (W/L)_1}{\mu_p C_{ox} (W/L)_2} \times V_{THN}}}{1 + \sqrt{\frac{\mu_n C_{ox} (W/L)_1}{\mu_p C_{ox} (W/L)_2}}}$$

$$V_{in}^o = \frac{1.8 - 0.5 + \left(\frac{100 \times 2}{50 \times 3}\right)^{1/2} \times 0.4}{1 + \left(\frac{100 \times 2}{50 \times 3}\right)^{1/2}}$$

$$V_{in} = V_{out} = 0.82 \text{ V}$$

$$I_{D1} = I_{D2} = \frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{2}{0.18}\right) (0.82 - 0.4)^2$$

$$I_{D1} = I_{D2} = 97 \mu\text{A}$$

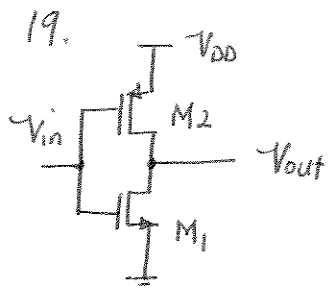


$$\left(\frac{W}{L}\right)_1 = \frac{2}{0.18}$$

$$\left(\frac{W}{L}\right)_2 = \frac{3}{0.18}$$

$$\lambda_n = 0.1 \text{ V}^{-1}$$

$$\lambda_p = 0.2 \text{ V}^{-1}$$

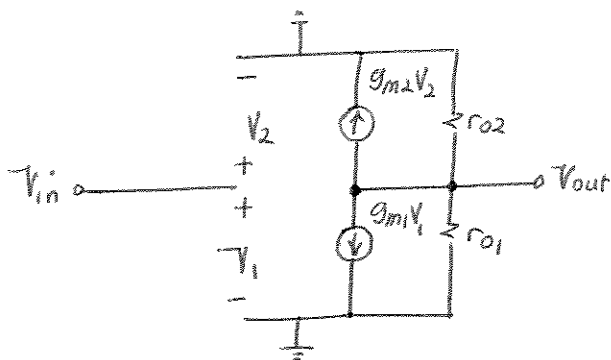Replacing  $M_1$  and  $M_2$  with their small-signal model in the saturation region yields:



$$V_{out} = (-g_{m1}V_1 - g_{m2}V_2)(r_{o1} || r_{o2})$$

$$V_1 = V_2 = V_{in}$$

$$V_{out} = -(g_{m1} + g_{m2})(r_{o1} || r_{o2}) V_{in}$$

$$\frac{V_{out}}{V_{in}} = -(g_{m1} + g_{m2})(r_{o1} || r_{o2})$$

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{THN})^2$$

$$g_{m1} = \frac{\partial I_{D1}}{\partial V_{in}} = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{THN}) = \frac{2I_{D1}}{V_{in} - V_{THN}}$$

$$g_{m1} = \frac{2 \times 9.7 \times 10^{-5}}{(0.817 - 0.4)} \rightarrow g_{m1} = 4.641 \times 10^{-4} \text{ S}$$

$$g_{m2} = \frac{2I_{D2}}{(V_{SG} - |V_{THP}|)} = \frac{2 \times 9.7 \times 10^{-5}}{(1.8 - 0.817 - 0.5)} \rightarrow \boxed{g_{m2} = 4.02 \times 10^{-4} \text{ S}}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)^2 (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$g_o = \frac{\partial I_D}{\partial V_{DS}} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)^2 (V_{GS} - V_{TH})^2 \lambda \approx \lambda I_D$$

$$r_o \approx \frac{1}{\lambda I_D}$$

$$r_{oN} \approx \frac{1}{0.1 \times 9.7 \times 10^{-5}} = 103.17 \text{ K}\Omega$$

$$r_{oP} \approx \frac{1}{0.2 \times 9.7 \times 10^{-5}} = 51.58 \text{ K}\Omega$$

$$\text{Gain} = \frac{V_{out}}{V_{in}} = - (4.641 \times 10^{-4} + 4.02 \times 10^{-4}) (51.58 \text{ K} \parallel 103.17 \text{ K})$$

$$\boxed{\text{Gain} = -29.8}$$




20.

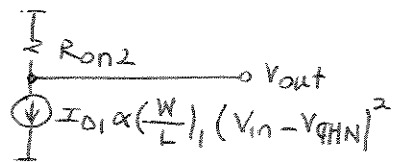(a) Length of  $M_1$  is increased

Let's assume that  $V_{in} < V_{TH1}$ , as a result  $M_1$  is off and  $M_2$  is on operating in the triode region. As  $V_{in}$  increases beyond  $V_{TH1}$ ,  $M_1$  starts pulling current (conducting) in the saturation region while  $M_2$  is still in the triode region, operating as a resistor; therefore,

CMOS inverter can be modelled as follows:



By increasing  $L_1$ ,  $I_{D1}$  is weakened due to the inverse proportionality; as a result, an excess  $V_{in}$  is required to drop  $V_{out}$  to the point where


$V_{out} = V_{in} + |V_{TH2}|$  and  $M_2$  is placed at the edge of saturation.

Therefore characteristic is shifted to the right and it will be steeper at the gain region where both  $M_1$  and  $M_2$  are in saturation region.

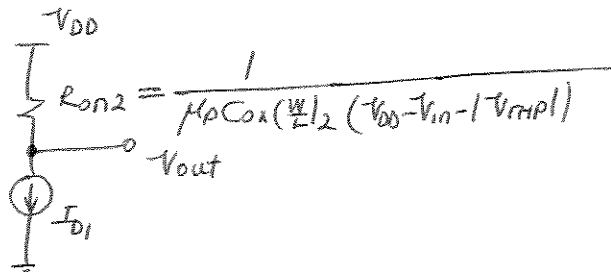
(b) Length of  $M_2$  is increased

Again if we assume that  $V_{in} < V_{TH1}$ ,  $M_1$  is off and  $M_2$  is operating in the triode region with no current. By increasing

$V_{in}$  above  $V_{TH1}$ ,  $M_1$  conducts in the saturation region while  $M_2$  is operating in the triode region. Using the same models as used in part (a) yields:



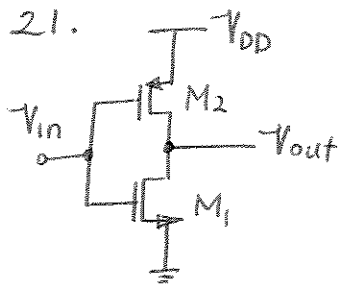
By increasing  $L_2$ ,  $R_{on2}$  becomes larger; as a result, lower value of  $I_{D1}$  causes comparable voltage drop at the output. This will drive  $M_2$  into the saturation with lower current ( $I_{D1}$ ) and, hence, lower value of  $V_{in}$ . Therefore, characteristic is shifted to the left and small signal gain will be higher.



$$\left(\frac{W}{L}\right)_1 = \frac{3}{0.18}$$

$$\left(\frac{W}{L}\right)_2 = \frac{7}{0.18}$$

VTC looks like the following figure

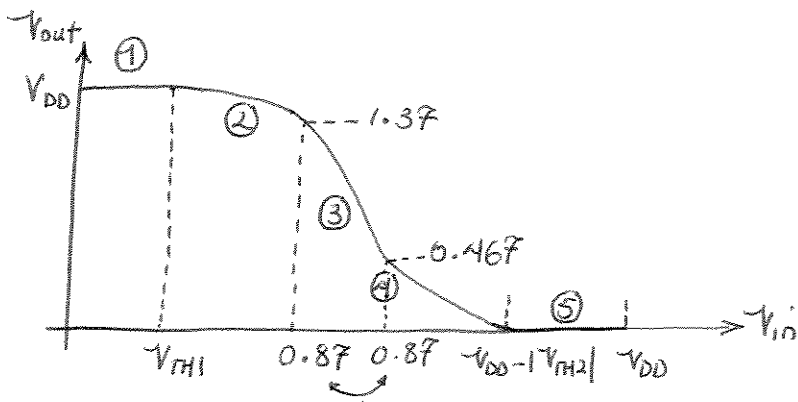

①  $M_1$  off,  $M_2$  in triode region

$$I_{D1} = \emptyset$$

$$I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - V_{in} - |V_{TH2}|) V_{SD} - V_{SD}^2 \right] = \emptyset$$

$$V_{SD} = 0 \rightarrow V_{out} = V_{DD} \quad (1)$$

②  $M_1$  in saturation,  $M_2$  in triode region

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - V_{in} - |V_{TH2}|) (V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right]$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \frac{3}{0.18} \times (V_{in} - 0.4)^2 = \frac{1}{2} \times 50 \times 10^{-6} \times \frac{7}{0.18} \times \left[ 2(1.8 - V_{in} - 0.5) \times (1.8 - V_{out}) - (1.8 - V_{out})^2 \right]$$

$$6(V_{in} - 0.4)^2 = 7 \left[ 2(1.3 - V_{in})(1.8 - V_{out}) - (1.8 - V_{out})^2 \right] \quad (2)$$

If  $V_{out}$  falls significantly,  $M_2$  enters saturation. That is  $V_{out} = V_{in} + |V_{TH2}|$ . Then  $M_2$  is about to exit the triode region.

Replacing  $V_{out}$  by  $V_{in} + |V_{TH2}|$  in (2) leads to:

$$6(V_{in} - 0.4)^2 = 7 \left[ 2(1.3 - V_{in})(1.8 - V_{in} - 0.5) - (1.8 - V_{in} - 0.5)^2 \right]$$

$$6(V_{in} - 0.4)^2 = 7(1.3 - V_{in})^2 \rightarrow \sqrt{\frac{6}{7}} (V_{in} - 0.4) = (1.3 - V_{in})$$

$$V_{in} = 0.867 \text{ V}, \quad V_{out} = 1.37 \text{ V}$$

$$(3) \quad \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2 (1 + \lambda_1 V_{out}) = \frac{1}{2} \mu_p C_{ox} \left( \frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 [1 + \lambda_2 (V_{DD} - V_{out})]$$

$$V_{out} = \frac{\mu_p C_{ox} \left( \frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 - \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2}{\lambda_2 \mu_p C_{ox} \left( \frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 + \lambda_1 \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2}$$

$$V_{out} = \frac{7(1.3 - V_{in})^2 - 6(V_{in} - 0.4)^2}{7\lambda_2(1.3 - V_{in})^2 + 6\lambda_1(V_{in} - 0.4)^2} \quad (3)$$

in region (3)  $M_1$  and  $M_2$  are both in saturation.

④  $M_1$  in triode region,  $M_2$  in saturation

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{TH1})V_{out} - V_{out}^2 \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \times (V_{DD} - V_{in} - |V_{TH2}|)^2 \quad (4)$$
$$6 \left[ 2(V_{in} - 0.4)V_{out} - V_{out}^2 \right] = 7(1.3 - V_{in})^2$$

If  $V_{out}$  falls sufficiently,  $M_1$  enters the triode region. That is, if

$V_{in} = V_{out} + V_{TH1}$ , then  $M_1$  is about to enter the triode region.

By substituting  $V_{in}$  with  $V_{out} + 0.4$  in (4), we have:

$$6 \left[ 2V_{out}^2 - V_{out}^2 \right] = 7(0.9 - V_{out})^2$$

$$V_{out} = 0.467, \quad V_{in} = 0.867$$

As channel length modulation has been neglected in this calculation the value of input voltage that makes CMOS inverter transition from region (2) to (3) is

the same as that which makes inverter transition from region (3) to (4).


The slope in region (3) is infinit; however, we assume a finite slope in that region to emphasize the behavior of inverter as to producing a high gain.

⑤  $M_1$  in triode region,  $M_2$  off

$$I_{D2} = 0, \quad I_{D1} = 0$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{TH1})V_{out} - V_{out}^2 \right] = 0 \rightarrow V_{out} = 0$$

22.

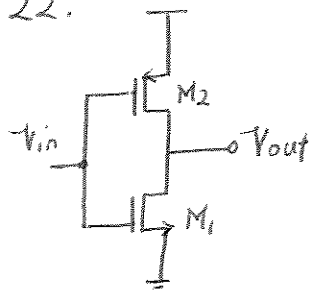

$$V_{in} = V_{out} = 0.5 \text{ V}$$

$M_1$  and  $M_2$  are both in saturation region

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{W}{L}\right)_1 (0.5 - 0.4)^2 = \frac{1}{2} \times 50 \times 10^{-6} \times \left(\frac{W}{L}\right)_2 (1.8 - 0.5 - 0.5)^2$$

$$\left(\frac{W}{L}\right)_1 / \left(\frac{W}{L}\right)_2 = 32$$

23. The value of the trip point has to be larger than the threshold voltage of NMOS transistor,  $0.4\text{ V}$ . Therefore,  $0.3\text{ V}$  cannot be the trip point of such an inverter.


24.

(a) If the inverter exhibits a very high voltage gain around the trip point, the range of input voltage values which guarantees that  $M_1$  and  $M_2$  are in saturation region is very narrow. Therefore this range can be fairly approximated with only one value of input voltage.

(b)  $(W/L)_1 = 3/0.18$  and  $(W/L)_2 = 7/0.18$

To calculate the minimum input voltage at which both transistors operate in saturation we assume

$M_1$  saturation  
 $M_2$  triode

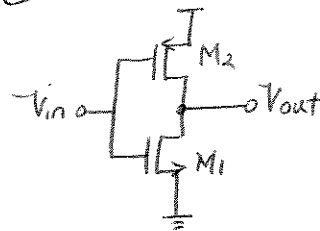

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - V_{in} - |V_{TH2}|)(V_{out} - V_{DD}) - (V_{out} - V_{DD})^2 \right]$$

$V_{out} = V_{in} + |V_{TH2}|$  places  $M_2$  at the edge of saturation

$$2 \times 3 \times (V_{in} - 0.4)^2 = 7 \times \left[ 2(1.8 - V_{in} - 0.5)(1.8 - V_{in} - 0.5) - (1.8 - V_{in} - 0.5)^2 \right]$$

$V_{in, \min} = 0.867$

To calculate  $V_{in, \max}$ , we assume that  $M_1$  and  $M_2$  are in triode and saturation region respectively

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{TH1})(V_{out} - V_{out}) \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2$$



When  $M_1$  is just going to leave the saturation and enters the triode region

$$V_{in} = V_{out} + 0.4^{(V_{TH1})}$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \frac{3}{0.18} \times \left[ 2(V_{out} + V_{TH1} - V_{TH1}) V_{out} - V_{out}^2 \right] = \frac{1}{2} \times 50 \times 10^{-6} \times \frac{7}{0.18} \times (V_{DD} - V_{in} - |V_{TH2}|)^2$$

$$\frac{6}{7} V_{out}^2 = (V_{DD} - V_{out} - |V_{TH1}| - |V_{TH2}|)^2$$

$$\frac{6}{7} V_{out}^2 = (0.9 - V_{out})^2$$

$$V_{out} = 0.467 \text{ V}, \quad V_{in} = 0.867 \text{ V}_{\text{max}}$$

To find the trip point,  $M_1$  and  $M_2$  are assumed to be in saturation.

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2$$


$$2 \times 3 \times (V_{in} - 0.4)^2 = 7 \times (1.8 - V_{in} - 0.5)^2$$

$$V_{in}^0 = 0.867 \text{ (a) trip point}$$







$$V_{in, \text{trip}} - V_{in, \text{min}} = 0$$

$$V_{in, \text{max}} - V_{in, \text{trip}} = 0$$

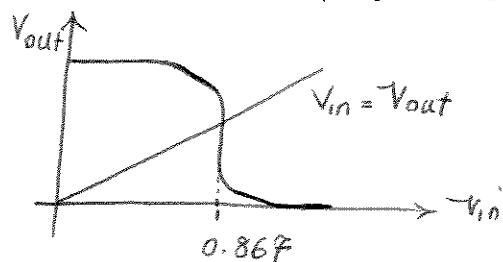
This result is not surprising because VTC of inverter has infinite slope at the region where both  $M_1$  and  $M_2$  are in saturation region



25.

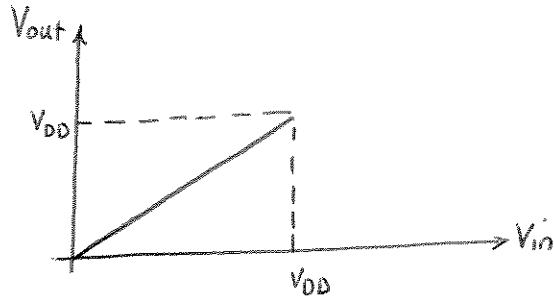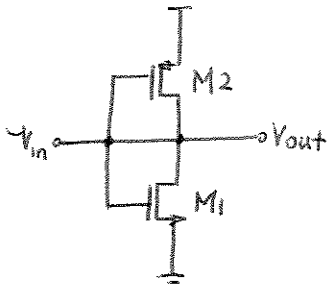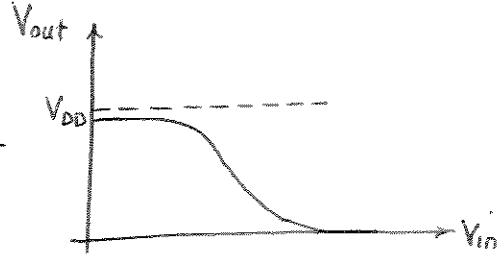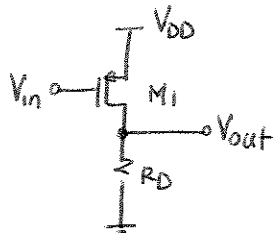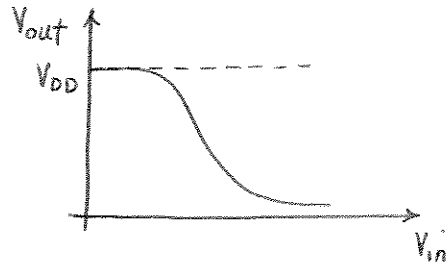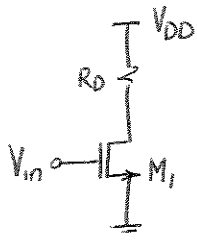

26.

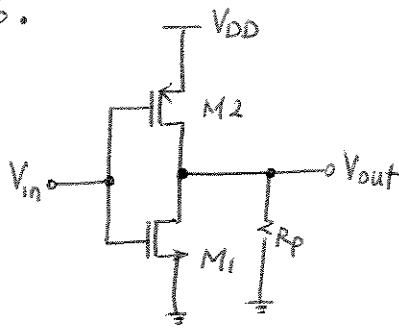


$$R_p = 2K$$

$$V_{OL}, V_{OH}, V_{in, trip} = ?$$

$$\left(\frac{W}{L}\right)_1 = 3/0.18$$

$$\left(\frac{W}{L}\right)_2 = 5/0.18$$

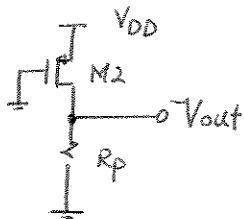To calculate  $V_{OH}$ ,  $V_{in}$  is assumed to be 0V



$$I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right]$$

$$I_{D2} = \frac{V_{out}}{R_p}$$

$$\frac{V_{out}}{R_p} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right]$$

$$V_{out} - 0.28V_{out} - 1.44 = 0$$

$$\boxed{V_{out} = V_{OH} = 1.348V}$$

$$\boxed{V_{OL} = 0} \text{ because } M_2 \text{ is off for } V_{in} = V_{DD}$$


(a) trip point  $V_{in} = V_{out}$

$$I_{D2} = I_{D1} + \frac{V_{out}}{R_p}$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 + \frac{V_{out}}{2000}$$

$$0.05V_{out}^2 + 0.59V_{out} - 0.3745 = 0 \rightarrow \boxed{V_{in} = V_{out} = 0.6V}$$

27.

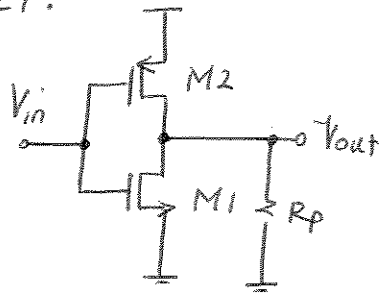

$$R_p = 2K$$

$$\left(\frac{W}{L}\right)_1 = 3/0.18$$

$$\left(\frac{W}{L}\right)_2 = 5/0.18$$

$$V_{in}^0 = V_{out} = 0.6V \text{ (a) trip point}$$

With  $R_p$

$$I_{D2} = I_{D1} + \frac{V_{out}}{R_p}$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 + \frac{V_{out}}{2000}$$

$$0.05 V_{out}^2 + 0.59 V_{out} - 0.3745 = 0$$

$$V_{in} = V_{out} = 0.6V$$

$$I_{D1} = \frac{1}{2} \times 100 \times 10^{-6} \times \frac{3}{0.18} \times (0.6 - 0.4)^2$$

$$I_{D1} = 3.33 \times 10^{-5} A$$

$$I_{D2} = I_{D1} + \frac{V_{out}}{R_p} = 3.33 \times 10^{-5} + \frac{0.6}{2000}$$

$$I_{D2} = 3.35 \times 10^{-4} A$$

$$g_{m1} = \frac{2I_{D1}}{V_{eff1}} = \frac{2 \times 3.33 \times 10^{-5}}{(0.6 - 0.4)} \rightarrow g_{m1} = 3.3 \times 10^{-3} S$$

$$g_{m2} = \frac{2I_{D2}}{V_{eff2}} = \frac{2 \times 3.35 \times 10^{-4}}{(1.8 - 0.6 - 0.5)} \rightarrow g_{m2} = 9.4 \times 10^{-3} S$$

$$A_V = -(g_{m1} + g_{m2}) \times R_p$$


$$A_V = -(3.3 \times 10^{-3} + 9.4 \times 10^{-3}) \times 2000$$

$$A_V = -25.4$$

Without  $R_p$

$$A_V \Rightarrow -\infty$$

28.

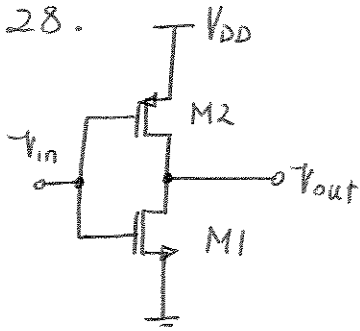

$$\left(\frac{W}{L}\right)_1 = 5/0.18$$

$$\left(\frac{W}{L}\right)_2 = 11/0.18$$

$$NM_L \text{ and } NM_H = ?$$

To calculate  $NM_L$ ,  $M_1$  and  $M_2$  are assumed to operate in the saturation and triode region respectively.

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - V_{in} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right] \quad (1)$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1}) = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ -2(V_{DD} - V_{out}) - 2(V_{DD} - V_{in} - |V_{TH2}|) \right] \times \left[ \frac{\partial V_{out}}{\partial V_{in}} + 2(V_{DD} - V_{out}) \frac{\partial V_{out}}{\partial V_{in}} \right]$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -1, \quad V_{in} = V_{IL}$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{IL} - V_{TH1}) = \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2V_{OH} - V_{IL} - |V_{TH2}| - V_{DD} \right] \quad (2)$$

Obtaining  $V_{OH}$  from (2) and substituting in (1) yields:

$$V_{IL} = \frac{2\sqrt{\alpha} (V_{DD} - V_{TH1} - |V_{TH2}|)}{(\alpha - 1)\sqrt{\alpha + 3}} - \frac{V_{DD} - \alpha V_{TH1} - |V_{TH2}|}{\alpha - 1}$$

$$\alpha = \frac{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2} = \frac{100}{50} \times \frac{5}{11} = \frac{10}{11}$$

$$V_{IL} = \frac{2\sqrt{10/11} (1.8 - 0.4 - 0.5)}{(10/11 - 1)\sqrt{10/11 + 3}} - \frac{1.8 - (10/11) \times 0.4 - 0.5}{10/11 - 1}$$

$$V_{IL} = 0.7516 \text{ V}$$

To determine  $NM_H$ ,  $M_1$  and  $M_2$  are assumed to operate in the triode and saturation region respectively.

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{TH1})V_{out} - V_{out}^2 \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}| - V_{in})^2 \quad (3)$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2V_{out} + 2(V_{in} - V_{TH1}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] = -\mu_p C_{ox} \left(\frac{W}{L}\right)_2 \times (V_{DD} - V_{in} - |V_{TH2}|)$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -1 \text{ yields}$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ V_{out} - V_{in} + V_{TH1} + V_{out} \right] = -\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)$$

$$100 \times 5 \times \left[ 2V_{out} - (V_{in} - 0.4) \right] = -50 \times 11 \times (1.8 - 0.5 - V_{in})$$

$$V_{out} = 1.05V_{in} - 0.915 \quad (4)$$

Substituting (4) in (3) yields an equation versus  $V_{in}$  as follows:

$$10 \times \left[ 2(V_{in} - 0.4)(1.05V_{in} - 0.915) - (1.05V_{in} - 0.915)^2 \right] = 11 \times (1.3 - V_{in})^2$$

$$1.025V_{in}^2 - 21.115V_{in} + 19.64225 = 0$$

$$V_{in} = V_{IH} = 0.9765 \text{ V}$$

$$NM_H = V_{DD} - V_{IH}$$

$$NM_H = 0.823 \text{ V}$$

$$29. \quad NML = 0.6 \text{ V}$$

$$(W/L)_1 / (W/L)_2 = ?$$

$$V_{IL} = \frac{2\sqrt{a}(V_{DD} - V_{TH1} - |V_{TH2}|)}{(a-1)\sqrt{a+3}} - \frac{V_{DD} - aV_{TH1} - |V_{TH2}|}{a-1}$$

$$a = \frac{\mu_n C_{ox} (W/L)_1}{\mu_p C_{ox} (W/L)_2}$$

$$0.6 = \frac{2\sqrt{a}(1.8 - 0.4 - 0.5)}{(a-1)\sqrt{a+3}} - \frac{1.8 - a \cdot 0.4 - 0.5}{a-1}$$

$$a = 3\sqrt{\frac{a}{a+3}} - \frac{1.3 - 0.4a}{0.6} + 1$$

$$a = \frac{a+3}{9} \times \left[ a-1 + \frac{1.3 - 0.4a}{0.6} \right]^2$$

$$\boxed{a=1}$$

$$(W/L)_1 / (W/L)_2 = \frac{\mu_p C_{ox}}{\mu_n C_{ox}} = \frac{1}{2}$$

$$\boxed{(W/L)_1 / (W/L)_2 = \frac{1}{2}}$$




$$30. V_{IL} = \frac{2\sqrt{a}(V_{DD} - V_{TH1} - |V_{TH2}|)}{(a-1)\sqrt{a+3}} - \frac{V_{DD} - aV_{TH1} - |V_{TH2}|}{a-1}$$


$$a = \frac{\mu_n \left(\frac{W}{L}\right)_1}{\mu_p \left(\frac{W}{L}\right)_2}$$

$$a \rightarrow 0 \quad V_{IL} = V_{DD} - |V_{TH2}|$$

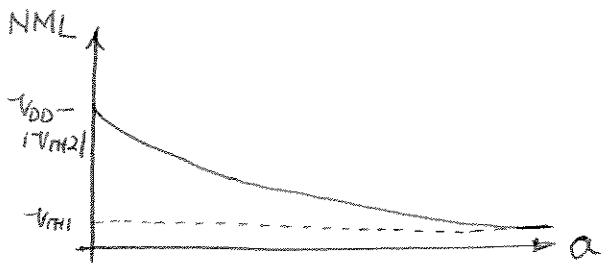
$$a \rightarrow \infty \quad V_{IL} = V_{TH1}$$



If  $a = \frac{\mu_n}{\mu_p} \times \frac{(W/L)_1}{(W/L)_2} \rightarrow 0$ , it implies that PMOS transistor is extremely stronger than NMOS. Therefore, as  $V_{in}$  increases from 0V, the output of inverter stays at  $V_{DD}$  until input reaches  $V_{DD} - |V_{TH2}|$ . At that point, PMOS is cut off and  $V_{out}$  sharply drops to 0V.

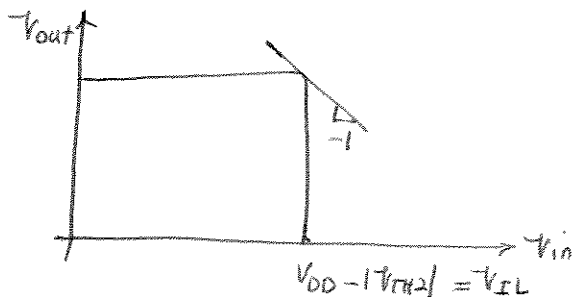

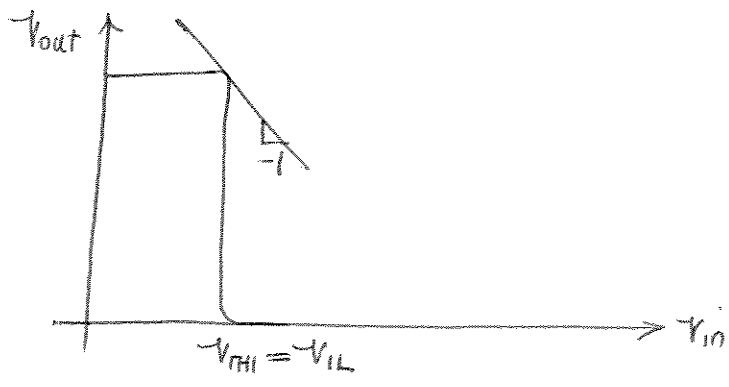When  $a \rightarrow \infty$ , NMOS is prevailing and once input voltage hits the threshold voltage of NMOS, output voltage falls sharply to 0V.




31.

$$NM_H = V_{DD} - \frac{2a(V_{DD} - V_{TH1} - |V_{TH2}|)}{(a-1)\sqrt{1+3a}} + \frac{V_{DD} - aV_{TH1} - |V_{TH2}|}{a-1}$$

$$a = \frac{\mu_n \left(\frac{W}{L}\right)_1}{\mu_p \left(\frac{W}{L}\right)_2}$$


$$a \rightarrow 0 \quad NM_H = |V_{TH2}|, \quad V_{IH} = V_{DD} - |V_{TH2}|$$
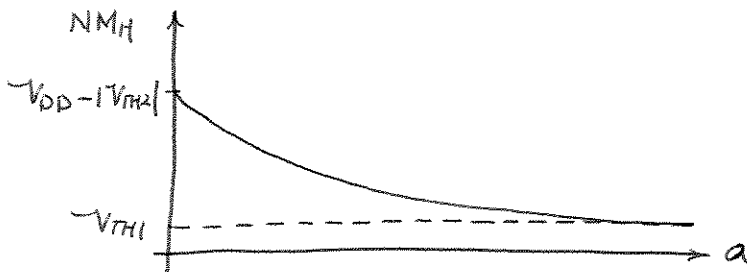
$$a \rightarrow \infty \quad NM_H = V_{DD} - V_{TH1}, \quad V_{IH} = V_{TH1}$$




If  $a = \frac{\mu_n}{\mu_p} \times \frac{(W/L)_1}{(W/L)_2} \rightarrow 0$ , it implies that PMOS transistor is much

stronger than NMOS. Therefore, as  $V_{in}$  increases from 0V, the output of inverter remains at  $V_{DD}$  until input reaches  $V_{DD} - |V_{TH2}|$ . At that point, PMOS is cutoff and  $V_{out}$  sharply drops to 0V.

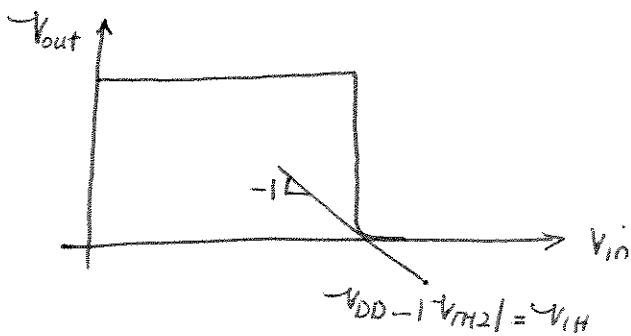


When " $a$ " approaches infinity, NMOS is prevailing and once input voltage hits the threshold voltage of NMOS, output voltage falls sharply to

0V.

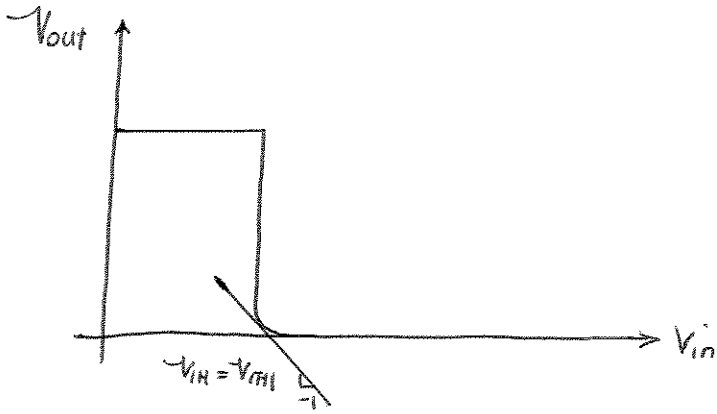

Note that the separation between  $V_{ih}$  and  $V_{il}$  depends on the slope of VTC in the transition region. If " $a$ " approaches either "0" or infinity, VTC exhibits infinite gain in its transition region. Therefore  $V_{il}$  and  $V_{ih}$  coincide.

32.

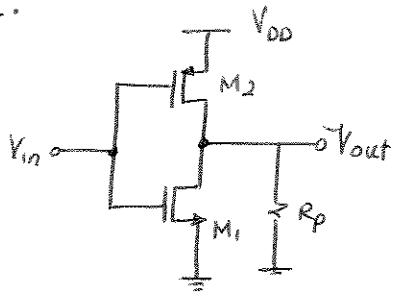

$$R_p = 2k$$

$$NML, NM_H = ?$$

$$\left(\frac{W}{L}\right)_1 = 3/0.18$$

$$\left(\frac{W}{L}\right)_2 = 5/0.18$$

To calculate  $NML$ ,  $M_1$  and  $M_2$  are assumed to be in the saturation and triode region respectively.

$$I_{D2} = I_{D1} + \frac{V_{out}}{R_p} \quad (V_{in} = V_{IL})$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - V_{in} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right] =$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 + \frac{V_{out}}{R_p} \quad (1)$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -1, \quad V_{in} = V_{IL}$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ -2(V_{DD} - V_{out}) - 2(V_{DD} - V_{in} - |V_{TH2}|) \frac{\partial V_{out}}{\partial V_{in}} + 2(V_{DD} - V_{out}) \frac{\partial V_{out}}{\partial V_{in}} \right] =$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1}) + \frac{1}{R_p} \frac{\partial V_{out}}{\partial V_{in}}$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{IL} - V_{TH1}) - \frac{1}{R_p} = \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2V_{OH} - V_{IL} - |V_{TH2}| - V_{DD} \right] \quad (2)$$

$$V_{OH} = 1.01 V_{IL} + 0.73$$

Replacing  $V_{out}$  in (1) with its equivalent versus  $V_{IL}$  obtained from (2) yields:

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - V_{IL} - |V_{TH2}|)(V_{DD} - 1.1V_{IL} - 0.73) - (V_{DD} - 1.1V_{IL} - 0.73)^2 \right] =$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{IL} - V_{TH1})^2 + \frac{1.1V_{IL} + 0.73}{R_p}$$

$$\frac{1}{2} \times 50 \times 10^{-6} \times \frac{5}{0.18} \left[ 2(1.8 - V_{IL} - 0.5)(1.8 - 1.1V_{IL} - 0.73) - (1.8 - 1.1V_{IL} - 0.73)^2 \right] =$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \frac{3}{0.18} (V_{IL} - 0.4)^2 + \frac{1.1V_{IL} + 0.73}{2000}$$

$$-52.5 \times 10^{-3} V_{IL} - 0.6195 V_{IL} + 0.229875 = 0$$

$$\boxed{V_{IL} = NML = 0.36 \text{ V}} < V_{TH1} \quad \text{NOT ACCEPTABLE!}$$

This is less than threshold voltage of  $M_1$ ; therefore, this answer is not acceptable. It means that  $M_1$  is off and should be left out in this calculation.

$$I_{D1} = 0, \quad I_{D2} = \frac{V_{out}}{R_p}$$

$$\mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2V_{OH} - V_{IL} - |V_{TH2}| - V_{DD} \right] = -\frac{1}{R_p}$$

$$50 \times 10^{-6} \times \frac{5}{0.18} \times \left[ 2V_{OH} - V_{IL} - 0.5 - 1.8 \right] = -\frac{1}{2000}$$

$$\boxed{V_{OH} = V_{out} = 0.5V_{IL} + 0.97} \quad (3)$$

$$\frac{1}{2} \times 50 \times 10^{-6} \times \frac{5}{0.18} \times \left[ 2(1.8 - V_{IL} - 0.5)(1.8 - 0.5V_{IL} - 0.97) - (1.8 - 0.5V_{IL} - 0.97)^2 \right] =$$

$$\frac{0.5V_{IL} + 0.97}{2000}$$

$$0.1875 V_{IL}^2 - 0.6225 V_{IL} + 0.192675 = 0$$

$$\boxed{V_{IL} = NML = 0.345 \text{ V}}$$

To determine  $NM_H$ ,  $M_1$  and  $M_2$  are assumed to operate in the triode and saturation region respectively.

$$I_{D2} = I_{D1} + \frac{V_{out}}{R_p} \quad (V_{in} = V_{IH})$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{TH1}) V_{out} - V_{out}^2 \right] + \frac{V_{out}}{R_p} \quad (4)$$

$$-\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|) = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2V_{out} + 2(V_{in} - V_{TH1}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] + \frac{\partial V_{out}}{\partial V_{in}} \frac{1}{R_p}$$

$$-\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|) = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ V_{out} - V_{in} + V_{TH1} + V_{out} \right] - \frac{1}{R_p}$$

$$-50 \times 10^{-6} \times \frac{5}{0.18} \times (1.8 - V_{in} - 0.5) = 100 \times 10^{-6} \times \frac{3}{0.18} \times (2V_{out} - V_{in} + 0.4) - \frac{1}{2000}$$

$$\boxed{V_{out} = \frac{0.1V_{in} + 0.59}{1.2}} \quad (5)$$


Combining equs (4) and (5) yields:

$$\frac{1}{2} \times 50 \times 10^{-6} \times \frac{5}{0.18} (1.8 - V_{in} - 0.5)^2 = \frac{1}{2} \times 100 \times 10^{-6} \times \frac{3}{0.18} \left[ 2(V_{in} - 0.4) \frac{0.1V_{in} + 0.59}{1.2} - \frac{(0.1V_{in} + 0.59)^2}{1.2^2} \right] + \frac{0.1V_{in} + 0.59}{1.2 \times 2000}$$

$$-0.291 V_{in}^2 + 1.3182 V_{in} - 0.75531 = 0$$

$$V_{in} = V_{IH} = 0.673 \text{ V} \rightarrow \boxed{NM_H = V_{DD} - V_{IH} = 1.127 \text{ V}}$$

33.

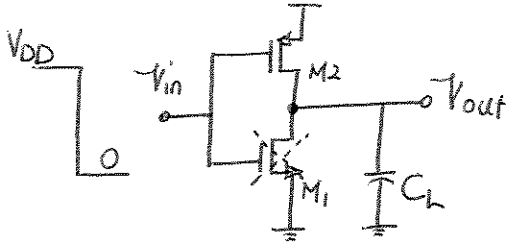

$$V_{out}(t=0) = 0$$

$$(W/L)_2 = 6/0.18$$

$$C_L = 50 \text{ fF}$$

$0 < V_{out} < |V_{TH2}|$ ;  $M_2$  in the saturation

$$C_L \frac{dV_{out}}{dt} = I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 = \frac{1}{2} \times 50 \times 10^{-6} \times \frac{6}{0.18} (1.8 - 0.5)^2 = 1.4 \times 10^{-3} \text{ A}$$

$$V_{out}(t) = \frac{I_{D2}}{C_L} \times t$$

$$|V_{TH2}| = \frac{I_{D2}}{C_L} \cdot T_1 \rightarrow T_1 = \frac{C_L \times |V_{TH2}|}{I_{D2}} = 50 \times 10^{-15} \times \frac{1.4 \times 10^{-3}}{1.4 \times 10^{-3}} \times 0.5$$

$$T_1 = 17.75 \text{ pS}$$

$|V_{TH2}| < V_{out} < V_{DD}/2$ ,  $M_2$  in triode

$$C_L \frac{dV_{out}}{dt} = I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - |V_{TH2}|)(-V_{out} + V_{DD}) - (V_{DD} - V_{out})^2 \right]$$

$$\frac{dV_{out}}{2(V_{DD} - |V_{TH2}|)(-V_{out} + V_{DD}) - (V_{DD} - V_{out})^2} = \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 dt$$

$$\frac{1}{(V_{DD} - V_{out}) \left[ 2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out}) \right]} = \frac{1}{2(V_{DD} - |V_{TH2}|) \left[ \frac{1}{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})} + \frac{1}{V_{DD} - V_{out}} \right]}$$



$$\frac{1}{2(V_{DD} - |V_{TH2}|)} \left[ \frac{dV_{out}}{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})} + \frac{dV_{out}}{V_{DD} - V_{out}} \right] = \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left( \frac{W}{L} \right)_2 dt$$

$$\ln \frac{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})}{V_{DD} - V_{out}} = \mu_p \frac{C_{ox}}{C_L} \left( \frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|) t + C$$

$$\frac{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})}{V_{DD} - V_{out}} = K \cdot \exp \left[ \mu_p \frac{C_{ox}}{C_L} \left( \frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|) t \right]$$

Time origin is assumed to be at  $t = T_1 = 17.75 \mu s$

$$V_{out}(t=0) = |V_{TH2}| \rightarrow K = 1$$

$$\frac{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})}{V_{DD} - V_{out}} = e^{\mu_p \frac{C_{ox}}{C_L} \left( \frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|) t}$$

$$\begin{aligned} \text{(a) } V_{out} = V_{DD}/2 \quad T_2 &= \frac{\ln(3 - 4|V_{TH2}|/V_{DD})}{\mu_p \frac{C_{ox}}{C_L} \left( \frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|)} \\ &= \frac{\ln(3 - 4 \times 0.5/1.8)}{50 \times 10^{-6} \times \frac{1}{50 \times 10^{-75}} \times \frac{6}{0.18} \times (1.8 - 0.5)} \end{aligned}$$

$$T_2 = 1.467 \times 10^{-11}$$

$$T_0 \rightarrow V_{DD/2} = T_1 + T_2 = 17.75 + 14.67$$

$$T_0 \rightarrow V_{DD/2} = 32.43 \mu s$$

34.  $|V_{TH2}| < V_{out} < 0.95V_{DD}$   $M_2$  in Triode

$$\frac{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})}{V_{DD} - V_{out}} = e^{\mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|) t}$$

$$\begin{aligned} \textcircled{a} V_{out} = 0.95V_{DD}, \quad T_2 &= \frac{\ln(39 - 40|V_{TH2}|/V_{DD})}{\mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \\ &= \frac{\ln(39 - 40 \times 0.5/1.8)}{50 \times 10^{-6} \times \frac{1}{50 \times 10^{-15}} \times \frac{6}{0.18} \times (1.8 - 0.5)} \end{aligned}$$

$$T_2 = 7.68 \times 10^{-11}$$


$T_1 = 17.75 \mu s$  from previous problem

$$T_{0 \rightarrow 0.95V_{DD}} = T_1 + T_2 = 17.75 + 76.8$$

$$T_{0 \rightarrow 0.95V_{DD}} = 94.55 \mu s$$

$$(T_{0 \rightarrow 0.95V_{DD}}) / (T_{0 \rightarrow V_{DD}/2}) \approx 3$$

35.

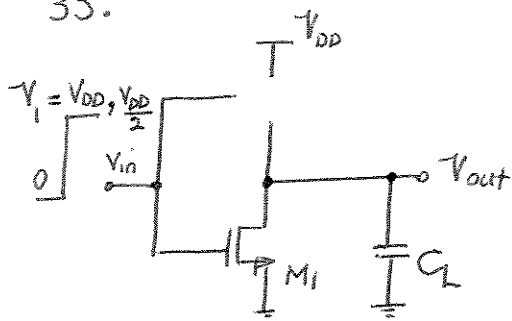

$$V_{out}(t=0) = V_{DD}$$

$$C_L = 30 \text{ fF}$$

$$\left(\frac{W}{L}\right)_1 = 1/0.18$$


$$T_{V_{DD} \rightarrow V_{DD/2}} = ?$$

$$\left(\frac{W}{L}\right)_2 = \text{Not necessary}$$

$$V_i = V_{DD} \text{ or } V_{DD/2}$$

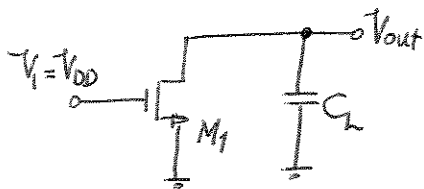(a)  $V_i = V_{DD}$

$$V_{DD} - V_{TH1} \leq V_{out} \leq V_{DD} \quad M_1 \text{ Saturation}$$



$$\frac{V_{DD}}{2} \leq V_{out} \leq V_{DD} - V_{TH1} \quad M_1 \text{ Triode}$$

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})^2 = -\frac{1}{2} \times 100 \times 10^{-6} \times \frac{1}{0.18} (1.8 - 0.4)^2 = 5.44 \times 10^{-4} \text{ A}$$

$$dV_{out} = -\frac{I_{D1}}{C_L} \cdot dt$$

$$V_{out}(t) - V_{DD} = -\frac{I_{D1}}{C_L} t \rightarrow V_{out}(t) = V_{DD} - \frac{I_{D1}}{C_L} t$$

$$T_{V_{DD} \rightarrow V_{DD} - V_{TH1}} = \frac{V_{TH1} \times C_L}{I_{D1}} = \frac{0.4 \times 30 \times 10^{-15}}{5.44 \times 10^{-4}} = 2.2 \times 10^{-11} \text{ s}$$

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - V_{TH1})V_{out} - V_{out}^2 \right]$$

$$\frac{dV_{out}}{2(V_{DD} - V_{TH1})V_{out} - V_{out}^2} = -\frac{1}{2} \mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 dt$$

$$\frac{1}{[2(V_{DD} - V_{TH1}) - V_{out}]V_{out}} = \frac{1}{2(V_{DD} - V_{TH1})} \left[ \frac{1}{2(V_{DD} - V_{TH1}) - V_{out}} + \frac{1}{V_{out}} \right]$$

$$\frac{1}{2(V_{DD} - V_{TH1})} \left[ \frac{dV_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} + \frac{dV_{out}}{V_{out}} \right] = -\frac{1}{2} \mu_n \frac{C_{ox}}{C_L} \left( \frac{W}{L} \right)_1 dt$$

$$-\ln \left[ 2(V_{DD} - V_{TH1}) - V_{out} \right] + \ln V_{out} = -\mu_n \frac{C_{ox}}{C_L} \left( \frac{W}{L} \right)_1 (V_{DD} - V_{TH1}) t + C$$

$$\frac{V_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} = K \cdot \exp \left[ -\mu_n \frac{C_{ox}}{C_L} \left( \frac{W}{L} \right)_1 (V_{DD} - V_{TH1}) t \right]$$

$$V_{out}(t=0) = V_{DD} - V_{TH1} \quad \text{Note that time origin is assumed to be } 2.2 \times 10^{-11}$$

$$K = 1 \rightarrow$$

$$\frac{V_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} = e^{-\mu_n \frac{C_{ox}}{C_L} \left( \frac{W}{L} \right)_1 (V_{DD} - V_{TH1}) t}$$

$$V_{out} = \frac{V_{DD}}{2} \rightarrow \frac{V_{DD}/2}{2(V_{DD} - V_{TH1}) - V_{DD}/2} = e^{-\mu_n \frac{C_{ox}}{C_L} \left( \frac{W}{L} \right)_1 (V_{DD} - V_{TH1}) T_{(V_{DD} - V_{TH1}) \rightarrow V_{DD}/2}}$$


$$T_{(V_{DD} - V_{TH1}) \rightarrow V_{DD}/2} = \frac{\ln \left( 3 - \frac{2V_{TH1}}{V_{DD}} \right)}{\mu_n \frac{C_{ox}}{C_L} \left( \frac{W}{L} \right)_1 (V_{DD} - V_{TH1})}$$

$$= \frac{\ln(3 - 4 \times 0.4 / 1.8)}{100 \times 10^{-6} \times \frac{1}{30 \times 10^{-15}} \times \frac{1}{0.18} \times (1.8 - 0.4)} = 2.88 \times 10^{-11} \text{ s}$$

$$T_{V_{DD} \rightarrow V_{DD}/2} = T_{V_{DD} \rightarrow V_{DD} - V_{TH1}} + T_{(V_{DD} - V_{TH1}) \rightarrow V_{DD}/2}$$

$$T_{V_{DD} \rightarrow V_{DD}/2} = 5 \times 10^{-11} = 50.86 \text{ ps}$$

(b)  $V_i = V_{DD}/2$

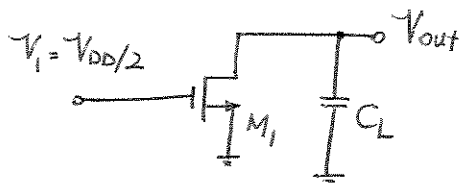

$V_{DD}/2 - V_{TH1} < V_{out} < V_{DD}$   $M_1$  in Saturation

$V_{DD}/2 < V_{out} < V_{DD}$   $M_1$  in Saturation

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD}/2 - V_{TH1})^2 = -\frac{1}{2} \times 100 \times 10^{-6} \times \frac{1}{0.18} (0.9 - 0.4)^2$$


$$= 6.944 \times 10^{-5}$$

$$V_{out}(t) = V_{DD} - \frac{I_{D1}}{C_L} \times t$$

$$V_{DD}/2 = V_{DD} - \frac{I_{D1}}{C_L} \times T_{(V_{DD} \rightarrow V_{DD}/2)} \Rightarrow T_{(V_{DD} \rightarrow V_{DD}/2)} = \frac{(V_{DD}/2) \times C_L}{I_{D1}}$$

$$T_{(V_{DD} \rightarrow V_{DD}/2)} = 3.888 \times 10^{-10}$$

36.

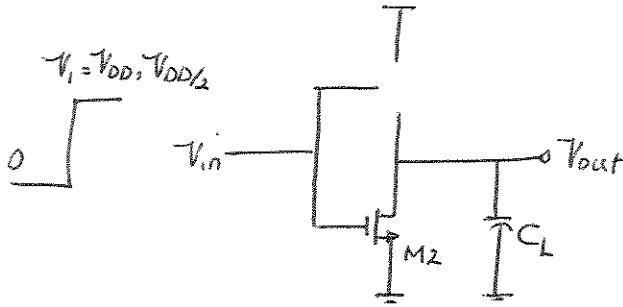

$$V_{out}(0) = V_{DD}$$

$$\left(\frac{W}{L}\right)_1 = 1/0.18$$

$$C_L = 30 \text{ fF}$$

$$T_{V_{DD}} \rightarrow 0.05 V_{DD} = ?$$

(a)  $V_i = V_{DD}$       $V_{DD} - V_{TH1} < V_{out} < V_{DD}$   $M_1$  in Saturation

$0.05 V_{DD} < V_{out} < V_{DD} - V_{TH1}$   $M_1$  in Triode

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})^2 = -\frac{1}{2} \times 100 \times 10^{-6} \times \frac{1}{0.18} (1.8 - 0.4)^2 = 5.44 \times 10^{-4} \text{ A}$$

$$V_{out}(t) = V_{DD} - \frac{I_{D1}}{C_L} \times t$$

$$T_{V_{DD} \rightarrow V_{DD} - V_{TH1}} = \frac{V_{TH1} \times C_L}{I_{D1}} = \frac{0.4 \times 30 \times 10^{-15}}{5.44 \times 10^{-4}} = 2.2 \times 10^{-11} \text{ S}$$

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - V_{TH1}) V_{out} - V_{out}^2 \right]$$

$$\frac{1}{2(V_{DD} - V_{TH1})} \left[ \frac{dV_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} + \frac{dV_{out}}{V_{out}} \right] = -\frac{1}{2} \mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 dt$$

$V_{out}(t=0) = V_{DD} - V_{TH1}$  Note that time origin is assumed to be  $2.2 \times 10^{-11} \text{ S}$

$$\frac{V_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} = e^{-\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1}) t}$$

$$V_{out} = 0.05V_{DD}$$

$$\frac{0.05V_{DD}}{2(V_{DD}-V_{TH1})-0.05V_{DD}} = e^{-\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 (V_{DD}-V_{TH1}) T_{(V_{DD}-V_{TH1}) \rightarrow 0.05V_{DD}}}$$

$$T_{(V_{DD}-V_{TH1}) \rightarrow 0.05V_{DD}} = \frac{\ln(39 - 40V_{TH1}/V_{DD})}{\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 (V_{DD}-V_{TH1})}$$

$$= \frac{\ln(39 - 40 \times 0.4 / 1.8)}{100 \times 10^{-6} \times \frac{1}{-15} \times \frac{1}{30 \times 10} (1.8 - 0.4)}$$

$$T_{(V_{DD}-V_{TH1}) \rightarrow 0.05V_{DD}} = 131.33 \text{ pS}$$

$$T_{(V_{DD} \rightarrow 0.05V_{DD})} = T_{(V_{DD} \rightarrow V_{DD}-V_{TH1})} - T_{(V_{DD}-V_{TH1}) \rightarrow 0.05V_{DD}}$$

$$= 2.2 \times 10^{-11} + 1.3133 \times 10^{-10}$$

$$T_{(V_{DD} \rightarrow 0.05V_{DD})} = 153.33 \text{ pS}$$

(b)  $V_i = V_{DD}/2$   $V_{DD}/2 - V_{TH1} < V_{out} < V_{DD}$   $M_1$  in Saturation

$0.05V_{DD} < V_{out} < V_{DD}/2 - V_{TH1}$   $M_1$  in Triode

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD}/2 - V_{TH1})^2 = -\frac{1}{2} \times 100 \times 10^{-6} \times \frac{1}{0.18} (0.9 - 0.4)^2$$

$$= 6.944 \times 10^{-5} \text{ A}$$

$$V_{out}(t) = V_{DD} - \frac{I_{D1}}{C_L} \times t$$

$$V_{DD/2} - V_{TH1} = V_{DD} - \frac{I_{D1}}{C_L} T_{(V_{DD} \rightarrow V_{DD/2} - V_{TH1})}$$

$$T_{(V_{DD} \rightarrow V_{DD/2} - V_{TH1})} = \frac{(V_{DD/2} + V_{TH1}) \times C_L}{I_{D1}}$$

$$T_{(V_{DD} \rightarrow V_{DD/2} - V_{TH1})} = 5.616 \times 10^{-10}$$

for  $0.05V_{DD} < V_{out} < V_{DD/2} - V_{TH1}$

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD/2} - V_{TH1})V_{out} - V_{out}^2 \right]$$

$$\frac{V_{out}}{2(V_{DD/2} - V_{TH1}) - V_{out}} = e^{-\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 (V_{DD/2} - V_{TH1}) t}$$

$$V_{out} = 0.05V_{DD} \rightarrow \frac{0.05V_{DD}}{2(V_{DD/2} - V_{TH1}) - 0.05V_{DD}} = e^{-\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 (V_{DD/2} - V_{TH1}) \times T}$$

$$\begin{aligned} T_{(V_{DD/2} - V_{TH1} \rightarrow 0.05V_{DD})} &= \frac{\ln(19 - 40V_{TH1}/V_{DD})}{\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 (V_{DD/2} - V_{TH1})} \\ &= \frac{\ln(19 - 40 \times 0.4 / 1.8)}{100 \times 10^{-6} \times \frac{1}{30 \times 10^{-15}} \times \frac{1}{0.18} (0.9 - 0.4)} \\ &= 2.5 \times 10^{-10} \end{aligned}$$

$$T_{(V_{DD} \rightarrow 0.05V_{DD})} = T_{(V_{DD} \rightarrow V_{DD/2} - V_{TH1})} + T_{(V_{DD/2} - V_{TH1} \rightarrow 0.05V_{DD})}$$


$$T_{(V_{DD} \rightarrow 0.05V_{DD})} = 5.616 \times 10^{-10} + 2.5 \times 10^{-10} = 811.5 \text{ pS}$$



By decreasing  $V_{in}$  from  $V_{DD}$  to  $V_{DD}/2$ , the time it takes the output to reach  $0.05V_{DD}$  will be 5.3 time larger!

$$\frac{T(V_{DD} \rightarrow 0.05V_{DD})(V_{in} = V_{DD})}{T(V_{DD} \rightarrow 0.05V_{DD})(V_{in} = V_{DD}/2)} = \frac{811.5 \text{ p}}{153.33 \text{ p}} \approx 5.3$$

37.

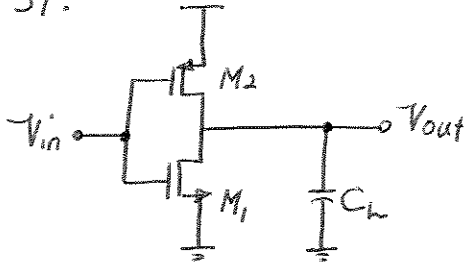

$$\left(\frac{W}{L}\right)_1 = 1/0.18$$

$$\left(\frac{W}{L}\right)_2 = 3/0.18$$

$$C_L = 80 \text{ fF}$$

$$T_{PHL}, T_{PLH} = ?$$

To calculate  $T_{PLH}$ 

$$0 < V_{out} < |V_{TH2}| \quad M_2 \text{ in Saturation}$$

$$|V_{TH2}| < V_{out} < V_{DD}/2 \quad M_2 \text{ in Triode}$$

$$|I_{D2}| = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2$$

$$V_{out}(t) = \frac{|I_{D2}|}{C_L} t$$

$$= \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2 t$$

$$V_{out}(T_{PLH1}) = |V_{TH2}|$$

$$T_{PLH1} = \frac{|V_{TH2}| \times C_L}{\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2}$$

for  $M_2$  operating in Triode region

$$C_L \frac{dV_{out}}{dt} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right]$$

$$\frac{dV_{out}}{2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2} = \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 dt$$

Defining  $V_{DD} - V_{out} = u$  and noting that  $\int \frac{du}{au - u^2} = \frac{1}{a} \ln \frac{u}{a-u}$ ,

$$\frac{-1}{2(V_{DD} - |V_{TH2}|)} \ln \frac{V_{DD} - V_{out}}{V_{DD} - 2|V_{TH2}| + V_{out}} \left| \begin{array}{l} V_{out} = V_{DD}/2 \\ V_{out} = |V_{TH2}| \end{array} \right. = \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 T_{PLH2}$$

$$T_{PLH2} = \frac{C_L}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \ln \left( 3 - 4 \frac{|V_{TH2}|}{V_{DD}} \right)$$

$$T_{PLH} = T_{PLH1} + T_{PLH2} = \frac{C_L}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \left[ \frac{2|V_{TH2}|}{V_{DD} - |V_{TH2}|} + \ln \left( 3 - 4 \frac{|V_{TH2}|}{V_{DD}} \right) \right]$$

$$T_{PLH} = \frac{80 \times 10^{-15}}{50 \times 10^{-6} \times \frac{3}{0.18} (1.8 - 0.5)} \left[ \frac{2 \times 0.5}{1.8 - 0.5} + \ln \left( 3 - 4 \frac{0.5}{1.8} \right) \right]$$

$$T_{PLH} = 1.0377 \times 10^{-10}$$

To calculate  $T_{PHL}$

$V_{DD} - V_{TH1} < V_{out} < V_{DD}$   $M_1$  in Saturation

$V_{DD}/2 < V_{out} < V_{DD} - V_{TH1}$   $M_1$  in Triode

$$T_{PHL1} = \frac{-\Delta V_{out} \times C_L}{I_{D1}} = \frac{V_{TH1} \times C_L}{\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})^2}$$

after this point in time.

$$C_L \frac{dV_{out}}{dt} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - V_{TH1}) V_{out} - V_{out}^2 \right]$$

$$V_{out}(t=0) = V_{DD} - V_{TH1}$$

$$\frac{1}{2(V_{DD} - V_{TH1})} \ln \frac{V_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} \left| \begin{array}{l} V_{out} = V_{DD}/2 \\ V_{out} = V_{DD} - V_{TH1} \end{array} \right. = -\frac{1}{2} \mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 T_{HL2}$$

$$T_{PHL2} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \times \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}}\right)$$

$$T_{PHL} = T_{PHL1} + T_{PHL2} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \times \left[ \frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}}\right) \right]$$

$$T_{PHL} = \frac{80 \times 10^{-15}}{100 \times 10^{-6} \times \frac{1}{0.18} (1.8 - 0.4)} \times \left[ \frac{2 \times 0.4}{1.8 - 0.4} + \ln \left(3 - 4 \frac{0.4}{1.8}\right) \right]$$

$$T_{PHL} = 1.3563 \times 10^{-10}$$

$$38. \quad V_{DD} = 1.8 + 1.8 \times 0.1 = 1.98$$

$$T_{PLH} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \left[ \frac{2|V_{TH2}|}{V_{DD} - |V_{TH2}|} + \ln \left( 3 - 4 \frac{|V_{TH2}|}{V_{DD}} \right) \right]$$

$$= \frac{80 \times 10^{-15}}{50 \times 10^{-6} \times \frac{3}{0.18} \times (1.98 - 0.5)} \left[ \frac{2 \times 0.5}{1.98 - 0.5} + \ln \left( 3 - 4 \times \frac{0.5}{1.98} \right) \right]$$

$$T_{PLH} = 8.846 \times 10^{-11}$$

$$\text{Decrease in } T_{PLH} = \left| \frac{8.846 \times 10^{-11} - 1.0377 \times 10^{-10}}{1.0377 \times 10^{-10}} \right| \times 100$$

$$= 14.75\%$$

$$T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[ \frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left( 3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right]$$

$$= \frac{80 \times 10^{-15}}{100 \times 10^{-6} \times \frac{1}{0.18} \times (1.98 - 0.4)} \left[ \frac{2 \times 0.4}{1.98 - 0.4} + \ln \left( 3 - 4 \frac{0.4}{1.98} \right) \right]$$

$$T_{PHL} = 1.1767 \times 10^{-10}$$

$$\text{Decrease in } T_{PHL} = \left| \frac{1.1767 \times 10^{-10} - 1.3563 \times 10^{-10}}{1.3563 \times 10^{-10}} \right| \times 100$$

$$= 13.24\%$$

$$39. V_{DD} = 0.9 \text{ V}$$

$$C_L \frac{dV_{out}}{dt} = I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2$$

$$T_{PLH} = \frac{\Delta V_{out} \times C_L}{I_{D2}} = \frac{(V_{DD}/2) \times C_L}{\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2}$$

$$= \frac{0.45 \times 80 \times 10^{-15}}{\frac{1}{2} \times 50 \times 10^{-6} \times \frac{3}{0.18} \times (0.9 - 0.5)^2}$$

$$T_{PLH} = 5.4 \times 10^{-10} = 540 \text{ pS}$$

$$T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[ \frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left( 3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right]$$

$$= \frac{80 \times 10^{-15}}{100 \times 10^{-6} \times \frac{1}{0.18} \times (0.9 - 0.4)} \times \left[ \frac{2 \times 0.4}{0.9 - 0.4} + \ln \left( 3 - 4 \frac{0.4}{0.9} \right) \right]$$

$$T_{PHL} = 5.186 \times 10^{-10} = 518.6 \text{ pS}$$

$$\text{Increase in } T_{PLH} = \left| \frac{5.4 \times 10^{-10} - 1.0377 \times 10^{-10}}{1.0377 \times 10^{-10}} \right| \times 100$$

$$= 420.38\%$$

$$\text{Increase in } T_{PHL} = \left| \frac{5.186 \times 10^{-10} - 1.3563 \times 10^{-10}}{1.3563 \times 10^{-10}} \right| \times 100$$

$$= 282.36\%$$

$$40. T_{PLH} = T_{PHL} = 80 \text{ ps}$$

$$C_L = 50 \text{ fF}$$

$$\left(\frac{W}{L}\right)_1, \left(\frac{W}{L}\right)_2 = ?$$

$$T_{PLH} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \left[ \frac{2|V_{TH2}|}{V_{DD} - |V_{TH2}|} + \ln\left(3 - 4 \frac{|V_{TH2}|}{V_{DD}}\right) \right]$$

$$80 \times 10^{-12} = \frac{50 \times 10^{-15}}{50 \times 10^{-6} \times (1.8 - 0.5) \times \left(\frac{W}{L}\right)_2} \times \left[ \frac{2 \times 0.5}{1.8 - 0.5} + \ln\left(3 - 4 \times \frac{0.5}{1.8}\right) \right]$$

$$\boxed{\left(\frac{W}{L}\right)_2 = \frac{2.4}{0.18}}$$

$$T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \times \left[ \frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln\left(3 - 4 \frac{V_{TH1}}{V_{DD}}\right) \right]$$

$$80 \times 10^{-12} = \frac{50 \times 10^{-15}}{100 \times 10^{-6} \times (1.8 - 0.4) \times \left(\frac{W}{L}\right)_1} \times \left[ \frac{2 \times 0.4}{1.8 - 0.4} + \ln\left(3 - 4 \times \frac{0.4}{1.8}\right) \right]$$

$$\boxed{\left(\frac{W}{L}\right)_1 = \frac{1}{0.18}}$$

41.

$$T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[ \frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln\left(3 - 4 \frac{V_{TH1}}{V_{DD}}\right) \right]$$

$$V_{TH1} = 0.4$$

$$\frac{2V_{TH1}}{V_{DD} - V_{TH1}} = \ln\left(3 - 4 \frac{V_{TH1}}{V_{DD}}\right) \rightarrow V_{DD} = V_{TH1} \left[ 1 + \frac{2}{\ln\left(3 - 4 \frac{V_{TH1}}{V_{DD}}\right)} \right]$$

$$V_{TH1} = 0.4 \rightarrow \boxed{V_{DD} = 1.57}$$

$$\frac{2V_{TH1}}{V_{DD} - V_{TH1}} = 0.1 \times \ln\left(3 - 4 \frac{V_{TH1}}{V_{DD}}\right) \rightarrow V_{DD} = V_{TH1} \left[ 1 + \frac{20}{\ln\left(3 - 4 \frac{V_{TH1}}{V_{DD}}\right)} \right]$$

$$V_{TH1} = 0.4 \rightarrow \boxed{V_{DD} = 8.16}$$



$$42. \left(\frac{W}{L}\right)_1 = 1/0.18$$

$$T_{PHL} = 100 \text{ pS}$$

$$C_L = 80 \text{ fF}$$

$$V_{DD} = ?$$

$$T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[ \frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln\left(3 - 4\frac{V_{TH1}}{V_{DD}}\right) \right]$$

$$100 \times 10^{-12} = \frac{80 \times 10^{-15}}{100 \times 10^{-6} \times \frac{1}{0.18} \times (V_{DD} - 0.4)} \times \left[ \frac{2 \times 0.4}{V_{DD} - 0.4} + \ln\left(3 - 4\frac{0.4}{V_{DD}}\right) \right]$$

$$V_{DD} = 0.4 + 1.44 \left[ \frac{0.8}{V_{DD} - 0.4} + \ln\left(3 - \frac{1.6}{V_{DD}}\right) \right]$$

$$\boxed{V_{DD} = 2.22}$$

43.  $T_{PHL} = 120 \text{ ps}$        $(W/L)_1 = ?$

$C_L = 90 \text{ fF}$        $V_{TH1} = ?$

$V_{DD} = 1.8$

$T_{PHL} = 160 \text{ ps}$        $T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[ \frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln\left(3 - 4\frac{V_{TH1}}{V_{DD}}\right) \right]$

$V_{DD} = 1.5 \text{ V}$

$C_L = 90 \text{ fF}$

$$120 \times 10^{-12} = \frac{90 \times 10^{-15}}{100 \times 10^{-6} \left(\frac{W}{L}\right)_1 (1.8 - V_{TH1})} \times \left[ \frac{2V_{TH1}}{1.8 - V_{TH1}} + \ln\left(3 - 4\frac{V_{TH1}}{1.8}\right) \right] \quad (1)$$

$$160 \times 10^{-12} = \frac{90 \times 10^{-15}}{100 \times 10^{-6} \left(\frac{W}{L}\right)_1 (1.5 - V_{TH1})} \times \left[ \frac{2V_{TH1}}{1.5 - V_{TH1}} + \ln\left(3 - 4\frac{V_{TH1}}{1.5}\right) \right] \quad (2)$$

Dividing Equations (1) and (2) yields:

$$0.75 = \frac{1.5 - V_{TH1}}{1.8 - V_{TH1}} \times \frac{\frac{2V_{TH1}}{1.8 - V_{TH1}} + \ln\left(3 - 4\frac{V_{TH1}}{1.8}\right)}{\frac{2V_{TH1}}{1.5 - V_{TH1}} + \ln\left(3 - 4\frac{V_{TH1}}{1.5}\right)}$$

$$V_{TH1} = 1.8 - \left(\frac{1.5 - V_{TH1}}{0.75}\right) \times \frac{\frac{2V_{TH1}}{1.8 - V_{TH1}} + \ln\left(3 - 4\frac{V_{TH1}}{1.8}\right)}{\frac{2V_{TH1}}{1.5 - V_{TH1}} + \ln\left(3 - 4\frac{V_{TH1}}{1.5}\right)}$$

This equation does not lead to a real value for  $V_{TH1}$  so we use another derivation

$$V_{TH1} = 0.45 \times \left\{ 3 - e^{\left[ 0.75 \frac{1.8 - V_{TH1}}{1.5 - V_{TH1}} \times \left[ \frac{2V_{TH1}}{1.5 - V_{TH1}} + \ln\left(3 - 4\frac{V_{TH1}}{1.5}\right) \right] - \frac{2V_{TH1}}{1.8 - V_{TH1}} \right]} \right\}$$

$$V_{TH1} = 0.39$$

$$\left(\frac{W}{L}\right)_1 = \frac{1.26}{0.18}$$

44.

$$T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[ \frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left( 3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right]$$

$\ln \left( 3 - 4 \frac{V_{TH1}}{V_{DD}} \right)$  is meaningless if  $V_{DD} < 4V_{TH1}/3$ .

Let's consider the case where  $V_{DD} = \frac{4}{3}V_{TH1}$ ; then,  $T_{PHL}$  is the time it takes

for the output to drop from  $V_{DD} = \frac{4}{3}V_{TH1}$  to  $\frac{V_{DD}}{2} = \frac{2}{3}V_{TH1}$ . However,


$$\left( V_{in}^0 = V_{DD} = \frac{4}{3}V_{TH1} \right) - \left( V_{out} = \frac{2}{3}V_{TH1} \right) = \frac{2}{3}V_{TH1} < V_{TH1}. \text{ In other words, } M_1$$

never enters the triode region in the region where  $T_{PHL}$  is calculated. The

logarithmic term is derived from equation in which  $M_1$  was assumed to be in

Triode region. Therefore the logarithmic term is meaningless for  $V_{DD} < \frac{4}{3}V_{TH1}$ .

45.

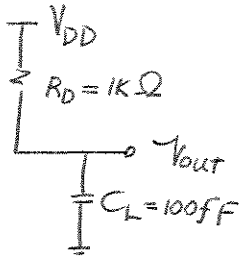

$$V_{R_D} = (V_{DD} - V_{out})$$

$$I_{R_D} = C_L \frac{dV_{out}}{dt}$$

$$P_{R_D}(t) = V_{R_D} \cdot I_{R_D} = C_L (V_{DD} - V_{out}) \frac{dV_{out}}{dt}$$

$$\begin{aligned} E_{R_D} &= \int_{t=0}^{\infty} P_{R_D}(t) dt = \int_{V_{out}=0}^{V_{DD}} (V_{DD} - V_{out}) dV_{out} = \frac{1}{2} C_L V_{DD}^2 \\ &= \frac{1}{2} \times 100 \times 10^{-15} \times (1.8)^2 \end{aligned}$$

$$E_{R_D} = 0.162 \mu J$$

46.  $10^6$  Gates

$$f = 2 \text{ GHz}$$

20% of gates switch in every clock cycle

$C_L = 20 \text{ fF}$  for each gate

$$P_{av} = ?$$

$$P_{av, \text{gate}} = f_{in} C_L V_{DD}^2$$

$$P_{av, \text{total}} = 0.2 \times 10^6 \times f_{in} C_L V_{DD}^2$$

$$= 0.2 \times 10^6 \times 2 \times 10^9 \times 20 \times 10^{-15} \times (1.8)^2$$

$$P_{av, \text{total}} = 25.92 \text{ W}$$

$$47. f = 2 \text{ GHz}$$

$5 \times 10^6$  Transistors with  $W = 1 \mu\text{m}$ ,  $L = 0.18 \mu\text{m}$ ,  $C_{ox} = 10 \text{ fF}/\mu\text{m}^2$

$$C_{\text{gate}} = WLC_{ox}$$

$$C_{\text{Load}} = 5 \times 10^6 C_{\text{gate}}$$

$$= 5 \times 10^6 WLC_{ox}$$

$$= 5 \times 10^6 \times 1 \mu\text{m} \times 0.18 \mu\text{m} \times 10 \text{ fF}/\mu\text{m}^2$$

$$C_{\text{Load}} = 9 \text{ pF}$$

$$P_{\text{av}} = f_{in} C_L V_{DD}^2$$

$$= 2 \times 10^9 \times 9 \times 10^{-9} \times (1.8)^2$$

$$P_{\text{av}} = 58.32 \text{ W}$$

48.

$$V_{DD} = V_{DD} + 0.1 V_{DD} = 1.98$$

$$\left(\frac{W}{L}\right)_1 = 2/0.18$$

$$\left(\frac{W}{L}\right)_2 = 4/0.18$$

$$I_{Peak} \Big|_{V_{DD}=1.8} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left(\frac{V_{DD}}{2} - V_{TH1}\right)^2 \left(1 + \lambda_1 \frac{V_{DD}}{2}\right)$$

$$= \frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{2}{0.18}\right) (0.9 - 0.4)^2$$

$$I_{Peak} \Big|_{V_{DD}=1.8} = 1.388 \times 10^{-4}$$

$$I_{Peak} \Big|_{V_{DD}=1.98} = \frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{2}{0.18}\right) (0.99 - 0.4)^2$$


$$I_{Peak} \Big|_{V_{DD}=1.98} = 1.9338 \times 10^{-4}$$

$$\text{Change in Crowbar Current} = \frac{1.9338 \times 10^{-4} - 1.388 \times 10^{-4}}{1.388 \times 10^{-4}}$$

$$\text{Change in Crowbar Current} = 39.24\%$$



49.

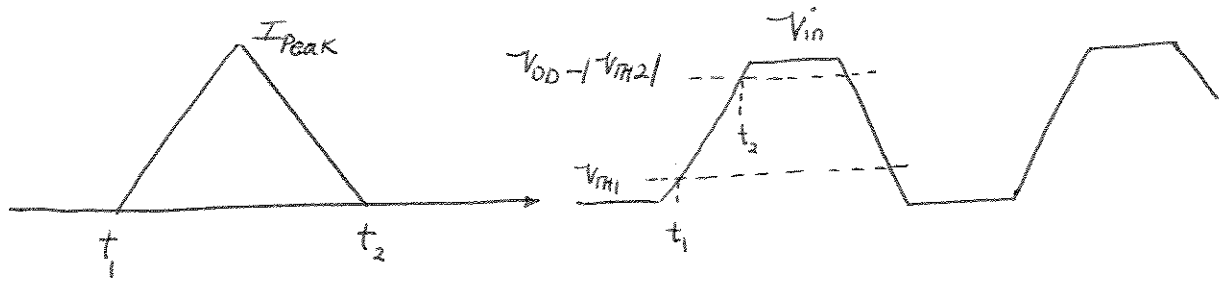

Total Energy drawn from  $V_{DD}$  during the interval  $[t_1, t_2]$  is:

$$E = V_{DD} \times I_{Peak} \times \frac{t_2 - t_1}{2}$$

In a periode the total energy is:

$$E_{tot} = 2 \times V_{DD} \times I_{Peak} \times \frac{t_2 - t_1}{2}$$

$$P_{av} = V_{DD} I_{Peak} (t_2 - t_1) f_1$$

$$\text{Slope of input voltage} = \frac{0.9V_{DD} - 0.1V_{DD}}{t_r} = \frac{0.8V_{DD}}{t_r}$$


$$(t_2 - t_1) = \frac{(V_{DD} - V_{TH1} - |V_{TH2}|) \times t_r}{0.8V_{DD}}$$

$$P_{av} = V_{DD} \times \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left(\frac{V_{DD}}{2} - V_{TH1}\right)^2 \times \frac{(V_{DD} - V_{TH1} - |V_{TH2}|)}{0.8V_{DD}} t_r \times f_1$$

$$P_{av} = \frac{1}{1.6} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left(\frac{V_{DD}}{2} - V_{TH1}\right)^2 (V_{DD} - V_{TH1} - |V_{TH2}|) f_1 \cdot t_r$$

$$P_{av} = 1.4 \times 10^{-5} \left(\frac{W}{L}\right)_1 \times t_r \times f_1$$


50.

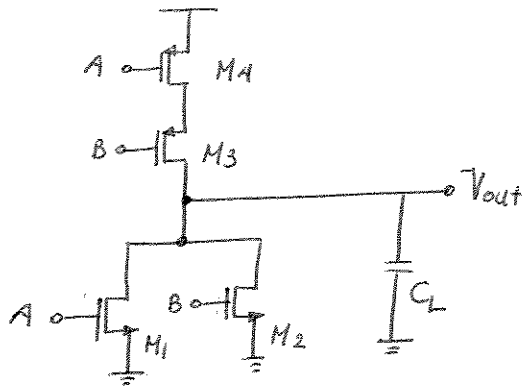

$$C_L = 20 \text{ fF}$$

$$f_i = 500 \text{ MHz}$$

$$P_{av} = ?$$


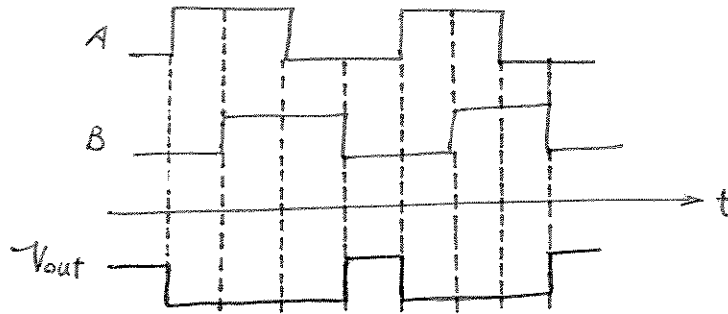


$$P_{av} = f_{in} C_L V_{DD}^2$$

$$= 500 \times 10^6 \times 20 \times 10^{-15} \times (1.8)^2$$

$$P_{av} = 3.24 \times 10^{-5} \text{ W}$$

51.

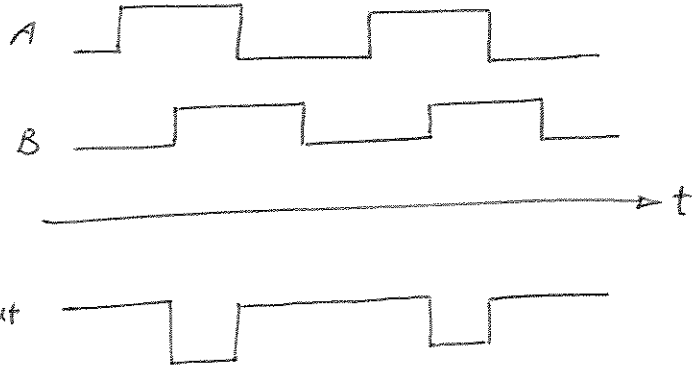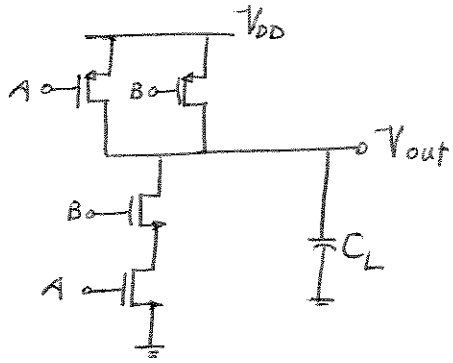


$$P_{av} = f_{in} C_L V_{DD}^2$$


$$= 500 \times 10^6 \times 20 \times 10^{-15} \times (1.8)^2$$

$$P_{av} = 3.24 \times 10^{-5} \text{ W}$$


52.

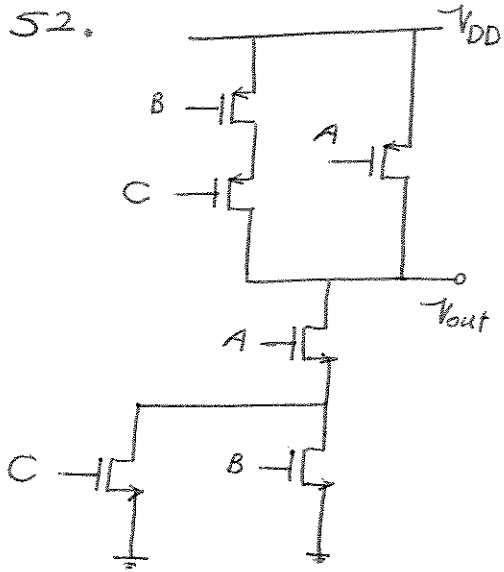


$$V_{out} = \overline{(B+C)A}$$

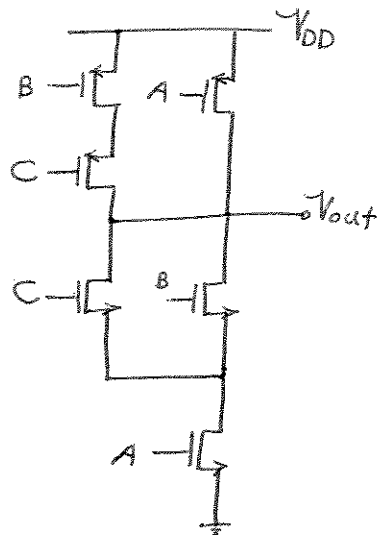


$$V_{out} = \overline{(B+C).A}$$

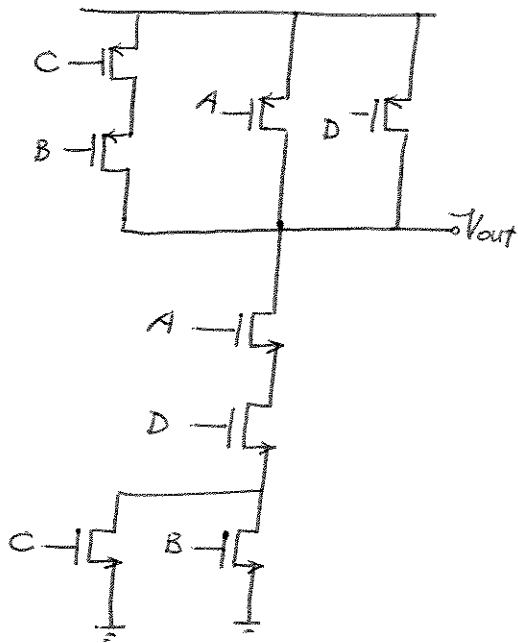

$$V_{out} = \overline{(B+C)D.A}$$

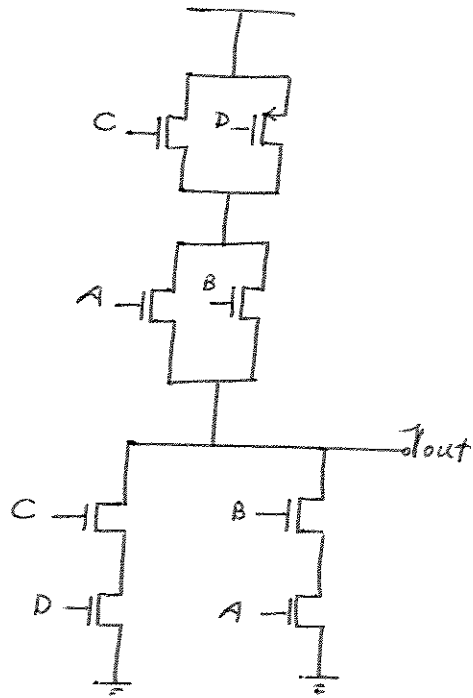


$$V_{out} = \overline{A.B + C.D}$$

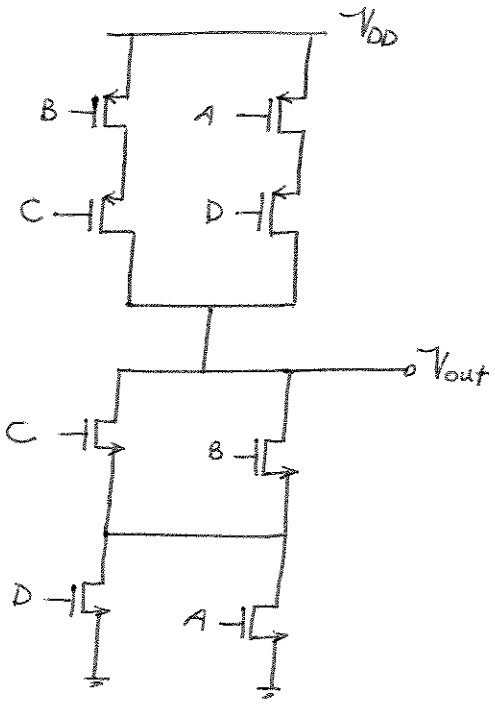

$$V_{out} = \overline{(A+D) \cdot (B+C)}$$

53.

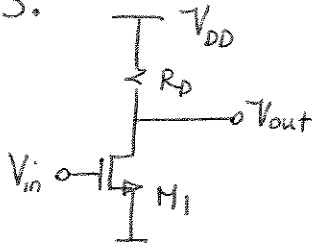

$$P_{\text{static}} = 0.5 \text{ mW}$$

$$V_{OL} = 100 \text{ mV}$$

$$\frac{(V_{DD} - V_{OL})^2}{R_D} + V_{OL} \times \frac{V_{DD} - V_{OL}}{R_D} = 0.5 \times 10^{-3}$$

$$\frac{(1.8 - 0.1)^2}{R_D} + 0.1 \times \frac{1.8 - 0.1}{R_D} = 0.5 \times 10^{-3}$$

$$\frac{1}{R_D} \times 3.06 = 0.5 \times 10^{-3}$$


$$\boxed{R_D = 6120 \Omega}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - V_{TH1})V_{OL} - V_{OL}^2 \right] = \frac{V_{DD} - V_{OL}}{R_D}$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{W}{L}\right)_1 \times \left[ 2(1.8 - 0.4)0.1 - 0.1^2 \right] = \frac{1.8 - 0.1}{6120}$$

$$\boxed{\left(\frac{W}{L}\right)_1 = \frac{3.7}{0.18}}$$

54.

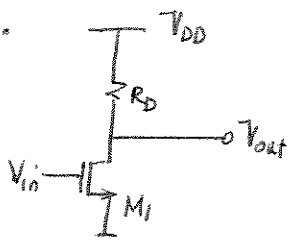

$$P_{\text{static}} = 0.25 \text{ mW}$$

$$NM_L = 600 \text{ mV}$$

$$\text{Small signal gain} = -g_m R_D$$

$$g_m = \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_{TH})$$

$$\mu_n C_{ox} \frac{W}{L} (V_{IL} - V_{TH}) R_D = 1$$

$$V_{IL} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right) R_D} + V_{TH}$$

$$NM_L = V_{IL} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right) R_D} + V_{TH}$$

$$\frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right) R_D} = (NM_L - V_{TH}) \rightarrow \left(\frac{W}{L}\right) R_D = \frac{1}{\mu_n C_{ox} (NM_L - V_{TH})}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) \left[ 2(V_{DD} - V_{TH}) V_{OL} - V_{OL}^2 \right] = \frac{V_{DD} - V_{OL}}{R_D}$$

$$\frac{1}{2} \mu_n C_{ox} \frac{1}{\mu_n C_{ox} (NM_L - V_{TH})} \times \left[ 2(V_{DD} - V_{TH}) V_{OL} - V_{OL}^2 \right] = (V_{DD} - V_{OL})$$

$$2(V_{DD} - V_{TH}) V_{OL} - V_{OL}^2 = 2(NM_L - V_{TH})(V_{DD} - V_{OL})$$

$$-V_{OL}^2 - 2(V_{DD} - V_{TH}) V_{OL} - 2(NM_L - V_{TH}) V_{OL} + 2(NM_L - V_{TH}) V_{DD} = 0$$

$$-V_{OL}^2 - 2(V_{DD} + NM_L - 2V_{TH}) V_{OL} + 2(NM_L - V_{TH}) V_{DD} = 0$$

$$V_{OL}^2 - 3.2 V_{OL} + 0.72 = 0$$

$$\boxed{V_{OL} = 0.2435}$$

$$\frac{(V_{DD} - V_{OL})^2}{R_D} + V_{OL} \times \frac{V_{DD} - V_{OL}}{R_D} = 0.25 \times 10^{-3}$$

$$\frac{(1.8 - 0.24)^2 + 0.24 \times (1.8 - 0.24)}{R_D} = 0.25 \times 10^{-3}$$

$$\boxed{R_D = 11206.55 \Omega}$$


$$\left(\frac{W}{L}\right) = \frac{1}{\mu_n C_{ox} (N_{ML} - V_{TH}) R_D}$$

$$\boxed{\left(\frac{W}{L}\right) = \frac{0.8}{0.18}}$$

$$\left(\frac{W}{L}\right) = \frac{1}{100 \times 10^{-6} (0.6 - 0.4) 11206.55}$$



55.

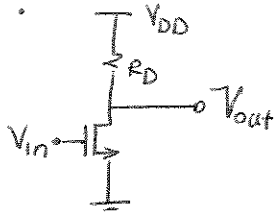

$$V_{OL} = 100\text{mV}$$

$$P_{av} = 0.25\text{mW}$$

$$\frac{(V_{DD} - V_{OL})^2}{R_D} + \frac{V_{OL}(V_{DD} - V_{OL})}{R_D} = P_{av}$$

$$\frac{(1.8 - 0.1)^2 + 0.1 \times (1.8 - 0.1)}{0.25 \times 10^{-3}} = R_D$$


$$R_D = 12240$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) \left[ 2(V_{DD} - V_{TH1})V_{OL} - V_{OL}^2 \right] = \frac{V_{DD} - V_{OL}}{R_D}$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{W}{L}\right) \times \left[ 2(1.8 - 0.4) \times 0.1 - 0.1^2 \right] = \frac{1.8 - 0.1}{12240}$$

$$\left(\frac{W}{L}\right) = \frac{1.85}{0.18}$$

56.

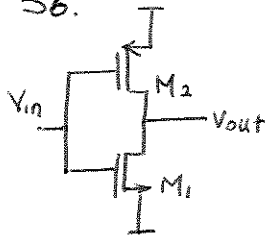

$$V_{in} = V_{out} = 0.8V, I_{D1} = I_{D2} = 0.5mA$$

$$\lambda_n = 0.1V^{-1}$$

$$\lambda_p = 0.2V^{-1}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 (1 + \lambda_n V_{out}) = I_{D1}$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{W}{L}\right)_1 (0.8 - 0.4)^2 (1 + 0.1 \times 0.8) = 0.5 \times 10^{-3}$$


$$\left(\frac{W}{L}\right)_1 = \frac{10.4}{0.18}$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 [1 + \lambda_p (V_{DD} - V_{out})] = I_{D2}$$

$$\frac{1}{2} \times 50 \times 10^{-6} \times \left(\frac{W}{L}\right)_2 (1.8 - 0.8 - 0.5)^2 [1 + 0.2 \times (1.8 - 0.8)] = 0.5 \times 10^{-3}$$

$$\left(\frac{W}{L}\right)_2 = \frac{12}{0.18}$$

57.

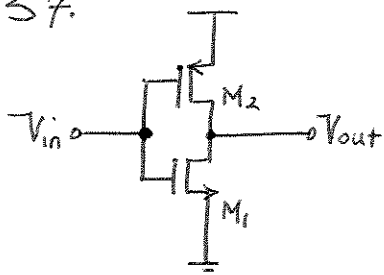

$$NM_L = NM_H = 0.7V$$

$NM_L$ :  $M_1$  in Saturation and  $M_2$  in triode

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - V_{in} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right] \quad (1)$$

Differentiating both sides with respect to  $V_{in}$

$$2\mu_n \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1}) = \mu_p \left(\frac{W}{L}\right)_2 \left[ -2(V_{DD} - V_{out}) - 2(V_{DD} - V_{in} - |V_{TH2}|) \frac{\partial V_{out}}{\partial V_{in}} + 2(V_{DD} - V_{out}) \frac{\partial V_{out}}{\partial V_{in}} \right]$$

$$(a) \quad V_{in} = V_{IL} \quad , \quad \frac{\partial V_{out}}{\partial V_{in}} = -1$$

$$\mu_n \left(\frac{W}{L}\right)_1 (V_{IL} - V_{TH1}) = \mu_p \left(\frac{W}{L}\right)_2 (2V_{OH} - V_{IL} - |V_{TH2}| - V_{DD}) \quad (2)$$

obtaining  $V_{OH}$  from (2), substituting in (1), we arrive at

$$V_{IL} = \frac{2\sqrt{a} (V_{DD} - V_{TH1} - |V_{TH2}|)}{(a-1)\sqrt{a+3}} - \frac{V_{DD} - aV_{TH1} - |V_{TH2}|}{a-1}$$

$$a = \frac{\mu_n \left(\frac{W}{L}\right)_1}{\mu_p \left(\frac{W}{L}\right)_2}$$

$NM_H$ ,  $M_1$  in triode and  $M_2$  in Saturation

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{TH1}) V_{out} - V_{out}^2 \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2$$

Differentiating both sides with respect to  $V_{in}$ :

$$\mu_n \left(\frac{W}{L}\right)_1 \left[ 2V_{out} + 2(V_{in} - V_{TH1}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] = 2\mu_p \left(\frac{W}{L}\right)_2 \times (V_{in} - V_{DD} - |V_{TH2}|)$$

Assuming  $\frac{\partial V_{out}}{\partial V_{in}} = -1$ ,  $V_{in} = V_{IH}$ , and  $V_{out} = V_{OL}$  obtaining

$$V_{IH} = \frac{2a(V_{DD} - V_{TH1} - |V_{TH2}|)}{(a-1)\sqrt{1+3a}} - \frac{V_{DD} - aV_{TH1} - |V_{TH2}|}{a-1}$$

$$V_{IL} = NM_L = 0.7$$

$$V_{IH} = V_{DD} - NM_H = 1.8 - 0.7 = 1.1$$

$$0.7 = \frac{2\sqrt{a}(1.8 - 0.4 - 0.5)}{(a-1)\sqrt{a+3}} - \frac{1.8 - 0.4a - 0.5}{a-1}$$

$$0.7(a-1) = \frac{1.8\sqrt{a}}{\sqrt{a+3}} - \frac{1.3 - 0.4a}{1}$$

$$0.7a - 0.7 + 1.3 - 0.4a = \sqrt{\frac{a}{a+3}} \times 1.8$$

$$\frac{0.6 + 0.3a}{1.8} = \sqrt{\frac{a}{a+3}} \rightarrow a^3 + 7a^2 - 20a + 12 = 0$$

$$a = \begin{cases} -9.3 \\ 1.3 \\ 1 \end{cases} \rightarrow \boxed{a = 1.3}$$

$$1.1 = \frac{2a(1.8 - 0.4 - 0.5)}{(a-1)\sqrt{1+3a}} - \frac{1.8 - 0.4a - 0.5}{a-1}$$

$$1.1(a-1) = \frac{1.8a}{\sqrt{1+3a}} - 1.3 + 0.4a$$

$$1.1a - 1.1 + 1.3 - 0.4a = \frac{1.8a}{\sqrt{1+3a}}$$

$$0.2 + 0.7a = \frac{1.8a}{\sqrt{1+3a}}$$


$$147a^3 - 191a^2 + 40a + 4 = 0 \rightarrow \begin{cases} a_1 = 1 \\ a_2 = 0.37 \\ a_3 = -0.073 \end{cases} \rightarrow \boxed{a = 0.37}$$

No it is not possible to design a CMOS inverter with  $NM_L = NM_H = 0.7$ .

The reason is that each value of  $a = \frac{\mu_n C_{ox} (W/L)_1}{\mu_p C_{ox} (W/L)_2}$  specifies a unique set of noise margins ( $NM_L, NM_H$ ).

Remember, the relative strength of NMOS and PMOS determines the noise margins interdependently.

58.

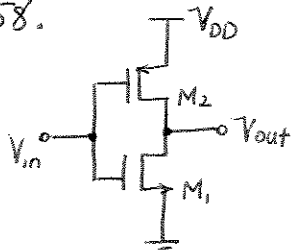

$$T_{PLH} = T_{PHL} = 100 \text{ ps}$$

$$C_L = 50 \text{ fF}$$

 $T_{PLH}$ 

$$|I_{D2}| = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2$$

$$V_{out}(t) = \frac{|I_{D2}|}{C_L} t$$

$$= \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2 t$$

$$T_{PLH1} = \frac{2|V_{TH2}|/C_L}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2}$$

$$|I_{D2}| = C_L \frac{dV_{out}}{dt}$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right] = C_L \frac{dV_{out}}{dt}$$

$$\frac{dV_{out}}{2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2} = \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 dt$$

$$\frac{-1}{2(V_{DD} - |V_{TH2}|)} \ln \frac{V_{DD} - V_{out}}{V_{DD} - 2|V_{TH2}| + V_{out}} \bigg|_{V_{out}=|V_{TH2}|}^{V_{out}=V_{DD}/2} = \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 T_{PLH2}$$

$$T_{PLH2} = \frac{C_L}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \ln \left( 3 - 4 \frac{|V_{TH2}|}{V_{DD}} \right)$$

$$T_{PLH} = T_{PLH1} + T_{PLH2}$$

$$= \frac{C_L}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \left[ \frac{2|V_{TH2}|}{V_{DD} - |V_{TH2}|} + \ln\left(3 - 4 \frac{|V_{TH2}|}{V_{DD}}\right) \right]$$

$$100 \times 10^{-12} = \frac{50 \times 10^{-15}}{50 \times 10^{-6} \left(\frac{W}{L}\right)_2 (1.8 - 0.5)} \left[ \frac{2 \times 0.5}{1.8 - 0.5} + \ln\left(3 - 4 \frac{0.5}{1.8}\right) \right]$$

$$\boxed{\left(\frac{W}{L}\right)_2 = \frac{1.9}{0.18}}$$

$T_{PHL}$

$$T_{PHL1} = \frac{2V_{TH1} C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})^2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - V_{TH1}) V_{out} - V_{out}^2 \right] = -C_L \frac{dV_{out}}{dt}$$

$$\frac{-1}{2(V_{DD} - V_{TH1})} \ln \frac{V_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} \Bigg|_{V_{out} = V_{DD}/2}^{V_{out} = V_{DD} - V_{TH1}} = \frac{1}{2} \mu_n C_{ox} / C_L \left(\frac{W}{L}\right)_1 T_{PHL2}$$

$$T_{PHL2} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \ln\left(3 - 4 \frac{V_{TH1}}{V_{DD}}\right)$$

$$T_{PHL} = T_{PHL1} + T_{PHL2} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[ \frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln\left(3 - 4 \frac{V_{TH1}}{V_{DD}}\right) \right]$$

$$100 \times 10^{-12} = \frac{50 \times 10^{-15}}{100 \times 10^{-6} \left(\frac{W}{L}\right)_1 (1.8 - 0.4)} \times \left[ \frac{2 \times 0.4}{1.8 - 0.4} + \ln\left(3 - 4 \times \frac{0.4}{1.8}\right) \right] \cdot \boxed{\left(\frac{W}{L}\right)_1 = \frac{0.85}{0.18}}$$