

See discussions, stats, and author profiles for this publication at: <https://www.researchgate.net/publication/283017591>

قاموس مصطلحات الفيزياء المشروحة، الجزء الأول: الالكترونية، تأليف د. يسري مصطفى، جامعة السايح من أبريل، 2010.

Book · September 2010

CITATIONS

0

READS

3,102

1 author:



Yosry Moustafa

Umm Al-Qura University & Mansoura University

107 PUBLICATIONS 899 CITATIONS

SEE PROFILE

Some of the authors of this publication are also working on these related projects:




ترجمة كتاب علم الصوتيات تأليف ليوأل. بيرناك [View project](#)



عناوين وملخصات الكتب المنشورة [View project](#)

قاموس

المصطلحات الإلكترونية

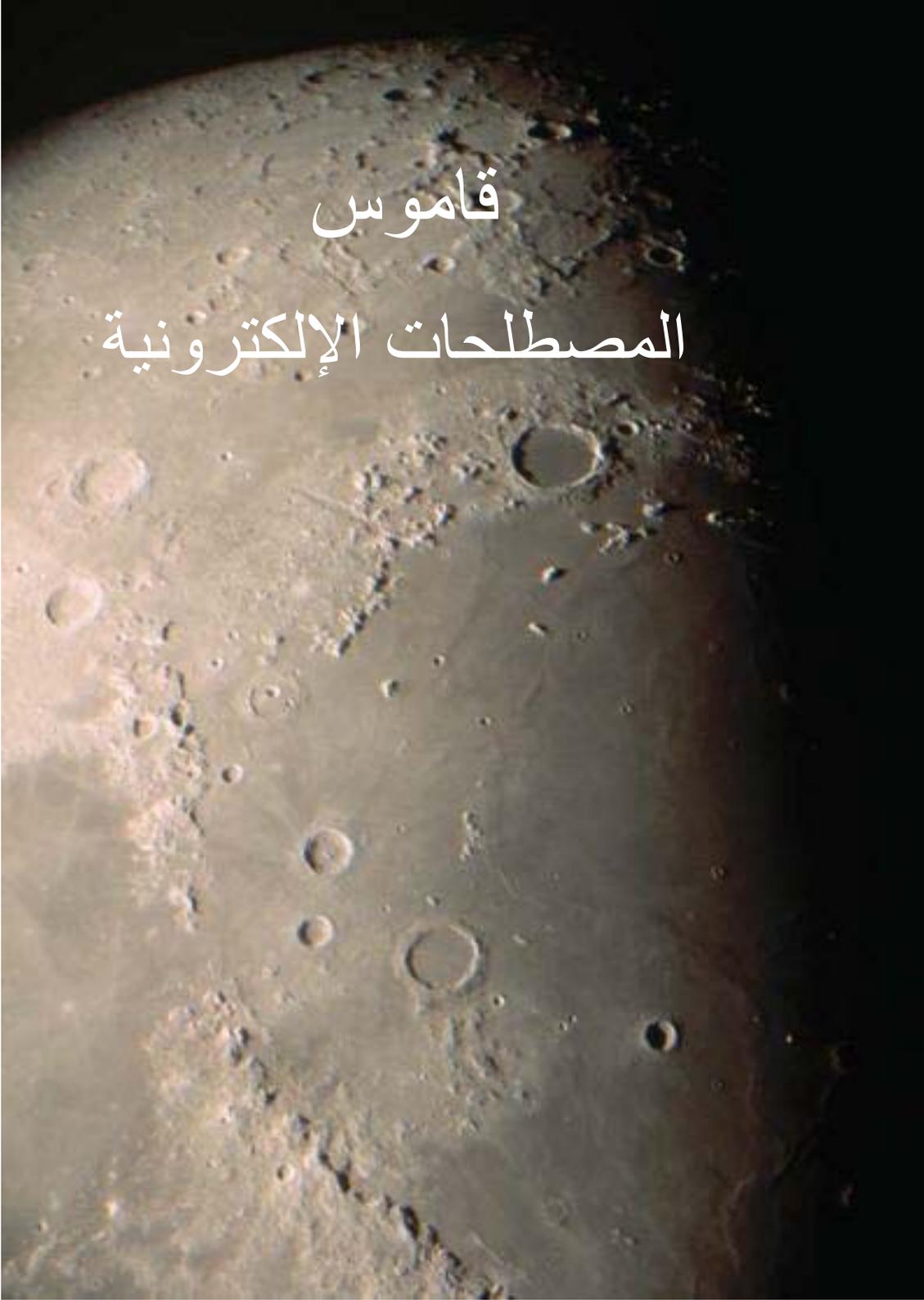

اسم الكتاب. قاموس المصطلحات الالكترونية المشروحة

اسم المؤلف. الاستاكتور يسرى مصطفى

– 2009- 608 :

ISBN978-9959-63-056-8 :

2010 :

هاتف 00218 .23 7626169-7626594-7626171 - 768237

فاكس: 00218 .23 .7624033-7600239

Website www.7@aprilu.ly

Email: Info7@7aprilu.ly

الزاوية – الجماهيرية العربية الليبية الشعبية الاشتراكية

()


750

150

/ .

Band width

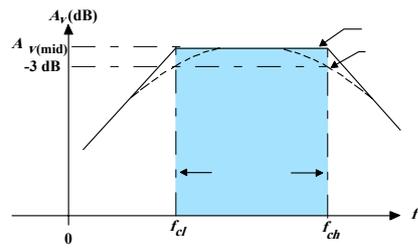f_{ch} f_{cl}
% 70.7 f_{ch} f_{cl}
.1 -3 dB



1

f_{cl}

20 dB/decade

f_{ch}

f_{ch} f_{cl}


Pulse width

%50

()

()

.2

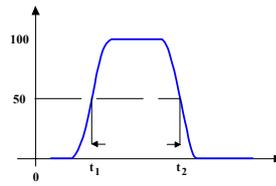

2

[Link](#)

-1 :

- 3

-2

Radio communication

Coupling

Acoustic coupling

Optical couplers


.(Opto- isolators)

()


() .()

3 .

4

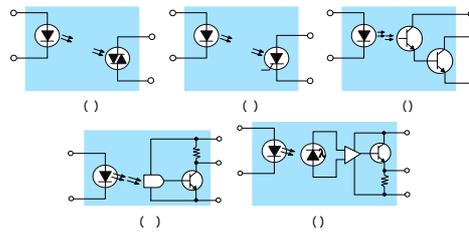

3

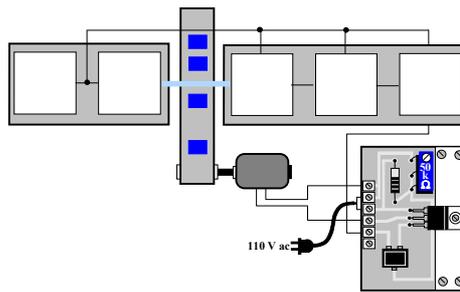

4

AC coupling

Butterworth response


20 dB/Decade

.5

Bessel response

.3

20 dB/Decade

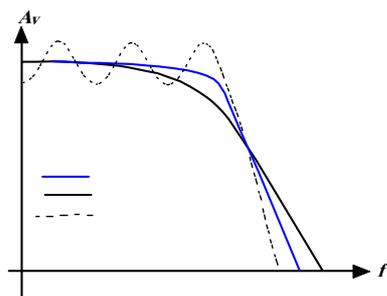

5

Frequency response

Chebyshev response

20 dB/Decade

5

Phase response

Thermal stability

Stability

.

ϱ)

.

(..

.

:

.

-2

-1

.

Electric polarization

.



Depletion

N-P

(MOSFET)

Electromagnetic

communication

Attenuation

Reliability

(discrete circuits)

.()

Secondary emission

()



Photoemission

)

(

Diffusion and drift





()

)

(


Performance

(parasitic)



Optical Fiber

.6

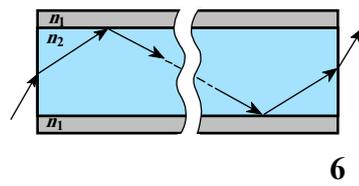

Electronic tubes

(Triode)

(Diode)

(Pentode)

(Tetrode)

Digital systems

NAND

(flip-flop)

$.9.11 \times 10^{-31}$ Kg

)

$n \quad 2n^2$

(

)

(

Emitter

()

Proton

1860

$(1.602 \times 10^{-19}$ Coulomb)


$(1.673 \times 10^{-27} \text{ Kg})$

Crystal

)

(

7

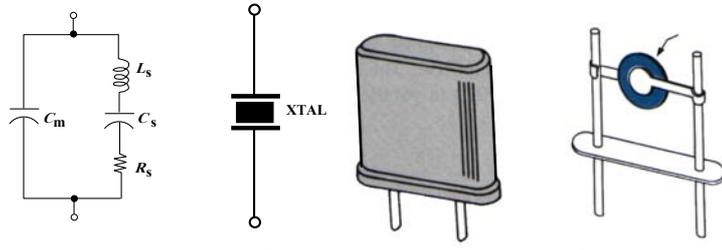

7

Ionization

()

)

(

Hysteresis

-1 :

()

- -2 .

Transistor

1947

(BJT)

.np

8 .

n .

nnp p

n p

.pnp

-


-

.

E , B, C

.

.

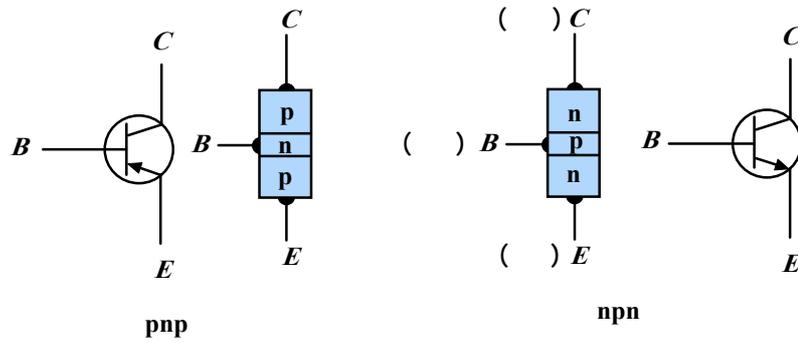

pnp

npn

8

npn

9

.pnp

-

BE


-

BC

/

:


.

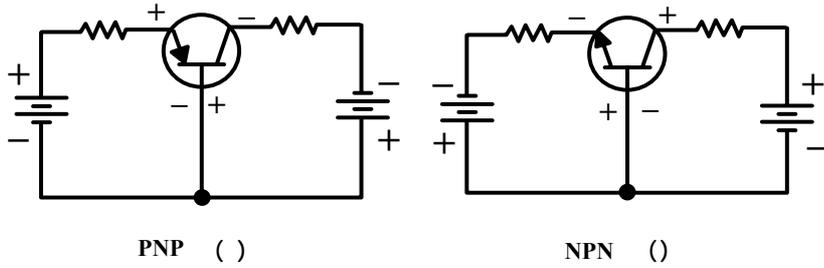

9

Alloyed transistor

.10

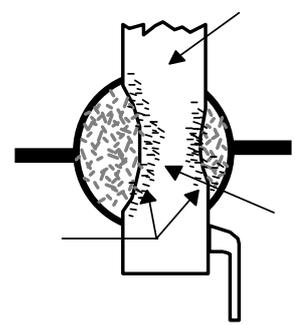


10

Unijunction transistor

np

(np)

.11

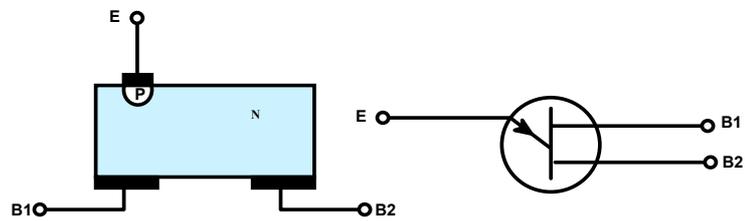

11

(E)

(UJT)

.(B₂)

(B₁)

(JFET)

UJT

.UJT

np

(BJT)

.(JFET)


Programmable

unijunction transistor

) SCR

.12

(

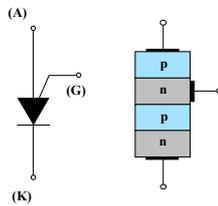

.PUT

12


np

np

0.7V

(PUT)

.13

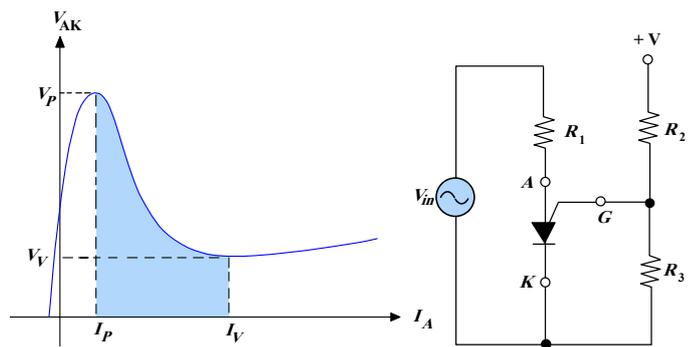

.PUT

13

The critical frequency

()

3dB

$$A_p \text{ (dB)} = 10 \log (0.5) = -3 \text{ dB} \quad :$$

70.7 %

:

$$A_v \text{ (dB)} = 20 \log (0.707) = -3 \text{ dB}$$

70.7 % 3 dB


Triac

SCR

SCR

() ()14 .(A_1 A_2)


14

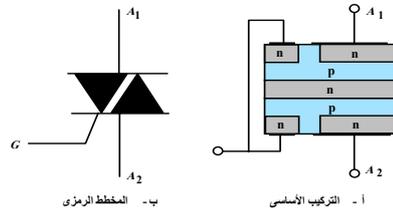

14

.SCR

I_H

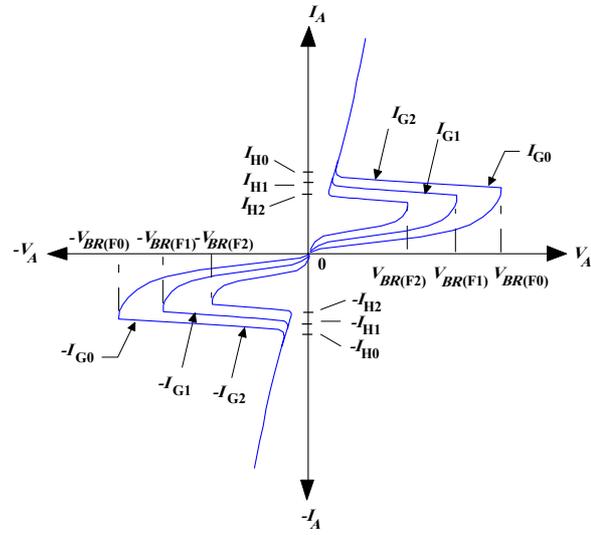

15

Saturation

)


(

Transistor linear operation

()

() .16

()

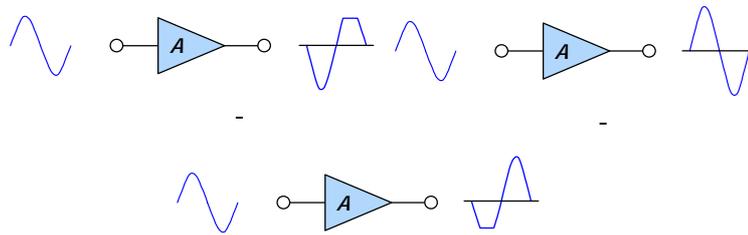

Transistor non-linear

operation

()

.

() .16 () ()

() () .

.

Hanging

() ()


Feedback

Negative feedback

()

.17

.180°

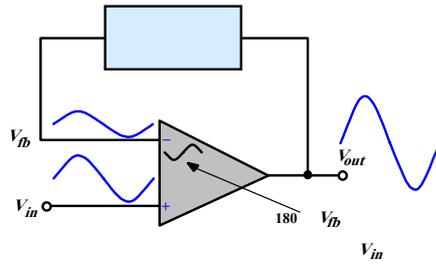

17

)

(100 000

(A_{cl})

1

1

Acoustic feedback

Positive feedback

(0°)

360°

Transconductance

JFET

g_m

(V_{GS})

(ΔI_D)

$(V_{DS=const})$

(S)

$$g_m = \Delta I_D / \Delta V_{GS}$$

) JFET


g_m

(18)

g_m

$(V_{GS} = 0)$

$(V_{GS(off)})$

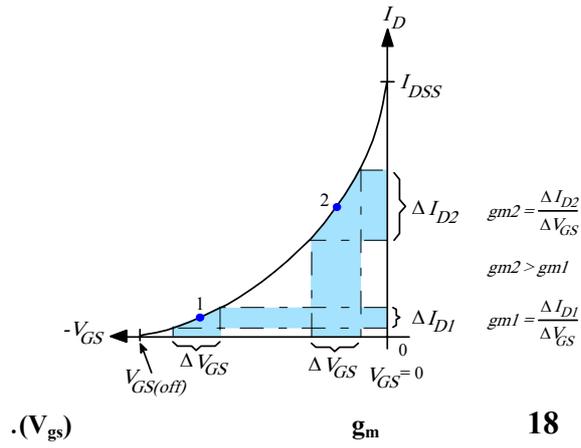

18


Electric current

$(/)$

Alternating overcurrents

() LC

.19

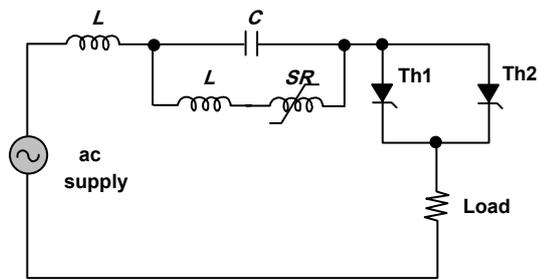


19

Direct overcurrents

.()

:

.20

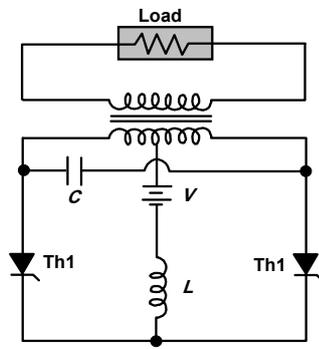

20

Thyrositors

.(nnp)

(SCR)

.(Triac)

(Diac)

(SCS)

Boolean algebra

Electric potential

()

()

Transient state of circuit

()

()

Electromagnetic induction

Step

)

.(

The differential Input

(180°)





.()21

.()

()21 .

()21

1

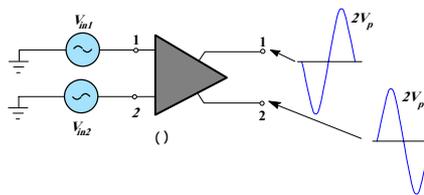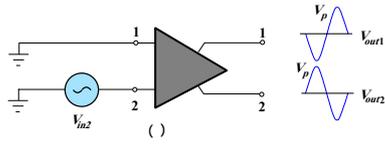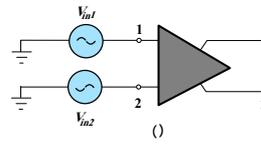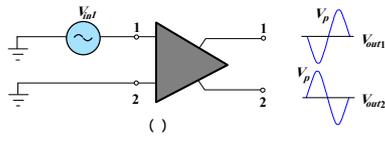

() ()
 () V_{in2}

() V_{in1}

21

() ()

() 1

2 1 .2 ()

()21

The inverting input

. 180

Single ended input

The Noninverting input

. 2

dB

(dB)

P_{out}/P_{in}

A_p

$$A_p \text{ (dB)} = 10 \log A_p$$

A_v

$$A_v \text{ (dB)} = 20 \log A_v$$

A_v


dB

DIAC


22

$A_2 A_1$

23

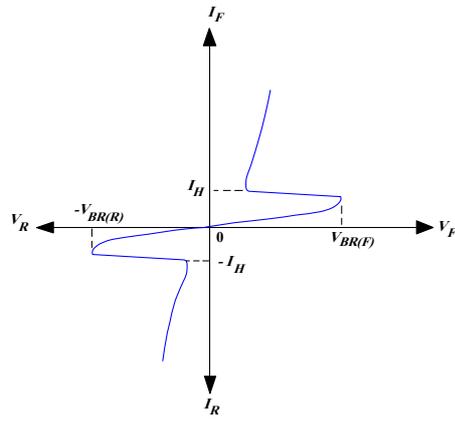

23

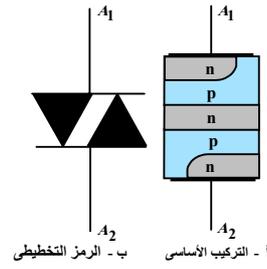


22

Stator

Internal capacitances of

transistor

24

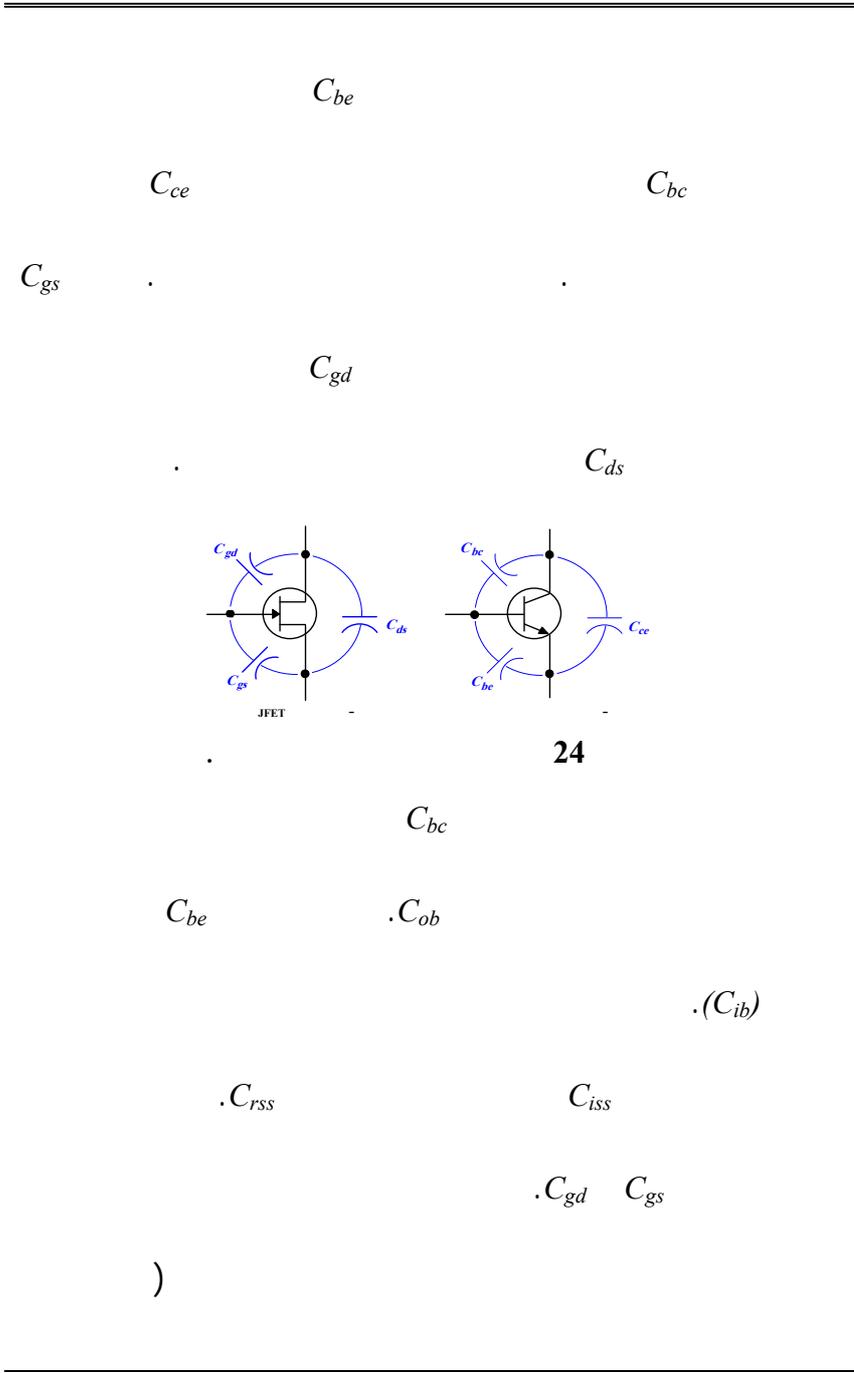


.(

$(C_{gs} \) C_{be}$

.()25

C_{be}

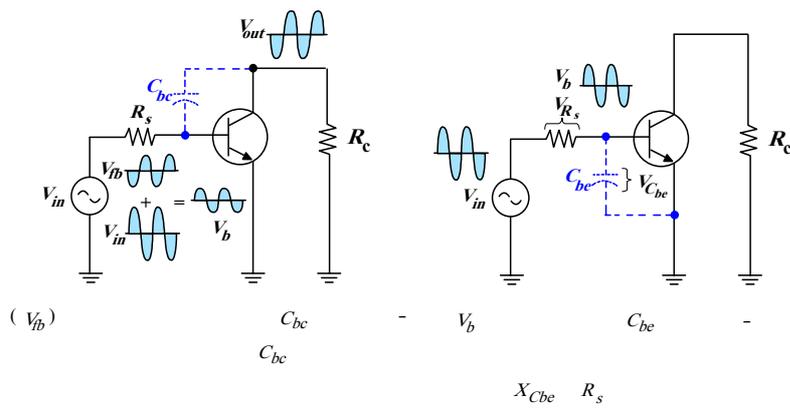

. $C_{be} \ C_{bc}$

25

$(C_{gd} \) C_{be}$

()

()25

Siemens

.(/)

Dominant network

RC

.-20dB/decade

Electric energy


The piezoelectric phenomena

.()

Inverters

:

26

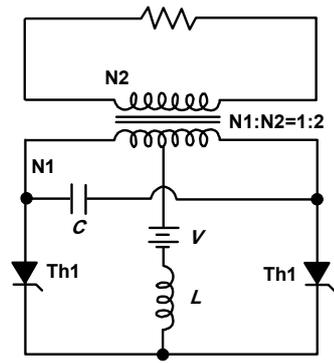

26

Counters

Atomic number

Alpha

$$\alpha_{dc} = \frac{I_C}{I_E}$$

$$) \quad 0.99 \quad 0.95$$

.(

$$\cdot \alpha_{dc} = \frac{\beta_{dc}}{\beta_{dc} + 1}$$

Photon


$$v \quad E = h\nu$$

h

.(eV)

Clipper

27

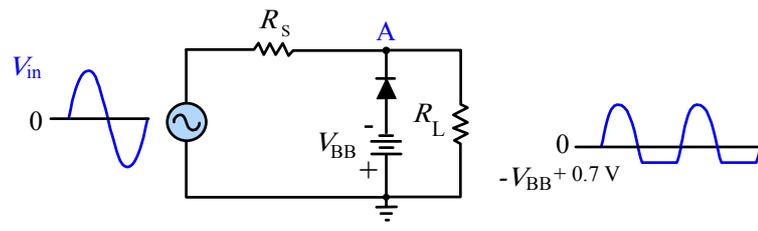

27

Trigger

)

.(....

Thermal triggering

Accidental triggering

Triggering due light radiation

Electric power

$$P = I \times V = I^2 \times R = \left(\frac{V^2}{R} \right)$$

()

.()

:

-1

-2

-3

The pole

Electromotive force, emf

Average value of periodic

function

$$I_P \quad I(t) = I_P \sin(\omega t)$$

□

$$I_{av} = 0.637 I_P \quad I_{av} = \frac{2}{\pi} I_P$$

Reactive value of periodic

function

$\cdot \sqrt{2}$

ω

I_p

$$I(t) = I_p \sin(\omega t)$$

$$I_{rms} = \frac{I_p}{\sqrt{2}}$$

$$\cdot I_{rms} = 0.707 I_p$$

Gain

:

$$A_v = \frac{V_{\text{output}}}{V_{\text{input}}} \quad -1$$

$$A_i = \frac{I_{\text{output}}}{I_{\text{input}}} \quad -2$$


$$A_p = \frac{P_{\text{output}}}{P_{\text{input}}} \quad -3$$

Overall gain

$$A_3 \quad A_2 \quad A_1 \quad 28$$

$$A' = A_1 \times A_2 \times A_3$$
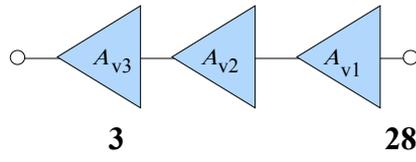
$$A'(\text{dB}) = A_1(\text{dB}) + A_2(\text{dB}) + A_3(\text{dB})$$



Total gain

Efficiency

Electricity



.

)

(

Coulomb

2.998×10^9 esu

6.24×10^{18}

Laser



.(LASER)


Timer 555 555

555

555

(flip-flop)

.29

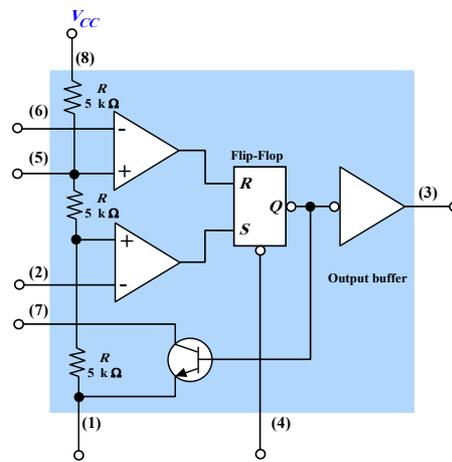

.555

29

555

Electric field

.

. / /

.

Magnetic field

(N)

) .(S)

(

.()

. (. /)

AC drives

. :

Synchronous drives

.

.

(wound :

field)


.(reluctance)

DC drives

.

.

Transformer

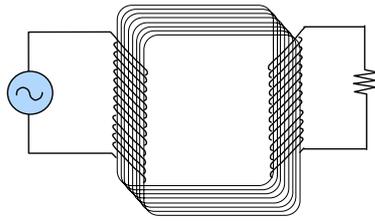


30

Visible spectrum

()

.31

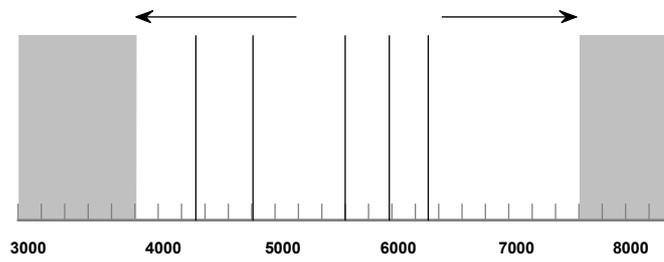


31

Active region

Buffer

32 .(driver)

ملاحظات	Q	A	E
	0	1	1
	1	0	1
حالة معاوقة عالية	*	*	0

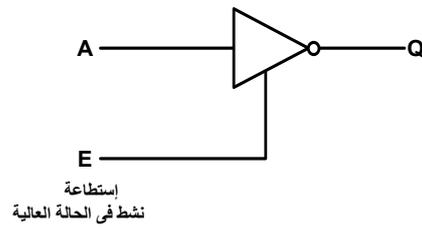

ب- جدول الصدق

أ- الرمز التخطيطي

Microprocessor

.CPU

Impedance

Coil reactance

$$L \quad f \quad X_L = 2\pi fL$$

The resistor

()

)

.(
(potentiometers)

Internal resistance

The capacitor


()

$$i(t) = C \frac{dv(t)}{dt}$$

$v(t)$ $i(t)$

.33

$$C \quad f \quad X_c = 1/2\pi fC$$

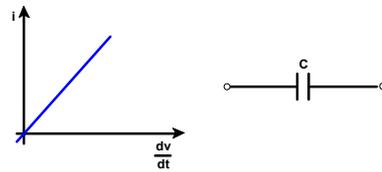

33

Clamper

.
(dc restorer)

The induction coil

()

.34

()


)

()

.(/

$$L = \frac{\mu N^2 A}{l}$$

.(shoke coil)

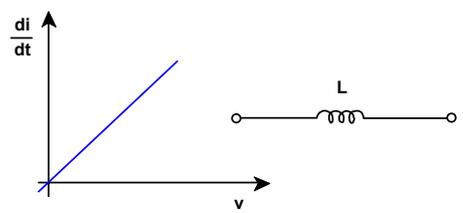

34

Capacitance reactance

)

(

Characteristic



Characteristic curve

Diode characteristic curve

(35)

$0.3V$

$0.7V$

.(


$$I = I_o (e^{V/V_t} - 1)$$

I_o V

I

0.025

V_t

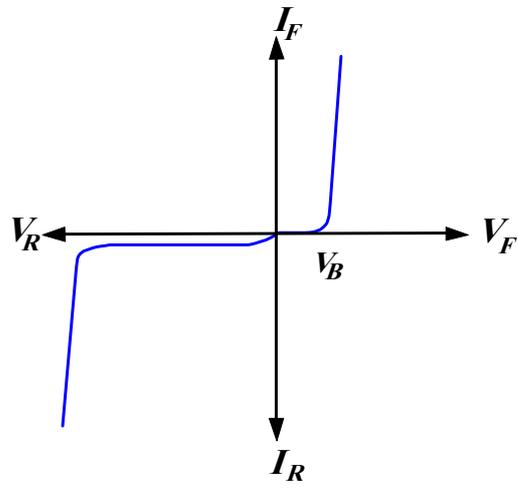

35

()

.()

Collector characteristic curves

.()36

npn

I_B

V_{CE}

I_C

I_B

V_{BB}

V_{CC}

V_{BB}

$V_{CE} = 0 \quad I_C = 0$

$V_{CC} = 0 \text{ V}$

I_C

V_{CE}

V_{CC}

.()36

B A

-

0.7 V

V_{CE}

I_C

I_C

$$I_C = \beta_{dc} I_B$$

B

V_{CC}

I_C



$()$

-

V_{CE}


I_B

$() 36$

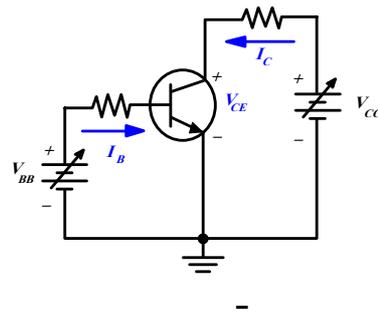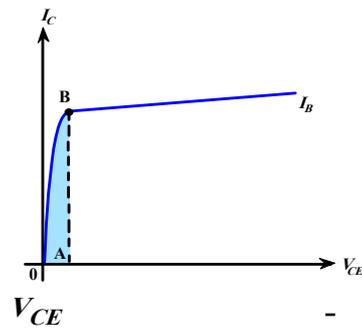

$()$ npn

$() 36$

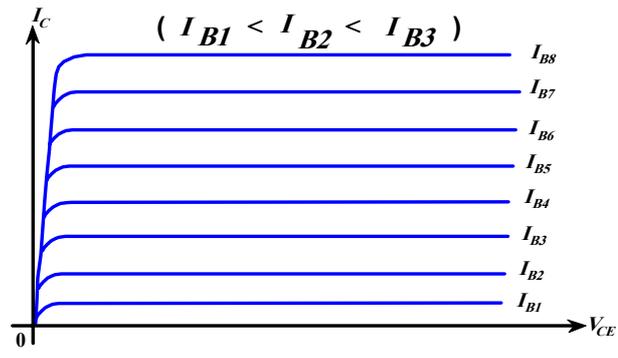


-
() 36

Conductors

.()

()

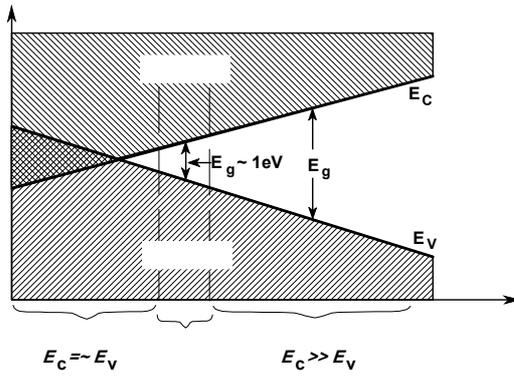

37

Insulators

()

.37

Semiconductor

37

()

Electromagnetic waves


Line drivers and receivers

)

(


: /

38

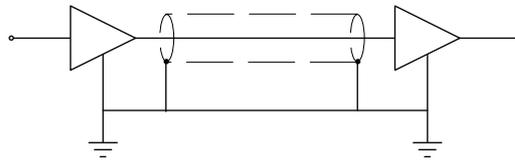

()

() 38

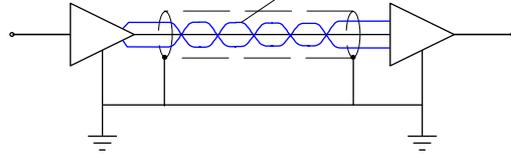

()

() 38

Percent of regulation


Signal sideband

Quiescent point


Acoustic transmission

Antenna

Atomic weight

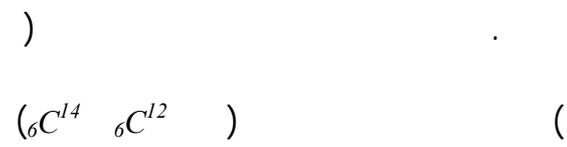

NP junction

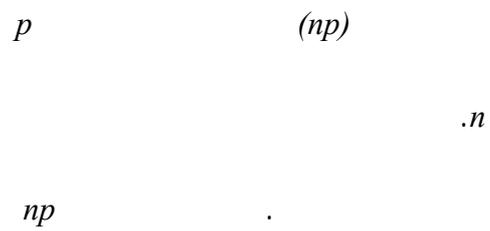

Absorption

.

Thermoionic emission

()

.

Field emission

(1 MV/cm)

(Mercury- -

.pool)

Propagation ()

()

Selectivity

Maximum power transfer

"

"

Drift


()

Roll-off

Gain roll-off

.39

20 dB

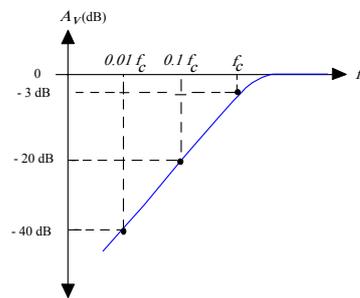


39

Bias

Emitter biasing

.40

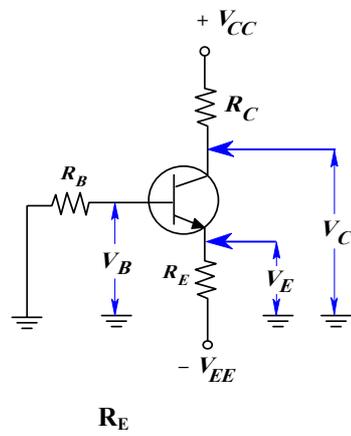

40


(V_{EE})

Transistor biasing

.40

Collector feedback bias

.41

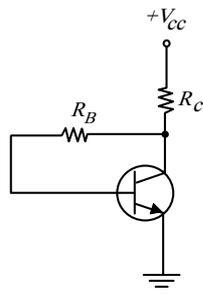


41

Base biasing

R_B

.()42

.()42

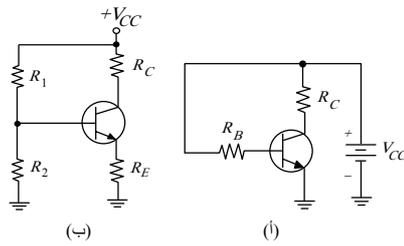

(ii)

(i)

()

() :



42

Forward bias

np

np

43

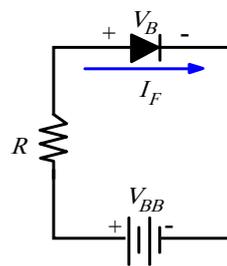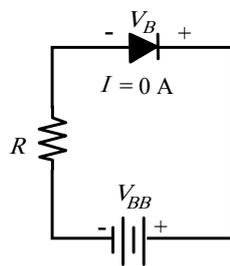

43

Reverse bias

.np

.() 43

Voltage-divider biasing

$$R_2 \ R_1$$

.()42


Midpoint Biasing

()

()

.44

Matching

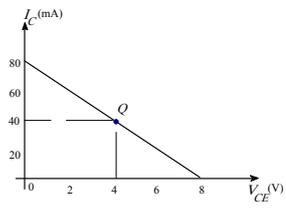

44

Impedance matching

Diode opening

()


Inversion

non-)

(inverting input)

(inverting input

Phase inversion

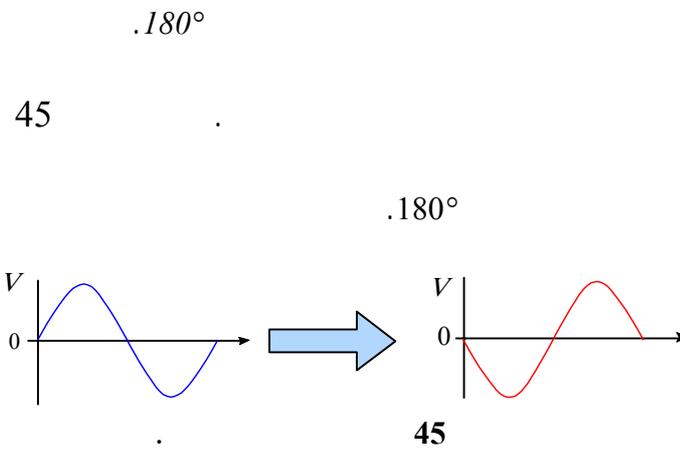

Secondary breakdown

:

()

Zener breakdown

()


Reverse breakdown

()

.46

)

.(

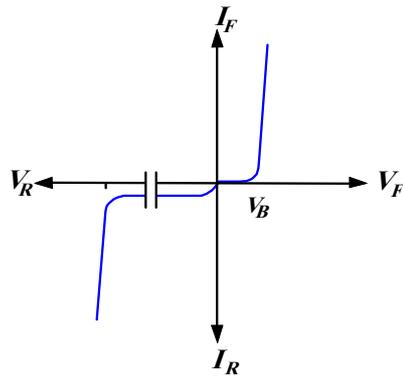

46



Skin effect

(*RF*)

Peltier effect


.(thermocouple)



Faraday's effect

Hall's effect

.47

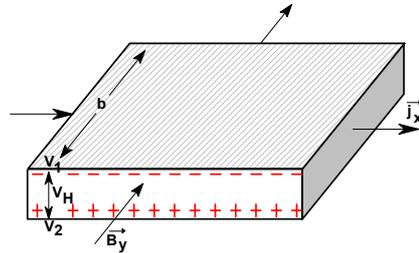

47


Tristate (or high ()

impedance) devices

0 1 :

() 48

ملاحظات	Q	A	E
	0	1	1
	1	0	1
حالة معروفة عالية	*	*	0

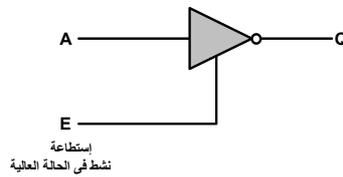

ب - جدول الصديق

أ - الرمز التخطيطي

48

Monochromatic

()

Minimum specifications

RC

resistance-

" - " "capacitance

"radio-controlled"

."RC model airplanes"

Ground

Virtual ground

Floating ground

Intrinsic semiconductors

()

Extrinsic semiconductor

()

n-type

p-type

Infrared light

.(750 400)

Maximum inverse voltage

Maximum ratings

Ampere

Octave

()

.()

1 kHz 10 Hz

1kHz


Large-signal

Radiation

()

Recombination

.49

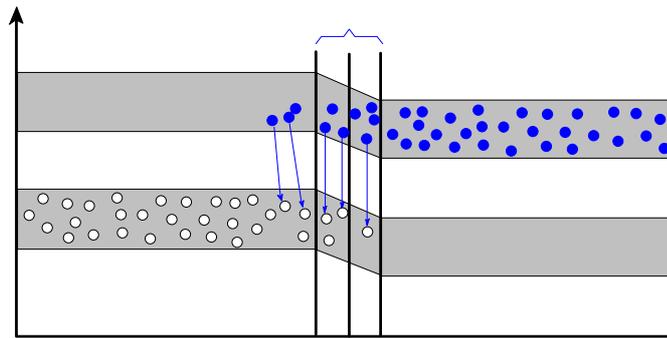

NP

49

Turn-off

()

Conduction electron

Free electron

Battery


Logic gates

(OR) (AND) :

(NAND) - (NOR) - (NOT)

Gate

.50

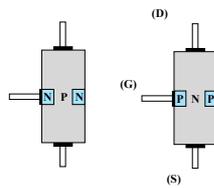

JFET

50

OR gate -


(OR) -

B A (1)

(0)

(0)


.51

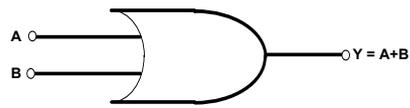

51

NOT gate -

52

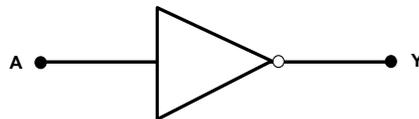

52


AND gate -

(AND)

(1)

(0)

.53

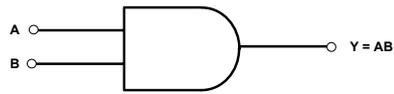

53

NOR gate

OR

NOT

OR.


B

A

(1)

54

NOT-OR.

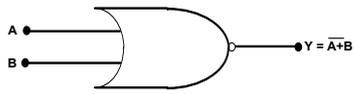

54

NAND gate

AND


.NOT

B A (1)

(0)

NOT-AND 1

.55

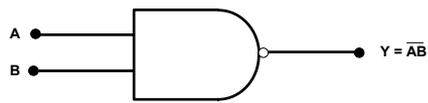

55

Beta

.200 50

Emitter-follower

Voltage-follower

Source-follower

Propagation delay

()

Electro-luminescence

Dissipation

Abnormal dissipation

Sampling

()

Fold-back current limiting

Automatic frequency control,

AFC

Automatic gain control, AGC

()

()

AC line voltage control

:

Speed control

(driving)

Frequency-domain analysis

-

-

-

Time-domain analysis

-

-

Loading

A/D conversion /

(A/D) /

A/D

()

D/A conversion /

D/A

/

D/A

.

()

Schematic

.

Tapered

.()

Conventional current flow

.

Abnormal oscillation

-1 :

-2 ()

-3

-4

E-MOSFET

E-MOSFET


E-MOSFET

D-


E-MOSFET

MOSFET

56

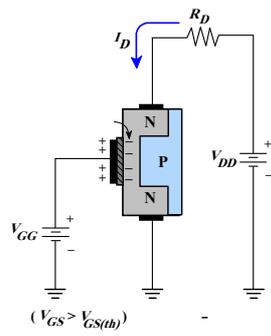

E-MOSFET

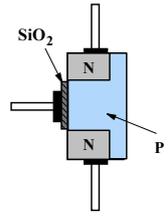

56

Dual gat MOSFET

MOSFET

MOSFET

MOSFET


FET

(RF)

RF

(AGC)

57

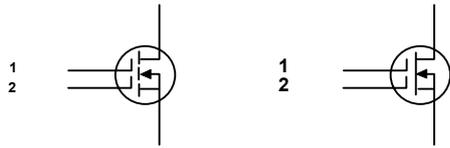

E-MOSFET

-

D-MOSFET

-

MOSFET

57

Switching transistor

Diffused base transistor

Field effect transistor, FET

FET



:

.

-


(JFET)

.(MOSFET)

58

.

.

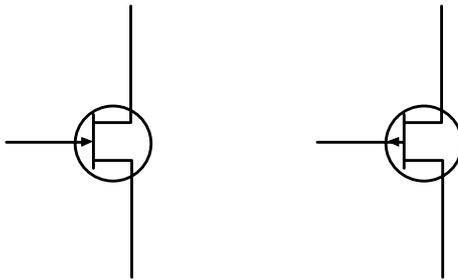

JFET

58

MOSFET

-

-

FET

.

:



Junction field effect

transistor, JFET

(JFET)

(FET)

)

JFET

JFET

()59


.(

JFET

()59

59


.JFET

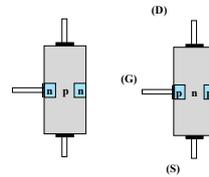

Darlington

phototransistor

60

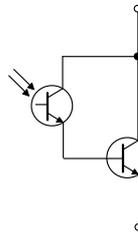

60

Phototransistor

np

.61


I_{CEQ}

I_{λ}

np


I_{λ}

61

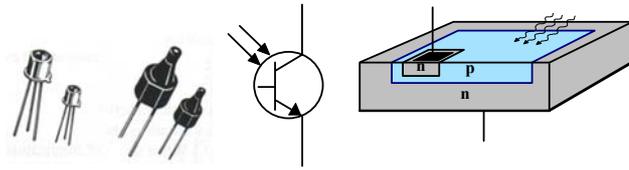

61




62

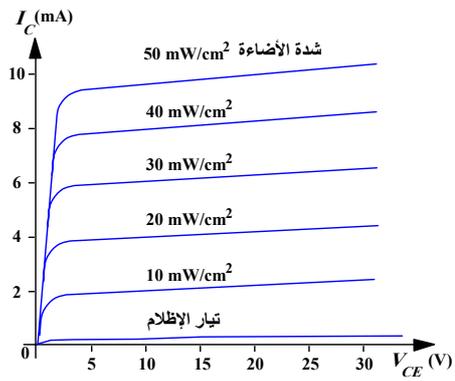

General Purposes Transistors

63

64

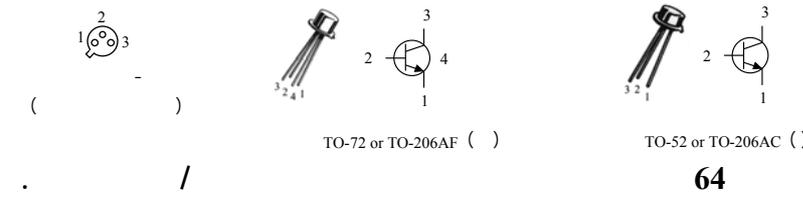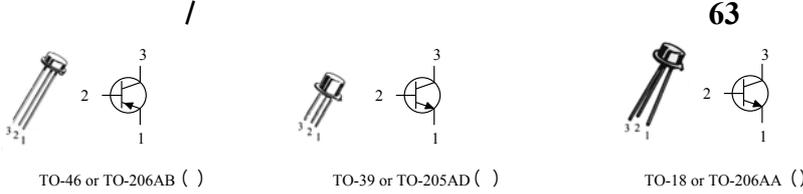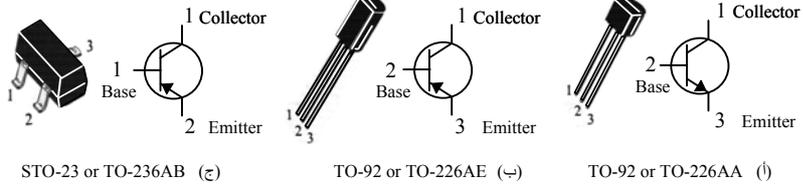

63


64

Radio frequency transistors

RF

65

.RF

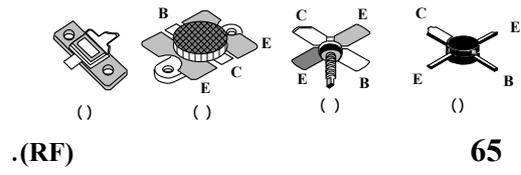

Power Transistors


(1A)

()

66

()

66

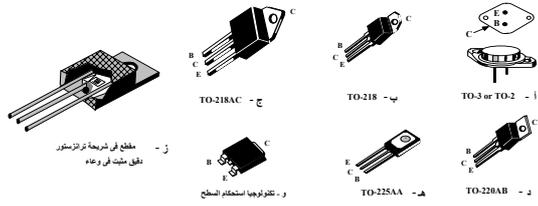


Threshold frequency

67

3dB

f_{th}

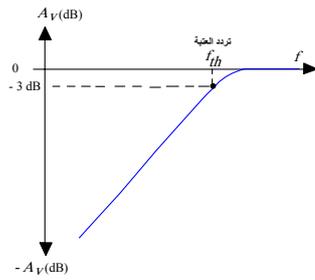

67

Cutoff frequency

Center frequency

()

f_o

RF

:

High frequency, HF

.30 MHz 3 MHz

Super high frequency

30 GHz 3 GHz

.SHF

Unity gain frequency

f_T

.

Intermediate frequency, IF

3000 300

.

Low frequency, LF

300 30

.

Very low frequency

30 3


.

Sum and difference frequencies

$$f_o \qquad \qquad \qquad f_i$$

$$(f_i - f_o)$$
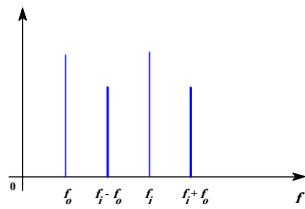
$$\qquad \qquad \qquad 68 \qquad \qquad \qquad (f_i + f_o)$$




68

Covalent

() 69

() 69

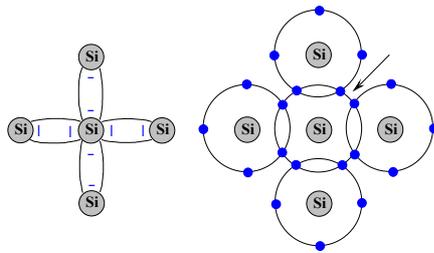

69

Leakage

Tesla


1 = 1) .

.(

Distortion

Output distortion

Q

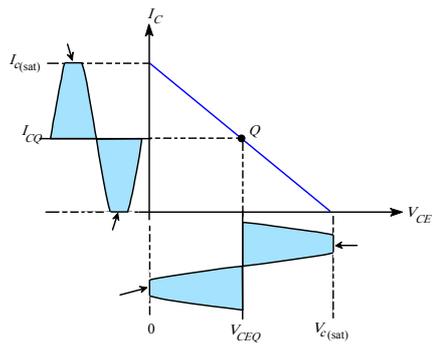

.70

Crossover distortion

- -

V_{BE}


-

71

$Q2$ $Q1$

-

.()

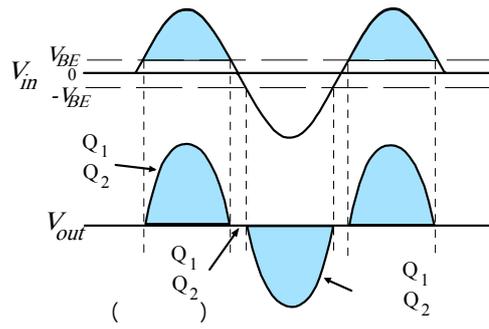



.B

71

Waveform distortion

(Harmonic)

72

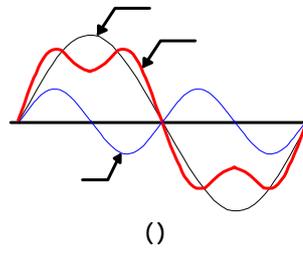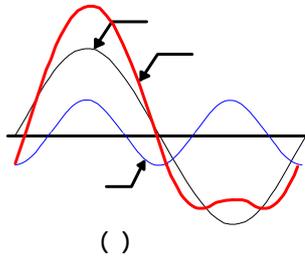

()

() :

72

Zeroing

Troubleshooting

Doping

()

()

Cascade

Frequency-division multiplex, FDM -

-

Modulation

()

()

Frequency modulation, FM

()

()

. 108 88

. 73 .

Amplitude modulation, AM

()


()

.74


)

()

(

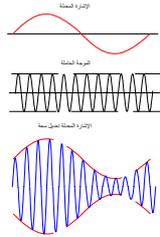

74

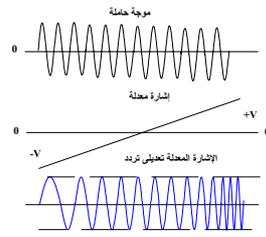

73

Enhancement ()

MOSFET

Compensation

Phase Lag Compensation

180°
 -20
 -20 dB/decade dB/decade

Biassing current

compensation in voltage follower

Input Offset Voltage Compensation

Discharge

Dynamic convergence

Bounding

Valence

)

.(

.. ..

Amplification

.

Sintering

.

Television

Analog

()

Load regulation


75

R_L

(I_{ZK})

(non-load -)

.(full-load)

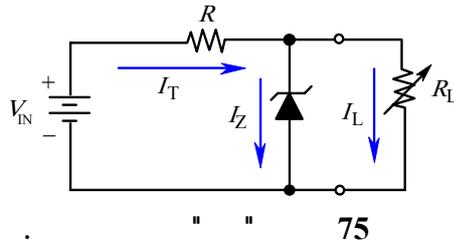

Line regulation


.76

./%V

()

0.05%/V

% 0.05

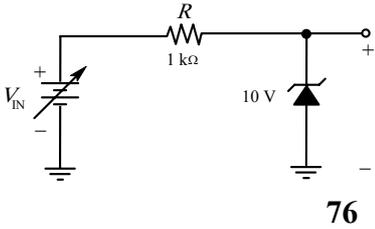

Interfacing

Harmonic

880 Hz

880 Hz

440 Hz

.220 Hz

Transconductance

Incandescence

.()

Holding current

()

.(I_H)

Surge current

Majority current

Minority current

np

Switching current

I_S (on) (off)

I_H

Dark current

Runway collector current

-

.

.

Bleeding current

Input bias current

Collector leakage current

Static reverse current

Gate trigger current

SCR

Alternating current

Eddy currents

Time constant

RC

%63

% 63

RC

.RC

RL

.C

R

.R

L

Dielectric constant

Bipolar

Truth table

(1 0)

Device


Forward-breakover voltage

$V_{BR(F)}$		<i>SCR</i>
	$V_{BR(F0)}$	$I_G=0$
..... $V_{BR(F2)}$	$V_{BR(F1)}$	$V_{BR(F)}$
	I_{G2}	I_{G1}

Ripple voltage

()

77

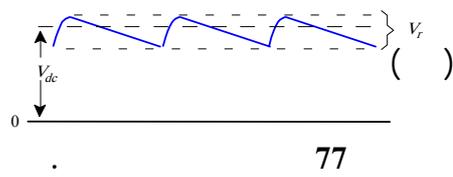

Pinch-off voltage


()

V_p

(Pinch-off)

V_p

.78

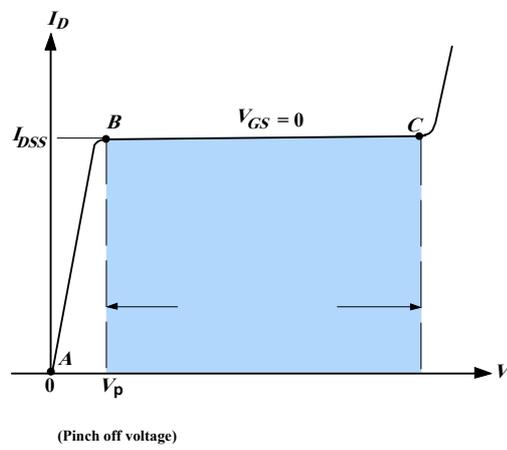

78

Potential barrier

.np

Open circuit voltage

Knee voltage

np

Isolation voltage

.7500 Vac

Cutoff voltage

V_{GS}

$(V_{GS(cutoff)})$

I_D

$V_{GS=0V}$ JFET

V_{DS}

(I_{DSS})

$V_{GS(off)}$

Input offset voltage

V_{os}

AC voltage

Majority carriers

)

.(

Minority carriers

)

.(

Mutual inductance

Distributed inductance

Instrument sensitivity

Load

-2

-1 :

-3

-4

Inductive load

.()

Least significant bit, LSB

1

1101


Most significant bit, MSB

Output

Load line

AC Load Line

.79

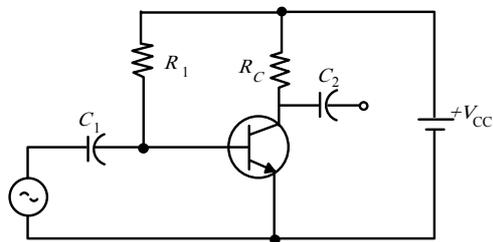

79

R_l


R_C

R_l

$$R'_L = \frac{R_L R_C}{R_L + R_C}$$

$$-\frac{1}{R'_L}$$

80

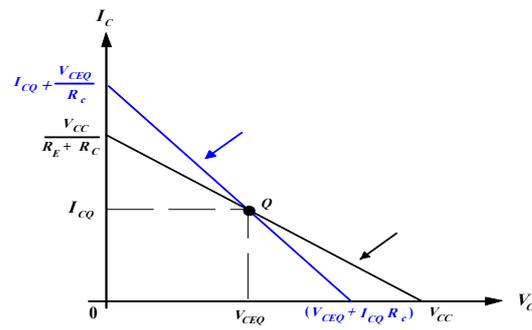

80

DC Load Line

V_{CE}

.80

V_{CE}

Q

Measurement error

-1 :

-2

-3

Linear

)

.(

Primary cell

Memory cell

(flip-flop)

.(1 0)

(latche)



Secondary cell

Mercury cell

Photo-voltaic or solar cell -

-

np

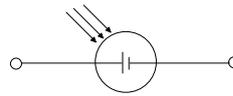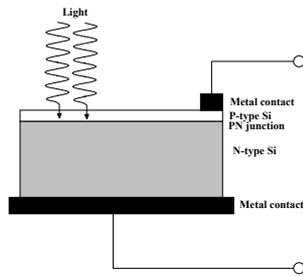


81

Alkaline cell

Nickel-cadmium cell

Squaring circuit

.82

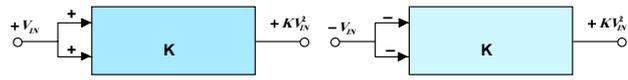

82

Single-phase rectifier

Three-phase rectifier

20 kW

Constant current circuit

Resonance circuit

$$f = \frac{1}{2\pi\sqrt{LC}}$$

Integrated circuit

Closed circuit television

Hybrid circuit

)

(

Dry circuit

50

200

Parallel resonance circuit

Astable circuit

Medium-scale integrated

circuit, MSI

.Large-scale integrated circuit, LSI

:

LSI	100	10	MSI
		.	100

Metal work function

.

:


()

Commutator

Diode

)

.(:

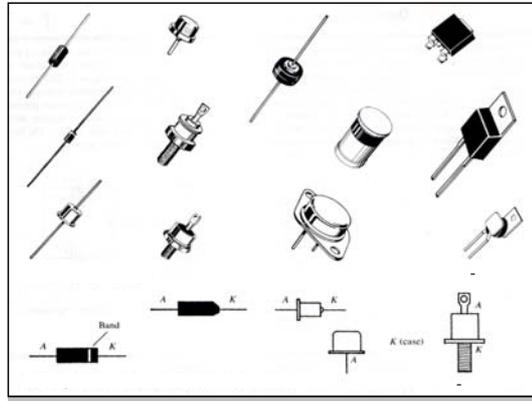

83

PIN

PIN

(intrinsic)

(N)

(I)

(P)


PIN

.PIN

PIN

.PIN

84

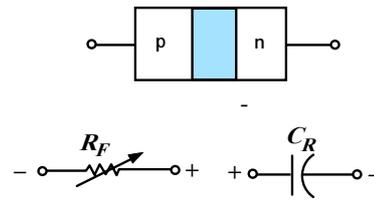

.PIN

84

Step-recovery diode

.np

)

(

LASER Diode

)


85

.LED

(

NP

.np

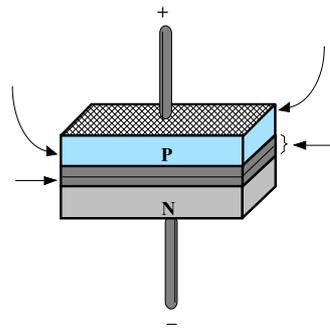


85

Gun diode

Tunnel diode

86

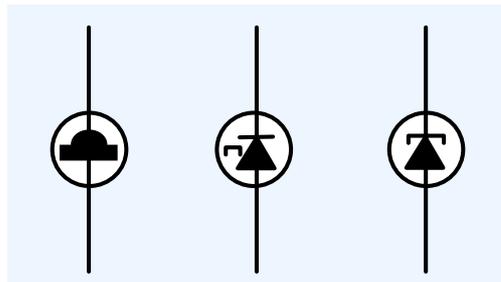

86

Light emitted diode, LED



:

n np

p

.

.

.(Electro luminescence)

(GaAsP)


(GaAs)

.(GaP)

.

.



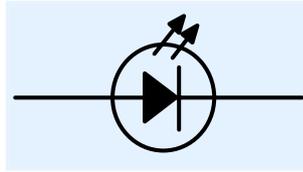

87

Surface-barrier diode

Zener diode

np

88




Schottky diode

)

(

89

.np

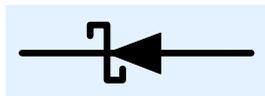


89

Shockley diode

.npnp

90

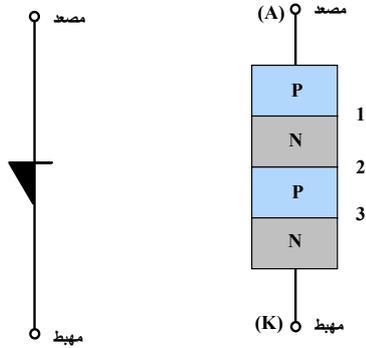


90

Photodiode

np

.np


91 *np*

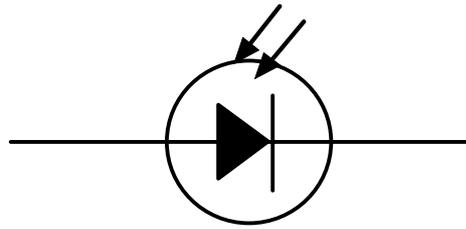

91

VARACTOR diode



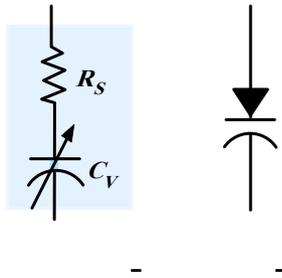

Input

Common mode input



.

.

.

.

.

()

60 Hz

.

Floating input

.



Voltage commutation

Load commutation

Current commutation


Forced-commutation

(SCR)

Control circuits

Commutation circuits

Snubber circuits

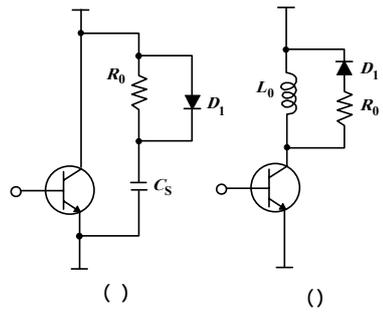

() () :

93

intrinsic

Memories

(microcomputer)

(ROM) ,

8 = 1)

.(

.ROM

()

.RAM random access memory

Acoustic memory

Atom


Germanium atom

32

.()94

32

4

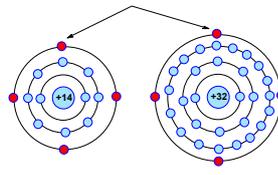

94

Silicon atom

14

14

4

.()94

4

4


Trivalent atom

Pentavalent atom

Ionic bond

) ()
. (

Covalent bond

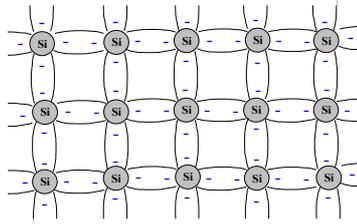

95

Radar

radio detecting and "

"ranging

Order

.(pole)

Bode-Plot


)

) .96 (

.(

()

.()

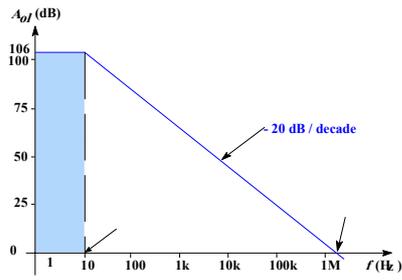

96

Binary digit

-1 :

-2


Digital

.(1 0)

Resonance

Phase angle

$V_b V_a \theta$

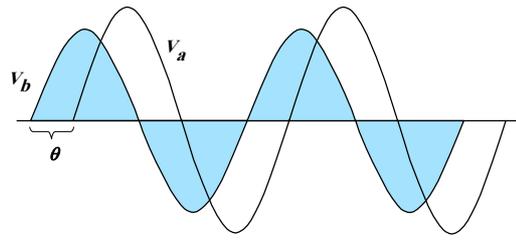

V_b V_a θ 97

Hold time

Turn-off time

5

200

Propagation time

Delay time

%10

Storage time

%90 %100

Electron-hole pair


-

-



Darlington pair

.98

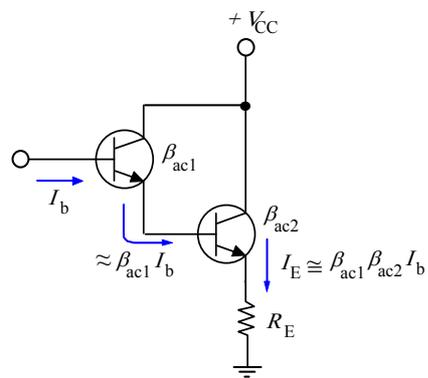

98

Electronic clock

Registers

()

8)

4

.(... 16

.

Shift registers

)

(

.

Mounting capacitance

.

Distributed capacitance

.

Miller's output capacitance

99

$$C_{out(Miller)} = C \left(\frac{A_V + 1}{A_V} \right)$$

)

C

.(FET

$C_{out(Miller)}$ 10

C_{bc} $\left(\frac{A_V + 1}{A_V} \right)$ C_{gd} C_{bc}

C_{gd}

Muller's input capacitance


99

C

$A_V \quad C_{in(Miller)} = C(A_V + 1)$

) C

.(FET

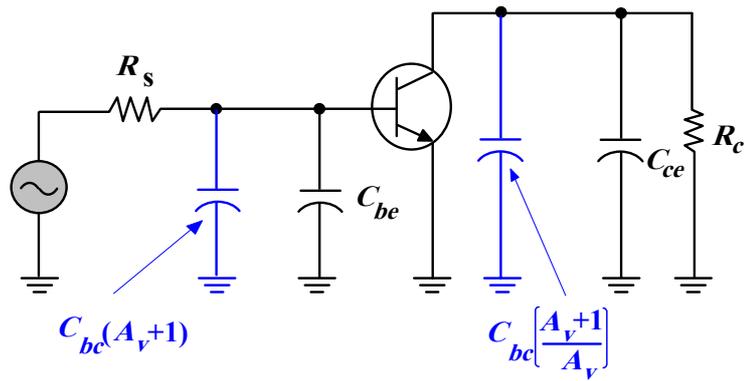

99

R-2R ladder

R-2R

/ .()

Permittivity

8.85×10^{-12}

.

/

.

/

Speaker

Audio

Sonar

Sound navigation "

"and ranging

Charger

Phase splitter

.180°

RC networks RC

RC

Network

-2

-1 :

-3

-4

Bypass RC network

RC

RC

Output RC-network

RC

RC

Input RC-network

RC

RC

N- Type semiconductor

)

)

(

.(

()

)

(

P- Type semiconductor

)

)

(

.(

(

)

.

.

Grid

-1 :

-3

-2

.



Electric charge

Dielectric strength


Magnetic field intensity

Spark

Oscillation conditions

(1) :


(2) 0°

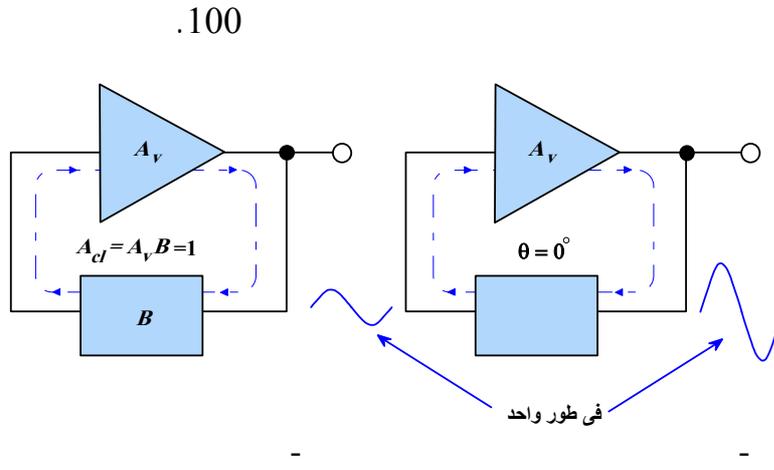

100

Oscillation start up conditions

101

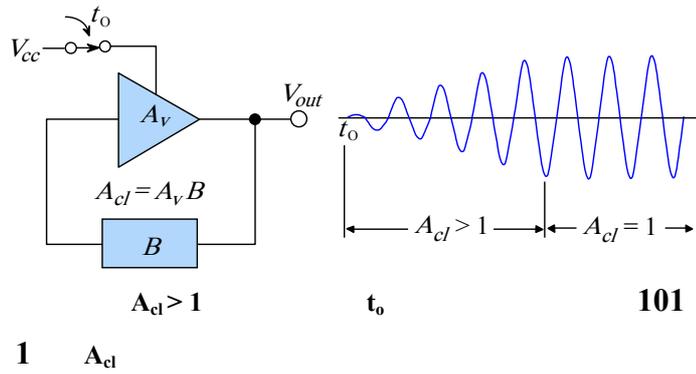

Interface latch chip

/ ()

Chip

Band ()

()

K- -1 :

- -2 . 3300 1100

390 *L*

. *X*- -3 . 1550


High fidelity, Hi Fi

(Hi Fi)

Pulse code

Resistance color code

.102

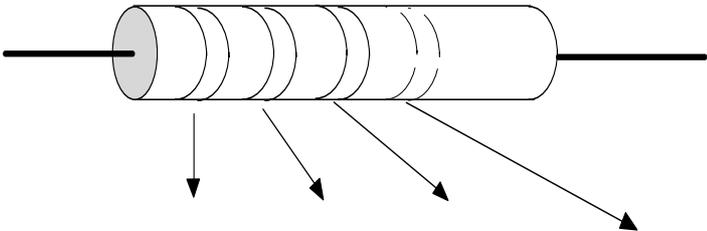

	0	0	1	± 5 %
	1	1	10 ¹	± 10 %
	2	2	10 ² (100)	± 20 %
	3	3	10 ³ (1000)	
	4	4	10 ⁴	
	5	5	10 ⁵	
	6	6	10 ⁶	
	7	7	10 ⁷	
	8	8	10 ⁸	
	9	9	10 ⁹	
	-	-	0.1	
	-	-	0.01	

Acceptors

()

3

()

Donors

()

5

Data sheet

Gain-bandwidth product

-

-


Coherent light

Depletion layer

np

()

.103

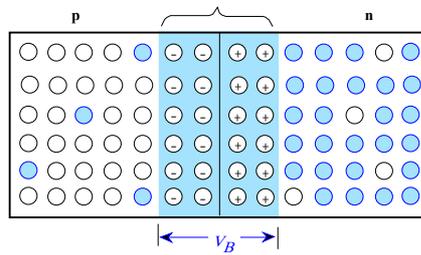

.NP

103

Terminal

Phase

Wave length

Spectrum

Spectral

Insulator

Mycalex

Damping factor

Ripple factor

()

Quality factor

Q

Q

f_o

$(Q < 10)$

$(Q > 10)$

)

.() (

Power factor

Crowbar

Binary counter

Decade

) 10
(
1Decade 100Hz 1kHz
0.1Hz 1Hz 10Hz 100Hz
.1 Decade

Electronics

(triode)

(vacuum diode)

(1950)

(solid state electronics)

(semiconductor devices)

Optoelectronics

()

.()

Power electronics

Radio astronomy

Passive component

Active component

Opto-isolators

Filament

Hole

Energy gap

.(eV)

Test

Diode investigation

()


()

.()104

(100 Ω)

()104

()104

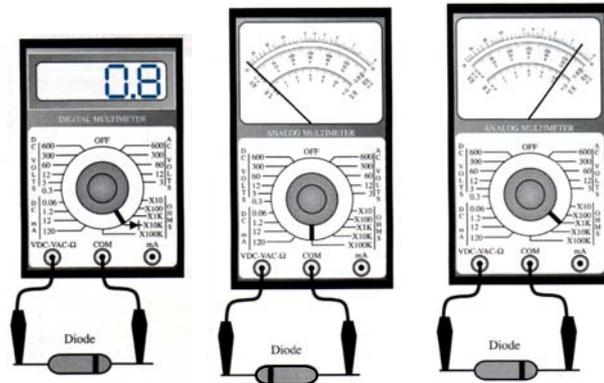

()

()

()

() :

104

()

()

+

(DMM)

Potential difference

()

.

Copper loss

)

.(

Thermal overload

.

.



Ultrasonic

.20 kHz

Flux

Ferrite

)

(

Schmitt trigger

Circuit breaker


Base

Left-hand rule

"

"

.() 105

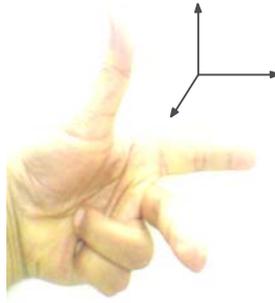

105

Right-hand rule

"

"


()105

Ohm's law

"

"

$(V=IR)$

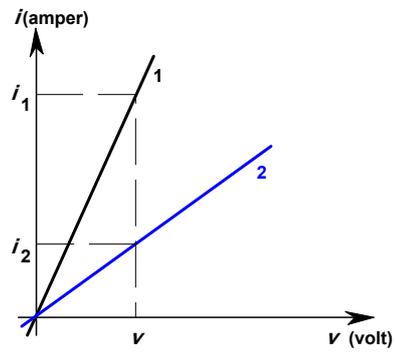

106

Faraday law

"


"

Coulomb law

"

.107

$$F \propto \frac{q_1 q_2}{d^2}$$

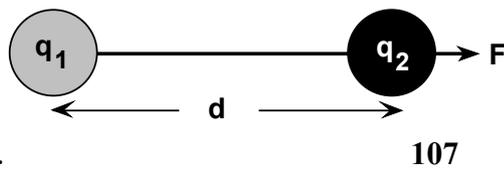

107

Kirchhoff's law for current

"

"



Kirchhoff's law for voltage

"

"

.

.

Lenz law

"

)

"

.

(

.

.



Gate triggering

Thyristor triggering

. (VFBO)

Trimmer

Diode shorting

Dead short

Cutoff

()

Core

Laminated core

Magnetic core

()

.()

Channel

-1 :

-2 .


-4 .

-3 .

.

Response measurement

using discret point methode

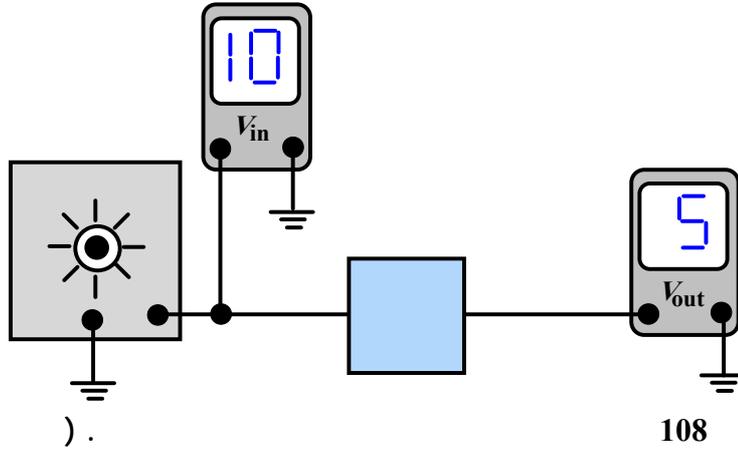

-1

).

-2

.(0 Hz)

-3



. -4

. -5

-6

.

Response measurement

using sweep frequency


.109

. / /

)

(



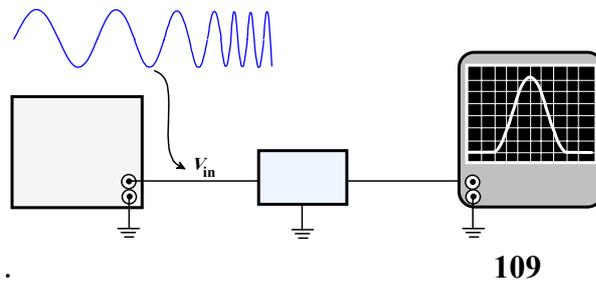

Telemetry

.()

Peak value

.()

Cathode

Detector

10.7MHz

.(IF)

FM

Automatic-direction finder,

ADF

Zero current detector

(0.7-0.5)

(zero crossing detector circuits)

Phase detector

:

Peak detector

Lie detector

)

(

FM detector

(FM)

f_o

Resistive temperature

detector

() ()

Thin film detector

Magnetic flux density

() ()

$$. (1 \text{ Tesla} = \frac{\text{Weber}}{\text{m}^2})$$



Transfer Gain

"

"

.200 mV/mA

Current gain

"

"

Voltage gain

"

"

Power gain

"

"

Closed-loop gain

.()

"

"

Open-loop gain

"

"

200000 50000

Common mode gain

()

.()

Rectifier efficiency

"

"

Microphone


.

Silver solder

.

Printed circuit board

.110

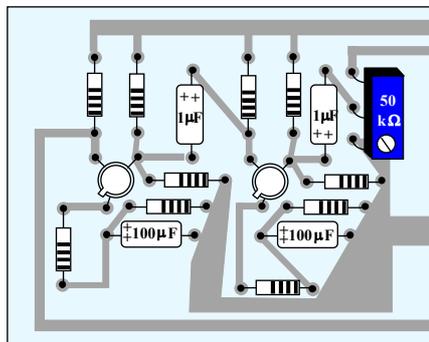

110

Protoboard

Lumen

Flux ()

Signal mixer

RF

.(10.7 MHz)

Maxwell

Center tap

Relay

Thermal relay

Oscilloscope



111

Curve Tracer

)

.(112




112

Temperature sensor

Decoder

16 4 8 3 4 2

113

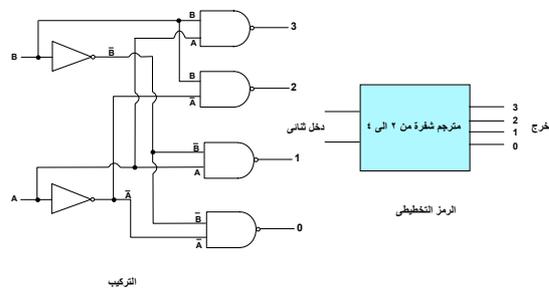

.4 2

113

AC/DC /

Neutral

.

Multivibrator

.

.

.

.()

.

Intermittent

Continuity

()

Thermostat

()

Electric field

Current divider

Collector

Limiter

FM limiter

(IF)

Motor-boating -

-1 :

-2 ()

Radio broadcast

Spectrum analyzer

(Domain)

Current to voltage converter

DC chopper

Dry type transformer

Depressor transformer

Oil transformer

Transducer

Acoustic transducer

Electroacoustic transducer /

/

Electromechanical transducer

()

.()

Electrochemical


transducer

Pulse transformers

Circuit diagram

Timing diagram

.114

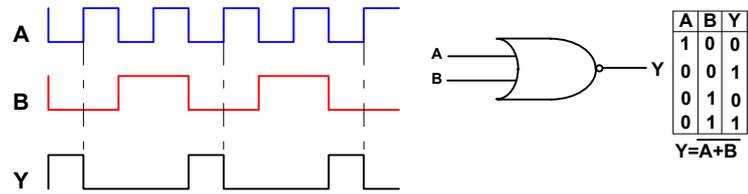

114

Vector diagram

.

Permanence

.

Capture range

.

f_0

Common mode range

.



$\pm 15V$


$\pm 10V$

Midrange

Oscillator

Tuned output oscillator

.115

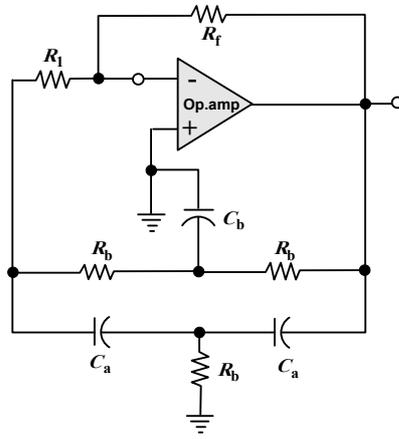

115

The Armstrong Oscillator


LC

.116

(tickler) " "

(L_P)

$$f_r = \frac{1}{2\pi} \sqrt{L_P C_1}$$

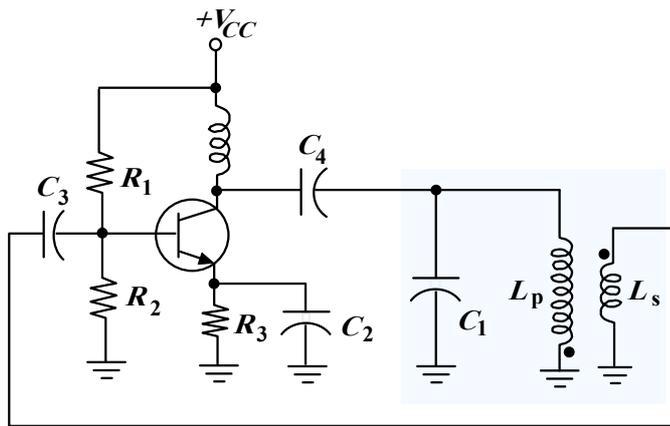

116

The phase shift oscillator


117

RC

.90°

.180° RC

180°

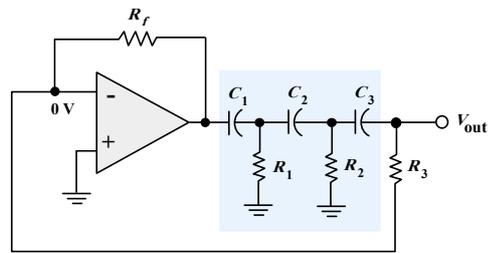

117

RC B

$$B = \frac{1}{29}$$

$$(R_3 \quad R_f) \quad 29$$

$$R_1 = R_2 = R_3 = R \quad f_r = \frac{1}{2\pi\sqrt{6RC}}$$

$$C_1 = C_2 = C_3 = C$$

Pierce oscillator

Twin –T Oscillator T

.RC *T*

T *RC*

.()118


T

(Band-stop) -

(Notch)

.()118

f_r

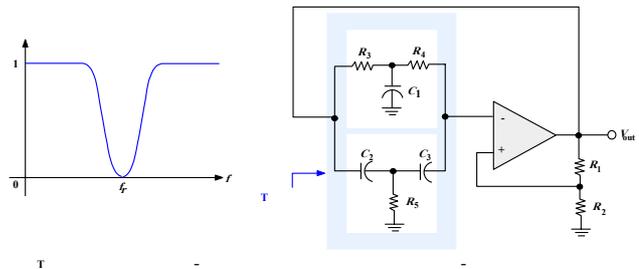

T - 118

f_r

f_r

(R_1, R_2)

R_1 ()

The Wien bridge oscillator

.120


C_1 R_1

: C_2 R_2

X_{C2} C_2

(f_r)

X_{C1}

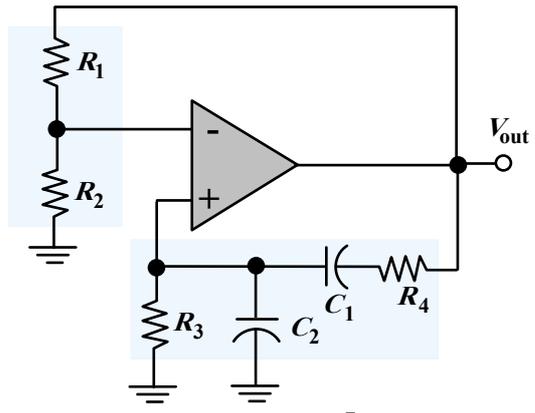


. " " 120

Clapp oscillator

C_3

.121
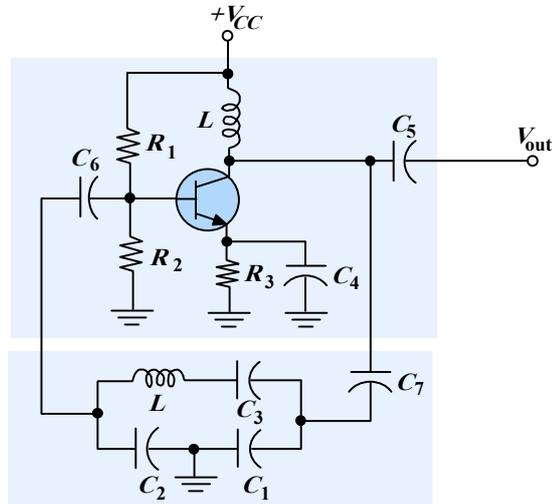
$$C_T \quad f_r \cong \frac{1}{2\pi\sqrt{LC_T}} \quad (Q = 10 \quad)$$




121

Colpitts oscillator

()

122

LC

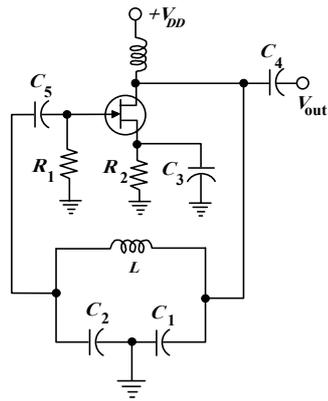

FET 122


Local oscillator

()

Hartley oscillator

$$Q > 10$$
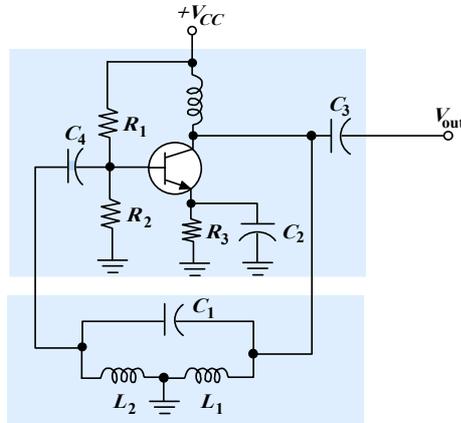
$$L_T = L_1 + L_2 \quad f_r \cong \frac{1}{2\pi\sqrt{L_T C_1}}$$



123

C_2 C_1

$$B \cong \frac{L_2}{L_1}$$

$$A_v > \frac{L_1}{L_2} \quad A_v > \frac{1}{B}$$

f_r

Q

Current mirror

-

.

Video

." I see "

Flip-flop

(bistable

.multivibrator)

)

)

(set

.(reset

.()

.

) .

.(

Zero-dB reference

—

.(0 dB)

—

(0 dB) 1

0 dB)

.(

Stage

.

Filter

.()

.

RL filter

RL

)

RL

.

(

Rectification filter

.124

-

(LP)

(HP)

RC

High-pass filter


Law-pass filter

The Sallen-Key high pass filter

-

-

.125

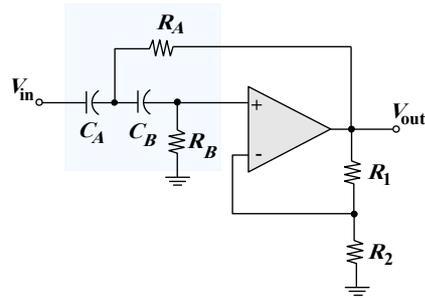

125

The Sallen-Key low pass

-

filter

-

VCVS


.(Voltage-controlled voltage source)

RC

-

126

-40dB/decade

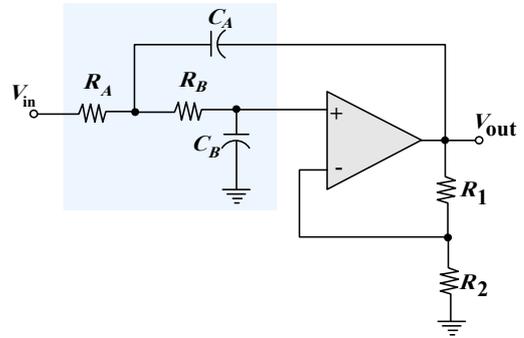

126

Band Stop filter

.(V)

High pass active filter

. *RC*

Active band pass filter

Passive filters

Active filter

Digitizer

Accumulator

-1 :

) -2

-3 (

.

Phase-locked loop

(PLL)

:

127

f_0

.

VCO

V_e

VCO

.VCO

.

V_d

VCO

VCO V_{CONT}

f_i


f_o (VCO)

PLL

VCO

ϕ

.LLP

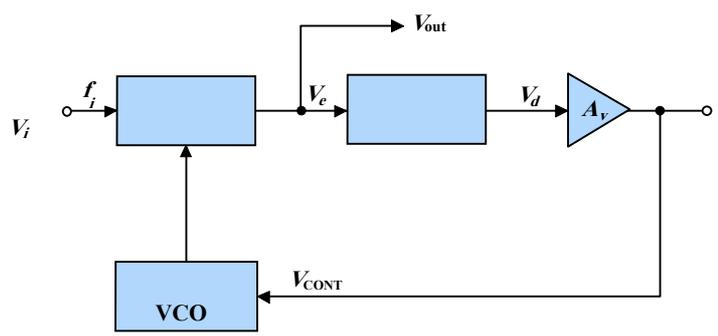

Closed-loop

Open-loop

Circuit admittance

Receiver

Sink

()

Alligator clip

)

(

Priority encoder

Binary coded decimal, BCD

.(1 0)

Drain

.

.

Power supply


()

128

.

.



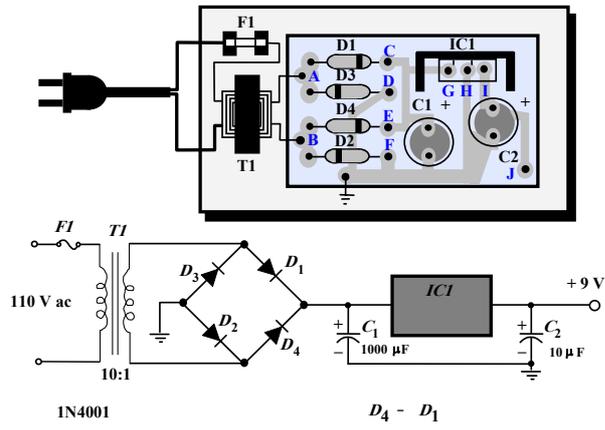

128

AC power supply

Constant-current source

Anode

Frequency multiplier

Voltage multiplier

.

129

C_1 :


V_P

$.D_2$ $2V_P$ C_1

$.2V_P$ D_3 C_2

C_3 C_1

$.3V_P$ $V_P + 2V_P$

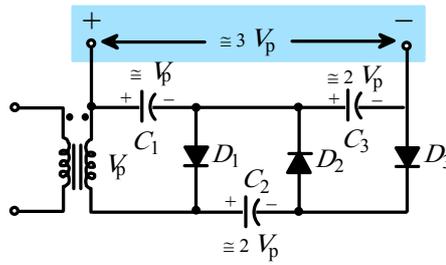


129

Scaling Adder

()

130
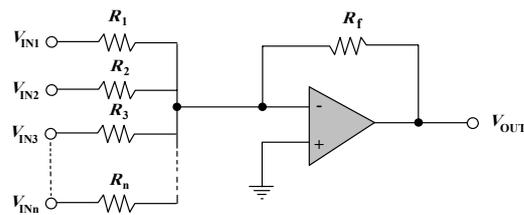
$$V_{OUT} = - \left(\frac{R_f}{R_1} V_{IN1} + \frac{R_f}{R_2} V_{IN2} + \dots + \frac{R_f}{R_n} V_{INn} \right)$$



n ()

130

R_f

$R \quad I$

$$R = \frac{0.5 R_f}{R + .2R_f}$$

Full adder

()

Phasing

()

Compliance

()

Automatic-data processing, ADP

DC Beta

Coefficient of coupling

DC alfa

Temperature coefficient of

frequency

Zener temperature-coefficient,

TC

1
0.1%/°C 12 V
0.012 V V_Z

Power loss factor

()

Hybrid parameters

(*h*)

h

.2

h	h	2
h_i		()
h_r		
h_f		
h_o		

Emitter impedance

Collector impedance

Op. Amp. output impedance



Op. Amp. Input impedance

Matched impedance

Roll off rate

20

.dB/Decade

40 dB/decade

dB/decade

60 dB/decade

Slew rate

(SR)

()

(step input voltage)


SR

/

Balanced modulator

(V_c)

(V_m)

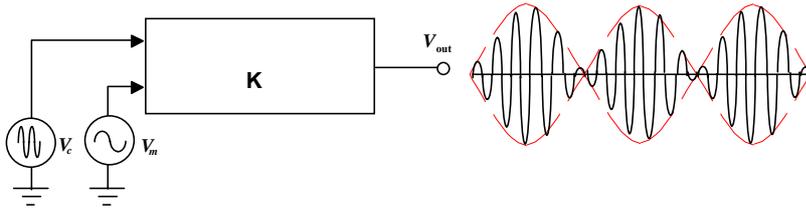

131

Ganged

)

(

Electromagnet

Differentiator

Duplexer

Single throw switch

Toggle switch

Silicon-controlled switch, SCS

(SCS)

SCS

(SCR)

SCS

SCR

SCS

.SCR

Dot convention

.

Comparator

()

.


Window comparator

.

.

Metal film resistor

.132

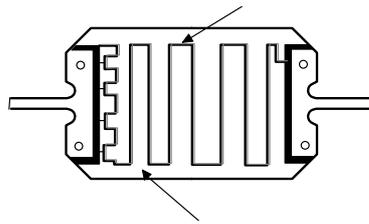

132

Drain-To-Source

()

Resistance

V_P

V_{DS}

V_{DS}

I_D

r_{ds}

Dropping resistor

Current limiting resistor

Thermistor

)

.)

Negative resistance

Positive resistance

Rectifier


Bridge rectifier

Full-wave rectifier

)

.(

133

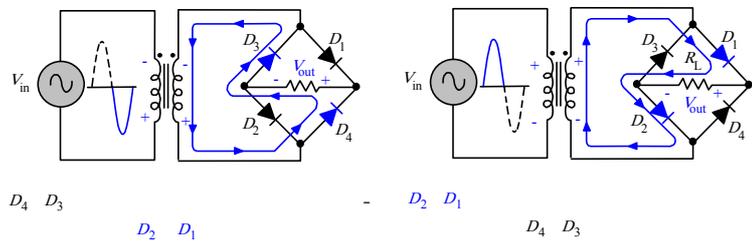

133

Center-tapped rectifier

Silicon-controlled rectifier

(SCR)

(npn)

SCR

SCR

SCR

()



Light-activated silicon

controlled rectifier

(LASCR)

SCR


LASCR

. SCR

() .

Half-wave rectifier

134

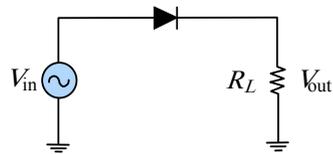

134

Ammeter

.

.

.

Multimeter

.

.()

/

Integrator

Amplifier

Instrumentation amplifier

(~300 mW)

($CMRR > 100$ dB)


) .

(

Small signal amplifier

Common-emitter amplifier

.135

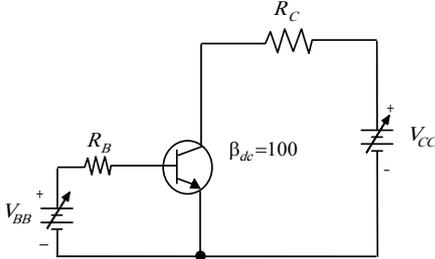

135

Common-gate amplifier


Intermediate frequency amplifier

Push-pull amplifier

Class A amplifier

- 136

180°

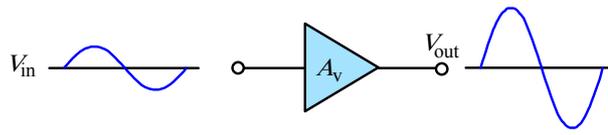

.() -

136

Class B amplifier -

180°

180°

.137

-

-


-

-

-

.

.

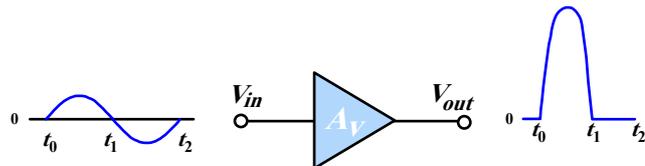

.() -

137

Class C amplifier -

-


138

180°

)

RF

(tuning

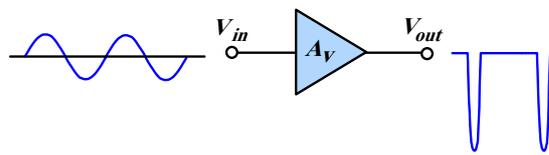


138

Complementary pair

pnp

npn

139

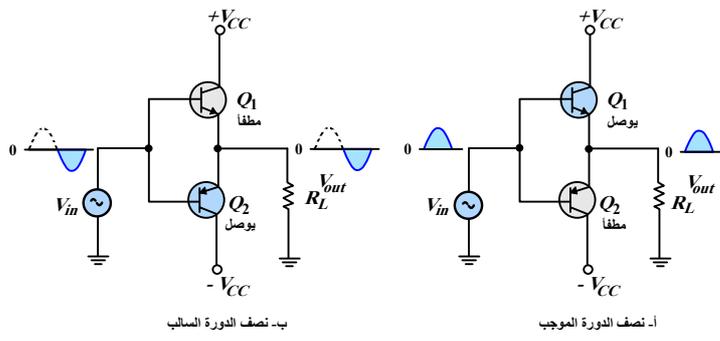


. () - - 139

Difference amplifier

Common-base amplifier

.140

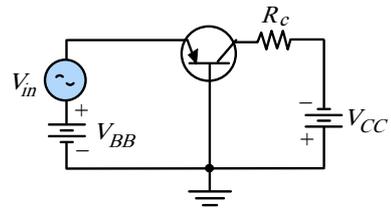

140

(CB)

CB

Averaging Amplifier

Common collector amplifier

(CC)

1

Common drain amplifier


Summing amplifier ()

Common source amplifier

Differential amplifier

)

.(

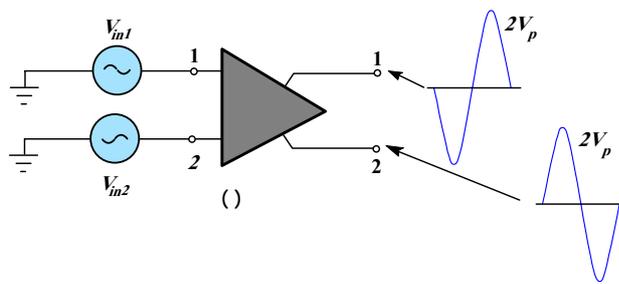

141

.141

Preamplifier


Audio amplifier

(AF)

Inverting amplifier

()

.142

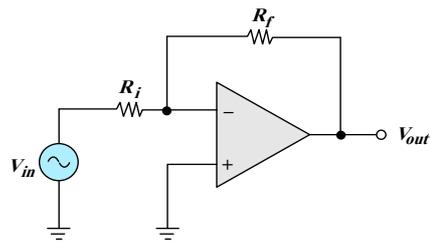

142

Noninverting amplifier


R_f R_i

R_f R_i

(V_f)

(V_{out})

.143

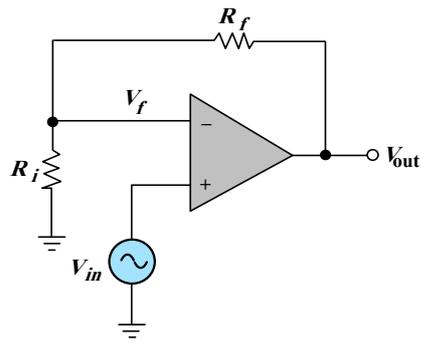

143

Power amplifier


Multistage amplifier

. () (

Tuned or frequency-selective

amplifier

()

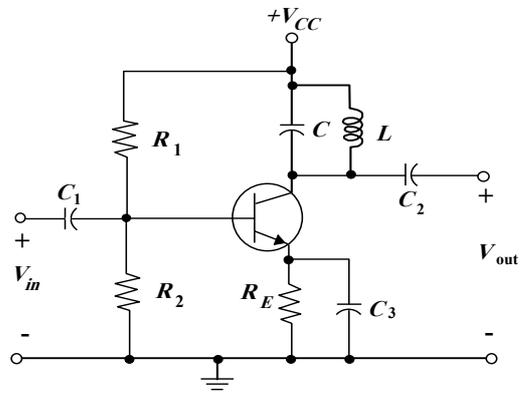

144

()

()


.144

Sense amplifiers

)

(

145

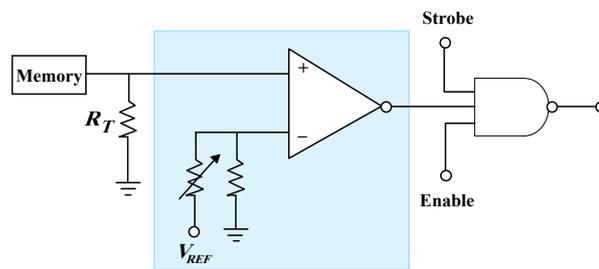


Untuned amplifiers

.(broadband amplifiers)

Speedup capacitor

Bypass capacitor

C_3 .146

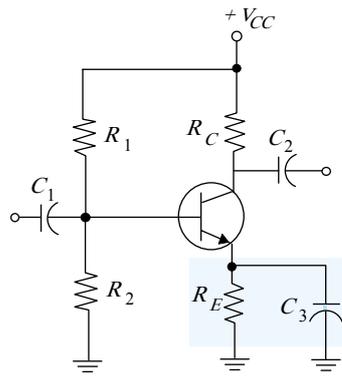

146

Tantalum capacitor

Coupling capacitor

C_1 146 .
.
 C_2

Electrolytic capacitor

Ceramic capacitor

Paper capacitor

Repeater

Toroidal coil

Solenoid

/

()

Bypass

Frequency discriminator

Source

Energized

Fuse

()

Direct-coupled transistor

logic

Resistor-transistor logic, RTL

—

—

Transistor-transistor logic, TTL

—

—

Diode-transistor logic, DTL

—

AND

OR

Voltage regulator



:

.(IC)

Adapter

Cathode

Sound waves

(20-2000 Hz)


Dekametric waves

Carrier wave

(RF)

Triangular wave


.147

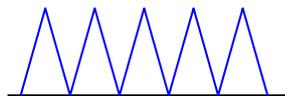

147


Square wave

.148

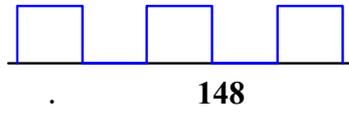

Rectangular wave

.149

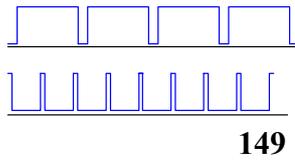

Horizontal polarized wave

Microwave

.EHF SHF UHF


Conductor

Solid Conductor

Superconductor

Function generator

150

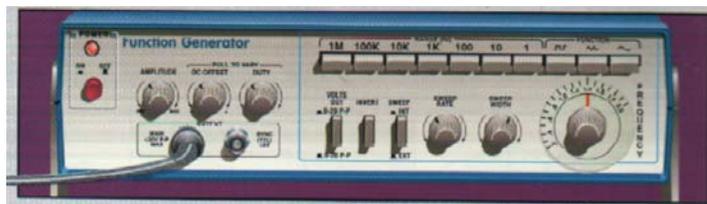

150

Pluses generator

AC generator

Enable pulse

Inhibit pulse

Mark-to-space ratio

()

Signal to noise ratio

DC Current Transfer Ratio

%100 %50

%50 —


.%500

Standoff ratio

Aspect ratio

4:3

.151

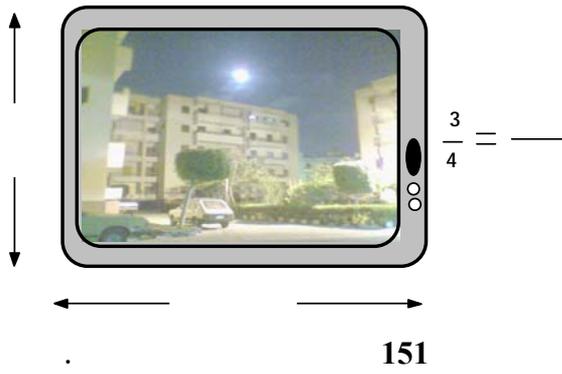

Common-mode rejection ratio,

CMRR

CMRR

CMRR

Power supply rejection ratio

Phase-alternation line, PAL

(phase-

alternation line)

50 625

Binary system

1 0 2

Passive system

Sequential with memory, SECAM

(Sequential

with memory)

Superposition theorem

)

(

Compensation theorem

"

(*I*)

(*R*)

()

(*V*)

$$V = IR$$

(R)

$$I = \frac{V}{R} \quad (I) \quad (V)$$

." ()

Pythagorean theorem

"


"

Thevenin theorem

"

()

()

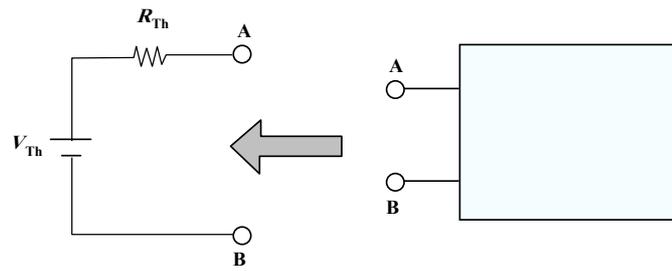

152

Miller's theorem

Norton theorem


"

()

()

.153

"

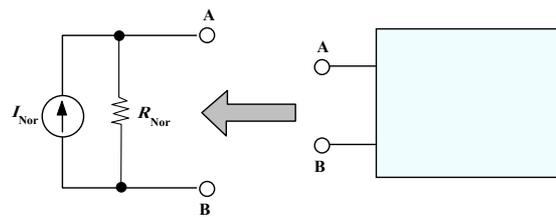

153

Transmission

-1 :

-2

Permeability

.□

Half-power points

Q point


Breakdown types

-1 :

-2 .

-3 .

154

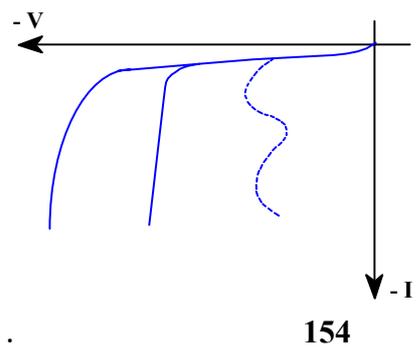

Diode types

()

-1 :

-2 .

-3 .

.

.

)

.

(

Mode

-2


-1 :

-3

Depletion mode

.(MOSFET) -

.()155

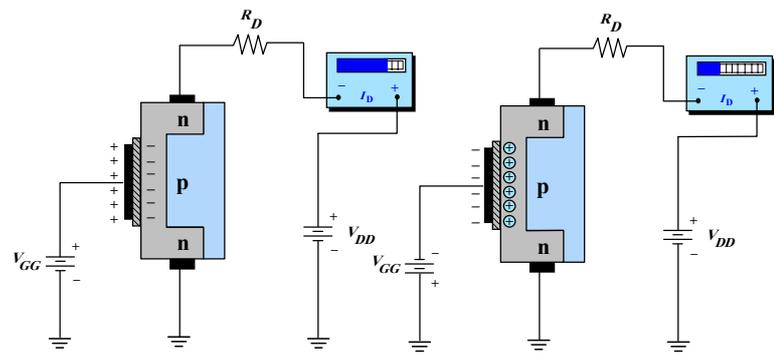

V_{GS}

$V_{GS(off)}$

V_{GS}

D-MOSFET

155

$(V_{GS(off)})$

MOSFET

JFET

$V_{GS(off)}$

V_{GS}

Enhancement mode

155 ()

()


Common-mode

.()

Intelligent communication terminals

Nucleus

156

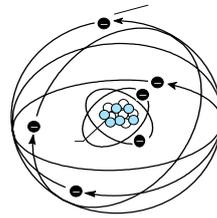

Telephone

Phase margin

180°

RC

(φ_{tot})

$\varphi_{\text{tot}} + 180^\circ$

φ_{pm}

.157


360°

$$180^\circ + \varphi_{\text{tot}} + \theta_{\text{pm}} = 360^\circ \quad (0 \quad 360^\circ)$$

$$\varphi_{\text{tot}} \quad \theta_{\text{pm}} = 180^\circ - |\varphi_{\text{tot}}|$$

180°

360°

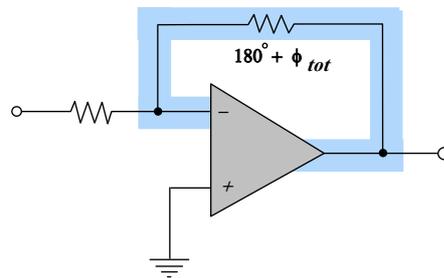

Diode drop

Thermal runaway

Receiving antenna

Transmitting antenna

Chassis

Execution unit

:

Arithmetic-logic unit, ALU

Visual Display unit

Junction

-2

-1 :

-3

1	Band width
2	Pulse width
2	Link
2	Radio communication
3	Coupling
3	Acoustic coupling
3	Optical couplers
5	AC coupling
5	Butterworth response
5	Bessel response
6	Frequency response
6	Chebyshev response
6	Phase response
6	Thermal stability
7	Stability
7	Electric polarization
8	Depletion
8	Electromagnetic communication
8	Attenuation
9	Reliability
9	Secondary emission
10	Photoemission
10	Diffusion and drift

11	Performance
12	Optical Fiber
12	Electronic tubes
13	Digital systems
14	Positive and negative logic systems
14	Electron
15	Emitter
15	Proton
16	Crystal
17	Ionization
17	Hysteresis
18	Transistor
21	Alloyed transistor
22	Unijunction transistor
23	Programmable unijunction transistor
25	The critical frequency
25	Triac
27	Saturation
28	Transistor linear operation
29	Transistor non-linear operation
29	Hanging
30	Feedback
30	Negative feedback
32	Acoustic feedback
32	Positive feedback
33	Transconductance
33	JFET
34	Electric current

35	Alternating overcurrents
35	Direct overcurrents
36	Thyristors
37	Boolean algebra
38	Electric potential
38	Transient state of circuit
39	Electromagnetic induction
39	Step
39	The differential Input
40	The inverting input
41	Single ended input
41	The Noninverting input
41	dB
42	DIAC
43	Stator
43	Internal capacitances of transistor
46	Siemens
46	Dominant network
46	Electric energy
47	The piezoelectric phenomena
47	Inverters
48	Counters
48	Atomic number
49	Alpha
49	Photon
49	Clipper
50	Trigger
51	Thermal triggering

51	Accidental triggering	
52	Triggering due light radiation	
52	Electric power	
53	The pole	
54	Electromotive force, emf	
54	Average value of periodic function	
55	Reactive value of periodic function	
55	Gain	
56	Overall gain	
57	Total gain	
57	Efficiency	
57	Electricity	
58	Coulomb	
58	Laser	
59	Timer 555	555
60	Electric field	
60	Magnetic field	
61	AC drives	
61	Synchronous drives	
61	DC drives	
62	Transformer	
63	Visible spectrum	
64	Active region	
64	Buffer	
65	Microprocessor	
65	Impedance	
65	Coil reactance	
66	The resistor	

67	Internal resistance	
67	The capacitor	
69	Clamper	
69	The induction coil	
70	Capacitance reactance	
70	Characteristic	
71	Characteristic curve	
71	Diode characteristic curve	
73	Collector characteristic curves	
75	Conductors	
76	Insulators	
76	Semiconductor	
77	Electromagnetic waves	
78	Line drivers and receivers	
79	Percent of regulation	
79	Signal sideband	
79	Quiescent point	
79	Acoustic transmission	
80	Antenna	
80	Atomic weight	
80	NP junction	
81	Absorption	
81	Thermoionic emission	
81	Field emission	
82	Propagation	()
82	Selectivity	
82	Maximum power transfer	
82	Drift	

83	Roll-off	
83	Gain roll-off	
84	Bias	
84	Emitter biasing	
85	Transistor biasing	
85	Collector feedback bias	
86	Base biasing	
87	Forward bias	
87	Reverse bias	
88	Voltage-divider biasing	
88	Midpoint Biasing	
88	Matching	
89	Impedance matching	
89	Diode opening	
89	Inversion	
90	Phase inversion	
90	Secondary breakdown	
91	Zener breakdown	
91	Reverse breakdown	
93	Skin effect	
93	Peltier effect	
94	Faraday's effect	
94	Hall's effect	
95	Tristate (or high impedance) devices	()
95	Monochromatic	
96	Minimum specifications	
96	RC	
96	Ground	

97	Virtual ground	
97	Floating ground	
97	Intrinsic semiconductors	
98	Extrinsic semiconductor	
98	Infrared light	
98	Maximum inverse voltage	
99	Maximum ratings	
99	Ampere	
99	Octave	
100	Telegraphy	
100	Interleaving	
100	Noises signals	
101	Large-signal	
101	Radiation	
102	Recombination	
102	Turn-off	
103	Conduction electron	
103	Free electron	
103	Battery	
103	Logic gates	
104	Gate	
105	OR gate	-
105	NOT gate	-
106	AND gate	-
106	NOR gate	-
107	NAND gate	-
107	Beta	
108	Emitter-follower	

108	Voltage-follower	
108	Source-follower	
108	Propagation delay	
108	Electro-luminescence	
109	Dissipation	
109	Abnormal dissipation	
109	Sampling	
109	Fold-back current limiting	
110	Automatic frequency control, AFC	
110	control, AGC Automatic gain	
111	voltage control AC line	
112	Speed control	
112	Frequency-domain analysis	-
113	Time-domain analysis	-
113	Loading	
113	A/D conversion	/
114	D/A conversion	/
114	Schematic	
114	Tapered	
114	Conventional current flow	
115	Abnormal oscillation	
115	E-MOSFET	
116	Dual gat MOSFET	MOSFET
117	Switching transistor	
117	Diffused base transistor	
117	Field effect transistor, FET	
118	MOSFET	-
119	Junction field effect transistor, JFET	

120	Darlington phototransistor	
120	Phototransistor	
122	General Purposes Transistors	
124	Radio frequency transistors	
124	Power Transistors	
125	Threshold frequency	
125	Cutoff frequency	
126	Center frequency	
126	RF	
126	High frequency, HF	
126	Super high frequency	
126	Unity gain frequency	
127	Intermediate frequency, IF	
127	Low frequency, LF	
127	Very low frequency	
127	Sum and difference frequencies	
128	Covalent	
129	Leakage	
129	Tesla	
130	Distortion	
130	Output distortion	
131	Crossover distortion	
132	Waveform distortion	
133	Zeroing	
133	Troubleshooting	
134	Doping	
134	Cascade	
134	Frequency-division multiplex, FDM	-

135	Modulation	
135	Frequency modulation, FM	
135	Amplitude modulation, AM	
136	Enhancement	()
136	Compensation	
137	Phase Lag Compensation	
137	Biasing current compensation in voltage follower	
137	Input Offset Voltage Compensation	
138	Discharge	
138	Dynamic convergence	
138	Bounding	
138	Valence	
139	Amplification	
139	Sintering	
139	Television	
140	Analog	
140	Load regulation	
141	Line regulation	
142	Interfacing	
142	Harmonic	
143	Transconductance	
143	Incandescence	
143	Holding current	
143	Surge current	
144	Majority current	
144	Minority current	
145	Switching current	
145	Dark current	

145	Runway collector current
146	Bleeding current
146	Input bias current
146	Collector leakage current
146	Static reverse current
147	current Gate trigger
147	Alternating current
147	Eddy currents
147	Time constant
148	Dielectric constant
148	Bipolar
148	Truth table
149	Device
149	Forward-breakover voltage
150	Ripple voltage
150	Pinch-off voltage
152	Potential barrier
152	Open circuit voltage
152	Knee voltage
153	Isolation voltage
153	Cutoff voltage
153	Input offset voltage
154	AC voltage
154	carriers Majority
154	Minority carriers
155	Mutual inductance
155	Distributed inductance
155	Instrument sensitivity

155	Load	
156	Inductive load	
156	Least significant bit, LSB	
156	Most significant bit, MSB	
156	Output	
157	Load line	
157	AC Load Line	
158	DC Load Line	
159	Measurement error	
160	Linear	
160	Primary cell	
160	Memory cell	
160	Secondary cell	
161	Mercury cell	
161	Photo-voltaic or solar cell	-
162	Alkaline cell	
162	Nickel-cadmium cell	-
162	Squaring circuit	
163	Single-phase rectifier	
163	Three-phase rectifier	
164	Constant current circuit	
164	Resonance circuit	
165	Integrated circuit	
165	Closed circuit television	
165	Hybrid circuit	
166	Dry circuit	
166	Parallel resonance circuit	
166	Astable circuit	

167	Medium-scale integrated circuit, MSI	
167	Metal work function	
168	Commutator	
168	Diode	
169	PIN	PIN
170	Step-recovery diode	
171	LASER Diode	
172	Gun diode	
172	Tunnel diode	
172	Light emitted diode	
174	Surface-barrier diode	
174	Zener diode	
175	Schottky diode	
176	Shockley diode	
176	Photodiode	
177	VARACTOR diode	
178	Input	
178	Common mode input	
179	Floating input	
180	Voltage commutation	
180	Load commutation	
180	Current commutation	
180	Forced-commutation	
181	Control circuits	
181	Commutation circuits	
181	circuits Snubber	
182	intrinsic	
182	Memories	

183	Acoustic memory	
183	Atom	
184	Germanium atom	
184	Silicon atom	
185	Trivalent atom	
185	Pentavalent atom	
185	Ionic bond	
185	Covalent bond	
186	Radar	
186	Order	
186	Bode-Plot	
187	Binary digit	
188	Digital	
188	Resonance	
188	Phase angle	
189	Hold time	
189	Propagation time	
189	Turn-off time	
189	Delay time	
190	Storage time	
190	Electron-hole pair	-
191	Darlington pair	
191	Electronic clock	
192	Registers	
192	registers Shift	
192	Mounting capacitance	
192	Distributed capacitance	
193	Miller's output capacitance	

193	Muller's input capacitance	
194	R-2R ladder	R-2R
195	Permittivity	
195	Speaker	
195	Audio	
195	Sonar	
196	Charger	
196	Phase splitter	
196	RC networks	RC
196	Network	
197	Bypass RC network	RC
197	Output RC-network	RC
197	Input RC-network	RC
198	N- Type semiconductor	
199	P- Type semiconductor	
199	Grid	
200	Electric charge	
200	Dielectric strength	
200	Magnetic field intensity	
200	Spark	
200	Oscillation conditions	
201	Oscillation start up conditions	
202	Interface latch chip	
202	Chip	
203	Band	()
203	High fidelity, Hi Fi	
203	Pulse code	
204	Resistance color code	

205	Acceptors	
205	Donors	
206	Data sheet	
206	Gain-bandwidth product	-
207	Coherent light	
207	Depletion layer	
208	Terminal	
208	Phase	
208	Wave length	
209	Spectrum	
209	Spectral	
209	Insulator	
209	Mycalex	
209	Damping factor	
210	Ripple factor	
210	Quality factor	
211	Power factor	
211	Crowbar	
212	Binary counter	
212	Decade	
212	Electronics	
213	Optoelectronics	
214	Power electronics	
214	Radio astronomy	
214	Passive component	
214	Active component	
215	Opto-isolators	
215	Filament	

215	Hole	
215	Energy gap	
216	Test	
216	Diode investigation	
218	Potential difference	
218	Copper loss	
218	Thermal overload	
219	Ultrasonic	
219	Flux	
219	Ferrite	
219	Schmitt trigger	
220	Circuit breaker	
220	Base	
220	Left-hand rule	-
221	Right-hand rule	-
221	Ohm's law	
222	Faraday law	
223	Coulomb law	
223	Kirchhoff's law for current	
224	Kirchhoff's law for voltage	
224	Lenz law	
225	Gate triggering	
225	Thyristor triggering	
225	Trimmer	
225	Diode shorting	
226	Dead short	
226	Cutoff	
226	Core	

226	Laminated core
227	Magnetic core
227	Channel
227	Response measurement using discret point methode
229	Response measurement using sweep frequency
230	Telemetry
230	Peak value
230	Cathode
230	Detector
231	Automatic-direction finder, ADF
231	Zero current detector
232	Phase detector
232	Peak detector
233	Lie detector
233	FM detector
234	Resistive temperature detector
234	Thin film detector
234	Magnetic flux density
235	Transfer Gain
235	Current gain
235	Voltage gain
235	Power gain
235	Closed-loop gain
236	Open-loop gain
236	Common mode gain
237	Rectifier efficiency

237	Microphone	
237	Silver solder	
238	Printed circuit board	
238	Protoboard	
239	Lumen	
239	Flux	()
239	Signal mixer	
239	Maxwell	
240	Center tap	
240	Relay	
240	Thermal relay	
240	Oscilloscope	
241	Curve Tracer	
242	Temperature sensor	
242	Decoder	
242	AC/DC	/
243	Neutral	
243	Multivibrator	
244	Intermittent	
244	Continuity	
244	Thermostat	
244	Electric field	
245	Current divider	
245	Collector	
245	Limiter	
245	FM limiter	
246	Motor-boating	-
246	Radio broadcast	

247	Spectrum analyzer	
247	Current to voltage converter	
247	DC chopper	
248	Dry type transformer	
248	Depressor transformer	
248	Oil transformer	
248	Transducer	
248	Acoustic transducer	
249	Electroacoustic transducer	/
249	Electrochemical transducer	
249	Electromechanical transducer	
249	Pulse transformers	
250	Circuit diagram	
250	Timing diagram	
251	Vector diagram	
251	Permanence	
251	Capture range	
251	Common mode range	
252	Midrange	
252	Oscillator	
252	oscillator Tuned output	
253	The Armstrong Oscillator	
254	The phase shift oscillator	
256	Pierce oscillator	
256	Twin –T Oscillator	T
257	The Wien bridge oscillator	
258	Clapp oscillator	
259	Colpitts oscillator	

260	Local oscillator	
260	Hartley oscillator	
262	Current mirror	
262	Video	
262	Flip-flop	
263	Zero-dB reference	-
263	Stage	
264	Filter	
264	RL filter	RL
264	Rectification filter	
265	Band pass filter	
265	State-variable band pass filter	
266	High-pass filter	
266	Low-pass filter	
267	The Sallen-Key high pass filter	-
267	The Sallen-Key low pass filter	-
268	Band Stop filter	
269	High pass active filter	
269	Active band pass filter	
270	filters Passive	
270	Active filter	
270	Digitizer	
271	Accumulator	
271	Phase-locked loop	
273	Closed-loop	
273	Open-loop	
273	Circuit admittance	
274	Receiver	

274	Sink
274	Alligator clip
274	Priority encoder
275	Binary coded decimal, BCD
275	Drain
275	Power supply
276	AC power supply
276	Constant-current source
276	Anode
277	Frequency multiplier
277	Voltage multiplier
278	Scaling Adder
279	Full adder
279	Phasing
279	Compliance
280	Automatic-data processing, ADP
280	DC Beta
280	Coefficient of coupling
280	DC alfa
280	Temperature coefficient of frequency
280	Zener temperature coefficient, TC
281	Power loss factor
281	Hybrid parameters
282	Emitter impedance
282	Collector impedance
282	Op. Amp. output impedance
283	impedance Op. Amp. Input
283	Matched impedance

283	Roll off rate
284	Slew rate
284	Balanced modulator
285	Ganged
286	Electromagnet
286	Differentiator
286	Duplexer
286	Single throw switch
287	Toggle switch
287	Silicon-controlled switch, SCS
288	Dot convention
288	Comparator
288	Window comparator
289	Metal film resistor
289	Drain-To-Source Resistance
290	Dropping resistor
290	Current limiting resistor
290	Thermistor
291	Negative resistance
291	Positive resistance
291	Rectifier
292	Bridge rectifier
292	Full-wave rectifier
293	Center-tapped rectifier
293	Silicon-controlled rectifier
294	Light-activated silicon controlled rectifier
294	Half-wave rectifier
295	Ammeter

295	Multimeter	
295	Integrator	
296	Amplifier	
296	Instrumentation amplifier	
297	Small signal amplifier	
297	Common-emitter amplifier	
298	Common-gate amplifier	
298	Intermediate frequency amplifier	
298	Push-pull amplifier	-
298	amplifier Class A	-
299	Class B amplifier	-
299	Class C amplifier	-
300	Complementary pair	
301	Difference amplifier	
301	Common-base amplifier	
302	Averaging Amplifier	
302	Common collector amplifier	
303	Common drain amplifier	
303	Summing amplifier	()
303	Common source amplifier	
304	Differential amplifier	
305	Preamplifier	
305	Audio amplifier	
305	Inverting amplifier	
306	Noninverting amplifier	
307	Power amplifier	
307	Multistage amplifier	
308	Tuned or frequency-selective amplifier	

309	Sense amplifiers	
310	Untuned amplifiers	
310	Speedup capacitor	
310	Bypass capacitor	
311	Tantalum capacitor	
311	Coupling capacitor	
312	Electrolytic capacitor	
312	Ceramic capacitor	
312	Paper capacitor	
313	Repeater	
313	Toroidal coil	
313	Solenoid	
314	Bypass	
314	Frequency discriminator	
314	Source	
314	Energized	
314	Fuse	
315	Direct-coupled transistor logic	
315	Resistor-transistor logic, RTL	-
315	Transistor-transistor logic, TTL	-
316	Diode-transistor logic, DTL	-
316	Voltage regulator	
317	Adapter	
317	Cathode	
317	Sound waves	
318	Dekametric waves	
318	Carrier wave	
318	Triangular wave	

319	Square wave
319	Rectangular wave
319	Horizontal polarized wave
320	Microwave
320	Conductor
320	Solid Conductor
320	Superconductor
321	Function generator
321	AC generator
321	Pluses generator
322	Enable pulse
322	Inhibit pulse
322	Mark-to-space ratio
322	Signal to noise ratio
322	DC Current Transfer Ratio
323	Standoff ratio
323	Aspect ratio
324	Common-mode rejection ratio, CMRR
324	Power supply rejection ratio
324	Phase-alternation line, PAL
325	Binary system
325	Passive system
325	Sequential with memory, SECAM
326	Superposition theorem
326	theorem Compensation
327	Pythagorean theorem
327	Thevenin theorem
328	Miller's theorem

328	Norton theorem
329	Transmission
329	Permeability
330	Half-power points
330	Q point
330	Breakdown types
331	Diode types
332	Mode
332	Depletion mode
334	Enhancement mode
335	Common-mode
335	Intelligent communication terminals
335	Nucleus
335	Telephone
336	Phase margin
337	Diode drop
337	Thermal runaway
338	Receiving antenna
338	Transmitting antenna
338	Chassis
338	Execution unit
339	Arithmetic-logic unit, ALU
339	Visual Display unit
339	Junction

فهرس المصطلحات

A/D conversion	/	113
Abnormal dissipation		109
Abnormal oscillation		115
Absorption		81
AC coupling		5
AC drives		61
AC generator		321
voltage control AC line		111
AC Load Line		157
AC power supply		276
AC voltage		154
AC/DC	/	242
Acceptors		205
Accidental triggering		51
Accumulator		271
Acoustic coupling		3
Acoustic feedback		32
Acoustic memory		183

Acoustic transducer	248
Acoustic transmission	79
Active band pass filter	269
Active component	214
Active filter	270
Active region	64
Adapter	317
Alkaline cell	162
Alligator clip	274
Alloyed transistor	21
Alpha	49
Alternating current	147
Alternating overcurrents	35
Ammeter	295
Ampere	99
Amplification	139
Amplifier	296
Amplitude modulation, AM	135
Analog	140

AND gate	-	106
Anode		276
Antenna		80
Arithmetic-logic unit, ALU		339
Aspect ratio		323
Astable circuit		166
Atom		183
Atomic number		48
Atomic weight		80
Attenuation		8
Audio		195
Audio amplifier		305
Automatic frequency control, AFC		110
control, AGC Automatic gain		110
Automatic-data processing, ADP		280
Automatic-direction finder, ADF		231
Average value of periodic function		54
Averaging Amplifier		302

B alanced modulator	284
Band ()	203
Band pass filter	265
Band Stop filter	268
Band width	1
Base	220
Base biasing	86
Battery	103
Bessel response	5
Beta	107
Bias	84
Biasing current compensation in voltage follower	137
Binary coded decimal, BCD	275
Binary counter	212
Binary digit	187
Binary system	325
Bipolar	148
Bleeding current	146
Bode-Plot	186

Boolean algebra		37
Bounding		138
Breakdown types		330
Bridge rectifier		292
Buffer		64
Butterworth response		5
Bypass		314
Bypass capacitor		310
Bypass RC network	RC	197
C apacitance reactance		70
Capture range		251
Carrier wave		318
Cascade		134
Cathode		230
Cathode		317
Center frequency		126
Center tap		240
Center-tapped rectifier		293
Ceramic capacitor		312
Channel		227

Characteristic		70
Characteristic curve		71
Charger		196
Chassis		338
Chebyshev response		6
Chip		202
Circuit admittance		273
Circuit breaker		220
Circuit diagram		250
Clamper		69
Clapp oscillator		258
amplifier Class A	-	298
Class B amplifier	-	299
Class C amplifier	-	299
Clipper		49
Closed circuit television		165
Closed-loop		273
Closed-loop gain		235
Coefficient of coupling		280
Coherent light		207

Coil reactance	65
Collector	245
Collector characteristic curves	73
Collector feedback bias	85
Collector impedance	282
Collector leakage current	146
Colpitts oscillator	259
Common collector amplifier	302
Common drain amplifier	303
Common mode gain	236
Common mode input	178
Common mode range	251
Common source amplifier	303
Common-base amplifier	301
Common-emitter amplifier	297
Common-gate amplifier	298
Common-mode	335
Common-mode rejection ratio, CMRR	324
Commutation circuits	181
Commutator	168

Comparator	288
Compensation	136
theorem Compensation	326
Complementary pair	300
Compliance	279
Conduction electron	103
Conductor	320
Conductors	75
Constant current circuit	164
Constant-current source	276
Continuity	244
Control circuits	181
Conventional current flow	114
Copper loss	218
Core	226
Coulomb	58
Coulomb law	223
Counters	48
Coupling	3
Coupling capacitor	311

Covalent	128
Covalent bond	185
Crossover distortion	131
Crowbar	211
Crystal	16
Current commutation	180
Current divider	245
Current gain	235
Current limiting resistor	290
Current mirror	262
Current to voltage converter	247
Curve Tracer	241
Cutoff	226
Cutoff frequency	125
Cutoff voltage	153
D /A conversion	/ 114
Damping factor	209
Dark current	145
Darlington pair	191

Darlington phototransistor	120
Data sheet	206
dB	41
DC alfa	280
DC Beta	280
DC chopper	247
DC Current Transfer Ratio	322
DC drives	61
DC Load Line	158
Dead short	226
Decade	212
Decoder	242
Dekametric waves	318
Delay time	189
Depletion	8
Depletion layer	207
Depletion mode	332
Depressor transformer	248

Detector	230
Device	149
DIAC	42
Dielectric constant	148
Dielectric strength	200
Difference amplifier	301
Differential amplifier	304
Differentiator	286
Diffused base transistor	117
Diffusion and drift	10
Digital	188
Digital systems	13
Digitizer	270
Diode	168
Diode characteristic curve	71
Diode drop	337
Diode investigation	216
Diode opening	89
Diode shorting	225
Diode types	331

Diode-transistor logic, DTL	-	316
Direct overcurrents		35
Direct-coupled transistor logic		315
Discharge		138
Dissipation		109
Distortion		130
Distributed capacitance		192
Distributed inductance		155
Dominant network		46
Donors		205
Doping		134
Dot convention		288
Drain		275
Drain-To-Source Resistance		289
Drift		82
Dropping resistor		290
Dry circuit		166
Dry type transformer		248

Dual gat MOSFET	MOSFET	116
Duplexer		286
Dynamic convergence		138
E ddy currents		147
Efficiency		57
Electric charge		200
Electric current		34
Electric energy		46
Electric field		60
Electric field		244
Electric polarization		7
Electric potential		38
Electric power		52
Electricity		57
Electroacoustic transducer	/	249
Electrochemical transducer		249
Electro-luminescence		108
Electrolytic capacitor		312
Electromagnet		286

Electromagnetic communication		8
Electromagnetic induction		39
Electromagnetic waves		77
Electromechanical transducer		249
Electromotive force, emf		54
Electron		14
Electron-hole pair	-	190
Electronic clock		191
Electronic tubes		12
Electronics		212
Emitter		15
Emitter biasing		84
Emitter impedance		282
Emitter-follower		108
E-MOSFET		115
Enable pulse		322
Energized		314
Energy gap		215
Enhancement	()	136
Enhancement mode		334

Execution unit	338
Extrinsic semiconductor	98
F araday law	222
Faraday's effect	94
Feedback	30
Ferrite	219
Field effect transistor, FET	117
Field emission	81
Filament	215
Filter	264
Flip-flop	262
Floating ground	97
Floating input	179
Flux	219
Flux ()	239
FM detector	233
FM limiter	245
Fold-back current limiting	109
Forced-commutation	180
Forward bias	87

Forward-breakover voltage		149
Free electron		103
Frequency discriminator		314
Frequency modulation, FM		135
Frequency multiplier		277
Frequency response		6
Frequency-division multiplex, FDM	-	134
Frequency-domain analysis	-	112
Full adder		279
Full-wave rectifier		292
Function generator		321
Fuse		314
Gain		55
Gain roll-off		83
Gain-bandwidth product	-	206
Ganged		285
Gate		104
current Gate trigger		147
Gate triggering		225
General Purposes Transistors		122

Germanium atom	184
Grid	199
Ground	96
Gun diode	172
H alf-power points	330
Half-wave rectifier	294
Hall's effect	94
Hanging	29
Harmonic	142
Hartley oscillator	260
High fidelity, Hi Fi	203
High frequency, HF	126
High pass active filter	269
High-pass filter	266
Hold time	189
Holding current	143
Hole	215
Horizontal polarized wave	319
Hybrid circuit	165

Hybrid parameters	281
Hysteresis	17
I mpedance	65
Impedance matching	89
Incandescence	143
Inductive load	156
Infrared light	98
Inhibit pulse	322
Input	178
Input bias current	146
Input offset voltage	153
Input Offset Voltage Compensation	137
Input RC-network	RC 197
Instrument sensitivity	155
Instrumentation amplifier	296
Insulator	209
Insulators	76
Integrated circuit	165
Integrator	295
Intelligent communication terminals	335

Interface latch chip	202
Interfacing	142
Interleaving	100
Intermediate frequency amplifier	298
Intermediate frequency, IF	127
Intermittent	244
Internal capacitances of transistor	43
Internal resistance	67
Intrinsic	182
Intrinsic semiconductors	97
Inversion	89
Inverters	47
Inverting amplifier	305
Ionic bond	185
Ionization	17
Isolation voltage	153
J_{FET}	33
Junction	339

Junction field effect transistor, JFET	119
K irchhoff's law for current	223
Kirchhoff's law for voltage	224
Knee voltage	152
L aminated core	226
Large-signal	101
Laser	58
LASER Diode	171
Law-pass filter	266
Leakage	129
Least significant bit, LSB	156
Left-hand rule	- 220
Lenz law	224
Lie detector	233
Light emitted diode	172
Light-activated silicon controlled rectifier	294
Limiter	245

Line drivers and receivers	78
Line regulation	141
Linear	160
Link	2
Load	155
Load commutation	180
Load line	157
Load regulation	140
Loading	113
Local oscillator	260
Logic gates	103
Low frequency, LF	127
Lumen	239
Magnetic core	227
Magnetic field	60
Magnetic field intensity	200
Magnetic flux density	234
carriers Majority	154
Majority current	144

Mark-to-space ratio	322
Matched impedance	283
Matching	88
Maximum inverse voltage	98
Maximum power transfer	82
Maximum ratings	99
Maxwell	239
Measurement error	159
Medium-scale integrated circuit, MSI	167
Memories	182
Memory cell	160
Mercury cell	161
Metal film resistor	289
Metal work function	167
Microphone	237
Microprocessor	65
Microwave	320
Midpoint Biasing	88
Midrange	252
Miller's theorem	328

Miller's output capacitance	193
Minimum specifications	96
Minority carriers	154
Minority current	144
Mode	332
Modulation	135
Monochromatic	95
MOSFET	118
Most significant bit, MSB	156
Motor-boating	246
Mounting capacitance	192
Muller's input capacitance	193
Multimeter	295
Multistage amplifier	307
Multivibrator	243
Mutual inductance	155
Mycalex	209
N-Type semiconductor	198

NAND gate	-	107
Negative feedback		30
Negative resistance		291
Network		196
Neutral		243
Nickel-cadmium cell	-	162
Noises signals		100
Noninverting amplifier		306
NOR gate	-	106
Norton theorem		328
NOT gate	-	105
NP junction		80
Nucleus		335
Octave		99
Ohm's law		221
Oil transformer		248
impedance Op. Amp. Input		283
Op. Amp. output impedance		282
Open circuit voltage		152
Open-loop		273

Open-loop gain		236
Optical couplers		3
Optical Fiber		12
Optoelectronics		213
Opto-isolators		215
OR gate	-	105
Order		186
Oscillation conditions		200
Oscillation start up conditions		201
Oscillator		252
Oscilloscope		240
Output		156
Output distortion		130
Output RC-network	RC	197
Overall gain		56
P - Type semiconductor		199
Paper capacitor		312
Parallel resonance circuit		166
Passive component		214

filters Passive	270
Passive system	325
Peak detector	232
Peak value	230
Peltier effect	93
Pentavalent atom	185
Percent of regulation	79
Performance	11
Perimitivity	195
Permanence	251
Permeability	329
Phase	208
Phase angle	188
Phase detector	232
Phase inversion	90
Phase Lag Compensation	137
Phase margin	336
Phase response	6
Phase splitter	196
Phase-alternation line, PAL	324

Phase-locked loop	مسار الطور المنغلق	271
Phasing	مطابرة	279
Photodiode	دايود فوتونى	176
Photoemission	الاتبعات الفوتونى	10
Photon	الفوتون	49
Phototransistor	ترانزستور فوتونى	120
Photo-voltaic or solar cell	خلية ضوئية - جهديه	161
Pierce oscillator	مذبذب بييرس	256
PIN	دايود PIN	169
Pinch-off voltage	جهد التلاقي	150
Pluses generator	مولد نبضات	321
Positive and negative logic systems	الأنظمة المنطقية الموجبة والسالبة	14
Positive feedback	التغذية المرتدة الموجبة	32
Positive resistance	مقاومة موجبة	291
Potential barrier	جهد الحاجز	152
Potential difference	فرق الجهد	218
Power amplifier	مكبر قدرة	307
Power electronics	علم إلكترونيات القدرة	214
Power factor	عامل القدرة	211

Power gain	كسب القدرة	235
Power loss factor	معامل فقد القدرة	281
Power supply	مصدر القدرة	275
Power supply rejection ratio	نسبة رفض مصدر القدرة	324
Power Transistors	ترانزستورات القدرة	124
Preamplifier	مكبر تمهيدي	305
Primary cell	خلية ابتدائية	160
Printed circuit board	لوحة الدائرة المطبوعة	238
Priority encoder	مشفر الأسبقية	274
Programmable unijunction transistor	الترانزستور أحادي الوصلة القابل للبرمجة	23
Propagation	انتشار (بث)	82
Propagation delay	تأخير الانتشار	108
Propagation time	زمن الانتشار	189
Protoboard	لوحة أولية	238
Proton	البروتون	15
Pulse code	شفرة النبضة	203
Pulse transformers	محولات النبضة	249
Pulse width	اتساع النبضة	2
Push-pull amplifier	مكبر الدفع - الجذب	298

Pythagorean theorem	نظرية بايثاجوران	327
Q point	نقطة التشغيل	330
Quality factor	عامل الجودة	210
Quiescent point	النقطة الهامدة	79
R -2R ladder	سلم R-2R	194
Radar	رادار	186
Radiation	إشعاع	101
Radio astronomy	علم الفلك الراديوى	214
Radio broadcast	محطة بث راديوى	246
Radio communication	اتصال راديوى	2
Radio frequency transistors	ترانزستورات التردد الراديوى	124
RC	أر سى	96
RC networks	شبكات RC	196
Reactive value of periodic function	القيمة المفاعلة للدالة الدورية	55
Receiver	مستقبل	274
Receiving antenna	هوائى استقبال	338
Recombination	إعادة إتحاد	102
Rectangular wave	موجة مستطيلة	319
Rectification filter	مرشح التقويم	264
Rectifier	مقوم	291

Rectifier efficiency	كفاءة المقوم	237
Registers	سجلات	192
Relay	مبدل	240
Reliability	الاعتمادية	9
Repeater	مكرر	313
Resistance color code	شفرة ألوان المقاومة	204
Resistive temperature detector	كاشف درجة الحرارة المقاومى	234
Resistor-transistor logic, RTL	منطق المقاومة-ترانزستور	315
Resonance	رنين	188
Resonance circuit	دائرة الرنين	164
Response measurement using discret point methode	قياس استجابة المرشح بطريقة النقطة المحددة	227
Response measurement using sweep frequency	قياس استجابة المرشح بطريقة مسح التردد	229
Reverse bias	انحياز عكسي	87
Reverse breakdown	انهيار عكسي	91
RF	تردد راديوى	126
Right-hand rule	قاعدة اليد-اليمنى	221
Ripple factor	عامل التموج	210

Ripple voltage	جهد التآرجح	150
RL filter	مرشح RL	264
Roll off rate	معدل الاتحدار	283
Roll-off	انحصار	83
Runway collector current	تيار المجمع الشارد	145
S ampling	تحديد العينات	109
Saturation	التشبع	27
Scaling Adder	مضيف القياس	278
Schematic	تخطيطي	114
Schmitt trigger	قادح شमित	219
Schottky diode	دايود شوتكى	175
Secondary breakdown	انهيار ثانوي	90
Secondary cell	خلية ثانوية	160
Secondary emission	الانبعاث الثانوي	9
Selectivity	انتقائية	82
Semiconductor	المواد شبه الموصله	76
Sense amplifiers	مكبرات حساسه	309
Sequential with memory, SECAM	نظام سيكام	325
registers Shift	سجلات الإزاحة	192
Shockley diode	دايود شوكلى	176

Siemens	السيمنز	46
Signal mixer	مازج إشارة	239
Signal sideband	النطاق الجانبي للإشارة	79
Signal to noise ratio	نسبة الإشارة إلى الضوضاء	322
Silicon atom	ذرة السليكون	184
Silicon-controlled rectifier	مقوم منضبط سيليكوني	293
Silicon-controlled switch, SCS	مفتاح منضبط سيليكوني	287
Silver solder	لحام فضة	237
Single ended input	الدخل أحادي النهاية	41
Single throw switch	مفتاح رمية واحدة	286
Single-phase rectifier	دائرة التقويم أحادية الطور	163
Sink	مسرب	274
Sintering	تلبد	139
Skin effect	أثر السطحية	93
Slew rate	معدل الانزلاق	284
Small signal amplifier	مكبر الإشارة الضعيفة	297
circuits Snubber	دوائر المصدات	181
Solenoid	ملف لولبي	313
Solid Conductor	موصل أصم	320
Sonar	سونار	195

Sound waves	موجات صوتية	317
Source	منبع	314
Source-follower	تابع المنبع	108
Spark	شرارة	200
Speaker	سماعة	195
Spectral	طيفي	209
Spectrum	طيف	209
Spectrum analyzer	محلل الطيف	247
Speed control	تحكم سرعة	112
Speedup capacitor	مكثف الإسراع	310
Square wave	موجة مربعة	319
Squaring circuit	دائرة التربيع	162
Stability	استقرارية	7
Stage	مرحلة	263
Standoff ratio	نسبة التحفظ	323
State-variable band pass filter	مرشح تمرير شريط الحالة المتغيرة	265
Static reverse current	تيار عكسي ساكن	146
Stator	الساكن	43
Step	الخطوة	39

Step-recovery diode	دايود الاسترجاع التدريجي	170
Storage time	زمن التخزين	190
Sum and difference frequencies	ترددات المجموع والفرق	127
Summing amplifier	مكبر المضيف (الجمع)	303
Super high frequency	تردد فائق العلو	126
Superconductor	موصل فائق	320
Superposition theorem	نظرية التراكب	326
Surface-barrier diode	دايود حاجز السطح	174
Surge current	تيار الاندفاع	143
Switching current	تيار التحول	145
Switching transistor	ترانزستور التحول	117
Synchronous drives	المحركات المتزامنة	61
T antalum capacitor	مكثف التنتالوم	311
Tapered	تدرج	114
Telegraphy	إبراق	100
Telemetry	قياس عن بعد	230
Telephone	هاتف	335
Television	تلفزيون	139
Temperature coefficient of frequency	معامل درجة الحرارة للتردد	280
Temperature sensor	متحسس الحرارة	242

Terminal	طرف	208
Tesla	تسلا	129
Test	فحص	216
The Armstrong Oscillator	مذبذب أرمسترونج	253
The capacitor	المكثف	67
The critical frequency	التردد الحرج	25
The differential Input	الدخل التفاضلي	39
The induction coil	الملف الحثي	69
The inverting input	الدخل العاكس	40
The Noninverting input	الدخل غير العاكس	41
The phase shift oscillator	مذبذب إزاحة الطور	254
The piezoelectric phenomena	الظاهرة الكهروضغطية	47
The pole	القطب	53
The resistor	المقاوم	66
The Sallen-Key high pass filter	مرشح سالين-كي للتمرير العالي	267
The Sallen-Key low pass filter	مرشح سالين-كي للتمرير المنخفض	267
The Wien bridge oscillator	مذبذب قنطرة فين	257
Thermal overload	فوق الحمل الحراري	218

Thermal relay	مبدل حراري	240
Thermal runaway	هروب حراري	337
Thermal stability	استقرار حراري	6
Thermal triggering	القدح الحراري	51
Thermistor	مقاومة حرارية	290
Thermoionic emission	انبعاث الأيونات الحراري	81
Thermostat	مثبت حراري	244
Thevenin theorem	نظرية ثيفينين	327
Thin film detector	كاشف ذو غشاء رقيق	234
Three-phase rectifier	دائرة التقويم ثلاثية الطور	163
Threshold frequency	تردد العتبة	125
Thyristor triggering	قدح الثايروستور	225
Thyristors	الثايروستورات	36
Time constant	ثابت الزمن	147
Time-domain analysis	تحليل حدود- الزمن	113
Timer 555	المؤقت 555	59
Timing diagram	مخطط زمني	250
Toggle switch	مفتاح مفصلي	287
Toroidal coil	ملف حلقي	313
Total gain	الكسب الكلي	57

Transconductance	التوصيلية الانتقالية	33
Transconductance	توصيلية انتقالية	143
Transducer	محول طاقة	248
Transfer Gain	كسب الانتقال	235
Transformer	المحول	62
Transient state of circuit	الحالة الانتقالية للدائرة	38
Transistor	الترانزستور	18
Transistor biasing	انحياز الترانزستور	85
Transistor linear operation	التشغيل الخطي للترانزستور	28
Transistor non-linear operation	التشغيل غير الخطي للترانزستور	29
Transistor-transistor logic, TTL	منطق ترانزستور- ترانزستور	315
Transmission	نفاذ	329
Transmitting antenna	هوائي إرسال	338
Triac	الترياك	25
Triangular wave	موجة مثلثيه	318
Trigger	القدح	50
Triggering due light radiation	القدح نتيجة الإشعاع الضوئي	52
Trimmer	قصاصه	225

Tristate (or high impedance) devices	أجهزة الحالة الثلاثية (أو المعاوقة الكبيرة)	95
Trivalent atom	ذرة ثلاثية التكافؤ	185
Troubleshooting	تصويب الأعطال	133
Truth table	جدول الصدق	148
Tuned or frequency-selective amplifier	مكبر متناغم أو منتقى للتردد	308
oscillator Tuned output	مذبذب الخرج المتناغم	252
Tunnel diode	دايود النفق	172
Turn-off	إغلاق	102
Turn-off time	زمن الإطفاء	189
Twin –T Oscillator	مذبذب توأم T	256
Ultrasonic	فوق صوتيه	219
Unijunction transistor	الترانزستور أحادى الوصلة	22
Unity gain frequency	تردد كسب الوحدة	126
Untuned amplifiers	مكبرات غير المتناغمة	310
Valence	تكافؤ	138
VARACTOR diode	دايود متغير السعة	177
Vector diagram	مخطط متجهي	251
Very low frequency	تردد منخفض جدا	127
Video	مرئي	262

Virtual ground	أرضى افتراضى	97
Visible spectrum	المدى المرئى من الطيف	63
Visual Display unit	وحدة عرض مرئية	339
Voltage commutation	دمج الجهد	180
Voltage gain	كسب الجهد	235
Voltage multiplier	مضاعف الجهد	277
Voltage regulator	منظم الجهد	316
Voltage-divider biasing	انحياز مجزئ الجهد	88
Voltage-follower	تابع الجهد	108
Wave length	طول موجى	208
Waveform distortion	تشوه شكل الموجة	132
Window comparator	مقارن النافذة	288
Zener breakdown	انهيار زينر	91
Zener diode	دايود زينر	174
Zener temperature coefficient, TC	معامل درجة الحرارة للزينر	280
Zero current detector	كاشف التيار الصفرى	231
Zero-dB reference	مرجع الديسيبل-الصفرى	263
Zeroing	تصفير	133

بعض المراجع المفيدة

REFERENCES

- Circuit Encyclopedia and Troubleshooting Guide, Vol. 1 & 2 , John D Lenk, McGraw-Hill, USA 1993.
 - Basic Electronics: Devices, Circuits and Systems, Michael M Cirovic, 2nd Edition, 1979, Reston Publishing Company, Inc. A Prentice-Hall company, USA.
 - Power Electronics: Devices, Circuits and Industrial Applications, V R Moorthi, Oxford University Press, 2005, USA.
 - Electronic Devices, Thomas L Floyd, 3rd Edition, Macmillan Publishing Company, 1992 USA.
 - Industrial Electronic, Noel Morris, 2nd Edition, McGraw-Hill Book Company, 1970, UK.
 - Electronics, D C Green, 5th Edition. Essex 1997, England.
 - A comprehensive Dictionary of Electrical Engennering, A. A. Al-Awsi, Arab Scientific Publisher, Biriut, 1988, Lebnon
 - الدوائر الكهربائية والالكترونية، د.يوسف محمود حفيظة، المركز الوطني لتخطيط التعليم والتدريب، طرابلس 2003-2004.
 - قاموس المصطلحات الكمبيوترية، قسم البحوث والدراسات التقنية بدار الراتب الجامعية، بيروت - لبنان.
-
-



/

- /
1975

-
50

)

.(