

تم تحميل هذا الملف من موقع المناهج الإماراتية



\*للحصول على أوراق عمل لجميع الصفوف وجميع المواد اضغط هنا

<https://almanahj.com/ae>

\* للحصول على أوراق عمل لجميع مواد الصف الثاني عشر اضغط هنا [12/ae/com.almanahj//:https](https://almanahj.com/ae/12)

\* للحصول على جميع أوراق الصف الثاني عشر في مادة تصميم ولجميع الفصول, اضغط هنا [12design/ae/com.almanahj//:https](https://almanahj.com/ae/12design)

\* للحصول على أوراق عمل لجميع مواد الصف الثاني عشر في مادة تصميم الخاصة بـ الفصل الثاني اضغط هنا

<https://almanahj.com/ae/12design2>


\* لتحميل كتب جميع المواد في جميع الفصول للـ الصف الثاني عشر اضغط هنا [grade12/ae/com.almanahj//:https](https://almanahj.com/ae/grade12)

للتحدث إلى بوت المناهج على تلغرام: اضغط هنا [bot\\_almanahj/me.t//:https](https://t.me/bot_almanahj)



# Pop Quiz 1 - 12 Advanced

@grade12ua\_e

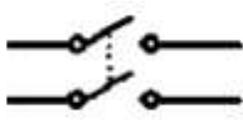Grade	12 ADVANCED	Chapter / Section	3.1 – Electrical Vehicle components
Student Name		Class	
Date			
1	<b>The speed of an AC motor is controlled by _____.</b>		
	A	changing the amount of electrical current passed through the motor	
	B	fixing the frequency of the source	
	C	fixing the amount of electrical current passed through the motor	
	D	varying the frequency of the source	
2	<b>Both AC &amp; DC motors convert electrical energy into _____ energy.</b>		
	A	chemical	
	B	elastic	
	C	mechanical	
	D	radiant	
3	<b>Identify the type of switch shown in the image below.</b>		
	A	single-pole single-throw	
	B	double-pole single-throw	
	C	single-pole double-throw	
	D	double-pole double-throw	
			
4	<b>A microcontroller is _____.</b>		
	A	a small semiconductor chip	
	B	a computer processor responsible for all calculations	
	C	a central control chip	
	D	an embedded system which does not run an operating system	
5	<b>Motor drivers _____.</b>		
	A	control the speed and direction of motors	
	B	only control the speed of a motor	
	C	only control the direction of a motor	
	D	control the Arduino	



# Pop Quiz 1 - 12 Advanced

6	<b>Bluetooth signals are transmitted by _____ waves.</b>	
	A	micro
	B	infrared
	C	ultraviolet
7	<b>Which pin on the Arduino board receives commands from the Bluetooth module?</b>	
	A	Tx
	B	Rx
	C	Data
8	<b>Identify the component shown.</b>	
	A	Micro processor
	B	Motor driver
	C	Bluetooth module
9	<b>What is the name of data that is sent to the Bluetooth module?</b>	
	A	messages
	B	comments
	C	minutes
10	<b>The Bluetooth Module should always be connected to _____ pin on the Arduino.</b>	
	A	3.3 V
	B	4 V
	C	5 V
		
<b>TOTAL MARKS</b>		<b>/ 10</b>