

# INDEX

- ABCD matrix, 54, 57, 63, 77, 476–9  
active antenna, 95, 97–9  
active circuits, 86, 95–9, 290–299  
active CRLH LWA, 289  
active filter, 290, 298–300  
active unilateral coupling, 291  
admittance inverter, 63, 259, 359, 425–7  
admittance matrix, 33, 172, 173  
aggressive space mapping (ASM), 204, 239, 491–5, 497–500  
air bridges, 29, 437  
alignment sensors, 316–24  
all-pass structure, 60, 411, 432, 503, 504  
alternate right-/left-handed (ARLH), 255–8  
Ampere law, 465  
anisotropy, 135, 346, 347  
anomalous dispersion, 441  
antenna directivity, 283  
antennas, 17, 30, 31, 47, 48, 66, 95, 97–9, 122, 164, 165, 214, 215, 219, 242, 244, 267, 282–90, 303–14, 316, 317, 378, 381–4, 406, 408, 447, 453  
antipodal printed dipole antennas, 31  
ARLH transmission line, 257, 258  
artificial materials, 119, 120, 440  
artificial periodic structures, 120  
artificial plasma, 123, 134  
artificial transmission lines, 1–5, 7, 19, 29, 31, 37, 44, 47–114, 120–122, 127, 131, 141, 216, 218, 231, 250, 251, 273, 339–95, 402, 428–41, 444, 472  
attenuation, 17, 19, 24, 25, 57, 78, 82, 85, 253, 381, 430  
attenuation constant, 6, 17–19, 21, 22, 24, 25, 27, 28, 49, 52, 53, 283, 285, 287, 288  
auxiliary uniform transmission line, 65, 68  
  
backfire, 52, 284  
backfire-to-endfire, 284  
backward Cerenkov radiation, 127, 129–31  
backward leaky wave antenna, 164  
backward leaky wave radiation, 127, 131, 285  
backward leaky waves, 53, 127, 131, 163, 164, 285  
backward media, 123, 125  
backward travelling waves, 42, 51, 63, 70  
backward wave propagation, 122, 125, 127, 128, 131, 158, 189, 204, 260, 438–40

- backward waves, 51, 122, 125–9, 131, 150, 151, 158, 187, 189, 204, 229, 260, 438–40
- backward-to-forward frequency scanning, 285
- backward-to-forward radiation, 285
- balance condition, 182, 236, 284, 432
- balanced artificial lines, 428
- balanced band pass filter, 418, 423–9
- balanced CRLH line, 156, 157, 220, 236, 270, 284, 423, 428, 445
- balanced hybrid cell, 263, 266, 268
- balanced transmission lines, 30, 411–29
- band pass filters, 362
- bandwidth, 24, 36, 40, 44, 48, 50, 65, 77, 78, 82, 87, 95, 99–101, 107, 109, 135, 143, 164, 165, 167, 183, 188, 189, 205, 215–25, 228, 240, 242, 251, 253, 257, 259–63, 267, 268, 270, 271, 273, 275–7, 290, 293, 295, 296, 305, 307, 308, 316, 326, 352, 362, 364, 367, 381, 405–8, 411–21, 424–6, 439–41, 444
- barium strontium titanate (BST), 345, 346, 375–7
- barium titanate ( $\text{BaTiO}_3$ ), 345
- beam steering, 381, 384
- bi-anisotropy, 135, 144
- biosensors, 302
- Biot–Savart law, 480
- bipolar junction transistor (BJT), 97
- bisymmetric resonators, 145, 320
- Bloch impedance, 56–64, 103, 105, 106, 120, 150–152, 155, 157, 159
- Bloch mode analysis, 48
- Bloch mode theory, 185
- Bloch waves, 48, 49, 53, 55, 56, 64, 77, 87
- Bragg condition, 51
- Bragg frequency, 86, 87, 92, 385–7, 393
- Bragg reflector, 93
- Bragg resonators, 92, 94
- branch line hybrid coupler, 228, 231, 240, 242–4, 249, 298
- bridged-T, 162, 430, 437–9, 503, 504
  - network, 430, 438, 439, 503
  - topology, 437–9, 504
- bright solitons, 395
- Brillouin diagram, 103
- Brillouin zone, 50, 51, 104
- broadband matching, 157
- broadside, 52, 144, 283, 284, 289, 384, 445
- broadside radiation, 283, 284
- broadside-coupled SRR (BC-SRR), 142–3, 146, 148
- Broyden matrix, 493, 495, 498, 499
- Butterworth low pass filter, 33
- cantilever beams, 342–4, 362–4
- cantilever RF-MEMS, 342, 362, 363, 372
- cantilever-type SRR, 362, 372, 374, 375
- capacitively loaded lines, 4, 104, 105, 107, 108, 111, 120
- carbon-doped resistive lines, 364
- characteristic dimension, 32
- characteristic impedance, 6–8, 13, 14, 17–19, 29–33, 36, 39, 42, 43, 54, 56, 57, 60, 62–4, 68, 78, 81–4, 87, 93, 99, 101, 103, 105, 110, 114, 120, 121, 151, 152, 154, 156–8, 168, 176, 177, 181–3, 205, 206, 214–17, 219, 221, 223, 224, 228–31, 233, 234, 237–40, 246–8, 260, 273, 289, 291, 296, 311, 323, 379, 380, 417, 429, 432–5, 437, 438, 442, 466–8, 474, 482, 489, 490, 495
- Chebyshev band pass filter, 275, 421, 426
- Chebyshev low pass filter, 39
- chipless RFID, 316, 406, 407
- chipless tags, 406–11
- chirp parameter, 99
- chirped delay lines (CDL), 86, 99–102
- chirping, 87
- circuit dual, 182, 404
- circulator, 123, 313, 324, 325, 409
- CL-loaded approach, 162–6, 204, 347
- closed waveguide, 65
- coarse model, 492–7, 500
- coaxial line, 1, 4, 467
- combiners, 40, 298, 299, 302
- common-mode
  - characteristic impedance, 114
  - filters, 316, 411, 412, 414, 416, 418–20, 425
  - impedance, 114
  - insertion loss, 413, 421
  - noise, 411, 412, 414, 421
  - noise rejection, 411, 421
  - stop band, 415
  - suppression, 114, 195, 402, 411–29

- common-mode rejection ratio (CMRR), 421, 425, 428
- complementary resonators, 146–9, 444
- complementary split ring resonator (CSRR), 147–9, 162, 167, 177–87, 189–96, 204–6, 223, 224, 226, 234, 236–40, 244, 245, 250–251, 253, 255, 257, 258, 262, 267, 269–71, 273, 315–17, 352–4, 356, 358, 370, 404, 405, 412–18, 444–6, 486–9, 491–7, 500
- complementary SR (CSR), 148, 240
- complex amplitudes, 65, 69, 70, 72, 75, 77, 483
- complex mode amplitude, 69–70
- complex modes, 55, 183, 187–9
- complex permittivity, 20
- complex propagation constant, 6, 17, 18, 25, 183, 186, 462
- complex waves, 183, 188
- composite right/left handed (CRLH), 122, 177, 182
- conduction
  - attenuation constant, 24, 28
  - current, 20, 25, 27, 135
  - current density, 20, 27
- conductivity, 17, 19–21, 25, 26, 147, 462, 480
- conductor losses, 5, 17, 18, 22, 25–8
- conductor-backed CPW, 29
- conjugate matching, 310–312
- constant reactance circumference, 470
- constant resistance circumference, 470, 471
- continuous medium, 120
- continuous spectrum, 65, 66
- conversion efficiency, 386, 393–5
- coplanar strips (CPS), 30, 31, 93
- coplanar waveguides (CPW), 4, 8, 29, 30, 33, 37, 68, 93, 105–8, 148, 162–5, 167–74, 176, 182, 191, 192, 194–8, 200, 202, 203, 225, 246–9, 251, 252, 255, 256, 270, 272, 273, 277, 279, 282, 285, 287, 289, 315–17, 319, 320, 322–7, 356–8, 360, 361, 370, 373, 376, 435, 437, 453, 467, 489
- coupled line microstrip band pass filters, 93, 254
- coupled lines, 31, 93–7, 101, 114, 251–7, 263, 265, 416, 435, 437
- coupled microstrip, 31, 437
- coupled mode equations, 65–7, 79–86, 101, 482–5
- coupled mode theory, 48, 64–86, 102
- coupled resonator band pass filters, 107
- couplers, 40, 108, 114, 215, 221, 223, 224, 226, 228, 231, 232, 240, 242–4, 249, 290, 298–300, 385, 403, 406, 447, 449
- coupling coefficient, 66–8, 70–73, 78–85, 88, 91, 99, 103, 221, 367, 482–3, 485
- CPW *see* coplanar waveguides (CPW)
- CPW band pass filters, 105–8, 255
- CRLH lines, 122, 154, 156–9, 161, 162, 164–7, 172, 182, 183, 195, 196, 200, 203, 215, 218–21, 231, 234, 236, 239, 240, 246, 249, 250, 270, 273, 274, 284, 289, 291, 296, 298–302, 376–8, 381, 385, 402, 423, 428, 430, 432–4, 437, 439, 440, 444–53
- CRLH-sensors, 302
- CRLH transmission line, 131, 150, 154–67, 172, 181–3, 195, 196, 200, 202, 203, 205, 214–304, 375–8, 380, 381, 385, 394, 402, 423, 428–30, 432–7, 439, 440, 444–53
- cross polarizabilities, 137, 138, 142
- cross polarization, 147, 191, 307
- cross-section method, 65–9
- crosstalk, 30, 411
- CSRR/gap-loaded lines, 234, 237–40, 487, 488, 494, 497
- CSRR/gap-loaded microstrip lines, 178, 181, 186, 191, 195, 239, 240
- CSRR-loaded microstrip lines, 178, 183, 185, 186, 191, 193, 195, 251, 355, 444, 445, 493, 495
- Curie temperature, 344, 345
- current density, 20, 27, 412, 480–481
- dark solitons, 395
- D-CRLH transmission line, 158–62
- Debye model, 135
- defect ground structures, 412
- defected ground planes, 48
- delay lines, 86, 99–102, 299, 402–11
- detuning, 314, 317, 318
- diamagnetic behavior, 136, 142, 144
- dielectric
  - attenuation constant, 24

- constant, 2, 8, 22, 23, 25, 34, 36, 38, 39, 43, 44, 68, 81, 85, 86, 90–93, 97, 100, 101, 107, 110, 142, 148, 170, 178, 180, 184, 185, 192, 193, 196, 197, 199, 201, 203, 206, 223, 234, 237, 244, 245, 248, 254, 256, 258, 263, 267, 269, 271–3, 276, 279, 280, 289, 311, 319, 323, 326, 345, 349, 355, 359, 363, 378, 383, 408, 417, 419, 421, 422, 426, 428, 442, 444, 453, 484–5, 496
- flux, 346
- loading, 300, 302, 315
- losses, 5, 6, 17–25, 83, 85, 346
- permittivity, 8, 20, 122, 135, 344, 345, 375
- differential band pass filter, 411, 421–3
- differential lines, 30, 114, 143, 195, 316, 411–22
- differential microstrip line, 31, 316, 411–13, 415
- differential port, 30
- differential sensor, 302, 304
- differential signal, 114, 411, 412, 414, 418, 420
- differential transmission lines, 402, 411
- differential-mode, 114, 412, 414, 419, 423–8
  - characteristic impedance, 114
  - impedance, 114
  - insertion loss, 413
- diffusion, 340
- diplexer meta-distributed amplifier, 296
- diplexers, 215, 242, 244–5, 250–282, 296, 297, 444–5
- discrete modes, 65–7, 295
- dispersion
  - engineering, 214, 215, 293
  - relation, 7, 54–9, 77, 102–5, 132, 140, 141, 154, 168, 176, 177, 181, 186–9, 403–6, 416, 432, 434, 437, 438, 503, 504
- displacement
  - current, 25, 135, 388, 480
  - flux, 19
  - sensors, 317, 318
- dissipation, 17, 344
- distortionless lines, 18, 19
- distributed amplifiers, 215, 290–298
- distributed circuit approach, 2
- distributed microwave components, 225
- distributed mixer, 290, 291
- distributed transconductance, 290, 291
- double Lorentz metamaterial transmission line, 159, 250
- double negative (DNG) media, 123
- double positive (DPS) media, 124
- double slit complementary SRR (DS-CSRR), 148, 414–22
- double slit SRR (DS-SRR), 143–4, 415
- drain line, 290, 291, 293, 295, 296
- Drude model, 134, 135, 182
- Drude–Lorentz model, 127, 135, 439
- DS-CSRR *see* double slit complementary SRR (DS-CSRR)
- DS-SRR *see* double slit SRR (DS-SRR)
- dual CRLH (D-CRLH) transmission line, 158–9
- dual-band
  - antenna, 305–7, 310, 311, 453
  - devices, 228–46, 273, 299
  - diplexer, 242, 244, 296, 297
  - filters, 298, 447
  - LWA, 289, 447, 453
  - matching networks, 310
  - UHF-RFID tag antennas, 311
  - UHF-RFID tags, 310–314
- dual-band band pass filter, 275, 277, 278
- dual-band band-stop filter, 244
- dual-band branch line hybrid coupler, 228, 231, 240, 243, 244
- dual-band meta-distributed amplifier, 296–8
- dual-band printed monopole antennas, 308
- dual-band recursive active filters, 290, 298–300
- duality, 142, 146–9, 404, 406, 415
- dumbbell-shaped resonators, 412, 413
- dumbbell-shaped slotted resonators, 412
- dynamic range, 302, 317, 320, 322, 324
- EBG *see* electromagnetic bandgaps (EBG)
- EBG reflectors, 86, 92
- EBG-based active circuits, 95
- EBG-based transmission lines, 71, 88, 93, 102
- E-CRLH SIW, 447, 452, 453
- effective complex permittivity, 20
- effective constitutive parameters, 152, 153, 167, 182

- effective dielectric constant, 8, 22, 23, 68, 100, 484–5  
 effective medium, 120–149, 151  
 effective medium metamaterials, 120–149  
 effective parameters, 120, 467  
 effective permeability, 120, 136–41, 147, 153, 168, 175, 176, 349, 440, 467  
 effective permittivity, 20, 22, 120, 123, 131–6, 141, 147, 153, 159, 167, 175–7, 346, 354, 439–41, 444, 445, 467  
 eigenmodes, 55, 186, 188, 189  
 eigenvalues, 55, 186, 187  
 eigenvectors, 55  
 EIRP *see* equivalent isotropic radiated power (EIRP)  
 EIW *see* electroinductive waves (EIW)  
 EIW lines, 402, 403, 405, 406  
 ELC *see* electric LC resonator (ELC)  
 electric dipole moments, 19, 134, 139  
 electric displacement, 20  
 electric LC resonator (ELC), 145–6, 148, 320, 322–4  
 electric polarization, 19, 344, 346  
 electric susceptibility, 19, 20, 134, 138  
 electric wall, 29, 31, 136, 145, 146, 315, 320, 324, 411, 421, 423, 425  
 electrical length, 7, 8, 12, 31, 32, 35, 36, 63, 93, 109, 110, 214, 215, 219, 231, 234, 237–40, 246, 248, 264  
 electroinductive waves (EIW), 187–9, 402–6  
 electromagnetic bandgaps (EBG), 47, 75, 77–9, 81–92, 95, 97–100, 114, 120, 251, 252  
 electromagnetic interference (EMI), 30, 411  
 electromagnetic metamaterials, 121  
 electron mean free path, 135  
 elliptic low pass filters, 33, 37  
 EMI *see* electromagnetic interference (EMI)  
 endfire, 52, 284  
 enhanced bandwidth components, 215–25  
 envelope detector, 324, 325, 340, 409  
 envelope solitons, 394  
 ENZ *see* epsilon-near-zero (ENZ)  
 epsilon negative-ENG-structures, 123  
 epsilon-near-zero (ENZ), 439–42  
 equivalent isotropic radiated power (EIRP), 312, 313  
 evanescent modes, 65, 188, 189  
 evanescent waves, 187  
 even mode, 285, 315, 411, 415, 416, 418, 421  
 extended CRLH (E-CRLH) transmission line, 159  
 external quality factor, 367  
 eye  
   diagram, 420  
   height, 420, 421  
   opening factor, 420, 421  
   width, 420  
 Fabry–Perot like resonances, 101  
 fast wave, 47, 51, 52, 130, 164, 283–5, 440  
 FBW *see* fractional bandwidth (FBW)  
 ferroelectric materials, 344–7, 375–7  
 ferromagnetic materials, 344  
 fiber Bragg gratings, 87  
 field theory, 2, 4, 467  
 filter central frequency, 93, 251, 260, 261, 275, 352, 359, 364, 367, 416, 425  
 filters, 13, 47, 120, 215, 340, 411, 414–18, 421  
 fine model, 492–4, 497–9  
 first neighbor approximation, 185, 403, 405  
 fishnet structures, 131  
 fixed-fixed beam RF-MEMS, 370  
 Floquet analysis, 48–53, 71  
 Floquet’s theorem, 48, 54  
 focusing, 127  
 folded complementary SIR, 148  
 folded dipole antenna, 314  
 folded stepped impedance resonator, 32, 141, 421  
 forward gain, 291, 293, 295  
 forward leaky waves, 53, 289, 453  
 forward output port, 290, 291  
 forward transmission line, 151, 153, 293  
 forward travelling waves, 51, 483  
 forward wave propagation, 149, 158, 438, 445  
 forward waves, 51, 149, 150, 156, 158, 187, 189, 438, 445  
 Foster reactance theorem, 161, 217, 439  
 fractional bandwidth (FBW), 44, 95, 107, 188, 251, 253, 257, 259, 261–3, 267, 270, 271, 273, 275–7, 367, 416, 417, 419–21, 424, 426  
 free-space wavenumber, 52, 53, 103

- frequency
  - multipliers, 340, 342, 385–7, 391
  - scanning, 283–5
  - triplers, 386
- frequency-modulated continuous-wave
  - ground penetrating radar (FMCW-GPR), 267
- fringing
  - capacitance, 179
  - fields, 21, 465
- fundamental harmonic, 49, 50
- fundamental mode, 4, 29, 66, 67, 131, 283–5, 305
- fundamental space harmonic, 48, 52, 53, 77
- gain, 50, 57, 105, 134, 191, 289–93, 295, 299, 300, 306, 313, 386, 440, 452
- gain-bandwidth product, 290, 293
- gate line, 290, 291, 293, 295, 296
- generalized bandpass filter network, 259, 271, 272
- generalized CRLH transmission line, 161, 429
- generalized D-CRLH line, 161
- generalized lattice network, 429, 430
- generalized order-4 transfer matrix, 186
- generalized reflection coefficient, 11, 79
- ground plane, 29, 31, 37, 38, 48, 64, 66–8, 71, 82, 86, 87, 91–4, 97, 98, 102, 107, 163, 177, 185, 197, 204, 224, 251, 253, 256, 269, 272, 274, 279, 307, 316, 317, 319, 320, 326, 352, 353, 356, 357, 360, 361, 376, 378, 382, 383, 412, 423, 424, 428, 495
- ground terminal, 30
- group velocity, 7, 49–51, 125, 127, 141, 151–3, 156–8, 385, 402, 404, 406, 440, 441
- group-delay, 99–102, 263
- half-mode SIW, 445
- harmonic generation, 385, 386, 393
- harmonic multiplication, 386
- harmonic rejection, 267
- harmonic suppression, 33, 86, 95–9
- HBV *see* heterostructure barrier varactors (HBV)
- Heaviside condition, 18
- Helmholtz equation, 461, 464
- heterostructure barrier varactors (HBV), 340–342, 385–7, 391
- high order CRLH transmission lines, 159–62, 447
- high pass filters, 42
- high-resistivity silicon, 20
- host line, 33, 37, 120–122, 154, 155, 162, 163, 165–7, 176, 196, 198, 206, 221, 228, 238, 244, 246, 315, 317, 322, 355, 364, 375, 380, 382, 423, 435, 441, 450
- hybrid
  - approach, 204–6, 258–70, 277
  - cell, 263, 266–8, 270
  - lines, 166, 204, 205
- IL *see* insertion loss (IL)
- image impedance, 63
- impedance
  - engineering, 121, 149, 214, 215, 227, 250, 291, 303
  - inverter, 12, 63, 218, 230, 231, 233–7, 239, 240, 244, 246–8, 259, 270–274, 362, 380, 425, 428, 434, 451, 453, 472
  - matrix, 430, 476
  - ratio, 35
- impulse compression, 385
- inductive loading, 108
- inductive transformer, 268, 270
- insertion loss (IL), 14, 24, 83, 85, 89, 99, 167, 178, 198, 240, 249, 253, 256, 263–5, 268, 270, 273, 281, 282, 299, 300, 350, 355, 367, 370, 371, 375, 379, 410, 413, 414, 418, 419, 421, 428, 476
- inter-resonator coupling, 183–90, 367, 414, 416
- inverse Doppler effect, 127
- inverse scattering method, 387
- inversion symmetry, 142, 191
- inverted microstrip line, 29
- invisibility cloaks, 120
- iterative impedance, 63–4, 430
- jitter, 420, 421
- Kirchoff's current law, 2
- Kirchoff's voltage law, 2
- Kuroda identity, 39, 40

- ladder network, 4, 33, 60, 122, 150, 440  
 Laplace equation, 465  
 Laplacian operator, 465  
 lattice network, 162, 402, 429–39, 503  
 leakage factor, 283  
 leaky wave(s), 17, 29, 48, 50–53, 127,  
 129–31, 163–5, 215, 282–90, 378,  
 381–5, 447, 453  
   propagation, 29  
   radiation, 50–52, 127, 129–31, 282–5, 287,  
   289, 453  
 leaky wave antennas (LWA), 17, 48, 164,  
 165, 215, 282–90, 378, 381–5, 447,  
 452, 453  
 left-handed (LH) media, 121, 123, 124  
 level sensors, 302  
 LH transmission line, 151, 219, 263,  
 290, 395  
 l'Hôpital's rule, 78  
 liquid crystal, 346–7, 377, 378, 381–5  
 long wavelength  
   approximation, 152, 219  
   condition, 121  
   limit, 132, 151, 152, 156, 295, 379,  
   380, 387  
   regime, 62  
 Lorentz model, 134, 135, 138, 439  
 loss factor, 28  
 loss tangent, 19–25, 185, 289, 319, 323, 359,  
 419, 422, 453  
 lossy medium, 462  
 lossy transmission line, 16–28  
 low pass filter prototype, 33, 39  
 low pass filters, 13, 33, 34, 37–41, 60,  
 103, 386  
 low temperature co-fired ceramic (LTCC),  
 164, 165, 411  
 low-loss approximation, 18  
 low-loss transmission lines, 17, 18, 21  
 LTCC *see* low temperature co-fired  
 ceramic (LTCC)  
 lumped components, 4, 231, 358  
 lumped element approach, 2  
 lumped elements, 2, 4, 5, 12, 17, 29, 30, 35,  
 39, 102–6, 132, 162–200, 224, 229, 231,  
 234, 250, 255, 280, 282, 296, 348, 353,  
 354, 358, 386, 387, 415, 423, 465, 472,  
 473, 491  
 LWA *see* leaky wave antennas (LWA)  
 magnetic coupling, 141, 191–3, 195,  
 349, 415  
 magnetic current, 280, 285, 287  
 magnetic LC (MLC) resonator, 148  
 magnetic permeability, 8, 122, 123, 138  
 magnetic polarizability, 136–8, 142, 147  
 magnetic susceptibility, 136, 138  
 magnetic wall, 21, 29, 146, 171, 172, 175,  
 195, 255, 285, 315, 316, 320, 326, 348,  
 411, 412, 425, 445, 488  
 magnetoelectric coupling, 139  
 magnetoinductive waves (MIW),  
 187, 402–11  
   delay lines, 404, 406, 407, 409, 411  
   MIW lines, 403, 406, 409  
 mass flow sensor, 302, 303  
 matched load, 9, 10, 13, 40, 51, 60, 63, 69,  
 283, 298, 409, 472, 474, 476  
 matching condition, 41, 73, 77, 79–81, 100  
 matching networks, 95, 98, 289, 290,  
 310, 311  
 Maxwell's equations, 2, 8, 27  
 MCM-D technology, 263  
 meander line antenna (MLA), 311, 312, 314  
 MEMS bridges, 371  
 metacircuits, 121  
 meta-distributed amplifier, 296  
 meta-distributed mixer, 291  
 metalines, 121, 149, 162, 167, 204, 221  
 metal-semiconductor junction, 340, 341  
 metamaterial, 4, 20, 51, 119–206, 214–327,  
 342, 344, 347–85, 439–53, 467,  
 491–502  
   resonators, 121, 311, 317, 342, 344, 371  
   transmission lines, 4, 51, 119–206,  
   214–327, 342, 344, 347–85, 439–53,  
   467, 491–502  
 micromaching technologies, 29  
 microstrip, 3, 4, 8, 22, 23, 28–31, 34, 36, 37,  
 39, 44, 48, 66–8, 80–82, 84–93, 95, 99,  
 101, 102, 107–14, 154, 162, 163,  
 177–86, 191, 193, 195, 196, 199–201,  
 206, 225, 234, 239, 240, 244, 246,  
 249–59, 262, 263, 271, 273, 282, 283,  
 285, 289, 316, 317, 324, 327, 348–55,  
 364, 365, 367, 373–6, 409, 411–13, 415,  
 416, 423, 424, 426, 438, 444–6, 453,  
 467, 491–5  
 microstrip differential lines, 411, 412

- millimeter wave, 29, 119, 435  
 mirrored SIR, 423, 425–9  
 mismatching, 5  
 MIW *see* magnetoinductive waves (MIW)  
 mixed coupling, 191–5, 415  
 mixers, 95, 215, 267, 290, 291, 298, 340  
 MLA *see* meander line antenna (MLA)  
 MNG *see* negative permeability materials (MNG)  
 mode conversion, 412, 413  
 mode interference, 49  
 monolithic microwave integrated circuits (MMIC), 29  
 monolithic NLTL, 386  
 mu negative-MNG-media, 123  
 multiband  
   components, 162, 215, 225–50  
   devices, 214, 225, 250  
   planar antennas, 303–14  
   printed dipole antennas, 214, 304–10  
   printed monopole antennas, 214, 304–10  
 multi-conductor line theory, 185  
 multifunctional filters, 250, 267  
 multimode propagation, 183  
 multiple tuned CSRR-loaded microstrip line, 251  
 multiple tuned SRR-loaded CPW stop band filter, 251  
 multiple tuning, 253  
 multiple-frequency-tuned EBG transmission lines, 88  
 multiport networks, 40, 185  
 multispurious suppression, 95  
 mu-near-zero (MNZ), 439  
 mushroom type configuration, 163  
 mutual inductance, 171, 176, 192, 193, 349, 403, 404, 407  
  
 NB-CSRR *see* non-bianisotropic complementary SRR (NB-CSRR)  
 NB-SRR *see* non-bianisotropic SRR (NB-SRR)  
 negative Goos–Hänchen shift, 127  
 negative group velocity, 153, 441  
 negative impedance converter (NIC), 440–442  
 negative permeability, 122, 123, 136, 141, 167, 177, 411, 439  
 negative permeability materials (MNG), 123, 136, 139, 141, 143, 144  
 negative permittivity, 123, 141, 445  
 negative refraction, 127–9  
 negative refractive index (NRI) media, 123  
 negative refractive media, 129  
 nematic liquid crystals, 346, 347  
 nematic state, 346  
 Nepers, 28  
 NIC *see* negative impedance converter (NIC)  
 NLTL *see* nonlinear transmission lines (NLTL)  
 non-bianisotropic complementary SRR (NB-CSRR), 148, 191, 194  
 non-bianisotropic SRR (NB-SRR), 142, 191, 194  
 non-Foster active components, 230  
 non-Foster elements, 439–41  
 non-Foster reactance, 429  
 non-Foster transmission lines, 402  
 non-homogeneous open lines, 4, 22, 28  
 nonlinear Schrödinger equation, 394, 395  
 nonlinear transmission lines (NLTL), 339, 385–95  
 nonlinearity, 339, 344, 385, 387, 391, 393, 394  
 non-spectral, 53  
 non-uniform transmission lines, 65  
 normalized admittance, 259, 471, 472  
 normalized attenuation constant, 287  
 normalized impedance, 273, 468–73, 476  
 normalized voltage, 474, 475  
 notch filters, 31–9, 316  
  
 OCSRR *see* open complementary SRR (OCSRR)  
 odd mode, 114, 251, 411, 415, 417, 421, 437  
 Ohm law, 20, 90  
 ohmic losses, 138  
 open complementary SRR (OCSRR), 148, 149, 166, 167, 195–204, 234, 235, 239, 240, 246, 248, 249, 270–282, 305–9, 349, 362, 375–9, 423–6, 490  
 open split ring resonator (OSRR), 146, 356  
 open stop band, 284  
 open stub, 35, 37  
 open transmission lines, 65, 66  
 open-circuit, 4, 10, 12, 39, 305, 424



- optimization space, 492, 493  
 OSRR *see* open split ring resonator (OSRR)
- paired strips transmission line, 31  
 paraelectric, 344, 345  
 paraelectric phase, 344  
 parallel coupled line bandpass filters, 251, 252, 256  
 parallel plate transmission line, 21, 27, 462, 465–7  
 parallel strips, 30, 167  
 parameter extraction, 163, 196–8, 200, 205, 262, 356, 425, 486–91, 493, 500  
 pass band ripple constant, 109  
 patch antenna, 95, 97  
 patch-loaded lines, 108, 110  
 PBG *see* photonic bandgaps (PBG)  
 PCB *see* printed circuit board (PCB)  
 PCs *see* photonic crystals (PCs)  
 PEC *see* perfect electric conductor (PEC)  
 penetration depth, 26  
 perfect electric conductor (PEC), 133, 147, 285  
 perfect magnetic conductor (PMC), 133, 147, 285  
 periodic bidirectional LWA, 283  
 periodic LWA, 283, 285  
 periodic structures, 47–114, 119–21, 125, 129–32, 188, 251, 262, 263, 282–4, 287, 289, 385, 403  
 periodic transmission lines, 47, 48, 51, 57, 62–3, 79, 86, 102, 114, 120  
 periodicity, 49, 51, 71, 108, 121, 159, 259, 262, 274, 283, 284, 289, 385, 386, 439, 440  
 permeability, 8, 20, 65, 120, 122, 123, 125, 126, 131, 136–41, 147, 153, 159, 167, 168, 175–7, 182, 349, 411, 439, 440, 460, 467, 480  
 permittivity, 2, 8, 19, 20, 22, 30, 65, 120, 122, 123, 125, 126, 131–6, 141, 145, 147, 153, 159, 167, 175–7, 182, 339, 344–6, 354, 375, 376, 383, 439–41, 444, 445, 448, 449, 453, 460, 462, 467  
 permittivity of vacuum, 22, 441  
 perovskite crystalline structure, 345  
 phase  
   constant, 6, 8, 17, 18, 25, 49, 50, 53, 66–8, 71, 76, 77, 93, 103, 105, 120, 121, 132, 150–153, 156, 157, 205, 215, 283, 287, 291, 293, 295, 296, 311, 379, 381, 382, 430, 432, 435, 461, 462, 482, 484, 495, 503  
   matching, 61, 73, 77, 79–81, 100  
   noise, 95  
   shifting lines, 197, 221  
   velocity, 7, 8, 22, 28, 30, 36, 47, 49, 51, 102, 105–7, 129, 157, 216, 229, 251, 437, 441, 462  
 phase-matching condition, 73, 77, 79–81, 100  
 photonic bandgaps (PBG), 47, 86  
 photonic crystals (PCs), 47, 120, 129  
 physical dual structures, 183  
 PIN diodes, 340–342  
 planar filters, 93–5, 102, 251, 444  
 planar technology, 34, 136, 144, 167, 224, 246, 270, 304, 406, 442  
 planar transmission lines, 1–44, 64, 68, 71, 153, 162  
 plane wave propagation, 153, 439, 460–467  
 plane waves, 7, 25, 27, 123–5, 132, 139, 153, 439, 460–467  
 plasma frequency, 123, 133, 135, 141, 167  
 PLH *see* purely left handed (PLH)  
 PMC *see* perfect magnetic conductor (PMC)  
 PN junction, 340, 341  
 PN rectifier diodes, 340  
 polarization, 19, 129, 131, 133, 134, 137, 140, 147, 148, 191, 307, 318, 344, 346, 348–51, 355, 356, 364, 380  
 power divider, 42, 218–22, 231–42, 246, 248–50, 267, 298, 299, 302, 362, 376, 451  
 power splitter, 40–43, 225, 234, 236, 249, 267, 428, 453  
 power transmission coefficient, 11, 313  
 power wave reflection coefficient, 11, 312  
 Poynting vector, 124, 128, 131  
 PRH *see* purely right handed (PRH)  
 printed circuit board (PCB), 2, 26, 402, 406, 442  
 printed monopole antennas, 307–10  
 propagation constant, 6, 17, 18, 25, 48, 49, 55, 62, 123, 183, 186, 187, 461–4, 467, 481  
 pull-down electrode, 343  
 pull-down voltage, 342–4  
 pulse  
   compression, 385  
   sharpening, 386  
   width, 406, 409

- purely left handed (PLH), 156, 220, 221, 228–31, 293, 295, 380, 432–4
- purely right handed (PRH), 155, 433, 434
- purely TEM wave, 20, 21, 28
- quad-band
  - branch line hybrid coupler, 249
  - devices, 162, 246–50
  - impedance inverter, 246, 248, 251
  - power divider, 248, 249
  - splitter, 447
  - Wilkinson power divider, 250
  - Y-junction power divider, 246, 249, 251
- quadrature hybrid coupler, 242
- quality factor, 22, 24, 25, 93, 95, 251, 316, 367, 374
- quasimicrostrip mode, 67
- quasi-Newton iteration, 493
- quasiperiodic EBG structures, 99, 100
- quasi-slot mode, 67
- quasi-TEM lines, 20, 467
- quasi-uniform LWA, 284
- radiation loss, 17, 24, 66, 443
- radiation pattern, 285, 286, 289, 306, 308, 310, 384, 452, 453
- radiofrequency (RF) bar codes, 303, 314–16, 324–7, 406, 411
- radiofrequency identification (RFID), 122, 304, 311, 313, 314, 316, 406–11
- radiofrequency-microelectromechanical system (RF-MEMS), 342–7, 352, 362–75, 377, 378, 381
- rat-race hybrid coupler, 221–5
- reactively loaded lines, 86, 102–14
- read range, 310, 312–14
- reciprocal network, 40, 478
- reciprocal system, 55
- reciprocity, 55, 64, 172, 191
- reconfigurable metamaterial transmission lines, 347–85
- reconfigurable stop band filter, 352, 368
- rectangular waveguide, 141, 441–5
- recursive active filters, 290, 298–303
- reference impedance, 69, 81, 84, 260, 312, 468, 472, 473, 489
- reference plane, 54, 57–9, 62, 69, 474, 475
- reflection coefficient, 9–11, 13, 15, 62, 79, 80, 88, 93, 114, 190, 191, 196, 197, 199, 242, 307–9, 312, 409, 468, 470–473, 476–8, 486, 488
- reflection zero, 61, 78, 110, 489, 490
- reflectors, 47, 68, 86, 92, 93, 406, 409
- refraction regime, 120
- resonant Bragg coupling, 100
- resonant cavity, 25, 92, 93
- resonant coupling, 73
- resonant-type approach, 131, 162, 165–204, 223
- resonant-type CRLH transmission line, 163, 195
- resonant-type metamaterial transmission line, 121, 122, 166, 167, 204, 347–8, 491–502
- return loss (RL), 10, 37, 39, 83, 85, 89, 112, 169, 228, 242, 257, 263, 265, 268, 270, 271, 275, 277, 282, 300, 313, 367, 369–71, 418, 419, 425, 428, 444, 447
- reverse gain, 291, 295–7
- reverse output port, 290, 291
- RF choke, 380
- RFID *see* radiofrequency identification (RFID)
- RF-MEMS *see* radiofrequency-microelectromechanical system (RF-MEMS)
- RF-MEMS switches, 344, 362, 364, 366, 367
- RF-MEMS-loaded SRR, 364, 365, 367
- Richard's transformations, 13, 39–41
- right-handed (RH) wave propagation, 122, 151, 154, 205
- ring resonator, 22, 23, 32
- ripple, 39, 44, 87, 91, 101, 109, 263, 273, 275, 277, 279, 421, 424, 426
- RL *see* return loss (RL)
- rotation sensors, 317, 320, 322, 324
- scattering matrix, 40, 242, 474–9
- scattering (S-)parameters, 48, 65, 69, 70, 75–7, 79–80, 113, 248, 279, 367, 371, 379, 434, 436, 479, 492, 500, 501
- Schiffman section, 437
- Schottky diodes, 340–342
- semiconductor diodes, 340
- semilumped components, 31, 32, 39, 102
- semilumped element approximation, 32, 33
- sensors, 122, 146, 195, 215, 300–304, 314–24
- series power divider, 219–22
- short-circuit stub, 109

- shrinking factor, 499
- shunt stub, 33, 39, 108, 163, 205, 223, 224
- signal integrity, 412, 420
- simplified coupled mode equations, 65, 482–3
- single mode operation, 66, 67, 79
- single negative (SNG) artificial structures, 123
- single tuned EBG, 97
- single-band components, 226
- single-ended bandpass filters, 423
- single-ended lines, 416
- single-ended microstrip transmission line, 31
- single-ended ports, 30
- sinusoidal steady-state conditions, 6
- SIR *see* stepped impedance resonator (SIR)
- SISS *see* stepped impedance shunt stub (SISS)
- SIW *see* substrate integrated waveguides (SIW)
- skin
  - depth, 25–8
  - effect, 26
- slot antennas, 30, 447
- slot lines, 30, 93, 287, 289
- slot mode, 29, 30, 197, 280, 319, 323, 326, 360, 361, 378
- slow wave
  - effect, 102–14, 120
  - factor, 402–6
  - periodic structures, 108
  - structures, 47, 107, 108
  - transmission lines, 4, 107, 108, 441
- SM *see* space mapping (SM)
- Smith chart, 5, 194, 196, 197, 199, 201, 468–73, 486, 488–90
- SMT *see* surface mount technology (SMT)
- Snell's law, 128
- solitary wave, 385, 389, 390
- soliton, 339, 385–95
- source impedance, 14, 16, 60
- source plane, 15, 16, 59, 63
- space harmonics, 48–53, 77, 130, 131, 283, 284
- space mapping (SM), 204, 491–502
- spatially integrating sensors, 302
- spatially resolved sensors, 302
- spectral, 53, 129, 155, 158, 310, 316
- spectral signature, 316
- spiral resonator (SR), 144, 146, 148, 240, 244, 311, 312, 314
- split cylinder resonator, 25
- split ring resonator (SRR), 32, 123, 131, 136–44, 146–9, 156, 167–9, 171, 174–7, 182, 191–6, 250–251, 255–7, 270, 273, 287, 288, 300, 301, 305, 315–17, 321, 322, 326, 347, 348, 352, 356, 358, 362–5, 372–5, 404, 406, 408, 486
- spurious suppression, 86, 93–5, 105, 108, 250–255
- square resistance, 27
- square split ring resonators (SSRR), 406, 408
- SR *see* spiral resonator (SR)
- SRR *see* split ring resonator (SRR)
- SRR-loaded CPW, 168, 169, 171, 172, 179, 183, 191, 192, 195, 250, 251, 317
- SRR-loaded lines, 193, 301, 317, 349, 488–9
- SRR/strip-loaded CPW, 168, 169, 171, 172, 195, 270, 287
- SSRR *see* square split ring resonators (SSRR)
- standing wave, 10, 48
- stepped impedance low pass filter, 33, 34
- stepped impedance resonator (SIR), 32, 36, 37, 141, 144–5, 148, 224, 324–7, 421
- stepped impedance shunt stub (SISS), 33–7, 39
- stop band filters, 30, 36, 280
- stripline, 21, 28, 30, 467
- strontium titanate (SrTiO<sub>3</sub>), 345
- stub, 3, 4, 7, 31–9, 41, 108–10, 163, 204–6, 214, 215, 223, 224, 228, 250, 262, 268, 285, 468
- substrate integrated waveguides (SIW), 289, 402, 441–53
- subwavelength resolution, 127
- superluminal, 130, 153, 440, 441
  - group velocity, 441
  - phase velocity, 440, 441
- superposition hypothesis, 139
- surface mount technology (SMT), 162, 228, 231, 340
- surface resistance, 26
- susceptance slope, 161, 280, 424
- susceptibility tensor, 138
- suspended microstrip lines, 29
- symmetry properties, 31, 146, 195, 314–17
- synthetic lines, 4

- TDR *see* time domain reflectometry (TDR)
- TE *see* transverse electric (TE)
- telegrapher equations, 6, 153
- TEM *see* transverse electric and magnetic (TEM)
- temperature sensors, 302
- terminated transmission line, 8–16, 468, 470
- THz gap, 386
- time domain reflectometry (TDR), 316, 406–11
- time-averaged density of energy, 126, 466
- time-averaged flux of energy, 124
- time-bandwidth product, 99
- TM *see* transverse magnetic (TM)
- transfer matrix, 48, 53–65, 102, 150, 186
- transfer matrix method, 48, 53–65, 102
- transformation optics, 129
- transition frequency, 156, 157, 163, 164, 182, 183, 200, 220, 229, 284, 287, 289, 295, 432–5
- transmission coefficient, 11, 14, 22–5, 60–62, 102, 157, 191, 244, 257, 260, 299, 300, 304, 313, 315, 321, 322, 324, 326, 327, 355, 373, 374, 444, 447, 476, 478, 487, 488
- transmission gain, 313
- transmission line(s), 1–44, 47–114, 119–206, 214–327, 339–95, 402–53, 460–468, 470, 472, 482–3, 491–502
- calculator, 33, 68, 82, 416, 428, 495
- metamaterial, 121, 127
- with metamaterial loading, 121, 122, 214, 215, 250, 277, 303–27
- parameters, 5–8
- transmission power, 313
- transmission zero, 33, 36, 37, 39, 169, 172, 173, 175, 178, 179, 181, 182, 198, 204, 205, 237, 240, 255, 256, 259–63, 268, 270, 280, 290, 316, 326, 354, 364, 367, 382, 416, 419, 421, 423–5, 428, 487, 488
- transverse electric (TE), 4, 54, 141, 443, 444, 463
- transverse electric and magnetic (TEM), 4, 8, 20, 21, 28, 30, 54, 67, 68, 132, 133, 135, 153, 306, 313, 460–467
- TEM cell, 306, 313
- transmission line, 132, 133, 153, 464, 467
- wave propagation, 4, 8, 20, 21, 28, 153, 460–467
- transverse magnetic (TM), 141, 285, 443
- trap antennas, 214, 304
- travelling waves, 9, 10, 42, 51, 54, 63, 70, 462, 483
- tri-band components, 205, 250
- tri-band dipole, 305
- tri-band printed monopole antennas, 307, 309, 310
- tunable filters, 303, 340, 358, 359, 362, 367, 371, 372, 376, 377
- tunable LWA, 289, 381, 383, 385
- tunable metamaterial resonators, 342, 344, 371
- tunable metamaterial transmission lines, 342, 371
- tunable phase shifter, 378–81
- tuning diodes, 340, 347, 349, 355
- tuning range, 340, 347, 362, 369–71, 373, 375, 381
- tunneling, 341, 342
- two-port networks, 1, 5, 39, 57, 63, 64, 430, 473, 476, 477, 479
- UHF-RFID *see* ultra-high-frequency radiofrequency identification (UHF-RFID)
- UHF-RFID tags, 310–314
- ultra wideband (UWB), 112, 270, 428
- ultra-high-frequency radiofrequency identification (UHF-RFID), 310–314
- uniform LWA, 283, 284
- uniform transmission line, 65, 67, 68
- unit conductance circumference, 198, 200, 487–9
- unit resistance circumference, 471, 473
- unitarity, 76, 191
- unloaded quality factor, 24
- UWB *see* ultra wideband (UWB)
- UWB bandpass filters, 270, 428
- validation space, 492, 493
- varactor diodes, 340–342, 347, 348, 352, 353, 356–9, 362, 375, 379–81, 385
- varactor-loaded complementary split ring resonator (VLCSRR), 352–7, 362

- varactor-loaded open complementary split ring resonator (VLOCSRR), 356–9
- varactor-loaded open split ring resonator (VLOSRR), 356–9
- varactor-loaded split ring resonator (VLSRR), 347–53, 356
- varicap diodes, 340
- Veselago media, 123
- vias, 29, 163, 197, 205, 258, 279, 280, 319, 323, 326, 327, 352–6, 360, 361, 423, 441, 443, 444, 450, 453
- virtual ground, 29, 31, 380, 423
- VLCSSRR *see* varactor-loaded complementary split ring resonator (VLCSSRR)
- VLOCSRR *see* varactor-loaded open complementary split ring resonator (VLOCSRR)
- VLOSRR *see* varactor-loaded open split ring resonator (VLOSRR)
- VLSRR *see* varactor-loaded split ring resonator (VLSRR)
- voltage controlled capacitors, 340
- voltage controlled oscillators (VCO), 340
- voltage divider, 16
- voltage multipliers, 340
- voltage standing wave ratio (SWR), 10
- wave equation, 6, 124, 461, 462, 464
- wave impedance, 7, 8, 123, 313, 461–4
- waveguides, 1, 8, 29, 47, 48, 65, 66, 68, 123, 125, 141, 183, 277, 373, 402, 441–53
- wavelength, 2, 7, 22, 26, 30, 51, 60, 62, 64, 93, 105, 106, 108, 120, 121, 127, 132, 136, 144, 151, 152, 156, 158, 219, 221, 236, 237, 240, 242, 244, 246, 248, 256, 257, 263, 273, 275, 277, 282, 284, 295, 302, 305, 312, 369, 376, 379, 380, 387, 425, 428, 470
- wavenumber, 52, 53, 103, 132, 283, 461
- wideband band pass filters, 108–14, 167, 271, 273, 274
- wideband filters, 250, 267, 270–277
- wiggly-line filter, 93, 95, 96
- wire media, 132–6
- 0° phase shifting line, 221
- zero-resistance circumference, 472